

PRACTICAL WIRELESS

FEBRUARY
1975
25p

PW
'ASCOT'

STEREO CASSETTE DECK

FOR
Hi-fi Systems

PART 1



ALSO:-

**HOME TELEPHONE EXCHANGE
RADIO CONTROL SERIES PART 2-TRANSMITTER**

NEW EDU-KIT MAJOR

Completely Solderless Electronic Construction Kit
Build these projects without soldering iron or solder


- ★ 4 Transistor Earpiece Radio.
- ★ 6 Transistor Push Pull Amplifier.
- ★ Batteriless Crystal Radio.
- ★ Signal Tracer.
- ★ 7 Transistor Loudspeaker Radio MW/LW.
- ★ One Transistor Radio.
- ★ Signal Injector.
- ★ 6 Transistor Short Wave Radio.
- ★ 2 Transistor Regenerative Radio.
- ★ Transistor Tester NPN-PNP.
- ★ Electronic Metronome.
- ★ 3 Transistor Regenerative Radio.
- ★ 4 Transistor Push Pull Amplifier.
- ★ Electronic Noise Generator
- ★ Audible Continuity Tester.
- ★ Sensible Pre-Amplifier.

Total Building Costs
£7-23 P & Ins. 44p
(Overseas P & £1-85)
(+ 8% VAT 67p)

Components Include: 24 Resistors • 21 Capacitors • 10 Transistors • 31" Loudspeaker • Earpiece • Mica Baseboard • 3 12-way connectors • 2 Volume controls • 2 Slider Switches • 1 Tuning Condenser • 3 Knobs • Ready Wound MW/LW/SW Coils • Ferrite Rod • 6 1/2 yards of wire • 1 Yard of sleeving etc. • Parts Price List and Plans 50p. (Free with parts).

NEW ROAMER NINE

WITH V.H.F. INCLUDING AIRCRAFT

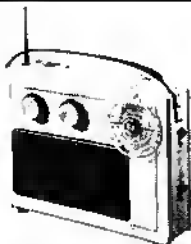


Nine Transistors, 9 Tunable wavebands as Roamer Ten. Built in ferrite rod aerial for MW/LW. Retractable chrome-plated telescopic aerial for VHF and SW. Push Pull output using 600mW transistors. 9 Transistors and 3 diodes, tuning condenser with V.H.F. section, separate coil for aircraft, moving coil loudspeaker, volume ON/OFF and wavechange controls. Attractive all white case with red grille and carrying strap. Size 9 1/2" x 7" x 2 1/2" approx. Parts Price List and Plans 40p (Free with parts).

Total Building Costs **£6-95** P & Ins. 44p
(Overseas P & £1-85)
(+ 8% VAT 56p)

NEW Everyday Series

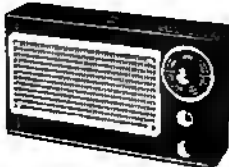Build this exciting New series of designs



E.V.S. 6 Transistors and 2 diodes. MW/LW. Powered by 4 1/2 volt Battery. Ferrite rod aerial, tuning condenser, volume control, and now with 3" loudspeaker. Attractive case with red speaker grille. Size 9" x 5 1/2" x 2 1/2" approx. Parts Price List and Plans 30p. Free with parts.

Total Building Costs **£2-95** P & Ins. 30p
(+ 8% VAT 23p)
(Overseas P & £1-25)

E.V.S. Case and looks as above. 6 Transistors and 3 diodes. Powered by 9 volt battery. Ferrite rod aerial, 3" loudspeaker, etc. MW/LW coverage. Push Pull output. Parts Price List and Plans 30p. Free with parts.


Total Building Costs **£3-60** P & Ins. 30p
(+ 8% VAT 29p)
(Overseas P & £1-25)

E.V.7. Case and looks as above. 7 Transistors and 3 diodes. Six wavebands. MW/LW, Trawler Band, SW1, SW2, SW3. Powered by 9 volt battery. Push Pull output. Telescopic aerial for short waves. 3" Loudspeaker. Parts Price List and Easy Build Plans 30p. Free with parts. Overseas P & £1-05.

Total Building Costs **£4-08** P & Ins. 31p
(Overseas P & £1-85)
(+ 8% VAT 32p)

ROAMER TEN

WITH VHF INCLUDING AIRCRAFT

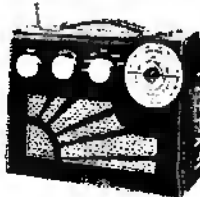

10 Transistors. Latest 4" 2 watt Ferrite Magnet Loudspeakers. 9 Tunable Wavebands, MW1, MW2, LW, SW1, SW2, SW3, Trawler Band, VHF and Local Stations also Aircraft Band.

On some cases the grill pattern will be horizontal bars and not as illustrated

Built in Ferrite Rod Aerial for MW/LW. Chrome plated 7 section Telescopic Aerial, can be angled and rotated for peak short wave and VHF listening. Push Pull output using 600mW Transistors. Car Aerial and Tape Record Sockets. 10 Transistors plus 3 Diodes. Ganged Tuning Condenser with VHF section. Separate coil for Aircraft Band. Volume on/off. Wave Change and tone Controls. Attractive Case in black with silver blocking. Size 9" x 7" x 4". Easy to follow instructions and diagrams. Parts price list and plans 50p (FREE with parts).

Total building costs **£8-50** P & Ins. 52p
(Overseas P & £1-86)
(+ 8% VAT 66p)

POCKET FIVE

NOW WITH 3" LOUD-SPEAKER



3 Tunable wavebands, M.W. L.W. and Trawler Band, 7 stages, 5 transistors and 2 diodes, supersensitive ferrite rod aerial, attractive black and gold case. Size 5 1/2" x 1 1/2" x 2 1/2" approx. Plans and Parts Price List 20p (Free with parts).

Total Building Costs **£2-50** P & Ins. 26p
(+ 8% VAT 20p)
(Overseas P & £1-25)



TRANSONA FIVE NOW WITH 3" LOUDSPEAKER

Wavebands, transistors and speaker as Pocket Five. Larger Case with Red Speaker Grille and Tuning Dial. Plans and Parts Price List 20p (Free with parts).

Total Building Costs **£2-75** P & Ins. 26p
(+ 8% VAT 21p)

(Overseas P & £1-25)

ROAMER EIGHT Mk I

NOW WITH VARIABLE TONE CONTROL



7 Tunable Wavebands: MW1, MW2, LW, SW1, SW2, SW3 and Trawler Band. Built in Ferrite Rod Aerial for MW and LW. Chrome plated Telescopic aerial can be angled and rotated for peak short wave listening. Push pull output using 600mW transistors. Car aerial and Tape record sockets. Selectivity switch. 8 transistors plus 3 diodes. Latest 3" 2 watt ferrite magnet loudspeaker. Air spaced ganged tuning condenser. Volume on/off, tuning, wave change and tone controls. Attractive case in rich chestnut shade with gold blocking. Size 9 x 7 x 4 1/2 in. approx. Easy to follow instructions and diagrams. Parts price list and plans 60p (FREE with parts).


Total building costs **£6-98** P & Ins. 47p
(Overseas P & £1-85)
(+ 8% VAT 56p)

TRANS EIGHT

8 TRANSISTORS and 3 DIODES

8 Tunable Wavebands: MW, LW, SW1, SW2, SW3 and Trawler Band. Sensitive ferrite rod aerial for M.W. and L.W. Telescopic aerial for Short Waves. 8in. Speaker. 8 Improved type transistors plus 3 diodes. Attractive case in black with red grille, dial and black knobs with polished metal inserts. Size 9 x 6 1/2 x 2 1/2 in. approx. Push pull output. Battery economiser switch for extended battery life. Ample power to drive a larger speaker. Parts price list and plans 35p (FREE with parts).

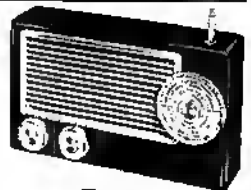Total building costs **£4-48** P & Ins. 33p
(+ 8% VAT 36p)
(Overseas P & £1-25)



ROAMER SIX

CASE AND LOOKS AS TRANS-EIGHT

Trawler band plus an extra Medium waveband for easier tuning of Luxembourg, etc. Sensitive ferrite rod aerial and telescopic aerial for Short Waves. 8in. Speaker. 8 stages—6 transistors and 2 diodes. Attractive black case with red grille, dial and black knobs with polished metal inserts. Size 9 x 6 1/2 x 2 1/2 in. approx. Plans and parts price list 35p (FREE with parts).

Total building costs **£3-98** P & Ins. 31p
(Overseas P & £1-85)
(+ 8% VAT 32p)

"EDU-KIT"



Build Radios, Amplifiers, etc. from easy stage diagrams.

Five units including master unit to construct.

Components include:

Tuning Condenser; 2 Volume Controls; 2 Slider Switches; Fine Tone 3" Moving Coil Speaker; Terminal Strip; Ferrite Rod Aerial; Battery Clips; 4 Tag Boards; 10 Transistors; 4 Diodes; Resistors; Capacitors; Three 4" Knobs. Units once constructed are detachable from Master Unit, enabling them to be stored for future use. Ideal for Schools, Educational Authorities and all those interested in radio construction. Parts price list and plans 40p (FREE with parts).

Total building costs **£5-50** P & Ins. 33p
(Overseas P & £1-86)
(+ 8% VAT 44p)

RADIO EXCHANGE LTD

★ Callers side entrance "Lavelle's" shop.
★ Open 10-1, 2.30-4.30, Mon.-Fri. 9-12 Sat.

To RADIO EXCHANGE CO., 61a HIGH STREET, BEDFORD, MK40 1SA
 Tel.: 0234 52367. Reg. No. 788972.
 I enclose £..... for
 Name
 Address
 (Dept. PW2.)

PRACTICAL WIRELESS

VOL. 50 NO. 10

ISSUE 816

FEBRUARY 1975

BRITAIN'S PREMIER MAGAZINE FOR THE DO-IT-YOURSELF RADIO AND ELECTRONICS CONSTRUCTOR

EDITOR

Lionel E. Howes, G3AYA

ASSISTANT EDITOR

Eric Dowdeswell, G4AR

ART EDITOR

Peter Metalli

PRODUCTION & NEWS

EDITOR Colin R. Riches

TECHNICAL SUB-EDITOR

Bill Tull

TECHNICAL ARTIST

Alan Martin

SECRETARIAL

Jenny Maunder
Susan King

ADVERTS. MANAGER

01-634 4293 Roy Smith

CLASSIFIED ADVERTS.

01-634 4301 Colin R. Brown

Published by IPC Magazines Ltd.,
Fleetway House, Farringdon Street,
London EC4A 4AD. Tel. 01-634 4444

SUBSCRIPTIONS

Publisher's Subscription Rate for one year to the UK is £3.25 and to the rest of the world £4.35 including postage. Enquiries to Subscription Department, IPC Magazines Ltd., Carlton House, 68 Gt. Queen Street, London, WC2 5DD. Phone 01-242 4477. International Giro facilities Account No. 5122007. Please state reason for payment "message to payee". Binders (£1.34) and indexes 30p (inc. VAT) can be supplied by the Binders Dept at the same address.

BACK NUMBERS

We regret that we are unable to supply back numbers of Practical Wireless. Readers are recommended to enquire at a public library to see copies. Requests for specific back numbers of Practical Wireless and Television only can be published in our CQ Column.

COPYRIGHT AND QUERIES

© IPC Magazines Limited 1975. Copyright in all drawings, photographs and articles published in "Practical Wireless" is fully protected and reproduction or imitation in whole or in part is expressly forbidden. All reasonable precautions are taken by "Practical Wireless" to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it and we cannot accept legal responsibility for it. Prices are those current as we go to press.

We regret that we cannot answer technical queries by telephone nor can we provide information or advice on manufacturers' products other than that given in the magazine. We will endeavour to assist readers who have queries relating to articles published but we cannot offer advice on modifications to our published designs. All correspondents expecting a reply should enclose a stamped addressed envelope.

● NEWS & COMMENT

- 890 POLLUTION—Leader article
- 891 NEWS . . . NEWS . . . NEWS . . .
- 906 TELEVISION—Coming in the February issue
- 915 NEXT MONTH IN PRACTICAL WIRELESS
- 921 ON THE AIR
- 921 Amateur Bands—Eric Dowdeswell, G4AR
- 922 Broadcast Bands—Medium Wave—Charles Molloy
- 922 —Short Wave—Derek Bell
- 929 HOTLINES on recent developments by Ginsberg
- 932 PRODUCTION LINES by Colin Riches

● CONSTRUCTIONAL

- 892 ELECTRONIC HOME TELEPHONE EXCHANGE—J. Thornton-Lawrence, T.Eng. (C.E.I.)
- 901 MODEL CONTROL BY RADIO—Part 2—The Controller—F. G. Rayer, G3OGR
- 909 ELECTRONIC SLAVE FLASH—Alan Ainslie
- 914 TAKE 20, No. 68, 9V POWER SUPPLY—David Andrews
- 916 P.W. 'ASCOT' STEREO CASSETTE DECK—Part 1—Keith Cummins & Tony Francis
- 924 P.W. 'KEMPTON' CAR STEREO CASSETTE PLAYER—Part 3—Keith Cummins & Tony Francis
- 930 SINGLE FREQUENCY AUDIO OSCILLATOR—A. Foord
- 938 LOW FREQUENCY AND MARINE RECEIVER—Part 2—Charles Heath

● OTHER FEATURES

- 913 COMPETITION
- 927 GOING BACK—Earlier days of Radio—Colin Riches
- 934 SPECIAL PRODUCT REPORT—HEATHKIT GD-39 ULTRASONIC INTRUSION ALARM
- 945 TECHNICROSS SOLUTION No. 8

HUGE DISCOUNTS

ON LEADING BRAND HI-FI ALL RSC PRICES INCLUDE VAT
LOW DEPOSIT CREDIT TERMS
 Full labour and material guarantees for 12 months

Model	List Price	RSC Price
WHARFEDALE DENTON	£45-49 Pr.	£29-95
WHARFEDALE LINTON	£56-33 Pr.	£38-95
LINEAR 202 AMPLIFIER	£39-23	£24-95
ROTEL RT222 AM/FM Tuner	£56-45	£38-95
ROTEL RT322	£73-16	£53-50
ROTEL RX150A Tuner/Amp	£77-09	£54-95
LEAK 2000 Tuner/Amp	£178-16	£149-50
Wharfedale Denton Tun/Amp	£93-28	£59-95
RANK 150a Stereo System	£137-35	£84-95

Also Shure Cartridges, Basf Tape, Koss H/Phones, etc.
 Prices of above correct at Nov 14 1974

AKAI TAPE UNITS All £1-30 carr.

Model	Rec. Price	£62-95	GXC 510D	Rec. Price	£189-90	£135-95
CS 30D	£86-90		GXR 82D	£122-65		£89-95
GXC 36D	£110-72	£72-50	4000 DS	£130-10		£94-95
GXC 38	£147-19	£105-95	4000 DB(Dolby)	£196-27		£139-95
GXC 38D	£137-38	£97-95	1722 L	£125-18		£91-95
GXC 46D	£157-59	£109-95	CR 31D	£98-10		£69-95
GXC 40T	£186-09	£135-95	CS 83D	£105-81		£75-95
GXC 75D	£199-90	£142-95				

GOLDRING GL72 T/Table & G800 £29-95 (Approx. value £46) Carr. 75p
GOLDRING GL75 T/Table & G800 £34-95 (Approx. value £65) Carr. 85p
PIONEER PL12D T/Table on plinth & cover £41-75 List £61-90
BSR TD85 8 track player. Special price £14-95
T/TABLES with MAGNETIC CARTRIDGE/PLINTH & COVER
GARRARD SP25 MK IV with G850 Special Price £22-95 (Carr. £1)
RANK BD2000 Rec. Price £67-25 £48-95(Carr. £1)

FANE HI-FI LOUSPEAKERS AT APPROXIMATELY HALF-PRICE

LAST CHANCE - UNREPEATABLE OFFER - NEW - BOXED - FULLY GUARANTEED for High-Fidelity NOT Group Disco use
 Available by Mail Order only due to small quantities of some models. SAE for leaflets. Please state impedance required where not ind.

Model	Price	Model	Price	Model	Price	Model	Price	Model	Price
5045	£2-75	807T 3Ω	£2-25	12110	£3-27	138110L1H	£2-50	138110T1H	£2-50
5046	£2-81	1001	£4-37	12110T	£3-37	138110T1H	£2-50	101150A	£4-27
5047	£1-08	1002	£4-19	12110T	£3-37	138110L1H	£2-50	101150A	£4-27
801	£3-83	1003	£3-85	12110T	£3-78	138111L1H	£3-87	101150A	£4-27
802	£3-69	1004	£3-50	12110T	£4-01	138112	£3-84	101150A	£4-27
802T	£3-82	1008	£2-92	12110L1H	£4-83	138113L1H	£4-15	101150A	£4-27
K05	£2-25	1001L1H	£5-06	138110	£2-18	138116	£4-51	101150A	£4-27
K05T	£2-50	1001L1H	£4-97	138110T	£2-31	138116L1H	£4-63	101150A	£4-27

RSC G66 MkII 6.6 WATT high quality STEREO AMPLIFIER


Controls: Bass, Treble, Vol. and Bal. 10 Transistors plus Diodes. Output rating 1.1 H.F.M. Frequency range 20-20,000 c.p.s. Bass Control - 12db. Treble Control - 13db. Selector switch for Crystal P.U. or Tape/Radio. For speaker output impedances of 3 - 15 ohms. For standard 200-250v. A.C. mains operation. Attractive Black and Silver finished metal fascia plate and matching control knobs. COMPLETE KIT OF PARTS INCLUDING FULLY WIRED PRINTED CIRCUIT



COMPREHENSIVE WIRING DIAGRAMS & INSTRUCTIONS £12-95 Carr. 40p
 OF FACTORY BUILT IN TEAK VENEERED CABINET £12-95 Carr. 40p
 as illustrated £18-95 or dep. £2-12 and 8 monthly payments £2-12 (Total £18-00)

HI-FI SPEAKER ENCLOSURES

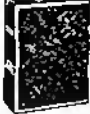Teak veneer Carr. 50p. Sizes approx. per cm.
 JE8 13 x 9 1/2 x 6 1/2 in. £3-95 } Both cut for 8in. speaker
 JE10 16 x 11 x 9 in. £5-95 }
 SE10 25 x 16 x 9 in. Cut for 10in. and Tweeter £8-95
 SE12 25 x 16 x 9 in. Cut for 12in. and Tweeter £8-95



AUDIOTRINE HI-FI SPEAKER SYSTEMS

Consisting of matched 12in. 11,000 Gauss 15 Watt 15 ohm high quality speaker, cross-over unit and tweeter. Smooth response and extended frequency range ensure surprisingly realistic reproduction. £6-95 Carr. 45p
 OR SENIOR 15 WATT INCLUDING £8-95 Carr. 50p
 HF123 13,000 GAUSS SPEAKER



AUDIOTRINE HIGH FIDELITY SPEAKERS

Heavy construction. Latest high efficiency ceramic magnets. Plasticised cone surround. "D" or "T" indicates Tweeter Cone providing extended frequency range up to 15,000 c.p.s. Impedance 3 or 8 1/2 ohms. PLEASE STATE CHOICE.
 Exceptional performance at low cost.
 HF808T 8" 10W £2-85 HF1200 12" 15W £6-50
 HF108D 10" 10W £3-50 HF128 12" 18W £7-95
 HF120 12" 15W £6-95 HF128D 12" 15W £6-50

AUDIO FIDELITY MODEL 80 HI-FI SPEAKER

A full range 8in. 10 watt unit for excellent sound quality, in suitable enclosure. Full P.V.C. cone surround and long throw voice coil to achieve very low fundamental resonance of 30 c.p.s. Tweeter cone filled to extend high note response. Frequency range 25 Hz to 16 KHz. Gauss 10,000. Impedance 8-16 Ω. £4-50 ra. £7-98
 MODEL 80 8" 15watt, with parasitic Tweeter, £6-99 ca. £10-95 pr.
 Response 25 Hz to 15 KHz, Gauss 13,000 Imp. 8-16Ω.

HI-FI 8" x 5" 7 watt LOUSPEAKERS £1-25

with parasitic Tweeter 8 ohm imp. Post and Packing 50p

R.S.C. TA6 6 Watt HI-FI AMPLIFIER

200-250v. AC mains operated. Response 30-20,000 c.p.s. S.M.I. Separate Bass and Treble "lift and cut" controls. 3 input sockets for Diode, Gram, Radio or Tape. Input selector switch. Output for 3-15 ohm speakers. Max. sensitivity 5mV. O.P.P. rating 1.1 H.F.M. Enclosed etched metal case 9 1/2 x 2 1/2 x 5 1/2 in. Silver finish fascia 10 1/2 x 4 1/2 in. Carr. FACTORY BUILT Complete kit, wiring diagrams and instructions. £7-95 Carr. 40p. £10-95

R.S.C. TA12 MKIII 6.5+6.5 WATT STEREO AMPLIFIER

Fully Transistorised. Hi-Fi copy of 6.5 watts per channel. Optimum performance with any crystal or ceramic P.U. Cartridge, Radio Tuner, Tape Rec. etc. Input Sel., Switch, Bass, Treble, Vol. & Bal. Controls. COMPLETE KIT OF PARTS WITH FULL £12-95 Carr. 40p. WIRING DIAGRAMS & INSTRUCTIONS
 Factory built with 12 inch guarantee £16-61 Or in Teak Dep. £2-30 & 8 monthly pymts 12 mins guarantee £19-55 Veneer housing £19-55 £22-50 (Total £22-50).

AUDIO FIDELITY FRI SPEAKER KIT


Response 30Hz-15KHz. Rating 15 watts in sealed cabinet, Imp. 8-15 ohms. 8" Bass Unit with P.V.C. Cone surround for ultra low resonance. Pressure Tweeter, Printed Circuit. Inductive (capacitive) Cross-over. Muffling £10-78
 Material, Screws, Terminal Panels. Carr. 75p.
 SPECIAL OFFER £14-99 Pair Carr. 75p. Carr. Free.



R.S.G. MkIII Super 30 High Fidelity Stereo Amplifier

BUILD AN AMPLIFIER WORTH APPROXIMATELY DOUBLE THE KIT PRICE INCLUDING CABINET
 Only high grade components by leading manufacturers

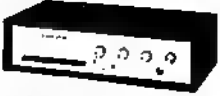- Push Button Selector Switching
 - Jack Socket for Headphones
 - Needs Indicator
 - Satin Silver Finish Metal Fascia
 - Solid State Circuitry
 - Twenty Silicon Transistors
 - Four Diodes, Four Rectifiers
- Send S.A.E. for full descriptive leaflet.



For Magnetic or Ceramic Pick-Ups regardless of Price. Output (per channel) 15 watts RMS into 8Ω. Frequency Response 7 Hz to 70 KHz ±13 dB.
 COMPLETE KIT (less cabinet). £22-50 Carr. 70p. Cabinet if req. £4-90 extra. Assembled unit in cabinet £42-60

'YORK' HIGH-FIDELITY 3 SPEAKER SYSTEM

★ Moderate size only 25 x 14 x 10 in. approx.
 ★ Response 30-20,000 c.p.s. Impedance 15 ohms
 Performance comparable with COMPLETE KIT units at twice the cost £25-95 Carr. 75p

Deposit £4-71 and 8 monthly payments £3-12 (Total £29-57)
 Consists of (1) 12in. 15w Bass unit with cast chassis. Roll rubber cone surround for ultra low resonance, (2) 3-way quarter section series cross-over system, (3) 8 x 4in. High flux midrange speaker, (4) Dome Pressure Tweeter, (5) Quantity acoustic damping material, (6) Handsome Teak veneered cabinet, (7) Circuit and full instructions.



R.S.C. TRANSFORMERS, L.F. CHOKES & RECTIFIERS FULLY GUARANTEED. Intermagned and interleaved where necessary. Primaries 200-350v. 60Hz Screened

MIDTET CLAMPED TYPE 7 1/2 x 2 1/2 x 2 1/2 in.	TOP SHROUDED DROP-THRO' TYPE	CHARGER TRANSFORMERS 0-9-15v. 7.5a. £1-75.	SELECTOR RECEPTORS P.W. (Bridge)
250v. 60mA, 6-3v. 2a. £1-50	250-0-250v. 70mA, 6-3v. 2a., 0-5-5-3v. 2a. £2-25	21a. £1-95; 3a. £2-00; 6a. £2-45; 6a. £2-75; 6a. £2-90	All 6 1/2v. D.C. output. Max. A.C. input 15v.
250-0-250v. 100mA, 6-3v. 2a. £1-60	250-0-250v. 100mA, 6-3v. 3-5a. £2-50	AUTO (Step Down) TRANSFORMERS	1a. 85p. 2a. 40p. 3a. 65p. 4a. 51p. 6a. 67p.
	250-0-250v. 100mA, 6-3v. 2a., 0-3-3-1a. £2-75	0-10/120v. 200-230-250v. 50-80 watts £2-50	L.F. CHOKES
	150-0-150v. 80mA, 6-3v. 2a., 0-5-5-3v. 2a. £2-75	150 watts, £2-50 250 watts £2-50 500 watts £2-50	150mA, 7-10H, 250 Ω £1-10; 100mA, 10H, 200 Ω 95p; 60mA, 10H, 400 Ω 85p.
	250-0-250v. 100mA, 6-3v. 4a., 0-5-5-3v. 3a. £3-75	OUTPUT TRANSFORMERS	
	300-0-300v. 100mA, 6-3v. 4a., 0-5-5-3v. 3a. £3-75	8Ω, Pentode 5000-3 Ω or 700-3 Ω. 85p	
	300-0-300v. 100mA, 6-3v. 4a., c.t. 6-3v. 1a. £4-50	Push-Pull 8 watts EL84 to 3 Ω or 15 Ω. £1-45	
	350-0-350v. 100mA, 6-3v. 4a., 0-5-5-3v. 3a. £3-75	Push-Pull 10 watts 6V, 3-5-8-15 Ω. £2-25	
	350-0-350v. 100mA, 6-3v. 4a., 0-5-5-3v. 3a. £4-50	Push-Pull EL84 to 3 Ω or 15 Ω 10-12 watts. £2-25	
	FLAMELET of TRANSFORMER POWER PACK	Push-Pull Ultra Linear for Mullard 610, etc. £2-75	
	Type 6-3v. 1-5a. £2; 6-3v. 2a. 85p; 6-3v. 3a. £2-45;	Push-Pull 15-18 watts, sectionally wound £1-65	
	6-3v. 6a. £2-25; 12v. 1a. 85p; 12v. 2a. or 24v. 1-5a. £2-25; 0-9-15v. 12a. £1-95; 0-12-25-42v. 2a. £2-75.	6L6, KTH6, etc., for 3 or 15 Ω. £2-20	
		Push-Pull 20 watt high quality sectionally wound EL34, 6L6, KT66 etc. to 3 or 15 Ω £2-50	

RSC 100 watt DISCO SYSTEM



Units listed below
 (a) DISCOMASTER TWIN TURNTABLE CONSOLE with integral 100W amplifier
 (b) PAIR OF HI-FI HEADPHONES
 (c) MATCHING DYNAMIC 'MIKE' (attached to h'phone)
 (d) PAIR 50 WATT SPEAKERS
 Black Rexine covered Cabinets. Size approx. 18" x 18" x 8"
 (a) (b) (c) & (d) Carr. £3-00
£159-95

RSC TDI DISCO CONSOLE

Incorporating twin Garrard SP25 or RSC MF60 type turntables and Sonotone or Acco cartridges with diamond styl. Separate Vol. controls for each turntable. Also MONITORING FACILITIES, plus Treble and Bass Controls. Separate input for 'mike's with vol. control switch. Black Vynide covered cabinet with lid. See illustration on left.
 Or Dep. 29-00 and 18 fortnightly pymts. £79-95
 Carr. £1-60

DEP. £19-95 & 18 fortnightly payments of £9-11 (Total £183-93).

STEREO VERSION OF ABOVE SYSTEM
 Or DEP £29-00 and 18 fortnightly pymts. £199-95
 Carr. £3-00 (Total £229-93)

TD'S STEREO VERSION OF ABOVE SYSTEM
 Terms. Dep. £15-00 and 18 fortnightly payments 29-51
 (Total £182-18) Carr. £1-60

DISCOMASTER TWIN TURNTABLE POWER CONSOLE £109-95 Carr. £2-50

Garrard SP25 or McDonald MF60 turntables. Sonotone or Acco cartridges with diamond styl. Facilities as TDI Console but with built-in 100 watt Power Amplifier, complete with lid. Or Deposit £12-95 and 18 fortnightly payments £8-31 (Total £188-32)

STEREO DISCOMASTER £145 Or DEP. £20 and 18 fortnightly pymts £8-15 (Total £186-70) Carr. £3

R.S.C. COLUMN SPEAKERS IDEAL FOR VOCALISTS AND PUBLIC ADDRESS
 All types 15 Ohms covered in Rexine and Vynide
TYPE C132 30-40 WATTS Fitted two exceptionally efficient, low feedback howl characteristic high flux 1 1/2" x 8" 20 watt speakers. Terms: Dep. £9-98 and 8 m'thly payments £2-67 (Total £25-31) Carr. 65p
TYPE C8/70 70 WATTS Fitted three 12" 25 watt Highly sensitive high flux speakers with high power voice coils. Size approx. 6 1/2" x 14" x 11". Dep. £5-12 & 8 m'thly pymts. £5-11 £39-95 (Total £46-90) Carr. 85p

FANE ULTRA HIGH POWER LOUDSPEAKERS

All power ratings are R.M.S. continuous. 2 YEARS' GUARANTEE High flux ceramic magnets. ALL CARRIAGE FREE.

'POP' 100	'POP' 60	'POP' 50
18" 100Watt 14,000 gauss 8/15Ω	15" 60 Watt 14,000 gauss 8/15Ω	12" 50 Watt 13,000 gauss 15Ω
£29-95	£16-95	£12-95
Dep: £8-80 & 5 m'thly payments £8-80 (Total £24-20)	Dep. £2-17 & 8 m'thly payments. £2-17 (Total £18-63)	Terms for pairs Dep £3-00 & 8 m'thly payments £3-10 Total £29-18

FOR BASS GUITAR, ELECT. ORGAN, ETC.

ALL RSC PRICES INCLUDE VAT INTEREST on Credit Purchases REFUNDED settled in 3 months

MINSTREL 8W GUITAR AMP.
 Incorporating Fremele and 12" x 8" or 10" Speaker. Output 8 watts R.M.S. Continuous. 3 Jack Inputs for Microphone and Instrument. Mains Neon Control: Volume, Tone, Tremolo Speed Tremolo Intensity.
 Terms: Deposit £9-95 and 8 monthly payments £2-50 (Total £29-95) Carr. free

FAL MAESTRO COMBINED 30W AMP. AND 12" SPEAKER £47-88 Carr. Free
 For Lead Guitar, Mic, Gram, Radio, Tape (Not for use with Bass Instruments) Inc. 3 inputs and 2 vol controls plus Treble & Bass, TREMOLO with associated controls. Attractively finished in black with silver-finished knobs. Compact size fitted carrying handle. Deposit £7-58 and 8 m'thly payments £5-75 (Total £29-88)

RSC 'PHANTOM 50' Rating 50 watts. 3 inputs, 2 vol. controls. Bass, Treble, Presence £55-00 Carr. £1-60
 Terms: Deposit £8-00 & 8 m'thly. pymts. £6-78 (Total £29-08)

FAL PHASE 50 Mk. III AMPLIFIER 50 WATT
 Solid state. 4 Separately controlled inputs Plus master vol. control. Ind. Bass and Treble Controls. Protective Circuitry against serious output overloading. Output for Speakers 8 to 15 ohms. Size 17" x 7" x 7 1/2". 200-250V. A.C. mains. Output 50 watts music rating. Or deposit 27-88 & 8 monthly payments £5-75. Total £33-88. Carr. Free

REGENT 50X 50 WATT AMP.
 A powerful high quality unit for lead, rhythm guitar, vocalists, gram, radio, tape. 60w Peak O/P rating. Not for Bass Guitars. * Two Fane heavy duty high flux 12in. spkr. * Four Jack inputs and two Volume Controls for instant use of up to four pick-ups or 'mike's'. Bass and Treble controls. Send S.A.E. for leaflet. Credit Terms: Deposit 29-95 & 18 fortnightly payments of £4-15 (Total £284-85). Carr. £2-60

REGENT 50B for Bass Guitar and general purposes. Or Dep. £10-85 & 18 fortnightly payments £4-73. (Total £98-00). Carr. £2-60

FAL DISCO PRE-AMPLIFIER T/Tape mixing inputs. Headphone Monitoring. Mic. Jack & Tape inputs. Independent Vol. Control. Std. 200-250V A.C. Mains operation. £18-50

'POP' 25/2 12" 30W. PH50 HIGH POWER TWEETER Rating 30 Watt Imp. 8Ω
 Dual cons. 15 ohm Imp. (Not for Bass Guitar use) £8-95 with 2 to 4 mft. Non elect. filter available 55p £5-95

GROUP EQUIPMENT PACKAGE OFFERS

F.A.L. PHASE 50 MK. III AMPLIFIER £47-88	PACKAGE PRICE
FR. FANE POP 60/6 60W L/SPEAKERS £17-80	Carr. £1-10
Terms: Deposit 27-88 and 8 monthly payments of 7-88 (Total £26-18)	£56-95
F.A.L. PHASE 50 MK. III AMPLIFIER £47-88	PACKAGE PRICE
FR. FANE POP 50 L/SPEAKERS £25-90	Carr. £1-10
Terms: Deposit £22-50 and 12 monthly payments of £4-20 (Total £27-40)	£63-95
F.A.L. PHASE 50 AMPLIFIER £47-88	PACKAGE PRICE
PAIR L12/25G 12" 25 WATT 15,000 GAUSS L/SPEAKERS (in cabinets) £26-99	Carr. £2-00
Terms: Deposit £22-00 and 12 monthly payments £4-20 (Total £27-40)	£63-95

HIGH QUALITY LOUDSPEAKER UNITS ALL TWO TONE VYNIDE AND VYNAIR FINISH

L12/2 50 WATT Fitted pair of 12" 30 watt high flux speakers for conservative rating. Impedance 8-15 ohms. Carr. £1-50
 Or deposit £5-11 and 8 monthly pymts. of £5-11. Total £25-99

L12/25G 12" 25 WATT 15,000 gauss 12in 15 ohms Terms for Pairs. Dep. £9-88 & 8 m'thly pymts £8-88 £12-95 (Total £28-88) Carr. 50p.

L12/10-15 10-15 Watt Veneered cabinet 12in 10-15 ohm. Carr. £1-50. Approx. 14" x 14" x 4". Dep. £5p. Terms for Pairs, Dep. £2-00 & 8 m'thly pymts £2-00 (Total £18-45).

GP30 AMPLIFIER
 For Guitar, Vocal or Instr. Group, Gram, Radio or Tape. 4 Inputs. 2 Vol. Controls. Current Valve. Peak clip rating. Strong Vynide covered cabinet with carrying handles. Black/Silver Face. Neon Indicator. For 200-250V A.C. For 3 or 16 Ω speakers. Send SAE for leaflet. Terms: Dep. £5-58 & 8 m'thly pymts £3-58 (Total £24-22) Carr. 75p

REGENT '50' AMPLIFIER
 As supplied with Regent 50x or 50B. Terms: Dep. £5-11 & 8 m'thly pymts £5-11 (Total £25-99) Carr. £1

TITAN 18" 100W SPEAKERS
 15 Ohm Impedance LIST PRICE £85 Carr 75p £25-95

NEW BRANCHES AT BOLTON, COVENTRY DONCASTER, PRESTON and STOCKPORT

OPEN ALL DAY SATURDAYS (5 Day Week)
BRADFORD 10 North Parade (Closed Wed.). Tel. 25349
BOLTON 23 Deansgate. (Closed Wed.). Tel. 33512
BIRMINGHAM 30/31 Great Western Arcade. Tel. 021-236 1279 (Closed Wed.).
COVENTRY 17 Shelton Square, The Precinct. Tel. 25983
DERBY 67 St. Peter's Street. (Closed Wed.). Tel. 41361
DARLINGTON 19 Northgate (Closed Wed.). Tel. 68043

Barclaycard and Access accepted
 All items subject to availability. Prices correct at 10.12.74 E. & O.E.

HI-FI CENTRES LTD.
DONCASTER 3 Queensgate, Waterdale Centre. (Closed Thurs). Tel. 63069
EDINBURGH 101 Lathian Rd. (Closed Wed.). Tel. 229 9501
GLASGOW 326 Argyle St. (Closed Tues.). Tel. 248 4158
HULL 7 Whitefriargate (Closed Thurs). Tel. 20505
LEICESTER 32 County Street (Closed Thurs). Tel. 58420
LEEDS 5-7 County (Mecca) Arcade, Briggate. (Closed Wed.). Tel. 28252
LIVERPOOL 73 Dale St. (Closed Wed.). Tel. 236 3573
LONDON 238 Edgware Road, W.2. (Closed Thurs.). Tel. 723 1829

MANCHESTER 80A Oldham Street (Closed Wed.). **MIDDLEBROUGH** 108 Newport Road (Closed Wed.). Tel. 47098
NEWCASTLE UPON TYNE 24 Newgate Shopping Centre (Closed Wed.). Tel. 21469

NOTTINGHAM 19/19A Market Street (Closed Thurs.). Tel. 48258
PRESTON 41 Friargate Walk, St. George's Shopping Prec. Tel. 61978
SHEFFIELD 13 Exchange Street (Can't Mkt. Bids.)
STOCKPORT (Closed Thurs.). Tel. 20716
 8 Little Underbank (Closed Thurs.). Tel. 480-0777
SUNDERLAND 5 Market Sq. (Closed Wed.). Tel. 70573





Newnes - Butterworths

Books on Radio, TV, Electronics etc . . .

- BEGINNER'S GUIDE TO COLOUR TELEVISION 2nd Edn. King. £2.10
- BEGINNER'S GUIDE TO ELECTRONICS 3rd Edn. Squires and Deason. £2.10
- DICTIONARY OF RADIO & TELEVISION. Pannett. £2.00
- ELECTRONICS: A COURSE BOOK FOR STUDENTS. Olsen. £2.85
- ELEMENTS OF TRANSISTOR PULSE CIRCUITS. Towers. £3.65
- GUIDE TO BROADCASTING STATIONS. 17th Edn. £0.90
- HI-FI AND TAPE RECORDER HANDBOOK. The King. £2.25
- INTEGRATED CIRCUIT POCKET BOOK. Hibberd. £2.70
- NEWNES COLOUR TV SERVICING MANUAL. VOL. 1. King. £5.20
- NEWNES RADIO ENGINEERS POCKET BOOK. 14th Edn. Moorshead. £1.30
- OPERATIONAL AMPLIFIERS. Clayton. £3.70
- OUTLINE OF RADIO AND TELEVISION. Hawker. £2.75
- PRINCIPLES & CALCULATIONS FOR RADIO MECHANICS. Part 1. Bravery-Gilbert. £1.65
- RADIO & AUDIO SERVICING HANDBOOK. 2nd Edn. King. £3.30
- RADIO, TELEVISION & AUDIO TEST INSTRUMENTS. 2nd Edn. King. £4.05
- RAPID SERVICING OF TRANSISTOR EQUIPMENT. 2nd Edn. King. £2.05
- RADIO VALVE AND TRANSISTOR DATA. 9th Edn. Ball. £1.00
- SOLID-STATE DEVICES & APPLICATIONS. Lewis. cased £3.25. limp £2.20
- SERVICING WITH THE OSCILLOSCOPE. King. £2.00
- TELEVISION ENGINEERS POCKET BOOK. 6th Edn. McGoldrick. £2.70
- TELEVISION SERVICING HANDBOOK. 3rd Edn. King. £4.10
- WIRELESS SERVICING MANUAL. 10th Edn. Cocking. £1.70

All these books, and many more, are available from

BELL'S TELEVISION SERVICES

190, KINGS ROAD, HARROGATE, YORKSHIRE. Telephone: 0423-55885

Prices include Post & Packing (U.K. only). Send large S.A.E. for FREE booklists. Open until 6 pm Daily and 8 pm Saturday

ENGINEERS

FREE

YOURSELF FOR A BETTER JOB WITH MORE PAY!

Do you want promotion, a better job, higher pay? "New Opportunities" shows you how to get them through a low-cost home study course. There are no books to buy and you can pay-as-you-learn.

This helpful guide to success should be read by every ambitious engineer. Send for this helpful 76 page FREE book now. No obligation and nobody will call on you. It could be the best thing you ever did.



CUT OUT THIS COUPON
CHOOSE A BRAND NEW FUTURE HERE!

Tick or state subject of interest. Post to the address below.

POST NOW

Build-As-You-Learn PRACTICAL RADIO AND ELECTRONICS (with kit)

Electronic Engineering

CITY AND GUILDS Installations and Wiring

Electrical Engineering

Computer Electronics

CITY AND GUILDS Electrical Technicians

Electrical Installations and wiring

Computer Programming

CITY AND GUILDS Telecommunications

Electrical Draughtsmanship

General Radio and TV Engineering

Radio Amateurs' Exam etc. etc.

Electrical Mathematics

Radio Servicing, Maintenance and Repairs

Translator Technology

To ALDERMAYSTON COLLEGE Dept. EPW-01 Reading RG7 4PF **EPW-01**

NAME (Block Capitals Please)

ADDRESS

Other subjects

Age

Accredited by C.A.C.C.

Member of A.B.C.C.

HOME OF BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

12" LONG PERSISTENCE CRT. Full spec. Price £8.50 to include V.A.T. and Carriage.

MAKE YOUR SINGLE BEAM SCOPE INTO A DOUBLE WITH OUR NEW LOW PRICED SOLID STATE SWITCH. 2 Hz to 8 MHz. Hook up a 9 volt battery and connect to your scope and have two traces for ONLY £3.25, P. & P. 25p. (Not cased, not calibrated.)

WIDE RANGE WOBBULATOR. 5 MHz to 150 MHz up to 15 MHz sweep width. Only 3 controls, preset RF level, sweep width and frequency. Ideal for 10-7 of TV IF alignment, filters, receivers. Can be used with any general purpose scope. Full instructions supplied. Connect 6 3V A.C. and use within minutes of receiving. All this for ONLY £3.75, P.&P.25p. (Not cased, not calibrated.) 20 Hz to 200 kHz WB.

SINE and SQUARE GENERATOR. Four ranges. Independent amplitude controls, thermistor stabilised. Ready to use, 9V supply required. £3.95 each, P. & P. 25p. (Not cased, not calibrated.)

GRATICULES 12cm x 14cm high quality plastic 15p each, P. & P. 5p.

Large quantity of good quality components — **NO PASSING TRADE** — so we offer 3lbs of **ELECTRONIC GOODIES** for £1.50. Post paid.

ROTARY SWITCH PACK—8 brand new switches (1 ceramic; 1 off 4pole 2 way etc.). 50p, P. & P. 20p.

P.C.B. PACKS S. & D. Quantity 2 sq ft—no tiny pieces. 50p plus P. & P. 20p.

CAPACITOR PACK—50 Brand new components, only 50p, P. & P. 20p.

TRIMMER PACK. 2 Twin 50/200pF ceramic 2 Twin 10/50pF ceramic; 2 min. strip with 4 preset 5/20pF on each; 3 air spaced preset 30/100pF on ceramic base. ALL BRAND NEW. 25p the lot. P. & P. 10p.

PHOTOCELL eqv. OCP71, 13p each. **MULLARD** OCP70—10p each.

DELIVERED TO YOUR DOOR 1 cwt of Electronic Scrap chassis, boards, etc. No rubbish. FOR ONLY £4.04.

MODERN TELEPHONES type 706. Two-tone grey, £3.75 each. Two-tone green £3.75 each. Black £3.75 each. P. & P. 35p.

Ideal **EXTENSION TELEPHONES** with standard GPO type dial, bell and lead coding. £1.75 each, P. & P. 35p.

HANDSETS — complete with 2 inserts and lead 75p each, P. & P. 37p. **DIALS** ONLY 75p each, P. & P. 25p.

HIGH VALUE—PRINTED BOARD PACK. Hundreds of components, transistors, etc.—no 2 boards the same—no short leaded transistor computer boards £1.75 post paid.

Beehive Trimmer 3/30 pf Brand new. Qty. 3—9 13p ea, P. & P. 15p 10—99 10p ea, P. & P. 25p; 100—999 7p ea, P. & P. free.

MF Crystal Drive Unit, 19in. rack mount. Standard 240V Input with superb crystal oven by Labgear (no crystals) £5 ea, Carr. £2.00

1000pf FEED THRU CAPACITORS only sold in packs of 10, 30p, P. & P. 10p.

ALWAYS some **CHEAP SCOPES** AVAILABLE—so build your own—send for our tube list with a S.A.E.

PLEASE ADD V.A.T. AT 8%
OPEN 9 a.m. to 6.30 p.m. ANY DAY

CHILTMead LTD

7/9 ARTHUR ROAD, READING, BERKS.
(near Tech. College) Tel.: Reading 382605/65916



Crescent Quality Components

BARGAIN CAPACITOR 2,200MFD at 85v. DC wkg.
Size = 2" x 1 1/2" diameter. Tag ended. All new and unused. Our price 35p.

STEREOMONO HEADPHONE VOLUME CONTROL BOX

Plug stereo phones into this control box and you then incorporate a right and left hand volume control and a stereo/monoswitch. Complete with stereo jack plug and 2m cable. A bargain at £1.



TWO WAY STEREO ADAPTOR

Stereo Jack plug to two stereo free sockets, complete with 110mm cable. For connecting two stereo inputs into one.

A bargain at 65p.



LIGHT EMITTING DIODES

TL208 (Red) With Chip 22p each
TL209 (Green) With Chip 33p each
TL209 (Yellow) With Chip 80p each
Mled 500 7092 Type 18p each

LED READOUTS
Ldtronix
DL707 .3 Character 14 Pin DIL 23-00
DL701 as above but ± 1 22-00
DL747 .6 Character 23-82

Miscellanea

3013 7 Segment 16 Pin DIL 41-38
30160 as above but ± 1 41-18
Clock Chip
CT7001 MOS/LSI Digital Clock/Calendar Chip Plus full Circuits and Information Leaflet 23-85
Circuits and Information Sheet 15p
Lit 704 Led Display for above 21-85
Or 4 for 25-25

WAFER SWITCHES

1 Pole 12 Way
2 Pole 3 Way
2 Pole 4 Way
2 Pole 6 Way
3 Pole 4 Way
4 Pole 3 Way
22p each



POTENTIOMETERS

All types 1" and less diameter

Bingles		Dual	
5K	Log or 5K	5K	
10K	Lin Lea 10K	10K	
20K	Switch 25K	20K	
50K	15p each 50K	50K	Less
100K	100K 45p each	100K	
200K	Double 200K	200K	
500K	Pole 500K	500K	
1M	Switch 1M	1M	
2M	30p each 2M	2M	

PRE SETS

Sub Miniature Skeleton Type 0-1 Watt Horizontal Mounting 100, 250 and 500 ohm, 1k, 2.5k, 5k, 10k, 25k, 50k, 100k, 200k, 250k, 500k, and 1M ohm 6p each

MAINS TRANSFORMERS

Open Type Double Wound Continuously Rated, two hole fixing clamp with colour coded fixing leads, varnish impregnated. Approx. size: 1 1/2" x 1 1/2" x 1 1/2" high
Fixing centres: 3 1/2".

TR1	20-0-20v 100 m/A	
TR2	12-0-12 v 100 m/A	All
TR3	0-0-9 v 100 m/A	240 Volt
TR4	6-0-6 v 100 m/A	Primary
TR5	3-0-3 v 100 m/A	

Our Price £1.28 each

200/250v MAINS RELAY

Heavy duty contacts 2-500 ohm coil. All new and unused D.P.D.T. mains relays 50p. Carr. Free. Special quantity 250 per 100 ct.

MINIATURE RELAYS

Brand new range of British made Relays. Size 1 1/2" x 1" x 1". All two changeovers with 250v 1.5A contacts and suitable for fitting on 1m Veroboard.

Type	Volts	Current	Ohms	All
27A	12v	173M/A	700	All
21A	12v	28M/A	430	£1-30
12A	6v	33M/A	180	each

DOUGLAS TRANSFORMERS

All types are standard 240 volt primary.
MT 102 ct. 0 = 19 = 25 = 33 = 40 = 50 at 500M/A

MT237cs	20-0-20 at 150M/A	£2-00 each
MT241cs	20-0-20 at 30M/A	£1-05
MT240cs	16-0-16 at 30M/A	£1-05
MT238cs	12-0-12 at 50M/A	£1-05
MT238cs	3-0-3 at 200M/A	£1-05

POWER PACKS

FP1 Switched 3 - 6 - 7 1/2 - 9 volt 400M/A Transistor and Zener Stabilised On/Off Switch and Polarly Reversal Switch, in a black metal case 25-25 each.
FP2 Switched 6 - 7 1/2 - 9 volt Battery Eliminator. Approx. size 2 1/2" x 2 1/2" x 3 1/2". Ideal for cassette recorders 22-75 each (philips type 23-00).
FP3 Car converter. From 12v Pos. or Neg. to 6 - 7 1/2 - 9 volt. Easy to fit and transistor regulated 23-90

VEROBOARD

2 1/2 x 3 1/2	82p	-15	Plain 15
2 1/2 x 5	84p	15p	
3 1/2 x 3 1/2	84p	15p	
2 1/2 x 5	89p	15p	
17 x 2 1/2	1-06p	77p	80p
17 x 3 1/2	1-45p	1-15p	75p
17 x 5	1-85p		1-10p

Pin insertion tool 72p
Spot face cutter 62p
Pkt. 36 pins (extra 1 or 15) 25p

LOUDSPEAKERS

2 1/2" 8 ohm	50p
2 1/2" 40 ohm	50p
2 1/2" 80 ohm	50p
5" 8 ohm	ceramic 41-25
6 1/2" 8 ohm dual cone	ceramic 42-50
10" 8 ohm dual cone	ceramic 43-75
7" x 4" 8 ohm	ceramic 41-80
8" x 5" 8 ohm Permanent Magnet	41-80



*EMI 13" x 8" 450 Kit 44-10
3 - 8 - 15 ohm 44-10
*Eal 15" x 8" 550 Kit 8 1/2 47-50

FANE ULTRA HIGH POWER LOUDSPEAKERS

*Pop 26/2 30 watt 150 ohm 12"	22-50
*Pop 25 60 watt 8/16 ohm 12"	41-50
*Pop 50 50 watt 15 ohm 12"	41-00
*Pop 60 60 watt 8/16 ohm 15"	43-70
*Pop 100 100 watt 8/16 ohm 15"	42-70

* Carr. on 1/8 over 13 x 8 and 12" 60p per L/R.

MAINS KEYNECTOR

Keyconnector connects any Electrical Equipment to the mains supply in seconds. Ideal for beach, garage demonstrations, etc. Multi connections can be made (max. load 13A fused). 43-25p.



ALUMINIUM BOXES

Metal project boxes give you work a professional finish

AB7	L	W	H	54p
AB8	4	4	1 1/2	63p
AB9	4	2 1/2	1 1/2	54p
AB10	4	2 1/2	1 1/2	68p
AB11	4	2 1/2	2	54p
AB12	3	2	1	45p
AB13	6	4	2	60p
AB14	7	5	2 1/2	84p
AB15	9	6	3	98p
AB16	10	7	3	£1-25
AB17	10	4 1/2	3	£1-00
AB18	12	6	3	£1-20
AB19	12	6	3	£1-50

ABS PLASTIC BOXES

Handy boxes for construction projects. Moulded extrusion rails for P.C. or chassis panels. Fitted with 1mm front panels.

1005	= 105mm x 75mm x 45mm = 61p
1006	= 150mm x 75mm x 47mm = 68p
1007	= 164mm x 124mm x 60mm = 90p
1021	= 105mm x 74mm x 45mm (sloping front) = 50p


BARGAIN BOARDS

Components galore for the experimenter Ex Computer boards with Resistors, Capacitors and useful Transistors - at least 4 transistors per board. Five boards £1-00.

CLEAR PLASTIC PANEL METERS

Size 59mm x 46mm x 35mm these meters require a 38mm hole for mounting.

ME6	= 0 to 50 micro amp Full Scale
ME7	= 0 to 100 micro amp Full Scale
ME8	= 0 to 500 micro amp Full Scale
ME9	= 0 to 1 mA Full Scale
ME10	= 0 to 5 mA Full Scale
ME11	= 0 to 10 mA Full Scale
ME12	= 0 to 50 mA Full Scale
ME13	= 0 to 100 mA Full Scale
ME14	= 0 to 500 mA Full Scale
ME15	= 0 to 1 amp Full Scale
ME16	= 0 to 50 volts A.C. Scale
ME17	= 0 to 300 volts A.C. Full Scale
ME18	= "B" Meter
ME19	= "VU" Meter

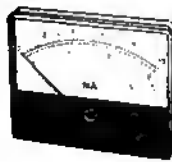

OUR PRICE £2-00

Q-MAX SHEET METAL PUNCHES

The easiest and quickest way of punching holes in sheet metal (up to 1-625mm Mild Steel)

DECOR	DALO	23PC	SIZE	PRICE
RTCH	RESIST	PEN	1"	68p
The Decoon Dalo 33PC is a unique instrument for the professional and amateur electronics engineer, enabling him to prepare in minutes a perfect printed circuit board				Key "A" 6p
OUR PRICE 80p				Key "B" 10p
ADD LUXURY TO YOUR CAR with a motor driven car aerial				Key "C" 20p

SPCC-	★	5 section	1 1/2"	21-05
	★	extended length 100cm	1 1/2"	21-10
	★	Length under fender 40cm	1 1/2"	21-25
	★	Cable length 120cm	2 1/2"	22-30
Supplied complete with fixing bracket and control switch				Key "E" 20p

1" SQUARE PUNCH complete with key 22-10

STOP PRESS

BBA0002	15 watt Amp Module	22-50
NE565	Timer I.C.	75p
MC1310P	Stereo Decoder I.C.	22-00
7805	Regulator	21-40
TIP 29A		55p
TIP 30A		82p
BC107		10p
BC 108		10p
BC109		10p



I.C. SOCKETS
D.I.L.
8 pin
14 pin
16 pin

BARGAIN TRANSFORMERS

12-0-12 volt 500m/a
240 volt primary transformer bargain. approx size = 60mm x 40mm x 50mm
fixing centres = 75mm
Our Price = £1-26.

18 volt 500m/a
240 volt primary transformer bargain. approx size = 60mm x 40mm x 50mm
fixing centres = 75mm
Our Price = £1-00.

BARGAIN BOX

Load buzzer mounted in a metal box complete with two U2 battery size holder. Designed and can be used as a fire alarm but is ideal as a door or Morse code practice buzzer. Approx. size - 2 1/2" x 6 1/2" x 1 1/2".
OUR PRICE - 50p.

**U.K. POSTAGE 15p
UNLESS OTHERWISE
STATED**

**V.A.T. Please add
8% to all Totals**

CRESCENT RADIO LTD.

All mail to 11 MAYES ROAD,
WOOD GREEN, LONDON N22 6TL
Phone: 01-888 3206

Callers Welcome at
15 Mayes Road & 13 South Mall, Edmonton N9.

If you construct
You should
own one.

**CRESCENT
CATALOGUE
Price 20p.**

SPOT FREQ. OSC UNITS. Suitable for testing A.F. & Vid Amps Scopes, Digital circs, Signal Injection etc. These give a 1 : 1 Square wave of 6v Pk Pk or 2.5v Pk Pk into 75 ohm uses 4 transis inc Unijunction osc. Contained in all case size 4½" x 1½" x 1½" fitted standard coax sk plug supplied, reqs supply of 9v DC. The following freq are available 100, 500c/s, 1, 5 & 10Kc. Price £2 other freqs in this range are available at 25p extra. Supplied with circ. **HEAD & MIKE SETS** for use with 19 set new boxed £2. U.H.F. W.M. absorbtion type range 410 to 470 Mc/s direct calibration req 150v Ht & 6.3 to work, can be used with phones £3. **METER UNIT** 270° scale 1 Ma FSD 3½" sq front scale 0 to 20 also as 100-0-100Ua meter in same case ex a/c £3-38. CRT type 7BP7A 7" flat face Blue/Yell phosfor 6.3 heater okay for SSTV new £2. **SCOPES** American general purpose bench scopes 115v 50c/s, single beam, 3" tube, Y amp 2c/s to 11 Mc/s at 50 Mill/V per inch. Time & voltage calibrators, with probes & accs tested with copy of inst book. £40. **LEDEX SWTS** coils 12/24v DC as 7 contact banks, also dual actuators allowing clock or anticlock rotation new £1-30. **TELEPRINTERS** Creed type 85R printing reperforators good cond £12. **H.T. TRANS** 230v prla, 1125-0-1125v at 565 Ma new £8-64 matching choke £1-50. **YAXLEY SWTS** all new unused with ceramic wafers, 2p 5w, 3p 3w, 4p 2w all 35p ea. 3p 11w 3b 75p ea, 6p 11w 6b & 12p 4w 6b £1 ea. larger type Inst swts with pax wafers new unused 8p 12w 8b & 2p 23w 2b both £1-30 ea. 7p 23w 7b £1-60 ea. H.D. Tx type ceramic 2p 3w 2b 4 pos new £1-70. **METER** 500 Ua 1½" dia scale 0 to 5 on small panel with swts £1-45. **TRIMMERS** 20pf ceramic air spaced new 10 for 65p. **VIDICON CAMERA TUBES** type P862 general purpose 6.3 95 Ma heater with data sheet tested £9-50 CRT type VCR138 3.5" green phosfor, 4v heater, 1.5Kv EHT, with base, mu metal shield & connections ex equip £4-40. **CONT METER** No. 1 Geiger counter .1 to 10 Mill/Rongt with mains P.U. new boxed & tested with carrying haversack £6-10. **HEADPHONE LEAD** with high to low res trans, 5ft lead with standard jack plug new 70p. **NEONS** small wire ended type new 10 for 70p. **TUNING CONDS** 50pf ½" shaft 55p. Also 2 gang 25pf ½" shaft 95p. **RELAYS** 12v 4p c/o sealed 75p also 2p c/o min type 40p. **SILICON DIODES** 200 PIV at 8 amps 4 for 75p. **COAX CABLE** good quality 75 ohm 15 mts for £1-20. **HEAD & MIKE SET** No. 15 for use with 88/31 set as boom type mike ex equip £2. **PLUGS & SKS** with cover & cable clamp 25 way 55p. 18 way 35p. Also miniature types 50 way £1, 36 way 75p. 24 way 50p. **MANUALS.** The following are Photostat copies R1155 A to N, R1475, 19 set, 62 set, R107, CT38, 13A, AR88D or LF, 1049 Mk. 1, all £2-42 ea, CR100 £3-85, CT316 £2-20, CT52/84 £1-32, R1392 £1-43, R209 Mk 1 & 2 £1-65, S640 £1-10, 88 set £1-21, 31 set £1-65, TF144G £1-21, 92 set £1-10, HRO Rx Ux & Octals £2-64. 730/4 £2-20, CD711. S2 £4. **CIRCS** only R3673, R220, CRT26, PCR 2 & 3, ARR-2, B44, all 70p ea. 1035 Mk. 1, 2 or 3: 1049 Mk 1 or 3a 88p ea. CT54 with P.U. 70p. R4187 £1-10, others available.

Above prices inc Carr and VAT. SAE for list No. 11 or enquiry. Goods ex equipment unless stated otherwise.

A. H. SUPPLIES

57 MAIN RD., SHEFFIELD S9 5HL. 444278 (0742)


QUALITY STEREO SOUND

SOLENT AUDIO SYSTEM

ALMOST 1/2 PRICE OFFER!

MADE TO SELL AT DOUBLE THE PRICE IN CABINET FORM
OUR PRICE £49-95

£5 down

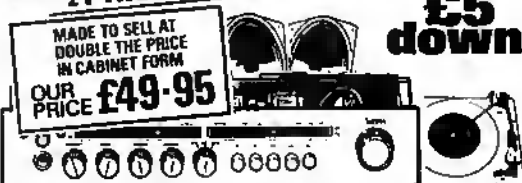

*Stereo Tuner Amplifier chassis with AM/FM radio covering long medium short and Stereo FM wavebands. Separate Base and Treble controls. Power output 7 watts R.M.S. per channel (frequency response 25-20,000 Hz) Tape record and playback facilities. Dimensions 18" x 8½" x 3¼". The very latest BSR automatic record deck with cue and pause control. Two matching elliptical speaker units.

Order early limited stocks available cash price £49-95. Credit Sale £5-00 deposit 9 monthly payments of £5-75 (Total Credit price £56-75). P. & P. £2-50. Send £7-50 today.

Chassis only available for cash at £35-00.

Full 12 months Guarantee.

CALLERS WELCOME.


Stereo headphones supplied with every complete order.

LEWIS radio

PW/2/75

100 CHASE SIDE SOUTHGATE
LONDON N14 5PL. Telephones: 01-882-1644

CARBON SLIDE POTENTIOMETERS

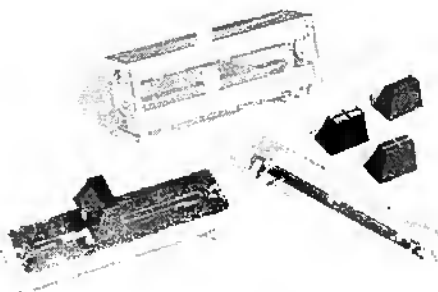

60mm Single Track including Black Knob 50p (inc. V.A.T.), 60mm Twin Track including Black Knob 60p (inc. V.A.T.), 60mm Quad Slide Potentiometers—Prices upon application. 1K, 5K, 10K, 25K, 50K, 100K, 500K ohms Log, Lin, Antilog. Metal Case. 3.2db Matched Track. 15mV Nominal Noise (B.S. 2122). Life Exceeds 20,000 cycles. Fixing Holes 2 x M3 on 80mm Centres.

Designed, Manufactured and Supplied by:—

RIVLIN INSTRUMENTS LTD

DOMAN ROAD, CAMBERLEY, SURREY GU15 3DJ

Send cash with order to above address. Postage and packing 15p per order. Trade enquiries invited.

AMM

and make no mistake

TMK 200 MULTIMETER KIT

Build yourself a quality 20000 opv. multimeter and save money. Complete kit with meter scale, movement and rotary range selector ready mounted in cabinet. All parts, batteries, test leads and instructions. Ranges: 0.6 6 30/120/600/1200V D.C. 0.6 30/120/600/1200V A.C. Current: 0.0 0.6/6/60/600mA. Resistance: 0 10/100k/1.1 Meg ohms. Decibels: -20 to +63dB. Size: 90 x 150 x 35mm

OUR PRICE £7.95 P & P 30p



U4323 MULTIMETER

20,000opv. Simple unit with audio/IF oscillator. Suitable for general receiver tuning. Resistance: 0.5/2.5/10/50/250/500/1000V DC. 2.5/10/15/250/500/1000V AC. 0.05/0.5/5 50 500mA DC. Resistance: x 10, x 100, x 1,000, x 10,000 (50k). 500k, 1k, 50k (centre scale). Battery operated. Size: 160 x 97 x 40mm. Supplied in carrying case complete with test leads.

OUR PRICE £7.70 P & P 30p



MODEL 500

30,000 opv with overload protection. Mirror scale. 0/0.5/2.5/10/25/100/250/500/1000V DC. 0/2.5/10/25/100/250/500/1000V AC. 0/0.5/0.5/5/50/500mA. 12A DC. 0/60k/6 meg/60 megohms.

OUR PRICE £13.95 Carr. paid



HIKI 730X

-30,500 opv. Overload protection. 6.30/60/300/600/1200V DC. 0.2/160/120/800/2700V AC. 60/μA/30mA/300mA. 2k/20k ohms. 2 Meg Ohm. -10 to 63dB.

OUR PRICE £7.50 P & P 30p



HIKI 750X VOLT-Ohm-MILLIAMETER

43 range. 0-0.30/6/1.5/3/6/12/30/60/150/300/600/1200V DC. 0-3/6/15/30/60/120/300/600/1200V AC. Current: 0-30/60mA/1.5/3/15/30/150/300mA/8/12A. Resistance: 0-3/200k/20Megohms. Decibels: -10 to +17dB. Output: -0.3/6/15/30/60/120/300V. Accuracy: 3% DC, ±4% AC. Sensitivity: 50,000 opv DC, 5,000 opv AC. 4 inch meter. Built in protection. Size: 57 x 102 x 153mm.

OUR PRICE £11.95 P & P 40p



U4324 MULTIMETER

High sensitivity, overload protected. 20,000opv. Ranges: 0.6/1.2/3/12/30/60/120/600/1200V DC. 3/6/15/30/60/150/300/600/1200V AC. Current: 0.06/0.6/6/60/600mA/3A DC. 0.3/3/30/300mA/3A AC. Resistance: 25/50 ohms/0.5/5/50/500k ohms/5 Megohms. Decibels: -10 to +12dB. Size 167 x 98 x 63mm. Supplied complete with test leads, spare diode and instructions.

OUR PRICE £9.25 P & P 30p



TMK MODEL TW50K

46 ranges, mirror scale. 50kV DC. 50kV AC. DC Volt: 0.125/0.25/1.25/2.5/5/10/25/50/125/250/500/1000. DC current: 25/50A/2.5/5/25/50mA. 12A. Resistance: 0.5/5/50/500/10k/100k/1Meg/10Meg/100Meg. -20 to +81.5dB.

OUR PRICE £12.50 P & P 24p



U435 MULTIMETER

20,000opv. Ranges: 75mV/2.5/10/25/50/100/250/500/1000V DC. 2.5/10/25/100/250/500/1000V AC. Current: 50mA/1/5/15/30/60/100mA/1A DC. 5/25/100mA/0.5/2.5/5A AC. Resistance: 0.3/3/30/300 ohms. Size: 205 x 110 x 84mm. Supplied complete with leads, crocodile clips and steel carrying case.

OUR PRICE £8.75 P & P 30p



HIKI MODEL 780X

100,000opv. Overload protection. Mirror scale. 0.3/0.6/1.2/1.5/3/6/12/30/60/120/300/600/1200V DC. 1.5/3/6/12/30/60/150/300/600/1200V AC. 0/6/30/60/120/300/600/150/500mA/8/12A DC. 2k/20k/200k/200Megohms. -20 to +63dB.

OUR PRICE £14.95 P & P 30p



U4312 MULTIMETER

Sturdy sturdy instrument for general electrical use. 6670 opv. 0/0.2/1.5/3/30/60/150/300/600/300V DC & 75mV/0.30/3.15/5/30/60/150/300/600/900V AC. 0/300mA/1.5/6/15/150/60/0.01/0.1/1/5/5A DC. 0/1/5/6/15/60/150/300/600mA. 0.2/200/3k/30k ohms. DC resistance 1%. AC 1.5%. Knife edge pointer, mirror scale. Complete with sturdy metal carrying case, leads and instructions.

OUR PRICE £10.25 P & P 50p



Model HT10084 MULTIMETER

Overload protected, shock proof circuitry. 8.5uA Wrist with mirror scale. Sensitivity 100kV. Polarity change over. Ranges: 0.5/2.5/10/25/50/100/200V DC. 2.5/10/50/100/200/500/1000V AC. 0-20/20k/220 Meg. ohms. DC current: 10/250mA/2.5/25/250mA/10A. AC current: -10A, -20 to +82B. Operates from 2 x 1.5V batteries. Size: 180 x 134 x 79mm.

OUR PRICE £17.50 P & P 40p



U91 Clamp VOLT AMMETER

For measuring AC voltage and current without breaking circuit. Ranges: 300/600V AC. Current: 10/25/100/250/500A. Accuracy 4%. Size 283 x 90 x 38mm. Complete with carrying case, leads and fuses.

OUR PRICE £13.50 P & P 30p



MODEL AS.1000 VOM

100,000 opv. Mirror scale. Built-in meter protection. 0.3/12/60/120/300/600/1200V DC. 0.6/30/120/300/600V AC. 0/10/10A/6.6/30mA/2k/20k/200 Meg Ohms. -20 to +17.6B.

OUR PRICE £17.50 P & P 30p



MODEL C720ZEN

20,000 opv DC. 10,000 opv AC. Mirror Scale. 5 25 50 250 600 1000 2500 V. DC. 10 50 100 500 1000 V. AC. DC Resistance x10, x100 (30k) centre scale) DC Current 50uA 2 SinA 250mA. -20 to +68 dB.

OUR PRICE £6.95 P & P 30p



KAMODEN HM720B FET VOM

Input impedance 10 Megohms. Ranges: 0.25/1.25/10/50/100/500/1000V DC. 0.2/5/10/50/100/500/1000V AC. 0/2.5/10/50/100mA DC. 0/5/10/50/500/5M 500 Megohms

OUR PRICE £21.00 P & P 40p



KAMODEN 360 MULTIMETER

High sensitivity. DC 100kOhm/V. AC 10kOhm/V. 5" mirror scale, overload protection. Ranges: 0.5/2.5/10/50/100V DC. 5/10/50/250/1000V AC. Current: 0.1/1/10/100 ohms/1/10/100 ohms/10/100 ohms. Decibels: -20 to +62B. Battery operated. Size: 180 x 140 x 60mm. Supplied complete with test leads etc.

OUR PRICE £17.50 P & P 40p



TMK MODEL 117 FET ELECTRONIC VOLT METER

Battery operated. 11 Meg input, 26 ranges. Large 4.5" mirror scale. Size: 149 x 117 x 60mm. 0.3-12000V DC. 3-300k/10MS AC. 8-800V P-P. DC current 0.12-12mA. Resistance up to 200Megohms. Decibels: -20 to +51dB. Supplied complete with leads and instructions.

OUR PRICE £18.50 P & P 20p



TMK 100K LAB TESTER

100,000opv. 6" scale. Buzzer, short circuit check. Sensitivity 100,000 opv. 50kV AC. DC Volt: 0.125/0.25/1.25/2.5/5/10/50/100/250/500/1000V AC. 3/10/50/250/500/1000V DC. current: 10/100mA/100/100/25/10A. Resistance: 1k/10k/100k/10 Meg/100 Meg ohms. Decibels: -10 to +45dB. Plastic case with carrying handle. Size: 130 x 172 x 39mm.

OUR PRICE £19.95 P & P 30p



370WTR MULTIMETER

Features AC current ranges: 20 000opv. 0/0.5/2.5/10/50/250/500/1000V DC. 0/2.5/10/50/250/500/1000V AC. 0/50mA/100/100mA/1A/10A DC. 0/100mA/1/10A DC. 0/100mA/1/10A AC. 0/100mA/1/10A AC. 0/100mA/1/10A AC. 5 Meg/50 Meg. Decibels: -20 to +62dB.

OUR PRICE £19.95 P & P 30p



KAMODEN 72.200 Multitester

High sensitivity tester. 20,000 opv Overload protected. Mirror scale. Ranges: 0.01/0.1/0.3/3/30/120/300/600/1200V DC. 0/3/12/60/300/1200V AC. 0/0.6/6/60/600mA/10A DC. 0/100mA/1A DC. 0/100mA/1A DC. 0/100mA/1A DC. 0/100mA/1A DC. 5 Meg/50 Megohms. Decibels: -20 to +62dB.


OUR PRICE £22.50 P & P 30p



U4317 MULTIMETER

High sensitivity instrument for field and laboratory work. Knife edge pointer, 36mm mirror scale. Overload protection. Ranges: 100mV/0.5/2.5/10/25/50/100/250/500/1000V DC. 0.5/2.5/10/25/50/100/250/500/1000V AC. Current: 50mA/0.5/1/5/10/50/250mA/1/5A AC. Resistance: 0.5/10/100/200 ohms/1/2k/30/300k ohms. Decibels: -5 to +10dB. Battery operated. Size: 210 x 115 x 30mm. Supplied in carrying case complete with leads.

OUR PRICE £16.50 P & P 40p

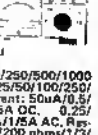

MODEL C720BFM

30,000 opv DC. 15,000 opv AC. 6 3 15 50 300 600 1200 V DC. 6 30 120 600 1200 V. AC. DC Resistance x1, x10, x100, 1000 (50k) centre scale) DC Current 30uA/3.30 600mA -20 to +63dB.

OUR PRICE £8.95 P & P 30p



MODEL U4311 Sub-standard Multi-range Volt-Ammeter

Sensitivity 330 Ohms/Volt AC and DC. Accuracy 0.5% DC. 1% AC. Scale length: 165mm. 0/300/750mA/1.5/3/7.5/15/30/75/150/300/750mA/1.5/3/7.5/15/30/75/150/300/750V AC. Automatic cut out device. Supplied complete with test leads, manual and test certificates.

OUR PRICE £52.00 P & P 50p



MODEL AF.105 VOM

50,000 opv. Mirror scale. Meter protection. 0/3/3/12/60/120/300/600/1200V DC. 0.6/30/120/300/600/1200V DC. Decibels: -20 to +62B. 0-30uA. 6-60/200mA. 2.2mA. 0.1/10k. 1m/10m/100 Meg Ohms. 20 to 17dB.

OUR PRICE £12.50 P & P 30p



LB3 TRANSISTOR TESTER

Tests ICO and ICS. PNP/NPN. Operates from 9V Battery. Instructions supplied.

OUR PRICE £3.95 P & P 20p



LB4 TRANSISTOR TESTER

Tests PNP or NPN transistors. Audio Indication. Operates on two 1.5V batteries. Complete with instructions etc.

OUR PRICE £4.50 P & P 20p



KAMODEN TT35 TRANSISTOR TESTER

High quality instrument to test reverse leak current and DC current. Amplification factor of NPN/PNP diodes, transistors, SCR's etc. 4" square clear scale meter. Operates from internal batteries. Complete with instructions, leads carrying handle.

OUR PRICE £17.50 P & P 40p



U4341 Multimeter & Transistor Tester

27 ranges. 15,700opv. Overload protected. Ranges: 0.3/1.5/6/30/60/150/300/600V DC. 1.5/7.5/30/150/300/750V AC. Current: 0.06/0.6/6/60/600mA AC. 0.3/3/30/300mA AC. Resistance: 0.01/0.1/1/10/100/1000/10000 Ohms. Battery operated. Supplied complete with probes, leads and steel carrying case. Size: 115 x 215 x 90mm.


OUR PRICE £10.50 P & P 30p



S100TR MULTIMETER TRANSISTOR TESTER

100,000opv. Mirror scale. Overload protection. 0.3/3/12/30/120/300V DC. 0.6/3/12/30/120/300V AC. 0/10k/100k/1M/10M/100M Ohms. Decibels: -20 to +50dB. 0.01-0.2 mFD. Transistor tester measures Alpha, Beta and ICS. Complete with instructions, batteries and leads.

OUR PRICE £19.95 P & P 25p

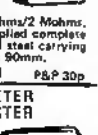

ALL PRICES EXCLUDE VAT

Also see following pages

SINCLAIR DM2 DIGITAL MULTIMETER

Will measure AC and DC volts, AC and DC current, and resistance in a total of 20 ranges. The large light emitting diode display will read on to 1999 and automatically indicate polarity. Indication of positive and negative overload is also provided. The instrument is fitted with a combined carrying handle and bench stand and sockets are provided for the connection of an external power supply.

RANGES:
DC VOLTS: 1v, 10, 100v, 1000v.
AC VOLTS: 1v, 10v, 100v, 1000v
DC CURRENT: 1mA, 10mA, 100mA, 1000mA
AC CURRENT: 1mA, 10mA, 100mA, 1000mA
RESISTANCE: 1k, 10k, 100k, 1000k

OUR PRICE £59.95 P & P 50p

SWR Meter Model SWR3

Handy SWR meter for transmitter antenna alignment, with built-in SWR strength meter. Accuracy 5%. Impedance 50 Ohm. Indicator 100uA DC. Full scale 5 section collapsible antenna. Size 145 x 50 x 60mm.

OUR PRICE £4.25 P & P 30p

C15 PULSE OSCILLOSCOPE

For display of pulsed and periodic waveforms in electronic circuits. VERT. BANDW. Bandwidth: 10MHz. Sensitivity at 100kHz: 1Vrms/mm: 0.1-25; 100uA: AMP. Bandwidth: 500kHz. Sensitivity at 100kHz: 1Vrms/mm: 0.3-25. Pulse triggered sweep 1-3000times. Free running 20-200kHz in nine ranges. Calibrator 30p, 200 x 360 x 430mm, 115-230V AC.

OUR PRICE £43.00 Carr. paid

RUSSIAN C116 Double Beam OSCILLOSCOPE

5MHz p.p.s. band. Separate Y1 and Y2 amplifiers. Rectangular 5" x 4" CRT. Calibrated triggered sweep from 0.2usec. to 100 micro-sec/m. Free running time base, 50Hz-1MHz. Built-in time base Calibrator and amplitude Calibrator. Supplied complete with all accessories and instruction manual.

OUR PRICE £87.00 Carr. paid

MODEL TE15 GRID DIP METER

Transistorised. Operates as Grid Dip Oscillator, Absorption Wave Meter and Oscillating Detector. Frequency range 40kHz-280MHz. In six coils, 500uA meter, 9V battery operation. Size: 180 x 80 x 40mm.

OUR PRICE £17.50 P & P 30p

TRANSISTORISED L.C.R. A.C. BR/B MEASURING BRIDGE

A new portable bridge offering excellent range and accuracy at low cost. Resistance: 6 ranges; 0.1 ohm-11.1 megohm. Inductance: 6 ranges; 1 microhenry-111 henries. Capacity: 6 ranges; 10pF-1110 microfarads. Ratio: 6 ranges; 1:1, 1000:1-1:11100. Bridge Voltage at 1.000cps. Operated from 3-volt battery. 100 microamp meter indication. Size 7 1/2" x 5" x 2"

OUR PRICE £25.00 P & P 30p

TE-200 RF SIGNAL GENERATOR

Accurate wide range signal generator covering 10 to 100 MHz on 6 bands. Directly calibrated Variable R.F. attenuator audio output. Xial socket for calibration 230 240V a.c. Brand new with instructions. Size 140mm x 215mm x 170mm.

OUR PRICE £17.50 P & P 50p

TE22 SINE SQUARE WAVE AUDIO GENERATOR

Sine 20cps to 200kHz. Square 20 cps to 30 kHz. Output impedance 500 Ohms. 200/250V AC operation. Supplied brand new guaranteed, with instruction manual and leads.

OUR PRICE £24.95 P & P 50p

ARF 300 AF/RF SIGNAL GENERATOR

All transistorised compact fully portable. AF sine wave 18Hz to 220 kHz. AF square wave 18Hz to 100kHz. Output Square Wave 100V P.P. 100kHz in 20MHz. Output 1V maximum. 220/240V AC operation. Complete with instructions and leads.

OUR PRICE £37.50 P & P 50p

WALKIE TALKIES SKYFONN2

Super low cost transmitter receivers. 100MW with call buzzer and on off volume control. 7 Transistors. Telescopic antenna.

OUR PRICE £28.95 per PAIR P & P 50p. NOT LICENSABLE IN THE U.K.

MODEL MC100 SINE SQUARE WAVE AUDIO GENERATOR

Range 19-220,000Hz Sine Wave 15-100,000 Hz Square Wave Output Sine or Square wave 10v P to 50 x 50 x 90mm Operation 220-240V A.C.

OUR PRICE £19.95 P & P 50p

POWER RHEOSTATS

High quality ceramic construction. Windings embedded in epoxy enamel. Heavy duty brush wiper. Continuous rating. Sine hole fixing. 3/4" diameter shafts. Bulk quantities available.

25 WATT 10 25 50 100 500-1000 2500 ohms. £1.15 P & P 10p
50 WATT 10 50 100 250 500. 1500 5000 ohms. £1.62 P & P 10p
100 WATT 1/5 10/25 50 250-500 2500 ohms £2.34 P & P 15p

SPECIAL PURCHASE (LIMITED QUANTITY)

Tannoy 12" DR/8 Bass Speakers
8 ohms 30 watt Heavy duty. Ideal for Hi-Fi A Group.

OUR PRICE £12.50 P & P 50p.

AUDIOTRONIC LE-102A INTERCOM

Beautifully made and finished in two tone ivory buff, the LE-102A is useful in the home, office or shop and is suitable for use as a baby alarm, Wall or desk mounting. 57mm speaker. mics give clear 2-way communication with on off volume control on master unit. Operates on 9V batt. Approx 60ft lead.

OUR PRICE £3.95 P & P 30p

PS200 Regulated POWER SUPPLY UNIT

Solid state. Variable output 5-20V DC up to 2 Amp. Independent meters to monitor voltage and current. Output 200/240V AC. Size: 190 x 136 x 98mm.

OUR PRICE £19.95 P & P 50p

TRITON 4318 PORTABLE 8 TRACK CARTRIDGE PLAYER WITH MW/LW RADIO

Will play 8 track stereo cartridge manually. Channel selector switch. Covers medium and long wave bands. Volume and tone controls. Earphone socket. Battery Mains operation.

OUR PRICE £11.95 P & P 50p

EA41 REVERBERATION AMPLIFIER

Self contained, transistorised battery operated. Simply plug in microphone, guitar etc. and output in your amplifier. Volume control and depth of reverberation control. Bandwidth cabinet, 184 x 77 x 108mm.

OUR PRICE £7.50 P & P 30p

LH025 STEREO HEADPHONES

Light weight headphones with padded ear-cups. 16 Ohms 20-20,000Hz. Complete with 5' lead and plug.

OUR PRICE £1.97 P & P 30p

DH025 STEREO HEADPHONES

Wonderful value and excellent performance combined. Adjustable head band. Impedance 8 ohms. 20-12,000Hz. Complete with lead and plug.

OUR PRICE £2.25 P & P 30p

TE1035 Stereo HEADPHONES

Low cost with excellent response. Foam rubber earcups. Adjustable headband. 8 ohms impedance. Frequency response 20Hz-18kHz. Complete with cable and stereo jack plug.

OUR PRICE £2.80 P & P 30p

SDMBV MONO/STEREO HEADPHONES

Volume control for each channel. 4/16 ohms impedance. Frequency response 20Hz-18kHz. Complete with 10ft. coiled lead and jack plug.

OUR PRICE £4.97 P & P 30p

BH001 HEADSET and 800m Microphone

Moving coil. Ideal for language teaching communications.

Headphone impedance 16 ohms. Microphone impedance 200 ohms.

OUR PRICE £5.95 P & P 30p

HANIMEX HRC 3075 CASSETTE RADIO

Covers Medium and FM wave-bands. Slider volume and tone controls. Battery Mains operation. Will record direct from radio or through built in condenser microphone. Complete with batteries, earphone, and cassette.

OUR PRICE £24.30 P & P 50p

SPECIAL OFFER! CONVERT YOUR STEREO SYSTEM TO 4D UNDER 10!

Exclusive offer of GOODWIN 4 CHANNEL CONVERTER and a pair of AD15 10 watt 8 ohm bookshelf speakers enables you to 'add 4D' sound to your existing system. Complete with simple connection details. Retail rental value £25.50.

OUR PRICE £15.80 P & P £1
GOODWIN CONVERTER available separately £3.95 P & P 50p

SPECIAL BARGAIN !! STEREOSOUND SPEAKERS

Matched pair of stereo bookshelf speakers. Deluxe oak veneered finish. Size: 368 x 229 x 190mm. 8 ohms. 8 watts RMS, 16 watts peak. Complete with Din lead.

OUR PRICE £12.95 PAIR P & P 50p

FM TUNER CHASSIS

6 transistor high quality tuner. Size only 153 x 101 x 63mm. 3 IF stages. Double tuned discriminator. Ample output to feed most amplifiers from an SV battery. Covers 88-108MHz. Ready built, ready for use. Fantastic value for money.

OUR PRICE £8.95 P & P 20p
Stereo Multiplex Adaptor £5.95 extra

Model A1018 FM TUNER

6 transistor high quality unit-3IF stages and double tuned discriminator. For use with most amplifiers. Covers 88-108MHz. Powered by 9V battery.

OUR PRICE £13.50 P & P 30p
Stereo multiplex adaptor £5.95 extra

ELECTRONIC CALCULATORS

We carry a tremendous range of both pocket and desk calculators from as little as £8.90. Owing to the demand it is not possible to include them in this advertisement, so send for our latest price list or call into any branch.

MINIATURE ORGAN MUSIC MASTER A100

Spanning nearly two octaves, including sensations - tonulations. This instrument will give hours of enjoyment to all the family. Beautifully finished. The Keyboard range can be adjusted to be in tune with any instrument. Operates from internal 9V battery. Fitted with on off switch, vibrato switch, earphone socket and 9V C.C. socket.

OUR PRICE £7.95 P & P 50p

BINATONE DIGITAL CLOCK

Attractive ivory case. Large clear numbers for hours, minutes and seconds. A.C. 240V operation. Size approx 8 1/2" x 7 1/2" inches.

OUR PRICE £4.50 P & P 30p

SINCLAIR IC12 INTEGRATED CIRCUIT AMPLIFIER

Complete with printed circuit mounting board.

OUR PRICE £1.50 P & P 15p.

SINCLAIR Project 80 Modules

240 Power Amp	£5.95	P & P 15p
480 Power Amp	£7.95	P & P 15p
Stereo 80 Pre-Amp	£13.95	P & P 15p
Active Filter Unit	£7.45	P & P 15p
180 Tuner	£8.95	P & P 15p
Stereo Decoder	£13.95	P & P 15p
P25 Power Supply	£5.95	P & P 15p
P26 Power Supply	£8.95	P & P 15p
P27 Power Supply	£8.95	P & P 15p
Transformer for P28	£4.95	P & P 15p
IC20 Stereo Amp kit	£7.95	P & P 15p
IC22 Power Supply kit	£5.95	P & P 15p

SINCLAIR Project 80 Packages

24240 Stereo 80 P25	£28.60	P & P 15p
24240 Stereo 80 P26	£31.30	P & P 15p
24260 Stereo 80 P28	£35.55	P & P 15p

TE1021 Stereo Listening Station

For balancing and pairing of loudspeakers with additional facility for stereo head-phones. Switching. Two gain controls, speakers on-off slide switch, stereo headphones socket.

OUR PRICE £2.25 P & P 15p

AUDIOTRONIC LOW NOISE CASSETTES

TYPE	5	10	25
C60	£1.57	£2.00	£7.08
C90	£2.24	£4.25	£15.00
C120	£3.72	£5.17	£18.24

P & P 3p each 10 and over Post Free

MP7 MIXER-PREAMPLIFIER

5 Microphone inputs each with individual gain controls enabling complete mixing facilities. Battery operated. Size: 235 x 127 x 76mm. Inputs: Mics. 3 x 3mV 50k; 7 x 3mV 400 ohms. Phono, Mho, 4mV 50k; Phono Ceramic 100mV 100k. Output 250mV 100k.

OUR PRICE £8.97 P & P 20p

AUDIOTRONIC AHA101 Stereo Headphone Amplifier

All silicon transistor amplifier operates from magnetic ceramic or tuner inputs with twin stereo headphones outputs and separate volume control for each channel. Operates from 9V battery. INPUTS: 5mV and 100mV. OUTPUT: 50mV per channel.

OUR PRICE £8.50 P & P 30p

JOYSTICK HIGH QUALITY CONSTRUCTION KITS

WE ARE APPOINTED STOCKISTS AT Oxford Street, 42 & 257 Tottenham Court Road, 34 Lisle Street, 152, Fleet Street, 311 Edwidge Road, CROYDON BIRMINGHAM KINGSTON LEICESTER NORTHAMPTON SOUTHEND TUNBRIDGE WELLS WOLVERHAMPTON branches, or by Mail Order.

All kits are complete with complete instructions and covered by full guarantee.

Post and Packing 75p per kit.

AF20 Alarm amplifier	£5.81
AF25 Alarm amplifier	£3.29
AF30 Alarm pre-amplifier	£3.20
AF35 Pre-amp amplifier	£2.42
AF30 0.5V mc. amplifier	£4.88
MP55 500Hz oscillator	£7.62
AF305 Intermix	£2.55
AF310 2 Input Amplifier	£2.55
M160 Multi vibrator	£2.18
M102 Transistor tester	£8.11
M181 VU Meter	£5.41
M191 200Hz audio meter	£5.23
LF380 Quadraphone driver	£ 6.42
AT5 Automatic light control	£ 3.78
AT30 Photo cell switch unit	£ 6.68
AT50 400VAC true light intensity sensor	£ 5.18
AT56 2 200VAC track light dimmer speed control	£ 6.75
AT60 1 channel light control	£ 10.82
AT65 2 channel light control	£ 16.32
GU320 2 tone auto tuner	£ 8.14
HFG1 Diode detector	£ 3.81
HFG5 FM transmitter	£ 5.21
HFG75 FM receiver	£ 13.96
HF310 FM stereo receiver	£ 18.24
HF325 Deluxe FM receiver	£ 26.51
HF330 Decoder HF310/325	£ 10.45
GP10 Stereo pre-amplifier for use with 2 x AF310	£ 27.98
GP12 Circuit board	£ 30.20
GP304 Circuit board	£ 21.33
HF380 1ch. ch. audio amplifier	£ 6.02
HF395 broadband audio amp	£ 2.19
NT10 Substantal power supply 1000VA, 9V	£ 16.22
NT300 Substantal p. supply 1.13.19	£ 13.19
NT310 Power Supply 740V AC on 2-18V DC at 2amps	£ 5.84
NT305 Voltage converter 15V AC to 5V DC with output 240V AC and 5-15V DC, 500mA.	£ 12.06

Amateur Electronics by JOY KIT. A comprehensive book for the amateur covers the subject from basic principles to advanced electronic technique. Complete with circuit board for AE1 to AE10 listed below.

OUR PRICE £3.30 (incl. VAT) P & P 20p plus VAT

AE1 100mW output stage	£ 1.55
AE2 PE amplifier	£ 1.32
AE3 Diode rectifier	£ 2.06
AE4 Flasher	£ 1.26
AE5 Variable multi vibrator	£ 1.14
AE6 Transistor multi vibrator	£ 1.11
AE7 RC generator	£ 1.08
AE8 Bass filter	£ 1.95
AE9 Treble filter	£ 1.95
AE10 CCR filter	£ 1.05

Also see previous page

ALL PRICES EXCLUDE VAT

SEW PANEL METERS

SEW PANEL METERS ARE STOCKED AT OUR 3 LITTLE ST., 311 EDGWARE RD. & 152 FLEET ST., BARNHURST or order by post.

USED EXTENSIVELY BY INDUSTRY, GOVERNMENT DEPARTMENTS, EDUCATIONAL AUTHORITIES ETC.
Over 200 ranges in stock—other ranges to order. Quantity discounts available. Send for fully illustrated brochure.

CLEAR PLASTIC MODEL SD640

Size: 85 x 84mm

50uA	£3.90
100uA	£3.95
200uA	£3.90
500uA	£3.75
50-0-500uA	£3.85
100-0-1000uA	£3.80
1mA	£3.75
5mA	£3.75
10mA	£3.75
50mA	£3.75
100mA	£3.75
500mA	£3.75
1A DC	£3.75
5A DC	£3.75
15V AC	£3.85
300V AC	£3.85
15V DC	£3.75
300V DC	£3.85



*Items with asterisk are Moving Iron type, all others are Moving Coil

CLEAR PLASTIC MODEL SD830	
Size: 110 x 80mm	
50uA	£4.40
100uA	£4.36
200uA	£4.30
500uA	£4.25
50-0-500uA	£4.35
100-0-1000uA	£4.30
1mA	£4.20
5mA	£4.20
10mA	£4.20
50mA	£4.20
100mA	£4.20
500mA	£4.20
1A DC	£4.20
5A DC	£4.20
15V AC	£4.30
300V AC	£4.30
15V DC	£4.20
300V DC	£4.30



CLEAR PLASTIC MODEL MR 65P

Size: 86 x 78mm

50uA	£4.05
100uA	£3.95
200uA	£3.90
500uA	£3.85
50-0-500uA	£3.95
100-0-1000uA	£3.90
500-0-5000uA	£3.80
1mA	£3.80
5mA	£3.80
10mA	£3.80
50mA	£3.80
100mA	£3.80
500mA	£3.80
1A DC	£3.80
5A DC	£3.80
10A DC	£3.80
15A DC	£3.80
30A DC	£3.80
50A DC	£3.80
5V DC	£3.80
15V DC	£3.80
20V DC	£3.80
25V DC	£3.80
30V DC	£3.80
35V DC	£3.80
40V DC	£3.80
45V DC	£3.80
50V DC	£3.80
55V DC	£3.80
60V DC	£3.80
65V DC	£3.80
70V DC	£3.80
75V DC	£3.80
80V DC	£3.80
85V DC	£3.80
90V DC	£3.80
95V DC	£3.80
100V DC	£3.80



CLEAR PLASTIC MODEL SW100

Size: 100 x 80mm

50uA	£4.70
100uA	£4.60
200uA	£4.50
500uA	£4.40
50-0-500uA	£4.60
100-0-1000uA	£4.55
1mA	£4.40
5mA	£4.40
10mA	£4.40
50mA	£4.40
100mA	£4.40
500mA	£4.40
1A DC	£4.40
5A DC	£4.40
15V AC	£4.55
300V AC	£4.55
15V DC	£4.40
300V DC	£4.50



CLEAR PLASTIC MODEL MR 46P

Size: 50 x 50mm

50uA	£3.30
100uA	£3.25
200uA	£3.20
500uA	£3.10
50-0-500uA	£3.25
100-0-1000uA	£3.20
500-0-5000uA	£3.05
1mA	£3.05
5mA	£3.05
10mA	£3.05
50mA	£3.05
100mA	£3.05
500mA	£3.05
1A DC	£3.05
5A DC	£3.05
10A DC	£3.05
15A DC	£3.05
20A DC	£3.05
25A DC	£3.05
30A DC	£3.05
35A DC	£3.05
40A DC	£3.05
45A DC	£3.05
50A DC	£3.05
55A DC	£3.05
60A DC	£3.05
65A DC	£3.05
70A DC	£3.05
75A DC	£3.05
80A DC	£3.05
85A DC	£3.05
90A DC	£3.05
95A DC	£3.05
100A DC	£3.05



BAKELITE MODEL S80 Enlarged Window

Size: 80 x 80mm

50uA	£4.60
100uA	£4.55
200uA	£4.50
500uA	£4.45
50-0-500uA	£4.55
100-0-1000uA	£4.50
1mA	£4.30
5mA	£4.30
10mA	£4.30
50mA	£4.30
100mA	£4.30
500mA	£4.30
1A DC	£4.30
5A DC	£4.30
10A DC	£4.30
15A DC	£4.30
20A DC	£4.30
25A DC	£4.30
30A DC	£4.30
35A DC	£4.30
40A DC	£4.30
45A DC	£4.30
50A DC	£4.30
55A DC	£4.30
60A DC	£4.30
65A DC	£4.30
70A DC	£4.30
75A DC	£4.30
80A DC	£4.30
85A DC	£4.30
90A DC	£4.30
95A DC	£4.30
100A DC	£4.30



EDGWISE MODEL PE70

Size: 90 x 34mm

50uA	£4.25
100uA	£4.20
200uA	£4.15
500uA	£4.00
50-0-500uA	£4.20
100-0-1000uA	£4.15
1mA	£3.95
5mA	£3.95
10mA	£3.95
50mA	£3.95
100mA	£3.95
500mA	£3.95
1A DC	£3.95
5A DC	£3.95
15V AC	£4.15
300V AC	£4.15
15V DC	£3.95
300V DC	£4.00



CLEAR PLASTIC MODEL MR 38P

Size: 42 x 42mm

50uA	£3.20
100uA	£3.15
200uA	£3.10
500uA	£3.00
50-0-500uA	£3.15
100-0-1000uA	£3.10
500-0-5000uA	£2.85
1mA	£2.85
5mA	£2.85
10mA	£2.85
50mA	£2.85
100mA	£2.85
500mA	£2.85
1A DC	£2.85
5A DC	£2.85
10A DC	£2.85
15A DC	£2.85
20A DC	£2.85
25A DC	£2.85
30A DC	£2.85
35A DC	£2.85
40A DC	£2.85
45A DC	£2.85
50A DC	£2.85
55A DC	£2.85
60A DC	£2.85
65A DC	£2.85
70A DC	£2.85
75A DC	£2.85
80A DC	£2.85
85A DC	£2.85
90A DC	£2.85
95A DC	£2.85
100A DC	£2.85



CLEAR PLASTIC MODEL MR 52P

Size: 60 x 60mm

50uA	£3.80
100uA	£3.75
200uA	£3.70
500uA	£3.65
50-0-500uA	£3.75
100-0-1000uA	£3.70
1mA	£3.50
5mA	£3.50
10mA	£3.50
50mA	£3.50
100mA	£3.50
500mA	£3.50
1A DC	£3.50
5A DC	£3.50
10A DC	£3.50
15A DC	£3.50
20A DC	£3.50
25A DC	£3.50
30A DC	£3.50
35A DC	£3.50
40A DC	£3.50
45A DC	£3.50
50A DC	£3.50
55A DC	£3.50
60A DC	£3.50
65A DC	£3.50
70A DC	£3.50
75A DC	£3.50
80A DC	£3.50
85A DC	£3.50
90A DC	£3.50
95A DC	£3.50
100A DC	£3.50



MODEL ED107 EDUCATIONAL METER

Size: 900 x 80 x 160mm including terminals

A range of high quality moving coil instruments ideal for school experiments and other bench applications. 2" full scale. The meter movement is easily accessible to demonstrate internal working.



CLEAR PLASTIC MODEL MR 85P

Size: 120 x 110mm

50uA	£5.80
100uA	£5.55
200uA	£5.50
500uA	£5.45
50-0-500uA	£5.55
100-0-1000uA	£5.50
500-0-5000uA	£5.35
1mA	£5.15
5mA	£5.15
10mA	£5.15
50mA	£5.15
100mA	£5.15
500mA	£5.15
1A DC	£5.15
5A DC	£5.15
10A DC	£5.15
15A DC	£5.15
20A DC	£5.15
25A DC	£5.15
30A DC	£5.15
35A DC	£5.15
40A DC	£5.15
45A DC	£5.15
50A DC	£5.15
55A DC	£5.15
60A DC	£5.15
65A DC	£5.15
70A DC	£5.15
75A DC	£5.15
80A DC	£5.15
85A DC	£5.15
90A DC	£5.15
95A DC	£5.15
100A DC	£5.15



CLEAR PLASTIC MODEL SD450

Size: 59 x 46mm

50uA	£3.60
100uA	£3.55
200uA	£3.50
500uA	£3.45
50-0-500uA	£3.55
100-0-1000uA	£3.50
1mA	£3.40
5mA	£3.40
10mA	£3.40
50mA	£3.40
100mA	£3.40
500mA	£3.40
1A DC	£3.40
5A DC	£3.40
10A DC	£3.40
15A DC	£3.40
20A DC	£3.40
25A DC	£3.40
30A DC	£3.40
35A DC	£3.40
40A DC	£3.40
45A DC	£3.40
50A DC	£3.40
55A DC	£3.40
60A DC	£3.40
65A DC	£3.40
70A DC	£3.40
75A DC	£3.40
80A DC	£3.40
85A DC	£3.40
90A DC	£3.40
95A DC	£3.40
100A DC	£3.40



BAKELITE MODEL MR 65

Size: 80 x 80mm

25uA	£5.40
50uA	£4.10
100uA	£4.05
500uA	£3.75
50-0-500uA	£4.05
100-0-1000uA	£4.00
500-0-5000uA	£3.70
1mA	£3.70
5mA	£3.70
10mA	£3.70
50mA	£3.70
100mA	£3.70
500mA	£3.70
1A DC	£3.70
5A DC	£3.70
10A DC	£3.70
15A DC	£3.70
20A DC	£3.70
25A DC	£3.70
30A DC	£3.70
35A DC	£3.70
40A DC	£3.70
45A DC	£3.70
50A DC	£3.70
55A DC	£3.70
60A DC	£3.70
65A DC	£3.70
70A DC	£3.70
75A DC	£3.70
80A DC	£3.70
85A DC	£3.70
90A DC	£3.70
95A DC	£3.70
100A DC	£3.70



240° Wide Angle

1mA METERS
MW1 - 6.60 x 60 mm
£6.50 P & P 15p
MW1 - 8.80 x 80mm
£8.90 P&P 15p.



YAMABISHI VARIABLE VOLTAGE TRANSFORMERS

Excellent quality at low cost. Input: 230V 50/60Hz. Output 0-260V.
MODEL S208 BENCH MOUNTING
P&P

1A	£10.50	50p
2.5A	£12.00	50p
5A	£17.50	50p
7.5A	£20.35	£1.00
10A	£23.75	£1.00
12A	£26.40	£1.00
20A	£35.00	£1.50
25A	£39.00	£1.50
40A	£72.00	£1.50

MODEL S208B PANEL MOUNTING
2.5A £12.00 50p



ALL PRICES EXCLUDE VAT

POSTAGE & PACKING 15p



FOR MAIL ORDER
We offer a speedy and efficient service by mail order. Remember to add 8% VAT to total value of goods including post and packing.

TO LASKYS CUSTOMER SERVICES DIVISION
Audiotronic House, The Hyde, London NW9 6JJ. Tel: 01-200 1321

Please send me the following items

TOTAL PURCHASE PRICE (inc P&P and VAT)

I enclose cheque postal order money order

I wish to pay by Barclaycard/Access and my number is

NAME
ADDRESS
Signature

32 Page
MI-FI

"VFA 5ft below ground, same as dipole. Elevated 15ft., 1 'S' point UP on dipole"—comparison report by WTOE, retd, U.S.A. Gov't, Electronics Engr.

ABOVE ALL

its the antenna system that counts!—However good your S.W. receiver and transmitter, if a PARTRIDGE SYSTEM cannot improve your signals, with the V.F.A. at same height, return the equipment (in re-saleable condition) for a cash refund!

PARTRIDGE have a complete V.F.A. SYSTEM correctly terminated for your equipment, ranging from modern communications gear to the most modest receiver, even small transistor radios. Don't be satisfied with anything but the patented and trade marks protected PARTRIDGE WORLD RECORD antenna system. **SELECT YOUR SYSTEM**— (Each System consists of the gold stove enamelled 7' 6" V.F.A. and matching finish JOYMATCH A.T.U.—despatched direct by parcel post—our risk)—

SYSTEM 'A' for Modern Communications Receivers	£29.58
SYSTEM 'D' for other S.W. and M.W. receivers, all types	£20.84
SYSTEM 'J' for transmitters, up to 500W PEP, 160 thru 10m	£33.59
JOYMATCH A.T.U. KIT (1-6MHz—32mHz)	£6.24
JOYMATCH A.T.U. KIT (500kHz—32mHz)	£6.24
Either KIT completely assembled ready for use	£7.55
JOYMATCH AERIAL BANDSWITCH" tuned Aerial, M.W. & S.W.	£8.24
SUPER SENSITIVE GEN. COVERAGE MED. & S.W. CRYSTAL SET ready to use, with aerial and earpiece	£3.92
HEADPHONES, communications, 8 ohms	£3.39
V.F.A. Stack Lashing (Supports VFA on Chimney Stack)	£2.51
V.F.A. Wall Bracket (Heavy duty)	£2.51
JOYMATCH Artificial Earth (Ground) Switch tuned	£6.24
A.G.T.U. Artificial Earth D.I.Y. add on unit for your A.T.U.	£0.60
Radials for A.G.T.U. cut to required band, each	£0.60
"Invisible Aerial" wire, tough PVC covered 22 swg, per 10 metres	£0.60
A.G.T.U. supplied fitted to existing JOYMATCH ATU's (radials extra)	£0.80
Coax. cable, receiving type 75 ohms, per 10 metres	£0.88
Aerial Wire 16 swg high qual. enam. ALUMINIUM, per 10 metres	£0.59
VALVES, Complete set for 9R59DS & 9R59DE, incl. O.A.2	£4.75

SEND STAMP FOR DETAILS



Phone 0843 62535

or 62839

(after office hours)

G3CED G3VFA



THIS CHRISTMAS

have a TV Tennis game exactly like the pub. Plug into your own TV aerial socket. Special features inc. score shown on screen, sound when ball hits bat etc.

Ball serves and speeds up automatically, bats will deflect the ball in five different directions, picture fully interlaced. Absolute game of skill for all the family, the TV game you'll never get tired of. This is the ultimate in TV games.

No other company can offer so many features, complete in Cabinet, tested and ready for use, normal price £199.00, special Christmas price £120.00. For the do-it-yourself enthusiasts logic card with vision modulator and sound amplifier assembled and tested £85.00 in Kit form. Logic card with Modulator printed circuit board and Instructions £14.50. All prices inclusive of VAT and delivery.

Send cheques and postal orders to Logic Leisure Ltd., Kingfisher House, 65 Park Road, New Barnet, Herts. Tel: 01-440 9173/4

Please send s.a.e. for further details. Callers welcome for demonstration. Trade enquiries welcome. Export can be arranged.

TECHNOMATIC LTD. 54 SANDHURST ROAD, LONDON NW9

AC196 11p	BFY62 15p	Rectifiers	BRIDGE RECTIFIERS
AC127 11p	MPF103 81p	1N4001 5p	50v 100v 400v 600v
AC128 11p	MPF104 81p	1N4004 8p	1A 2A 3A 4A 5A 6A
AC176 11p	MPF105 81p	1N4007 7p	30p 85p 45p 75p
AC187 12p	OC26 47p	BYV127 13p	4A 48p 48p 60p 70p
AC188 11p	OC28 85p	Signal Diodes	— 85p 75p 100p
AD140 48p	OC35 48p	1N914 4p	
AD181 38p	OC44 11p	1N4148 4p	50v 100v 400v 600v
AD182 38p	OC71 11p	0A93 6p	1A 48p 48p 60p 75p
AF115 18p	TIP2865 70p	0A90 6p	3A 48p 48p 75p 85p
AF117 18p	T1843 28p	0A92 6p	7A — 80p 85p 114p
BC107 5p	2N708 18p	0A95 6p	16A — 75p 95p 180p
BC108 8p	2N930 18p	Zeners	
BC109 10p	2N9646 32p	400MW 5p	
BC189 11p	2N4905 18p	1-5W 18p	
BC182 10p	2N395 8p	1-5W 85p	
BC189 10p	2N3093 18p	Other Diodes Tun'g	3A — 85p 95p 180p
BC184 11p	2N3050 40p	AEY11 60p	8A — 85p 120p 180p
BC212 11p	2N3702 11p	LED	10A — 100p 144p 165p
BC213 10p	2N3703 11p	TTL209 18p	14A — 145p 180p 205p
BC214 15p	2N3704 11p		
BD181 40p	2N3705 10p		
BD192 48p	2N3706 10p		
BFY50 13p	2N3707 11p		
BFY51 18p	2N3819 25p		

LINEAR ICs	TTL SERIES	MOSFETS
855 50p 535 21-59	7400 14p 7448 90p	2N140 85p
858 125p 8038 20-00	7401 15p 7478 80p	2N141 90p
887 80p CA3048 56p	7402 18p 7474 84p	40608 58p
708 25p MC1310 22-80	7404 18p 7475 88p	
723 85p MC1312 22-80	7405 20p 7476 92p	
741 25p MFC4000 40p	7410 15p 7480 84p	
747 70p TBA800 21-00	7413 30p 7480 48p	
748 38p TBA810 21-25	7420 15p 7493 46p	
7805 21-40 TBA820 80p	7430 15p 74107 46p	
7812 21-40 2N414 21-10	7441 75p 74121 84p	
7812 21-40 2N414 21-10	7447 95p 74141 84p	
Data sheet on above ICs 10p ea.		

FOR MORE SELECTION PLEASE REFER TO OUR ADVERTISEMENT IN P.E. & W.W.


Complete Semiconductor Kits (inc. DIL Sockets) for various projects available e.g.	SPECIAL PRICES
Tele-tennis	555 50p
Tri-colour Unit	723 55p
PE Minisonic Miniature battery-operated Sound Synthesiser	741 25p
Rhythm Generator	CA3046 55p
Novel Transistor Tester	MC1310P 2-40
Please send S.A.E. for prices.	MC1312P 2-20

Minimum Order £2. All prices exclusive of VAT. P. & P. 10p orders below £5. Trade, Colleges enquiries welcome.




I.L.P. (Electronics) Ltd

SHEER SIMPLICITY!

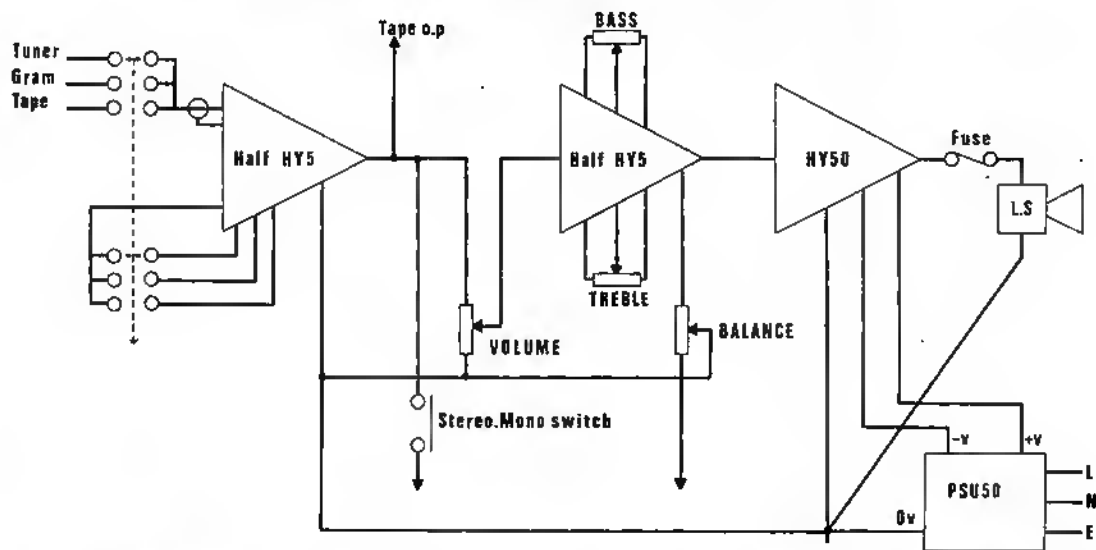

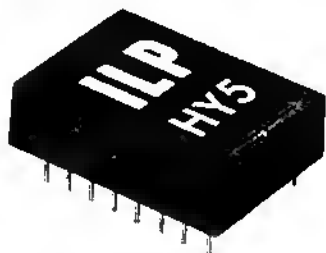MONO ELECTRICAL CIRCUIT DIAGRAM WITH INTERCONNECTIONS FOR STEREO SHOWN



The HYS is a complete mono hybrid preamplifier, ideally suited for both mono and stereo applications. Internally the device consists of two high quality amplifiers—the first contains frequency equalisation and gain correction, while the second caters for tone control and balance.

TECHNICAL SPECIFICATION

Inputs: Magnetic Pick-up 3mV RIAA; Ceramic Pick-up 30mV; Microphone 10mV; Tuner 100mV; Auxiliary 3-100mV; Input Impedance 47k Ω at 1kHz. Outputs: Tape 100mV; Main output 0db (0-775V RMS). Active Tone Controls: Treble \pm 12db at 10kHz; Bass \pm 12db at 100Hz. Distortion: 0-5% at 1kHz. Signal/Noise Ratio: 66db. Overload Capability: 40db on most sensitive input. Supply Voltage: \pm 18-25V.

PRICE £4.50 + 36p VAT
P. & P. free




The HY50 is a complete solid state hybrid HI-FI amplifier incorporating its own high conductivity heatsink hermetically sealed in black epoxy resin. Only five connections are provided, input, output, power lines and earth.

TECHNICAL SPECIFICATION

Output Power: 25W RMS into 8 Ω . Load Impedance: 4-16 Ω . Input Sensitivity 0db (0-775V RMS). Input Impedance: 47k Ω . Distortion: Less than 0.1% at 25W typically 0-05%. Signal/Noise Ratio: Better than 75db. Frequency Response: 10Hz-50kHz \pm 3db. Supply Voltage: \pm 25V. Size: 105 x 50 x 25mm.

PRICE £5.98 + 48p VAT
P. & P. free

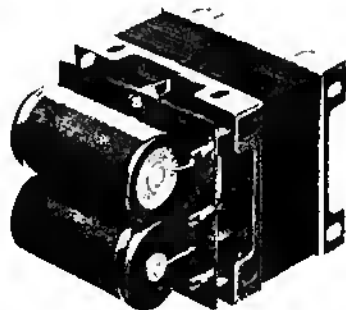

The PSU50 incorporates a specially designed transformer and can be used for either mono or stereo systems.

TECHNICAL SPECIFICATIONS

Output voltage: 50V (25-0-25V). Input Voltage: 210-240V. Size: L.70. D.90. H.60mm.

PRICE £6 + 48p VAT
P. & P. free

TWO YEARS' GUARANTEE ON ALL OUR PRODUCTS

I.L.P. Electronics Ltd.
Crossland House,
Nackington, Canterbury
Kent CT4 7AD
Tel (0227) 63218

Please supply, Total Purchase price
I Enclose, Cheque Postal Orders Money Order
Please debit my Access account Barclaycard account
Account number
Name & Address
Signature

TRANSFORMERS

POWER UNIT Type A125

Supplying 6 or 9 Volt DC at 200 mA.
In moulded case forming a 2 pin 5A mains plug.
2 metre output lead with 4-way multipole giving 2-1 and 2-5 ma sockets and 3-5 ma plug.
Price £2-25, Post 10p.



2" and 4" PANEL METERS

2"

4"

4mm Dia. Movement	I.H. Ohms	4mm Dia. Movement	I.H. Ohms
0-50 micro A.	1250	0-50 micro A.	1400
0-100 micro A.	680	0-100 micro A.	730
0-500 micro A.	170	0-500 micro A.	200
0-1 mA	170	0-1 mA	200
0-5 mA	170	0-5 mA	200
0-10 mA	8	0-10 mA	8
0-50 mA	0.5	0-50 mA	0.5
0-100 mA	0.5	0-100 mA	0.5
0-500 mA	0.5	0-500 mA	0.5
0-1 AMP	0.5	0-1 AMP	0.5
0-2 AMP	0.5	0-2 AMP	0.5
0-25 Volt	13K	0-25 Volt	13K
0-50 Volt	50K	0-50 Volt	50K
0-200 Volt	300K	0-200 Volt	300K
"m" Meter	170	"m" Meter	200
V/I Meter	3260	V/I Meter	3260

VU Meters are complete with detectors. Modern wide view.
Price 2" £2-15 Post 10p. Price 4" £2-15 Post 10p. Lamps 75p per set.

1/2 watt CARBON FILM RESISTORS

1/2 watt at 70°C E 12 range 10Ω-13M 5% (tol above 470 KΩ 10%). (tol at 95p per 100).

C1000 MULTIMETER

Special Offer

Compact General Purpose Mini Multimeter. Input Resistance 1000 ohms per volt



AC Volts	0-15, 50, 250, 1000 V
DC Volts	0-10, 50, 250, 1000 V
DC Current	0-5 mA
Resistance	0-100MΩ
Resistance	0-100KΩ ohm
Size	90 x 24 x 30 mm
Complete with Batteries, Test Prods.	
Instructions, Special price	£3-20 Post 20p.

C1001 MULTIMETER

Input Resistance 20,000 ohms per volt Overload protection 150 mA movement, clear scale Ranges—AC Volts 0-10, 50, 250, 1000V DC Volts 0-5, 25, 125, 500, 2500V DC Current 0-50 mA Resistance 0-60 Kohms, 0-4 Mohms Decibels -20 to +22 dB. Carrying Case, Test Prods. and Batteries included. Size: 11.5 x 8.3 x 2.7 cm. Price £3-85, Post 20p.

CASED TRANSFORMERS

Housed in smart resin-coated steel cases, with 3-core power cable and outlet socket, fused primary winding. Isolation types are fitted with 3-pin outlet sockets, and are available with 110 volt or 240 volt output. (Please state). Auto types are fitted with 2-pin flat style sockets up to 500 V.A. 3-pin sockets from 750 to 3000 V.A. See Auto and Isolation sections for prices.

SAFETY ISOLATING

Prim. 220-240V. Sec. 120-240V. Centre Tap with Screen.

V.A.	Ref. No.	Price £	Price Cancel £	Price 2 Pin Earth £	Price Open £	Post £
60	140	7-35	0-80	4-00	0-38	
100	150	8-22	0-80	4-80	0-32	
200	151	10-20	0-80	7-40	0-52	
250	152	11-58	0-80	8-88	0-55	
350	153	14-10	0-80	10-60	0-59	
600	154	15-63	0-80	12-38	1-00	
750	155	24-03	1-00	18-78	1-20	
1000	156	32-19	1-00	26-60	1-20	
1500	157	38-13	1-00	30-24	O.A.	
2000	158	45-25	1-00	34-68	O.A.	
3000	159	58-50	2-40	49-38	O.A.	

12 & 24 Volts Prim. 200-240V.

Atch.	No.	Ref. No.	Price £	Post £
0-3	12V	24V		
0-3	0-15	24V	1-84	0-29
0-6	0-25	11V	1-48	0-23
1	0-5	21V	1-58	0-23
2	1	7V	2-08	0-22
3	2	15	2-58	0-28
4	3	7V	3-50	0-42
5	4	10V	2-52	0-22
10	5	7V	4-80	0-53
12	6	11V	5-01	0-52
16	8	17	6-22	0-62
20	10	11V	9-47	0-69
30	15	18V	11-95	0-97
40	20	22V	13-28	1-00
50	30	22V	16-30	1-10

30 Volts

Prim. 200-240V. Sec. 12, 15, 20, 24, 30V.

Amps	Ref. No.	Price £	Post £
0.5	112	1-72	0-22
1	79	2-21	0-26
2	3	3-28	0-36
3	20	4-10	0-42
4	21	4-88	0-52
5	41	4-80	0-52
6	117	6-50	0-62
8	86	8-50	0-67
10	89	9-97	0-67

AUTO TRANSFORMERS

V.A.	Ref. No.	Price Cased £	Price Plug £	Price Open £	Post £
Tapped at 115, 220, 240 Volts					
20	113	3-00	0-15	1-55	0-30
Tapped at 115, 220, 230, 240 Volts					
100	4	5-80	0-15	3-98	0-39
200	65	6-40	0-15	4-60	0-40
300	66	7-27	0-15	5-28	0-52
300	67	9-90	0-15	8-28	0-57
750	81	12-58	0-75	9-78	0-82
1000	84	15-70	0-75	12-40	0-82
1500	93	18-88	0-75	16-38	1-50
2000	95	30-10	1-44	22-05	1-50
3000	73	42-58	1-90	32-00	1-90

50 Volts

Prim. 200-240V. Sec. 10, 25, 30, 40, 50V.

Amps	Ref. No.	Price £	Post £
0.5	102	2-33	0-30
1	103	3-00	0-28
2	104	4-57	0-42
3	105	5-20	0-52
4	106	6-89	0-52
6	107	11-17	0-67
8	118	14-19	0-97
10	119	16-47	0-97

60 Volts

Prim. 230-240V. Sec. 24, 30, 40, 43, 60V.

Amps	Ref. No.	Price £	Post £
0.5	124	2-98	0-28
1	125	2-98	0-28
2	127	4-63	0-42
3	123	6-84	0-52
4	128	7-94	0-67
6	44	8-86	0-67
8	129	10-15	0-89
10	131	13-58	1-00
12	132	16-15	1-00
12	180	16-00	1-10

MINIATURE AND EQUIPMENT

Prim. 240V with screen.

Sec. 1	Volts	Sec. 2	Milliamps	Ref. No.	Price £	Post £
2-0-5		200		258	1-23	0-10
0-6	0-6	500	330	264	1-30	0-10
0-6	0-6	1000	1000	212	1-38	0-22
0-0-5		100		13	1-23	0-10
0-0	0-0	330	330	253	1-43	0-10
0-0-5	0-0-5	500	500	207	1-75	0-22
0-0-10	0-0-10	1000	1000	206	2-20	0-36
0-15	0-15	200	200	298	1-24	0-10
20-0-20		30		341	1-28	0-10
0-20	0-20	150	150	237	1-80	0-20
0-15-20	0-15-20	500	500	205	2-47	0-38
0-2R	0-2R	300	300	314	1-72	0-22
0-0-0		3500	NO SCREEN	1117	3-00	0-40
20-12-0 12 20	0-15-20	700 (10V)		291	2-31	0-30
0-15-20	0-15-20	1000	1000	290	2-31	0-30
0-15-27	0-15-27	500	500	203	2-73	0-38
0-15-27	0-15-27	1000	1000	204	3-62	0-38

PLASTIC CASED SILICON BRIDGE RECTIFIERS

One Amp	Two Amp	Four Amp	Six Amp
30 P.I.V. 25p	50 P.I.V. 35p	100 P.I.V. 55p	50 P.I.V. 65p
100 P.I.V. 25p	100 P.I.V. 45p	200 P.I.V. 55p	100 P.I.V. 70p
200 P.I.V. 25p	200 P.I.V. 45p	400 P.I.V. 55p	200 P.I.V. 80p.
400 P.I.V. 30p	400 P.I.V. 50p	600 P.I.V. 75p	400 P.I.V. 90p.

ADD 10p P & P PER ORDER!

PLEASE

ADD 8% FOR VAT

POWER UNIT Type CC 12-05

Output switched 3, 4.5, 6, 7.5 and 12 volts at 500 mA D.C. Operates from 240 V mains. Suitable for: Radios, Tape Recorders, Record Players etc. Size 7.5 x 5.0 x 14.0cm. Price £3-85, Post 20p.



MINIATURE NEONS

5mm dia., 12mm length leads length approx. 20mm. Recommended ballast resistor 250K ohms for 240 Volt operation Price: Packet of 10 for 60p. Postage 10p.

A.S.P. LTD.

DEPT PW2, SIMMONDS ROAD, WINCHEAP, CANTERBURY, KENT. Tel: (0227) 52436

MASSIVE CLEARANCE BARGAINS

Bargain component parcels contain Resistors, Capacitors, Potentiometers, Knobs, Rotary and Slide Switches, JPs, Tag Strips, Drive Drums, Coil Formers, Wire, Grommets, Relays, Pulley Wheels, Magnets, Transistor Panels, etc. Save yourself £'s on these well selected parcels, 6lb net weight £1-00, p.p. 50p.

Brand New Wire-wound Resistors 1-7 watts, mostly Plessey GWS-1-3-5-7. Good selection. 100 for £1-00, p.p. 20p.

Mullard Ferrite Cores LA3 50p, LA4 75p, LA2100 50p.

SPECIAL OFFER. Metallized Polyester Capacitors by Eric, Mullard, etc. Values include .01/160V, .01/250V, .015/160V, .022/160, .033/160, .047/160V, .068/160V, .1/160-250V, .22/160V, etc. This is a bargain not to be missed. 100 for £1-50, p.p. 20p.

Assorted Capacitors, Silver Mica, Tubular and Disc Ceramics, Polystyrene, Tremendously good selection. 300 for £1, p.p. 20p.

Please add 8% V.A.T.

Mail Order Only.

XEROZA RADIO,
1, EAST STREET, BISHOPS TAWTON, DEVON.

FELSTEAD ELECTRONICS (PW88), LONGLEY LANE, GATLEY, CHEADLE, CHESHIRE SK8 4EE

STYLIS. Replacements for virtually all ACOS, BSE, COLLARD, GARRARD, PHILIPS, RONETTE, SONOTONE. Single Tip: Sapphire 10p, Double Tip: Can be Stereo/LP+75 or ST/LP Sapphire 87p, Double Tip: Diamond ST/LP+Sapphire 78 55p. Diamond ST/LP+Diamond STYLIF £1.25. For GOLDRING Diamond GB90, G300H and GB30 at £2.10 each. GB00E at £4.10. Charges 10p any quantity. FULL DETAILS STYLIS AND CARTRIDGE EQUIVALENTS INCLUDING SHURE, PICKERING, AUDIO-TECH, B & O, AND MANY MORE STYLIS FOR MAGNETO AND CRYSTAL PICK-UPS.

CARTRIDGES. All with stylis and fittings. Replacements for ACOS GP/91 6C (Stereo-mono compatible series) at £1.20, GP93 Stereo at £1.60, GP94 Stereo Ceramic at £2.80. Actual GP67-2, Front switch at £1.10, for BSR 23H, X5H and X6M at £1.50 each. SK53H and SK53L at £1.80 each. TCSH at £1.80, TCS Stereo, 3 pins £2.80; charges 10p any quantity.

RECORDING TAPE. ALL FINEST BRITISH MYLAR 5" 600ft. 40p; 5" 900ft. 60p; 6" 1200ft. 84p. 7" 1800ft. £1.10. Charges for 5" and 6" 1-4 13p each. 5 and over, 23p the c. Charges for 7", 1-3 13p each, 4-5 35p the lot, 6 and over 40p the lot.

SPEAKERS 2", 3, 8 or 84 ohms (state which) 55p. Charges 10p each.

CONNECTING WIRE. Pkts of 5 coils, asstd. coils each 5yds. Solid core 10p Flexible 12p (Charges 10p per pack).

BARRIAGES. Magnetic 2.5mm or 3.0mm plus (state which) 15p. CRYSTAL (3.6mm only) 35p (all 10p up to 6).

VIBRATORS. 7 pin SYNCL (12BR7 type) 75p. 4-pin NON-synch (121HD4) 45p (all 10p each).
Send SAE for free stylis, cartridge, accessories and components list. All prices include V.A.T.

NEW MULLARD & MAZDA VALVES

All individually boxed and guaranteed. Full trade discounts to bona fide companies. Price and availability lists on application.

EXPRESS POSTAGE

5p for 1 Valve. Each additional Valve add 2p.

DM70	0-61	ECL83	0-86	GY501	1-18	PL53	0-48	30C1/PCF80	
DY51	0-80	ECL88	0-84	K284	0-80	PL83	0-04	BZ84	0-54
DY86/7	0-41	EF80	0-42	PC86	0-95	PL84	0-69	30C15/	
DY80/2	0-48	FF83	0-88	FCR8	0-85	PL85	0-88	PCF800	1-01
EABCB80	1-04	EF85	0-82	PC884	0-84	PL86	0-84	30C17	1-00
EB01	0-84	EF88	1-16	PC885	0-80	PL87	0-84	30C18/	1-01
EB051	0-78	EF89	1-14	PC888	0-88	PL88	0-80	PCF865	1-01
EBF80	0-66	BF91	1-00	PC889	0-84	PY33	0-65	30F6/PCF818	1-03
EBF83	0-60	FF92	1-27	PCF89	0-80	PC81/800	0-49	30FL1/	
EBF89	0-68	EF95	1-47	PCF890	0-84	PC82	0-67	PCF800	0-80
EC86	0-73	EF183	0-63	PCF82	1-22	PC83	0-86	30FL2	0-80
EC88	0-78	EF184	0-63	PCF86	0-84	PC84	0-71	30FLJ1	1-19
EC89	0-68	EH90	0-85	PCF9200	1-00	PC85	0-49	30FL14	0-94
EC90	0-68	EL34	0-82	PCF201	1-00	PC86	0-88	30L1/PC83	
EC97	0-60	EL36	1-01	PCF801	0-84	U193	0-68		
EC98	0-47	EL31	0-85	PCF803	0-70	U199	0-68	30L15/	
EC99	0-44	EL84	0-87	PCF806	0-84	UABC80	0-80	PC805	1-04
EC983	0-47	EL84	0-87	PCF806	0-84	UABC80	0-80	30L17	0-87
EC984	0-48	EL86	0-82	PCL82	0-88	UBF89	0-65	30P4MR	1-29
EC985	0-71	EL81	0-80	PCL83	0-84	UOC86	0-69	30F12/	
EC988	0-84	EL90	0-76	PCL84	0-84	UOC81	1-19	PC801	1-01
EC989	0-84	EL90	0-76	PCL85	0-84	UOC82	0-72	30P19/	
EC990	0-84	EL90	0-76	PCL86/85	0-84	UOC83	0-72	PC802	0-89
EC991	0-84	EL90	0-76	PCL86/85	0-84	UOC84	0-80	30L17/	
EC992	0-84	EL90	0-76	PCL86/85	0-84	UOC85	0-82	PCL801	1-00
EC993	0-84	EL90	0-76	PCL86/85	0-84	UOC86	0-84	30FL13/	
EC994	0-84	EL90	0-76	PCL86/85	0-84	UOC87	0-82	PCL800	1-15
EC995	0-84	EL90	0-76	PCL86/85	0-84	UOC88	0-84	30FL14/	
EC996	0-84	EL90	0-76	PCL86/85	0-84	UOC89	0-84	PCL84	1-85
EC997	0-84	EL90	0-76	PCL86/85	0-84	UOC90	0-84	30FL13	1-18

TRANSISTORS-INTEGRATED CIRCUITS

All transistors, I.C.'s offered are new and branded. Manufactured by Mullard, Texas, RCA, Ferranti, Motorola, ITT, Fairchild, Lucas, etc. Quantity discounts on application. Send SAE for full lists.


EXPRESS POSTAGE

5p for 600 Transistor. For each additional add 1p.

AA119	0-07	HD144	0-80	OA200	0-08	ZTX200	0-16	2N2994	0-20
AA213	0-10	HD131	0-48	OA209	0-10	ZTX501	0-15	2N2904A	0-25
AA215	0-10	BD152	0-60	OC16	1-00	ZTX503	0-16	2N2905	0-22
AC107	0-85	BF115	0-22	OC20	2-00	ZTX501	0-25	2N2905A	0-22
AC126	0-25	BF147	0-26	OC23	1-25	ZTX590	0-18	2N2906	0-20
AC127	0-26	BF173	0-28	OC25	0-45	1N314	0-08	2N2928	0-10
AC128	0-20	BF179	0-38	OC29	0-70	1N4001	0-05	2N2953	0-20
AC175	0-26	BF180	0-35	OC35	0-53	1N4002	0-07	2N2955	0-20
AC187	0-20	BF181	0-35	OC40	0-40	1N4003	0-08	2N2928	0-10
AC188	0-20	BF194	0-12	OC42	0-40	1N4004	0-08	2N2914	0-25
ACY21	0-20	BF195	0-12	OC44	0-18	1N4005	0-10	2N2815	0-89
ACY39	0-85	BF197	0-18	OC45	0-18	1N4006	0-12	2N2928	0-11
AD140	0-80	BF200	0-25	OC46	0-15	1N4007	0-12	2N2929	0-12
AD149	0-80	BF201	0-25	OC48	0-15	1N4009	0-05	2N2974	0-14
AD171	0-80	BF202	0-25	OC49	0-15	1N4148	0-08	2N2976	0-15
AD182	0-80	BF210	0-61	OC52	0-65	18021	0-07	2N2976	0-12
AF115	0-25	BF229	0-28	OC54	0-20	18023	0-20	2N2977	0-18
AF116	0-25	BF229	0-28	OC56	0-15	18023A	0-20	2N2978	0-07
AF117	0-20	BF230	0-20	OC58	0-15	18024	0-20	2N2979	0-10
AF186	0-40	BF232	0-20	OC62	0-25	180301	0-28	2N2979	0-11
AF239	0-44	BF210	0-15	OC78	0-80	1N4148	0-08	2N2976	0-15
AGY37	0-80	BY126	0-14	OC77	0-85	18021	0-07	2N2976	0-12
AGY38	0-85	BY127	0-15	OC81	0-28	18023	0-20	2N2977	0-18
AGY49	0-85	BY128	0-15	OC82	0-28	18024	0-20	2N2978	0-07
AD149	0-80	BY129	0-15	OC83	0-25	180301	0-28	2N2979	0-11
AD182	0-80	BY210	0-61	OC140	1-00	2N2959	0-18	2N2971	0-10
AF115	0-25	BF229	0-28	OC170	0-85	2N2977	0-18	2N2919	0-11
AF116	0-25	BF229	0-28	OC171	0-20	2N2978	0-10	2N2820	0-20
AF117	0-20	BF230	0-20	OC200	0-55	2N2906A	0-18	2N2823	0-20
AF186	0-40	BF232	0-20	OC201	1-35	2N1151	0-85	2N2903	0-16
AF239	0-44	BF210	0-15	OC202	0-60	2N1208	0-28	2N2904	0-20
AGY37	0-80	BY126	0-14	OC203	0-55	2N1302	0-18	2N2906	0-25
AGY38	0-85	BY127	0-15	OC204	0-55	2N1303	0-18	2N2906	0-22
AGY49	0-85	BY128	0-15	OC205	0-55	2N1806	0-22	2N2905	0-16
AD149	0-80	BY129	0-15	OC206	0-55	2N1806	0-22	2N2906	0-12
AD182	0-80	BY210	0-61	OC207	0-55	2N1806	0-22	2N2906	0-11
AF115	0-25	BF229	0-28	OC208	0-55	2N1806	0-22	2N2906	0-16
AF116	0-25	BF229	0-28	OC209	0-55	2N1806	0-22	2N2906	0-20
AF117	0-20	BF230	0-20	OC210	0-55	2N1806	0-22	2N2906	0-12
AF186	0-40	BF232	0-20	OC211	0-55	2N1806	0-22	2N2906	0-16
AF239	0-44	BF210	0-15	OC212	0-55	2N1806	0-22	2N2906	0-16
AGY37	0-80	BY126	0-14	OC213	0-55	2N1806	0-22	2N2906	0-12
AGY38	0-85	BY127	0-15	OC214	0-55	2N1806	0-22	2N2906	0-16
AGY49	0-85	BY128	0-15	OC215	0-55	2N1806	0-22	2N2906	0-16
AD149	0-80	BY129	0-15	OC216	0-55	2N1806	0-22	2N2906	0-16
AD182	0-80	BY210	0-61	OC217	0-55	2N1806	0-22	2N2906	0-16
AF115	0-25	BF229	0-28	OC218	0-55	2N1806	0-22	2N2906	0-16
AF116	0-25	BF229	0-28	OC219	0-55	2N1806	0-22	2N2906	0-16
AF117	0-20	BF230	0-20	OC220	0-55	2N1806	0-22	2N2906	0-16
AF186	0-40	BF232	0-20	OC221	0-55	2N1806	0-22	2N2906	0-16
AF239	0-44	BF210	0-15	OC222	0-55	2N1806	0-22	2N2906	0-16
AGY37	0-80	BY126	0-14	OC223	0-55	2N1806	0-22	2N2906	0-16
AGY38	0-85	BY127	0-15	OC224	0-55	2N1806	0-22	2N2906	0-16
AGY49	0-85	BY128	0-15	OC225	0-55	2N1806	0-22	2N2906	0-16
AD149	0-80	BY129	0-15	OC226	0-55	2N1806	0-22	2N2906	0-16
AD182	0-80	BY210	0-61	OC227	0-55	2N1806	0-22	2N2906	0-16
AF115	0-25	BF229	0-28	OC228	0-55	2N1806	0-22	2N2906	0-16
AF116	0-25	BF229	0-28	OC229	0-55	2N1806	0-22	2N2906	0-16
AF117	0-20	BF230	0-20	OC230	0-55	2N1806	0-22	2N2906	0-16
AF186	0-40	BF232	0-20	OC231	0-55	2N1806	0-22	2N2906	0-16
AF239	0-44	BF210	0-15	OC232	0-55	2N1806	0-22	2N2906	0-16
AGY37	0-80	BY126	0-14	OC233	0-55	2N1806	0-22	2N2906	0-16
AGY38	0-85	BY127	0-15	OC234	0-55	2N1806	0-22	2N2906	0-16
AGY49	0-85	BY128	0-15	OC235	0-55	2N1806	0-22	2N2906	0-16
AD149	0-80	BY129	0-15	OC236	0-55	2N1806	0-22	2N2906	0-16
AD182	0-80	BY210	0-61	OC237	0-55	2N1806	0-22	2N2906	0-16
AF115	0-25	BF229	0-28	OC238	0-55	2N1806	0-22	2N2906	0-16
AF116	0-25	BF229	0-28	OC239	0-55	2N1806	0-22	2N2906	0-16
AF117	0-20	BF230	0-20	OC240	0-55	2N1806	0-22	2N2906	0-16
AF186	0-40	BF232	0-20	OC241	0-55	2N1806	0-22	2N2906	0-16
AF239	0-44	BF210	0-15	OC242	0-55	2N1806	0-22	2N2906	0-16
AGY37	0-80	BY126	0-14	OC243	0-55	2N1806	0-22	2N2906	0-16
AGY38	0-85	BY127	0-15	OC244	0-55	2N1806	0-22	2N2906	0-16
AGY49	0-85	BY128	0-15	OC245	0-55	2N1806	0-22	2N2906	0-16
AD149	0-80	BY129	0-15	OC246	0-55	2N1806	0-22	2N2906	0-16
AD182	0-80	BY210	0-61	OC247	0-55	2N1806	0-22	2N2906	0-16
AF115	0-25	BF229	0-28	OC248	0-55	2N1806	0-22	2N2906	0-16
AF116	0-25	BF229	0-28	OC249	0-55	2N1806	0-22	2N2906	0-16
AF117	0-20	BF230	0-20	OC250	0-55	2N1806	0-22	2N2906	0-16
AF186	0-40	BF232	0-20	OC251	0-55	2N1806	0-22	2N2906	0-16
AF239	0-44	BF210	0-15	OC252	0-55	2N1806	0-22	2N2906	0-16
AGY37	0-80	BY126	0-14	OC253	0-55	2N1806	0-22	2N2906	0-16
AGY38	0-85	BY127	0-15	OC254	0-55	2N1806	0-22	2N2906	0-16
AGY49	0-85	BY128	0-15	OC255	0-55	2N1806	0-22	2N2906	0-16
AD149	0-80	BY129	0-15	OC256	0-55	2N1806	0-22	2N2906	0-16
AD182	0-80	BY210	0-61	OC257	0-55	2N1806	0-22	2N2906	0-16
AF115	0-25	BF229	0-28	OC258	0-55	2N1806	0-22	2N2906	0-16
AF116	0-25	BF229	0-28	OC259	0-55	2N1806	0-22	2N2906	0-16
AF117	0-20	BF230	0-20	OC260	0-55	2N1806	0-22	2N2906	0-16
AF186	0-40	BF232	0-20	OC261	0-55	2N1806	0-22	2N2906	0-16
AF239	0-44	BF210	0-15	OC262	0-55	2N1806	0-22	2N2906	0-16
AGY37	0-80	BY126	0-14	OC263	0-55	2N1806	0-22	2N2906	0-16

R T V C FOR AUDIO AT A BUDGET

COMPLETE STEREO SYSTEM System 1. £51-00

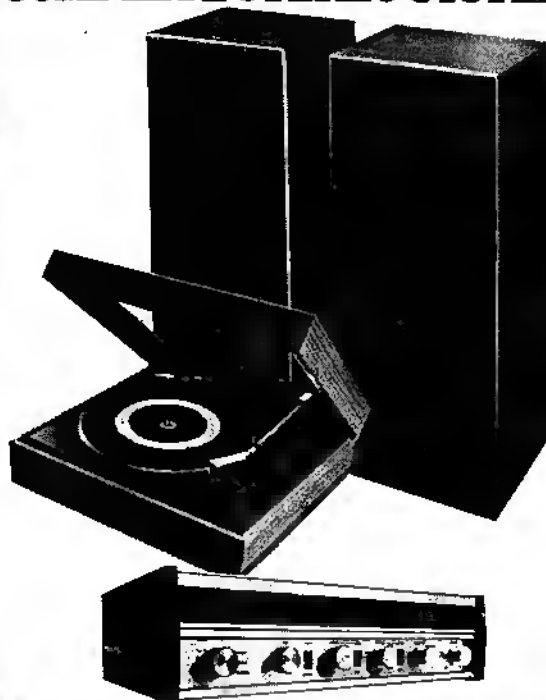

40 Watt Amplifier. Viscount III - R102 now 20 watts per channel.
 System 1 includes:
 Viscount III amplifier - volume, bass, treble and balance controls, plus switches for mono/ stereo on/off function and bass and treble filters. Plus headphone socket.
 Specification
 20 watts per channel into 8 ohms. Total distortion @ 10W @ 1kHz 0-1%. P.U.I. (for ceramic cartridges) 150mV into 3 Meg. P.U.I. (for magnetic cartridges) 4mV @ 1kHz into 47K, equalized within ± 1dB R.I.A.A. Radio 150mV into 220K. (Sensitivities given at full power). Tape out facilities: headphone socket, power out 250mW per channel. *Tone controls and filter characteristics:* Bass: +12dB to -12dB @ 60Hz. Bass filter: 6dB per octave cut. Treble control: treble +12dB to -12dB @ 15kHz. Treble filter: 12dB per octave. *Signal to noise ratio:* (all controls at max.) - 58dB. Crosstalk better than 35dB on all inputs. Overload characteristics better than 26dB on all inputs. Size approx. 13 1/2" x 9" x 3 1/2".
 Garrard SP 25 Mk III deck with magnetic cartridge, de luxe plinth and hinged cover.
 Two Duo Type II matched speakers - Enclosure size approx. 17 1/2" x 10 1/2" x 6" in simulated teak. Drive unit 13" x 8" with parasitic tweeter, 10 watts handling.

Complete System £51-00

System 2. £69-00

Viscount III amplifier (As System 1)
 Garrard SP 25 Mk III deck (As System 1)
 Two Duo Type III matched speakers - Enclosure size approx. 27" x 13" x 11 1/2"
 Finished in teak veneer. Drive units 13" x 8" bass driver, and two 3" (approx.) tweeters. 20 watts R.M.S., 6 ohms frequency range - 20 Hz to 18,000 Hz.

Complete System £69-00

PRICES: SYSTEM 1

Viscount III R102 amplifier	£24.20 + £1 p & p
2 Duo Type II speakers	£14.00 + £2.20 p & p
Garrard SP 25 with Mag. cartridge de luxe plinth and hinged cover	£21.00 + £1.75 p & p
total:	£59.20

Available complete for only: **£51-00**
 + £3.50 p & p

PRICES: SYSTEM 2

Viscount III R102 amplifier	£24.20 + £1 p & p
2 Duo Type III speakers	£39.00 + £4.00 p & p
Garrard SP 25 with Mag. cartridge de luxe plinth and hinged cover	£21.00 + £1.75 p & p
total:	£84.20

Available complete for only: **£69-00**
 + £4.00 p & p



STEREO 21 * QUALITY SOUND FOR LESS THAN £20-00

Stereo 21, easy to assemble audio system kit. No soldering required.

The unit is finished in white P.V.C. and the acrylic top presents an unusually interesting variation on the modern deck plinth.

Includes: - BSR 3 speed deck, automatic, manual facilities together with stereo cartridge.

Two speakers with cabinets.

Amplifier module. Ready built with control panel, speaker leads and full, easy to follow assembly instructions.

Specifications: For the technically minded: -

Input sensitivity 500mV. Aux. input sensitivity 120mV. Power output 2.7 watts per channel.

Output impedance 8-15 ohms. Stereo headphone socket with automatic speaker cutout. Provision for auxiliary inputs - radio, tape, etc., and outputs for taping discs. Overall dimensions. Speakers approx. 15 1/2" x 8" x 4". Complete deck and cover in closed position approx. 15 1/2" x 12" x 6".

Complete only **£19.55 + £1.60 p & p**. Extras if required. Optional Diamond Styl **£1.37**.

Specially selected pair of stereo headphones with individual level controls and padded earpieces to give optimum performance, **£3.85**.



BUILD YOUR OWN * STEREO AMPLIFIER


For the man who wants to design his own stereo - here's your chance to start, with Unisound - pre-amp, power amplifier and control panel. No soldering - just simply screw together. 4 watts per channel into 8 ohms. Inputs: 120mV (for ceramic cartridge). The heart of Unisound is high efficiency I.C. monolithic power chips which ensure very low distortion over the audio spectrum. 240V. AC only. **£7-64 + 55p. p & p**

8 TRACK HOME CARTRIDGE PLAYER



Elegant self selector push button player for use with your stereo system. Compatible with Viscount III system. Unisound module and the Stereo 21. Technical specification Mains input, 240V. Output sensitivity 125mV. Comparable unit sold elsewhere at £24.00 approx. Yours for only **£11.95 + 90p p & p**.

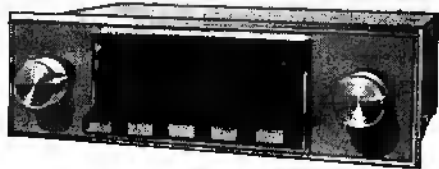PUSH BUTTON CAR RADIO KIT * The Tourist II



NO SOLDERING REQUIRED!

NOW BUILD YOUR OWN PUSH BUTTON CAR RADIO
Easy to assemble construction kit comprising fully completed and tested printed circuit board on which no soldering is required. All connections are simple push fit type making for easy assembly. Fine tuning push button mechanism is fully built and tested to mate with printed circuit board.

Technical specification: (1) Output 4 watts R.M.S. output. For 12 volt operation on negative or positive earth. (2) Integrated circuit output stage, pre-built three stage IF Module. Controls volume manual tuning and five push buttons for station selection, illuminated tuning scale covering full, medium and long wave bands.

Size chassis 7" wide, 2" high and 4 1/4" deep approx **£7.70** + 55p p & p

Speaker including baffle and fixing strip **£1.65** + 23p. p & p.

Car Aerial Recommended — fully retractable **£1.37** + 20p. p & p

The Tourist I Kit For the experienced constructor if you can solder on a printed circuit board you can build this model.

Same technical specification as Tourist II **Price £6.60** + 55p p & p.

EMI SPEAKERS AT FANTASTIC REDUCTIONS



**20 WATT
SPEAKER SYSTEM ***
System consists of a 13" x 8" (approx) elliptical woofer unit with a 3" x 5" (approx.) mid range unit incorporating parabolic tweeter and crossover components. Circuit Diagram Technical Specification:


Base Unit
Flex density-100 K, speech coil-1 1/2", Cone. Triple laminated paper with P.V.C. surround.
Mid Range Unit
Flex density-33K, speech coil-1" with parabolic tweeter.

Power Handling
10 watts R.M.S., impedance - 8 ohms, frequency response - 20 Hz to 18,000 Hz.

OUR PRICE

£6.60. Complete

+ 90p p & p.

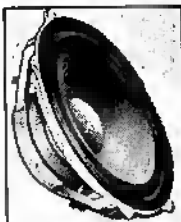


15" 14A/780 BASS UNIT

Bass unit on a rigid diecast chassis. Superior cone material handles up to 50 watts RMS, and is treated to give a smooth frequency response. Resistance 10 Ohm. Flux density 340,000 Maxwells. Impedance at 1 kHz is 8 ohms. 3" voice coil.

Recommended retail price **£40.80.**

OUR PRICE £18.70

+ £1.50 p & p

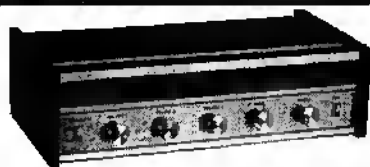

DISCO AMPLIFIER*

Reliant Mk IV Mono Amplifier, ideal for the small disco or house parties. Outputs 20 watts R.M.S. into 8 ohms (suitable for 15 ohms).

Inputs *4 electrically mixed inputs. *3 individual mixing controls.

*Separate bass and treble controls common to all 4 inputs.

*Mixer employing F.E.T. (Field Effect Transistors) *Solid State circuitry.

*Attractive styling.

INPUT SENSITIVITIES - Input - 1.) Crystal mic, guitar or moving coil mic, 2 and 10mV. (Selector switch for desired sensitivity).

-Inputs - 2), 3), 4). Medium output equipment - ceramic cartridge, tuner, tape recorder, organs, etc. - all 250mV sensitivity. AC Mains. 240V operation. Size approx: 12 1/2" x 6" x 3 1/2". **£15.00** + 60p. p & p

PORTABLE DISCO CONSOLE*



INCORPORATES: Pre-Amp with full mixing facilities, including switched input for mic with volume control, switched input for auxiliary with volume control, bass and treble controls, volume control and stand control for turntables.

Two B.S.R. single play professional series decks, fitted with crystal cartridges. The turntables are designed and precision engineered. They combine clean modern styling with superb reproduction. Their many special features include square section aluminium tonearms, (high precision low mass design fully counterbalanced, with calibrated stylus pressure control for perfect tracking), and conveniently grouped easy to read linear controls. The turntables have viscous cueing devices which allows the tonearms to be placed or lifted at any point on the record.

The two lightweight cartridge shells have slide-in-holders to facilitate easy inspection of needles and cartridges.

TECHNICAL SPECIFICATION:

Pre-amp - Output - 200mV.

Auxiliary inputs - 200mV and 750mV into 1 meg.

Mic input - 8mV into 100K, 240 volt operation.

Turntables capacity - 7", 10" or 12" records.

Rumble, wow and flutter -

Rumble Better than -35dB. Wow Better than 0.2%.

Flutter Better than 0.06% (Gaumont kalea meter).

Finish - Satin black mainplate with black turntable

met inlaid with brushed aluminium trim. Tonearm

and controls in black and brushed aluminium.

Console size -

Unit Closed - 17 1/2" x 13 1/2" x 8 1/2" (approx.)

Unit Open - 35 3/4" x 13 1/2" x 4 1/2" (approx.)

This disco console is ideally matched for the Reliant IV and Disco 50 or any other quality amplifier.

The unit is finished in black PVC with contrasting simulated teak edging diamond spun control knobs with matching control panel.

Yours for only £45.00 + £3.50 P. & P.



DO NOT SEND CARD

Just write your order giving your credit card number

Mail orders to Acton. Terms C.W.O. All enquiries stamped addressed envelope. Goods not despatched outside U.K. Leaflets available for all items listed thus * Send stamped addressed envelope. All items subject to availability. Prices correct at 1st Nov. 1974 and subject to change without notice. All prices include V.A.T. at 8% rate.

Personal Shoppers Edgware Road: 9a.m.-5.30p.m. Half day Thurs. Acton: 9.30a.m.-5p.m. Closed all day Wed.



Radio and TV
Components
(Acton) Ltd.

21c High Street, Acton, London W3 6NG
323 Edgware Road, London W2

TECHNICAL TRAINING

in radio television and electronics

Whether you are a newcomer to radio and electronics, or are already engaged in the industry, ICS can help you. We can further your technical knowledge and provide the specialised training so essential to success, or prepare you for a recognised examination. ICS have helped thousands of ambitious men to move up into higher paid jobs - we can do the same for you. *Take one of these courses.*

CITY & GUILD CERTIFICATES:-

Telecommunications Technicians
Radio, TV and Electronics Technicians
Electrical Installations Technicians
Electrical Installation Work
Technical Communication
Radio Amateur

MPT General Radio Communications Cert.

DIPLOMA COURSES:-

Electronic Engineering, Maintenance
Radio, TV, Audio Engineering and Servicing (inc. Colour TV)
Electrical Engineering, Installations
Computer Engineering & Programming
New Self-Build Radio Courses

QUALIFY FOR A NEW CAREER

Home study courses for leading professional examinations and diploma courses for business and technical subjects:-

G.C.E.

60 subjects at 'O' and 'A' levels

Accountancy	Engineering	Motor
Administration	Farming	Personnel
Advertising	Heating	Purchasing
Air Conditioning	Industrial	Sales
Building	Management	Secretarial
Construction	Marketing	Storekeeping
Catering	Mechanical	Work Study

POST THIS COUPON TODAY

To: INTERNATIONAL CORRESPONDENCE SCHOOLS

Dept. 232C, Intertext House, LONDON
SW8 4UJ or telephone 01-622 9911

Please send me full details of your courses for:-

(State Subject)

Name

Address

Occupation Age

Accredited by the Council for the Accreditation of Correspondence Colleges

SPARKRITE Mk II

Electronic Ignition...

Better on all points

Because you keep your points!

The SPARKRITE MK.2 is a full capacitive discharge electronic system. Specifically designed to retain the points assembly with all the advantages and none of the disadvantages. No mistra because contact breaker bounce is eliminated electronically by a pulse suppression circuit which prevents the unit firing if the points bounce open at high rpm. Contact breaker burn is eliminated by reducing the current to about 1/50th of norm, thus avoiding arcing. But you can still revert to normal ignition if need be. In seconds, if points go (very unlikely) you can get replacements anywhere. All these advantages.

- Fitted in 15 minutes. ● Up to 20% better fuel consumption. ● Ignition all weather starting. ● Cleaner plugs - they last 5 times longer without attention.
- Faster acceleration. ● Faster top speeds.
- Coil and battery last longer. ● Efficient fuel burning with less air pollution.

The kit comprises everything needed

Heady drilled scratch and rust resistant case, metalwork, cables, coil connectors, printed circuit board, top quality 5 year guaranteed transformer and components, full instructions to make positive or negative earth system, and 6 page installation instruction leaflet.

WE SAY IT IS THE BEST SYSTEM AT ANY PRICE!

PRICES

DIY Kit only £10.93 incl. VAT and P & P
Heady Built Unit £13.86 incl. VAT and P & P
(Both to fit all cars with coil distributor ignition up to 5 cylinders)

We can supply units for any test of engine vehicle (two or motorcycle) with coil contact breaker ignition

Details on request! Call in and see us for a demonstration

ELECTRONICS DESIGN ASSOCIATES

(Dept. PW2) 82 Bath Street, Walsall WS1 3DE Phone 33652



Phoenix Electronics (Portsmouth) Ltd.

139-141 Havant Road,
Drayton, Portsmouth, Hants
PO6 2AA

Full member of AFDEC—the industry's association of franchised electronic component distributors.

Our prices include VAT at the current rate—and carriage on all goods is free.

Send for our catalogue and price list—we'll mail that to you free, too.

COMPONENTS FOR I.C. APPLICATIONS BY MR. J. B. DANCE

SAJ110	£1-96	SAJ180	£1-96	SAK110/115	£1-23
TAA775G	£1-23	TAA930A	£1-23	TBA790KSD	£1-96
TBA800	£1-96	TBA950	£1-76	TCA250	£1-96

Please send your catalogue—free!

Name

Address

..... PEP/1A

CUSTOM CABINETS, 331 High Street, Rochester, Kent. Tel: Medway (0634) 404199.

Speaker Cabinets in kit form represent HUGE SAVINGS



2' x 12" Cabinet



4' x 12" Cabinet



Disco Console (includes lid not shown)
Takes two slaves

For a long time now a large number of customers have asked us to produce cabinets in kit form, and above we show examples of cabinet styles and these are now available either fully built or in kit form ready for you to produce a professional finish in a very short time!

Kits are available in all specifications and all the kits contain everything you need as follows :-

- 1) 4 sides with handle cutouts, front edges rounded, 1 back with jack socket hole, and 1 baffleboard with speaker cutout
- 2) P.V.C. cut to size for frame and back, plus false front and back timbers, white front piping and speaker cloth
- 3) Recessed handles with fixing screws, jack socket, all fixing screws, corner plates, glue, and full instructions!

PRICE & TYPE LIST

Type	Size	Price manufactured	Kit price
2 x 12" (illustrated above)	36" x 18" x 13" x 3/4"	£19.50	£12.50
4 x 12" (illustrated above)	31" x 31" x 13" x 3/4"	£24.50	£17.50
4 x 12" P.A. Column	48" x 27" x 13" x 3/4"	£30.00	£21.50
1 x 18"	31" x 31" x 13" x 3/4"	£24.50	£17.50
1 x 15" with two top horn cutouts	36" x 20" x 13" x 3/4"	£21.00	£13.50
Mini Disco (state deck cutout BSR, GARRARD etc.)	33" x 20" x 10" x 1/2"	£20.00	£13.00
Maxi Disco (illustrated) (state deck cutout BSR, GARRARD etc.)	42" x 20" x 10" x 1/2"	£25.00	£18.50

Please ask for quotation on any other type or size of cabinet you may require.
ALL OUR PRICES INCLUDE VAT AND UK DELIVERY

BYWOOD CHANTICLEER

- * READ: TIME AND ALARM
- * ELECTRONIC 'BEEP' ALARM TONE
- * TEN MINUTE 'SNOOZE' FEATURE
- * BRIGHT, CLEAR DISPLAY
- * NO MOVING PARTS
- * EXECUTIVE STYLING
- * SOLID STATE RELIABILITY

Digital clock

The heart of the CHANTICLEER is a tiny electronic package containing thousands of transistors which divide the 50 cycles/second mains frequency into precise time units. The clock "movement" in fact has no moving parts to wear out or tick or tock or hum or click.

RECOMMENDED
PRICE

£19.95 + VAT

BYWOOD

**COMPLETELY ELECTRONIC
NO MOVING PARTS**




Alarm

Has a.m. or p.m. setting with alarm on/off indicator. A gentle electronic 'beep' tone with special snooze feature that resets the alarm for ten-minute intervals. The snooze is activated by simply tilting the clock forward and then releasing. Upon cancelling, the alarm can be immediately reset for the same time next day.

BYWOOD ELECTRONICS
181 Ebbens Road
Hemel Hempstead
Herts. HP3 9RD.
Tel. 0442 62757

LISTEN TO

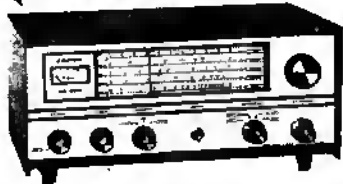CODAR® THE WORLD!★ **CR70A****COMMUNICATION RECEIVER**

The CODAR CR70A is an outstanding general coverage communication receiver, ideal for the keen S.W.L.

It tunes from 540 metres medium through to 10 metres with no gaps. Covers shipping, coastguard and distress frequencies, all six amateur bands 160-10 metres, international broadcast, Met. stations etc. etc. giving world-wide reception. Exclusive features include Air-spaced CODAR-COIL HI-"Q" Aerial input, illuminated Meter and Slide Rule Scale, Two Speed vernier tuning, Switched B.F.O. for CW/SSB signals. Separate output for Tape recorder.

Ready to plug in to 200/240 volts A.C. it only needs your aerial and a 2/3 ohm loudspeaker to bring the world to your finger tips. 12 months full guarantee.

★ **IMPORTANT NOTE**


This fine receiver is not a mass produced item, but each set is hand built to your order, individually checked and air tested. Please allow for this when ordering—your delivery date will be shown on your receipt, sent by return.



ON THE DESIGN STAFF—
G3SZM G3JRE

CODAR®

VALCON WORKS · BURRELL BUILDINGS · CHURCHILL INDUSTRIAL ESTATE · LANCING · SUSSEX
WORLD-WIDE MAIL ORDER—EXPORT QUOTES FREE. **BN15 - 8TZ**

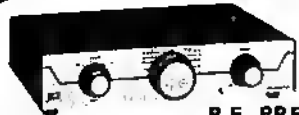★ **MADE TO ORDER!****£37.15!**VAT PAID
CARR. 85p★ **P.R.40** ★**£10.93!**VAT PAID
CARR. 32p**R.F. PRESELECTOR**

The PR40 R.F. Preselector is the solid state version of the world famous PR30 which it now supersedes.

It employs Silicon "N" Channel FET (Field Effect Transistor) front end followed by silicon NPN Broad Band R.F. Amp. and will substantially improve receiver performance over the range 1.5 to 35 MHz, providing a considerable increase in gain up to an overall average of 30dB, with improved image rejection and noise ratio.

Supplied complete with co-ax plug (less standard 9 volt PP6 Battery). 12 months Guarantee ...

**MULTIBAND-6** ★**SHORT WAVE RECEIVER KIT****£16.90!** CARR. 43p


All transistor T.U.F. Receiver tunes 550 KHz to 30 MHz (540 to 10 metres) complete coverage—no gaps. Medium waves—Trawlers—Ship / Shore Telephone—All Six Amateur Bands 160-10 metres—International Broadcast from Australia, Far East, Russia, USA etc. using 4 miniature plug in Coils. Hi-Gain FET Regen. Det./AF/AF Module giving full loudspeaker output to any external 2/3 ohm speaker. Receives AM/CW/SSB. Separate Electrical Bandsread, Calibrated Main Tuning.

A Quality CODAR-KIT with 12 months Guarantee. No technical knowledge required, simple to build, printed circuit and Pictorial Instruction Manual, fully detailed step by step.

Complete Kit with 4 Coils (less standard PP6 battery).

ILLUSTRATED LEAFLETS FREE ON REQUEST

TO COPE WITH INCREASING DEMAND—PLEASE
NOTE NEW SALES OFFICE TEL No. 02-73-38345
MON-THURS-9.30 a.m.-4.30 p.m.

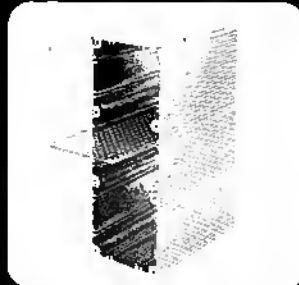Verobox**ALUMINIUM ENCLOSURES**

- 6 standard sizes available from your local retailer.
- Made from precision extrusions with integral board guide slots.
- Finned sides improve appearance and radiate heat.
- Parallel sides for ease of component mounting.

vero

VERO ELECTRONICS LTD.
Eastleigh, Hants. SO5 3ZR
Tel: Chandler's Ford 2952 Telex: 47551

Subsidiaries and Agents
throughout the World

TELEVISION CAMERA KITS

Complete kits are available for both "Mullard" and "P.E." design. Each kit includes a comprehensive construction manual, and a completely FREE technical back up service to ensure your success. VHF and UHF Modulator Kits also available to allow standard domestic T.V. to be used as monitor.

All parts available separately, including a wide range of lenses, vidicon tubes, special mains transformers and focus/scan coil assemblies, ready built cameras also available. Complete kits also available P.W. tele-tennis game. Send 5" x 7" S.A.E. for full details or come along for a demonstration and a chat with our technical staff.

GROFTON ELECTRONICS

124 Colne Road, Twickenham,
Middlesex, TW2 6QS


Tel: 01-898-1569

Telex 934642 Cadanac LDN

MAINS UNITS for all types of TRANSISTOR EQUIPMENT

RUN YOUR TRANSISTOR RADIO OR CASSETTE RECORDER FROM YOUR CAR BATTERY (Similar to illustration)

This unit enables you to run your cassette tape recorder from the car whilst travelling. It is easily fitted and comes complete with fitting instructions. Please state make of cassette, voltage and type of plug required.

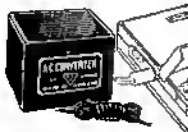**ONLY £2.86**

RUN YOUR TAPE RECORDER OFF AC MAINS

Mains unit supplied complete and ready to plug into your cassette recorder. (State voltage, make and type of plug required, if in doubt send diagram of recorder socket.)

**ONLY £3.40**

RUN YOUR TRANSISTOR RADIO OFF AC MAINS

For single outputs, 6v, 9v **£2.86**

For two separate outputs, 6v + 6v,

9v + 9v **£3.52** per unit. (Please state outputs required.)

All units are completely isolated from mains by double wound transformer ensuring 100% safety. All British Made. All Prices Inc. V.A.T. and P. & P.

R.C.S. PRODUCTS (RADIO) LTD.
(Dent. PWJ)

31 Oliver Road, Walthamstow, London, E17
Full refund if not completely satisfied.

ELECTROVALUE

APPOINTED STOCKISTS FOR SIEMENS QUALITY PRODUCTS

Present

top quality electronic components for price-minded buyers

112 p. CATALOGUE • FREE POSTAGE (U.K.) • ATTRACTIVE DISCOUNTS • SPECS. GUARANTEED

A 100 OF THE BEST

From our transistor stock

2N1307	47p	BC149C	14p
2N2640	51p	BC158B	15p
2N3053	30p	BC159	15p
2N3054	60p	BC167B	13p
2N3055	70p	BC168B	12p
2N3702	11p	BC169B	52p
2N3703	10p	BC169C	12p
2N3704	11p	BC170B	26p
2N3705	10p	BC182L	12p
2N3794	18p	BC184L	12p
2N5819	28p	BC219L	12p
2N4062	11p	BC214L	14p
2N4443	93p	BC257A	14p
2N5062	42p	BC259B	14p
2N5183	20p	BCY58	30p
2N5459	32p	BD130	90p
4C351	48p	BD131	48p
4C382	44p	BD132	52p
4C502	46p	BD135	37p
4C636	£1-36	BD136	39p
4C659	£1-10	BDY20	83p
AC128	17p	BF194	15p
AC131R	23p	BFR39	23p
AC152	27p	BFR79	23p
AC153K	37p	BFX29	27p
AC176	24p	BFX84	27p
AC170K	38p	BFY51	23p
AC187K	31p	BRV39	50p
AD188K	29p	BY164	31p
AD133	£1-12	C106B1	42p
AD138	£1-11	C106D1	62p
AD149	52p	C1406	78p
AD161	42p	MJ481	£1-20
AD162	40p	MJ491	£1-35
AF200U	40p	MJ2955	80p
AF206	80p	MJE371	89p
BI005	36p	MJE521	81p
BA138	71p	MJE2955	£1-12
BB103	24p	MJE5055	68p
BB105	24p	OA91	6p
BB109	15p	SD4	3p
BC107A	19p	Y1P31A	70p
BC107B	19p	TIP32A	85p
BC106B	18p	TIP21A	80p
BC109C	14p	TIP42A	£1-90
BC109B	18p	W02	38p
BC109C	18p	ZTX30A	14p
BC141A	12p	ZTX30A	23p
BC147B	13p	ZTX500	14p
BC149B	12p	ZTX504	45p

10% MORE IN CATALOGUE 7

BAXANDALL SPEAKER KIT

As designed by P. J. Baxandall and described originally in "Wireless World." Simple to assemble, fantastically good results and a greater money saver. Carries 10 watts RMS, 15 ohms impedance. Size 18in x 12in x 10in. Complete kit, including pack-flat cabinet, £18-90.

The size and weight of this product obliges us to charge 70p part cost of carr. In U.K. Equaliser Assembly, £2-80. Loudspeaker Unit 59RM109, £2-85. Cabinet Kit (to Baxandall design), £14-80. Cross-over choke for additional woofer to above, £1-50.

DISCOUNTS

Available on all items except those shown with NETT PRICES 10% on orders from £5 to £14-99, 15% on orders £15 and over.

FREE POSTAGE

In U.K. for pre-paid mail orders. For mail orders for £2 list value and under there is an additional handling charge of 10p. Overseas orders - carriage charged at cost. Giro A/C No. 331671/4502

RESISTORS

Code	Watts	Ohms	t to 9	10 to 99	100 up
(see note below)					
C	1/3	4-7-470K	1-3	1-1	0-9 nett
C	1/2	4-7-10M	1-3	1-1	0-9 nett
C	3/4	4-7-10M	1-5	1-2	0-97 nett
C	1	4-7-10M	3-2	2-5	1-02 nett
MO	1/2	10-1M	4	3-3	2-3 nett
WW	1	0-22-3-9Ω	11	10	8 nett
WW	3	1-10K	9	8	6 nett
WW	7	1-10K	11	10	8 nett

Codes:

C = carbon film, high stability, low noise.
MO = metal oxide. Electrosl TR5 ultra low noise.
WW = wire wound. Plessey.

Values: All E12 except C 1/3, C 1/2 and MO 1/2.
E12: 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and their decades.
E24: as E12 plus 11, 13, 16, 20, 24, 30, 36, 43, 51, 62, 75, 81 and their decades.

Tolerances:

5% except WW 10% ± 0-05Ω below 10Ω and 1/2W MO 2%.

Prices are in pence each for quantities of the same ohmic value and power rating. NOT mixed values. (Ignore fractions of one penny on total value of resistor order). Prices for 100 up in units of 100 only

POTENTIOMETERS

ROTARY, CARBON TRACK.

Double wipers for good contact and long working life

P.20 SINGLE linear 100 ohms to 4-7 megohms, each 14p

P.20 SINGLE log. 4-7 Kohms to 2-2 megohms, each 14p

JP.20 DUAL GANG 1in. 4-7 Kohms each 48p

JP.20 DUAL GANG log. 4-7 Kohms to 2-2 megohms, each 48p

JP.20 DUAL GANG Log/antilog 10K, 22K, 47K, 1 megohm only, each 48p

JP.20 DUAL GANG antilog 10K only 48p

2A. DP mains switch for any of above 14p extra.

Decades of 10, 22 and 47 only available in ranges above.

Skeleton Carbon Presets, Type PR, horizontal or vertical 6p each

SLIDER

Linear or log mono 4-7K to 1 meg. in all popular values each 30p

STEREO, matched tracks, lin. or log in all popular values from 4-7K to 1 meg. 60p

Escutcheon plates, mono, black, white or light grey, each 10p

Control knobs, blk/wht/red/yel/gm/blk/dk. grey/lt. grey, each 7p

ELECTROLYTIC CAPACITORS

Axial Lead	3V	6-3V	10V	15V	25V	40V	63V	100V
qF	3V	6-3V	10V	15V	25V	40V	63V	100V
0-47	—	—	—	—	—	11p	—	—
1-0	—	—	—	—	—	—	3p	8p
2-2	—	—	—	—	15p	—	3p	8p
4-7	—	—	—	11p	—	3p	8p	8p
10	—	—	—	—	3p	8p	8p	8p
22	—	—	8p	—	8p	8p	10p	10p
47	8p	—	8p	—	8p	8p	10p	10p
100	8p	8p	8p	8p	8p	10p	12p	13p
220	8p	8p	8p	10p	10p	11p	17p	20p
470	8p	8p	10p	11p	13p	17p	24p	45p
1,000	15p	13p	13p	17p	20p	25p	41p	—
2,200	15p	13p	23p	26p	37p	41p	—	—
4,700	28p	30p	39p	44p	58p	—	—	—
10,000	42p	48p	—	—	—	—	—	—

MINITRON DIGITAL INDICATORS

3015F Seven segment filament compatible with standard logic modules, 0-9 and decimal point: 9mm characters in 16 lead DIL. £1-20
Suitable BCD decoder driver 7447 £1-15
3015G showing + or - Δ t & dec. pl. £1-20

LEDs (Light Emitting Diodes) 25p
Photo Cells Cadmium Sulphide, each 40p

ANTEX Soldering Irons

CN240 £2-25 Spare bits 32p
CCN240 £2-70 Spare bits 48p

DESOLDER BRAID

8 ft strip 70p

WAVECHANGE SWITCHES

1 pole 12 way; 2 pole 8 way
3 pole 4 way; 4 pole 5 way each 39p
TAG STRIP 26 way 11p

NUTS, SCREWS, etc.

In lots of 100 each
4BA NUTS 34p; 6BA NUTS 30p
1/4 BA Screws 28p; 1/8 BA Screws 24p
Threaded pillars 6BA, 1/4" hexagonal £1-40

Plain spacers 1/4" round £1-12

Other sizes available

ENAMEL COPPER

WIRE IN 2 ounce reels

15, 18, 20, 22 SWG 34p
24, 25, 28, 30 SWG 38p
32, 34 45p; 36, 38, 40 54p

DIN CONNECTORS

	Socket	Plug
1 way loudspeaker	10p	12p
3 way audio	10p	12p
5 way audio 180	12p	15p
5 way audio 240	12p	15p
6 way audio	13p	15p

EV CATALOGUE 7

2nd printing—Green and yellow Cover

112 pages, thousands of items; Illustrations; diagrams; much useful technical information. The 2nd printing has been updated as much as possible on prices. It costs only 25p post free including return voucher for 25p for spending when ordering goods list value £5 or more.

QUALITY GUARANTEE

All goods are sold on the understanding that they conform to manufacturers' specifications and satisfaction is guaranteed as such—no rejects, 'seconds' or sub-standard merchandise is offered for sale. Prices quoted do not include V.A.T. for which 6% must be added to total net value of order. Every effort is made to ensure the correctness of information and prices at time of going to press. Prices subject to alteration without notice.

ELECTROVALUE LTD

All postal communications, mail orders etc. to Head Office at Egham address, Dept. PW.12. S.A.E. with enquiries requiring answers.

28, ST. JUDES ROAD, ENGLEFIELD GREEN, EGHAM, SURREY TW20 0HB Telephone Egham 3603 Telex 264475 Shop hours 9-5.30 daily; Sat. 9-1 p.m.

NORTHERN BRANCH: 680, Burnage Lane, Burnage, Manchester M19 1NA Telephone (061) 432 4945 Shop hours 9-5.30 daily; Sat. 9-1 p.m.

U.S.A. CUSTOMERS are invited to contact ELECTROVALUE AMERICA, P.O. Box 27, Swarthmore PA 19081.

The largest selection

EX COMPUTER BOARDS

Packed with transistors, diodes, capacitors and resistors—COMPONENT VALUE £1.50, 3 for ONLY 65p + p & p 30p
SPECIAL One on above PLUS Power Transistors ONLY 65p each + p & p 15p
PAKOLINE BOARD 7 1/2" x 9" approx. 4 for 80p + p & p 20p.

FIBRE-GLASS PRINTED CIRCUIT BOARDS

16 1/2" x 4" approx. 2 for 55p

DECON-DALO 33PC Marker

65ch resistant printed circuit marker pen 99p each

VERBOARDS

Packs containing approx. 300eq. lvs. various sizes, all 1 matric 55p

REPANCO CHOKES & COILS

RF Chokes
 CH1. 2-5mH 85p CH2. 5-0mH 90p
 CH3. 7-5mH 81p CH4. 10mH 85p
 CH5. 1-5mH 85p

COILS

DRX1 Crystal set 81p DRX2 Dual range 46p

COIL FORMERS & CORES

NORMAN 1" Cores & Formers 5p
 1" Cores & Formers 10p

SWITCHES

DP/DT Toggle 85p DP/ST Toggle 90p

FUSES

1 1/2" and 20mm. 100mA, 200mA, 250mA, 500mA, 1A, 1.5A, 2A
 QUICK-BLOW 5p ea.

EARPHONES

Crystal 2-5mm plug 49p
 Crystal 3-5mm plug 42p
 4 ohms 2-5mm plug 22p
 4 ohms 3-5mm plug 22p

DYNAMIC MICROPHONES

H1223, 200 ohms plus on/off switch and 2-5mm and 3-5mm plugs 11.95

3-WAY STEREO HEADPHONE JUNCTION BOX

H17012 £1.87

2-WAY CROSSOVER NETWORK

K4907, 80 ohms Imp. Insertion loss 3dB £1.21

CAR STEREO SPEAKERS

(Angle) £2.95 per pair.

BI-PAK

CATALOGUE AND LISTS
 Send S.A.E. and 10p.

INSTRUMENT CASES



Black Vinyl covered

No.	Length	Width	Height	Price
HV1	30"	2 1/2"	1 1/2"	£1.25
HV2	11"	6"	2"	£1.75

ALUMINIUM BOXES

BA1	5 1/2"	4"	1 1/2"	49p
BA2	4"	4"	1 1/2"	49p
BA3	4"	2 1/2"	1 1/2"	49p
BA4	5 1/2"	4"	1 1/2"	55p
BA5	4"	2 1/2"	1 1/2"	49p
BA6	3"	2"	1 1/2"	42p
BA7	2"	2"	1 1/2"	35p
BA8	4"	4"	2"	£1.10
BA9	6"	4"	2"	70p

P & P 10p on each box

BIB HI-FI ACCESSORIES

De Luxe Groov-Kleen

Model 42 £1-95

Chrome Finish

Model 60 £1-50



Ref. B Stylus & Turntable Cleaning Kit 85p
 Ref. 36A. Record/Stylus Cleaning Kit 85p
 Ref. 43. Record Care Kit £2.42
 Ref. 31. Cassette Head Cleaner 85p
 Ref. 32. Tape editing Kit £1.85
 Model 0. Wire Stripper/Cutter 85p

Ref. 46. Split level 62p
 Ref. F. Hi-Fi Cleaner 81p
 Ref. 32A. Stylus Balance £1.87
 Ref. J. Tape Head Cleaning Kit 85p
 Ref. 66. Hi-Fi Stereo Hints & Tips 42p
 Ref. 45. Auto changer groove cleaner £1.08

ANTEX SOLDERING IRONS

X25. 25 watt £2.05
 CXN 240. 15 watt £2.45
 Model U. 15 watt £2.20
 8K2. Soldering Kit £2.25
STANDS: ST3, Suitable for all models £1
SOLDER: 18SWG Multicores 7oz £1.81
 25SWG 7oz £1.81. 18SWG 22oz 61p
 22SWG Tube 82p

PLUGS AND SOCKETS

PLUGS
 PB 1 D.I.N. 2 Pin (Speaker) 0-11
 PB 2 D.I.N. 3 Pin 0-15
 PB 3 D.I.N. 4 Pin 0-18
 PB 4 D.I.N. 5 Pin 180° 0-18
 PB 5 D.I.N. 5 Pin 240° 0-18
 PB 6 D.I.N. 6 Pin 0-17
 PB 7 B.I.N. 7 Pin 0-18
 PB 8 Jack 2.5mm Bore 0-18
 PB 9 Jack 3.5mm Plastic 0-18
 PB 10 Jack 3.5mm Screened 0-18
 PB 11 Jack 1" Plastic 0-15
 PB 12 Jack 1" Screened 0-22
 PB 13 Jack Stereo Screened 0-30
 PB 14 Phone 0-10
 PB 16 Car Aerial 0-22
 PB 18 Co-Axial 0-18

ANTEX BITS and ELEMENTS

Bits No.
 102 For model GN240 3/32" 42p
 104 For model GN240 3/16" 42p
 1100 For model CGN240 3/32" 42p
 1101 For model CGN240 3/16" 42p
 1102 For model CGN240 1/4" 42p
 1020 For model G240 3/32" 42p
 1021 For model G240 1/8" 42p
 1022 For model G240 3/16" 42p
 50 For model X25 3/32" 42p
 51 For model X25 1/8" 42p
 52 For model X25 3/16" 42p

ELEMENTS

ECN 240 £1.30 ECUN 240 £1.32
 EG 240 £1.07 EX 25 £1.15

ANTEX HEAT SINKS 10p

V.A.T. included in all prices. Please add 10p P. & P. (U.K. only). Overseas orders—please add extra for postage.

NEW COMPONENT PAK BARGAINS

Pack No.	Qty.	Description	Price
C1	200	Resistors mixed values approx. count by weight	0.85
C2	150	Capacitors mixed values approx. count by weight	0.85
C3	30	Precision Resistors mixed values 1%, 2%	0.85
C4	75	1/4 W Resistors mixed preferred values	0.85
C5	5	Pieces assorted Ferrite Rods	0.85
C6	2	Tuning Gangs, MW/LW VHF	0.85
C7	1	Pack Wire 50 metres assorted colours	0.85
C 8 10		Reed Switches	0.85
C 9 3		Micro Switches	0.85
C10 45		Assorted Pots & Pre-Set	0.85
C11 2		Jack Sockets 3 x 3.5m 2 - Standard Switch Type	0.85
C12 30		Paper Condensers preferred types mixed values	0.85
C13 20		Electrolytic Trans. types	0.85
C14 1		Pack assorted Hardware—Nuts/Bolts, Grommets etc.	0.85
C15 5		Mains Slide Switches	0.85
C16 20		Assorted Tag strips & Panels	0.85
C17 10		Assorted Control Knobs	0.85
C18 4		Isolated Wave Change Switches	0.85
C19 2		Relays 4-24V Operating	0.85
C20 1		Pack sheets of Copper Laminate 20 sq. ins	0.85

INLINE SOCKETS

PS 21 D.I.N. 2 Pin (Speaker) 0-14
 PS 22 D.I.N. 3 Pin 0-20
 PS 23 D.I.N. 5 Pin 180° 0-20
 PS 24 D.I.N. 5 Pin 240° 0-20
 PS 25 Jack 2.5mm Plastic 0-18
 PS 26 Jack 3.5mm Plastic 0-18
 PS 27 Jack 1" Plastic 0-30
 PS 28 Jack 1" Screened 0-35
 PS 29 Jack Stereo Plastic 0-30
 PS 30 Jack Stereo Screened 0-30
 PS 31 Phone Screened 0-16
 PS 32 Car Aerial 0-22
 PS 33 Co-Axial 0-22

SOCKETS

PS 35 D.I.N. 2 Pin (Speaker) 0-08
 PS 36 D.I.N. 3 Pin 0-11
 PS 37 D.I.N. 5 Pin 180° 0-11
 PS 38 D.I.N. 5 Pin 240° 0-11
 PS 39 Jack 2.5mm Switched 0-12
 PS 40 Jack 3.5mm Switched 0-12
 PS 41 Jack 1" Switched 0-20
 PS 42 Jack Stereo Switched 0-30
 PS 43 Phone Single 0-08
 PS 44 Phone Double 0-10
 PS 46 Co-Axial Surface 0-10
 PS 47 Co-Axial Flush 0-20

LEADS

LR 1 Speaker lead 3 pin D.I.N. plug to open ends approx. 3 metres long (coiled) 0-20

CABLES

CP 1 Single Lapped Screen 0-07
 CP 2 Twin Screened 0-11
 CP 3 Stereo Screened 0-12
 CP 4 Four Core Common Screen 0-28
 CP 5 Four Core Individually Screened 0-30
 CP 6 Microphone Fully Braided Cable 0-10
 CP 7 Three Core Mains Cable 0-09
 CP 8 Twin Oval Mains Cable 0-07
 CP 9 Speaker Cable 0-05
 CP 10 Low Loss Co-Axial 0-12

CARBON POTENTIOMETERS

Log and Lin
 47K, 10K, 22K, 47K, 100K, 220K, 470K, 1M, 2M
 VC 1 Single Less Switch 0-15
 VC 2 Single D.P. Switch 0-28
 VC 3 Tandem Less Switch 0-40
 VC 4 JK Lin Less Switch 0-15
 VC 5 100K Log anti-Log 0-40

HORIZONTAL CARBON PRESETS

0-1 watt 0-06 each
 100, 220, 470, 1K, 2.2K, 4.7K, 10K, 22K, 47K, 100K, 220K, 470K, 1M, 2M, 4.7M

IT'S NEW IT'S POWERFUL AND IT LOOKS GOOD!



(15 + 15w R.M.S.)
ORDER NOW— ONLY £39.95 p & p 50p.
 Or write for full details

WORLD SCOOP JUMBO SEMICONDUCTOR PACK

Transistors—German and Silicon Rectifiers
 Diodes—Triacs—Thyristors—IC's and
 Zeners ALL NEW AND CODED.
APPROX 100 PIECES
 Offering the amateur a fantastic bargain Pak and an enormous saving—identification and data sheet in every Pak.
Only £2 p. & p. 20p

RECORD STORAGE/CARRY CASES

7" KP, 181" x 7" x 8", 150 records) £2.10
 12" LP, 181" x 7 1/2" x 10 1/2", (50 records) £2.95

CASSETTE CASES

Holds 12, 10" x 3 1/2" x 5", Lock & Handle. £1.90

SPECIAL PURCHASE

2N3055, Silicon Power Transistors NPN. Famous manufacturers out-of-spec devices free from open and short defects—every one tested 115v, 200, Metal base.
OUR SPECIAL PRICE 8 for 4!

LOW COST CAPACITORS

0.01µF 40v. 5p each
 600µF 60v. Electro. 10p each

REPANCO TRANSFORMERS

240v. Primary. Secondary voltages available from selected tapplings 4v, 7v, 8v, 10v, 14v, 15v, 17v, 19v, 21v, 25v, 31v, 33v, 40, 50 and 55v-0-25v.

Type	Amps.	Price	P & P
MT50/1	1	£1.95	80p
MT50/1	1	£2.49	85p
MT50/2	2	£3.30	40p

CARTRIDGES

AC08
 H993-1 250mV at 120m/sec £1.85
 H993-1 250mV at 1m/sec £1.85
 H994-1 100mV at 1m/sec £2.80
 TTC
 J-2005 Crystal/Hi Output £1.05
 J-3010C " " " " " " £1.20
 J-3005 Stereo/Hi Output £1.20
 J-2105 Ceramic/Std Output £1.75
 J-2203 Magnetic 5mV/cm/sec, including stylus £4.95
 J-2203B Replacement stylus for above £3.00
 AT-75 Audio-technica magnetic cartridge 4mV/cm/sec £3.80

CARBON FILM RESISTORS

The E12 Range of Carbon Film Resistors, 1/8th watt available in PAKS of 50 pieces, assorted into the following groups—
 R1 60 Mixed 100 ohms-820 ohms 50p
 R2 50 Mixed 1K ohms-82K ohms 50p
 R3 50 Mixed 10K ohms-82K ohms 50p
 R4 50 Mixed 100K ohms-1 Meg. ohms 50p
THESE ARE UNBEATABLE PRICES—JUST 1p EACH INCL. V.A.T.

BI-PAK SUPERIOR QUALITY LOW - NOISE CASSETTES

CGO, 86p C90, 48p C120, 80p


VISIT OUR COMPONENT SHOP
 18 BALDOCK ST., WARE, Herts. (A10)

Open Mon, Sat. 9-5.30 p.m. Tel. 61593

-the lowest prices!

BI-PAK QUALITY COMES TO AUDIO!

AL10/AL20/AL30 AUDIO AMPLIFIER MODULES

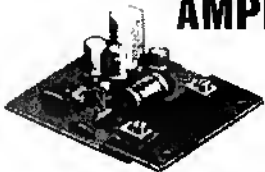

The AL10, AL20 and AL30 units are similar in their appearance and in their general specifications. However, careful selection of the plastic power devices has resulted in a range of output powers from 3 to 10 watts R.M.S. The versatility of their design makes them ideal for use in record players, tape recorders, stereo amplifiers and cassette and cartridge tape players in the car and at home.

Parameter	Conditions	Performance
HARMONIC DISTORTION	$P_o = 3 \text{ WATTS } f = 1\text{KHz}$	0-25%
LOAD IMPEDANCE	—	8-16 Ω
INPUT IMPEDANCE	$f = 1\text{KHz}$	100 k Ω
FREQUENCY RESPONSE $\pm 3\text{dB}$	$P_o = 2 \text{ WATTS}$	50 Hz - 20KHz
SENSITIVITY for RATED O/P	$V_s = 28\text{V}, R_L = 8 \Omega f = 1\text{KHz}$	75mV R.M.S.
DIMENSIONS	—	3" x 2 1/2" x 1"

The above table relates to the AL10, AL20 and AL30 modules. The following table outlines the differences in their working conditions.

Parameter	AL10	AL20	AL30
Maximum Supply Voltage	25	30	30
Power output for 2% T.H.D. (RL = 8 Ω f = 1 KHz)	3 watts R.M.S. Min.	5 watts R.M.S. Min.	10 watts R.M.S. Min.

AUDIO AMPLIFIER MODULES
 AL 10. 3 watts R.M.S. £2.50
 AL 20. 5 watts R.M.S. £2.55
 AL 30. 10 watts R.M.S. £2.50

PRE-AMPLIFIERS

PA 12. (Use with AL10, AL20 & AL30) £4.25
 PA 100. (Use with AL60) £18.15

TRANSFORMERS

T461 (Use with AL10) £1.60 P & P 15p
 T838 (Use with AL20, AL30) £2.30 P & P 15p
 BMT80 (Use with AL60) £2.75 P & P 25p

PA 12. PRE-AMPLIFIER SPECIFICATION

The PA 12 pre-amplifier has been designed to match into most budget stereo systems. It is compatible with the AL 10, AL 20 and AL 30 audio power amplifiers and it can be supplied from their associated power supplies. There are two stereo inputs, one has been designed for use with Ceramic cartridges while the auxiliary input will suit most Magnetic cartridges. Full details are given in the specification table. The four controls are, from left to right: Volume and on/off switch, balance, bass and treble. Size 102mm x 84mm x 35mm.

Frequency response-- 20Hz - 50KHz ($\pm 3\text{dB}$)
 Bass control-- $\pm 32\text{dB}$ at 60Hz
 Treble control-- $\pm 14\text{dB}$ at 14KHz
 *Input 1. Impedance 1 Meg. ohm
 Sensitivity 500mV
 †Input 2. Impedance 30 K ohms
 Sensitivity 4mV


Look for our

SEMICONDUCTOR ADVERTISEMENTS in
 Practical Wireless Wireless World Radio Constructor

ALL PRICES INCLUDE V.A.T.

The STEREO 20

The 'Stereo 20' amplifier is mounted, ready wired and tested on a one-piece chassis measuring 20 cm x 14 cm x 5.5 cm. This compact unit comes complete with on/off switch, volume control, balance, bass and treble controls, Transformer, Power supply and Power amps. Attractively printed front panel and matching control knobs. The 'Stereo 20' has been designed to fit into most turntable plinths without interfering with the mechanism or alternatively, into a separate cabinet. Output power, 20w peak. Input 1 (Cer.) 300mV into 1M. Freq. res. 20Hz-25KHz. Input 2 (Aux.) 4mV into 30K. Harmonic distortion. Bass control $\pm 32\text{dB}$ at 60Hz typically 0-25% at 1 watt. Treble con. $\pm 14\text{dB}$ at 14KHz.

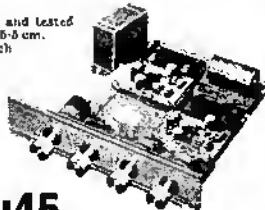

£14.45

TC20 TEAK VENEERED CABINET

For Stereo 20 (front board omitted) size 10 1/2" x 8 1/2" x 3", £3.95, plus 30p postage

SHP80 STEREO HEADPHONES

4-16 ohms impedance. Frequency response 20 to 20,000Hz Stereo/mono switch and volume control £4.95

NOW WE GIVE YOU 50w PEAK (25w R.M.S.) PLUS THERMAL PROTECTION! The NEW AL60 Hi-Fi Audio Amplifier FOR ONLY £4.25

- Max Heat Sink temp. 90°C.
- Frequency Response 20Hz to 100KHz
- Distortion better than 0.1% at 0-1KHz
- Supply voltage 15-50 volts

- Thermal Feedback
- Latest Design Improvements
- Load—3, 4, 8 or 16 ohms
- Signal to noise ratio 80dB
- Overall size 63mm x 105mm x 13mm

Especially designed to a strict specification. Only the finest components have been used and the latest solid state circuitry incorporated in this powerful little amplifier which should satisfy the most critical A.F. enthusiast.



STABILISED POWER MODULE SPM80

SPM80 is especially designed to power 2 of the AL60 Amplifiers, up to 15 watt (r.m.s.) per channel simultaneously. This module embodies the latest components and circuit techniques incorporating complete short circuit protection. With the addition of the Mains Transformer BMT80, this unit will provide outputs of up to 1-3 amps at 35 volts. Size: 63mm x 105mm x 30mm. These units enable you to build Audio Systems of the highest quality at a hitherto unobtainable price. Also ideal for many other applications including—Disc Systems, Public Address Intercom Units, etc. Handbook available 10p PRICE £3.25

TRANSFORMER BMT80 £2-15 p. & p. 28p

STEREO PRE-AMPLIFIER TYPE PA100

Built to a specification and NOT a price, and yet still the greatest value on the market, the PA100 stereo pre-amplifier has been conceived from the latest circuit techniques. Designed for use with the AL50 power amplifier system, this quality radio unit incorporates no less than eight silicon planar transistors, two of these are specially selected low noise NPN devices for use in the input stages. Three switched stereo inputs, and rumble and scratch filters are features of the PA100 which also has a STEREO/MONO switch, volume, balance and continuously variable bass and treble controls.



SPECIFICATION

Frequency Response 20Hz - 20KHz $\pm 3\text{dB}$ better than 0.1%
 Harmonic Distortion 3-25 mV into 50K Ω
 Inputs: 1. Tape Head 75 mV into 50K Ω
 2. Radio, Tuner 3 mV into 50K Ω
 3. Magnetic P.U. 3 mV into 50K Ω
 All input voltages are for an output of 250mV. Tape and P.U. inputs regulated to RIAA curve within $\pm 1\text{dB}$. from 20Hz to 20KHz.
 Bass Control $\pm 15\text{dB}$ at 20Hz
 Treble Control $\pm 15\text{dB}$ at 20 KHz
 Filters: Rumble (High Pass) 100Hz
 Scratch (Low Pass) 8KHz
 Signal/Noise Ratio better than - 65dB
 † 28V
 † 35 volts at 20mA
 Supply 252mm x 82mm x 35mm
 Dimensions ONLY £14.25

MK 60 AUDIO KIT

Comprising: 2 x AL60, 1 x SPM80, 1 x BMT80, 1 x PA 100, 1 front panel, 1 kit of parts to include on-off switch, neon indicator, stereo headphone sockets plus instruction booklet. Complete Price: £28.75 plus 30p postage

TEAK 60 AUDIO KIT

Comprising: Teak veneered cabinet size 10 1/2" x 11 1/2" x 3 1/2", other parts include aluminium chassis, heatsink and front panel bracket, plus back panel and appropriate sockets etc. Kit price: £29.50 plus 30p postage

Giro No. 388-7006

Please send all orders direct to warehouse and despatch department

BI-PAK

P.O. BOX 6, WARE, HERTS

Postage and packing add 11p. Overseas add extra for airmail.
 Minimum order 55p. Cash with order please.
 Guaranteed Satisfaction or Money Back

POLLUTION

WHEN Samuel Morse first pressed his key and sent the letter 'A' (dit-dah) he heralded the start of communication by a method now universally referred to as the Morse Code.

In the days of the spark transmitter and coherer receiver radio communication was fraught with many problems. Atmospheric conditions, electrical storms and static were about the only phenomena that inhibited etheric communication. The spark transmitter with its familiar "buzz" spreading over a wide band of frequencies certainly made life easy on the receiving side—no tuning was required—it was possible to receive many stations all at the same time.

With the advancement of radio communication techniques and the introduction of the superheterodyne receiver, the art of communication by *wireless waves* has become commonplace. Our readers who monitor the many wavebands for one reason or the other, surely have cursed when reception has been all but obliterated by man-made electrical interference of one kind or the other. Interference of this nature is widespread and is on the increase. The introduction of a multitude of devices that produce electrical arcing or sparking either when switches or electric motors are operated all add to the levels of electronic pollution. The short wavebands are polluted with a proliferation of garbling jammers running RF output powers in the megawatt region. The orbital scrapyard surrounding Mother Earth is rapidly filling with devices emitting weird noises and interference to our radio telescopes is on the increase.

We were told that VHF FM broadcasting would be the answer to the medium wave interference problem. We now find that the VHF FM band is a truly excellent medium for the reception of every piece of electrical interference in the neighbourhood. Thermostats, boilerstats on gas-fired domestic systems, fridges, washing machines, hairdryers, sewing machines—the list is endless. One *device* that causes interference over a wide band (from long waves to the 10m band and beyond) is the modern TV receiver—especially the more recent models that incorporate thyristor switching in the line timebase output circuit, which is now a most virulent source of "electronic pollution". This also applies to domestic thyristor lighting dimmers and thyristor/triac psychedelic lighting displays for the home and discotheque. It would appear that we are really up against it. One step forward in one field of technology inevitably results in a backward step for the listener wherever he may be! We all contribute in one way or the other to the levels of "electronic pollution".

The Post Office will investigate certain forms of interference—a pamphlet* is available at most post offices—but before we all deluge the P.O. with unnecessary moans, read the leaflet carefully and ascertain whether your "electronic pollution" problems are covered by existing legislation.

You never know—you may be the offender yourself!

LIONEL E. HOWES—Editor.

* Good Radio and Television Reception—Form T113G.

NEWS...

45W UHF Transistor

LATEST in the series of UHF power transistors from Motorola is the MRF621. Designed for 12.5V operation between 406 and 512MHz, the MRF621 forms an ideal basis for power amplifiers in commercial/industrial u.h.f. mobile radio equipment. This advanced device will provide 45W Pout at 470MHz with a 12.5V collector supply. At rated power output minimum power gain is 4.8dB with a collector efficiency of 55% minimum. No degradation in output power occurs when working into a 20:1 VSWR at any phase angle.

Sonab wins Design Award

FOUR products in the current range of Sonab hifi equipment have received Design Awards for 1974 from the Swedish Society of Industrial Designers (SID).

The award-winning Sonab products are the R4000 tuner-amplifier; the 0A12 pair of loudspeakers; the 55S turntable and H20 headphones—all designed for Sonab by Lars Lallerstedt.

Scottish stereo

FROM the start of programmes last October, some of Radio Scotland's music and light entertainment programmes and certain Radio 4 items were being broadcast in stereo from the Kirk o'Shotts v.h.f. transmitter. Radio 2 and Radio 3 were already in stereo.

The stereo signals are re-broadcast by the relay stations at Ashkirk (serving much of the Border country), Ayr, Campbeltown, Forfar (covering most of Angus), Lochgilphead, Perth, Pitlochry, Millburn Muir (Vale of Leven), Rosneath (Gareloch) and Toward. Some of these stations are a long way from Kirk o'Shotts and the quality and consistency of the re-broadcast stereo signals will not be known for some time, after tests have been carried out.

Canadian tower

A £1.25 million contract to equip the new third-of-a-mile CN observation and communications tower in Toronto, Canada, with a complete antenna complex for all f.m. and TV broadcasting services has been won by the Telecommunications Division of EMI Ltd, Hayes, Middlesex.

When completed, the 1805 foot high CN tower in Toronto will be the tallest self-supporting structure in the world. The antenna system surmounting the main concrete tower will be carried on a 220 ton needle-shaped steel structure over 300 feet tall.

Transmissions from this height give major benefits in range and the elimination of "ghosting" but, at over 1500 feet, the arduous climatic conditions found normally even at ground level during the Canadian winter are aggravated by extremely severe icing, snow and high winds. For this reason, an important part of the contract comprised the provision of a glass reinforced plastic radome. This will be designed and constructed in Britain by Hunting Industrial Plastics Ltd, and erected to protect the mast structure during the winter.

The complete installation to be provided by EMI comprises a formation of four arrays arranged as follows:—Channel 5, Canadian Broadcasting Corporation. Intended for colour TV transmissions, this is a single channel, directional v.h.f. antenna having a gain of 8. The array is 55 feet tall and is at a mean height of 1,572 feet. Channel 9, CFTO-TV Ltd. Also intended for colour TV transmissions this second directional v.h.f. is similar to that for channel 5, but has a gain of 11 radiated from a 49 foot high array located at a mean height of 1,635 feet. Channel 19 and 25, CBC and Educational. An omnidirectional u.h.f. array for colour TV. It is arranged as a dual antenna, with one channel allocated to CBC and the second to the educational transmissions. Positioned on the mast at a mean height of 1,695

feet, this array is 60 feet tall and has a gain of 31. FM Transmissions. The master f.m. antenna occupies the lowest section of the mast, and has a mean height of 1,513 feet. Measuring 60 feet high by 26 feet diameter, this antenna is being manufactured under licence from Alford Manufacturing Co of the USA, and is based upon those supplied for the Empire State Building and Hancock Tower, Chicago.


The array comprises a high-power circularly polarised antenna, and enables the simultaneous transmission of eleven f.m. sound broadcasts. Although not yet allocated, provision is also being made for two further arrays to accommodate channels 45, 51 and 57 and channel 79. These will comprise a 50 foot long, three channel u.h.f. array for channels 45, 51 and 57, with a 25 foot long by 5 foot diameter omnidirectional type u.h.f. array for channel 79.

On the f.m. array cross dipoles are employed, whilst channels 5 and 9 are equipped with conventional dipoles. Additionally, the channel 19 and 25 array is provided with Emislot panels, and provision is made for these panels on the two remaining arrays.

The tower (pictured Aug. 15).
Below: the tower compared with other buildings.



1800

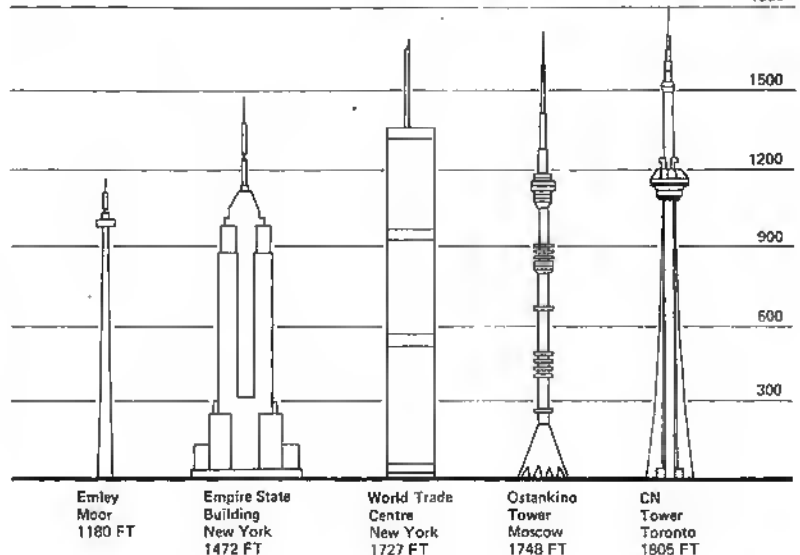

ELECTRONIC HOME TELEPHONE EXCHANGE

J. Thornton Lawrence T. Eng (C.E.I.)

SEVERAL mail order firms dealing in surplus electronic equipment are offering for sale, at very reasonable prices, ex G.P.O. telephones complete with dial and bell. Two of these telephones can be connected to provide ringing and speech communication between, for example, workshop and house, bedroom and downstairs, office and shop, etc. A simplified circuit of the telephone is shown in Fig. 1 and the method of connection in Fig. 2.

and heavy current through the LF choke. On releasing the dial, the "normally closed" dial contacts open and close ten times producing a substantial pulsing voltage across the line.

This voltage is passed through the bell series capacitor of the called telephone and rings the bell. When the dial comes to rest the N.O. contacts open and current again flows through the transmitter. The called subscriber lifts his handset and his transmitter is also energised.


During speech, variations in transmitter resistance will cause speech voltages to be developed across the line and incoming speech voltages will operate the receiver (earphone). The LF choke provides a direct current path to energise the transmitters whilst presenting a high AC impedance to the speech signals.

The dial pulsing rate is different from the frequency normally used for ringing the bell and some improvement in ringing can be made by suitable adjustment to the bells. To do this the base of the telephone should be removed. The bell fixing hole is made off-centre and loosening the fixing screw will allow the bell to be rotated, then tightened, to give the best sounding ring.

After using a simple two telephone system for some time the need was felt for a system incorporating several extensions and the automatic telephone exchange, which is the subject of this article, was developed. In the past, home telephone exchanges have used Uniselectors for calling and speech routing, but as the Unselector is very noisy in operation an alternative system was designed using solid state devices and reed relays. The reed relays are used for ringing purposes and the diodes used for speech routing.

TWO TELEPHONE OPERATION

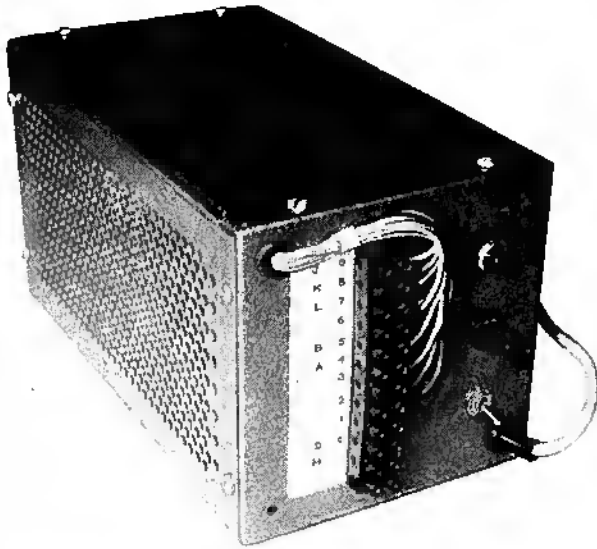
The two telephones are connected in parallel and fed with direct current through an LF choke as shown in Fig. 2. When calling, the caller lifts his handset and the rest contacts close thus energising



his transmitter (carbon microphone) as shown in Fig. 1. He then dials "0" and the "normally open" dial contacts close causing a short circuit across the line

SPEECH ROUTING

The basic arrangement of diodes for speech-routing is shown in Fig. 3. With the receivers at rest, the telephones draw no current and both diodes are non-conducting. If the handset is lifted at Subscriber 1, D13 will conduct and D14 will remain non-

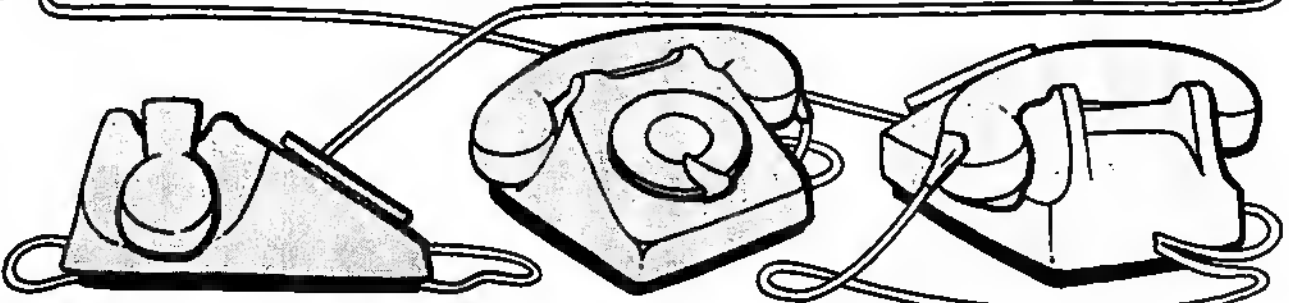

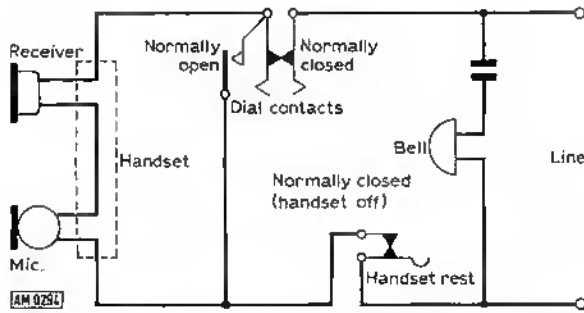


Fig. 1: With the handset lifted the contacts in a simple dial telephone circuit are in the position shown here.

★ components list

Resistors

R1 100Ω	R5 330Ω	R9 4.7kΩ
R2 330Ω	R6 330Ω	R10 4.7kΩ
R3 2.2kΩ	R7 1kΩ	R11 3.3kΩ
R4 2.2kΩ	R8 1kΩ	R12-20 47kΩ

All ½ watt 5%
 R21 500Ω 2W WW
 R22 125Ω 5W WW
 VR1 50kΩ miniature preset, horizontal mounting

Capacitors

C1 50μF 6V	C6 0.1μF
C2 10μF 6V	C7 0.1μF
C3 200μF 6V	C8 4000μF 40V
C4 0.01μF	C9 8μF 250V
C5 100μF 6V	

Semiconductors

Tr1 BC184B	Tr2 BC214B	Tr3 BC184B
D1-22 1S44 (or 1N914)		IC1 7413
D23 VR475F (4.75V zener)		IC2 7490
D24 1S3007 (7V zener)		IC3 74121
D25 10DB1A (1A bridge rec.)		IC4 74145

Miscellaneous

F1 fuse 250mA anti-surge. F2 500mA fuse, F3 500mA fuse. L1 LF choke 3H 350Ω (see text). LP1 Mains neon indicator, RLA to RLJ Reed relays 700Ω (Doram 348-970). S1 DPST toggle. T1 transformer mains/16.3V (Doram 196-218). T2 transformer mains/20 + 20V (Doram 196-319). Case 5" x 5" x 8" long (Lektrokrit, Home Radio) or similar.

The PCB can be obtained from J. Stuart, 40 Aberconway Road, Prestatyn, Clwyd, LL19 9HL for £2 inclusive of post and packing.

conducting because of the associated resistor R13 maintaining line 2 at the battery supply voltage.

If Subscriber 2 handset is now lifted D14 will now also conduct and speech communication can take place through D13 and D14, the LF choke being the common impedance as before.

RINGING SYSTEM

The simplified arrangement for ringing is shown in Fig. 4. When the handset is lifted at Sub. 1, D13 conducts as before and as the voltage on the line is greater than +7 volts D12 remains non-conductive. When the dial on Sub. 1 is operated, the line voltage falls to zero and D12 conducts and passes dialling pulses into the counting and ringing circuit.

If the caller, Sub. 1, has dialled "2," the counting and ringing circuit will energise reed relay Sub. 2 and cause a 60 volt peak-peak AC signal to be connected to line 2 thus ringing the bell at Sub. 2. As soon as the handset at Sub. 2 is lifted, D14 (omitted from Fig. 4 for clarity) conducts, allowing speech communication as described previously. A separate reed relay is required for each subscriber.

CIRCUIT OPERATION.

The full circuit is given in Fig. 5 and Fig. 6. The circuit operation begins when the caller lifts his handset. Assume that, as before, the caller is Sub. 1. When the handset is lifted, current will flow from the +20 volt supply through L1, D13 and Sub. 1 telephone to the common line, Fig. 6. This telephone is now energised and the voltage across the line is approximately 8 to 16 volts, depending on the total resistance of the telephone.

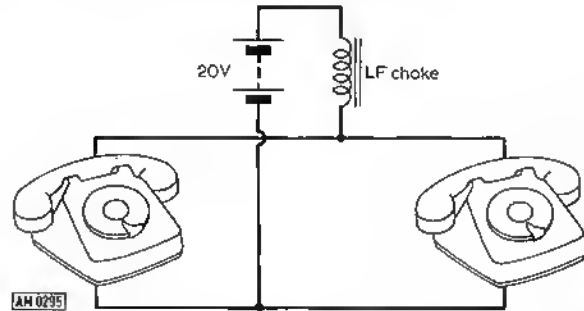


Fig. 2: Basic connections for a two telephone system.

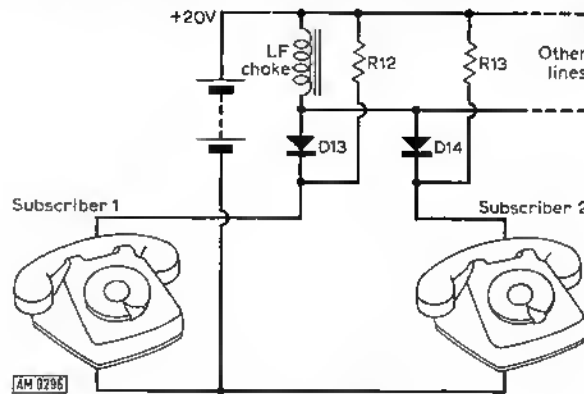


Fig. 3: Simplified speech switching circuit.

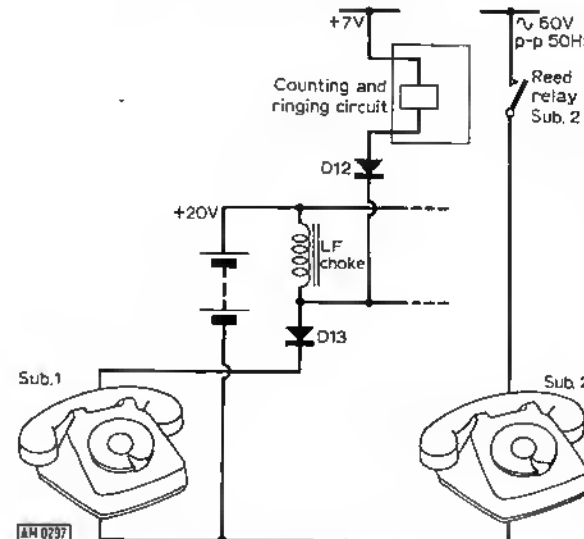


Fig. 4: Ringing circuit in a simple form.

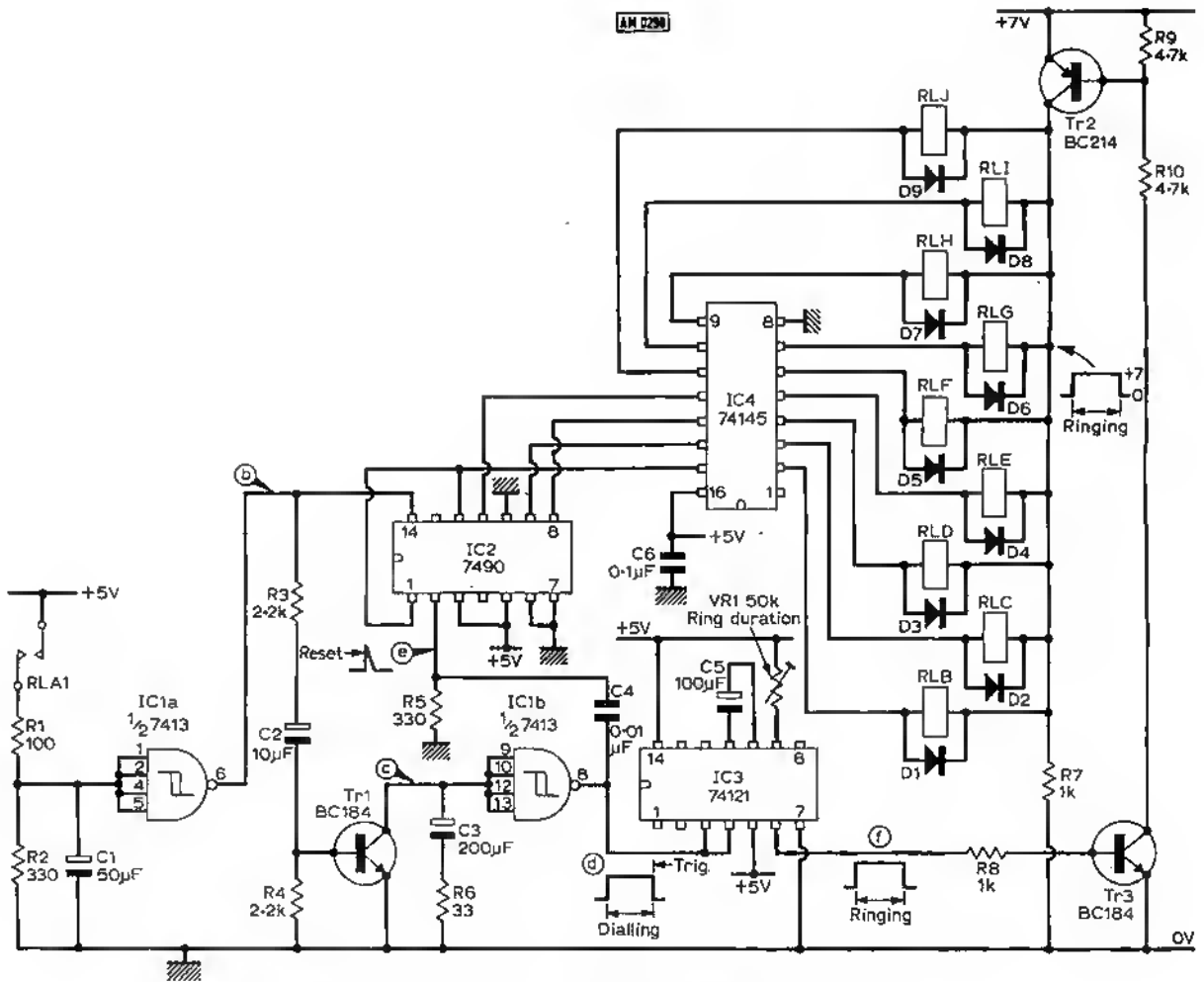


Fig. 5: Counting and ringing circuit in the exchange described in the text.

Assume that Sub. 1 dials Sub. 3. On the backward rotation of the dial, the line is shorted by the dialling contacts and the voltage across the line is zero. Current now flows through relay A, D12 and D13, thus energising relay A (Fig. 6). When Sub. 1 releases the dial it returns to rest and in so doing contacts open and short the line three times, finally coming to rest with the telephone energised as previously. The waveforms are shown in Fig. 8.

The contacts of relay A connect R1 to the +5 volt supply, Fig. 5, and a logic 1 level is applied to the Schmitt trigger gate IC1a. A Schmitt trigger is used in this position so that the input signal can be smoothed by R1, C1 to eliminate spurious signals caused by contact bounce and yet provide a fast-switching clean output suitable for driving the logic circuits. The output of IC1a, containing the dialled information now follows two routes, to Tr1 and IC2.

In order to detect the completion of a group of dialling pulses and to produce a signal at the end of this group it is necessary to have an electronic circuit equivalent to a "slugged" relay. This is formed by Tr1 and IC1b. The first of the dialling pulses turns Tr1 hard on, discharging C3 and causing the inputs of IC1b to be at logic 0 and thus the output of IC1b to be at logic 1. This positive transition is differentiated by C4 and R5 to produce a positive pulse to logic 1 which resets the 7490 decade counter to zero.

Between each dialling pulse C3 begins to recharge from the input current of IC1b but does not reach logic 1 level because the next dialling pulse discharges it again. However, after the last dialling pulse, the input to IC1b rises to logic 1 and the output flips to logic 0. The other route for the dialling pulses is direct to the input of the 7490 decade counter, IC2. The counter counts on the negative-going edge of each dialling pulse and in our example would count 3 (binary 0011).

It will be noted from the waveforms that a negative step (to logic 0) occurs when the dial is first rotated and this is counted by the decade counter, but as the counter is reset to zero on the leading edge of the first true dialling pulse, it does not cause a dialling error.

The binary coded decimal output from IC2 is fed directly to the 74145 decoder-driver, IC4, where, in our example, output 3 would be clamped to the 0v line and all other outputs would be non-conducting.

Returning now to IC1b, at the end of a group of dialling pulses, the output flips from logic 1 to logic 0. This negative transition triggers the 74121 monostable IC3, which produces a logic 1 output pulse having a duration set by VR1 (1.5 seconds approx.). The positive pulse from IC3 turns on Tr3 and Tr2, thus energising only relay D as this is connected to the 0v line through the No. 3 output of IC4.


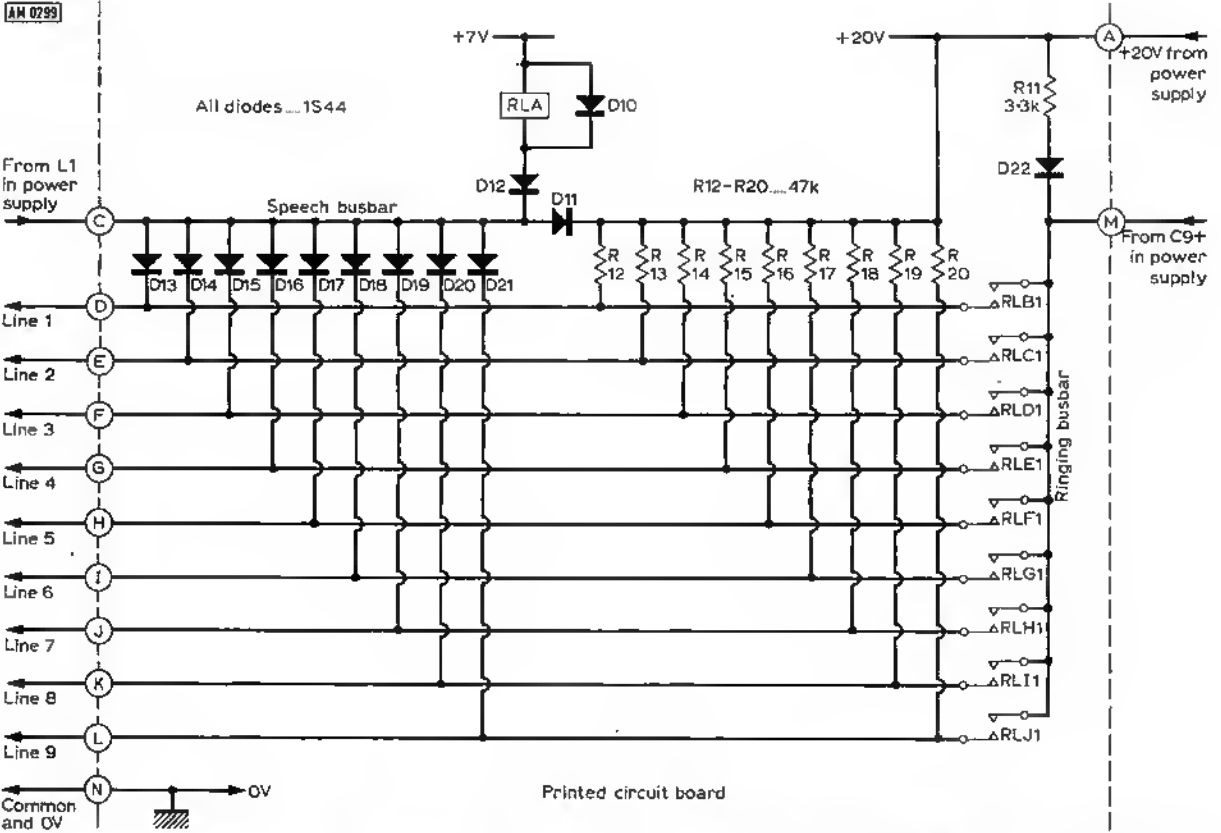
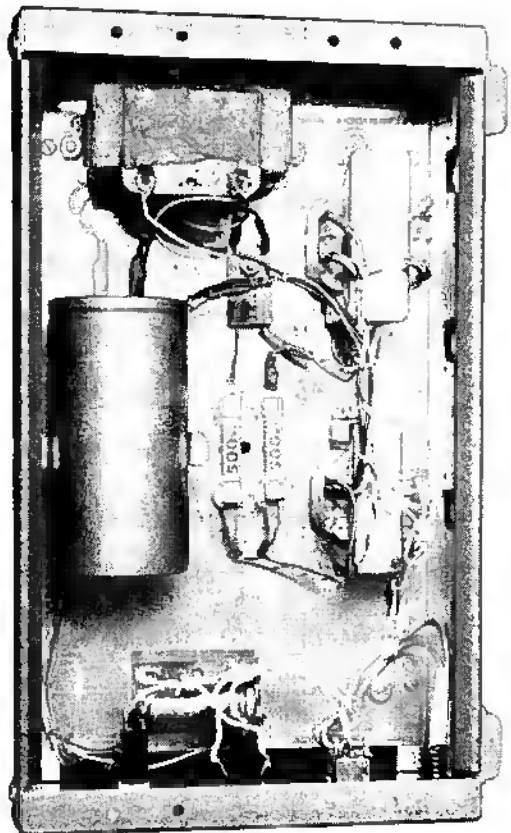


Fig. 6: Remainder of the exchange, showing the speech switching and ringing circuitry. Below left, the finished PCB of an earlier version of the exchange in which five IC's were used instead of four. Below right, power supply panel.

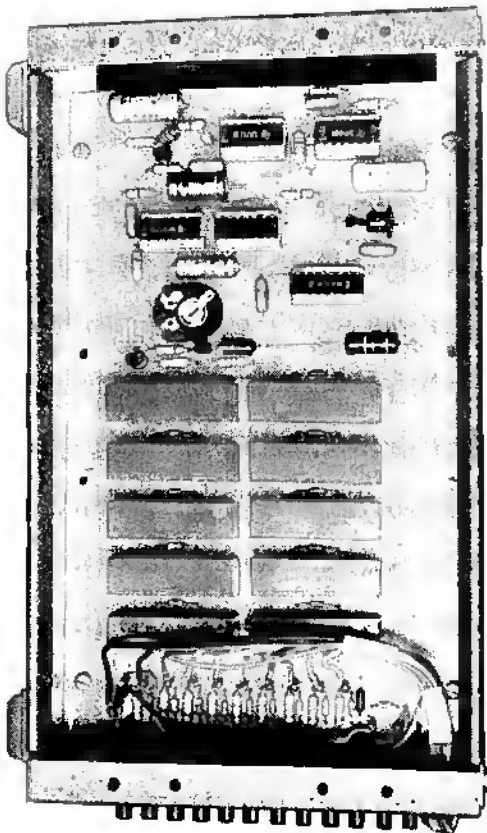

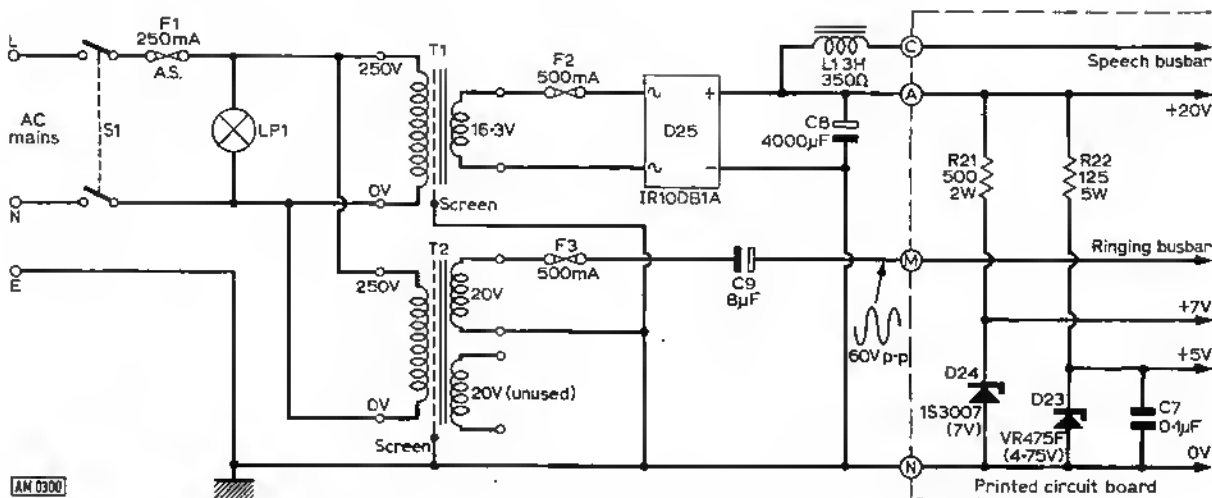


Fig. 7: Power supply circuit, the panel for which is mounted on the righthand side of the unit shown on the first page.

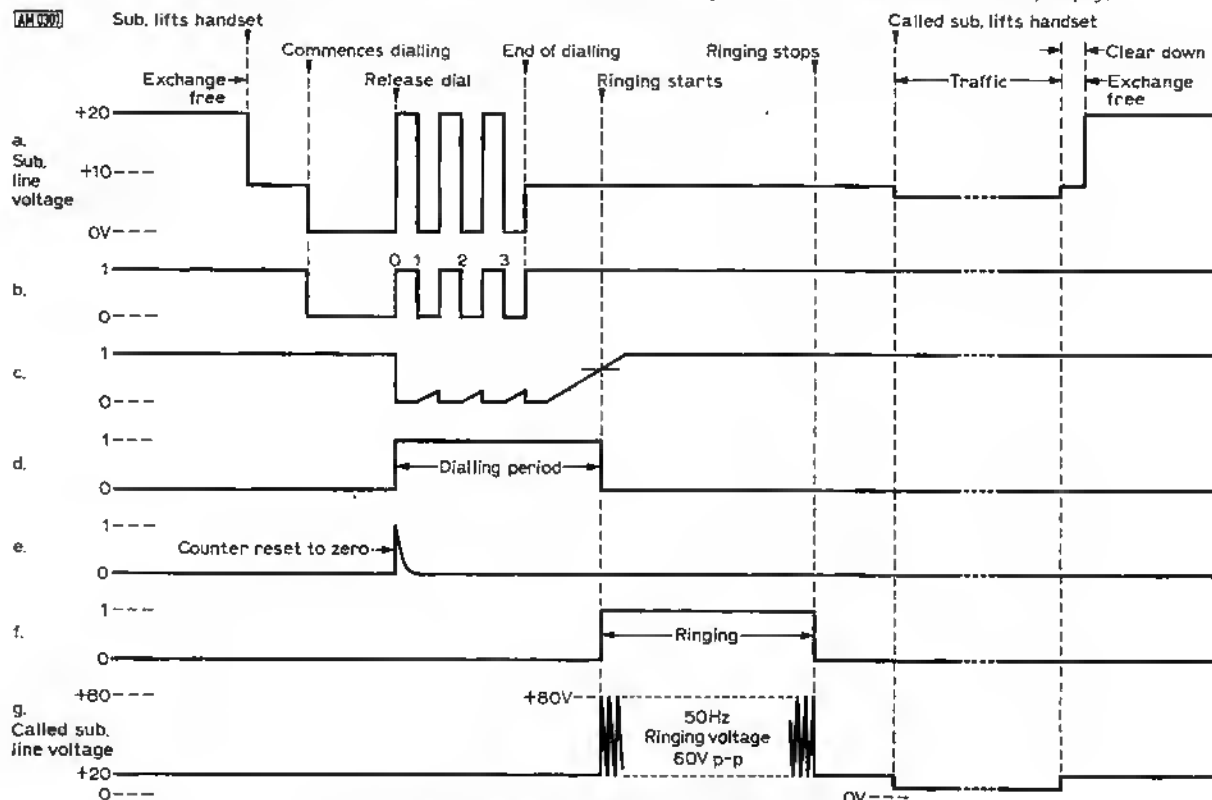


Fig. 8: Waveforms and timing diagram in the dialling sequence.

The reed relay D connects an AC ringing signal of 60 volts peak-peak from T2 to line 3 which rings the bell in Sub. 3 telephone for a duration set by VR1. When Sub. 3 lifts his handset, current flows through D15 thus connecting both telephones to the Speech Bus bar, permitting two-way conversation. At the completion of the call the caller and the called replace their hand sets causing D13 and D15 to disconnect. No other "clearing down" is required, the decade counter is reset to zero at the commencement of the next call.

The 50Hz ringing voltage from T2 is AC coupled to the Ringing Bus bar, by C9 and the negative peaks cause D22 to conduct, charging C9 and thus prevent-

ing the negative half cycles from swinging below +20 volts. This ensures that when the ringing signal from the Ringing Bus is connected to a subscriber it will not cause the associated speech routing diode to conduct and will prevent the ringing signal from appearing on the Speech Bus.

The inductance of the LF choke, L1, is not critical but the resistance should be approximately 350 ohms. If a choke of the correct resistance is not available, one having a lower resistance may be used with a suitable resistor connected in series to raise the total resistance to the correct value.

The power supply for the telephone exchange is in operation continuously and consumes approximately

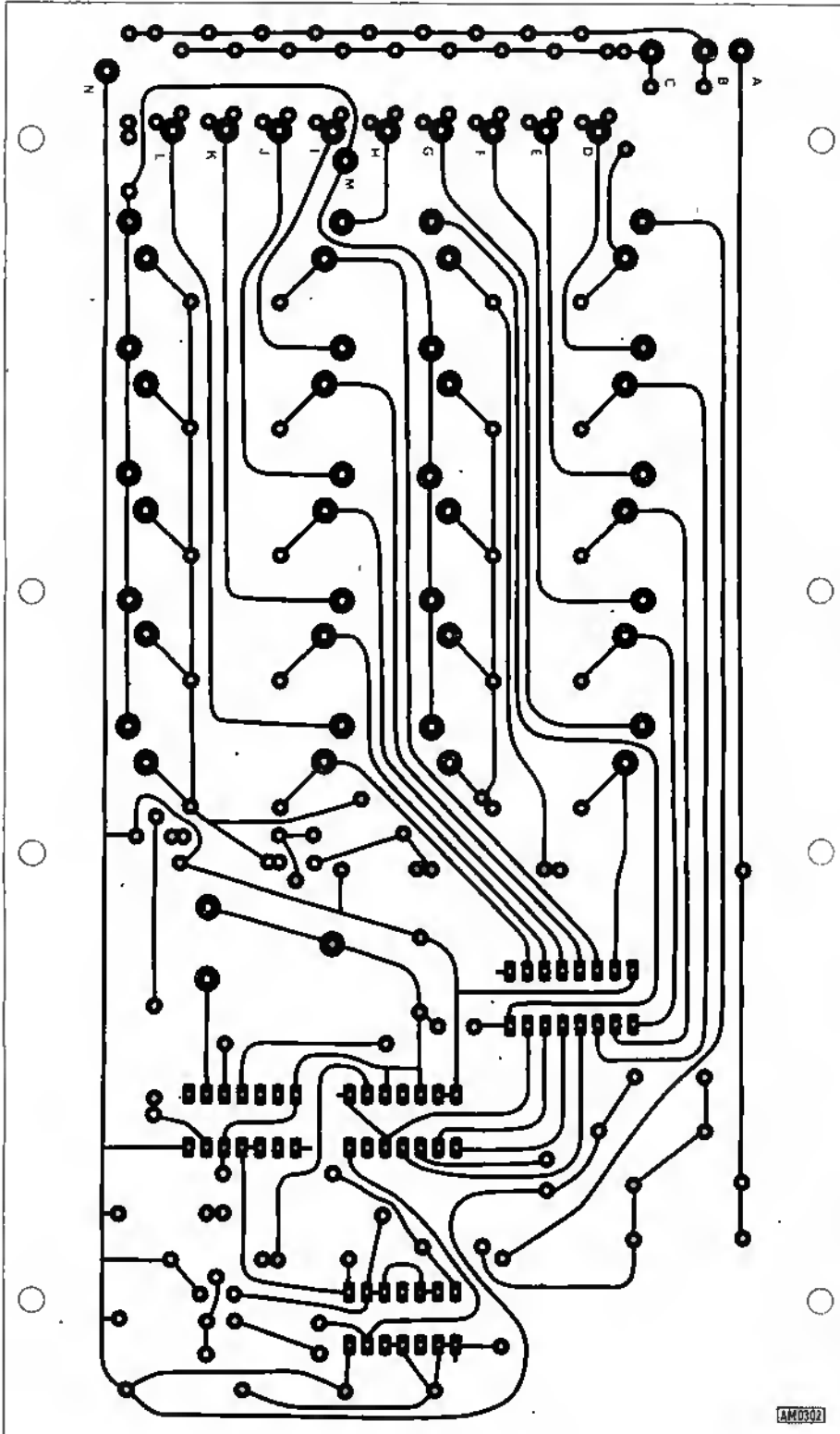


Fig. 9: The PCB layout is given here actual size so that it may be copied.

3 watts. Transformer T1, bridge rectifier D25 and C8 provide the +20 volt supply for powering the telephones and this is also the source of the +5 volt and +7 volt supplies which are regulated by zener/break-down diodes D23 and D24 respectively, Fig. 7.

Transformer T2 provides the ringing voltage for the Ringing Bus. Both transformers are adequately fused for safe unattended operation.

All the circuitry with the exception of the power supply components is built on a 8in x 4³/₄in printed

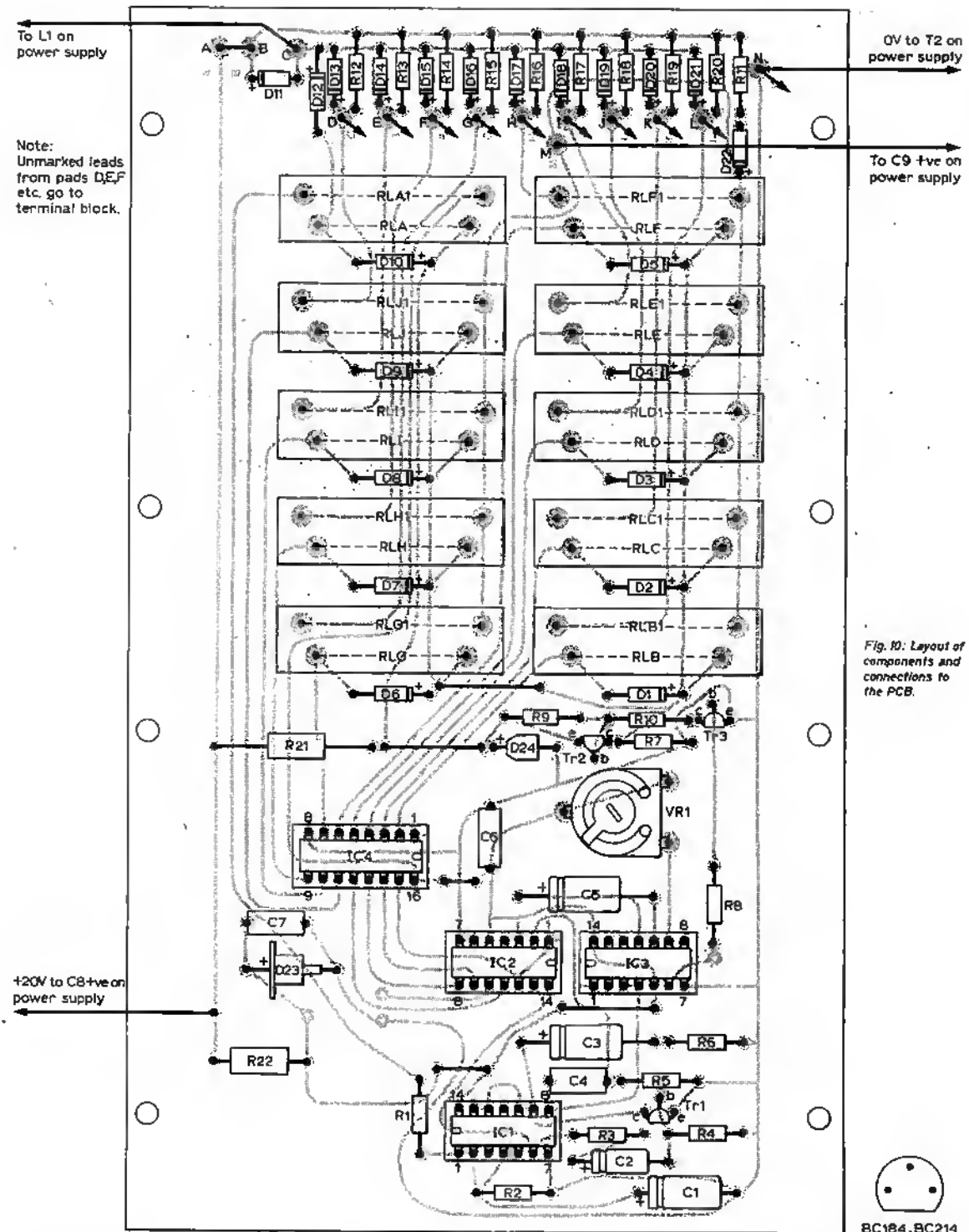


Fig. 10: Layout of components and connections to the PCB.

circuit board, Fig. 9/10. The power supply components are mounted on a similar sized metal plate and the complete unit is housed in a 5in x 5in case 8½in long, constructed from Lektrokit parts.

CONNECTION AND OPERATION

Each telephone is connected between the appropriate line terminal and the common line terminal. Dial-

ling is carried out in the usual way and VR1 may be adjusted to give the required length of ring. The telephone bells may be adjusted for best ringing as described previously.

The system has the advantage that when the two subscribers are in communication a further subscriber may be dialed and join in the conversation. Two telephones may be connected in parallel on one line if required.

Complete the coupon and we'll send you our new catalogue. Completely free.



The new Heathkit catalogue is now out. Full as ever with exciting, new models. To make building a Heathkit even more interesting and satisfying.

And, naturally, being Heathkit, every kit is absolutely complete. Right down to the last nut and bolt. So you won't find yourself embarrassingly short of a vital component on a Saturday evening--when the shops are shut.

You'll also get a very easy to understand instruction manual that takes you step by step through the assembly.

Clip the coupon now and we'll send you your free copy to browse through.

With the world's largest range of electronic kits to choose from, there really is something for everyone.

Including our full range of test equipment, amateur radio gear, hi-fi equipment and many general interest kits.


So, when you receive your catalogue you should have hours of pleasant reading.

And, if you happen to be in London or Gloucester, call in and see us. The London Heathkit Centre is at 233 Tottenham Court Road. The Gloucester showroom is next to our factory in Bristol Road.

At either one you'll be able to see for yourself the one thing the catalogue can't show you.

Namely, how well a completed Heathkit performs. Heath (Gloucester) Limited, Dept. PW-25, Bristol Road, Gloucester, GL2 6EE. Tel: Gloucester (0452) 29451.

AM/FM digital electronic clock-radio.

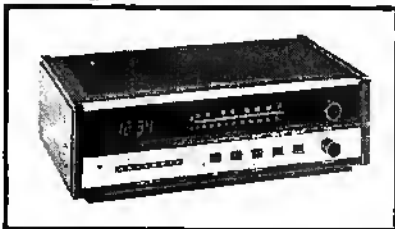

An oscilloscope from the Heathkit range.



Digital electronic car clock/elapsed timer.



The new Heathkit catalogue. Out now. FREE.

To: Heath (Gloucester) Limited, Dept. PW-25, Gloucester, GL2 6EE. Please send me my free Heathkit catalogue.

Name _____ Address _____

Postcode _____

Remember easy terms are available with the Heathkit Monthly Budget Plan.



no extras
all prices inc VAT
FREE delivery



ALL ITEMS SUBJECT TO
MANUFACTURERS INCREASE
AND AVAILABILITY
**Personal
Callers are
Welcome!**

**High Quality
Construction
Kits, stocked at
all branches
Send for
catalogue!**

AMPLIFIERS
Teleton SAQ3078 +8 watt £27-00
Rotel RA211 £43-95
RA311 £54-95
RA611 £86-95
Leak Delta 30 £54-75
Samsui AU101 £48-25
AU505 £74-95
Sinclair 2000 £34-95
Sinclair 4000 £45-95

TUNERS & RECEIVERS
Leak Delta AM/FM £58-75
Sinclair 2000/4000 Tuner £34-95
Rotel RT222 £42-75
Rotel RX150A Tuner/
Amp. £59-95
Rotel 152A £69-95
Samsui
210 AM/FM/MPX £84-25
310 AM/FM/MPX £99-50
350A AM/FM/MPX £106-95

RECORD DECKS
SP25 Mk III £11-00
Garrard SP25 MkIV £12-95
BSR MP60 £11-95
BSR Invicta P & C/SC7M £9-95
Garrard
SP25 MkIV P & C/G/800 £21-00
AP76 Module £30-00
Goldring GL78 P & C/
G800E £59-95
Connoisseur
BD1 Kit £13-50
BD2 Chassis/SAU2 £32-50
SAU2 £14-25
SCU1 £5-95

TAPE DECKS (Insurance 2-00)
Akai
4000DS Reel to Reel £93-95
4000DB Reel to Reel
Dolby £149-50
1721L Special Offer £77-95
GXC36D £82-00
GXC38D £103-95
CS33D £79-95
Akai CR81D 8-track Rec.
player £73-95

SPEAKERS
Chassis Speakers
EMI (Plain) 13in x 8in,
3, 8 or 15 ohm Bass unit £2-30
with Single Tweeter
(only 8ohm) £2-45
with Twin Tweeter £3-95
Type 350 Kit 15 watt 8 ohm £8-25
13in x 8in Bass unit
15 watt 8 ohm £4-95
8in x 5in 5 watt 3, 8 or
15 ohm £1-50
8in x 5in 10 watt
Dualcone 8 ohm £2-50
6 1/2" 10 watt 8 ohm £2-65
8in 10 watt 8 ohm £3-90
12in 20 watt 8 ohm £6-95
Fane 8in 4 or 15 ohm £2-25
Fane 7in x 4in 3 or 8 ohm £1-20
Elac 8in 8 ohm Dualcone £2-50
Elac 10in 8 ohm Dualcone £3-75
Goodman 6 1/2in 8 ohm
Dualcone £2-40
Baker Group 25 12in 8 or
15 ohm £7-95
Adastra "Top 20" 12in
25 watt 8 or 15 ohm £8-25

Adastra 'Hi-Ten' 10in
10 watt 8 or 15 ohm £3-60
Also 5in 8 ohm speaker £0-99
2 1/2in 8 or 64 ohm
speaker £0-50

WHARFEDALE SPEAKER
BARGAINS
Denton 1 pr. £26-75
Denton 2 pr. £32-00
Linton 2 pr. £40-75
Glendale 3 pr. £60-95
Kingsdale 3 ea. £44-95
Dovedale 3 ea. £44-95

KITS
Linton 2 pr. £20-95
Glendale 3 pr. £35-95
Dovedale £35-50

**SPEAKER CABINETS IN
KIT FORM (Teak Veneer)**
12in x 8in x 6in
(8 x 5 or 7 x 4 cutout) £2-50
14in x 12in x 9in
(10", 8 x 5, 8", 6 1/2" & 3 1/2") £3-75
18in x 14in x 9in
(8" x 7" or 13 x 8) £4-95
22in x 14in x 9in
(12" & 7" or 13 x 8) £6-25

TWEETERS & CROSSOVERS
EMI 3 1/2" c/magnet in 3 or
8 ohm £1-25
Cone Tweeter 10 watt
8 or 15 ohm (K2006) £2-70
Cone Tweeter 3 watt
8 ohm (K2003) £1-55
Horn Tweeter 8 ohm
(K2007) £6-50
Dome Tweeter 8 ohm
(K2011) £5-50
2-way Crossovers (CN23,
CN28, CN116) £1-30
3-way Crossover (CN38) £2-75

CARTRIDGES & STYLII
ACOS
GP91/25C or 3CS
(ster. comp) 1-10 1-25
GP93/1 or 95/1
ster. cryst. 1-35 1-25
GP94/1 or 96/1
ster. ceram. 1-75 1-25
GP101 cryst.
comp. 90 —
GP104 ster.
ceram. 1-75 1-25
BSR
XSM or XSH
cryst. comp. 1-75 1-25
SX6M or SX6H
cryst. ster. 2-00 1-25
SC5M ster. ceram. 2-75 1-25

SONOTONE
9TAHC or
9TAHC/G
(Oiam.) 1-85 1-25
3509 Magnetic 1-90 1-25
AUDIO TECNICA
AT55 1-95 —
EMPIRE 999 REX 3-95 —
GOLDRING
G850 2-95 1-95

G800 3-95 1-95
G800H 3-95 1-95
G800E 6-99 3-95
SHURE
M44G 4-95 3-95
M35E 6-25 4-95
M75EJ Type 2 11-75 8-25
M75EJ Type 2 9-75 6-25
V15 Type 3 32-25 —

MICROPHONES
UD130 50K/600 ohm
uni-dir. ball metal £5-95
UD147 £9-25
Condenser Mic. 600 ohm
uni-dir £9-50
Cassette Stick Mic. with
R/Control £1-60
Mic-Mixers Mono/stereo £5-50
AKAI ADM14 £5-95

HEADPHONES
Rotel
RH430 £4-75
RH 630 £7-75
RH 700 £11-50
Koss
K711 £10-95
KRO711 £10-95
K6 £11-50
K6LC £14-00
KO727B £16-00
KO747 £20-75
HVI £21-95
PRO4AA £26-95
PRO54 £29-95
K6LCQ £26-00
Samsui SS10 £14-20
Headphone adaptor
(Junction box) £2-50
extension lead 2ft curly £1-35

CASSETTES
C40 C60 C90 C120
Low Noise — 35p 45p 55p
Philips — 55p 75p 110p
Memorex 45p 75p 110p 155p
Ampex (360) 45p 55p 70p 99p
Ampex
(20-20+) 59p 65p 99p 135p
Chromium
Dioxide — 99p 140p —
Cassette Head Cleaner 45p
Ampex Head Cleaner/Damage £1-65
BIB Stereo Test Cassette £2-15
Cassette Racks (hold 6) £0-45
Cassette Rotating Racks
(hold 20) £3-50
Cassette Carrying Case
(BIB) (hold 12) £1-60
8-Track Cartridge Blanks
C40 C64 C80
Ampex 80p 95p £1-10
8-track H/Cleaner
Demagnetiser £1-90
8-track Carrying Cases
(BIB) £1-65

TAPES & CASSETTES
Std LP DP Cases
5" 55p 65p 1-00 20p
5 1/2" 65p 86p 1-35 25p
7" 80p 110p 1-85 30p
High frequency/Ampex
5" — 1-40p 1-55p
7" — 1-90p 2-95p
AKAI Metal Reel 7" £1-99

CALCULATORS
Sinclair Cambridge Build £19-95
Scientific £29-95

SINCLAIR PROJECT 80
Stereo Pre-amp. £11-95
Active Filter Unit £6-95
Z40 15 watt Amp £5-45
Z60 25 watt Amp £6-95
P25 Power Supply for 240 £4-98
P26 Power Supply for 240 £7-98
P28 Power Supply for 260 £7-98
FM Tuner £11-95
Stereo Decoder £7-45
Q16 Speaker £7-10

PORTABLE RADIOS
Vega Jade £5-75
Vega Zircon £8-25
Vega Sapphire £7-25
Vega VEF206 £13-95
Micado LM/MW/FM/5SW
Murphy
B833 MW/VHF £9-95
BA838 LW/MW/VHF
M/Batt £18-50
MAS003 Head Set
Radio LW £7-95
Bush
VTR165 LW/MW/VHF £22-00
VTR127 LW/MW/VHF £15-50
VTR178 VHF/MW/2SW/
AIR M/Batt £27-50
VTR 175 LW/MW/VHF £13-95
VTR188 LW/MW/VHF/
2SW M/Batt £31-95
BY5661 LW/MW/VHF £14-95

CLOCK RADIOS
Bush CR128 LW/MW £13-60
Bush CR132 MW/VHF £24-95
Murphy MV5600
MW/VHF £22-95

CASSETTE RECORDERS
Murphy BA206 £16-95
Bush TP66 M/Batt £25-75
Murphy BA200 M/Batt £22-75
Bush BT8504 (miniature) £25-50

RADIO CASSETTES
(Mains/Batt.)
Micado B155 AM/FM £25-95
Murphy BA209 MW/VHF £33-50

**STEREO RECORD PLAYER
& SYSTEM**
Bush SPR58 £29-50
Bush SPR59 £31-50
Bush A1005 £56-50
Hanimex H101 £39-95
Hanimex HRCS060 8-track
AM/FM/MPX + Speaker £116-95

CAR AUDIO
Bush Car Cassette BT8501 £34-75
Hitachi Car Radio
WM702R LW/MW £16-50
KM1510 LW/MW/VHF £32-50
Hitachi Car Cassette
CS114 £45-00

ALL ITEMS SUBJECT TO
MANUFACTURERS INCREASE
AND AVAILABILITY


**PERSONAL CALLERS
WELCOME**

ALL MERCHANDISE FULLY GUARANTEED

**NEWMART
ELECTRONICS**

Mail Order Dept **pw2**
Belmont St, Monton,
Eccles, Manchester.
Tel: 061-789 5268

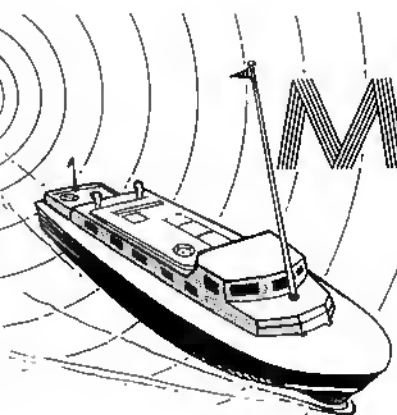Manchester
30-32 Shudehill. tel 061-832 7710
Leeds
4 New Market St tel 0532 42708
Liverpool
15 Whitechapel tel 051-236 0738



MODEL CONTROL

PART 2: THE CONTROLLER BY RADIO

F. G. RAYER G3OGR

A MODEL Control Licence is obtainable, without difficulty, on application, see panel, allowing operation in two bands 26.96-27.28MHz and 458.5-459.5MHz. Transmitting equipment for the 27MHz band is easily built and the transmitter described here is for this band and crystal controlled to ensure the frequency is within the band. The limitation on power is easily met since the circuit used is incapable of exceeding the power permitted. The type of emission A2 (modulated carrier) also falls within the licence conditions.

The transmitter may be used with a receiver of the type described in Part I but both transmitter and receiver are compatible with commercially made equipment using the same mode of control.

Equipment of this type is intended for the control of a land model, model boat or plane.

SYSTEM OF WORKING

This is a single channel of control to the model, with the equipment outlined in Fig. 1. The transmitter is hand held, with a push button which forms an on-off switch. Signals are radiated from a telescopic aerial and picked up by a short aerial on the model. The received signal closes a relay which in turn switches an electrical-mechanical device, termed the actuator, on or off. The actuator fitted in the large model boat used by the author allows switching on or off, or reversing, of the main propulsion motor by short blips. Turning the rudder to port or starboard is achieved with long blips, the rudder returning to straight ahead with no signal (transmitter button released). The boat can thus be started, stopped, turned either way, sailed straight ahead or astern.

The transmitter described here will operate with tone-controlled super-regenerative receivers. However, the receiver already described is crystal controlled since this has the advantages of stable operation on the required channel without the need for constant re-adjustment as well as freedom from interference by other radio controlled transmitters on adjacent frequencies.

AM 0284


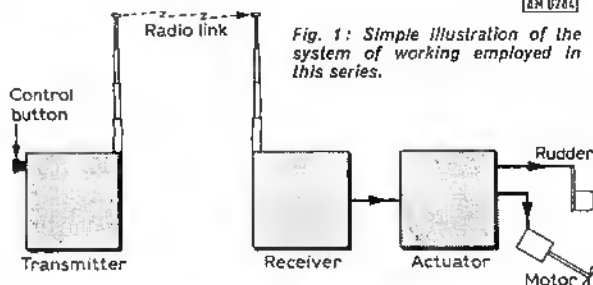


Fig. 1: Simple illustration of the system of working employed in this series.

TRANSMITTER CIRCUIT

This is shown in Fig. 2. Tr1 and Tr2 comprise the RF section while Tr3, Tr4 and Tr5 form the tone modulator circuit. Tr1 is the crystal controlled oscillator, the collector circuit being tuned to near resonance by the adjustable core of L1. This oscillator circuit proved to be reliable, with no critical adjustments required and it gave a good output.

The coupling winding L2 applies drive to the amplifier Tr2 whose collector coil L3 is also tuned. The coupling winding L4 energises the aerial. This circuit is designed for a 48in. telescopic aerial which is easily obtainable and does not prove to be unwieldy with a hand-held transmitter.

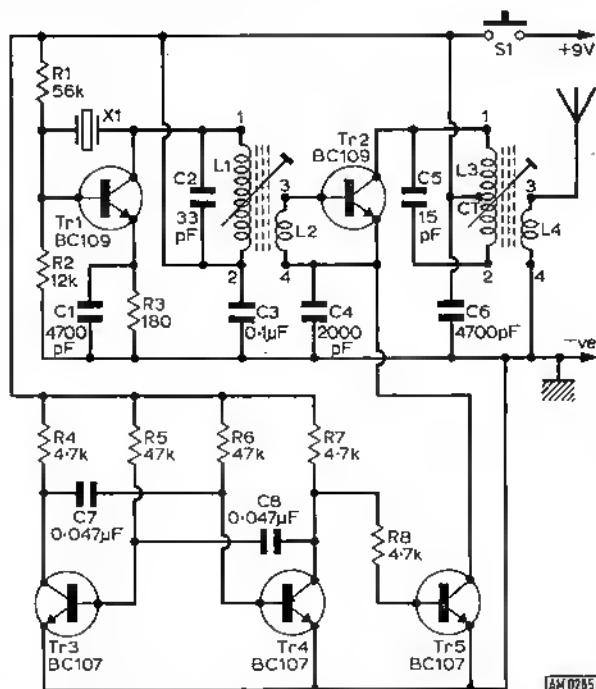


AM 0285

Fig. 2: Complete circuit of the five transistor transmitter.

Tr3 and Tr4 form the tone generator and, with the single channel receiver described, the frequency of the tone is not very important. Tr5 is alternatively driven in and out of conduction thus modulating the amplifier Tr2. This method avoids the need for a transformer or other components for modulation purposes.

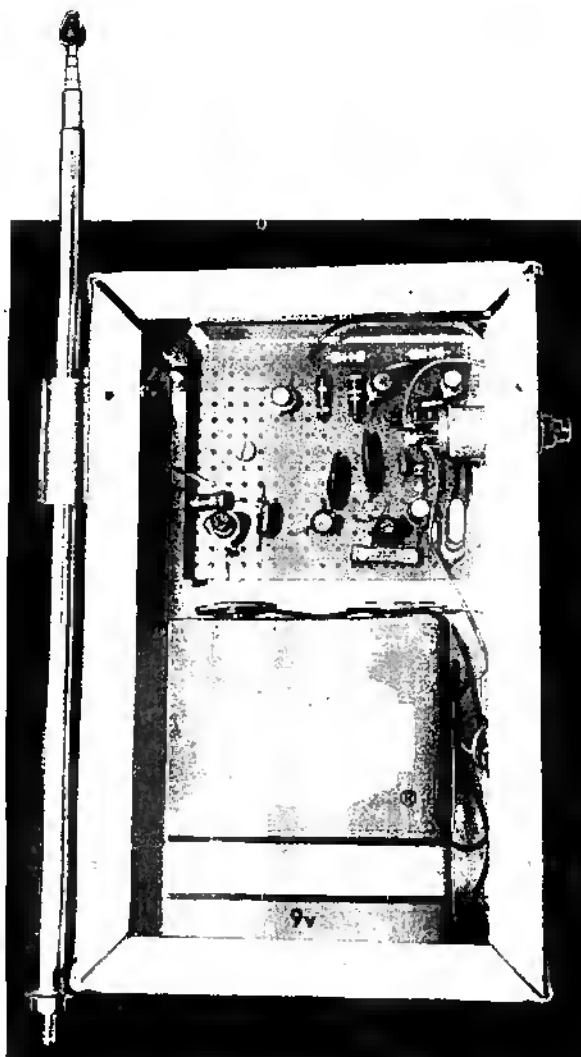The circuit is intended for use with a single PP9 battery which is fitted in the case. A 20in. aerial on



The front cover of the controller box is removed to show the transmitter circuit board.

the receiver and equipment at ground level was found to give reliable control easily in excess of 100 yards which was well outside the limit at which it was wished to observe and sail the model, even with the transmitter aerial not fully extended.

It should be noted that it is possible to increase power by increasing the battery voltage, provided dissipation in any stage does not exceed 300mW. Radiation may also be increased by placing a loading coil between pin 3 on L4 and the aerial, and space is left for this on the circuit board, though it was not required.


Note that the push-button S1 gives complete on-off switching of the transmitter so that no other switch is required. Where a single channel tone is used with a super-regenerative receiver it is usual to leave the transmitter RF carrier on continuously, to reduce the receiver response to interference or spurious operational signals. Should the transmitter be used for this purpose S1 should key only the modulation tone section, Tr1 and Tr2 operating continuously, an additional on-off switch being fitted in the battery circuit.

CRYSTAL FREQUENCIES

If a super-regenerative or tunable receiver is to be used with this transmitter any crystal in the 26.96 to 27.28MHz band will be suitable, as the receiver can be adjusted accordingly.

For the receiver described in Part 1 transmitter and receiver crystals are obtained as a pair the difference in frequency between them corresponding to the intermediate frequency of the receiver. For the receiver, this difference may be 455, 465 or 470kHz. The crystals actually used were 27.005MHz for the transmitter, and 27.460kHz for the receiver. However, the selectivity of the receiver plus crystal control permits the working of a number of transmitters without interference and pairs of crystals for various channels are obtainable.

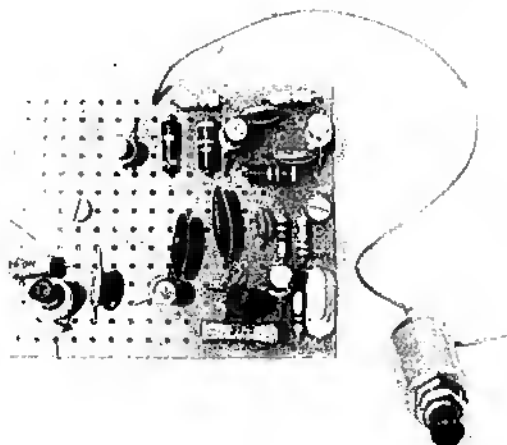Provided transmitter and receiver are working correctly together a change of frequency would only be needed where two or more models are used together and the transmitters chance to be on the same or adjacent frequencies.



The finished circuit board which should be tested and adjusted before fixing it into the case.

CONSTRUCTION

The board is about 2 $\frac{5}{8}$ x 2 $\frac{1}{4}$ in. and both sides are shown in Fig. 3. Drill holes for the crystal holder tags, for two bolts MC which are necessary to mount the

TAKE NOTE!

The use of radio for controlling a model is permitted only under the authority of a licence issued by the Home Office. This authorises the use of A1, A2, F1 and F2 emissions in the frequency band 26.96 to 27.28 MHz with a maximum effective radiated power of 1.5 watts and in the band 458.5 to 459.5 MHz with a maximum effective radiated power of 0.5 watt. The licence authorises the use of the apparatus anywhere in the UK and is valid for five years. Applications for the licence should be sent to:—Home Office (Radio Regulatory Division), Waterloo Bridge House, Waterloo Road, London SE1 8UA together with the fee of £1.50 NO EXAMINATION IS REQUIRED.



Now there's Doram, you need never wait for electronic components.

7-day service.

Buy the new Doram catalogue and you could have your components within 7 days of our receipt of your order.

If you don't, you'll have your money back and no questions asked.

What you won't get is a tedious wait. Which goes on. And on. And on. And on. You know just where you are with Doram.

Millions of components.

Doram is a brand-new deal for serious amateurs. It's a complete door-to-door components service operated by mail order.

You buy the Doram catalogue for 25p (that's a yearly reference book for the price of a pint) and then you order from it.

We're big enough to offer you stocks of millions of components on over 4,000 product lines.

And so confident of our service that if we can't supply the part you want within 7 days of receiving your order, we'll give you your money back. Immediately.

No-quibble guarantee.

It's just about impossible to buy a defective part from us. Because our checking is so pains-taking.

But even if the unthinkable does happen—and you're unlucky—then we'll still make you happy quickly.

Because we offer a no-quibble replacement part service.

And our guarantee is guaranteed by the fact that we belong to the biggest electronics distribution Group in Britain.

All branded goods.

All goods supplied are branded goods. Made by big-name manufacturers like RS, Mullard, SGS-ATES, Ferranti, Sico, etc.

www.americanradiohistory.com

Doram brings the amateur the sort of service only professionals have enjoyed before.

So don't delay. Use the coupon. Send today for your first Doram catalogue. It can make your life a whole lot easier.

For 25p that can't be bad, can it?

I ENCLOSE 25p* PLEASE SEND ME THE NEW DORAM CATALOGUE.


Name

Address

Doram Electronics Limited,
PO Box TR8,
Wellington Road Industrial Estate,
Wellington Bridge, Leeds LS12 2UF.

*This will be refunded on orders of £5 (less VAT) or more received by us before March 31st, 1975.

DORAM
PW/2/75

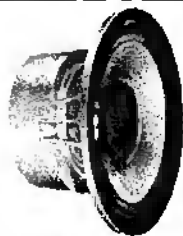

WILMSLOW AUDIO

THE Firm for speakers!

SPEAKERS

Baker Group 25 3, 8 or 15 ohm £7-75
 Baker Group 35 3, 8 or 15 ohm £8-50
 Baker Group 50/12 8 or 15 ohm £12-50
 Baker Deluxe 12" d/cone £10-75
 Baker Major " " £8-50
 Baker Regent £7-75
 Baker Supra £14-50
 Baker Auditorium 12 £12-50
 Celestion MH1000 horn £10-95
 Celestion PST8 for Unilux £2-55
 Celestion G12M 8 or 15 ohm £12-00
 Celestion G12H 8 or 15 ohm £15-00
 Celestion G15C 8 or 15 ohm £24-00
 Celestion G15C 8 or 15 ohm £33-00
 Coral 6 1/2" d/cone roll aurr. 8 ohm £2-50
 Coral 8" d/cone roll aurr. 8 ohm £3-25
 EMI 13 x 8 3, 8 or 15 ohm £2-25
 EMI 13 x 8 150 d/c 3, 8 or 15 ohm £2-50
 EMI 13 x 8 450 1/4w 3, 8 or 15 ohm £3-75
 EMI 13 x 8 type 350 8 or 15 ohm £4-25
 EMI 13 x 8 20 watt base £4-00
 EMI 6 1/2" 93850 4 or 8 ohm £3-00
 EMI 5" 98132CP 8 ohm £2-50
 EMI 8 x 5 d/cone roll aurr 10 watt £2-50
 EMI 2 1/2" tweeter 97492AT £65
 Eagle DT33 30 watt tweeter £3-45
 Eagle HT15 horn tweeter £3-80
 Eagle CT5 cone tweeter £1-75
 Eagle CT10 tweeter 8 or 16 ohm £2-55
 Eagle MHT10 horn tweeter £3-80
 Eagle crossover CN25, CN28, CN216 £1-50
 Eagle FR4 £2-30
 Eagle FR65 £8-35
 Eagle FR9 £10-95
 Elec 9 x 5, 59RM109 15 ohm, 59RM114 8 ohm £2-80
 Elec 6 1/2" 6RM171 d/c roll aurr. £3-50
 Elec 6 1/2" 6RM220 d/cone £2-80
 Elec 4" tweeter TW4 £1-21
 Elec 10" d/cone 10RM239 8 ohm £2-85
 Elec 8" BC5175 3 ohm £2-50
 Fane Pop 15 watt 12" £4-90
 Fane Pop 25/2 25 watt 12" £4-95
 Fane Pop 40 watt 10" £4-50
 Fane Pop 50 watt 12" £11-00
 Fane Pop 50 watt 12" £12-50
 Fane Pop 55 12" 60 watt £13-00
 Fane Pop 60 watt 15" £22-50
 Fane Pop 700 watt 18" £28-00
 Fane Crescendo 12A 100 watt 12" £28-00
 Fane Crescendo 12B base £28-00
 Fane Crescendo 15" 100 watt £34-00
 Fane Crescendo 18" 150 watt £48-50
 Fane 801T 8" d/c roll aurr. £7-00
 Fane 807T 8" d/c roll aurr. £3-85
 Fane 808T 8" d/c £2-75
 Fane 791 twin ribbon horn £35-00
 Fane 910 horn £12-75
 Fane 920 horn £33-00

Goodmans BP 8 or 15 ohm £5-00
 Goodmans 10P 8 or 15 ohm £5-30
 Goodmans 12P 8 or 15 ohm £12-95
 Goodmans 12P-D 8 or 15 ohm £19-75
 Goodmans 12P-G 8 or 15 ohm £13-75
 Goodmans Audiomax 12AX 100 watt £37-50
 Goodmans Audiomax 15AX £41-25
 Goodmans 15P 8 or 15 ohm £21-00
 Goodmans 18P 8 or 15 ohm £36-00
 Goodmans Midax 750 £10-00
 Goodmans Axent 100 tweeter £7-25
 Goodmans Audium 100 12" £12-00
 Goodmans Axiom 401 12" £17-25
 Goodmans Twinaxiom 8 £8-25
 Goodmans Twinaxiom 10 £9-00
 Kef T27 £5-25
 Kef T15 £8-00
 Kef B110 £7-25
 Kef B200 £8-25
 Kef B139 £14-25
 Kef DN8 £2-00
 Kef DN12 £4-95
 Kef DN13 £3-30
 STC4001G super tweeter £6-10
 Richard Allan CG8T 8" d/c 1/4 aurr. £4-35
 2 1/2" 84 ohm, 70mm 80 ohm, 70mm 8 ohm £4-35
 2 1/2" 75 ohm -50
 7" x 4" 3 or 8 ohm £1-40
 5" x 5" 3 or 8 ohm £1-50
 10" x 8" 3, 8 or 15 ohm £2-30

SPEAKER KITS

Baker Major Modula each £10-75
 Fane Mode One each £8-90
 Goodmans DIN 20 each £9-75
 Helma XLK 25 pair £22-00
 Helma XLK 30 pair £16-85
 Helma XLK 50 pair £31-95
 Keff1 2 each £24-75
 Keff1 3 each £26-75
 Richard Allan Twinkl each £8-95
 Richard Allan Triple 8 each £13-75
 Richard Allan Triple each £19-95
 Richard Allan Super Triple each £23-75
 Wharfedale Linton 2 kit pair £19-25
 Wharfedale Glendale 3 kit pair £34-60
 Wharfedale Dove Dale 3 kit pair £32-50

PA/DISCO AMPLIFIERS

(carr. and Ins. £t)

Baker Major 100 watt	£49-75
Linear 30/40	£30-00
Linear 40/60	£35-00
Linear 80/100	£58-00
Linear 100 watt slave	£44-00

Eagle PA range in stock—ask for catalogue.

Wire Wound Resistors. Our selection of mixed values. 30 for £1.50, 100 for £4.00.

Audio Amplifier Module. Mullard LP1173, output power, nominal 10 watt, supply voltage +24 volt, with data and circuit, £2.50.

Ferguson Stereogram Chassis Model 3357, all transistor, medium long, VHF/FM, 3 watts per channel S/M, with connection data, less tuning scale, £20.

Crystals HCU: 52-03333 MHz: 52-02500; 52-01667; 51-56667; 51-58330; 37-76250; 37-75000; 12-895-8; 12-891-6; 12-700-0; 9-458-33; 9-456-25; 9-455-55; 9-533-33; 9-531-94; 9-530-55; 9-090-62; 9-087-550p each.

Electrolytics. 32/32/32µF, 325v, 2" x 1 1/2" 35p; 80µF 150V 12" x 1" 20p; 2000µF 30v, 2 1/2" x 1" 25p; 2000µF 35v 3" x 1" 30p; 470µF 100v 3" x 1 1/4" 25p; 2000, 2000µF 25v 2" x 1 1/4" 35p; 30,000µF 25v 4 1/2" x 2 1/2" 50p; 700µF 200v 3 1/2" x 1 1/4" 30p; 16,16µF 275v 1 1/2" x 1" 20p; 40/40/20µF 275v 3" x 1" 20p; 4500/900/900µF 30v 2 1/2" x 1 1/4" 50p; 4000µF 35v 3" x 1 1/4" 40p; 4000µF 35v 3" x 1 1/4" 35p; 2500µF 40v 2 1/2" x 1 1/4" 40p; 4000µF 18v 2" x 1" 20p; 470µF 25v 1 1/2" x 1" 15p.

Matched pair of bookshelf speakers. Teak finish, size 12" x 8" x 5", 8" x 8" ohms ceramic, 5 watts RMS. Complete with din leads. £11.00 pair.

Thorn TV IF chassis, 950 series (less valves), £1.75.

UHF 625 transistor push button tuner (NSF Telefunken) as used on Decca MS2400. Brand new and boxed, £3.25.

Light Dependent Resistors (RCA SC353B) 30p each, 4 for £1.00.

P-C Boards (not computer panels), 1 off 6 transistor single wave band, 1 off 4 transistor audio, 1 off 3 transistor £1.60, three boards.

Rank EVR Teleplayer colour transistor panels, type and components on new panels listed as follows, £2.50, each panel. Z605—14 off BC148; 2 RCA ca3054 (ic); 1 crystal 4-433618 MHz—Z607—12 off BC148; 1 BC108; 1 BC158; 1 RCA ca3046 (ic), 1 RCA ca3045 (ic); Z608—23 off BC148; 2 BC158—Z612—12 off ME4103; 2 BC-251B; 1 BFY50.

Mains Droppers, 10 mixed values, £1.00.

Edgewise Level meters, 200µA, size 1 1/2" overall, 50p.

Chrome Plastic knobs, 3 types, 4 off each with spring clip, £1.25.

Aluminium Chassis, 7 1/2" x 5 1/2" x 2 1/2" 70p; 10" x 7 1/2" x 2 1/2" 85p; 11" x 7 1/2" x 2 1/2" 95p.

BSR P128, similar to HT70 single play, with heavy die cast turntable, less cartridge, £11.00.

Transistorised FM tuner head, with A.M. gang, slow motion drive 88-108 Mcs, with circuit diagram, £2.30. Ferguson Stereogram Chassis. MW/LW/VHF with tuning scale (5+5 watts sine wave) 15 ohms £28.50.

15 ASSORTED SWITCHES £2.00. 50—3 way to 7 way TAG STRIPS. £1.25.

ALMA REED RELAY TYPE DRH. 3 VOLTS, 55p.

REPANCO & DENCO COILS. NEW/BOXED OUR SELECTION—5 FOR £1.25

Goods not despatched outside UK (Post and packing free in UK) 15p handling charge on orders under £1.00. All items include VAT

SURPLECTRONICS
 216 LEAGRAVE ROAD,
 LUTON, LU3 1JD, BEDS.

Free with speaker orders over £7—
 "Hi-Fi Loudspeaker Enclosures" book. All units guaranteed new and perfect. Prompt despatch. Carriage and packing: speakers 30p each, speaker kits 75p each (£1.50 pair) tweeters and crossovers 20p.

ALL PRICES QUOTED INCLUDE VAT.

WILMSLOW AUDIO (Dept. PW)

Loudspeakers: Swan Works, Bank Square, Wilmslow, Cheshire. SK9 1HF
 Discant Radio, PA, Hi-Fi: 10 Swan St. Wilmslow
 Send stamp for free booklet "Choosing a Speaker"



Agfa Cassettes

The best buy!

Agfa Low Noise Cassettes AT LESS THAN HALF PRICE!

AGFA HIGH DYNAMIC SUPER

AGFA STEREO-CHROM CHROMIUM DIOXIDE

	1	5	10
CG8	37p	£1-80	£3-30
CG9	50p	£2-48	£4-05
CT10	15p	£3-10	£6-20
CG8+6	50p	£2-40	£4-70
CG9+6	48p	£3-35	£6-00
CT10	19p	£4-90	£9-85
CG8	15p	£4-20	£8-30
CG9	£1-08	£3-35	£10-00


SAME DAY DESPATCH. P. & P. 15p per order

WILMSLOW AUDIO

(DEPT. PW)

10 SWAN STREET, WILMSLOW, CHESHIRE, SK9 1HF

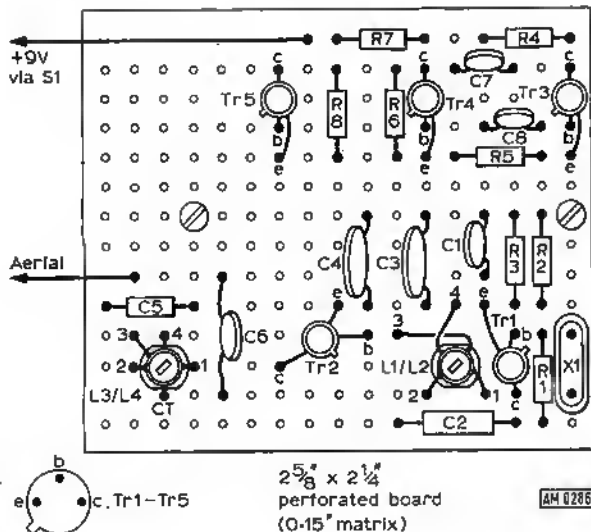Cut-price prerecorded cassettes—send stamp for list



board as possible, wind on 14 turns close wound and apply a little quick-drying adhesive. Take the end down through hole 2, scrape the wire, and solder to C3. L2 is wound in the same way 4 turns, immediately alongside L1. The beginning of L2 goes through hole 4, and the end through hole 5.

L3 has 17 turns in all, Begin at 1, against the board, and wind $8\frac{1}{2}$ turns, scrape the wire, twist to form a loop and solder for the centre tapping CT. Wind a further $8\frac{1}{2}$ turns in the same direction and cement end 2. L4 is 5 turns of thin insulated wire, such as 22SWG connecting wire, wound on top of L3. Take the beginning to MC and the end to hole 3, across the board, and up as shown for the aerial connection. A connection can now be made to CT of L3 and end 2 can be connected to C5. A few spots of adhesive will keep L4 in place.

Fit a flexible lead from R7 to the push switch S1 and take the second switch tag to a further lead, with a battery positive clip.

CASEWORK

The transmitter is intended to be used in a metal case which is held in the hand. The case is made from a 6 x 4 in. universal chassis with an additional 6 x 4 in. plate for the back. The 6 x 2 in. sides and 4 x 2 in. top and bottom are assembled with bolts and the front plate is similarly attached. Drill this plate to take the bolts of the circuit board and hold the board about $\frac{3}{16}$ in. clear of the metal using spacers or extra nuts.

Fit S1 to the side of the case so that it comes readily to finger or thumb when holding the case. The aerial is fitted to the opposite side, near L4, and insulated from the metal case by insulated bushes and washers, or by using two pieces of $\frac{1}{16}$ in. thick paxolin, one for each side of the metal, with insulating washers between to prevent contact with the metal. The simpler type of telescopic aerial may require a mount formed from scrap metal, in which it is a sliding fit. Some aeriels have a bracket of this type already provided.

The battery occupies the bottom of the case and a small bracket on the back plate holds the battery in position.

★ components list

Resistors

R1 56k Ω	R5 47k Ω
R2 12k Ω	R6 47k Ω
R3 180 Ω	R7 4.7k Ω
R4 4.7k Ω	R8 4.7k Ω
All $\frac{1}{4}$ W 5 or 10%	

Capacitors

C1 4700pF disc ceramic	C5 15pF tub ceramic
C2 33pF tub ceramic	C6 4700pF disc ceramic
C3 0.1 μ F disc ceramic	C7 0.047 μ F
C4 2000pF ceramic	C8 0.047 μ F


Semiconductors

Tr1/2 BC109	Tr3/4/5 BC107
-------------	---------------

Miscellaneous

Coil formers, 4mm. with cores (4). Crystal 27MHz, see text and Part 1. Crystal holder type HC6U. Case 6 x 4 x 2 in. with extra plate 6 x 4 in. (Home Radio). Telescopic aerial. Push switch, normally off. Veroboard 2 $\frac{1}{2}$ x 2 $\frac{1}{2}$ in. 0.15 in matrix.

Fig. 3: Constructional information for the circuit board, the winding details for the coils being shown below.

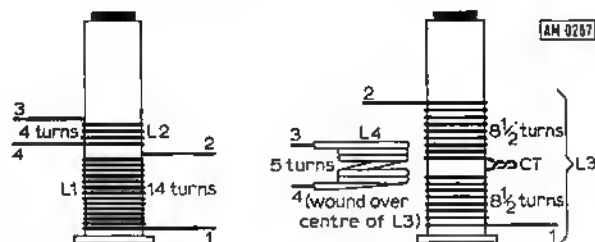

Note: L1, L2 and L3... 32 swg enameled copper wire, close wound. L4... 22 swg insulated connecting wire, close wound.

board and provide a return to the metal case, and holes to give a push fit for the coil formers which are also secured with adhesive.

Position items as shown in Fig. 3, turn the board over and solder finally snipping off excess leads. Sleeving is put on all wires which may touch other wires or joints. Connections should be short and direct in the RF section.

It was found best to wind the coils when the formers have been cemented in position. To wind L1, take a length of 32SWG enameled wire, scrape one end, pass this down through hole 1, Fig. 3, and solder it to C, Tr1. Draw the wire taut and beginning as near the

TESTING

The transmitter should be tested and provisionally tuned before fixing it into the case. Connect a 9V battery placing a meter, set to the 100mA range, between battery negative and one of the bolts MC. Temporarily take the aerial lead to a bulb holder, one side of which is returned to a bolt MC. Fit a 6V 0.04A bulb.

With S1 closed, rotate the core of L1 until the meter current begins to rise. When this happens, rotate the core of L3 while observing the bulb. Tune L3 and L1 for maximum brightness. Check that the oscillator starts when S1 is opened and then closed. If it does not, re-adjust L1 core until it oscillates every time. With optimum tuning, the bulb should light quite brightly.

To check for the modulating tone, use either the monitor, of Part 3, or receiver. Alternatively, connect a pair of headphones to a few turns of wire, with a diode in one lead, and bring this near L3, when the audio tone should be heard strongly.

FINAL TUNING

If the aerial is closed and L1 and L3 are adjusted for best brilliance of a 6V 0.04A bulb held temporarily from aerial to case this will probably give all the range required when the aerial is subsequently extended. However, more accurate tuning is possible with a field-strength indicator or monitor, Part 3. This is placed a little distance from the transmitter and tuning adjusted for the best reading obtainable. The aerial should be fully extended with the transmitter held in the hand at about chest height. It is usual for both transmitter and receiver aerials to be roughly vertical to avoid directional effects.

When controlling the equipment at short range, it will be found that adjustments are not critical and the transmitter aerial need not be extended very far. But adjustments to secure the maximum radiated field strength are, of course, important when trying to achieve the maximum possible range. If there is any chance of a model being lost, a test should always be made at maximum range, before releasing it. Avoid letting the distance approach the known maximum range in case reduced battery power or other circumstances result in control being lost.

NEXT MONTH WE DESCRIBE THE ACTUATING MECHANISM AND A MONITOR AND FIELD STRENGTH INDICATOR.

AVAILABLE NOW!

REPRINT OF PW's TELE-TENNIS SERIES

July-November 74

Send 75p + 5p (post & packing) to :-
Chief Cashier (PW Tele-Tennis),
I.P.C. Magazines,
Tower House, Southampton St.,
London, WC2E 9QX

TELEVISION

IN THE FEBRUARY ISSUE

CRT TESTER AND REACTIVATOR

This useful piece of servicing equipment enables c.r.t.s., both monochrome and colour, to be quickly tested for emission and leakage and re-activated as necessary. A selector switch enables the individual guns of colour tubes to be checked and compared. Two reactivation treatments are provided.

AUTOMATIC CUT-OFF CORRECTION

One of the problems with a three-gun colour tube is that the guns age at different rates. This means that the grey scale should be reset several times during the life of a tube. In the latest B and O chassis however a patented circuit is used to correct the cut-off point of each gun automatically before the start of each scanned field, thus maintaining the correct grey-scale adjustment. The operation of this novel circuit will be explained.

SERVICING TV RECEIVERS

The next chassis to be dealt with by Les Lawry-Johns is the current Decca Single-standard one used in Models MS1700, MS2001 and MS2401.

TWO-TERMINAL STABILISERS

A review of the many two-terminal devices that can be used to provide voltage and current stabilisation, outlining their operation and characteristics. Leading from simple diodes up to the TAA550 type i.c. stabiliser.

TRANSISTOR VIDEO CIRCUITS

The second part of S. George's series on video circuits and faults looks at solid-state circuits. Because of the very different characteristics of transistors, circuit design and the faults experienced differ markedly from those associated with valves as outlined in Part 1.

PLUS ALL THE REGULAR FEATURES

TO
(Name of Newsagent)

Please reserve/deliver the FEBRUARY issue of
TELEVISION (25p) and continue every month until
further notice.

NAME

ADDRESS

SAXON

Money saving high performance audio equipment
DIRECT FROM OUR OWN FACTORIES

GUARANTEED TESTED HIGH PERFORMANCE MODULES—now better value than ever

SA35 £5.45

35W RMS 25-50V
7 transistors, 7 diodes

Carriage free

- ★ 25Hz-25kHz
- ★ 0.2% distortion
- ★ Noise—80dB
- ★ 500mV into 20K
- ★ 4-16 ohms
- ★ Simple wiring
- ★ Short and open circuit proof
- ★ Continuously rated
- ★ Top-grade components

SA50 £6.90


50W RMS 25-65V
7 transistors, 7 diodes

Carriage free

SA100 £12.50

100W RMS 45-70V
10 transistors, 7 diodes

Carriage free

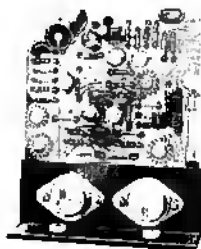

THE SA100 MODULE

POWER SUPPLIES

UNSTABILISED—READY WIRED

PU45

Suits 2 SA35 or 1 SA50 (4 ohm) £5.45

Carriage 30p

PU70

Suits 2 SA50 (8 ohm) or 2 SA100 £8.45

Carriage 40p

STABILISED

PS45

Suits 2 SA35 or 2 SA50 (8 ohm) £4.45

Carriage free

MT45

Transformer for above £3.50

Carriage 30p

PS70

Suits 2 SA100 £5.45

Carriage free

MT70

Transformer for above £4.90

Carriage 40p

N.B. PS70 is not suitable for the SA50

MK II STEREO DISCO MIXER £22.50

Carr. 30p

This well tried unit mixes two decks, handles any ceramic cartridge, mic override plus separate full range bass and treble controls on both mic and deck inputs. Ample headphone power is available for P.F.L. May be used for mono and its mains operated. Fitted with sturdy screening case. Controls: Mic vol, base, treble. Left/Right fade, deck volume, bass, treble, h/phone select, vol, Mains. Size 17 1/2in x 3in x 4in deep.



DISCO MODULE £9.50

Carr. 20p

Thousands sold of this extremely popular mono version. A mic input may be fitted using the VA30 (see below). Low consumption from a 9V battery. Features the same high standards of reproduction as the Stereo version. Controls: h/phone select, vol, Left deck vol, Right deck vol, bass, treble, master vol. Size 12 1/2in x 3in x 2in deep.



3-CHANNEL SOUND-LITE £22.50

Carr. 30p

Only SAXON can supply such incredible value for money. This unit features 3kW power handling, full-wave control, bass, middle, treble AND master controls. Twin loudspeaker jacks for "through" connections. It may be used free standing or will panel mount next to either of the above. Also features unique CUT-BACK circuitry for extra wide range response. Size 12in x 3in x 2 1/2in deep. Professional standards at a price you can afford!



SINGLE CHANNEL VERSION £7.50

Recently reduced in price due to increasing sales, handles 1kW. Full wave operation. Carr. free

ADD 8% VAT TO ALL ORDERS

MULTI-PURPOSE MIXERS

M4HL

£19.50 Carr. 50p

M6HL


£29.50 Carr. 30p

Featuring multiples of our VA30 module, the M4HL and M6HL fulfil the requirements of all clubs, groups, etc. where a high quality mixer is required. Each channel has one high and one low impedance input, plus volume, treble and bass controls. Input impedances may, if required, be easily changed. The M4HL has four channels, and one output, and the M6HL six channels (12 inputs) and a master control and two outputs. Either unit may be used free-standing or panel mounted. These mixers will feed all types of amplifier. Recommended for their versatility and high performance, and excellent value for money.

VA30 CHANNEL MODULE £3.50

Carr. free

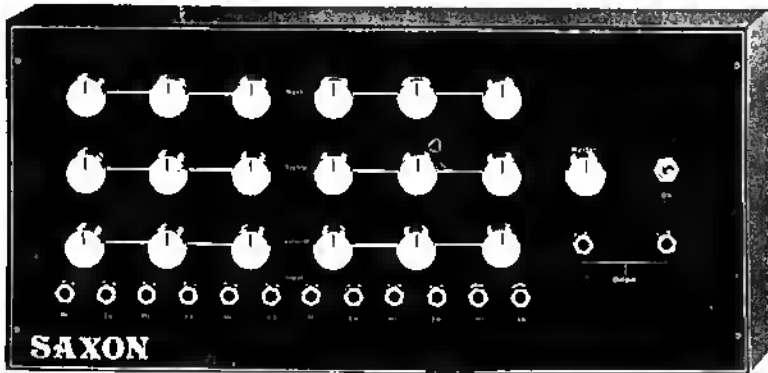This is the basic channel module in the above mixers and may also be used for extra inputs on either the mono or stereo mixers. Fitted with volume, bass and treble controls, requires just a jack and supply (9-100V)




SAXON CSE 100

COMPLETE AMPLIFIER

£39.90

Carr. free

100W of speech and music—Two separately controlled inputs. Wide range bass and treble controls. Sturdy and attractive vinyl case. Twin outputs. Ideal for groups, discos, etc. Fully tested and guaranteed. 50W version identical in appearance.

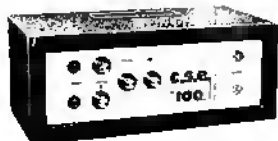

CSE50

£29.50 Carr. free

NEW !!

SAXON MULTIMIX 100 £57.00

Carr. free

100W rms four inputs slider controls plus master slider. Wide range bass and treble controls. Fantastic value, ideal for complete disco's, groups, clubs etc. SAXON MULTIMIX 50—Exactly as above but 50W rms. £45.00

CALLERS AND MAIL ORDER

SAXON ENTERTAINMENTS LIMITED

327-333 WHITEHORSE ROAD · CROYDON CR0 2HS

(Please quote magazine when ordering)

SHOP HOURS: 9 a.m.-5 p.m. — LUNCH 12.30-1.30 p.m. MAIL ORDER DESK: 10 a.m.-3 p.m. 24-HOUR ANSWER SERVICE. TEL. 01-684 6385. TECHNICAL ENQUIRIES: 01-684 0098.

SEND 10p FOR OUR 26 PAGE MANUAL—full circuits & details.

TERMS OF BUSINESS: C.W.O. C.O.D. or ACCESS (just send in card number). Send 50p for C.O.D.

Please send S.A.E. with all enquiries.

VAT @ 8% must be added to all orders including carr. charges.


How to order the cassette unit for your Kempton or Ascot player.

As a reader of Practical Wireless, you can get the cassette mechanism for your car stereo player direct from Goldring.

The units for both the PW Kempton and Ascot are made by Lenco and based on the famous STARR design, with wow and flutter reduced to 0.3% max.


All you have to do is send the coupon to us, with a cheque or PO made out to Goldring Ltd. Be sure to state which unit you need. For the Kempton, it's Lenco FFR at £18.90; for the Ascot, it's Lenco CRV at £19.98. Prices include packing, carriage and VAT.

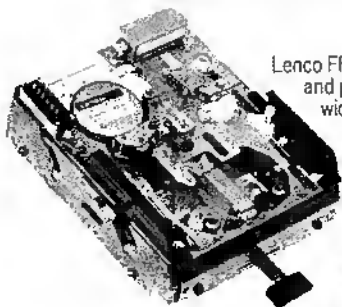The units are also available from selected distributors.



Lenco FFR for the Kempton. Robust and precision engineered, it's widely used in industry and by Europe's largest car stereo manufacturer.

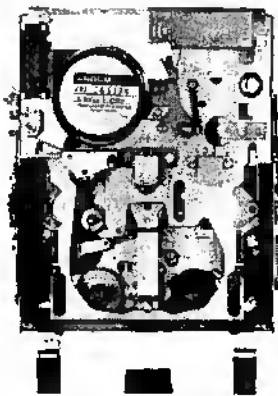Lenco CRV for the Ascot. A record/replay unit made to hi-fi standards. Features of the Ascot Player include dynamic noise reduction, auto-stop and cassette ejection at end of play.



To: Goldring Ltd, 10 Bayford Street, Hackney, London E8 3SE.

Please send me: Lenco FFR at £18.90


Lenco CRV at £19.98

I enclose PO, cheque for £

NAME

ADDRESS

Goldring

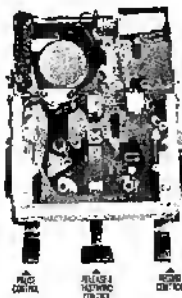

GARRARD CT4'S' MK III STEREO CASSETTE PLAYER & RECORDER

has full facilities for record, playback, pause, erase, rest, fast forward and reverse wind, automatic tape end stop and cassette release.

Robust, precision engineered mechanism based on the "STARR" patented design. Ideal for use in Car stereo cassette players, HI-FI stereo cassette recorders, industrial and many other applications.

Send cheque or Postal Orders for **£19.98** (£18.50 + 8% VAT) (includes post and packing) to:

BOTHWELL ELECTRIC SUPPLIES
(Glasgow) LIMITED
431 Sauchiehall Street
GLASGOW G2 3LG Tel: 041-332 6184
Scotland's Leading Electronics Centre


CJL PRICES INCLUDE P&P AND V.A.T.

- AERIAL**, telescopic, 15-120cm. £1.20
- AERIAL**, telescopic, h and v swivel, 15-80cm. . . £1.78
- EARPHONE**, stethoscope style, 8 ohm dynamic. . £1.00
- HAND DRILL**, (Laytool), Compact precision drill .5/16" chuck. Gears totally enclosed, S/L bearings. . . £2.90
- INTEGRATED CIRCUITS**
- AUDIO POWER AMPLIFIER** (National) LM380 . . . £1.00
- A.M. RADIO RECEIVER** (RCA) CA3123E . . . £1.40
- F.M. STEREO DECODER** (Motorola) MC1310P . . £2.80
- I/C TIMER** (Signetics) NE555V £0.78
- I.L. SOCKETS** (pk of 3) 8 pin £0.50 14 pin £0.55
- KEYNECTOR**, rapid connect-single/multiple leads to mains. Built-in piano switches, neon & 13A fuse. . . £3.20
- MICROPHONE**, lightweight dynamic, remote start/stop 200 ohms, 100-10,000Hz, 5mV average output. . . £1.80
- MULTIMETER**, small and attractive, Vdc-10.50, 250, 1,000. Vac-10.50, 250, 1,000. Idc-100mA, R-150k. . £4.95
- POWER SUPPLY COMPONENTS**
- SILICON BRIDGE RECTIFIER**, 100 P.I.V./2A . . . £0.40
- ELECTROLYTIC CAPACITOR**, 2,200uF/50V . . . £0.57
- ELECTROLYTIC CAPACITOR**, 5,000uF/25V . . . £0.63
- SILICON POWER TRANSISTOR**, 2N3055 £0.60
- VOLTAGE REGULATOR** (Fairchild) uA7805 . . £1.70
- VOLTAGE REGULATOR** (Signetics) NE550A . . £0.80
- SIGNAL INJECTOR** produces audio through video signals, excellent servicing amplifiers, radios, televisions, etc. . £3.92
- SOLDERING IRON**, 25 WATT, (Antex), X25, 240V, Very low leakage, 1/8" long life bit (interchangeable). . . £1.85
- 3/32" bit £0.45 3/16" bit £0.45 Element £0.95
- STAND**, (Antex), ST3, High grade base, chrome plated spring, sponges and accommodation for spare bits. . £0.95
- SPEAKER**, miniature, 8 ohms, 70mm dia. £0.80

CJL CJL LTD. P.O. BOX 34, CANTERBURY, CT1 1YT

ELECTRONIC SLAVE * FLASH *

Alan Ainslie

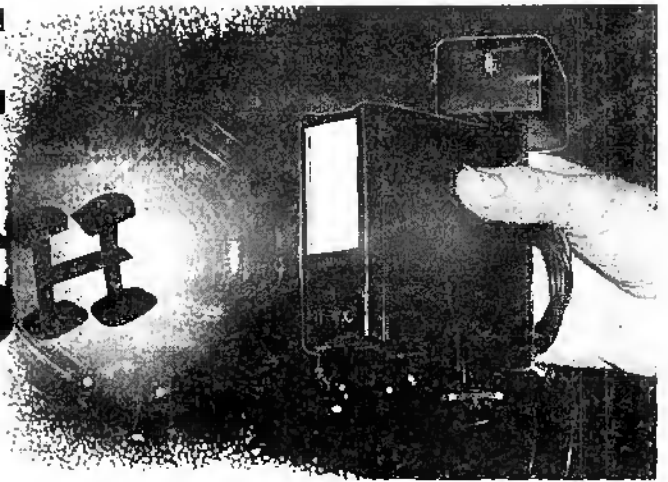

ONE of the drawbacks of conventional flash photography (with the gun mounted on the camera) is that little modelling is possible with such simple lighting. Quite obviously it would be better to use several flashguns all fired simultaneously and placed in such positions as would give the most effective lighting. Conventionally the guns are connected to the camera by extension leads which tend to get in the photographer's way and get tangled up.

During recent years there have appeared on the market 'Slave Flash' units which pick up the light from the main flashgun and fire the slave almost simultaneously without the need for connecting wires. Most of these units are battery operated and amplify the pulse from a phototransistor to switch on a thyristor which in turn fires the flashgun.

For occasional use a battery operated unit can be a severe disadvantage as one might leave the unit switched on for a period, and be unaware of the state of the battery after storage. However, using the latest techniques it is possible to construct a slave flash that needs no battery power.

TYPICAL FLASHGUN

Fig. 1 shows the tube firing circuitry of a normal electronic flashgun. In normal operation the 0.01 μ F capacitor charges to 300V via both 2.2M Ω resistors. Closing the camera shutter discharges the capacitor

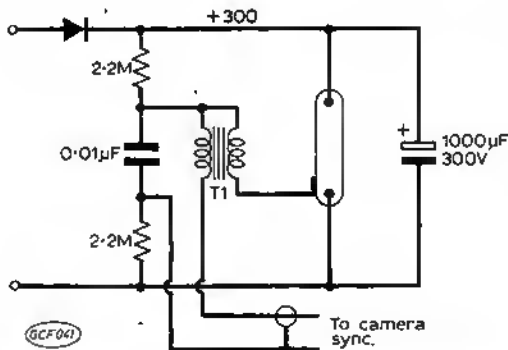


Fig. 1: Typical tube firing circuit of an electronic flashgun.

into transformer T1. The secondary of T1 produces oscillations of a few KV peak amplitude which triggers the tube drawing energy from the 1000 μ F capacitor. The purpose of the 2.2M Ω resistors is to isolate the sync connections from the tube circuitry, sparing the photographer electrical shocks when the equipment is earthed in any way—intentionally or not.

Current available at the sync terminals amounts to a few μ A, whereas the open circuit voltage is a few hundred volts. It is therefore essential if any attempt be made to draw current from the unit through the sync lead the current should be very small so that the voltage dropped across the 2.2M Ω resistors is not excessive. In this way the full voltage is still available across the capacitor to discharge into T1. Drawing too much current reduces the capacitor voltage and results in uncertain operation.

CIRCUIT

The full circuit of the slave flash unit is shown in Fig. 2. The current flowing from the sync lead charges C2 to a voltage set by zeners D1 and D2. These are 10V devices but the very small currents cause the zener voltage to rise by about 25%. Therefore C2 charges to about 25V. The voltage across C2 acts as the supply for the phototransistor Tr2, which is a Photo Darlington device connected as an emitter follower. At tiny currents the 2N5777 has a good

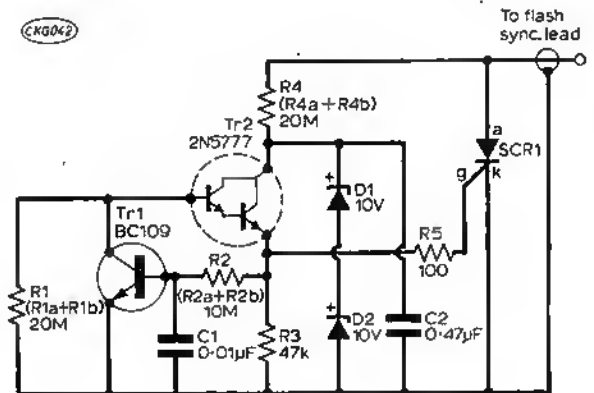


Fig. 2: Circuit of slave flash unit.



View of the completed slave flash unit, right. The photo-Darlington transistor can be seen through the aperture at the front.

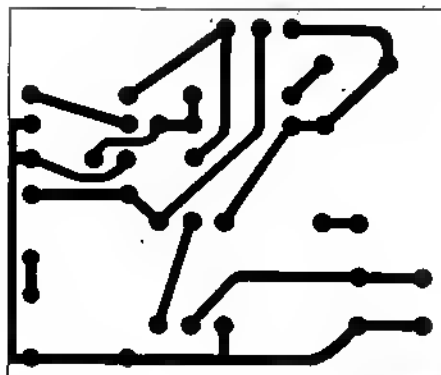




Fig. 3: above, details of the PCB actual size which must be made of fibreglass. Below, layout of components on the PCB together with a photograph of the finished board.

degree of gain while under quiescent conditions it is almost cut off. Any tendency to increase conduction through an increase in ambient light level is counteracted by Tr1.

An increase in Tr2 emitter current would increase the voltage across R3, biasing Tr1 further on and so draining base current from Tr2. This negative feedback compensates for wide variations in ambient light levels.

A transient increase in Tr2 emitter current due to the light from a flashgun, however, does not cause the feedback loop to operate due to C1 decoupling Tr1 base. Consequently Tr2 discharges C2 into R3 and the gate of the thyristor—turning the thyristor on. As soon as the thyristor switches on it effectively shorts the sync leads, resulting in the flashgun firing. The current on the sync lead falls to a very small value after the flash, as the 1000 μ F capacitor is now discharged. This current is less than the holding current for the thyristor which switches off.

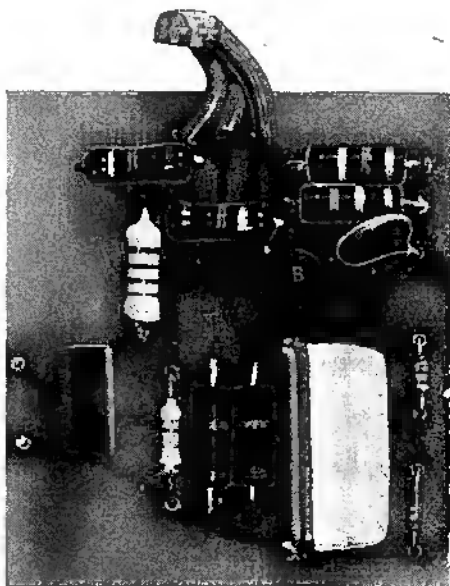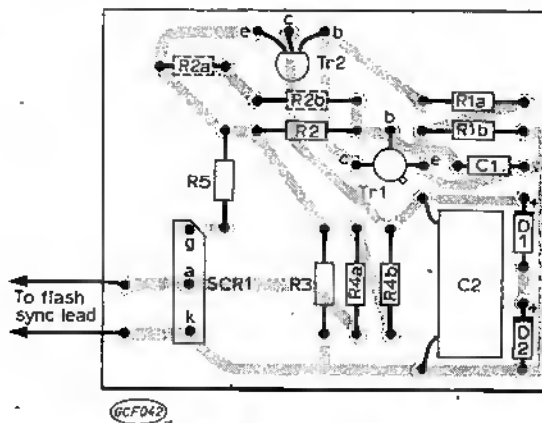The recycling time of the slave unit is a few seconds longer than that of the flashgun. Normally it will not exceed 15 seconds.



are to be drilled and then filling in free hand. The actual design is drawn on to the copper with one of the readily available resist pens or enamel paint.

When the resist is dry the board is ready to be etched by floating face down on a saturated solution of ferric chloride. With fresh solution the etching should take less than half an hour at room tempera-


CONSTRUCTION

The circuit operates with very small currents at medium voltages. Any PCB leakage therefore, would adversely upset the operation of the unit which rules out Phenolic or SRBP board for construction due to the rather high, and unpredictable leakage of such boards. Good quality glass fibre is the only satisfactory medium for this circuit.

The unit is made up on a small PCB as shown in Fig. 3. For those constructors, perhaps photographers, not fully familiar with PCB etching a reasonably detailed description will follow.

PRINTED CIRCUIT BOARD

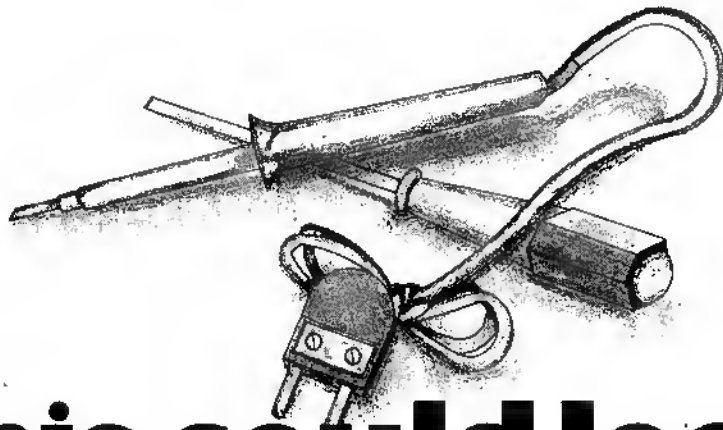The drawings show the board full size. A piece of fibreglass board is first cut to size with the edges filed smooth. The copper is polished with fine wire wool and should be rubbed over with a cloth moistened with trichloroethylene to remove any grease from the surface. The design of the conductors can be transferred with carbon paper or by punching through with a compass where the holes



This could lead to something big.

A soldering iron and a screw driver. If you know how to use them, or at least know one end from the other, you know enough to enrol in our unique home electronics course.

This new style course will enable anyone to have a real understanding of electronics by a modern, practical and visual method. No previous knowledge is required, no maths, and an absolute minimum of theory.


You build, see and learn as, step by step, we take you through all the fundamentals of electronics and show you

how easily the subject can be mastered and add a new dimension not only to your hobby but also to your earning capacity.

This course is accepted by and used in a large number of schools and colleges and forms an invaluable grounding for professional training in the subject. All the training is planned to be carried out in the comfort of your own home and work in your own time. You send them in when you are ready and not before. These culminate in a final test and a certificate of success.

1

Build an oscilloscope.

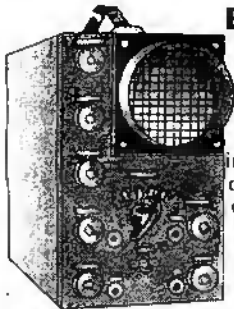

As the first stage of your training, you actually build your own Cathode ray oscilloscope! This is no toy, but a professional test instrument that you will need not only for the course's practical experiments, but also later if you decide to develop your knowledge and enter the profession. It remains your property and represents a very large saving over buying a similar piece of essential equipment.

2



Read, draw and understand circuit diagrams.

In a short time you will be able to read and draw circuit diagrams, understand the very fundamentals of television, radio, computers and countless other electronic devices and their servicing procedures.


3



Carry out over 40 experiments on basic circuits.

We show you how to conduct experiments on a wide variety of different circuits and turn the information gained into a working knowledge of testing, servicing and maintaining all types of electronic equipment, radio, t.v. etc.

PLUS

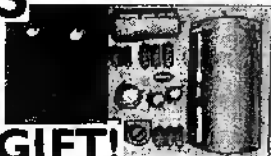

FREE GIFT!

ALL STUDENTS ENROLLING IN OUR COURSES RECEIVE A FREE CIRCUIT BOARD ORIGINATING FROM A COMPUTER AND CONTAINING MANY DIFFERENT COMPONENTS THAT CAN BE USED IN EXPERIMENTS AND PROVIDE AN EXCELLENT EXAMPLE OF CURRENT ELECTRONIC PRACTICE

To find out more about how to learn electronics in a new, exciting and absorbing way, just clip the coupon for a free colour brochure and full details of enrolment.

WAA

Brochure without obligation to:
BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL, Dept WL/25
P.O. Box 156, Jersey, Channel Islands.

NAME.....

ADDRESS.....

(Block caps please)

ERSIN



for fast easy reliable soldering

EASY TO USE DISPENSERS AND REELS

IDEAL FOR HOME CONSTRUCTORS

Ersin Multicore Solder contains 5 cores of non-corrosive flux, instantly cleaning heavily oxidised surfaces. No extra flux is required.

SAVBIT handy solder dispenser



A coil of Ersin Multicore Savbit Solder in a dispenser 7 1/2 in. of 18 s.w.g. (2.2 metres of 1.22mm). The Solder that reduces the wear of soldering iron bits.

Size 5
32p

SAVBIT solder for general purpose work

A handy plastic reel of SAVBIT alloy. 63ft of 18 s.w.g. (19.2 metres of 1.22mm)

Size 12 £1.72



ALU-SOL for soldering aluminium

New Multicore Alu-sol flux-cored solder in 18 s.w.g. No extra flux needed. Plastic reel holds 36ft. Supplied with full instructions. Also available in solder dispensers.

Size 4 £2.32



Fine gauge solder for soldering small components

Fine gauge solder for soldering small components 138ft of 22 s.w.g. (42.0 metres of 0.71mm) Ersin Multicore 5 core solder wound on a plastic reel. Suitable for intricate work and small components.

Size 10 £1.44



For soldering fine joints

Dispensers of Ersin Multicore Solder make those small jobs easier. 21ft of 22 s.w.g. (6.4 metres of 0.71mm) solder, specially suitable for soldering fine wires, small components and for repairing printed circuits.

Size 15 36p

Or size 19A for kit wiring or Radio and T.V. repairs 7ft. (2.1 metres) of 18 s.w.g. (1.22mm) Ersin Multicore Solder.

Size 19A 34p

NEW BIB WIRE STRIPPER & CUTTER



Fitted with unique 8 gauge selector with hand locking device and easy grip handles. Spring incorporated for automatic opening. Strips insulation from flex and cables in seconds and can also be used as a cutter.

Model 8B, 70p

NEW SOLDER WICK



Absorbs solder instantly, from tags and printed circuits. Only needs 40 to 50 Watt soldering iron. Quick and easy to use. Does not need flux and is non-corrosive.

Size 18 90p

Bib Hi-Fi Accessories Limited,

Sole U.K. Sales Concessionaires, P.O. Box 78 Hemel Hempstead, Herts. HP2 7EP

Prices shown are recommended retail excluding V.A.T. From Electrical and Hardware Shops. If unobtainable, send 15p P&P. Prices and specifications subject to change without notice.

G. F. MILWARD, 369 Alum Rock Road, Birmingham B8 3DR. Tel. 021-327 2339

We are glad to say that it is now possible to supply from stock the following integrated circuits. ALL ARE BRANDED, FULL SPECIFICATION devices offered at unbeatable prices

1/99				100/499				500/1000			
7400	£0-15	£0-125	£0-10	7442	£0-845	£0-537	£0-43	7494	£0-495	£0-412	£0-33
7401	£0-15	£0-125	£0-10	7443	£1-275	£1-082	£0-85	7495	£0-83	£0-525	£0-42
7402	£0-15	£0-125	£0-10	7445	£0-855	£0-712	£0-57	7496	£0-72	£0-60	£0-48
7403	£0-15	£0-125	£0-10	7446	£1-05	£0-875	£0-70	74104	£0-315	£0-282	£0-21
7404	£0-18	£0-15	£0-12	7446A	£1-05	£0-875	£0-70	74105	£0-315	£0-282	£0-21
7405	£0-18	£0-15	£0-12	7447	£1-05	£0-875	£0-70	74107	£0-315	£0-282	£0-21
7406	£0-375	£0-312	£0-25	7447A	£1-05	£0-875	£0-70	74121	£0-315	£0-282	£0-21
7407	£0-375	£0-312	£0-25	7448	£0-855	£0-712	£0-57	74122	£0-85	£0-375	£0-30
7408	£0-15	£0-125	£0-10	7450	£0-15	£0-125	£0-10	74123	£0-83	£0-525	£0-42
7409	£0-15	£0-125	£0-10	7451	£0-15	£0-125	£0-10	74141	£0-75	£0-625	£0-50
7410	£0-15	£0-125	£0-10	7453	£0-15	£0-125	£0-10	74151	£0-89	£0-575	£0-46
7412	£0-195	£0-182	£0-13	7454	£0-15	£0-125	£0-10	74153	£0-89	£0-575	£0-46
7413	£0-345	£0-287	£0-23	7460	£0-15	£0-125	£0-10	74155	£0-89	£0-575	£0-46
7416	£0-345	£0-287	£0-23	7472	£0-255	£0-212	£0-17	74158	£0-89	£0-575	£0-46
7417	£0-345	£0-287	£0-23	7473	£0-153	£0-282	£0-21	74980	£1-005	£0-837	£0-67
7420	£0-15	£0-125	£0-10	7474	£0-315	£0-282	£0-21	74181	£1-005	£0-837	£0-67
7423	£0-27	£0-225	£0-18	7475	£0-485	£0-387	£0-31	74182	£1-005	£0-837	£0-67
7425	£0-27	£0-225	£0-18	7476	£0-315	£0-282	£0-21	74183	£1-005	£0-837	£0-67
7428	£0-27	£0-225	£0-18	7480	£0-835	£0-382	£0-28	74185	£1-425	£1-187	£0-95
7427	£0-27	£0-225	£0-18	7482	£0-75	£0-625	£0-50	74174	£1-29	£1-00	£0-88
7430	£0-15	£0-125	£0-10	7483	£0-825	£0-687	£0-53	74175	£0-875	£0-812	£0-65
7432	£0-25	£0-225	£0-18	7485	£1-275	£1-082	£0-85	74192	£1-275	£1-082	£0-85
7437	£0-27	£0-225	£0-18	7486	£0-315	£0-282	£0-21	74193	£1-275	£1-082	£0-85
7438	£0-27	£0-225	£0-18	7490	£0-485	£0-387	£0-31	74198	£2-10	£1-75	£1-60
7440	£0-15	£0-125	£0-10	7492	£0-485	£0-387	£0-31	74199	£2-10	£1-75	£1-60
7441A	£0-635	£0-8975	£0-55	7493	£0-485	£0-387	£0-31				

To secure the above prices, all orders for these devices must exceed £25 in total value. Price rating is established by TOTAL NUMBER OF DEVICES ORDERED. Any mix may be made. For special quotations for large orders ring 021-327 2339 NOW!

BRAN TUB !!!

- ★ Resistors, Wire-wound and Carbon
- ★ Capacitors, Silver-mica, Paper, Ceramic, Polyester and Electrolytic
- ★ Controls, Volume, Pre-set, Carbon, Wire
- ★ Diodes, Silicon, Germanium, Zener
- ★ Transistors, Silicon, Germanium

All the above are new and unused stock.

We have made up packs of 2lb gross weight, all are different in content, and contain a mixture of components from the above list. This is a fantastic unrepeatable offer that will enable you to get a good stock of spares at a tiny fraction of normal price!

To make things even more interesting - TWENTY OF THESE BAGS ALSO CONTAIN A POUND NOTE! TWENTY CUSTOMERS WILL BE VERY PLEASED INDEED!

And the price that we are asking? Only £1-50 including both postage and VAT!

Rush your order now! This offer is only made to reduce our surplus stock! It is unlikely that in these days of rising prices we shall ever be able to repeat it!

NEW! NEW! NEW! NEW!

An aerosol spray providing a convenient means of producing any number of copies of a printed circuit both simply and quickly. Method: Spray copper laminate board with light sensitive spray. Cover with transparent film upon which circuit has been drawn. Expose to light. (No need to use ultra-violet.) Spray with developer, rinse and etch in normal manner.

Light sensitive aerosol spray £1-00 plus Developer and Etchant 50p postage

FIBRE-GLASS COPPER LAMINATE

Single-sided 75p sq. ft.

Double-sided £1 sq. ft.

Cut in any multiple of 6"

To a maximum size of 3' x 4'

POSTAGE 25p

NOTE: ALL GOODS PLUS 8% VAT (EXCEPT OVERSEAS)

POSTAGE 25p

★ components list

Resistors		
R1 (R1a + R1b)	20M Ω	
R2 (R2a + R2b)	10M Ω (see text)	
R3	47k Ω	
R4 (R4a + R4b)	20M Ω	
R5	100 Ω	
Capacitors		
C1	0.01 μ F	10V ceramic
C2	0.47 μ F	100V
Semiconductors		
Tr1	BC109	
Tr2	2N5777 (General Electric)	
D1	10V 400mW Zener	
D2	10V 400mW Zener	
SCR1	MCR120 or 2N5064 (RCA)	
Miscellaneous		
Printed circuit board fibreglass 2 $\frac{1}{2}$ x 1 $\frac{1}{2}$ in., 3mm female connector, plastic box.		

ture after which it should be washed and the resist removed with a solvent such as trichloroethylene or paint stripper. The holes are all drilled with a number 60 drill in a hand brace or preferably in a pedestal drill.

BOARD ASSEMBLY

20M Ω resistors are specified for two of the resistors in this unit. 10M Ω is usually the highest value obtainable "over the counter" at a reasonable cost, and so each 20M Ω resistor is in practice two 10M Ω in series, i.e. R1a=10M Ω and R1b=10M Ω , therefore R1=20M Ω .

The space shown for R2 allows for a single 10M Ω resistor. However, a particularly good BC109 will work with R2 as 20M Ω which gives a higher overall gain to the unit. The position for the two resistors in this case is shown dotted in the diagram. The unit photographed has R2 as a single 20M Ω resistor.

C1 and C2 should be low leakage components. Generally, reputable film devices should prove satisfactory.

Tr1 should be a device of a reputable manufacturer in order that the leakage currents be low, while Tr2 is specified as a 2N5777 as this is the cheapest device of the 2N5777/79/78/80 range—any of which is suitable for this application.

The thyristor used in the prototype was a general purpose 300V device by IR. However, the devices specified are the Motorola MCR120 or 2N5064 which have low gate currents.

The screened cable by convention is positive on the inner conductor and negative on the shield.

TESTING

The PCB when constructed can be easily tested by connecting to a flashgun with a 3mm socket and trying it by exposing Tr2 to the flash from another gun. Should any malfunction be apparent, voltage tests can only be carried out with a valve voltmeter or high impedance (10M Ω) oscilloscope. Even then the readings may well be subject to considerable error. In the development of the original a 90M Ω precision resistor was used in series with a 10M Ω probe and a DC coupled 'scope.

FINAL ASSEMBLY

The assembled PCB has to be placed in a small container for protection and ease of use. The prototype was fitted quite conveniently into an old "Cosmocord" Phono cartridge box. This box has a transparent plastic lid which is ideal as it allows Tr2 to be illuminated. The transparent lid can be painted from the inside except for a small aperture at one end for Tr2. The sensitive side of the device is the convex surface, which should therefore face outwards.

The slave unit is best fitted with a 3mm socket, but these can be hard to obtain. As an alternative the female end of a flash extension cable can be used, as in the prototype.

CONCLUSION

The slave flash unit fires the second flash usually within 5mS of the first flash. This means that with focal plane shutters on their fastest X sync speeds no difficulty should arise. With leaf shutters 1/125 of a second should be regarded as the maximum usable speed.

Although operating range depends on the power of the main flash gun, the slave unit will fire line-of-sight to about 40 feet and by reflected light from an average scene at 20 feet. These figures are based on the main flash being a guide number 32 gun (at 25 ASA) which is the least powerful available. **PW**

YOU COULD MISS
YOUR SHARE OF
£500 WORTH OF
HEATHKIT EQUIPMENT
IF YOU DON'T
MAKE A DATE
WITH NEXT MONTH'S
P W
AND ENTER OUR
FREE COMPETITION!

TAKE 20

DAVID ANDREWS

No. 68 9V POWER SUPPLY

A series of simple transistor projects, using not more than twenty components.

WE cannot claim any form or originality for this month's project; however it is offered as a compensation for those who need a very straightforward power supply. There has been a large number of fairly sophisticated pieces of equipment published in these pages and it is difficult to sort out the power supply stages in some of these projects. "Pinching" the power stage circuitry from one project to fit another used to be quite commonplace but these days there is often as much complexity in the supply stage as in the piece of equipment being supplied.

One thing is sure about our project this month—complexity is out. There are certain limitations to it but at the same time there are many changes that can be rung with the circuit as it stands, to provide alternative voltages and currents. As there are few difficulties in respect of the workings of the circuit we shall devote much of this part to explaining how one can make the necessary changes to give alternative outputs. First of all we had better describe the circuit as shown in Fig. 1.

Design

In any power supply we have to use a transformer to provide isolation from the mains and generate a lower level voltage, usually slightly higher than that which we ultimately want. The output from the 10V secondary winding of the transformer, T1, is quoted in RMS terms (root mean square value); this means that the AC output voltage will rise to peak values, a factor of root two (1.414) times the quoted RMS value. The bridge rectifier comprising D1 to D4 gives full wave rectification and the capacitor C1 charges up to the peak voltage, in this case approximately

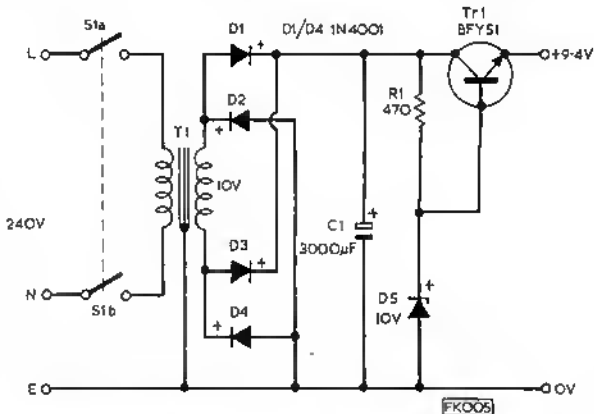


Fig. 1: Circuit of the 9 volt stabilised power supply with a maximum current rating of 200mA.

14V. If no current is drawn from the capacitor the voltage produced by the charge stored will be extremely stable and free from AC ripple. It would be naïve to expect a power supply to be entirely from ripple so it is worth spending a moment or two explaining how the value of C1 is selected.

This is basically a "bucket" capacitor which charges up rapidly from the low impedance source of the transformer and diodes when the AC voltage rises in a positive direction. When the input AC voltage falls the diodes become reverse biased and the stored charge on the capacitor cannot leak away back through the transformer. Assuming no current is drawn from the capacitor by load circuitry a few cycles of the mains will "fill" the capacity of the

—continued on page 928

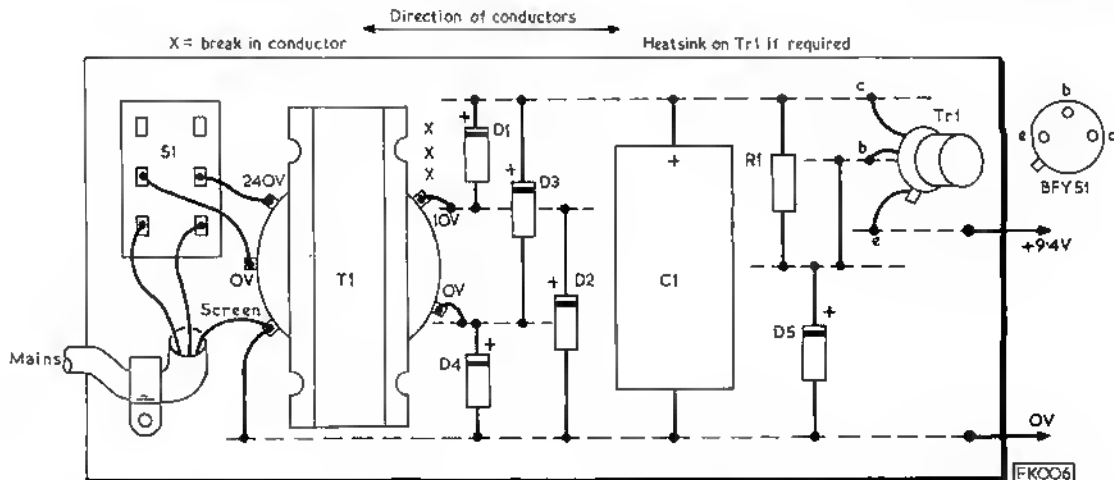


Fig. 2: The unit can be assembled on plain veroboard with pins or on veroboard with copper rails as shown here. A heatsink is advisable on the transistor.

FREE INSIDE!

IN NEXT MONTH'S PRACTICAL WIRELESS

FREQUENCY ALLOCATION

KHz MHz

Wall Chart

At last! Now you can relate the dial on your receiver to the stations you want to hear, in terms of frequency or wavelength, long waves to UHF.

PW 'Easybuild' ELECTRONIC ORGAN Part 1

This four-octave tabletop instrument features 8ft and 16ft pitch with three voices per pitch, each with slider level control. A keyboard split facility gives greater tonal flexibility while a fine tuning control plus variable depth vibrato complete the musical specification. Outputs are provided for internal or external loudspeakers, headphones, or drive for a hi-fi system. A single PCB carries most of the circuitry which is based on CMOS micro-circuits.



PW FREE COMPETITION

£500

worth of HEATHKIT
equipment to be won!

MANY OTHER CONSTRUCTIONAL
ARTICLES, SPECIAL FEATURES
AND REGULAR COLUMNS.

ON SALE IN FEBRUARY

P.W. 'ASCOT' STEREO PART 1

CASSETTE

THOSE readers who have followed the series of articles on the car cassette player will probably have been interested in the possibility of constructing a domestic mains-powered cassette recorder/player. It was our intention from the outset to produce such a machine and we first discuss the design philosophy involved.

A cassette recorder is not a particularly easy piece of apparatus to design. A manufacturer can set up special machining facilities to enable production to be efficiently carried out, but the home constructor is faced with different problems. The projects he builds will in all probability be "one off" efforts; as a result he cannot reasonably be expected to provide facilities better than a well-equipped domestic workshop, and at worst, may have only a work-table, vice and toolbox.

It is totally unrealistic to attempt to construct the deck mechanics so we have a Goldring Lenco model CRV mechanism with a DC motor and electronic speed control. The constructor has to build the casing and chassis work, mount the deck and build up the circuitry on Veroboard.

Anyone experienced in the handling of commercial tape recorders will know that the multiple switching involved between the basic play and record functions is usually both mechanically and electrically complicated. This can pose many problems for the would-be constructor, and to reduce the difficulties we have employed separate recording and playback amplifiers. A degree of electronic switching is used and this simplifies the problem further.

Some readers may feel that the use of separate amplifiers is somewhat extravagant. In fact this is not the case. The special switching mentioned before is avoided and much expense saved in that direction. Also, trouble-shooting is eased by the use of separate, less complicated amplifiers.

Another problem which can beset the constructor is the winding of coils. Tape machines usually employ tuned circuits as bias traps and also in the oscillator circuit providing HF bias and erase head drive when recording. Our machine has eliminated the use of such coils by a special approach to the recording amplifier design, and by using the erase head itself as the inductive part of the oscillator circuit. It will be seen from the foregoing remarks that the entire project has been orientated for the home constructor, and should therefore be considered in this light.

The use of a DC motor for the tape deck makes the machine speed independent of mains frequency and, by removing a potential source of fields in the form of an AC motor, the overall problem of hum pickup is eased. The supply voltage for the electronics is obtained via a stabiliser unit which is complete in a TO3 type transistor casing. The machine is therefore very tolerant of mains voltage and frequency fluctuations.

NOISE

A considerable amount of thought has been directed towards reducing background noise. A tape cassette, when used for stereo recording, employs four tracks on a tape $\frac{1}{8}$ in wide, moving at only $1\frac{1}{2}$ in per second. As a result, the output from the tape head is very low, usually between 300 and 500 microvolts, and considerable amplification of the weak signals is required. Low noise transistors are employed in the input stages of the amplifier, but the signal to noise ratio could still be improved. The use of Dolby-type systems was contemplated, but these are both complicated and difficult for the constructor to set up. Also, tapes have to be recorded using the system.

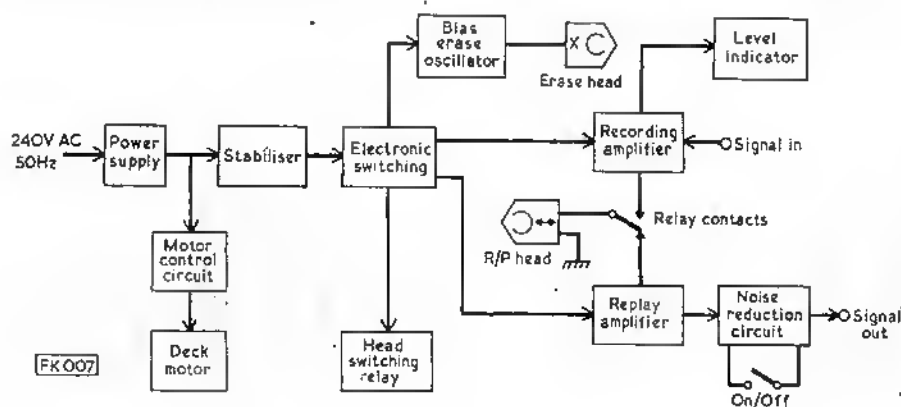


Fig. 1: Block diagram of the P.W. "Ascot" stereo cassette deck.

DECK



TH CUMMINS & TONY FRANCIS*

It was finally decided to use a dynamic noise reduction system, which reduces the response at the higher audio frequencies in the absence of such signals on the tape. This reduces hiss considerably and has the advantage that the system will operate on any tape; special recording techniques not being required.

As it is intended that the machine be used with an existing amplifier, outputs are provided at "LINE OUT" level only, for feeding the main amplifier. No audio output stages are provided. Inputs are provided for both line and microphone. Bias is switchable for the use of standard ferric oxide or the low noise chrome dioxide tape.

The foregoing description has been basically a synopsis of the design approach. We shall now examine the circuits in detail. In order that the circuit may be easily identified, the reader is referred to Fig. 1. Here the interconnections between the basic blocks are clearly illustrated.

POWER SUPPLIES

The basic power supply for the amplifier and erase oscillator is +12V, which is switched to the amplifiers as required. Rather than have elaborate switching arrangements and release mechanism linked to the stop facility on the machine, electronic switching is employed. The circuit of the power supply and switching is shown in Fig. 2.

The AC mains supply is introduced via the on-off switch S1 and fuse F1 to the mains transformer T1. The transformer secondary supplies 15V AC to the indicator lights which are situated within the V.U. meters, and also feeds D1-4, a bridge rectifier which converts the supply to DC. The DC supply is smoothed by the 5000 μ F capacitor, C1. The motor control circuit is fed directly from this source, which also connects to the regulator ICL. The +12V stabilised supply is conveyed via fuse F3 to the final filter capacitor C2, from whence it feeds the electronic switching and amplifiers.

* Hamilton Electronics Ltd.

ELECTRONIC SWITCH

The active elements of the electronic switch are the transistors Tr1, Tr2 and Tr3. The first two form a complementary bistable circuit, the base bias of one being derived from the collector of the other. When the machine is switched on both Tr1 and Tr2 are cut off. It will be seen that the collector of Tr1 connects, via R4, to a supply rail marked C. Also connected to this rail is the diode D5, relay RLA and the recording indicator lamp LP3.

The reader will probably have deduced that rail C has to be switched to +12V for the machine to record. By this means, the record/playback head relay is energised and power is fed to the bias/erase oscillator connected to rail C. Also rail B, which feeds the recording amplifier, is energised via D5 and the record lamp is illuminated. When rail C is energised, the forward bias is removed from the base of Tr3 which cuts off, together with Tr17, thus interrupting the power supply to rail A, which feeds the replay amplifier circuit. Tr17 provides additional smoothing of rail A.

The machine normally starts in the replay mode, which means that rail A is available, and rails B & C absent. The change-over is achieved by pressing S2, which makes only for the duration of being pressed. This short-circuits Tr2, and in so doing connects the base of Tr1 to earth via R3. Since the emitter of this pnp transistor is at +12V the device turns on, so applying power to rail C and establishing conditions for recording as previously described. Also, as rail C is now at the +12V level, this voltage is applied to the base of Tr2 via R5, so turning the device on. As a result, the conduction of Tr2 keeps Tr1 turned on even when S2 is released. The circuit is now said to be "latched-up".

Switch S3 is mounted on the deck mechanism and closes when a cassette is inserted. This open-circuits the base feed to Tr2 when the cassette is

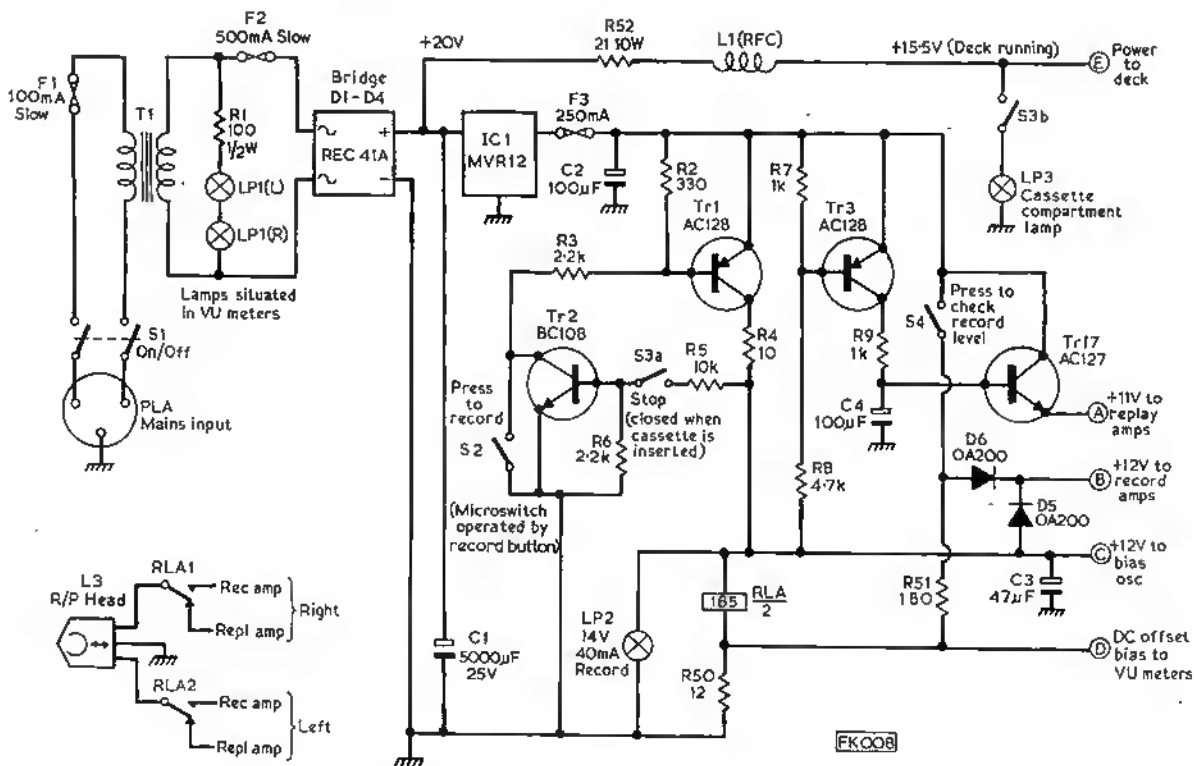


Fig. 2: Circuit diagram of the power supply and electronic switching. Relay RLA connects the record/playback head to the appropriate amplifier.

ejected, so "unlatching" the record switching circuit and ensuring that the machine has reverted to the play mode. It will be seen also that interruption of the supply mains will likewise result in the circuit unlatching.

Switch S4 is provided so that it is possible to monitor an incoming recording signal on the VU meters without having to have the machine actually switched fully to record. It connects the stabilised +12V supply via D6 directly to rail B, which feeds the recording amplifier. Diode D5 is reverse-biased under these conditions so no power is fed to the erase oscillator, head switching relay, record lamp or latching circuit. When starting a new recording directly, the cassette is inserted while S2 is held down. C3 and C4 are antiparasitic capacitors while R4 and R9 are surge-limiting resistors.

A lamp is provided in the cassette compartment, which enables the amount of tape used to be assessed. It illuminates the cassette from above, so enabling the tape to be seen in the window. Because this lamp is situated near the record/playback head, it is fed with smoothed DC to avoid any problem from hum pickup. For long life, a 24V bulb is used.

BIAS AND ERASE OSCILLATOR

In Fig. 3 we show the circuit of the bias and erase oscillator. The tuned circuit consists of L2, C6 and C7. The junction of C6 and C7 provides a capacitive tap across the circuit which is used as a feedback point. The operation is based on the use of complementary transistors Tr4 and Tr5. Each transistor in effect represents a differential load, the emitters working into the feedback point at the junction of C6 and C7. Voltage magnification takes

place across the tuned circuit, and this is coupled to the base network of the transistors by the capacitor C5. Resistors R12, R13, R14 and R15 bias the transistors on sufficiently at the application of power to enable the circuit to commence oscillation. The use of this type of circuit, being symmetrical, reduces even harmonic distortion which can seriously impair the signal to noise ratio. Odd harmonics have far less effect.

The bias signal is taken from the top end of the erase head. Two levels are provided, one for standard

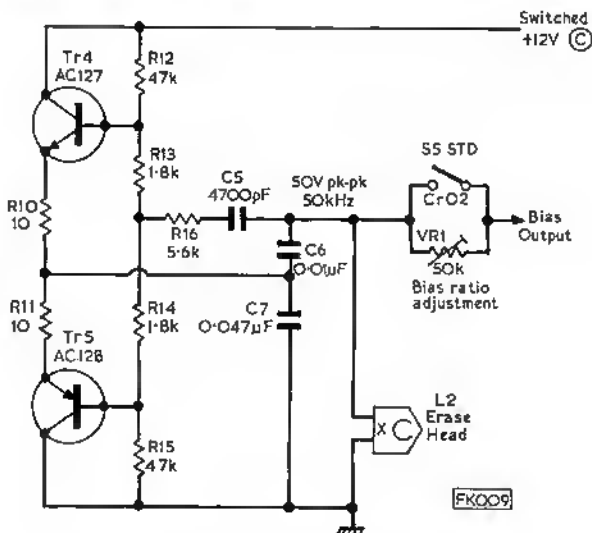


Fig. 3: The bias and erase oscillator circuit uses the erase head as its inductive element.

and one for chromium dioxide tape. The higher level for chrome tape is achieved by shorting out VR1 with S5. Setting-up instructions are dealt with later.

RECORDING AMPLIFIER

Now we come to the recording amplifier, shown in Fig. 4. This amplifier has to lift the incoming signal to a suitable level, and feed it to the head in the recording mode. It is also necessary to provide a meter for monitoring signal level.

The first stage, Tr6, uses a low-noise BC109c to amplify the low-level microphone signals. The auxiliary input from the DIN socket is attenuated down to microphone level, and is connected when the microphone is removed from its jack. While it may be thought that the signal to noise ratio will suffer because of this, in fact the arrangement is completely satisfactory. The recording level is adjusted by VR6, which is placed immediately after the input stage.

The more complicated part of the circuit involves Tr7, Tr8 and Tr9. This section is the recording amplifier proper, and we must first consider its special requirements.

The head has an impedance of 18k Ω at 50kHz, and requires a bias current of 500 μ A. 9V rms of bias therefore have to be present across the recording head, and this signal will obviously feed back into the recording amplifier via R30.

It is common practice to insert a parallel tuned circuit, resonant at the bias frequency, in series with the audio feed to the head. This "bias trap" prevents the bias entering the recording amplifier. The reader will realise, of course, that this involves coils, one in each channel of a stereo recorder. Our design has obviated the need for a bias trap coil, by rendering the effective output impedance of the recording amplifier extremely low at 50kHz. R30 and the output impedance form a potential divider, which ensures that less than 100mV of bias is found at the output of the recording amplifier.

It may not be obvious why the bias should be kept at a low level within the amplifier; one reason is that an excessive level would limit the output swing available, so introducing premature overloading and intermodulation. Another reason is that the bias is really an interference signal as far as the audio is concerned, and spurious beat frequencies can occur resulting in "birdies" on the final recording.

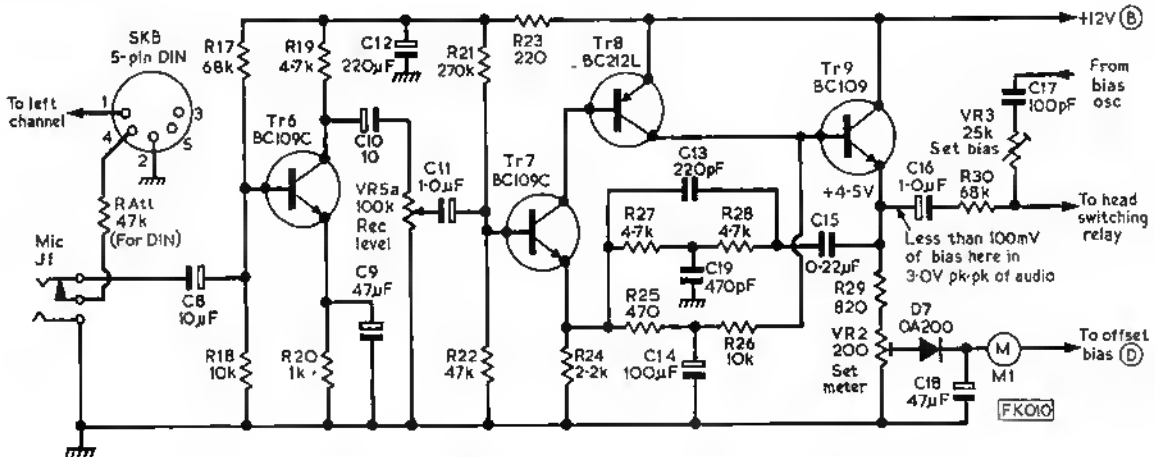


Fig. 4: Circuit diagram of one channel of the recording amplifier. VR5 is a dual-ganged slider potentiometer with one track controlling the record level and the other the playback volume.

In order to record linearly, it is necessary to ensure that the output impedance to the head is high. The effects of head inductance are thereby swamped and the current through the head will be proportional to the applied voltage. It follows therefore that the magnetisation of the tape will be proportional to the input voltage—the signal we wish to record. The simplest means of achieving the required characteristic is to place a resistor in series with the head. Obviously this involves a loss of signal, but we should remember that the head only needs 50 μ A of recording current into an impedance of 500 Ω .

The recording amplifier is designed to produce about 3V peak to peak signal, at low impedance, which is then fed to the head via the 68k Ω resistor R30. It should also be remembered that we have to introduce a bias signal into the head. This is adjusted to the correct level by VR3. C17 represents a high impedance at audio frequencies while allowing the bias signal to pass with little attenuation.

We shall now examine the output end of the recording amplifier in detail. Three transistors are employed, the first two forming a complementary amplifier pair, with the last acting as an emitter-follower to provide a low output impedance. The DC working point of the circuit is stabilised, the components concerned are the input potential divider R21-R22 which sets the base level of Tr7, R24, R25 and R26. R25 and R26 form the upper leg of a divider completed by R24.

Substantial DC feedback is therefore applied around the complete loop. AC feedback around this path is prevented by decoupling R25 and R26 with the capacitor C14. R25 therefore represents, in parallel with R24, an impedance across which AC feedback may be introduced. The AC feedback network consists of C15 (DC blocking), R27, R28, C13 and C19. C13 has a low impedance at the bias frequency and allows heavy feedback to occur at 50kHz. This maintains the low output impedance at bias frequency referred to earlier.

★ components list

Resistors

R1 100Ω	R19 4.7kΩ	R37 220kΩ H.S.
R2 330Ω	R20 1kΩ	R38 47kΩ
R3 2.2kΩ	R21 270kΩ	R39 2.2kΩ
R4 10Ω	R22 47kΩ	R40 10kΩ
R5 10kΩ	R23 220Ω	R41 330Ω
R6 2.2kΩ	R24 2.2kΩ	R42 2.2kΩ
R7 1kΩ	R25 470Ω	R43 1kΩ
R8 4.7kΩ	R26 10kΩ	R44 5.6kΩ
R9 1kΩ	R27 4.7kΩ	R45 27kΩ
R10 10Ω	R28 4.7kΩ	R46 33kΩ
R11 10Ω	R29 820Ω	R47 4.7kΩ
R12 47kΩ	R30 68kΩ	R48 15kΩ
R13 1.8kΩ	R31 470kΩ H.S.	R49 4.7kΩ
R14 1.8kΩ	R32 100kΩ H.S.	R50 12Ω
R15 47kΩ	R33 2.2kΩ	R51 180Ω
R16 5.6kΩ	R34 10kΩ	R52 21Ω 10W
R17 68kΩ H.S.	R35 100Ω	Ratt 47kΩ (DIN)
R18 10kΩ	R36 2.2kΩ	330kΩ (0.5v)

All 1/4W ± 5% except R52

Variable resistors

VR1 50kΩ	VR2 200Ω	VR3 25kΩ
VR4 100kΩ	all skeleton presets	
VR5a/b	100kΩ + 100kΩ dual slider, log.	

Capacitors

C1 5000μF 25V	C12 220μF 25V°
C2 100μF 25V	C13 220pF (C)
C3 47μF 25V	C14 100μF 10V
C4 100μF 25V	C15 0.22μF (P)
C5 4700pF (P)	C16 1μF 25V (T)
C6 0.01μF (P)	C17 100pF (M) or (S)
C7 0.047μF (P)	C18 47μF 10V
C8 10μF 10V	C19 470pF (M) or (S)
C9 47μF 3V	C20 10μF 10V (T)
C10 10μF 25V	C21 100pF (S)
C11 1μF 25V	C22 100μF 10V
	C23 50μF 25V
	C24 10μF 25V
	C25 100μF 10V
	C26 0.1μF (C)
	C27 0.01μF (C)
	C28 0.01μF (C)

C29 0.022μF (C)

C30 10μF 25V

C31 1μF 25V

C32 220μF 25V

Key to capacitor types: (C) Ceramic, (M) Mica, (P) Polyester, (S) Polystyrene, (T) Tantalum. Remainder electrolytic.

Semiconductors

Tr4, Tr17, AC127 Tr1, Tr3, Tr5 AC128
 Tr2 BC108 Tr9, Tr12, Tr14-Tr16 BC109
 Tr6, Tr7, Tr10 BC109c Tr8, Tr11, Tr13 BC212L
 D1-D4 100V 2-2A Bridge D5-D7 OA200
 D8, D9 OA91 IC1 12V Regulator in TO3
 can (RS Components MVR12)

Switches

S1 DPST Min. toggle switch
 S2 SPST Sub-min microswitch
 S3 Part of deck assembly
 S4 SPST Push switch
 S5 DPST Min. toggle switch

Miscellaneous

T1 15V 1-8A secy.; RLA 4pco Min. Relay, 12V coil;
 M1 100μA Miniature edgewise meter with lamp-
 holder;
 L1 2A 9μH Suppressor choke; L2 Erase head;
 L3 Record/playback head; (L2, L3 supplied with
 deck)
 F1 100mA Delay fuse with holder; F2 500mA
 Delay fuse with holder; LP1 6V LES Lamp; LP2
 14V 40mA Red lamp; LP3 24V LES Lamp with
 holder; J1 3.5mm switched jack; PLA Mains plug,
 3-pin, with socket and lead; SKB 5-pin DIN chassis
 socket (180°); Cassette mechanism Goldring-Lenco
 CRV, stereo with DC motor.

NOTE

Two each of the following components are required for the two stereo channels:—
 R17-R49, Ratt, C8-C32, Tr6-Tr16, D7-D8, M1,
 J1, VR2-VR5, LP1.

The symmetrical network R27, C19 and R28 produces negative feedback falling off at the higher audio frequencies, and this offsets head and tape losses by providing a degree of emphasis at these frequencies. On replaying the tape, the levels are restored to normal, and noise is reduced by the same process.

The signal for recording appears at the emitter of Tr9 and is applied to the recording head via C16, the DC blocking capacitor, and R30, mentioned earlier. The emitter load is completed by R29 and VR2. A proportion of the voltage developed across VR2 is applied to diode D7. This silicon diode needs approximately 600mV applied in the forward direction before it can conduct, and the setting of VR2 enables the diode to be biased to a point just short of conduction. Audio modulation causes the voltage to increase on positive half cycles, so that current "spills over" through the diode and into the capacitor C18. The selected V.U. (Volume Unit) meter has an impedance which needs no further series resistance, and the meter is connected directly to C18.

The time-constant of C18 and the V.U. meter impedance is chosen so that the circuit has a

sharper attack than decay time, enabling peak modulation to indicate reasonably quickly. Since the V.U. meter is effectively buffered by R29 from the emitter of Tr9, the non-linear characteristic of the diode and meter circuit is prevented from having a distorting effect on the audio signal.

A relay is used to connect the head to either the recording or the playback amplifier as required. The relay is RLA shown in Fig. 2. To offset the DC bias applied to the V.U. meter via D7, the earthy side of the meter is returned to R50, placed between the relay coil and earth.

Next month, in Part 2, we describe the replay amplifier and dynamic noise reduction circuitry and the motor control, before passing on to the first stage of construction—building the cabinet.

ON THE AIR

AMATEUR BANDS

by Eric Dowdeswell G4AR

COMMENT accompanying the many logs this month seems to favour a listeners competition of some kind. While I am only too glad to organise one and even arrange some small trophy there remains a basic problem. How does one submit confirmation of stations heard? It is bad enough getting QSL's I know and indeed quite costly these days but if the competition is to have any worthwhile meaning then how are the claims of the leading contenders to be verified? We all know it is too easy to sit down and copy the calls of DX stations being worked by some high power G DX'er without being really sure that we have genuinely copied the call of the DX station ourselves! Transmitting amateurs can get QSL's or submit a statement that the QSL's have been seen by some responsible club official but what can the SWL do? Submit a tape recording? How about the first SWL to submit a card from an amateur station in each of the six continents after a certain deadline? Jot down your ideas with your next log.

First newcomer this month is **A. Doherty** (Portrush, Co. Antrim) whose FR50B brought in 'funnies' BY1MAO and ZA1ZA among an otherwise excellent log for 80m SSB. Also has a war surplus R119 probably best employed as a paper weight! Sorry, forgot to say he is also BRS34968. **Stephen Terry** (Banbury, Oxon) has had his dormant interest in SWL'ing revived by a strong injection of FR50B producing a good assortment on four bands. I hope, Stephen, you will do the set justice by feeding it from a decent aerial in future. A first letter from **Stephen Lawrence A8719** (Market Harboro) reports a string of JA and allied prefixes on 15m from his 9R59DS and multiband dipole plus a 180ft wire. His sole goodie on 80m was VS6DO with infrequently heard KL7 on 20m.

Next newcomer is **Roger Trett** (Norwich) who reports a 'new toy in the shape of a Yaesu FR50B'. He's concentrating on getting a 30ft tower up soon complete with 8 element yagi for 2m plus a good long wire for the HF bands. Which will all come in very useful after Roger has passed his RAE which he will have taken by the time this appears in print. Back to regular **Tim Charles** (Colchester) who supports the idea of a band/countries sort of table in which he would be well away judging by his figures.

But he admits to just one country on 160m! Something wrong somewhere OM . . . this past weekend I worked 12 countries on CW including four W's in a few hours operating in the CQ WW contest. Make a point of listening in the CQ 160m CW contest during the last weekend of January, when intense activity can be assured. Tim seems to be convinced that Father Christmas will be wanting a large stocking in which to deposit a new receiver on the big day!

Steve Blake (Aylesbury) has parted with his ex-WD gear in favour of a Codar CR70A plus PR30 pre-selector and homebrew ATU. Steve A8597 is appalled, like many others, at the behaviour of certain people on 80m and trusts that they will eventually grow up one day. Hear, hear! Steve's plans include a move to 2m with a converter and cubical quad. **Michael Green A8088** (Northwich, Cheshire) reports that ST2AY is old friend GW3UPK, heard on 80m (and sought by me on 160m!) and that JY9US is ex-W3HLR c/o US Embassy, Aman. **Paul Barker** (Sunderland) our SSTV expert reports a fine catch in K0YKJ Boulder, Colorado on 21MHz SSTV. Contest prefixes noted were CV4 Uruguay and CT7 Portugal.

Max France (Warrington) has made a scoop with ZL4JF on Campbell Island on 80m SSB which must be near the ultimate in DX from this part of the world, while still remaining earthbound! Max reports a move to the relative quiet of 160m copying 15 countries on SSB over the weekend. Tim Charles to note! Max is also an RAE-taker in the December exam and we wish him luck. **John Porter** (Baslow, Derbys.) also noted strange prefixes such as CF Canada and those mentioned above, plus 9H4 the pretty little island of Gozo nestling alongside Malta.

Eric Carlington (Lymington) stuck to 10m in contrast to most other reporters finding the band open from 0800 to 1630 with such juicy ones as WB2VUO/VQ9 on Chagos Is. and VQ9HCS on Astove Is. **Tim Charles**, again, reporting on his go in the 40m SSB contest when he copies 277 stations 'without stopping up all night!' His best, in my opinion, was KS6DW, a good one on any band.

Back to the first-loggers in the form of **John Martin A8781** (Kingsbridge, S. Devon) who recently completed the building of his Heathkit SW717, coupled to a tapped dipole. John, only 16, is studying for his RAE and learning Morse and putting up some verticals and putting an S-meter in his set and, and . . . where on earth does he get the time! **Andrew Swiffin's** first log to the column also concentrated on 10m. His PW Comprehensive Multiband receiver is fed with a multiband dipole mounted in the loft. I forgot to say that Andrew is A8603 and lives in Cheadle, Cheshire.

Log extracts

Tim Charles:—80m PJ8KGI ZL2GX ZL3ES ZL4AV 601AO 9M2AQ 40m FB8TD OA4XX XT2MB YN0KI ZL2VC 5T5TS 5V4IW 20m DJ6QT/CT3 FK8XA HL9KT KG6SX T19K ZLIKE ZL3SW 5T5KFZ 9H4D.

A. Doherty:—80m FL6CVC PJ2CW S21CW VP8NP 4S7PB.

Stephen Terry:—80m FL8DJ OX3DL S21CW ZD7FT 20m DU2VZ KX6BU ST2SA VR6TC ET2AP 8P6FU 15m A9XV ZD3G ZE6JL.

Stephen Lawrence:—80m VS6DO 15m JA0PFU JG1OQZ JR1MCK.

Roger Trett:—20m P29FV ZF1XG 15m FY7AN H18MAG 10m CR6RJ 9G1AR.

Steve Blake:—80m EP2LT FL80M JY3ZH KS6DH VPIFF YK4TU ZL3ACJ 20m 3D2AJ 3D2AN (Fiji) 15m VP9HM YN9GL.

Michael Green:—80m JY9GR ST2AY VP9AF 20m JY9US VS5MC ZD3M 15m HS4AFD.

Paul Barker:—20m CT7SH CX7B JY9US VP2MCU XU1DX (Khymer Rep.) 7P8AQ 7X0WW 9L7JT 15m CV4C K0YKJ (SSTV) 10m A4XFE (Oman) HZ1KE 3B8CV.

Max France:—160m HB0LL OE3AML OH3MG PA0HIP 4X4UR 4U1TU 9H1BX 80m CR7JO EP2TW FC6CX EP8DH HZ1KE ST2AY TN8AD 5R8AC 7X4MD.

John Porter:—15m KV4AD KZ5BC TU2EF 20m DUXKE FP8DH HZ1TA MID OY1A PZ9AA VP8NS.

Eric Carling:—10m TI3BVF PJ2RR HK4DF FL8HM ZD8RD A6XT ZD3X XU1DX 6W8FP 8RIG.

John Martin:—15m EL2FP KG4NY VP2GTE VP2EY 80m ST2AY UA9GBO ZL4KF ZL4BX.

Andrew Swiffin:—20m KL7HRB ZL1AJL 3D2AJ 4W1GM 15m FY0BHI VP2GMB VP5WW ZB2GM 10m CE6EZ CX5CB CV4C.

CW stations in bold, remainder SSB.

BROADCAST BANDS

MEDIUM WAVE BROADCASTS

by Charles Molloy

ARTHUR TAIT (Lerwick, Shetland) asks 'Am I the only UK listener to clearly pick-up Faroes Radio from Torshavn on 584kHz (513)?' Using an Armstrong 626 tuner-amp and a 25ft loft aerial, Arthur enjoys regular reception of Torshavn in the Faroe Islands and mentions that this station has a request programme on Sunday afternoons at 1400hr. This 5kW broadcaster is sometimes heard in southern UK in spite of interference from Vienna, Paris and Madrid, all on the same channel. It has been logged occasionally by the writer at the 0715hr sign-on, using a communications receiver (Marconi Mercury) and a medium wave loop antenna. Torshavn will verify a correct reception report with a picturesque QSL card which makes the effort involved in logging this elusive station well worth while.

Brendon McNamee has moved from Portrush to Loughborough. He has been using an outdoor UHF TV aerial connected to his Sharp BZ-23 portable

receiver from medium wave reception at his new QTH. His log includes BBC local radio outlets at Derby on 115kHz (271m), Humberside on 1484kHz (202m), Nottingham on 1520kHz (197m), Leicester on 1594kHz (188m). **R. Dixon** who lives in Grimsby has only a limited space available and he wonders what type of aerial would be suitable to hear as many as possible of the BBC and commercial radio stations which have opened up over the British Isles. An outdoor TV aerial (as used by Brendon McNamee) makes a good aerial for use on the medium waves. Connect the outer (screen) of the co-ax TV downlead to the aerial terminal on the receiver and, if possible, connect the receiver earth terminal to a good earth connection. Results will much depend upon the length of the downlead.

Brian Murray, our regular reporter from Edinburgh is still active on the medium wave with his GEC BC3248 receiver and end-fed 25ft outdoor aerial. Brian reports hearing Murcia in Spain on 854kHz at 0023hr, CSB2 in Lisbon, Portugal on 1034kHz at 0030hr; Radio Centro in Madrid on 1385kHz at 0038hr and Radio Swansea was heard testing on 1169kHz. **J. Livsey** (Rochdale) has been having trouble with his ITT/KB Tiny 3 receiver. When tuned to the medium waves, reception is marred by 'a conglomeration of CW, RTTY and a very active amateur band'. The trouble of course lies in the aerial tuned circuit which probably is not working or mis-tuned and image frequencies, 1550 to 2500kHz, are being received at the same time as the medium wave band. Receiver mis-alignment can give similar troubles and whenever weak CW signals are heard at the high frequency end of the MW band, this should be suspected.

Asiatic stations are often heard on the medium waves during the winter months. Listen during the late evening for Kuwait on 539kHz; Riyadh in Saudi Arabia on 587kHz; Kermanshah, Iran on 985kHz; Bagdad on 760kHz; Kabul, Afghanistan on 1280kHz; Kuwait on 1345kHz; Bagdad on 1360kHz; Ahwaz, Iran on 1390kHz and Dubai, United Arab Emirates on 1480kHz. The 1000kW Voice of Free Asia in Thailand transmits on 1580kHz (between W. Germany on 1586kHz and Italy/Norway on 1578kHz). This station comes on the air for half an hour nightly at 2200hr with news in Cambodian and it is often heard here in the UK.

SHORT WAVE BROADCASTS

by Derek Bell

NOW that the Far Eastern DX season is with us, by coincidence comes a letter from **Leonard Adlard** of Leigh-on-Sea, who has a problem. His daughter lives in Bangkok, Thailand and he wishes to hear the same radio programmes that she does in order to establish some sort of link with her.

A pity, Mr. Adlard, but the only thing you will hear is the overseas service of Radio Thailand. This is on 9655 and 12450 aimed at North America, it has news in English but this is at 0045, 1030 and 1115. I personally have not heard them for many a long day but if you care to, contact the Public Relations Dept. Bangkok, Thonburi Metropolis 2, Thailand. However, some of our readers may be able to help so drop me a line folks if you can assist.

Our old friend **Albert Ord** has moved house, now being safely esconced at Bolden Colliery, Tyne and Wear, and he writes that he can pull in the following:



5805 R. Sanaa, Yemen in Arabic at 2000.
 11970 Voice of Nigeria in English at 1830.
 17690 R. Bangladesh in English at 1230.
 on his Trio 9R5 9DS plus Hamgear Preselector and Joystick.

He also heard R.S.A. in Chichiwa on 11970 at 1700, this in itself is not a difficult station to hear, but this part of R.S.A.'s service is not intended for the UK and the aerials would be on a beam for Rhodesia, Zambia and Malawi area. I am sorry Albert, but your question about artificial earth equipment is surrounded by patents and all sorts of legal tie-ups.

November the first, as you perhaps know, heralded the change to winter schedules for many of the short wave stations. K. W. Snipe (sorry no christian name), whose QTH is on the Isle of Wight, notices that the strength of certain stations is dropping and that he has to use aerials of progressively greater length. He also writes to say that Radio Pekin has changed to 7590, 6860, 6270 for their English transmissions.

Robert Hill of Hough, near Crewe, sends us more information on changed transmission times. He writes to let us know that R. Nacional de Brazil now transmits in German and Portuguese on 11780 with a sign-off at 2200. The English service now moves to 9605. Robert, it seems, has a slight problem. Not content with DXing with his Pye Invicta 8027, his GEC UHF TV set has got into the act and he reports that it has been "putting out" the Deutsche Welle signature tune"! Robert then goes on to ask if this is a stray signal. Well, my own TV has given me the Radio Tirana sign-on tune, lying behind a satellite transmission from the US. I would say it is cross-modulation but that blanket covers a lot of freak happenings. Perhaps someone, with more knowledge of TV than I, can provide the answer.

The item on QSL timing in a previous Short Wave News has sparked off some interest, in the form of a letter from a DXer from "way back", namely Lex Arnold. He writes from Hemel Hempstead to send a list of QSL's that have reached him along with the time taken:

Helsinki	1 week
RSA	3 weeks
Pekin	3 weeks

but the top is R. Nacional de Brazil at a staggering five weeks. Lex then goes on to point out that he has heard Polish Pathfinders on 6830 at 1530 with folk and pop music. So come on you music buffs, this is a station that is very rarely reported, have a listen and let us all know what it sounds like.

Two sheets of eye-catching orange note paper herald some very valuable info from Malcolm Collins of Middlebrough. Driving a Prinzsound R888 hooked on to 45ft of wire, this correspondent, in his first try at reporting to SWN, tells us that he has latched on to the Deutsche Welle relay tests from Malta on 9610 at 0030. Malcolm also reports Radio-diffusion Television Ivorienne on 11920 at 2208 in French. This imposing title covers a 100 watter at Abidjan that puts out French and local vernacular programmes for the Ivory Coast.

Radio Norway in English on 6185 at 1200 is the

"cream of the crop" from David Brooks of Melton Mowbray, who has a Grundig "Yacht Boy". It seems that David has the unenviable record of having been waiting 190 days for a QSL from Belgrade. Paul Broadhurst of Tickenham down in the Zider lands of Somerset is a QSL fan and sent me the contrast of Bulgaria taking 270 days and R. Finland taking nine. Finally on QSL's for this month Trevor Bland of Lea, Lincolnshire, writes to ask how long he would have to wait for a QSL from All-India Radio. Sad news Trevor, because back in October they were reported taking 128 days and sending by seamount. Return airmail postage would help!

Northwards to Scotland goes your intrepid reporter now, first to answer Brian Murray of Edinburgh, who while listening to his GEC BC3248 which hangs on the end of a 25ft end fed aerial, came up with Radio Norway on 6185 at 1220 in English, the same service as reported by our earlier contributor. Well gents, a little bird tells me that this new frequency was chosen by R. Norway because they found that they were being interfered with by the BBC and to avoid fuss, they moved!

A scion of the clan, Douglas Mackenzie of Griefi is our second Scot and he would like to know something about public service stations, and if any DX club has been formed for them. The short answer Douglas is, NO. Under British law it is illegal to report or to listen to such stations, and therefore no club can be formed in Britain for them.

Three letters now all asking the same thing, D. Vbranch of Annesley, Notts, A. E. M. McCarthy of Southampton, and the gentlemen of High School of Stirling Radio Club. These folk are all newcomers to the short wave scene, and all would like information. To them I can only say that to fulfil these requests would take the whole of this magazine, resulting in the Editor standing me against a wall and shooting me!

What I can tell you though is that Radio Nederland, P.O. Box 222, Hilversum, Holland, publish some superb free leaflets covering most aspects of the hobby and they are well worth getting in touch with.

The time has come for me to close this month's column. To my surprise the mail was 300% up on my first effort, and to all whose worthy efforts have not been included my apologies and keep trying. Two small items to wind up, Reg Kennedy of World Radio Club writes that his times of transmission have changed from January 4th:

1330 to 1345
2315 to 2330
2030 to 2045
0815 to 0830

While for philatelists, Andrew Knock of Witham, Essex, reports that Sri Lanka on 15425 at 1545 on Sundays is now putting out a stamp programme followed by BBC World Service news.

BROADCAST BANDS

Short Wave reports by the 15th of the month to Derek Bell c/o Practical Wireless, Fleetway House, Farringdon Street, London, EC4A 4AD.

Medium Wave Logs to Charles Molloy, 132 Segars Lane, Southport, PR8 3JG.

AMATEUR BANDS

Logs covering any amateur band/s in band/alphabetical order by the middle of the month to Eric Dowdeswell G4AR, Silver Firs, Leatherhead Road, Ashted, Surrey, KT21 2TW.



PW
KEMPTON

CAR STEREO CASSETTE PLAYER

PART THREE

KEITH CUMMINS & TONY FRANCIS*

METALWORK

The mechanism and amplifier panel are arranged side by side in a metal case, whose overall dimensions fit a standard car radio slot. The case is built from four pieces of 16 or 18 s.w.g. aluminium. These are a bottom section with sides formed by bending upwards, a front panel, a rear panel and a lid.

The rear panel, besides providing access for external connections, acts as a heat sink for the four output transistors. The front panel carries the volume, tone and balance controls and a pilot lamp, and is slotted for the insertion of the cassette. The deck mechanism control lever is brought out through a smaller slot. No on-off switch is provided; insertion of the cassette switches the machine on. Automatic ejection occurs at the end of the cassette, while fast wind and manual eject are selected by the control lever.

Measurements for the metalwork are shown in Figs. 5 and 6. To avoid trouble later on, the various parts should be offered up to their appropriate fitting points to ensure that the drilling has been accurately carried out. Burrs should be removed carefully. Failure to pay attention to this point could result in disastrous short-circuits occurring, particularly through the mica insulators on the output transistors. Great care should be taken with the marking and drilling. Remember that it is best to measure twice and cut or drill once, rather than have to start again.

The diagrams should be studied carefully before commencing anything. The most difficult parts of making the case are the bending, which must of course be accurate, and the cutting of the slots in the face-plate. If a bending machine is available the job is easy, so it is worth trying to gain access to one. Failing this, a vice and wooden blocks will have to suffice, though it is best to use 18 s.w.g. aluminium in this case. The cutting of slots requires some very careful filing if the job is to look professional and, even more important, if the cassette mechanism is to operate easily.

ASSEMBLY

When the case has been built, the deck mechanism can be assembled into it using the small bracket shown in Fig. 5 to support the right rear corner. Then the output transistors and other components attached to the case rear panel can be bolted on before it is fitted to the main casing.

Mount the completed amplifier board in the case, and connect it to the remainder of the equipment as shown in Fig. 7. The output transistors are wired to the amplifier board by suitably neat loomed cable connections and the power input and speaker output leads taken through the grommet positions in the back panel.

The connection between the tape head and the amplifier board has to be made, and the controls wired according to the diagrams. Once the controls and panel light have been attached to the front panel (the balance control used in the prototypes was fixed with Araldite), the panel can be finally positioned and secured to the front of the machine.

A 3A fuse should be fitted in the power input line to the machine. The speaker leads can be taken either to separate speaker DIN cable-mounting sockets, or to one 3 pin DIN socket, using pin 2 as a common return.

A check with a multimeter should next be made, using the lowest resistance range, to ensure that no short-circuits are present either in the wiring, across the power input, or from the output transistor collectors to the case. The resistance reading between the bases of each pair of output transistors should be set to zero by adjustment of the quiescent current potentiometers, VR4. Note that the zero position is at opposite ends of the track for the right and left hand channel pots.

TESTING

The fuses should be left out of the output stages at this point and the machine powered up from a tapping on a car battery, say 8 volts, to see whether the mechanism runs. A cassette should be inserted, and if it appears that the mechanism shows signs of running correctly, the voltage may be increased to 12. Keeping the volume down, the current across each vacant fuse position should be metered and adjusted to 10 mA, using the potentiometers VR4. After setting up this quiescent current, the fuses may be fitted and the speakers connected for a test of all functions and controls.

The alignment of the tape head should be checked when playing a cassette. The head is secured by two screws: the one with spring under it (on the right when viewed from the front) is adjusted for maximum treble response. The other screw sets the head height and should not be touched.

* Hamilton Electronics Ltd.

Mark fixing holes in lid and rear plate using lower case section as a template

Mark out each transistor position using mounting washer as template

Brackets for under-dashboard mounting if required.
(fit to case before mounting cassette mechanism)

Drilling key:

a... $\frac{1}{4}$ dia., b...2BA clear, c...4BA clear, d...6BA clear, e...6BA tapped.
*...are drilled 4BA, while accepting 6BA bolt for deck securing, to allow for tolerances.

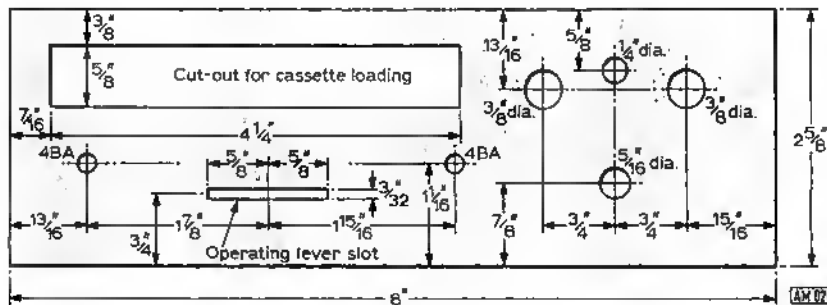


Fig. 5: Dimensions and assembly of the metalwork forming the case.

Fig. 6: Drilling and cutting details for the front panel. The slots for the cassette mechanism must be accurately cut for smooth operation.

Finally, it will be necessary to adjust the motor speed so that the resultant tape speed is correct. VR51 on the motor control panel sets this. A simple way is to use a previously recorded cassette, and time the period a given item runs on another machine. The potentiometer may then be adjusted so that the time taken is the same on the car player.

Now, some remarks on using a positive-earthed system. You will have noticed that the amplifier board earthing occurs via the output transistors and ends up at the deck mechanism. Also, all the output transistors are fitted with insulating washers. Therefore it is relatively simple to reverse polarity on the amplifier section, though the change-over for the deck mechanism needs more care. The alternative arrangements are illustrated in Fig. 7.

A disadvantage of using a positive-earthed system is the fact that the "earth" of the head windings is

then at $-12V$ with respect to the chassis. Care should be taken to ensure that a short circuit between the cable screen and chassis cannot occur at the head.

FAULTFINDING

If all is well with your tests, the machine should now be running normally, and the effect of all the controls may be finally checked before fitting the top cover to the machine and mounting it in the car.

In the event of a fault being evident, the following checks will help to reveal the cause:

1. The emitter voltages of the output transistors should be approximately half the battery voltage.
2. Likewise, a reading of about half the positive rail voltage should be obtained at the emitter of Tr5 and the collector of Tr2 if these stages are operating normally.

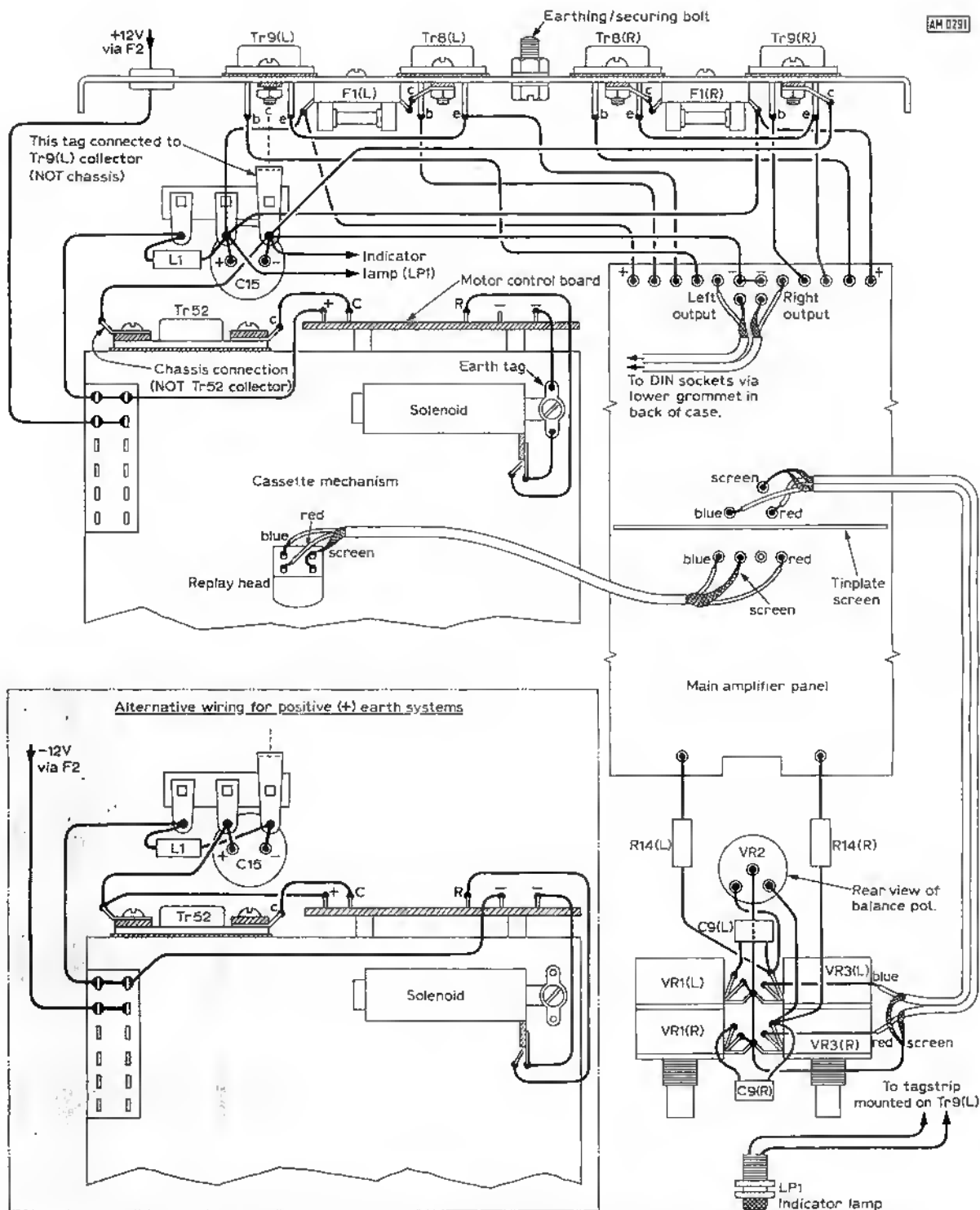



Fig. 7: Wiring diagram, including details of changes required for positive earth working. Connections between the Motor Control board and the motor, the commutating switch and Tr 52 base and emitter are not shown.

3. If one channel operates while the other does not, transposing the leads from the volume control slider between channels will show whether the pre-amp or the main amplifier is at fault. If the output changes channel, the pre-amplifier is defective, while if it does not, the fault lies in the main

amplifier.

It would seem opportune at this point to re-stress the need for constructional accuracy in making up the unit. We are all inclined to think that the other fellows are the only ones to make a mistake, while really we are as fallible as the rest. So be careful,

GOING BACK...

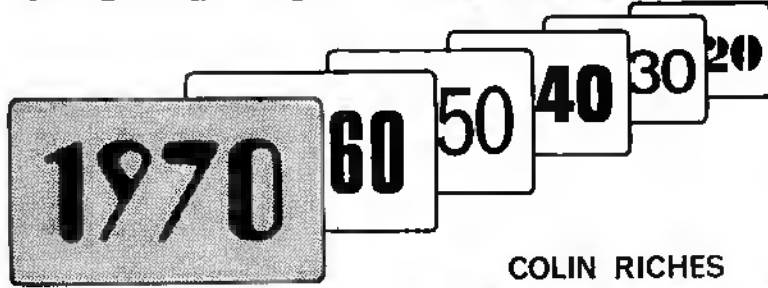


COLIN RICHES

OUR friends at the BBC have issued a record entitled "Fifty Years of Royal Broadcasts—1924 to 1974". This magnificent collector's piece is a natural successor to the very popular record which I reviewed some time ago called "BBC 1922-72, 50 Years of Broadcasting."

This new record is a double-album which recalls some of the most famous and memorable Royal and National events which have taken place over the past 50 years.

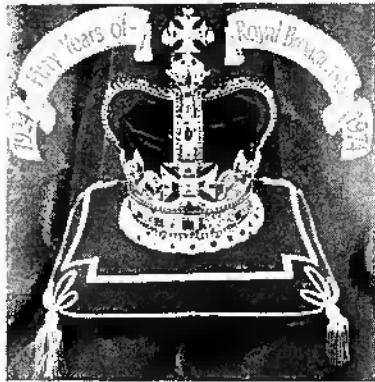
Narration is by Robert Hudson from a script by John Laird. It has been compiled from recordings from the BBC Archives and



The record sleeve which shows a full-colour picture of the Crown.


covers recordings from the very first Royal broadcast in 1924 by H.M. King George V to the wedding of H.R.H. Princess Anne and Mark Phillips.

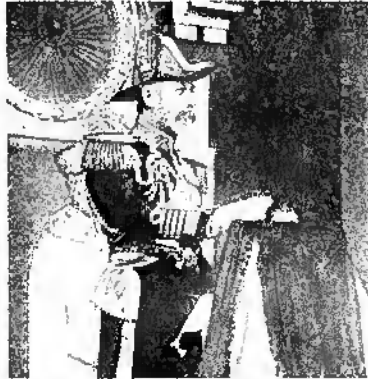Other recordings include the September 1936 march of miners through London singing "Ebenezer"; H.R.H. Prince Edward (1936) making his speech of abdication to the Nation; the two princesses broadcasting to the children of the nation on 13 October, 1940; the Christmas 1944 broadcast by George VI—the last Christmas message of the war—and many others.




23rd April 1924. H.M. King George V opens the British Empire Exhibition. This was the very first broadcast by a British Monarch

It is interesting to compare King George V's formality and sense of wonderment at the miracle of radio in his speech at the opening of the 1924 British Empire Exhibition, with the Queen's wonderful informality when she remarks "My husband and I—we, and by that I mean both of us..." in a speech at a luncheon to celebrate their 25th wedding anniversary. H.R.H. the Duke of Edinburgh also demonstrates his informal approach to broadcasting when he recites a limerick about the "young man from Khartoum."

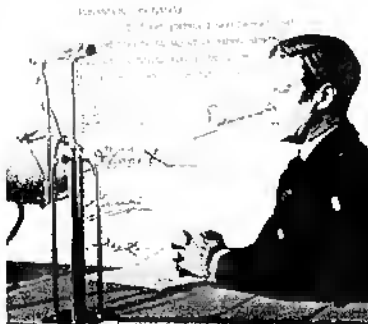

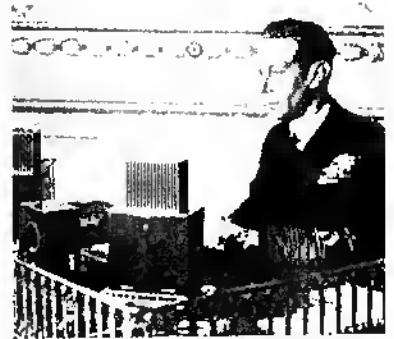11th December 1936. H.R.H. The Prince Edward speaks to the nation from Windsor Castle, following his abdication so that he could marry the woman he loved so dearly.



25th December 1944, H.M. King George VI broadcasts on the last Christmas Day of the war.

This double album also contains reminders of events and situations of national importance like the Rt. Hon. Neville Chamberlain's "peace in our time" speech. The grave voice of Lionel Marson announces the Nazi takeover of Poland in the Second World War. The sounds of war are recorded and on 23rd September, 1940, H.M. King George VI announces the creation of the George Cross for civilian acts of valour. On side 2 of the album the King speaks to the Empire on the last Christmas day of the war. On May 8th, 1945, an excited Stuart Hibberd informs the nation that peace has been declared.

Princess Elizabeth and her little sister Margaret broadcast to the children of the world. They say,



"My sister is by my side and we are both going to say 'goodnight' to you. Come on Margaret! Goodnight children, Goodnight and good luck to you all!"

"When peace comes, it will be for us, the children of today, to make the world of tomorrow a better and happier place."

There is also a very emotional track of the V.E. Day crowds in Whitehall singing "God Save the King."

Side 3 starts with H.M. The King speaking on the first Christmas Day of peace. The 26th April,



21st April 1947. H.R.H. The Princess Elizabeth in Cape Town broadcasts her Speech of Dedication on her 21st Birthday.

1948, Silver Jubilee Celebrations of Their Majesties King George VI and Queen Elizabeth, who speak to the peoples of the Commonwealth is a very interesting track. We also hear a magnificent recording of the wedding of H.R.H. Princess Elizabeth to the Duke of Edinburgh.

John Snagge, on 6th February, 1952, announces the sudden death of H.M. King George VI and there is a beautiful recording of Queen Elizabeth's Coronation in Westminster Abbey.

Side 3 ends with Her Majesty broadcasting to her people on the Coronation Day.

Side 4 starts with the 1953 "Ceremony of the Keys" at Edinburgh Castle, and the Rt. Hon. Winston Churchill speaking in the Guildhall at the luncheon given by the Corporation of London to welcome back The Queen and The Duke after their Canadian tour.

The July 1st, 1969, Investiture of The Prince of Wales is recorded with the Prince proving that he can actually speak Welsh by saying, "Rydych chi'n canu yn iawn. Diolch yn fawr" (Your



Rydych chi'n canu yn iawn. Diolch yn fawr. July 1st 1969—the investiture of the Prince of Wales.

singing is fine. Thank you very much).

The collection of recordings finishes with the wedding of Princess Anne to Captain Mark Phillips.

These two records, which come in a very attractive presentation folder come complete with a 12-page booklet of photographs and excerpts from the speeches. The BBC number is REJ 187 and the price is £4.42.

I would say to you collectors of vintage equipment and recordings and to those of you who just love to bathe in the nostalgia of the "gold old days" that this double album is well worth every penny of the £4.42.

If you want to buy a copy, you can go to almost every record shop in the country. Please don't go to the BBC, however, because they are unable to supply their records and tapes direct. Incidentally, the BBC tell me they hope to issue their records on cassette and cartridge also.

We wish to thank the BBC for allowing us to use photographs contained in the 12-page booklet which accompanies this album.

TAKE 20—continued from page 914

capacitor and from that moment on there will be no change in voltage across it (this, of course, assumes that you do not have a leaky capacitor!). If, however, one is drawing current from the capacitor with a load the charge stored will reduce during the period when the AC input voltage falls away from peak; this causes a slight fall in voltage but is rapidly corrected when the AC rises to its next peak positive value.

The more current one draws from the capacitor the greater will be the momentary fall in voltage. We end up with a 100Hz ripple on the DC voltage across the capacitor. Its frequency is 100Hz because of the full wave rectification action of the diode bridge. The greater the load current the greater will be the ripple. To avoid extreme values of ripple one should aim to have a large value of capacitance which is charged up from as low an impedance source as possible and try to avoid drawing too much load current.

Stabilisation

The foregoing assumes we have no stabilisation but in this case we have included a first order degree of stabilisation which helps reduce the ripple content of the output voltage and also ensures that the output is fairly constant under a wide range of loads and mains voltages. We have adopted the straightforward series stabiliser circuit which is simply an emitter follower (Tr1). The voltage at the emitter of Tr1 will be set by any voltage we apply to its base. In actual fact the voltage we obtain at the

output will be approximately 600mV less than the base voltage because of the forward voltage drop across the base/emitter junction. The base voltage (or reference voltage) must come from a source that is capable of supplying enough current to satisfy the input requirements of an emitter follower. That is to say, we must be capable of passing base current equal to the load current divided by h_{FE} for the transistor in question.

★ components list

T1, transformer, Mains/10V 250mA
 D1/4, 1N4001. D5, 10V 400mW zener diode.
 R1, 470Ω ½W. C1, 3000μF 20V. Tr1, BFY51.
 S1, DPST toggle 250V. Heatsink for Tr1, TO5 style.

We are using a 400mV 10V zener diode D5 fed through a low value resistor R1 to provide this current. Irrespective of the voltage at the top end of R1 the voltage across the zener will be 10V so obviously the supply voltage must be greater than 10V for this to be possible. Consequently any variations in the supply voltage will not change the voltage across the zener. This statement is only true to the first order of approximation because the voltage of a zener is only constant when the current flowing through it is constant. Nevertheless variations in supply voltage produce only small voltage variations across the zener. Having said that the output voltage will equal the base voltage you should now see how we get a reasonably good degree of voltage stabilisation.

HOTLINES

ON RECENT DEVELOPMENTS

THE SIZE OF THINGS

Two items of news have reached me from the US which might be of interest to readers. The first concerns the size of things. Apparently the funds available for "advanced technology research" for 1975 are a staggering \$90 million. This is money made available to the US Army's Ballistic Missile Defense System Command. One of the things that some of this money is to be spent on is miniaturisation—and I do mean miniaturisation. A spokesman is quoted as saying that the size of radar units could be eventually reduced by up to 90%. Since the commercial and industrial worlds of electronics nearly always benefit from the spin-off which comes from the military, readers can appreciate the implications. Perhaps that wristwatch television is just around the corner.

A WATCH ON TIME!

A friendly industrial spy, just back from the US informs that the digital watch scene will almost certainly hot up next year. He visited something like 24 different manufacturers in the States and everyone appears to be manufacturing millions and millions of circuits for digital watches. With a hard time coming for the industry, and these manufacturers having all these circuits to unload, I believe that the digital watch with its current price tag in the UK of £200 or so will come spiralling down very fast indeed. So, if you're going to buy a digital watch—watch it, the market I mean, and perhaps wait a little while and save yourself some hard cash.

DIGITAL MULTIMETERS

Digital multimeters are in the news again but the cheapest I have found is the ISA DMM3. It costs £40 and covers the usual current, voltage and resistance. It does incorporate one clever idea. On the face of it, the voltage range covers up to 1kV. Once the input gets over this the instrument goes into "over-range". This effectively protects it from blowing up. Interesting thing is that the over-range permits double the rating to be used—and the digital readout will display just what this

reading is. So, if you were on the 0-1A current range (for example) and you put 1.890 through it, the readout would read 1.890A. The dodge is that you effectively get twice the range. Thus the 0-1kV range will read, in fact, 0-2kV automatically and the 0-1A current range reads 0-2A automatically and so on.

VIDEO SYNTHESIZER

With accent these days on television "games" such as Tele-Tennis and the like, a topical product is the colour-video synthesizer. What does it do? Well, if you think of sound synthesizers where all sorts of funny little squeaks (some musical others mystical) can be played, then just translate this idea into colour video where all sorts of coloured shapes and patterns (static or moving) can be displayed on a television screen.

The digitally-based system is called Spectre (I might have expected that) and it can display its self-generated images in up to 64 different colours. It also boasts the capability of 16 levels of luminescence and can input also from TV cameras (including monochrome) ordinary film and still life photographs and pictures.

Spectre controls colour and brightness by using digital signals on an X-Y axis technique. The user has a matrix of sockets which can be "programmed" by plugging in diodes to form the shapes, etc. In the pipeline (so I'm unofficially told) is a keyboard which gives the user a chance to "play" preset chords of colour and shapes. I wonder whether Leonardo da Vinci should be played largo or pianissimo, or whether Kenny Ball and his jazzmen will soon give us their rendition of the Mona Lisa?

ENERGY SOURCES

With the ever increasing cost of fuel it just has to mean that there is a great deal of research going into other forms of energy. Any cut back by the US military could mean that effort might be channelled into this energy problem. Just imagine what could be achieved if the effort on energy was the same as that on military and space items.

One area already bearing fruit is that of harnessing solar energy. Admittedly efficiencies are low, but


then it's early days. Up till now, most people have looked upon the solar cell as a discrete "thing" up to 2in. in diameter. Not any more. One go-ahead company has started to produce solar cells, well, not so much cells as strips. This manufacturer is turning out single crystal silicon solar cells which are in ribbon one inch wide by six feet long. Efficiency is given as 10% so far. Maybe this method could outstrip all others?

LED

There's a standard schoolboy joke about things on the other side of the world being upside down, but in electronics it's almost a true statement. Hitachi, the Japanese company, has developed a light emitting diode (LED) display where the light shines through the substrate—sort of upside down. But before you say "Why doesn't somebody tell them", think of the many advantages of doing things upside down. First, it means easier production for people who are using these LEDs. Instead of individually wiring each segment to the circuitry, one can use flip-chip techniques where the contacts from each segment (because they're on the underneath side) can be bonded down direct. Again, in the more conventionally produced LEDs, the contacts on top of the diode tend to block off some of the light trying to get out of the top surface directly above them, i.e., from the viewing surface. In the Hitachi approach, the light is being seen from the other side, the side opposite to the contacts and thus there's no "hole" where these metallic ohmic contacts are. Another point is that gallium phosphide used in these devices has quite a large refraction index. Goody, goody say the Japanese coz that means all the emitted rays of light which strike the internal surface at an angle greater than 17° are totally reflected back internally. Ah so grasshopper, time for you to glow!


Ginsberg

SINGLE FREQUENCY

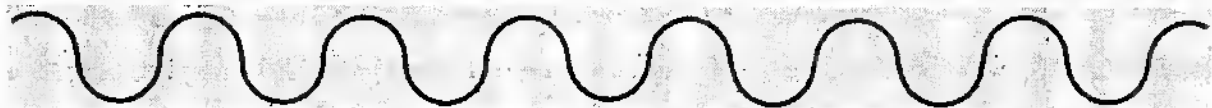

A. FOORD

Audio Oscillator

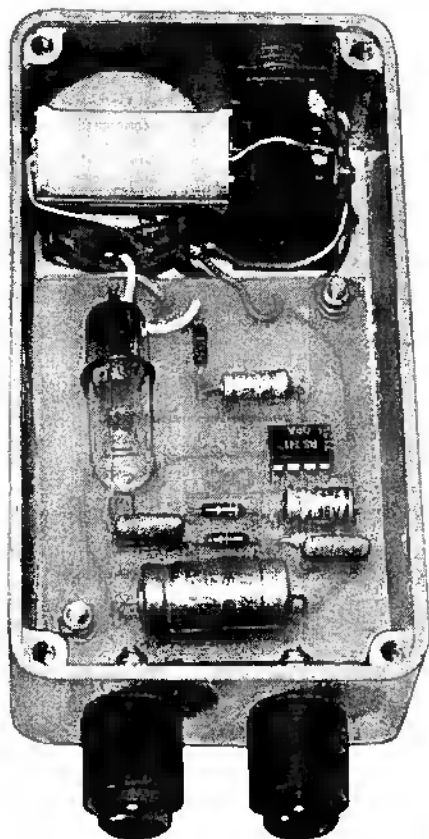

selective network comprising resistors and capacitors.

The basic diagram for the Wien Bridge type oscillator to be used is shown in Fig. 1. Components R1, R2, C1 and C2 form a frequency selective network. In order for oscillation to occur there must be zero phase shift between the input of the amplifier and the output at only one frequency. The frequency selective network acts as a low Q filter having a resonant frequency:

$$f = \frac{1}{2\pi R_1 R_2 C_1 C_2} \text{ Hz}$$

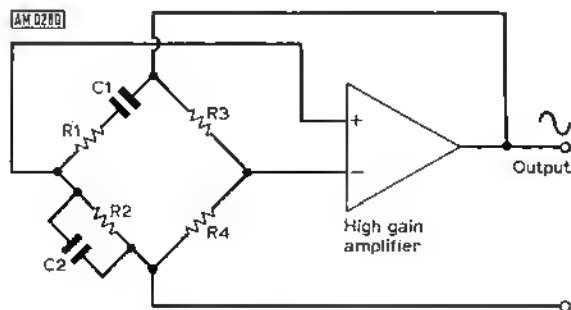


Fig. 1: The audio oscillator is based on the Wien Bridge circuit shown here plus a high gain amplifier.

At this particular frequency the network reduces the signal at the non-inverting (+) input to a third of that at the output of the amplifier. In order to maintain oscillations the amplifier must make up for this loss by having a gain of three.

THERMISTOR STABILISATION

The circuit of Fig. 1 is a perfectly good oscillator in theory, but in practice certain difficulties must be overcome. If the gain of the amplifier is less than three, or the loss of the network more than a third, oscillation will be very slow to build up or at worst may not start at all. On the other hand if the amplifier has a gain of more than three or the network loss is less than predicted then oscillations will build up in amplitude causing distortion to occur. It is clear that some form of automatic gain control is required.

In the practical circuit of Fig. 2 the resistor R1 of Fig. 1 has been replaced by a thermistor TH1. The thermistor has a negative temperature coefficient, i.e. its resistance decreases as it warms up, either because of ambient temperature rises or because current is flowing through it. When power is first applied to the oscillator the cold thermistor will have a high resistance and provided it has been properly

IN audio applications a wide range oscillator is often used with an oscilloscope or audio millivoltmeter to plot the frequency response of an amplifier, filter or tone control. While this approach is invaluable for design work, the basic equipment is expensive and may cost more than a modest hi-fi system.

This article describes a single frequency oscillator which may be used for signal injection where an established design needs testing. Component values are given for operation at 1kHz, the standard test frequency in audio work, but this frequency may be altered over a wide range if it is so desired.

THE WIEN BRIDGE

Resistance-capacitance tuned oscillators are essentially positive feedback amplifiers in which the positive feedback is applied through a frequency


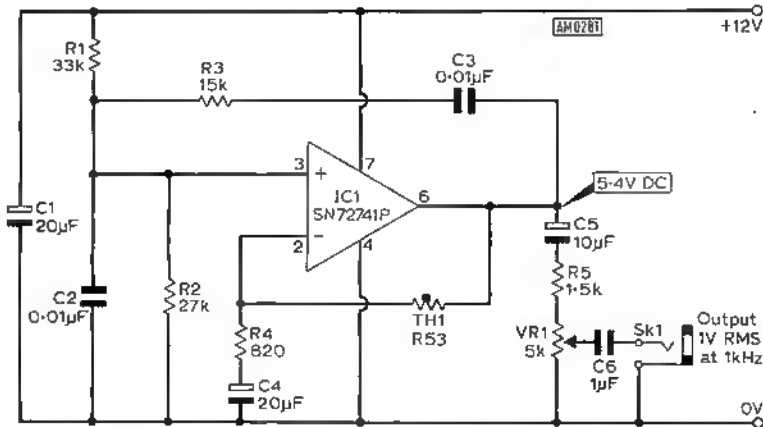
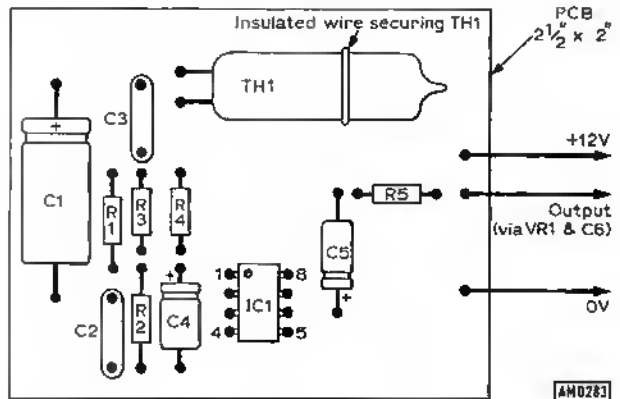


Fig. 2: left, complete circuit of the fixed frequency oscillator. Fig. 3: below, layout for the printed circuit board, shown actual size, together with the component positions. Output control VR1, socket Sk1 and capacitor C6 are mounted on the case, as shown in the photograph.

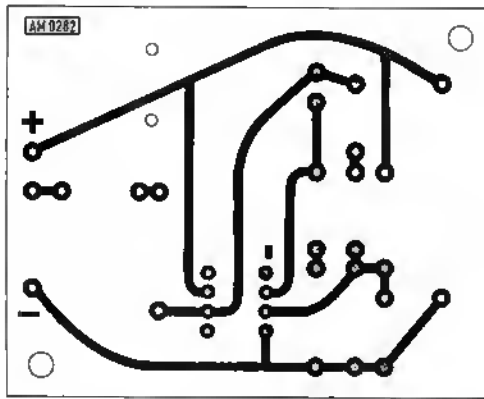

selected will give the amplifier a gain of more than three allowing oscillations to build up quickly. As the thermistor passes current it warms up, its resistance decreases and the amplifier gain is maintained at exactly three giving a low distortion output at constant amplitude.

A high gain operational amplifier type 741 is used in the oscillator but not with its usual dual power supply. Resistors R1 and R2 form a bias network which produce a DC voltage of approximately 5.4V at the output. The output voltage then swings about this point. Resistors R1 and R3 in parallel are effectively the R2 of Fig. 1. The gain of the amplifier is determined by the thermistor resistance and R4.

The capacitors C1 and C4 are decoupling components. The output coupling capacitor C6 is smaller than might be expected for audio applications because the frequency response does not have to extend below 1kHz. This has the advantage that a non-polarised high voltage component may be specified, allowing signals to be injected into high voltage valve circuits if required.

ALTERNATIVE FREQUENCIES

As mentioned earlier other frequencies may be produced by altering the value of the network components. It is easiest to change C3 and C2 since the resistors also form part of a biasing chain. If the frequency is reduced C6 may need to be increased by a similar ratio. The frequency response of the 741 puts a limit on the maximum frequency of a few kilohertz.

★ components list

Resistors

- R1 33kΩ
- R2 27kΩ
- R3 15kΩ
- R4 820Ω
- R5 1.5kΩ
- All 1/4W 5%
- VR1 5kΩ potentiometer

Capacitors

- C1 20µF 25V
- C2 0.01µF polyester
- C3 0.01µF polyester
- C4 20µF 16V
- C5 10µF 16V
- C6 1µF polyester

Integrated Circuit

- IC1 SN72741P (or any type 741)

Miscellaneous

- TH1 Type R53 thermistor
- Sk1 Jack socket
- PCB, case, supply terminals (2), knob

CONSTRUCTION

The construction is quite straightforward. A printed circuit board and component layout are shown in Figs. 3 and 4.

The current consumption of the circuit is only 17mA and any supply voltage from 9V upwards is suitable. Battery operation is quite feasible, thus making possible a self-contained unit.

PRODUCTION LINES

colin riches

CALCULATING PYE

Pye Limited are out for a slice of the £35 million calculator market. They are now offering three models—all featuring rechargeable batteries and mains adaptor/battery recharger.

Model 630 is just a basic calculator and solves normal arithmetical problems (price £35.60). Model 640, priced at £47.70 has a memory store facility and Model 650 (priced at £56.95) performs square roots etc.

Pye Limited, P.O. Box 49, Cambridge.

"SCIENTIFIC" KIT


The "Scientific" pocket calculator is now available in kit form direct from Sinclair Radionics, London Road, St Ives, Hunts, at £19.95.

Apart from the basic four (+ - × ÷) operator keys the "Scientific" incorporates the following additional functions: logarithms to base 10, antilogarithms, sine, cosine, tangent, arcSine, arcCosine and arcTangent. These enable rapid squaring, doubling and x^y including square and other roots. Post fixed operators give full calculation facility on all functions.

Entry and result are in scientific notation with a signed 5 digit mantissa and a signed 2 digit exponent giving the "Scientific" a capacity for very large or very small numbers from 10^{-99} to 10^{99} .

The calculator kit which is powered by four standard Mallory batteries giving around 25 hours of continuous use, can be assembled in around 3 hours. It comprises coil, L.S.I. chip, interface chips, case moulding with buttons, windows and display, printed circuit board, keyboard panel, components pack (diodes, resistors, capacitors) battery assembly and on/off switch, soft carrying wallet plus a comprehensive instruction booklet both for assembly and use. The only additional equipment required is a soldering iron (1/16 inch bit) and a pair of cutters. Any queries regarding construction can be directed to Sinclair's service department. *Sinclair Ltd., London Road, St. Ives, Hunts, PE1 4HJ.*

BATTERY LEVEL INDICATOR

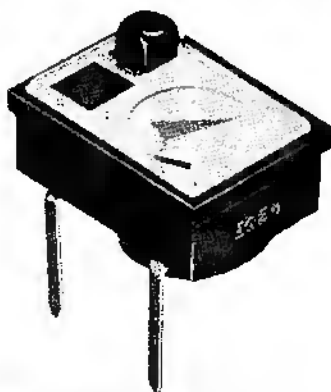

Egen Electric have introduced a low-cost battery-level indicator.

The indicator, which measures 16mm in height and 22mm in width, can be mounted by a spring clip fixing to the case or to a PCB with solder tags. It takes no current until an integral push-button switch is depressed. The pointer then moves into either the red or green portion—the limits being set to match the requirements of the particular circuit it is used in by installing the appropriate shunt or series resistor in the measuring circuit. Details of prices etc. may be obtained by writing to *Egen Electric Ltd., Canvey Road, Canvey Island, Essex, SS8 0PG.*

RECORD CORNER

"Goon Show Classics" (REB 177) is the latest Goon album to be released by the BBC Records and Tapes Department and comprises two famed good show broadcasts. Side 1 is the "Dreaded Batter Pudding Hurler of Bexhill-on-Sea". It was first broadcast in 1954 and tells of the investigation to find out who had the audacity to chuck 38 batter puddings at little Minnie Bannister.

Side 2 features the "Mysteries of Pliny the Elder"—broadcast in 1957—and tells of a football match in the E.U.F.A. Cup between the Ancient Britons and the Romans.


Not many comedy shows have had such a profound and lasting effect on the British public as the Goon Shows and though it is now over 20 years since the first Goon Show was broadcast, the BBC feel there is still a tremendous interest shown in the zany humour of Messrs. Milligan, Secombe and Sellers.

Both shows feature these three plus the Ray Ellington Quartet, Max Geldray and Wallace Greenslade.

The record is priced at £2.46 and is available from most good record stores.



UKA STEREO-8

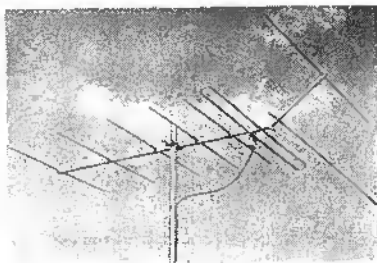

This eight-element model is the star performer in the extensive Fuba aerial range imported into the UK by Audio Workshops Ltd.

Designed for reception in the worst possible conditions the Stereo 8 will often provide good signals in areas where previously no useful signal was obtainable. Particularly suitable for long-distance reception, continental or otherwise, the Stereo 8 is probably the highest performance i.m. aerial available in the UK—as its development is the result of technical design applications by Fuba's team of professional equipment engineers.

The model has a detachable junction box with correct matching for either 75Ω coaxial cable or 300Ω balanced twin feeder. This feature, which is almost unobtainable from UK manufacturers, gives the UKA Stereo 8 unparalleled matching characteristics. The junction box is designed for simple, very easy cable fitting with no screws to lose. It will easily take any diameter of cable. Fitted with a double reflector for best front-to-back ratio, the aerial performance is fully specified according to internationally recognised procedures. The rectangular boom gives strength and correct element alignment thus avoiding the "hedgehog" effect well known in this country and the aerial is designed for outdoor use, but may be left mounted.

Clamps are supplied to suit masts of up to 2 inch (50mm) diameter.

All alloy parts have a protective coating for longer life, and steel parts are cadmium plated to provide protection from corrosion and rust.

Technical specification: Gain: 2·8 to 9·9dB (average 9·0dB). Front-to-back ratio: 20 to 27dB (average 24dB). Standing wave ratio: Typically 1·2 over most of the band, covering the full internationally agreed European band. Cable connection: Unbalanced coaxial cable or balanced twin feeder. Output Impedance: 75Ω unbalanced or 300Ω balanced, balun incorporated in junction box.

Audio Workshops, 29 High Street, Robertsbridge, Sussex.

EKCO ZU440

Another unit from the Pye/Ekco stable is the ZU440. It is described in some circles as a TAPC/DJ—that's sales jargon for a tuner/amplifier/player/cassette unit. The "DJ" part stands for "disc jockey" facility—this enables announcements to be made over the loudspeaker system whilst using tuner, records or cassettes. Output power of the amplifier is 15W per channel. The turntable motor is belt-driven and the cassette recorder has a special magnetically-coupled clutch. A DNL switch on the recorder can be used when recording quiet passages of music to cut down hiss.



The ZU440 has a built-in amblophony circuit which simulates quadraphonic sound (they call it "Stereo 4") when two extra speakers are used. Other features include switchable AFC, automatic recording level control, stylus pressure gauge and four preset push-button controls on the stereo tuner in addition to manual tuning. The ZU440 comes complete with matched teak-veneered speakers with 8in. bass/midrange drive unit and 1in. dome tweeter.

The recommended retail price of the ZU440 is £273·93 and further details may be obtained from Pye Limited, P.O. Box 49, St. Andrews Road, Cambridge, CB4 1DS.

TEXAN-SWEDISH STYLE

The "Texan U66", which we had on show at the recent Audio Fair is not available in Great Britain in kit form at the present time.

Many visitors to our stand showed a great deal of interest in the U66 which also employs an FM tuner with preset tuning controls.

The phono input impedance at 1kHz is 47kΩ and sensitivity for 25W output is quoted as 3·4mV.

Tape input impedance at 1kHz is 100kΩ and sensitivity is variable with a 100mV minimum. Tape recorder output is 100mV.

Tone controls: Treble = ±14dB at 10kHz. Bass = ±16dB at 25Hz. Top Cut Filter = -10dB at 15kHz and

Loudness = +10dB at 50Hz.

Power output is 25W per channel with both channels driven. Speaker impedance can be anywhere between 4-16Ω. Distortion is quoted as being less than 0·1% at 1kHz (25W).

The FM Tuner section has three preset controls covering the frequency range of 87 to 102MHz. Sensitivity is 2μV and the tuner features AFC. The decoder stereo separation is 50dB at 1kHz. The pilot tone rejection is greater than 40dB and there is automatic stereo/mono switching.

If you would like further information now, please write to U66 Elektronik A. B., (Practical Wireless) Valigatan 8, 411 16 Gothenburg, Sweden.



The U66 Swedish Texan amplifier

SPECIAL PRODUCT REPORT

ULTRASONIC INTRUSION ALARM

"There are two transceivers in this picture. The one you can't see is protecting the one you can".

WITH the recorded increase of petty theft by breaking and entering of private premises, we were prompted to look around the market for a reasonably priced alarm system for domestic use which would afford a general degree of protection.

In view of our previous experience of the Heathkit range, which also has a high degree of interest for the home constructor, the Heathkit GD-39 attracted our attention, for this fulfills both our primary and secondary aims.


The Heathkit GD-39 home protection alarm, as received, was well packed and protected from transit damage.

Following the manual instructions all parts were checked and found to be correct. The easy step-by-step instructions were first read through and then assembly was commenced. After a pleasant and instructive two evenings of construction the GD-39 was completed and ready for setting up.

To avoid upsetting the household a low power 240V domestic lamp was used for initial testing purposes.


In the assembly manual, at the commencement of the operation test, a "caution" is printed regarding the two screws used during set-up. Take heed, for this is important, for the threads of the screws, which play no active part after set-up, are tapped into the SRBP circuit board. In the event of any reader making the same error as we did, for we overtightened one screw, a suitable screw can be affixed to the rear of the board, with a nut.

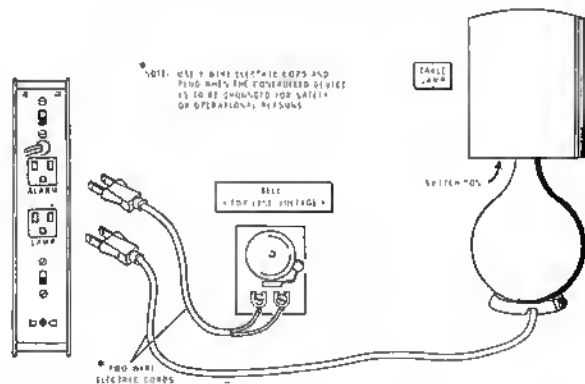With the normal amount of trepidation and holding of



Showing how an alarm bell and lamp can be used with the GD-39.

HEATHKIT GD-39

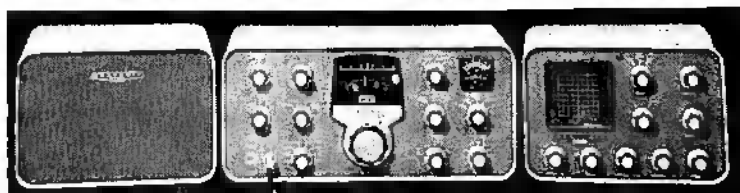

Top shelf, 9th book from the left, the Heathkit GD-39.

MANUFACTURERS' SPECIFICATIONS

Operating range:

Varies with installation. Typical maximum range is 25 feet.

Operating times:

Turn-on delay: Approximately 10 seconds.

Alarm delay: 20 to 30 seconds (lamp-on time).

Automatic reset delay: 20 to 30 seconds (alarm-on time).

Ultrasonic frequency:

Approximately 41kHz.

Power outlets:

Two AC sockets: One for Lamp, one for Alarm.

Power outlet current:

Three amperes total for both sockets.

Power requirements:

110-130 or 220-260 VAC, 50/60 Hz, 1.5 watts.

Dimensions:

Chassis only, 2in wide x 9½in high x 7in deep (approximately). In book-style cover, 2½in wide x 10½in high x 7½in deep (approximately).

Net weight:

Approximately 3 lbs in book-style cover; approximately 2½lbs without cover.

breath, the unit was switched "on". As usual, we were surprised when all went well except for one "dry" joint. At this stage we must make comment on the excellent "Kit Builders Guide" which is issued with every Heathkit. It contains all the general assistance information, to give a beginner confidence to tackle these kits, even if for the first time of doing so.

Our interest now was naturally how the GD-39 would perform under varying environmental domestic conditions, and the following tests were made, carried out in a detached private house.

Tuned to the highest sensitivity, movement of a 6' tall man could not be detected beyond 18' unless movement was

**ALL MAIL ORDER BY
RETURN. C.O.D. SERVICE
WELCOME**

C. T. ELECTRONICS

V.A.T.
Unless otherwise stated all
prices are EXCLUSIVE of V.A.T.
Please add 8% to all orders.
Carriage: orders under £5 plus
20p. Over £5 post free.

All mail order and enquiries to 270 Acton Lane

Tel: 01-994 6275

SEMICONDUCTORS

AC107	35p	BCY32	35p	MM1712	60p
AC125	25p	BCY34	60p	MPP102	45p
AC126	25p	BCY38	60p	MPP103	45p
AC127	27p	BCY39	£1.00	(2N5457)	35p
AC128	25p	BCY55	£1.50	HP104	45p
AC176	25p	BCY70	22p	QN5458	35p
AC188	30p	BCY71	22p	MP105	45p
AC177	25p	BCY72	22p	(2N5459)	35p
ACY18	30p	BD121	75p	OA47	10p
ACY19	30p	BD123	75p	OA70	10p
ACY20	25p	BD124	65p	OA79	10p
ACY21	30p	BD131	60p	OA81	10p
AD140	60p	BD132	75p	OA90	10p
AD142	50p	BD133	75p	OA91	10p
AD149	50p	BD156	75p	QA200	18p
AD161	44p	BDY11	£1.40	QA202	18p
AD162	44p	BDY17	£1.60	QA210	15p
AF114	25p	BDY19	£1.90	QA211	15p
AF115	25p	BDY20	£1.40	OC15	30p
AF116	25p	BF152	20p	OC19	85p
AF117	25p	BF194	14p	OC22	55p
AS221	60p	BF195	15p	OC28	60p
AS223	60p	BF197	20p	OC35	60p
BA102	30p	BF200	30p	OC38	65p
BA112	50p	BE224	30p	OC42	40p
BA114	33p	BFK29	30p	OC44	20p
BA158	15p	BFK34	30p	OC45	25p
BC107	12p	BFK35	30p	OC71	12p
BC108	12p	BFK36	30p	OC72	29p
BC109	14p	BFK38	30p	OC75	25p
BC113	15p	BFY10	35p	OC76	25p
BC115	15p	BFY44	50p	OC77	40p
BC117	20p	BFY50	25p	OC21	25p
BC118	12p	BFY51	25p	OC23	25p
BC147	11p	BFY52	25p	OC24	25p
BC148	11p	BFY53	25p	OC138	30p
BC149	12p	BFY59	25p	OC170	25p
BC153	15p	BSW63	65p	OC171	30p
BC157	14p	BSW68	65p	OC200	60p
BC158	15p	BY127	20p	OC201	60p
BC159	15p	BY164	85p	OC202	75p
BC182	12p	IS100	15p	TIP229A	45p
BC183	12p	IS103	15p	TIP30	55p
BC194	14p	MJ340	50p	TIP31A	57p
BC216	25p	MJ481	95p	TIP32A	69p
BC212	14p	MJ2801	£1.25	TIP33A	£1.00
BC212L	15p	MJ2801	£1.95	TIP34A	£1.40
BC213	14p	MJE340	50p	TIP35A	£3.20
BC214	14p	MJE370	75p	TIP36A	£3.50
BC215	20p	MJE371	90p	TIP41A	70p
BC232	25p	MJE520	65p	TIP42A	85p
BC233	40p	MJE525	£1.20	TIP29B	54p
BCY30	30p	MJE555	75p	TIP30B	60p
BCY31	55p	MM1613	45p		

TIP31B	65p	2N2216	25p
TIP32B	77p	2N2219	25p
TIP33B	£1.06	2N2222	20p
TIP34B	£1.62	2N2224A	25p
TIP35B	£2.71	2N2306	70p
TIP36B	£3.50	2N2377	30p
TIP41B	78p	2N2640	50p
TIP42B	95p	2N2846	£1.50
TIP29C	68p	2N2804	25p
TIP30C	72p	2N2906	25p
TIP31C	80p	2N2907	25p
TIP32C	£1.09	2N2926	12p
TIP33C	£1.29	2N3053	23p
TIP34C	£1.80	2N3054	65p
TIP35C	£3.00	2N3055	50p
TIP36C	£3.74	2N3232	70p
TIP41C	90p	2N3525	85p
TIP42C	£1.00	2N3543	30p
TIS50	40p	2N3702	14p
ZTX107	15p	2N3703	12p
ZTX300	15p	2N3705	12p
ZTX501	20p	2N3706	12p
ZTX502	20p	2N3707	12p
ZTX531	30p	2N3708	12p
ZTX550	25p	2N3717	£1.70
H659	8p	2N3772	£2.50
H659A	8p	2N3773	£2.50
IN316	10p	2N3911	35p
IN4001	8p	2N3920	55p
IN4002	9p	2N3925	85p
IN4003	10p	2N3926	22p
IN4004	10p	2N3925	25p
IN4005	12p	2N4058	12p
IN4006	14p	2N4059	16p
IN4007	16p	2N4060	12p
IN4146	75p	2N4060	12p
2N696	25p	2N4061	12p
2N708	12p	2N4126	17p
2N708A	15p	2N4286	15p
2N715	15p	2N4287	15p
2N716	15p	2N4288	15p
2N730	15p	2N4289	15p
2N732	20p	2N4290	15p
2N733	20p	2N4444	£1.90
2N1302	16p	2N4871	35p
2N1303	16p	2N4903	£1.10
2N1304	25p	2N5069	£1.10
2N1305	25p	2N5191	90p
2N1306	25p	2N5194	£1.10
2N1307	25p	40360	50p
2N1308	25p	40361	50p
2N1309	25p	40362	50p
2N1613	25p	40669	50p
2N1711	25p	40673	50p
2N2147	70p	DE151	£1.00
2N2150	50p	Microwave	
2N2217	25p	Diode	

S.C.R.s	
CRS1/05	40p
CRS1/10	50p
CRS1/20	60p
CRS1/40	60p
CRS1/60	90p
CRS1/80	90p
CRS3/10	80p
CRS3/40	90p
CRS7/400	£1.00
CRS16/100	85p
CRS16/200	90p
CRS16/600	£1.80
C106B	45p
C106D	70p
40669	90p
TIC44	35p
2N4444	£1.90
BT10/500A	90p

TRIACS	
TXL228B 8A 400V	85p
SC40D	£1.40
SC40E	£1.65
SC45D	£1.70
SC45E	£2.10
SC50D	£2.42
SC50E	£2.70
DIAC	25p

★ SPECIAL OFFERS ★

MINIATURE MAINS TRANSFORMER.
PRI 240V. SEC. 12V, 100MA Manual. Hinchley
Size 1" x 0.35" x 0.65" P.C. Mount. Price
100-4p ea. 1000-3p ea.

3 CORE PVC INSULATED MAINS
CABLE. GREY ML6850, 3x7/2mm. Price
100m-£4.50, 1900m-£35, 10,000m-£330.

0-47 mfd. 50V MYLAR FILM CAPACITOR.
Size 1" x 0.35" x 0.65" P.C. Mount. Price
100-4p ea. 1000-3p ea.

240V. A.C. SOLENOID. Reversible operation;
twin coil. Size approx. 2 1/2 x 1 1/2 x 1 1/2 in.
90p ea.

25 unmarked OC71 transistors £1.00
30 Unmarked 250mW Zener diodes, 4-7V,
5-1V, 8-2V, 7-5V, 9-1V, 10V, Measured and
tested £1.00

Please state voltage required.
50 GE Diode OA47 equivalent. £1.00

TRANSFORMER: DOUGLAS PRI. 0, 115,
220, 240 SEC. 25-0-25-0-8V, 2A, £4.50
+ 50p p.p.

TRANSFORMER
PRI. 0, 115, 160, 205, 225, 245. SEC. 35-0-35,
1.2A £4.50 + 50p p.p.

MULLARD TUBULAR CERAMIC UHF
TRIMMERS (PROFESSIONAL)

Type 692 0-8-2-2p } Price 10p ea.
801 0-8-2-2p }
891 0-5-1-3p }

QUANTITY DISCOUNTS PLEASE TELE-
PHONE

1000pF Feedthrough capacitor 5p ea.
Miniature tubular P.C. trimmers
3-5-13pF
6-30pF
MC1300Q £2.25
MC1301P £2.60

10p ea.
50p ea.
4p c/o Varley 700Ω relay

METAL BOXES

ALUMINIUM BOXES IDEAL FOR VEROB-
BOARD WITH BSAE & P.K. SCREWS

AB7	2 1/2" Long	5 1/2" Wide	1 1/2" High	55p
AB8	4"	4"	1 1/2"	55p
AB9	4"	2 1/2"	1 1/2"	55p
AB10	4"	5 1/2"	1 1/2"	55p
AB11	4"	2 1/2"	2"	65p
AB12	4"	2 1/2"	1 1/2"	50p
AB13	6"	4"	2 1/2"	75p
AB14	7"	5"	2 1/2"	90p
AB15	8"	6"	3"	£1.16
AB16	10"	7"	3"	£1.32
AB17	10"	4 1/2"	3"	£1.10
AB18	12"	5"	3"	£1.32
AB19	12"	8"	3"	£1.30

ALUMINIUM BOXES WITH SLOPING
TOP PANEL—IDEAL FOR PRE-AMPS,
ETC., USING SLIDER CONTROLS

AB20 8" Long 9" Wide 3 1/2" High at back £2.20
2" High at front 8" Slope to front

With P.K. Screws
AB21 As above but 10" long £2.20
AB22 As above but 12" long £2.60

ELECTRONIC COMPONENTS

BARGAIN COMPONENT PACKS
ALL COMPONENTS NEW & UNUSED

£1 plus 25p p.p. per pack, £3 for 5 packs p/troe
Pack No.

- 500 Carbon resistors, 1, 1/2, 2 watt.
- 100 Electrolytic Condensers.
- 250 Ceramic, Polystyrene, Silver Mica, etc., Condensers.
- 250 Polyester, Polycarbonate, Paper, etc., Condensers.
- 25 Potentiometers, assorted.
- 250 High-stab. 1%, 2%, 5% resistors.
- 50 Assorted Teststrips.
- 1lb. Assorted nuts, bolts, washers, spacers, etc.
- 25 Assorted switches, rotary, lever, micro, toggle, etc.
- 10 50 Preset Potentiometers.
- 11 Trial mixed component pack £1.
- 12 Jumbo mixed pack £5.

DIGITAL INTEGRATED CIRCUITS

SN7400	18p	SN7427	42p	SN7470	30p
SN7401	15p	SN7428	50p	SN7471	30p
SN7402	20p	SN7430	20p	SN7472	30p
SN7403	20p	SN7432	20p	SN7473	40p
SN7404	20p	SN7433	70p	SN7474	55p
SN7405	20p	SN7437	50p	SN7476	45p
SN7406	30p	SN7438	50p	SN7480	80p
SN7407	30p	SN7440	20p	SN7481	£1.25
SN7408	20p	SN7441A	15p	SN7482	80p
SN7409	40p	SN7442	75p	SN7484	80p
SN7410	18p	SN7443	£1.00	SN7485	45p
SN7411	23p	SN7445	£1.70	SN7490	75p
SN7412	20p	SN7446	£2.00	SN7491A	15p
SN7413	40p	SN7447	£1.50	SN7492	75p
SN7416	30p	SN7450	75p	SN7493	50p
SN7420	20p	SN7451	20p	SN7494	80p
SN7422	30p	SN7453	20p	SN7495	80p
SN7423	38p	SN7454	20p	SN7496	£1.90
SN7425	38p	SN7460	20p	SN7497	£2.25

SN74100	£2.00	SN74165	£2.00
SN74104	£1.45	SN74166	£4.00
SN74105	£1.00	SN74187	£4.25
SN74107	55p	SN74170	£4.10
SN74110	60p	SN74172	£2.00
SN74111	45p	SN74173	£2.00
SN74119	£1.90	SN74176	£1.60
SN74121	65p	SN74177	£1.60
SN74122	£1.35	SN74180	£1.55
SN74123	£2.00	SN74181	£6.00
SN74141	£1.00	SN74182	£2.00
SN74145	£1.50	SN74184	£2.45
SN74150	£1.35	SN74185A	£2.40
SN74153	£1.40	SN74190	£1.95
SN74154	£2.00	SN74191	£1.95
SN74155	£2.55	SN74192	£2.00
SN74158	£1.55	SN74193	£2.00
SN74162	75p	SN74194	£2.50
SN74163	£1.40	SN74195	£1.85
SN74164	£2.75	SN74196	£1.50
		SN74198	£3.00
		SN74199	£2.60

VEROBORD

2 1/2 x 3 1/2	0-1	0-15
2 1/2 x 3	32p	23p
2 1/2 x 5	35p	35p
3 1/2 x 3 1/2	35p	35p
3 1/2 x 5	40p	41p
1 7/8 x 2 1/2	£1.05	79p
1 7/8 x 3 1/2	£1.43	£1.12
1 7/8 x 5	£1.84	

PIN INS. TOOL 72p
SP.F. CUTTER 52p
100 PINS DS 30p
100 PINS DS 30p
300 PINS DS £1.20
500 PINS DS £1.20

ALSO STOCKED

Electrolytic Capacitors, Mullard, Sprague, Lorlin, etc. Polyester, Polystyrene, Silver Mica Capacitors, etc. Resistors 1/4W-10W. Potentiometers; carbon, wirewound, Preset. Rectilinear multitrack, Antex Soldering Irons, switches, rotary, slide, toggle, etc. Cable, veroboard.

POTENTIOMETERS

Linear or Log	Single	Double
Rotary Pots	15p	42p
Relay Switched	25p	

★ SPECIAL OFFERS ★

RECORD PLAYBACK HEADS (TRUVOX)

Individual prices of these are:
 2 track record playback heads 55p each.
 1 track record playback heads 80p each.
 Erase heads are also available separately
 2 track 45p.
 1U metal mounting shields 47p each.
 2 track heads already fixed on heavy mounting plate with shield £1.60.

NEED A SPECIAL SWITCH

Double Leaf Contact. Very slight pressure closes both contacts. 5p each. 10 for 74p. Plastic pushrod suitable for operating. 7p each. 10 for 68p.



1 R.P.M. MOTOR + GEAR BOX
 Made by the famous Chamberlain & Hookham Ltd. These could be made to drive clock or similar. Really robust reliable unit. Price £1.25 each.

AUTO-ELECTRICAL CAR AERIAL

with dashboard control switch—fully extendable to 40in or fully retractable. Suitable for 12V positive or negative earth. Supplied complete with fitting instructions and ready wired dashboard switch. £5.95 plus 25p post and insurance.

MAINS TRANSISTOR POWER PACK

Designed to operate transistor sets and amplifiers. Adjustable output 6v, 9v, 12 volts for up to 500mA (class B working). Takes the place of any of the following batteries: PP1, PP3, PP4, PP6, PP7, PP9 and others. KE comprises: mains transformer rectifier, smoothing and load resistor, condensers and instructions. Heat snip at only £1.50.

MINIATURE WAFER SWITCHES

2 pole, 2 way—4 pole, 2 way—3 pole, 3 way—4 pole, 3 way—2 pole, 4 way—3 pole, 4 way—2 pole, 5 way—1 pole, 12 way. All at 80p each.

MULTI-SPEED MOTOR.

Six speeds are available 600, 800 and 1,100 r.p.m. and 8,000, 12,000 and 15,000 r.p.m. Shaft is 1/8 in. diameter and approximately 1 1/2 in. long. 230/240v. Its speed may be further controlled with the use of our Thyristor controller. Very powerful and useful motor size approx. 2 in. dia. x 6 in. long. Price £1.80 plus 25p postage and insurance.



SLIDE SWITCHES

Slide Switch. 2-pole changeover panel mounting by two S.R.A. screws. Size approx. 1 1/2 in x 1 1/2 in rated 250V lamp. 10p each. 10 for 90p. Ditto as above but for printed circuit 8p each. 10 for 72p. **8-pole Miniature Slide Switch.** DPDT 18mm (Pin approx.) between fixing centres. 20p each or 10 for £1.80. HP Change over spring return 250V 1 amp. 15p.

15A ELECTRICAL PROGRAMMER

Learn in your sleep: Have radio playing and kettle boiling as you awake switch on lights to ward off intruders—have a warm house to come home to. All these and many other things you can do if you invest in an electrical programmer. Clock by famous maker with 12 amp. on/off switch. Switch-on time can be set anywhere to stay on up to 5 hours. Independent 50 minute memory logger. A beautiful unit. Price £2.80 + 20p p. & p. or with glass front, chrome bezel, £1.00 extra.

BALANCED ARMATURE UNIT

500 ohm, operates as speaker or microphone, as useful in intercom or similar circuits. 37p each.

12 VOLT 1 1/2 AMP. POWER PACK


This comprises double-wound 230/240V mains transformer with full wave rectifier and 20000 mF smoothing. Price £2.50 plus 20p post & packing. **Heavy Duty Mains Power Pack.** Output voltage adjustable from 15-40V in steps—maximum load 250W—that is from 6 amp at 40V to 15 amp at 15V. This really is a high power heavy duty unit with dozens of workshop uses. Output voltage adjustment is very quick—simply interchange push on leads. Silicon rectifiers and smoothing by 3,000mF. Price £5.95 plus £1.00 post.

PC BOARD MARKER

Valve action fibre tipped marking pen filled with black etch resist—It's easy with this to make a perfect PC board. Just draw straight on to the copper—allow 15 minutes to dry, then immerse in ferric chloride or other etchant on removal the circuit stands in high relief. 99p.

HONEYWELL PROGRAMMER

This is a drum type timing device, the drum being calibrated in equal divisions for switch setting purposes with trips which are infinitely adjustable for position. They are also arranged to allow 2 operations per switch per rotation. There are 15 changeover micro switches each of 10 amp type operated by the trips thus 15 circuits may be changed per revolution. Drive motor is mains operated 5 revs. per min. Some of the many uses of this timer are Machinery control, Boiler firing, Dispensing and Vending machines, Display lighting animated and signs, Signalling, etc. Price from makers probably over £20 each. Special snip price £7.50 plus 23p post and insurance. Don't miss this terrific bargain.

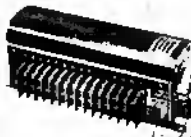


TANGENTIAL HEATER UNIT

This heater unit is the very latest type, most efficient, and quiet running. Is as fitted in Hoover and blower heaters. Comprises motor, impeller, 2kW, element allowing switching 1, 2kW, and with thermal safety cut-out. Can be fitted into any metal line case or cabinet. Only needs control switch. £2.75. Don't miss this. Control Switch, 44p. P. & P. 50p.

STEREO RADIO CABINET

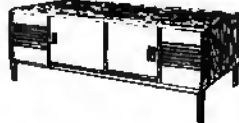Long, Low and Modern. Teak veneered with sliding front and tapered leg. Speaker spaces each end. Size approx. 4ft. 2in x 13in x 15in. Probably cost over £20 to make. Our Price £8.10 each.



TWENTYLITE

Fluorescent lighting units with polyester choke and finished white enamel. 24 in. model. Ideal kitchen, bedroom, hallway, porch, lift, etc., with tube. Assembled ready to install. Price £2.80 + 30p p. & p.



THIS MONTH'S SNIP

SOUND TO LIGHT UNIT
 Add colour or white light to your amplifier. Will operate at 2 or 3 lamp transmission 4-way Unit in Box all ready to work. £7.95 plus 95p VAT and postage.



HORSTMANN 24-HOUR TIME SWITCH

With 8 position programmer. When fitted to hot water systems this could programme as follows:—

Programme	Hot Water	Central Heating
0	Off	Off
1	Twice Daily	Off
2	All Day	Off
3	Twice Daily	Twice Daily
4	All Day	All Day
5	Continuously	Continuously



Butable of course, to programme other than central heating and hot water, for instance, programme upstairs and downstairs electric heating or heating and cooling or taped music and radio. In fact there is no limit to the versatility of this Programmer. Mains operated. Size 3 1/2 in x 3 1/2 in x 2 1/2 in deep. Price £3.65 as illustrated but less case.

SHORTWAVE CRYSTAL SET

Although this uses no battery it gives really amazing results. You will receive an amazing assortment of stations over the 19.25-31.39 & 49 metre bands—Kit contains chassis front panel and all the parts. £1.25—crystal earphone 50p.




MULLARD UNILEX STEREO SYSTEM

There is no doubt that it is a good system, we believe that for the money it is without comparison. We demonstrate gladly at our Tamworth Road depot. Prices of the individual items for this:—

1 Unilex Amplifier	Ref. EP.9000	£1.00
1 Unilex Amplifier	Ref. EP.9000	£1.40
1 Unilex Pre-Amp	Ref. EP.9001	£1.95
1 Unilex Power Unit	Ref. EP.5002	£2.58
1 Control panel kit with spun aluminium faced knobs		£3.30

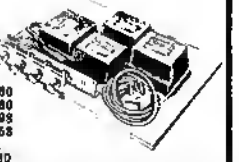Pair of 15 ohm speakers made by Goodmans are also available if required, price £3.30 the pair. No extra postage if ordered with the above, otherwise add 25p.



SPECIAL PRICES TO COLLEGES AND INSTITUTIONS WISHING TO INCLUDE THIS KIT IN THEIR CURRICULUM


SWITCH TRIGGER MATS

So thin is undetectable under carpet but will switch on with slightest pressure. For burglar alarms, shop doors, etc.

24in x 18in	£1.80
13in x 18in	£1.50

HORSTMANN "TIME AND SET" SWITCH

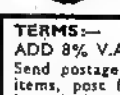(A 30 amp Switch). Just the thing if you want to come home to a warm house without it costing you a fortune. You can delay the switch on time of your electric fires, etc., up to 14 hours from setting time or you can use the switch to give a boost on period of up to 3 hours. Equally suitable to control processing.



Two models 15 amp £2.18, 30 amp £3.35. P. & P. 25p each

AM/FM TUNER

Unit made by the American GEC company. 8 transistors, all-wired ready to work. Complete with tuner condenser, needs only scale and pointer. Tunes AM range 540 to 1620 KHz, FM range 88 to 108 MHz. Switches for on-off and AFC. Output for MXP or direct. Special snip price £5 plus 30p post. Three or more post free.

7 WATT STEREO AMPLIFIER

Again by the American GEC company. This has exceptionally good tone quality. It complete with pre-amp and treble base, volume and balance controls. Also has mains smoothing circuit and rectifiers so requires only mains transformer. Output for 15 ohm speakers. Inputs for tuner, pick-up, mike, etc. Special snip price £8 plus 30p post. Three or more post free.

COMPLETE SYSTEM

AM/FM and MPX Tuner
 Decoder and stereo amplifier. Specifications of tuner and amplifier are approximately as given above. This is ready built and tested system complete with scale and pointer, ready to install into suitable cabinet. (Our big stereo cabinet should be ideal for this.) Limited quantity, £15 each.

AMPLIFIER PANELS

Very nice looking, polished black presspan with fixing holes, 6 phone sockets and changeover slide switch and is printed as sketch. Price is 80p.

BATTERY CHARGERS

Famous Atlas in metal case with meter, output leads terminated by crocodile clips. For 6 or 12V charging simply by changing the plug on front panel. Ready built new and still in maker's original packing. Two models: 1 1/2 amp £1.99 and 3-4 amp £2.95. Please add 40p postage for one and 75p postage for two.



ONLY
£1
 FOR
5
 ELECTRIC MOTORS

5 powerful battery motors as used in racing cars and power models. Output and types vary to make them suitable for hundreds of different projects—tools, toys, models, etc. All brand new reversible and for 10 to 12v. Bats, wiring diagrams included. Post and VAT 30p.

FREE DETAILS OF HOW TO MAKE MINIATURE POWER STATION

NEW ITEMS THIS MONTH

Car Cassette Power Kit. With a stabilised output of 6v, 9v or 12v. The kit comprises transistors, zener diode, resistors and condensers. Price £2.10. Suitable plastic case 40p extra.
Black Light as used in discotheques and for stage effects, etc. Virtually no white light appears until the rays impinge on luminous paint or white shirts, etc. We offer 12" 8w tubes complete with starter, choke, lamp holders and starter holder. Price £2.76 + 30p post. Tubes only £2 + 30p post.
8 KV Rectifiers. For replacement in colour TVs or for experimenting with really high voltage for doublers and triplers, etc. Famous maker. 45p each. Quantity prices available.
Meters. All Bush mounting with 0-2 amp 50p, 0-3 amp 60p, 0-4 amp 75p, 0-8 amp 85p.
Rectifiers. All 25v full wave (bridge) with cooling fan. 11-12 amp 25p, 3-4 amp 25p, 6-7 amp 21.25, 15 watt Screen Grid. Suitable for equipment wiring, multi-way telephone installations, etc. Each core has seven strands copper, PVC insulated and colour coded differently from every other core. These are then laid together encased first by a metal screen and then grey PVC. Price 80p metre or 10 metres £2.50.
Touch Switch. This switch suitable for up to 10 amps mains voltage. Stands up approximately 1" rather like a joy stick and no matter which direction it is pushed, it makes contact. Base size approximately 2 1/2" x 2". Price 25p each.
Light Switch. Automatically switches on lights at dusk and off at dawn. Can also be used where light and dark is a convenient way to stop and start an operation. Requires only a pair of wires to the normal switch. In bakelite box normal switch plate size. 1 amp model £2.85.



exaggerated. At this setting the device was ultra-sensitive to the movement of curtains, within 1' of the unit, disturbed by the wind through an open window.

At the lowest sensitivity, movement within inches of the unit was not detected. The most satisfactory setting was slightly above mid-point, when adequate coverage of a room approx 16ft square was achieved.

However with the unit placed 6ft away from the open doorway of the room, movement was detected in the passageway, and to a limited extent, in two adjacent small rooms. This is due, no doubt, to "spillage" of the standing waves into adjacent areas.

Obviously, the best position for the GD-39 will be, for general use, at a point within the house which must be used to gain access to other areas.

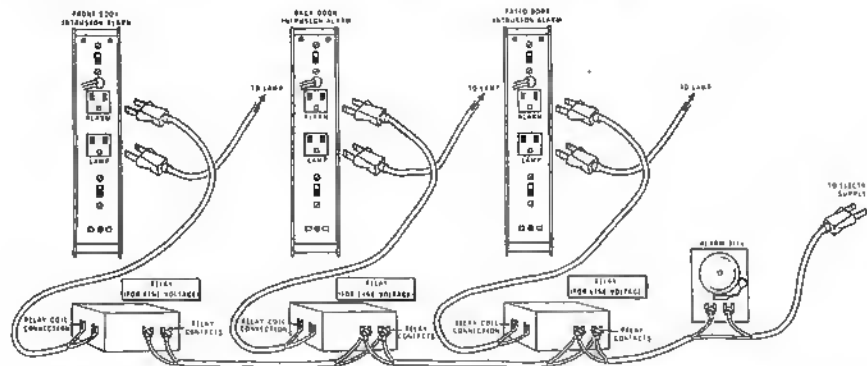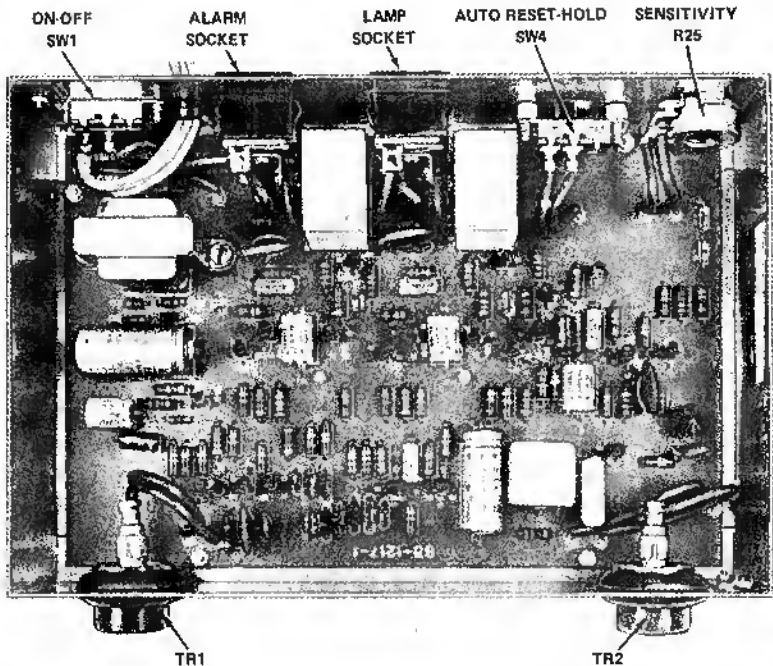Operation of radio and TV sets, electro-mechanical relays, thermostats and fluorescent light tubes failed to create an alarm condition. Convected heat from a gas fire, placed in the proximity of the unit had no effect but a 3kW electric fan heater directed towards the unit, from a safe distance, did so, due no doubt to the high local temperature over ambient.



Printed circuit layout showing component positions, sockets and controls.

Diagram to show how three Intrusion Alarms may be wired to give comprehensive protection to a complete building.

The GD-39 has wiring options for either 110 or 220VAC operation and during assembly take note of the option instructions.

During operation, or under alarm condition, this supply is switched by an internal relay to two USA type sockets at the rear of the GD-39. On our final installation, for we had obtained the optional extras, a.c. mains alarm bell, and quiet buzzer with its transformer, from Heathkit, the alarm bell was wired direct from the outlet socket (and directly earthed), but the quiet buzzer was wired via a relay.

Adequate information is provided in the manual for wiring options. We would point out to our readers, that in event of a mains supply disconnection to the GD-39 it is rendered inoperative.

Normally, more sophisticated systems incorporate a battery standby but this of course would represent cost addition to the price.

Ultrasonic movement detector suitable for providing audible or visual warning of intrusion of a specific area. Can be connected by itself or with other detection devices to a variety of signalling devices or can be used for simple switching purposes. Frequency approx 41kHz. The device is housed in a case which simulates a book approx 10 x 7 1/2 x 2 1/2 in. This disguise could well prevent the device from being noticed by an intruder.

Method of function

An RF signal is transmitted by one transducer. A receiving transducer receives the transmitted signal and monitors it for a change in amplitude. If a change is detected (produced by a moving object) then the lamp and alarm outlets are switched on until they are reset either automatically or manually.

The a.c. mains 6in heavy duty alarm bell was mounted under the eaves at the front of the house. It has not gone unnoticed by neighbours and local tradesmen. One question—in particular that has been asked upon a number of occasions—"Is it connected to the local police station?". The reply has been—"you will have to find out!" The large out door alarm bell alone—mounted in a prominent position is no doubt a psychological deterrent to the would-be intruder. The Heathkit GD-39 is excellent value for money. Installation of the basic alarm system is extremely easy to install and affords a high degree of protection. Top marks for this one Heathkit!

The GD-39 kit is manufactured by Heath Co., U.S.A. but is distributed in the United Kingdom by Heath Gloucester Ltd., with a one year warranty on all parts.

The GD-39 kit is priced at £29.90. The indoor buzzer alarm with transformer (GDA-39-10G) costs £5.80 and the large 6in alarm bell (GDA-39-20G) costs £10.90. All prices include 8% VAT and carriage (U.K. only) HEATH (GLOUCESTER) LTD., BRISTOL ROAD, GLOUCESTER GL2 6EE (Telephone GLOUCESTER 29451).

low frequency & marine receiver

PART
2

CHARLES HEATH

AUDIO AMPLIFIER

This board is approximately 4½ x 2in and both sides are shown in Fig. 9. The tags MC are fixed by ½in long 6BA bolts. Extra nuts on these bolts allow the finished amplifier to be mounted on the chassis supporting the tuning capacitor.

Insulated sleeving will be required on most leads here. It will be found helpful to use black on the negative line, red for positive circuits, and some other colour elsewhere.

Solder on insulated leads for the speaker, for S5 (battery positive) and from C20. The amplifier can be tested by connecting a 2/3-ohm speaker, 9V battery, and feeding an audio signal to C20 taking care that this is not at such a high level as to cause overloading. The pre-set resistor VR2 is initially set at about half value and is adjusted either with the aid of a meter, or by ear. If a meter is used, set VR2 so that the amplifier draws about 8-10mA with no signal. Otherwise rotate VR2 to reduce its value until audio distortion sets in, then turn it back just sufficiently to overcome this.


PANEL AND CHASSIS

It is necessary to assemble these before the circuit boards can be fitted. First drill the panel for the dial, using the template provided by the manufacturer as guidance. Fit the ball drive as in Fig. 10, but leave the transparent cover off.

In order that drive and gang can be accommodated, ¾in has to be cut off the spindle of the gang. This is best done by gripping the unwanted end in a vice, meanwhile supporting the capacitor with the hand while sawing through the spindle. Take care that metal fragments do not get into the capacitor and remove any burrs on the spindle with a file. The capacitor is then placed as in Fig. 10.

Drilling positions for the bolts securing it, can now be marked on the 7 x 4in flanged plate. Holes can also be drilled in the plate and panel, enabling them to be fitted together. Note that the plate is towards the top of the case, so that Fig. 10 is actually an underside view.

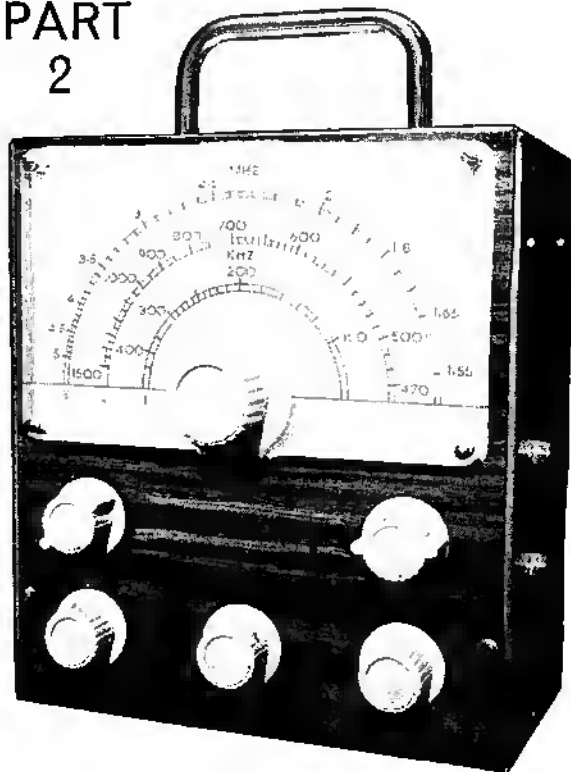These items can now be bolted tightly together. Check that the drive and capacitor rotate smoothly. Should any small adjustment be necessary, the fixing holes can be elongated with a very small round file. Bolts holding the flange to the panel should be countersunk as they will be under the tuning scale.



The five controls below the main tuning are as follows:—Top left: mode switch OFF—CW/SSB—AM. Bottom left: BFO pitch control. Bottom centre: Audio volume control. Top right: Band selector switch. Bottom right: RF trim.

Note that just sufficient is cut out of each corner flange, as in Fig. 10, to allow the side flanges of the case to fit.

Secure the IF and BFO boards in the way described. The rear bracket supporting the larger board also provides a shorter earth circuit return to the gang.

The audio amplifier is on top of the chassis plate, with T2 towards the outside.


COILS AND SWITCHING

The coils are placed as in Fig. 10. The switch will come in this position, but is above the coils on the panel. Connections from the board to the switch are as in Fig. 5.

If there is any doubt about the switch connections, check the switch with a meter or other means of showing continuity, so that all tags for each pole will be wired correctly. Alternatively, check that proper results are obtained with coils for only one band, at first. Then add the second band and check, finally wiring the third band.


The coil pins should be clean, and not heated for a lengthy time when soldering. No stress should be put on the pin until it is cool. Connections to VC1 and VC2 are as shown.

SUPERSOUND 13 HI-FI MONO AMPLIFIER

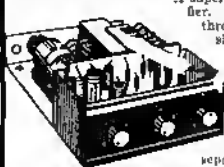

A superb solid state audio amplifier. Brand new components throughout. 5 silicon transistors plus 2 power output transistors in push-pull. Full wave rectification. Output approx. 13 watts r.m.s. into 8 ohms. Frequency response 12Hz-30KHz \pm 3dB. Fully integrated pre-amplifier stage with separate Volume, Bass boost and Treble cut controls. Suitable for 8-16 ohm speakers. Input for ceramic or crystal cartridge. Sensitivity approx. 40mV for full output. Supplied ready built and tested, with knobs, switchgear panel, input and output plugs. Overall size 8" high x 5" wide x 7 1/2" deep. AC 200/250V. Price £18.50. P. & P. 50p.

DE LUXE STEREO AMPLIFIER

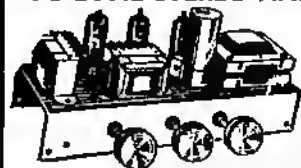

A.C. mains 200-240 v. U.S.A. 1 to 5 heavy duty fully insulated mains transformer or with full wave rectifier. 2 to 4 giving a u a c smoothing with negligible hum. Valve line up: 2 x ECL86 Triode Pentodes, 1 x E230 as rectifier. Two dual potentiometers are provided for bass and treble control, giving bass and treble boost and cut. A dual volume control is used. Balance of the left and right hand channels can be adjusted by means of a separate 'Balance' control fitted at the rear of the chassis. Input sensitivity is approximately 300mV for full peak output of 4 watts per channel (8 watts mono), into 8 ohm speakers. Full negative feedback in a carefully calculated circuit, allows high volume levels to be used with negligible distortion. Supplied complete with knobs, chassis size 11" w x 4" d. Overall height including valves 6". Ready built & tested to a high standard. £10.75. P. & P. 50p.

POWER SUPPLY UNIT 200/240V. A.C. input. Four switched fully smoothed D.C. outputs giving 5v, 40v, 175v, and 0v, and 12v. at 1 amp on load. Fitted insulated output terminals and pilot lamp indicator. Hammer finish metal case overall size 3" x 3 1/2" x 2 1/2". Suitable for Transistor Radios, Tape Recorders, Amplifiers etc. etc. Ready built and tested. Price £5.20 P. & P. 35p.

VYAIR & REXINE SPEAKERS & CABINET FABRICS ap. 54 in. wide. Our price £1.90 sq. length. P. & P. 15p per yd. (min. 1 yd.). S.A.E. for samples.

HARVERSON'S SUPER MONO AMPLIFIER

A super quality gram amplifier using a double wound fully insulated mains transformer, rectifier and ECL86 triode pentode valve as audio amplifier and power output stage. Impedance 8 ohms. Output approx. 3.5 watts. Volume and tone controls. Chassis size 10 1/2" wide x 3 1/2" deep x 6 1/2" high overall. AC mains 200/240v. Supplied absolutely Brand New completely wired and tested with good quality output transformer. Price £4.20 P. & P. 40p BARGAIN PRICE

FEW ONLY!

High grade mains transformer with grain orientated laminations. Primary 200/240 Secondary 18.5 volts at 0.5 amps and 4.5 volts at 1 amp. Size 2" h x 2 1/2" w x 2" d overall. £1.35 plus 25p P. & P.

BRAND NEW MULTI-RATIO MAINS TRANSFORMERS. Giving 13 alternatives. Primary: 0-210-400v. Secondary combinations 0-5-10-15-20-25-30-35-40-50v, half wave at 1 amp, or 10-10-10, 20-0-20, 30-0-30v, at 2 amps full wave. Size 3in. long x 3 1/4in. wide x 3in. deep. Price £2.00 P. & P. 40p.

MAKES TRANSISTORS. For transistor power supplies. Pri. 200/240v. Sec. 0-2 at 500 mA. £1.25. P. & P. 25p. Pri. 200/240v. Sec. 12-0-12 at 1 amp. £1.40. P. & P. 25p. Pri. 200/240v. Sec. 10-0-10 at 2 amp. £2.00. P. & P. 35p.

3 VOLT RELAY

100 mA electric pole normally closed. 2 for 60p + 15p P. & P.

GENERAL PURPOSE HIGH STABILITY TRANSISTOR PRE-AMPLIFIER

For P.U. Tape, Mike, Guitar, etc. and suitable for use with valve or transistor equipment. 0-18v. battery or from B.T. line 200/300v. Frequency response 13Hz-35KHz. Gain 26dB. Solid encapsulation size 1 1/2" x 1 1/2". Brand new complete with instructions. Price 1.20p. P. & P. 15p.

HANDBOOK OF TRANSISTOR EQUIVALENTS AND SUBSTITUTES
A must for servicemen and home constructors. Including many 1000's of British, U.S.A. European and Japanese transistors. ONLY 40p. Post 6p.

8 Reference Encyclopedias for Electronic Engineers and Designers, covering between them transistor characteristics, diode and transistor equivalents. Many thousands of up to date European types listed. Diode Equivalents, 80p; Transistor Equivalents, 90p; Transistor Characteristics, £1.15; POST FREE All three together, £2.80

NEW ISSUE

Thyristor, Triac, Dinc etc. encyclopedias 85p. Post Free 8 pole 3 way 2 bank low loss Vaylax type switches 1 1/2" sections. Standard spindle. 8 switches 65p + 10p P. & P.

Open 9.30-5.30 Monday to Friday, 9.30-5 Saturday Closed Wednesday

All prices and specifications correct at time of press and liable for alteration.

HARVERSONIC MAINS OPERATED SOLID STATE STEREO FM TUNER




Enjoy fabulous stereo radio at this fabulous low introductory price!

Designed and styled to match our 10 + 10 amplifier but will suit any other standard stereo amplifier. The design incorporates the very latest circuitry techniques with high gain, low noise IF stages. Automatic frequency control to "lock-on" station and prevent drift. IC stereo decoder for maximum stereo separation. I.E.D. for stereo beacon indicator. Nominal output 1 watt 100mV. Approximate size 12" wide x 8" deep by 2 1/2" high. Supplied ready built, fully tested and fully guaranteed (not available in kit form). Price £23.00 Post and Packing 60p.

STEREO-DECODER

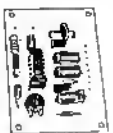£12.95 2" x 3" 1" ready built. Pre-aligned and tested. Sens. 20-500 mV for 9-16V ac. earth operation. Can be fitted to almost any FM VHF radio or tuner. Stereo beacon light can be fitted if required. Full details and instructions (inclusive of hints and tips) supplied. £5.00 plus 10p. P. & P. Stereo beacon light if required 40p extra.



SPECIAL BARGAIN OFFER!

Limited number of BSR C123 Auto Changer De Luxe with lightweight tubular arm and stereo cartridge. Brand new. ONLY £28.00 + p. & p. 60p.

LATEST!!! Sensitivity Uni-directional ultra-linear condenser microphone as used by many professionals. Very low acoustic feedback. Available in impedance or low impedance. State which required. £12.50 plus 25p P. & P.

LATEST ACO'S GPM/180 mono compatible cartridge with 1/2" stylus for LE/PL/78. Universal mounting bracket. £1.40. P. & P. 15p.

CERAMIC STEREO CARTRIDGE. Universal Mounting brackets and turnover stylus. 70mV per channel output. ONLY £1.75 + 10p P. & P.

MONO COMPATIBLE STEREO CARTRIDGE 7/10 stylus Diamond Stereo LP and Seraphine 78. ONLY £2.27 P. & P. 10p. Also available fitted with twin Diamond T/O stylus for Stereo LP, £2.70. P. & P. 15p.

LATEST T/O STEREO / COMPATIBLE CARTRIDGE for EP/PL/78/seraphine £2.80 P. & P. 15p. **LATEST T/O MONO COMPATIBLE CARTRIDGE** for playing EP/PL/78 mono or stereo records on mono equipment. Only £1.47. P. & P. 15p.

QUALITY RECORD PLAYER AMPLIFIER MK. II

A top quality record player amplifier employing heavy duty double wound mains transformer, ECL86, EL84, and rectifier. Separate Bass, Treble and Volume controls. Complete with output transformer matched for 3 ohm speaker. Size 7in. wide x 3in. deep x 6in. high. Ready built and tested. Price £5.50. P. & P. 50p.

ALSO AVAILABLE mounted on board with output transformer and speaker. Price £6.70. P. & P. 60p.

HI-FI LOUDSPEAKER SYSTEM MK II

Beautifully made, simulated teak finish enclosure with attractive slatted front. Size 16 1/2" high x 10 1/2" wide x 9" deep (approx.). Fitted with E.M.I. Ceramio Magnet 13" x 8" bass unit, H.F. tweeter unit and crossover. AVAILABLE IN NOMINAL 4 Ohm, 8 Ohm to 15 Ohm impedance (state which).

OUR PRICE £9.50 each Carr. 90p

Cabinet Available Separately £5.00, Carr. 50p
Also available in 8 ohms with EM1 13" x 8" bass speaker with parasitic tweeter £8.00, Carr. 90p.

LOUDSPEAKER BARGAINS

5in. 3 ohm £1.25. P. & P. 15p. 7 x 4in. 5 ohm £1.40. P. & P. 20p. 10 x 6in. 3 or 15 ohm £2.10. P. & P. 30p. E.M.I. 8 x 6in. 3 ohm with high flux magnet £1.70. P. & P. 20p. E.M.I. 13" x 8in. with high flux ceramic magnet with parasitic tweeter 3, 8 or 15 ohm £5.50. P. & P. 30p. E.M.I. 13 x 8in. 3, 8 or 15 ohm with built-in tweeter and crossover network £4.25. P. & P. 30p. E.M.I. tweeter. Approx. 3 1/2". Available 3 or 8 or 15 ohms. £1.25 + 20p. P. & P.


BRAND NEW. Bakers Loudspeakers at substantial discounts. 12in. 15w. H/D Speakers, 3, 8 or 15 ohms. State which. Current production by well-known British maker. Now with Hi Flux ceramic ferrous magnet assembly £7.50. Guitar models: 25w £7.50, 25w £7.50. P. & P. 45p.

"POLY PLANAR" WAFER-TYPE, WIDE RANGE ELECTRO-DYNAMIC SPEAKER

Size 11" x 14" x 1 1/2" deep. Weight 19oz. Power handling 20W r.m.s. (40W peak). Impedance 8 ohm only. Resonance 40Hz-25KHz. Can be mounted on ceilings, walls, doors, under tables, etc., and used with or without baffle. Send S.A.E. for full details. Only 68 00 each.

NOW ALSO AVAILABLE. 8", 10 watts, r.m.s. 20 watt peak 40Hz-20,000Hz. Overall depth 3". Ideal for Hi-Fi or for use in cars. £4.32 + 30p P. & P.

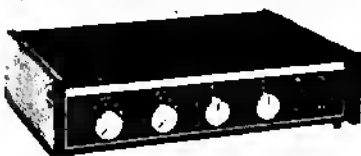HARVERSONIC SUPER SOUND 10 + 10 STEREO AMPLIFIER KIT




A really first-class Hi-Fi Stereo Amplifier Kit. Uses 14 transistors including Silicon Transistors in the first five stages on each channel resulting in even lower noise level with improved sensitivity. Integrated pre-amp with Bass, Treble and two Volume Controls. Suitable for use with Ceramic or Crystal cartridges. Very simple to modify to suit magnetic cartridge—instructions included. Output stage for any speakers from 8 to 15 ohms. Compact design, all parts supplied including drilled metalwork high quality rear drilled printed circuit board with component identification clearly marked, smart brushed anodised aluminium front panel with matching knobs, wire, solder, nuts, bolts—no extras to buy. Simple step by step instructions enable any constructor to build an amplifier to be proud of. Brief specification: Power output: 14 watts r.m.s. per channel into 8 ohms. Frequency response \pm 3dB. 12-20,000 Hz. Sensitivity: better than 80mV into 1M Ω . Full power bandwidth: \pm 3dB 12-15,000 Hz. Bass boost approx. to \pm 12dB. Treble cut approx. to -16dB. Negative feedback 18dB over main amp. Power requirements 35v, at 1.0 amp. Overall Size 12" w. x 8" d. x 2 1/2" h.

Fully detailed 7 page construction manual and parts list free with kit or send 15p plus postage. S.A.E. **AMPLIFIER KIT** £12.95 P. & P. 30p (Magnetic input components 35p extra) **POWER PACK KIT** £4.92 P. & P. 40p **CABINET** £4.92 P. & P. 40p


(Post Free if all units purchased at same time)
Full after sales service

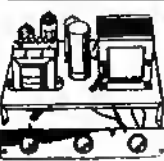Also available ready built and tested £28.00. Post Free. *Note: The above amplifier is suitable for feeding two mono sources (i.e. mike, radio, twin record decks, etc.) and will then provide mixing and fading facilities for medium powered Hi-Fi Discosque use, etc.*




3-VALVE AUDIO AMPLIFIER HA34 MK II

Designed for Hi-Fi reproduction of records. A.C. Mains operation. Ready built on plated heavy gauge metal chassis, size 7 1/2" w. x 4 1/2" x 4 1/2" h. Incorporates ECC83, EL84, E230 valves. Heavy duty, double wound main transformer and output transformer matched for 3 ohm speaker. Separate volume control and now with improved wide range tone controls giving bass and treble lift and cut. Negative feedback line. Output 4 1/2 watts. Front panel can be detached and be extended for remote mounting of controls. Complete with knobs, valves, etc. wired and tested for only £8.50. P. & P. 45p.

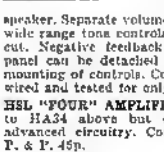

HSL 'FOUR' AMPLIFIER KIT

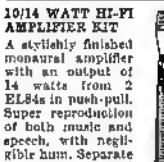Similar in appearance to HA34 above but employs entirely different and advanced circuitry. Complete set of parts, etc. £5.50 P. & P. 45p.



10WATT HI-FI AMPLIFIER KIT

A stylishly finished monaural amplifier with an output of 14 watts from 2 EL84s in push-pull. Super reproduction of both music and speech, with negligible hum. Separate inputs for mike and gram allow records and announcements to follow each other. Fully shrouded section wound output transformer to match 5-15 Ω speaker and 2 independent volume controls, and separate bass and treble controls are provided giving good lift and cut. Valve line-up 2 EL84s, ECC83, E786 and E230 rectifier. Simple instruction booklet 15p + SAE (Free with parts) All parts sold separately. ONLY £10.25 P. & P. 60p. Also available ready built and tested £14.00 P. & P. 70p.

HI-FI STEREO HEADPHONES

Adjustable headband with comfortable flexible ear-cuffs. Well and fitted with standard stereo 1/4 inch jacks. Frequency response 30-15,000Hz. Matching impedance 8-16 ohms. Easily converted for Mono. PRICE £3.50. P. & P. 25p.

12in. "RA" TWIN CONE LOUDSPEAKER. 10 watts peak handling. 3 or 8 or 15 ohm (state which) £3.00 P. & P. 35p.

PRICES INCLUDE VAT

(Please write clearly)
PLEASE NOTE: P. & P. CHARGES QUOTED APPLY TO U.K. ONLY. P. & P. ON OVERSEAS ORDERS CHARGED EXTRA.

HARVERSON SURPLUS CO. LTD.

(Dept. P.W.) 170 HIGH ST., MERTON, LONDON, S.W.19 Tel.: 01-540 3985

A few minutes from South Wimbledon Tube Station.

SEND STAMPED ADDRESSED ENVELOPE WITH ALL ENQUIRIES


BENTLEY ACOUSTIC CORPORATION LTD.

7a GLOUCESTER ROAD, LITTLEHAMPTON, SUSSEX
All prices inclusive of V.A.T. Telephone 6743

QBZ	.40	61AG	.28	61L7	.55	12Q7GT	.45	35Z3	.75	1Y7B76	.35	EP73	1.50	6Z34	.60	UHF80	.40	Transistors	AF117	.21	HYZ13	.28		
OZ4	.47	6BC8	.80	8L18	.55	12B7	.30	35Z4GT	.70	1Y902	.35	EP80	.25	6Z37	1.00	UHF89	.40	& Diodes	AF121	.33	PNY11A	.25		
1A8	.45	6BE6	.35	6L19	2.00	12B7	.40	35Z5GT	.75	8B00C	2.20	EP83	1.00	HA8C80	.60	UD191	.77	1N4744	.15	AP124	.28	FSY11A	.25	
1A60T	.60	6BH6	.80	6L20	.75	12B17	.35	.45	.50	12BP7	1.40	EP89	.34	11L29	.80	UC92	.55	2N404	.20	AF126	.19	OA8	.47	
1A70T	.65	6BJ8	.65	6N7GT	.80	12B7	.45	.30	1.00	12BP7	1.50	EP95	.45	11L33DD	.75	UC94	.70	2N4768	.55	AF126	.20	OA10	.47	
1B8GT	.85	6C47A	.55	6Q7A	.58	12B7	.65	6BR5	.65	8B00C	2.50	EP99	.45	11L34	1.00	UC94H	0.00	2N3147	.84	AF126	.20	OA10	.47	
1H8GT	.60	6BR7	.60	6Q7GT	.60	12B7	.75	6C5	.80	8P20C	6.00	EP91	.37	11L41DD	.82	UC94	.75	2N2889	.16	BA116	.20	OA10	.47	
1L4	.28	6BH8	1.50	6Q7M1	.55	1417	.65	60CD6G	1.25	8B07	1.00	EP92	.50	11L42DD	.82	UC94H	.40	2N2053	.68	BA129	.14	OA81	.10	
1N8GT	.85	6HS7	1.40	6R7M	.80	1487	.80	60E15	.75	8A182CCL	.25	EP97	.80	11L43	1.00	UC94H	.38	2N3121	2.75	BA130	.11	OA85	.09	
1R6	.45	6HW6	.80	6R7M	.78	18A05	.50	60L6GT	.55	8L148	.58	EP98	.80	11L44	1.00	UC94H	.38	2N3121	2.75	BA130	.11	OA85	.09	
1R4	.85	6HW7	.70	6B47	.44	1906	6.00	68A2	.60	EA60	.27	EP99	.30	11L45	1.00	UC94H	.38	2N3121	2.75	BA130	.11	OA85	.09	
1U4	.80	6H26	.48	6S7GT	.33	20D4	2.00	85A3	.80	EA76	1.00	EP104	.35	11L46	1.00	UC94H	.38	2N3121	2.75	BA130	.11	OA85	.09	
1V6	.75	6H4	.35	6M7	.44	20F7	.75	90M1	2.50	EA80	1.00	EP104	.35	11L47	1.00	UC94H	.38	2N3121	2.75	BA130	.11	OA85	.09	
2D21	.45	6C84	.50	6H17	.44	20L1	1.10	90C1	.75	EA89	.75	EP100	.55	11L48	1.00	UC94H	.38	2N3121	2.75	BA130	.11	OA85	.09	
20K5	.55	6C84	.40	6H17	.55	20P2	.80	90L2	2.40	ZAP42	.75	EL32	.60	11L49	1.00	UC94H	.38	2N3121	2.75	BA130	.11	OA85	.09	
2X3	.80	6C9	1.00	6H7GT	.48	20P4	1.00	105H2	.75	EA84	.75	EL34	1.00	11L50	1.00	UC94H	.38	2N3121	2.75	BA130	.11	OA85	.09	
8A4	.30	6CD6G	1.25	6R7GT	.48	20P5	1.80	105H0	.60	EB34	.35	EL36	2.50	11L51	1.00	UC94H	.38	2N3121	2.75	BA130	.11	OA85	.09	
8D4	.40	6C84	.75	8V6	.17	28A6G	.80	807	1.00	EBH1	.30	EL37	2.50	11L52	1.00	UC94H	.38	2N3121	2.75	BA130	.11	OA85	.09	
8Q4	.60	6C84	.85	8V6T	.48	28L6G	.80	8799	1.00	EBD41	.75	EL41	.80	11L53	1.00	UC94H	.38	2N3121	2.75	BA130	.11	OA85	.09	
8R4	.55	6C84	.85	8X4	.40	28Y6G	.70	8057	1.00	EBD81	.35	EL41	.80	11L54	1.00	UC94H	.38	2N3121	2.75	BA130	.11	OA85	.09	
8R8GT	.384	.60	6C84	.75	8X5GT	.48	28Z4G	.40	8062	1.00	EBP80	.39	EL43	.55	11L55	1.00	UC94H	.38	2N3121	2.75	BA130	.11	OA85	.09
3V4	.70	60C6	.75	786	.75	28Z6	.80	8067	1.00	EBF84	.48	EL44	.81	11L56	1.00	UC94H	.38	2N3121	2.75	BA130	.11	OA85	.09	
4CR8	.84	8GW4	1.00	7B7	.70	28Z6G	.70	71R3	.63	EBF69	.32	EL45	.43	11L57	1.00	UC94H	.38	2N3121	2.75	BA130	.11	OA85	.09	
6C08	.55	8H7	.75	717	.75	28D7	1.00	8062	.50	EBL21	2.00	EL46	.38	11L58	1.00	UC94H	.38	2N3121	2.75	BA130	.11	OA85	.09	
6R4V4	.85	8H7A	.75	717	.75	30A5	.85	9006	.30	EC86	.70	EL41	.80	11L59	1.00	UC94H	.38	2N3121	2.75	BA130	.11	OA85	.09	
6U4B	.45	6HW6	.75	717A	.75	30C15	.80	ACPEN	1.00	EC88	.70	EL60	1.20	11L60	1.00	UC94H	.38	2N3121	2.75	BA130	.11	OA85	.09	
6V4G	.60	6E6	1.00	7Z4	.80	30C17	.80	ACPFEN	1.00	EC91	.45	EL60	1.20	11L61	1.00	UC94H	.38	2N3121	2.75	BA130	.11	OA85	.09	
5Y8GT	.45	8F1	.75	8D7	.85	30C18	.80	DD	1.00	EC93	1.50	EL60	1.20	11L62	1.00	UC94H	.38	2N3121	2.75	BA130	.11	OA85	.09	
6Z3	.75	8P6G	.50	10C2	.85	30F6	.80	ACPEN	.60	EC96	.95	EL60	1.20	11L63	1.00	UC94H	.38	2N3121	2.75	BA130	.11	OA85	.09	
2Z4G	.45	6F19	.70	10D7	.75	30FL1	.67	AC/TH1	.81	ECU40	1.00	EL61	.85	11L64	1.00	UC94H	.38	2N3121	2.75	BA130	.11	OA85	.09	
6Z4GT	.45	6F14	.75	10F1	.75	30FL2	.67	AL60	1.00	ECG81	.34	EL62	.85	11L65	1.00	UC94H	.38	2N3121	2.75	BA130	.11	OA85	.09	
680L2	.30	8F15	.65	10P9	.65	30FL7	.80	AT14	.30	ECG82	.33	EL63	.85	11L66	1.00	UC94H	.38	2N3121	2.75	BA130	.11	OA85	.09	
6A8G	1.25	8F23	.85	10L19	.55	30FL13	.55	AZ1	.25	ECG83	.33	EL64	.85	11L67	1.00	UC94H	.38	2N3121	2.75	BA130	.11	OA85	.09	
8C7	.48	8F24	.85	10LD11	.70	30FL14	.75	AZ11	.60	ECG84	.33	EL65	.85	11L68	1.00	UC94H	.38	2N3121	2.75	BA130	.11	OA85	.09	
6A16	.27	8F28	1.00	10L12	.75	30L15	.74	AZ41	.25	ECG85	.40	EMH803	.25	11L69	1.00	UC94H	.38	2N3121	2.75	BA130	.11	OA85	.09	
6A16	.60	8F28	.87	10P14	2.00	30L17	.70	B133	2.00	ECG86	.85	EL66	.40	11L70	1.00	UC94H	.38	2N3121	2.75	BA130	.11	OA85	.09	
6A16	.85	8F32	.50	12A6	1.00	30P4MR	.70	GL33	1.60	ECG88	.85	EL67	.40	11L71	1.00	UC94H	.38	2N3121	2.75	BA130	.11	OA85	.09	
6A16	.40	606G	.60	12A06	.70	1.00	606G	.70	606G	.70	606G	.70	606G	.70	606G	.70	606G	.70	606G	.70	606G	.70	606G	.70
6A16	.80	6018A	.75	12A16	.65	30P12	.80	606G	.70	606G	.70	606G	.70	606G	.70	606G	.70	606G	.70	606G	.70	606G	.70	
6A16	.85	60K6	.85	12A25	.65	30P19	.80	DAF81	.30	606G	.70	606G	.70	606G	.70	606G	.70	606G	.70	606G	.70	606G	.70	
6A16	.70	60G7	.75	12A28	.60	30P4	.75	DAF86	.60	606G	.70	606G	.70	606G	.70	606G	.70	606G	.70	606G	.70	606G	.70	
6A16	.45	6H6GT	.25	12A06	.45	30P11	.85	DF90	.30	606G	.70	606G	.70	606G	.70	606G	.70	606G	.70	606G	.70	606G	.70	
6A16	.80	6J20T	.45	12A4V	.60	30PL13	.93	DF91	.30	606G	.70	606G	.70	606G	.70	606G	.70	606G	.70	606G	.70	606G	.70	
6A16	1.00	6J6	.30	12D46	.45	30PL14	1.10	DF96	.50	606G	.70	606G	.70	606G	.70	606G	.70	606G	.70	606G	.70	606G	.70	
6A16	.45	6J7G	.80	12D66	.60	30PL15	.90	DK40	.70	606G	.70	606G	.70	606G	.70	606G	.70	606G	.70	606G	.70	606G	.70	
6A16	.30	6K48A	.75	12H17	.50	35A3	.85	DK91	.70	606G	.70	606G	.70	606G	.70	606G	.70	606G	.70	606G	.70	606G	.70	
6A16	.45	6K7D	.30	12E1	8.00	35C6	.75	DK96	.80	606G	.70	606G	.70	606G	.70	606G	.70	606G	.70	606G	.70	606G	.70	
6A16	.85	6K8G	.45	12J7GT	.80	8D5	.75	DL96	.85	606G	.70	606G	.70	606G	.70	606G	.70	606G	.70	606G	.70	606G	.70	
6A16	.75	8L1	2.00	12K15	1.00	35L6GT	.75	DM70	.60	606G	.70	606G	.70	606G	.70	606G	.70	606G	.70	606G	.70	606G	.70	
6B8G	.30	6L6GT	.88	12K7GT	.50	30W4	.50	DM71	1.50	606G	.70	606G	.70	606G	.70	606G	.70	606G	.70	606G	.70	606G	.70	

MATCHED TRANSISTOR SETS—
LP16 (AC113, AC114, AC137, AA120) 58p
per pack. 1—OC84 & 2—OC81, 47p.
1—OC44 & 2—OC45, 47p. 1—OC82D &
2—OC82 83p. Set of 3—OC83 72p.

VALVES ALSO REQUIRED FOR CASH, LOOSE OR BOXED, BUT MUST BE NEW. OFFERS MADE BY RETURN.
All goods are unused and subject to the standard 90 day guarantee. Cash or cheque with order only. Despatch charges—Orders below £5, add 10p total to cover up to three items. (Each additional item 5p extra. Orders between £5 and £10 add 25p total. Orders over £10 are post free. Same day despatch. Any parcel insured against damage in transit for only 3p per parcel extra. Terms of business free on request. Many others in stock too numerous to mention. Please enclose S.A.E. for reply to any correspondence.

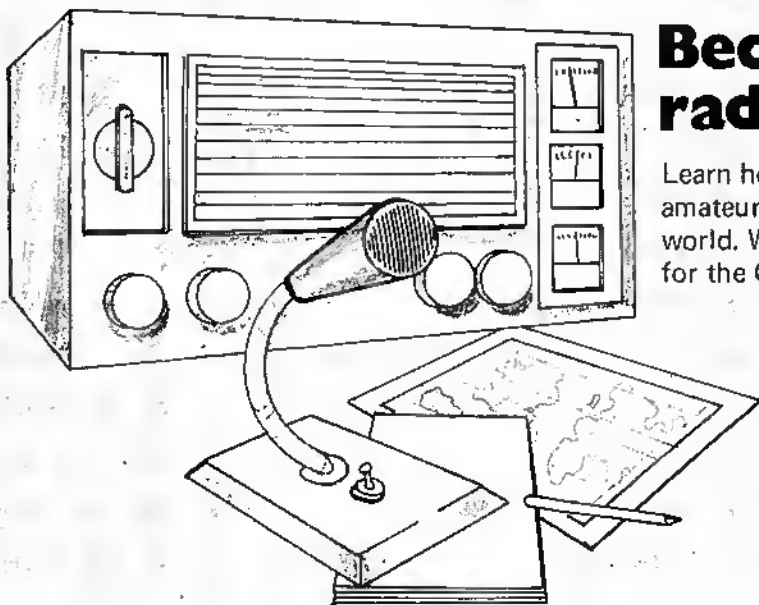


Become a radio amateur.

Learn how to become a radio-amateur in contact with the whole world. We give skilled preparation for the G.P.O. licence.


Free!

Brochure, without obligation to:
BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL, Dept., w.B.25
P.O. Box 156, Jersey, Channel Islands.

NAME _____
ADDRESS _____ Block caps please

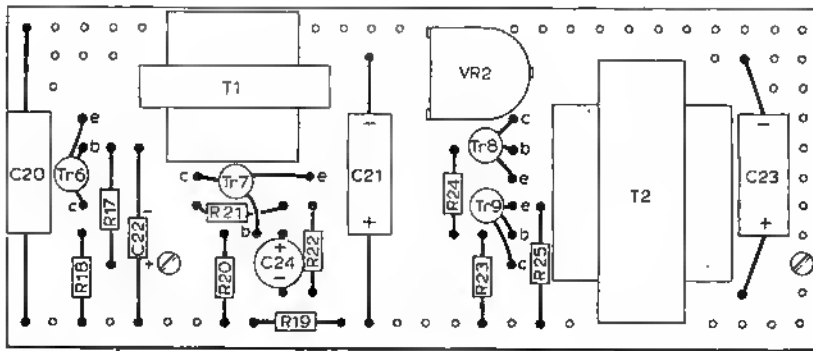

GCF026

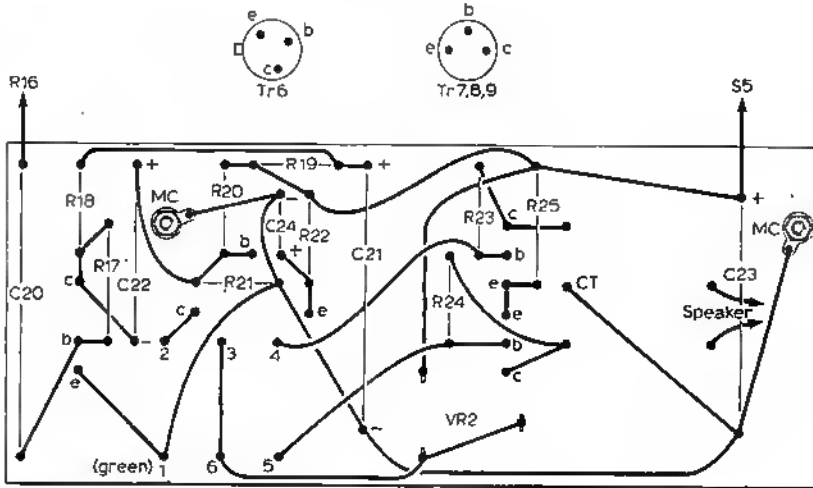

▲ Fig. 9: above, gives full constructional information on the audio circuit board.

▼ Fig. 10: below, shows the wiring required between the band-change switch and the various coils in the aerial and oscillator stages.

LOUDSPEAKER


The speaker is bolted to the side near the chassis, the aperture being covered with material or perforated metal and leads from T2 secondary passing through the chassis to the speaker. This side is bolted to the end flange of the chassis, and fixed to the panel with a self-tapping screw.

Remaining connections to the volume control and other points can now be completed, enabling the receiver to be tested before adding the remaining side, top and bottom. R16 is soldered directly on to VR1. Connections are near the panel so that the PP9 battery can rest between the boards when the bottom is added.


IF ADJUSTMENT

If a signal generator is available, use this in the normal way to check the alignment of the IFT's at 1.6MHz. Should any cores need adjusting, a wedge-shaped or metal tool must not be used, as if a core is cracked it may be impossible to remove. The TT5 tool available from the IFT maker, is recommended, or a similar core adjusting tool if this is unobtainable.

When no signal generator is available, tune in any stable transmission found, removing the aerial if necessary, so that volume is not too high, even with VR1 well advanced. Each core can now be rotated slightly, as necessary, for best volume. Very little adjustment may be required, but each core should have a definite peak giving best results. Once the cores are set they should be left without further adjustment.

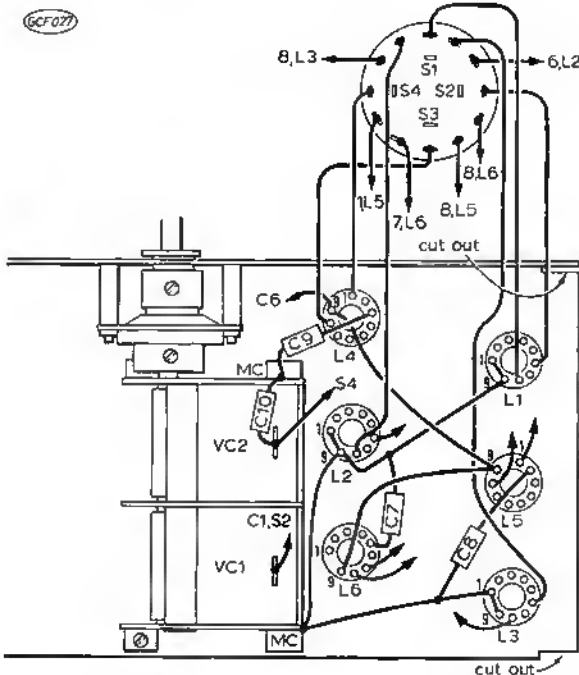

GCF071

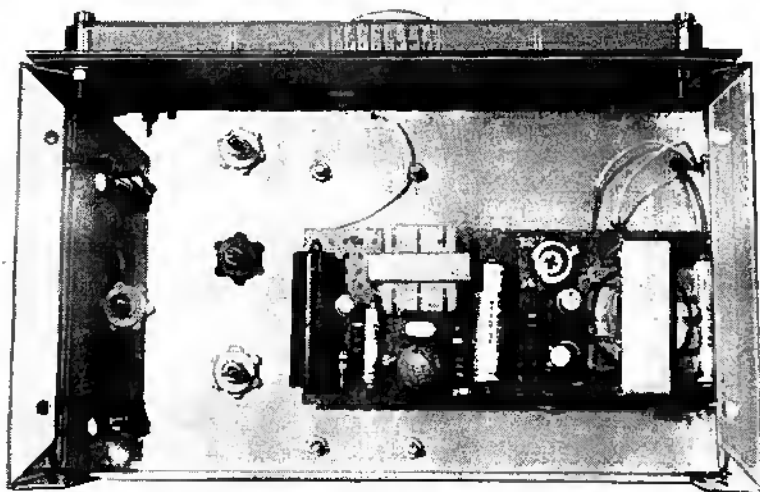

This shot was taken before the top of the cabinet was fitted. It shows the audio amplifier board of Fig. 9, with the coils L1 to L6 mounted at the left.

RF ALIGNMENT

Band 2 is probably the easiest to align. If a generator is available, set L5 core to tune 470kHz with the gang fully closed. Otherwise tune in a station of known frequency near the LF end of the band, and adjust L5 core to secure a suitable dial reading.

With TC1 about half closed, adjust L2 core for best volume, tuning in a signal a little removed from the extreme LF band end. TC1 should then be rotated to allow signals to be peaked up for best volume at any frequency throughout the band, while not being fully opened or fully closed. L2 core can be slightly re-adjusted, to avoid unnecessary modification to TC1 when tuning through the band, and both cores can then be locked with 6BA nuts.

Band 3 is dealt with in a similar manner. The IF band end can be found by tuning in a signal near 1.55MHz (1550kHz). This band includes 1.6MHz, but reception is impossible for a small range of frequencies each side of this, which is common to the IF amplifier. After setting L6 core to secure suitable coverage, the core of L3 is adjusted in a similar manner to that employed with the MW band aerial coil.

Band 1 can then be aligned noting that quite small changes to the positions of the coil cores will have considerable influence on the frequencies tuned. However, the adjustments of each range are separate from those of the other wavebands.

BFO ADJUSTMENT

Tune in a stable signal, such as a MW broadcast station, half close VC4, and with the switch in its third position, rotate the core of L7 until a loud heterodyne is heard. L7 is adjusted for the silent or zero beat position. When this is so, rotating VC4 either way should cause an audio tone which rises in pitch.

CW will be heard as a clicking sound, if strongly received, and is made audible by switching in the BFO, and rotating VC4 for the wanted audio tone. In some cases having VC3 one side of the zero beat position may give greater freedom from interference than if it is placed the opposite side.

SSB signals are most likely to be heard in the 3.6-3.8MHz region. To render these intelligible, tune in correctly, then with the BFO on, adjust the BFO frequency slowly for best readability. If the BFO is the wrong side of the SSB, it cannot resolve the signal. The lower sideband is normally transmitted by amateur stations, and the upper side band is used by marine stations in the 1.6-3.8MHz band. If the SSB is very strong, better reception is possible by detuning TC1 to reduce signal strength.

There is enough coupling from L7 due to the proximity of the boards, but this can be increased by running an insulated lead from BFO to D1. Solder the lead to the junction of C16 and C17. Run it across to D1, avoiding the battery, and thread the insulated end through the board in the hole adjacent to that used for the positive end of D1. No actual connection is made here.

CALIBRATION

A temporary pointer is provided, and scale markings can be made along its straight edge, which corresponds to the hair line on the usual pointer or cursor. Dial markings can be obtained by any of the usual means. That is, from a signal generator; from known stations; or from the harmonics of a crystal or harmonic marker.

After calibration, the dial is assembled with the transparent cover in position.

CASE

A strong case of quite good appearance is made by assembling the universal chassis members, with the panel covered in self-adhesive wood-grain style material before assembly. If this is done, a washer should be put under each fixing bush nut.

Four feet are attached with 6BA bolts, and a carrying handle is fitted to the top. Insulated sockets for aerial and earth are on one side, the earth socket being connected to the metal. The battery should be sandwiched between stout folded card to insulate it from the boards. Self-tapping screws hold the back in place. Appearance is improved and the top is more easily fitted if its end flanges are cut off.

BI-PRE-PAK

Bargains in Semi-Conductors, Components Modules and Equipment

Electronic Transistor Ignition £6.00 Complete kit p. & p. 110

Now in kit form, we offer this "up-to-the-minute" electronic ignition system. Simple to make, full instructions supplied with these outstanding features, Transistor and conventional switchability, burglar proof lock-up and automatic alarm, negative and positive compatibility.

Extension Telephones

Ideal for toys 70p each P. & P. 25p.

New X Hatch Generator Mk.2

Essential for alignment of colour guns on all colour T.V. receivers. Featuring plug in IC's and a motor sensitive sync pick-up circuit. The case is virtually unbreakable—ideal for the engineer's toolbox—only measures 3" x 6 1/2" x 3".

Ready built unit only **£9.95** Complete kit **£7.95**

(Includes p. & p. but no batteries)

LM380 AUDIO IC

We have just received a large consignment of LM380 IC's. These are specially selected to a higher grade and are marked with the number SL60745.

This fantastic little 3 watt audio IC only requires two capacitors and two potentiometers to make an amplifier with volume and tone control. The quality is good and has to be heard to be believed.

Our special price **£1.00** ea. complete with data and projects book

Over 1,000,000 Transistors in stock

We hold a very large range of fully marked, tested and guaranteed transistors, power transistors, diodes and rectifiers at very competitive prices. Please send for free catalogue.

Our very popular 4p transistors
 TYPE "A" PNP Silicon alloy, TO-3 can
 TYPE "B" PNP Silicon, plastic encapsulation
 TYPE "E" PNP Germanium AF or RF
 TYPE "F" NPN Silicon plastic encapsulation
 TYPE "G" NPN Silicon similar ZTX 300 range

8 RELAYS various types p & p 27p **£1.00 p**

UHF TV Tuner Units
 Brand new by a famous manufacturer
 Data supplied **£2.50**

B.P.P. CATALOGUE
 20 pages packed with bargains. Size 1 1/2" x 8 1/2". Send large S.A.E. with 6p stamp.

Plastic Power Transistors

IN TWO RANGES



These are 40W and 60W Silicon Plastic Power Transistors of the very latest design, available in NPN or PNP at the most shatteringly low prices of all time. We have been selling these successfully in quantity to all parts of the world and we are proud to offer them under our Tested and Guaranteed terms.

Range 1. VCE. Min 15. HFE Min 15.			
40 Watt	1-12	13-21	22-34
90 Watt	20p	18p	11p
	24p	22p	29p
Range 2. VCE. Min. 40. HFE Min 40			
40 Watt	1-12	13-21	22-34
90 Watt	35p	28p	24p
	35p	35p	34p

High Speed Magnetic Counters 4 digit (non-reset) 24V or 48V 4 x 1 x 1 in 33p & p.

INTEGRATED CIRCUITS

We stock a large range of IC's at very competitive prices (from 10p each). These are all listed in our FREE Catalogue, see coupon below.

METRICATION CHARTS now available. This fantastically detailed conversion calculator carries thousands of classified references between metric and British (and U.S.A.) measurements of length, area, volume, liquid measure, weights etc.
 Pocket Size 12p Wall Chart 11p

LOW COST DUEL IN LINE I.C. SOCKETS
 14 pin type at 15p each / Now new low profile 16 pin type at 17p each / type

BOOKS

We have a large selection of Reference and Technical Books in stock. Details are in our latest Catalogue. Send for it TODAY, using the coupon below. N.B. Books are void of V.A.T.
 Send for lists of publications

Our famous P1 Pak is still leading in value

Full of Short Lead Semiconductors & Electronic Components, approx. 170. We guarantee at least 30 really high quality factory marked Transistors PNP & NPN, and a host of Diodes & Rectifiers mounted on Printed Circuit Panels. Identification Chart supplied to give some information on the Transistors.

Pak P.1. 50p

TERMS OF BUSINESS

V.A.T. Prices shown do not include V.A.T. Please add 8% to total value of your order including postage. No V.A.T. on overseas orders.

POSTAGE Except where stated, add 15p for postage & packing in U.K. Overseas—add £1., any difference being charged or refunded.

PAYMENT Cash with order, Cheque or money order. Minimum value—50p. You can also pay by ACCESS.

IMPORTANT—Every effort is made to ensure accuracy of prices and description at time of preparing this advertisement and going to press. Prices are subject to alteration without notice.

SPECIAL BPP PAKS Tested & Guaranteed



all at **50p** each

- B79 4 IN4007 Sil. Rec. diodes. 1,000 PIV 1 amp. plastic
- B81 10 Reed Switches, 1" long 1/4" dia. Highspeed P.O. type
- H33 100 Mixed Diodes, Germ. Gold bonded, etc. Marked and Unmarked
- H34 30 Short lead Transistors, NPN Silicon Planar types
- H39 6 Integrated circuits 4 gates BMC 962, 2 flip flops BMC 945
- H41 2 BD131/BD132 Complementary Plastic Transistors
- H65 4 40381 Type NPN Sil. transistors TO-5 can comp. to H65
- H66 4 40382 Type PNP Sil. transistors TO-5 can comp. to H65

Special Bargain Paks (unmarked, untested)



all at **50p** each

- B1 50 Germanium Transistors PNP, AF and RF
- B66 150 Germanium Diodes Min. glass type
- B83 200 Transistors, manufacturers' rejects, AF, RF, Sil. and Germ.
- B84 100 Silicon Diodes DO-7 glass equiv. to OA200, OA202
- B90 100 Sil. Diodes sub. min. IN 914 and IN916 types
- H20 20 BY126/7 Type Silicon Rectifiers 1 amp. plastic. Mixed vols
- H34 15 Power Transistors, PNP, Germ. NPN Silicon TO-3 Can
- H67 10 3819N Channel FET's plastic case type.

Sterling Sound Audio Modules

A new development by BI-PRE-PAK for enthusiasts who like building at keen prices.

SEE OUR SPECIAL AD. PAGE 954

A rev. counter for your car

The "Tacho Block" enables you to turn any 0.1 mA meter into an accurate linear rev. counter. The block is encapsulated and easily fitted into any car with conventional coil ignition. Each **£1.00**

To BI-PRE-PAK 222 West Rd., Westcliff-on-Sea, Essex

Please send latest B.P.P. Catalogue. (I enclose large S.A.E. envelope with 6p stamp.)

Please send

Enclosed £..... Inc. V.A.T. cheque/money order (Write on more paper if necessary)

NAME


ADDRESS

BI-PRE-PAK LTD

Dept. D. 222-224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX.
 TELEPHONE: SOUTHTEND (0702) 46344.

Co Reg. No. 623713

BIG Discounts

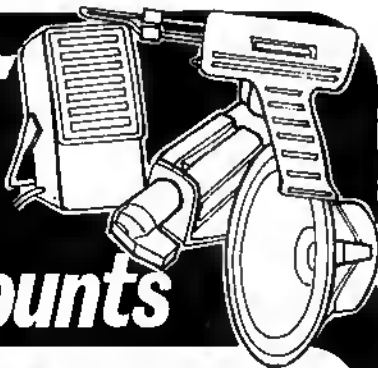

ALL PRICES INCLUDE V.A.T.

SPEAKER BARGAINS		GOODMANS 5 1/2" 8 ohm	
EMI 13" x 8" 3, 8 or 15 ohm	£	Dualcone	£
Plain	2-05	ELAC 8" 8 ohm Dualcone	2-25
With Co-Axial Tweeter		ELAC 8 ohm Dualcone 10 watt	3-50
8 ohms only	3-20	FANE 7" x 4" 3 or 8 ohm	1-00
Twin Tweeter	3-70	ADAstra 10" 8 or 15 ohm,	
Type 350		10 watt	3-45
8 or 15 ohm,		BAKER GROUP 25 12" 8 or	
20 watt	7-50	15 ohm, 25 watt	7-95
5 1/2" 8 ohm, 10 watt	2-40	P. & P.	30
8" 8 ohm, 10 watt	3-75	5" 8 ohm, C/Mag.	85
12" 3 ohm, 20 watt	6-70	2 1/2" 8 ohm or 64 ohm	80
8" x 5" C/Mag. 5 watt	1-25	P. & P.	15
8" x 5" Dualcone			
8 ohm, 10 watt	2-45		
TWEETER & CROSSOVER			
EMI 3 1/2" 3 or 8 ohm C/Mag.	1-20	Dome Tweeter 8 ohm, 30 watt	5-40
Cone Tweeter 8 or 15 ohm,		Crossovers CN23 (3 ohm),	
10 watt	2-40	CN26 (8 ohm), CN215 (16	
Cone Tweeter 8 ohm, 3 watt	1-45	ohm)	1-20
Horn Tweeter 8 ohm, 20 watt	5-40	P. & P.	10
KIT FORM CABINETS TEAK VENEER			
12 x 12 x 6 with 8" 8" x 5" or		18 x 11 x 9 with 13" x 8" cutout	
6 1/2" and 3 1/2" cut-out.	2-45	for EMI 350	4-25
17 x 10 x 9 with 8" or 13" x 5"		P. & P. ea.	45
cut-out	3-50		
MICROPHONES			
CM70 Planet stick metal,		TW209	5-75
switch crystal	1-55	CONDENSER MIKE 600 ohm,	
DM160 Dynamic omni-dir.		uni-dir.	9-35
ball metal	3-85	Cassette Stick Mike with R.	
UD130 50K/800 ohm, uni-dir		Control on/off switch	
ball metal	5-95	(2-5 & 3-5mm J/Pls)	1-45
		P. & P.	20
SOLDERING IRONS			
ANTEX CN240 15 watt	1-80	X25 25 watt (low	
SK F Kit (15 watt iron		leakage)	1-80
2 spare Bils etc.)	3-30	P. & P.	10
CARTRIDGES & STYLII			
ACOS GP81/25C or 35C ster.		SONOTONE	
comp.	1-00	9TAHC or 9" AHC/G Diam.	1-80
GP83/1 or 95/1 ster.		3509 Ster. ceram. Diam.	1-80
cryst.	1-35	GOLDRING G850	2-85
GP94/1 or 96/1 ster.		G900	3-85
ceram.	1-75	G800E	8-90
GP101 cryst. comp.	0-80	P. & P.	10
GP104 ster. ceram.	1-65	D. Diamond Stylis for above..	1-25
BSR X5M or X5H cryst. comp.	1-70	G800/G850	1-95
5X6M or SX6H cryst.		G800E	3-95
comp.	1-90	P. & P.	05
SCSM ster. ceram.	2-80		
CALCULATORS, SINCLAIR			
Cambridge	18-60	Scientific	20-90
BATTERY ELIMINATORS			
240v Input 6, 7-5 or 9 300mA	2-05	6, 7-5 or 8 d.c. output at	
12v d.c. Input (specify output)		300mA	2-30
		P. & P.	15
TAPES			
5" 50p	85p	1-00p	
5 1/2" 85p	80p	1-40p	
7" 35p	1-10p	1-80p	
LOW NOISE CASSETTES			
1-5	6-10	11-20	
C60	35p	33p	30p
C90	45p	43p	40p
C120	55p	53p	50p
8TB ACCESSORIES			
Tape Editing Kit Ref. 23	1-35		
Recording Tape			
Solicer	Ref. 20	1-15	
Cassette Tape, editing Ref. 24	1-50		
Cassette Salvage Kit Ref. 29	45		
12" Cassette Case Ref. 34	1-50		
Stylus Balance Ref. 32A	1-20		
Spirit Lever Ref. 45	50		
Hi-Fi Stereo Test Cassette	2-10		
Groove-Kleen Record Cleaner	1-90		
P. & P.	10		
WHARFEDALE SPEAKER BARGAINS			
Linton 2 Kit (pr)	19-00	1-00	
Glendale 3 Kit (pr)	23-50	1-50	
Dovedale 3 Kit (pr)	32-00	1-50	
Denton 2 Speaker (pr)	30-00	2-00	
Linton 2 Speaker (pr)	39-50	2-00	
Dovedale 3 Speaker			
(each)	42-00	2-00	
Glendale 3 Speaker (pr)	37-00	3-00	
Kingsdale 3 Speaker			
(each)	59-95	3-00	

Send 25p for COMPLETE CATALOGUE, refundable upon first order. ALL OUR MERCHANDISE IS FULLY GUARANTEED. Subject to manufacturer increase and availability.

Riversdale Electronics

Mail Order Department RW2

P.O. Box 470, Manchester M60 4BU.

PE SCORPIO Mk 2 ignition system kit new from ELECTRO SPARES

* 6 OR 12 VOLT
* + VE AND - VE GROUND

Here's the new, improved version of the original PE Scorpio Electronic Ignition System—with a big plus over all the other kits—the PE Scorpio Kit is designed for both positive and negative ground automotive electrical systems. Not just +ve ground. Nor just -ve ground. But both! So if you change cars, you can be almost certain that you can change over your PE Scorpio Mk. 2 as well. Containing all the components you need, this Electro Spares PE Scorpio Mk. 2 Kit is simply built, using our easy-to-follow Instructions. Each component is a branded unit by a reputable manufacturer and carries the manufacturer's guarantee. Ready drilled for fast assembly. Quickly fitted to any car.

When your PE Scorpio Mk. 2 is installed, you instantly benefit from all these PE Scorpio Mk. 2 advantages.

- ★ Easier starting from cold ★ Firing even with wet or oiled-up plugs ★ Smoother running at high speed
- ★ Fuel saving ★ More power from your engine
- ★ Longer spark plug life ★ No more contact-breaker burn

Electro Spares prices:

De luxe Kit only £11.50 inc. VAT and p & p.
Ready Made Unit £14.75 inc. VAT and p & p.
State 6V or 12V system.

Send SAE now for details and free list.

FM VARICAP STEREO TUNER

As featured in the May 1973 issue of 'Practical Electronics', Superb Hi-Fi tuner Kit now available from Electro Spares. Including cabinet and all components - pre-set Mullard modules for R.F. and I.F. circuits. Motorola I.C. Phase Lock Loop Decoder for perfect stereo reception. No alignment needed. Guaranteed first time results - or send it back, and we'll return it in perfect order (for a nominal handling charge). Electro Spares price only £28.50 inc. VAT and p & p.

'GEMINI' STEREO AMPLIFIER

A superb unit with a guaranteed output of 30 watts RMS per channel into 8 ohms. Full power THD is a mere 0.02%, and frequency response is -3 dB from 20 Hz to 100 kHz into 8 or 15 ohms. Electro Spares have already sold 100s and 100s of these Kits. Get yours now! Depending on your choice of certain components, the price can vary from £60 to £60 inc. VAT and p & p.

★ All components as specified by original authors, and sold separately if you wish.

★ Full constructional data book with specification graphs, fault finding guides, etc. 55p plus 4p postage.

★ Price List only. Please send S.A.E. (preferably 9 x 4 minium) for full details.


ELECTRO SPARES




The Component Centre of the North
288 ECCLESALL RD., SHEFFIELD S11 8PE (C)
Tel: Sheffield (0742) 668888

PW TECHNIGROSS PUZZLE No. 8

presented last month

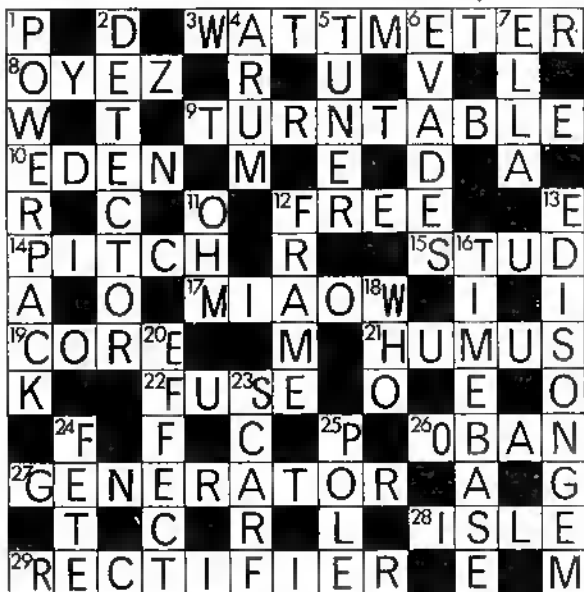

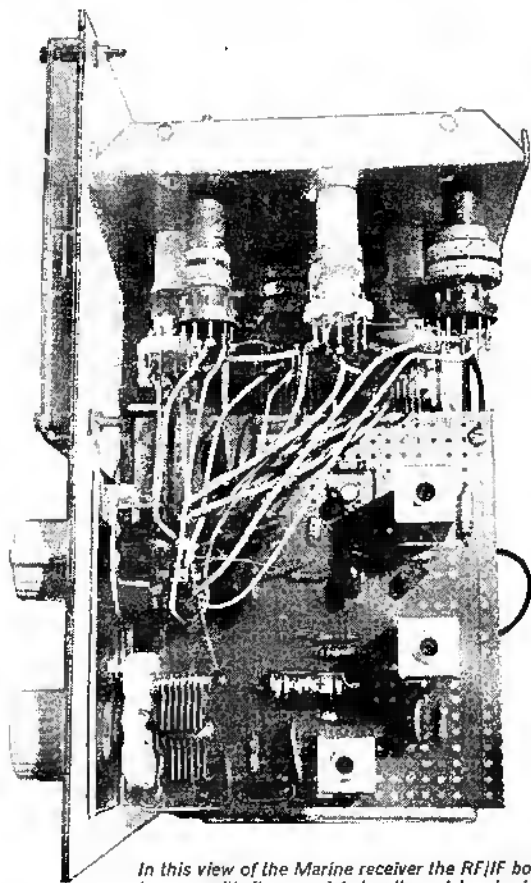L.F. AND MARINE RECEIVER—continued from page 942



In this view of the Marine receiver the RF/IF board is seen with its associated coils and bandswitch.

P. W. KEMPTON—continued from page 926

check everything twice and you may save yourself hours of stripping down and trouble-shooting later. Once you tear the unit apart to look for a fault, the finished item will never look quite as neat as when it was first completed.

INSTALLATION

Mounting the unit in the car can be achieved in either of two ways. If a slot is available as part of the car's dashboard layout, the unit may be inserted from the front and held by a bracket constructed to meet the earthing bolt at the rear. The bracket is finally tightened to draw the machine in securely. Alternatively, the unit may be mounted beneath the dash panel or parcel tray using two angle-brackets. If this method is to be used, the bolts for the brackets should be fitted prior to assembly of the main unit, since it is impossible to fit them with the deck and amplifier panel in position.

Finally, make sure that the cases of the four output transistors cannot come into contact with any metalwork and so short-circuit. If necessary a strip of insulating material (srpb) may be fixed to the rear of the machine by the earthing bolt.

AERIAL SYSTEM

For best possible results, some attention is necessary to the aerial-earth system. What is used here can also depend on the more important frequencies and purpose in view.

Quite a number of the stronger transmissions can be received with a short aerial, and no earth connection, however, for weaker and more distant signals, an earth will increase signal strength considerably. For maximum range on the 160m band, and indeed most other bands, a quite long, outdoor aerial will greatly improve reception. Such an aerial is likely to cause overloading with powerful BBC and other broadcasts, and results are then better if either a short wire is used, or a small pre-set capacitor is placed in the aerial lead, or the aerial lead is twisted round an insulated wire which in turn runs to the receiver. PW


The speakers should be fitted in the car, bearing in mind the required stereo effect. If they can be built into the door panels, good results are obtained but a lot of work is needed. There is also the hazard of a short-circuit developing in the wiring because of the opening and closing of the doors. Probably the favourite place is the rear window ledge. A satisfactory stereo effect is usually obtained and the wiring up presents little difficulty. PW

ALL OUR PRICES INCLUDE V.A.T.

BSR HI-FI AUTOCHANGER

STEREO AND MONO

Plays 12", 10" or 7" records
Auto or Manual. A high
quality unit backed by BSR
reliability with 12 months
guarantee. AC 200/250V.
Size 13 1/2" x 11 1/2".
Above motor board 3 1/2".
Below motor board 2 1/2".
With STEREO/MONO CARTRIDGE



£7-95 Post 45p.

PORTABLE PLAYER CABINET

Modern design. Size 16" x 15" x 7" rextone covered. Large front grille. Hinged Lid. Chrome fittings. Motor board cut for BSR deck. Few only in red and black, cut for Garrard deck.

£4-50 Post 45p.

SOLID MAHOGANY PLINTH

With P.V.C. Cover. Cut out for most H.E.R. or Garrard decks. Size 13 1/2" x 14 1/2" x 7 1/2".

£6-50 Post 45p.

BSR JUNIOR SINGLE PLAYER

Heavy duty 4-speed motor with separate pick-up arm fitted LP/78 turnover mono compatible cartridge.

£4-95 Post 25p.




R.C.S. DISCO DECK SINGLE RECORD PLAYER

Fitted with auto stop, stereo/mono cartridge. Baseplate. Size 11 1/2" x 8 1/2". Turntable. Size 7in diameter. A.C. mains. 220/250V motor has a separate winding 14 volt to power a small amplifier. 3 speeds plays all size records.

£5-50 Post 25p.

COMPACT PORTABLE STEREO HI-FI

Two full size loudspeakers 13 1/2" x 10" x 3 1/2". Player unit clips to loudspeakers making it extremely compact. Overall size only 13 1/2" x 10" x 3 1/2". 3 watts per channel, plays all records 33 rpm 45 rpm. Separate volume & tone controls 240V A.C. mains.

Attractive Teak finish Weight 13lbs.

Bargain Price **£25** 85p carriage

SPECIAL OFFER! SMITH'S CLOCKWORK 15 AMP TIME SWITCH 0-60 MINUTES

Single pole two-way Surface mounting with timing screws. Will replace existing wall switch to give light for return home, garage, automatic anti-burglar lights etc. Variable knob Turn on or off at full or intermediate settings. Fully insulated. Makers last list price 24-50. Brand new and fully guaranteed. OUR PRICE **£1-95** Post 25p.



CASSETTE RECORDER MOTOR ONLY. 6 Volt.

Will replace many types £1-25. Ideal for models.

BLANK ALUMINIUM CHASSIS. 18 s.w.c. 2 1/2in sides 8 x 4in 65p; 8 x 4in 53p; 10 x 7in 65p; 12 x 8in 85p; 14 x 8in 95p; 16 x 6in 90p; 12 x 3in 50p; 16 x 10in 41p.

ALUMINIUM BOXES 3 x 3 x 3in 60p; 4 x 4 x 4in 70p; 4 x 4 x 4in 80p; 6 x 4 x 4in 81p; 12 x 4 x 4in 81p.

ALUMINIUM PANELS 18 s.w.c. 6 x 4in 12p; 8 x 6in 19p; 14 x 8in 29p; 10 x 7in 24p; 12 x 8in 25p; 12 x 8in 84p; 16 x 6in 24p; 14 x 8in 40p; 12 x 12in 47p; 18 x 10in 60p.

S.R.B.P. PAXOLIN PANEL 10 x 8in 50p.

1 1/2inch DIAMETER WAVECHANGE SWITCHES 45p. EA. 2 p. 2-way, or 2 p. 6-way, or 3 p. 4-way., 1 p. 1.2-way, or 4 p. 2-way, or 4 p. 3-way.

TOGGLE SWITCHES. 4p. 20p; dp. 25p; dp. dl. 30p.

R.C.S. STABILISED POWER PACK KITS

All parts and instructions with Zener Diode. Printed Circuit Bridge Rectifiers and Double Wound Mains Transformer. Input 200/240V a.c. Output voltages available 8 or 9 or 12 or 15 or 18 or 20V d.c. at 100mA or less. PLEASE STATE VOLTAGE REQUIRED. £2-20 Post 20p Details S.A.E. Size 3 1/2" x 4 1/2" x 1 1/2".

R.C.S. GENERAL PURPOSE TRANSISTOR PRE-AMPLIFIER BRITISH MADE

Ideal for Mike, Tape P.U., Guitar, etc. Can be used with Battery 8-12v. or H.T. Hinc 200-300V. D.C. operation. Size 1 1/2" x 1 1/2" x 1 1/2". Response 25 c.p.s. to 25 Kc/s. 28 db gain. For use with valve or transistor equipment. £1-25 10p Full instructions supplied. Details S.A.E.

NEW TUBULAR ELECTROLYTICS		CAR TYPES	
4/350V 14p	250/22V 14p	16-18-16/275V 45p	
4/350V 14p	600/25V 20p	50-50/300V 50p	
4/350V 13p	1000/25V 25p	32-32/250V 20p	
15/350V 22p	1000/50V 47p	32-32/450V 50p	
25/500V 50p	8-16/450V 25p	100-50-60/350V 85p	
25/25V 10p	8-16/450V 25p	100-50-60/350V 85p	
60/50V 10p	16-16/450V 40p	32-32-32/350 45p	
100/25V 10p	32-32/350V 40p	600MFD/350V 95p	

LOW VOLTAGE ELECTROLYTICS

1. 2. 4. 5. 8. 16. 25. 30. 50. 100. 200mF 15V 10p.
100mF 12V 10p; 25V 25p; 50V 30p.
100mF 12V 10p; 25V 35p; 50V 47p; 100V 70p.
2000mF 6V 25p; 25V 42p; 50V 57p; 4700/63V 85p.
3500mF 6V 85p; 3000mF 25V 47p; 35V 85p.
5000mF 6V 25p; 12V 42p; 25V 70p; 35V 85p; 50V 95p.
500V-0.01 to 0.05 4p; 0-1 10p; 0-25 12p; 0-47 25p.
CERAMIC 1pF to 0.01mF. 4p. Silver Mica 2 to 5000pF. 4p.
PAPER 550V-0.1 7p; 0.5 18p; 1mF or 2mF 150V 15p.
MICRO SWITCH single pole changeover 20p
MICRO SWITCH sub min 25p
TWIN GANG. "0-0" 200pF+170pF. £1-10.
Slow motion drive 255pF+385pF with 25pF-25pF. 50p;
500pF standard twin gang 75p. 120 PF twin gang 60p.
SHORT WAVE SINGLE. 10pF, 30p; 250pF, 65p; 60pF, 55p.

ELAC 8 x 5in. HI-FI SPEAKER. TYPE 508R. THIS FAMOUS AND WIDELY USED UNIT NOW AVAILABLE AT BARGAIN PRICE

10 WATT. 8 OHM. CERAMIC MAGNET. **£2-95**

NEON PANEL INDICATORS. 250V AC/DC Amber, 30p

RESISTORS. 1 w. 1/4 w. 1/2 w., 20p., 1p; 2 w. 5p. 10 1/2 to 10K. HIGH STABILITY. 1/4 w. 2c. 10 ohms to 8 meg., 10c. Dillo 6c., Preferred values 10 ohms to 10 meg., 4p.

WIRE-WOUND RESISTORS. 5 watt. 10 watt. 15 watt. 10 ohms to 100K. 10p each; 2w 5 ohms to 8 1/2 ohms 10p.

TAPE OSCILLATOR COIL. Valve type. 25p.

FERRITE ROD B. 1/4" x 20p; 1/2" x 20p; 3/4" x 20p.

MAINS TRANSFORMERS ALL POST 25p each

250-0-250V 80MA. 6.3-2A £2-50.
250-0-250 80 mA. 6.3 v. 3.5 a. 6.3 v. 1 a. or 5 v. 2 a. £4-00
250-0-250 80 mA. 6.3 v. 3.5 a. 6.3 v. 1 a. or 5 v. 2 a. £5-00
300-0-300 v. 120 mA. 6.3 v. 4 a. C.T.; 8.3 v. 2 a. £4-00
MINIATURE 200 v. 20 mA. 6.3 v. 1 a. 2 1/2" x 2 1/2" 75p
MIDGET 220 v. 45 mA. 6.3 v. 2 a. 2 1/2" x 2 1/2" 80p
HEATER TRANS. 6.3 v. 3 amp. £1-20. 1 amp. 85p
GENERAL PURPOSE LOW VOLTAGE. Tapped outputs at 2 amp. 3.4, 5, 8, 10, 15, 18, 24 and 30 v. £4-00
1 amp. 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 £4-00
2 amp., 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 £8-00
3 amp., 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 £7-50
5 amp., 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 £9-75
6, 8, 10, 12 or 15 v. 5 amp. £1-60. 6-0-5 v. 500 mA 90p v. 1 amp 95p. 5 v. 300 mA 75p. 12 v. 500 mA 85p. 12 v. 750 mA 95p. 48v. 2 amp. tapped 12 v. or 36 v. £2-50. 20V 3 amp. £2. 40V 3 a. £2-50. 22V 0.22U 4 a. 80p.
AUTO TRANSFORMERS. 115v to 230v or 230v to 115v. 150w. £4-00; 500w. £7-50; 750w. £15-00; 1000w. £18-00.
CHARGER TRANSFORMERS. Input 200/250v. Output for 6 or 12v. 1 amp. £1-50. 2 amp. £1-30. 4 amp. £3
BATTERY CHARGERS. Ready built with leads and clips 1 amp. £2. 4 amp. £4; 6 amp. £4-50.
FULL WAVE BRIDGE CHARGER RECTIFIERS: 8 or 12v. outputs. 1 amp. 40p; 2 amp. 55p; 4 amp. 85p.

MAINS ISOLATING TRANSFORMER

Primary 0-110-230v. Secondary 0-230v. 3 amps. 720 watts. Insulated terminals. Varnish impregnated. Fully enclosed in steel case with fixing feet. **£12** Carr. Famous make. (Value £19) OUR PRICE **85p** Suitable for outside use.

SET OF 3 MOTORS FOR COLLARO STUDIO 115 volt TAPE DECK £1-50 Post 50p.

VOLUME CONTROLS 80 Ohm Coax 5p rd.

5 K. ohms to 2 Meg. LOG or LIN. L/S 20p. D.P. 35p. EGRESS L/S 55p. D.P. 75p. EDGE 25. S.P. Transistor 25p.

Whewound controls 1 1/2in. diam. 3 watt. 10 ohms to 100K

British made with long spindles. dia. 80p as.

DUAL CONCENTRIC POT 500K LOG + 500K LIN D.P. switch. Inner spindle 3 1/2in; outer spindle 2 1/2in. 75p.

E.M.I. 13 1/2" x 8 in. SPEAKER SALE!

With twin tweeters. And crossover. 10 watt. State 3 or 8 or 15 ohm. As illustrated. Post 25p


With hard tweeter cone and ceramic magnet. 10 watt. Gains res. 45-60 cps. £2-75

Fix 10,000 gauss. State 3 or 8 or 15 ohm. Post 25p

Bookshelf Cabinet 16-18 x 8in. Teak Veneer Post 45p

E.M.I. 6 1/2in. HI-FI WOOFER

8 ohm. 10 watt. Large ceramic magnet Special Rubber cone surround. Frequency response 30-12,000 c.p.s. Ideal P.A. Columns. Hi-Fi Enclosure Systems, etc. Suitable cabinet 12" x 8" x 6 1/2" 40p. Suitable Tweeter £2-00.



ELAC CONE TWEETER

The moving coil diaphragm gives a good radiation pattern to the higher frequencies and a smooth extension of total response from 1,000 cps to 18,000 cps. Size 8 1/2" x 3 1/2" dia. Deep. Rating 10 watt. 3 ohm. Crossover £1.25

£1-90 Post 20p

GOODMANS 8 in. WOOFER

8 ohm 12 watt. Deep cone. Heavy ceramic magnet. Bass response 30-8,000 cps. Frequency response 30-8,000 cps. Ideal bass unit for £3-75 Hi-Fi systems



LOUDSPEAKER P.M. & OHMS. 7 x 4in. £1-25; 8 1/2in. £1-50; 8 x 6in. £1-75; 10 x 6in. £1-50; 11 1/2in. £2-00.

SPECIAL OFFER LOUDSPEAKERS! All Brand New. 3 ohm. 2 1/2in; 2 1/2in; 3 1/2in; 5in. 8 ohm. 2 1/2in; 2 1/2in; 5in x 3 1/2in; 5in. 15 ohm. 3 1/2in; 6 x 4in; 6in x 3in; 7 x 4in; 8 x 5in. 25 ohm. 2 1/2in; 3in; 6 x 3in; 5in. 35 ohm. 3in; 6in. 80 ohm. 2 1/2in; 2 1/2in. 120 ohm. 3in.

£1 EACH.

LOUDSPEAKER VOLUME CONTROL 15 ohm 10 watt with 1in line threaded bush for wood panel; mounting 65p.

RICHARD ALLAN TWIN CORE LOUDSPEAKERS. 5in. diameter 4W £2-50, 10in. diameter 5W £2-95; Post 25p. 12in. diameter, 5W, £3-50; 3 or 8 or 15 ohm models. SPEAKER COVERING MATERIALS. Samples Large S.A.E. Horn Tweeters 2-16Kc/s. 10W 8 ohm or 10 ohm £2-20. 2in. Line Horn Tweeters 2-18 Kc/s. 15W. 8 ohm £4-00. TWO-WAY 3,000 & 8,000 c.p.s. CROSS OVERS 3, 8 or 15 ohm £1-25. 3-WAY CROSSOVER 800 cps and 3000 cps (25 watt) £1-95.

DECCA DOME TWEETER 18,000 cps. 25 watts. 8 ohm. Price £3-30.

ELECTRO MAGNETIC PENDULUM MECHANISM

1.5v d.c. operation over 250 hrs. continuous on 5P2 battery. 1 1/2" x 1 1/2" x 1 1/2" size and speed. Ideal display for electro-mechanism or for metronome; stereo etc. 85p. Post 20p

R.C.S. VALVE AMPLIFIER

2 Stage Triode Pentode valve. 3 watts 3 ohm output. Volume on/off and tone controls AC mains. Complete and tested. With Loudspeaker. **£4-50** Post 25p.

WEYRAD COILS

PS07AC-60p. EA2W 85p. Twin Gang £1-10.
PS08-40p. OPTI 65p. Printed Circuit 85p.
PS07CC-40p. LPDT4. 65p.

COAXIAL Plug 10p. PANEL SOCKETS 10p. LINE 16p. OUTLET BOXES, SURFACE MOUNTING 25p.

BALANCED TWIN RIBBON FEEDER 300 ohms, 7p rd.

JACK SOCKET 8in. open-circuit 14p. closed circuit 25p.

Chrome Lead Socket 45p. Phone Plug 6p. Phone Socket 5p.

JACK PLUGS 8in. Chrome 20p; 8-8mm Chrome 12p. DIN SOCKETS Chassis 3-pin 10p; 5-pin 10p. DIN SOCKETS Lead 3-pin 18p; 6-pin 15p. DIN PLUGS 3-pin 18p; 5-pin 25p. VALVE HOLDERS 5p; CERAMIC 10p; CANS 5p.

FM/VHF AERIAL FEEDER CABLE

300 ohm suitable for stereo 7p per yard.

BRITISH FM/VHF TUNING HEART

88 to 108 Mc/s British made. 2 Transistors ready aligned—requires 10.7 Mc/s I.F. Complete with tuning gauge. Connections supplied but some technical experience required. SUITABLE I.F. STRIP 24-95. Post 20p.

Our Price **£3-95**

ALL PRICES INCLUDE VAT MINIMUM POST AND PACKING 20p. CALLERS WELCOME

RADIO COMPONENT

Illustrated Brochure, Radio Books & Component Lists 10p. Written guarantee.

ALL OUR PRICES INCLUDE V.A.T.

E.M.I. WOOFER AND TWEETER KIT

THE PAIR. Post 45p. (Available separately. Woofer £4.25; Tweeter £1.50.)

£5-75

Comprising a fine example of a Woofer 10 1/2" x 8 1/2" in. with a massive Ceramic Magnet, 44oz, Gauge 13,000 lines, Aluminium Cone centre to improve mids and top response. Also the E.M.I. Tweeter 8 1/2" in. square has a special lightweight paper cone and magnet flux 18,000 lines. Crossover condenser and full instructions supplied.

Impedance Standard 8 ohms
12 watts
Maximum power 25 to 18,000 cps
Useful Response 45 cps
Bass Resonance 45 cps

SUITABLE ENCLOSURE 20 x 13 x 8 in. MODERN DESIGN, TEAK WOOD FINISH.



£10-50
Post 75p

ELAC 8in. or 10 x 6in. HI-FI SPEAKER



Dual cone plasticized roll surround. Large ceramic magnet. 30-18,000 cps. Bass resonance 65 cps. 8 ohm impedance. 8in. 10 watts

£3-75

TEAK VENEER HI-FI SPEAKER CABINETS

Fluted Wood Fronts

MODEL "A", 20 x 13 x 8 in. For 12in. dia. **£10-50** Post 75p

MODEL "B", 18 x 10 x 8 in. For 12 x 8in. or **£6-60** Post 45p

MODEL "C", 18 x 8 x 8 in. For 8 x 6in. **£4-95** Post 35p

LOUDSPEAKER CABINET WADDING 18in. wide, 20p ft.



BAKER RECOMMENDED 12 inch Enclosure 4 cubic ft. HI-FI CABINET £18-60. Carr. £2 each. Size 20 x 20 x 12in. Teak Finished Fluted Front.

TEAKWOOD LOUDSPEAKER FRONT GRILLS Modernize your cabinets with a Grooved look. Sizes—18 1/2" x 10 1/2"—75p. 10 1/2" x 7 1/2"—45p.

BARGAIN 4 CHANNEL TRANSISTOR MONO MIXER. Add musical highlights and sound effects to recordings. Will mix Microphones, records, tape and tuner with separate controls into single output. 8 volt battery operated. **£4-50**



STEREO VERSION OF ABOVE £5-85.

BARGAIN FM TUNER. 68-102 Mc/s Six Transistor. 9 volt. Printed circuit. Calibrated slide dial tuning. Walnut Cabinet. £14



BARGAIN FM TUNER. £10

BARGAIN 3 WATT AMPLIFIER. 4 Transistor Push-Pull Ready built with volume, treble and bass controls. 18 volt battery operated. £3-50

WAFER HEATING ELEMENTS THIN

OFFERING 100% USES for every type of heating and drying applications in the home, garage, greenhouse, factory (available in manufacturing quantities). Approx. size 10 1/2" x 8 1/2" x 1/4" in. Operating voltage 200/250V. a.c. 200 watts approx. Printed circuit element enclosed in asbestos filled with connecting wires. Completely flexible providing safe Black heat. British-made for use in photocopyers and print drying equipment. Ideal for home handymen and experimenters. Suitable for Heating Pads, Food Warmers, Convactor Heaters, etc. Must be clamped between two sheets of metal or asbestos, etc., to make efficient clothes dryer, towel rails—ideal for airing cupboards. Ideal for anti-frost devices for the garage—preventing frozen radiators or acting as oil pump heater. Use in the greenhouse for seed raising and plant protection. Invaluable aid for bird houses, incubators, etc., can be used in series for lower heat. Or in parallel for higher heat applications.

ONLY 40p EACH (FOUR FOR £1-50)
ALL POST PAID—Discounts for quantity.

BAKER MAJOR 12" £8-50



30-14,500 c/s. 12in. double cone, woofer and tweeter cone together with a BAKER ceramic magnet assembly having a flux density of 14,000 gauss and a total flux of 145,000 Maxwells. Bass resonance 40 c/s Rated 20 watts. NOTE: 3 or 8 or 16 ohms must be stated.

Module kit, 30-17,000 c/s with tweeter, crossover, baffle and instructions. **£10-95**

Please state 3 or 8 or 16 ohms.

"BIG SOUND" BAKER SPEAKERS

Robustly constructed to stand up to long periods of electronic power. As used by leading groups and discos

Useful response 30-13,000 cps. Bass Resonance 55 cps.

GROUP "25" **£7-75**
12in. 25 watt
3, 8 or 16 ohms.

GROUP "35" **£8-50**
12in. 35 watt
3, 8 or 16 ohms.

GROUP "50" **£17-80**
15in. 50 watt
8 or 16 ohms.

GROUP 50/12in. **£12-95**
50 watt 8 or 16 ohms

Group + PA Cabinets in stock Sand for leaflet.



MAJOR 100 WATT ALL PURPOSE TRANSISTOR AMPLIFIER

All purpose transistorised. Ideal for Groups, Disco and P.A. 4 inputs speech and music. 4 way mixing. Output 8/15 ohm a.c. Mains. Separate treble and bass controls. Guaranteed. Details SAE.



£49 Carr. £1-00

NEW MODEL--MAJOR 50 WATT £39-85. Carr. £1. 4 inputs 2-way mixing. 2 outputs separate treble and bass controls. Ideal disco or p.a. amp.

DE LUXE 100 WATT VALVE AMPLIFIER CHASSIS

4 input 10 wide range controls. For Mikes, Discos, Organs, Guitars, etc. 4, 8 & 16 ohm loudspeakers matching 200-00.

THE "INSTANT" BULK TAPE ERASER & HEAD DEMAGNETISER.

Suitable for cassettes, and all sizes of tape reels. A.C. mains 200/250V. Label S.A.E. **£3-75** Post 30p



QUALITY LOUDSPEAKER ENCLOSURE

Teak veneered 1 1/2" thick wood cabinet. Size 18 1/2" x 18 1/2" x 8 1/2" in. Weight 2 1/2 lbs. This cabinet features a wide mesh Silver Grill covering a separate compartment for mounting Tweeters or Mid-Range Horn. The fully sealed bass compartment is cut out for 8 inch Woofer. £7-60 Carr. 85p. Rosewood Version 28-50 Carr. 85p. Baffle could be cut to take larger speaker.



SPECIAL OFFER

100 Ohm 20 watt Rheostat 2 1/2 in diam. Ceramic Former. Brown Terminals 1/2 in. diam. spindle. 95p. Post 25p. AC mains relay 3 pole change over 75p.



REVERSIBLE 4 POLE MOTOR
1,400 r.p.m. Reversible 42 Watt. **£2-25**
spindle 1 1/2" x 7/32", size 3 1/2" x 3". Post 35p
As illustrated, 240v. AC mains.

E.M.I. TAPE MOTOR

4 pole, 840 v. 135 mA. Size 3 1/2" x 2 1/2" x 2 1/2" in. **£1-85**
1290 rpm. Spindle 3/4 in diameter. Post 30p.

BAKER HI-FI SPEAKERS HIGH QUALITY — BRITISH MADE

REGENT 12in. 15 watts

An inexpensive unit for the beginner in high fidelity and for general purposes. May be used to improve any Radio, Amplifier, Hi-Fi or Television receiver.

Bass Resonance 45cps
Flux Density 12,000gauss
Useful response 45-13,000cps
3 or 8 or 16 ohm models.



£7-75

DE-LUXE Mk II 12in 15 watts

Especially designed to provide full range reproduction at an economical cost. Suitable for use with any high fidelity system. Built-in concentric tweeter cone.

Bass Resonance 80cps
Flux Density 14,000gauss
Useful response 25-18,000cps
8 or 16 ohms models.



£9-75

SUPERB 12in. 20 watts

A high quality loudspeaker. Its remarkable low cone resonance ensures clear reproduction of the deepest bass. Fitted with a special copper drive and concentric tweeter cone resulting in full range reproduction with remarkable efficiency in the upper register.

Bass Resonance 25cps
Flux Density 16,500gauss
Useful response 20-17,000cps
8 or 16 ohms models.




£13-80

AUDITORIUM 12in. 25 watts

A full range reproducer for high power. Electric Guitars, public address, multi-speaker systems, electric organs. Ideal for Hi-Fi and Disco-theques.

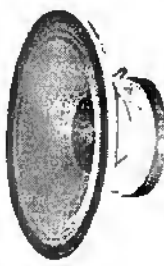Bass Resonance 35cps
Flux Density 15,000gauss
Useful response 25-18,000cps
8 or 16 ohms models.



£12-95

AUDITORIUM 15in. 35 watts

A high wattage loudspeaker of exceptional quality with a level response to above 6,000 cps. Ideal for Public Address, Discoteques, Electronic Instruments and the home Hi-Fi.

Bass Resonance 35cps
Flux Density 15,000gauss
Useful response 20-14,000cps
8 or 16 ohms models.



£17-80

Hi-Fi Enclosure Manual containing plans, formulae, crossover data and cubic tables. 60p. Post 3p.

CUSTOMERS FREE CAR PARK

SPECIALISTS

(Exports Remit cash and extra postage.)

OPEN 9-6. WEDNESDAY 9-1. SATURDAY 9-5. Closed for lunch 1-15-7-30

337 WHITEHORSE ROAD . CROYDON

Buses 50, 68, 159. Rail Selhurst

Telephone 01-684-1665



"I MADE IT MYSELF"

Imagine the thrill you'll feel! Imagine how impressed people will be when they're hearing a programme on a modern radio you made yourself.

Now! Learn the secrets of radio and electronics by building your own modern transistor radio!

Practical lessons teach you sooner than you would dream possible.

What a wonderful way to learn—and pave the way to a new, better-paid career! No dreary ploughing through page after page of dull facts and figures. With this fascinating Technatron Course, you learn by building!

You build a modern Transistor Radio . . . a Burglar Alarm. You learn Radio and Electronics by doing actual projects you enjoy—making things with your own hands that you'll be proud to own! No wonder it's so fast and easy to learn this way. Because learning becomes a hobby! And what a profitable hobby. Because opportunities in the field of Radio and Electronics are growing faster than they can find people to fill the jobs!

No soldering—yet you learn faster than you ever dreamed possible.

Yes! Faster than you can imagine, you pick up the technical know-how you need. Specially prepared step-by-step lessons show you how to read circuits—assemble components—build things—experiment. You enjoy every minute of it!

You get everything you need. Tools. Components. Even a versatile Multimeter that we teach you how to use. All included in the course. **AT NO EXTRA CHARGE!** And this is a course anyone can afford. (You can even pay for it by easy instalments).

So fast, so easy, this personalised course will teach you even if you don't know a thing today!

No matter how little you know now, no matter what your background or education, we'll teach you. Step by step, in simple easy-to-understand language, you pick up the secrets of radio and electronics.

You become a man who makes things, not just another of the millions, who don't understand. And you could pave the way to a great new career, to add to the thrill and pride you receive when you look at what you have achieved. Within weeks you could hold in your hand your own transistor radio. And after the course you can go on to acquire high-powered technical qualifications, because our famous courses go right up to City & Guilds levels.

Send now for FREE 76 page book—see how easy it is—read what others say!

Find out more now! This is the gateway to a thrilling new career, or a wonderful hobby you'll enjoy for years. Send the coupon now. There's no obligation.

POST TODAY FOR FREE BOOK

To: ALDERMASTON COLLEGE
DEPT. CPW 02
READING RG7 4PF

CPW02

Yes, I'd like to know more about your course. Please send me free details—plus your bi 76-page book that tells about all your courses.


NAME

ADDRESS



HOME OF BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

NEW ALL SILICON!

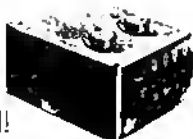

PRACTICAL WIRELESS

ELECTRONIC IGNITION SYSTEM

This Capacitor-Discharge Electronic Ignition System was described in *Practical Wireless*, and has proved extremely popular.

The kit is supplied with a ready-drilled roller-tinned printed-circuit board and fully machined die-cast case with AMP Electrical Spade Connector Block together with a custom wound transformer, first grade components and full constructional details.

The original circuit employed Germanium Power Transistors for the negative earth version. **WE OFFER SILICON P.N.P. POWER DEVICES AT NO EXTRA COST!** All components are available separately. Case size 4 1/2" x 3 3/4" x 2". Complete assembly and construction manual free with kit, available separately 25p.

SUITABLE FOR 12V SYSTEMS WITH NEG. OR POS. EARTH.


PRICE: £9.50 U.K. ORDERS PLEASE ADD VAT

Quantity Discounts:

| | | |
|--------------------|------------------|------------------|
| Trade and Overseas | 1-5 Nett | 6-9 less 10% |
| Enquiries Invited | 10-49 less 15% | 50-99 less 20% |
| Mail Order Only. | 100-999 less 25% | 1000 up less 30% |

PLEASE STATE POS. OR NEG. EARTH WHEN ORDERING

DABAR ELECTRONIC PRODUCTS

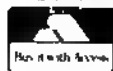

98 LICHFIELD STREET
WALSALL, Staffs WS1 1UZ



PC ETCHING KIT
Contains 1lb ferric chloride, 100 sq. ins copper clad board, DALO etch resist pen, abrasive cleaner, dish for etching and instructions. £3.30.

RESISTORS & CAPACITORS
500 ass'd. resistors £1.40, 2500 £5, 200 poly. ceramic, mica capacitors £1, 15 different trimmers, air-spaced and compression up to 1250pF £1.

VEROBOARD
100 sq ins assorted sizes and pitches, about 8 bits £1.10.

SPECIAL OFFER OF 741C DIL I.C.'s
10 for £2.60
25 for £5.75
100 for £21.00

FERRIC CHLORIDE
Anhydrous technical quality in 1lb double sealed packs. 1lb 80p, 3lb £1.65, 10lb £4.45, 100lb £35.

PO AMPLIFIER UNIT
Contained in steel case 5 1/2 x 5 x 3 1/2" are 2 x 6ET18 transistors on heat sinks, 3 dot cores, 2 30V zeners, 4 audio transformers, 1 1/2 R's & C's With circuit £1

SEMICONDUCTORS
All new full spec devices: AC127 AC128 AC176 AC177 AC187 AC188 all 20p; DC107, 8, 9 10p; 2N3055 38p, 723C 75p; 741C 35p; 1N914 4p; 1N4001 5p; 1N4004 8p; 1N4007 12p; 200V 1 1/2A 10p; 400mW zenors 10p; 400V 5A 10p £1

All new full spec devices: AC127 AC128 AC176 AC177 AC187 AC188 all 20p; DC107, 8, 9 10p; 2N3055 38p, 723C 75p; 741C 35p; 1N914 4p; 1N4001 5p; 1N4004 8p; 1N4007 12p; 200V 1 1/2A 10p; 400mW zenors 10p; 400V 5A 10p £1

GREENWELD ELECTRONICS (PW2)

Head office, mail-order dept. Wholesale/Retail shop: 51 SHIRLEY PARK RD. SOUTHAMPTON, SO1 4FX. Tel (0703) 772501. Also callers welcome at 21 Deplford Broadway SE8, Tel. 01-692 2098 & 38 Lower Addiscombe Rd., Croydon, Tel. 01-588 2950.

71b BARGAIN PARCELS
Hundreds of new components—pots, resistors, capacitors, switches, + PC boards with transistors and diodes. Also loads of odds and ends. Contents always changing as new goods come in. Amazing value at £2.30.

COMPUTER PANELS
Always thousands in stock, all sizes shapes and prices from 5p. 31bs assorted £1.40, 71bs £2.65, 561bs £35. 12 high quality panels with power transistors, IC's, trimpos etc £2.50. Pack containing about 500 components inc at least 50 transistors 95p. Pack of boards with 50 14 pin DIL DTL IC's £1.

TRANSFORMERS
All mains primary, 5.0-5V → 100mA 85p; 9-0V → 100mA 90p; 12-0-12V → 100mA 95p; 16-0-16V with 1V → 1 1/2A £2; 24-0-24V → 800mA £1.85; 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 20, 24, 30V → 1A £2.45; The following are ex-equip: 22j-0-22jV → 1A £2; 12V → 15A £3.50; 15V → 5A £2; 55V → 5A £4.

MULTIMETERS
LT101: 0-10-50-1000V AC & DC, 0-1-100mA DC, 0-150KΩ Only £3.50.
IT12: 20,000 Ω V, 0.5-25-50-250-500-2500V DC, 0-10-50-100-500-1000V AC, 0-50μA-2-5-250mA, 0-60k-6MΩ, → 20 to 4-22dB. Protected meter movement £6.20

POWER SUPPLIES
G101. Contains mains transformer, 2A thermal cut-out and bridge rect. Will give 1.7-10-5V output with 2 extra capacitors (provided) £1.25.
G102. These are stabilized power supplies giving 7.1V → 225mA. Voltage can be altered by changing zener. Not working, but only minor faults £1.

MAPLIN

ELECTRONIC SUPPLIES

Get your 1975 CATALOGUE!



Includes dozens of useful & interesting circuits you can build; data; hundreds of pictures, transistor equivalents list and hundreds of new lines. Packed with information. Only 35p.

SUPERSONIC SAME-DAY-SERVICE—MEANS QUALITY COMPONENTS—FAST!

● RESISTORS

CARBON FILM
 1/4W 1Ω to 1M: 5%, 1M2 to 10M: 10% E12
 1/2W 1Ω to 10Ω: 5%, 1M2 to 10M: 10%
 E12 11Ω to 910k: 5% E12 & E24 1p each

METAL OXIDE WIREWOUND
 1/2W 10Ω to 1M: 2% E12 & E24 4p each
 3W 0.22Ω, 0.27Ω, 0.33Ω, 0.47Ω: 10% 17p each
 1Ω to 270Ω: 5% E12 13p each
 Other ranges stocked. See our catalogue for details.
 E12: 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and decades.
 E24: 11, 13, 16, 20, 24, 30, 36, 43, 51, 62, 75, 91 and decades.

● POTENTIOMETERS

Rotary miniature carbon track 1" spindle.
 Values available: 5k, 10k, 25k, 50k, 100k, 200k, 500k, 1M, 2M.
 Log. Single-gang 16p
 Lin. Single-gang (+ 1K) 16p
 Log. or Lin. Single-gang with switch 38p
 Log. or Lin. Dual-gang without switch 49p
 Slider 50mm track. Metal case: overall length 88-15mm (knob extra 7p)
 Log. or Lin. Single-gang 1k, 5k, 10k, 25k, 50k, 100k 36p each
 Log. or Lin. Dual-gang 1k, 5k, 10k, 25k, 50k, 100k 45p each
 Presets: 0.1W. Vertical or Horizontal.
 100Ω, 220Ω, 470Ω, 1k, 2.2k, 4.7k, 10k, 22k, 47k, 100k, 220k, 470k, 1M 7p each

● CAPACITORS

Sub-miniature Axial lead electrolytic
 Mid V Price Mid V Price
 1 53 5p 68 6.3 5p
 1.5 63 5p 68 15 6p
 2 63 5p 68 25 14p
 3 63 5p 100 4 5p Mid V Price
 4 63 5p 100 10 5p 470 5.3 6p
 6 63 5p 100 25 6p 470 10 14p
 8 63 5p 100 40 6p 470 25 16p
 10 25 5p 100 63 16p 470 40 25p
 10 25 5p 150 6.3 6p 680 5.3 14p
 15 16 5p 150 16 6p 680 15 28p
 18 40 5p 150 25 6p 680 20 25p
 15 63 5p 150 40 14p 680 40 28p
 22 10 5p 150 63 16p 1000 4 14p
 22 25 5p 225 4 6p 1000 10 16p
 22 63 5p 220 10 6p 1000 16 28p
 33 6.3 5p 220 15 6p 1000 25 28p
 33 16 5p 220 25 14p 1500 0.5 15p
 39 40 5p 33 40 6p 1500 10 25p
 47 4 5p 220 63 25p 1500 16 28p
 47 10 5p 330 4 6p 2200 0.3 25p
 47 25 5p 330 10 6p 2200 10 25p
 47 0 5p 330 16 14p 3000 0.3 25p
 47 83 5p 330 63 22p 3700 0.3 25p

● MAINS CONNECTORS

P360 3-pin 1.5A Chassis Plug with Line Socket 30p
 SA2100 3-pin 5A Chassis Plug 25p
 SA 1852 Line Socket (nr SA2100) 25p
 P497 9-pin 5A Chassis Socket with Line Plug 55p

● TRANSISTORS & DIODES

| | | | |
|--------------|--------|---------------|-------|
| AC127 | 15p | BY126 | 13p |
| AC128 | 15p | BY127 | 13p |
| AC170 | 17p | BY164 | 49p |
| AD161/102 MP | 35p | BY278H series | |
| BA100 | 8p | MPF102 | 13p |
| BA145 | 25p | OA81 | 35p |
| BC107 | 10p | OA200 | 7p |
| BA109 | 10p | OC71 | 20p |
| BC109 | 15p | SC140D | 88p |
| BC106C | 15p | T1843 | 28p |
| BC142 | 28p | WG05 | 30p |
| BC143 | 28p | W040 | 32p |
| BC147 | 10p | IN914 | 4p |
| BC148 | 10p | IN4001 | 6p |
| BC149 | 12p | IN4002 | 6p |
| BC168C | 12p | IN4003 | 7p |
| BC169C | 12p | IN4004 | 7p |
| BC178 | 17p | IN4005 | 8p |
| BC182L | 15p | IN4004 | 8p |
| BC183L | 15p | IN4007 | 9p |
| BC184L | 12p | IN1148 | 4p |
| BC212L | 14p | 2N1302 | 20p |
| BC213L | 14p | 2N1303 | 20p |
| BC214L | 13p | 2N1304 | 30p |
| BCF71 | 22p | 2N1711 | 24p |
| BD131 | 45p | 2N2910 | 25p |
| BD132 | 44p | 2N2640 | 45p |
| BD131/ED132 | 2N2905 | 88p | |
| MP | £1.20 | 2N2936 Or. | |
| BD135 | 30p | Ye. or Gn 10p | |
| BD139 | 49p | 2N3053 | 18p |
| BD140 | 49p | 2N3055 | 49p |
| BF250 | 25p | 2N3819 | 25p |
| BF259 | 25p | 2N5458 | 51p |
| BFX29 | 30p | 7460 | 16p |
| BFX30 | 38p | 7443 | 8p |
| BFX64 | 30p | 7447 | £1.10 |
| BFX85 | 36p | 7473 | 54p |
| BFX87 | 30p | 7474 | 44p |
| BFY88 | 25p | 7480 | 95p |
| BFY89 | 25p | 7480 | 95p |
| BFY61 | 25p | 74121 | 38p |
| BFY52 | 28p | | |

L.E.D. RED 2mcd 1" only 15p
 Panel mfg. chip (Other colours and 7-acc. displays in our catalogue) 15p

● INTEGRATED CIRCUITS

| | |
|-----------------------------|-------|
| CA3045 (14-pin DIL) | 89p |
| LM0042CH (TO99) | £4.25 |
| MC1310P (14-pin DIL) | £2.50 |
| MC1490 (UA796) (14-pin DIL) | 95p |
| MFC4000H | 38p |
| NE5204G | 65p |
| NE535V (8-pin DIL) | 85p |
| SC1495 (14-pin DIL) | £2.70 |
| SG3402 (14-pin DIL) | £1.69 |
| µA741C (8-pin DIL) | 35p |
| µA741C (14-pin DIL) | 45p |
| µA747C (14-pin DIL) | £1.05 |
| µA7490 (8-pin DIL) | 89p |
| ZN414 (TO18) | £1.20 |

VOLTAGE REGULATORS

| | |
|---|-------|
| µA7805 5V 1.5A (TO9) | £1.75 |
| µA7815 15V 1.5A (TO9) | £2.30 |
| MVR 5V, 12V, 15V, 500mA (TO9) | £1.60 |
| µA78M05 5V 500mA (Plastic power) | £1.30 |
| µA78M15 15V 500mA (Plastic power) | £1.30 |
| µA78L05 5V 100mA (TO92) | 80p |
| µA78L15 15V 100mA (TO92) | 90p |
| µA723C Variable 2 to 37V (TO99 or 14-pin DIL) | 75p |

Our catalogue contains application circuits and data for all the above I.C.'s and many more.

● DISCOUNTS

Details in our catalogue. Start collecting MES Discount Vouchers NOW!

● SWITCHES

Rotary adjustable step 1 pole, 2 to 12 way; 2 pole, 2 to 6 way; 3 pole, 2 to 4 way; 4 pole, 2 or 3 way 30p each
 Slide Sub-min DPDT 9p
 Slide Min. DPDT 18p
 Push to make Non-locking SPST 14p
 Push-on, Push-off Locking DPDT 250V 4A 48p
 Rocker White DPST 250V 10A 40p
 Rotary Mains DPST 250V 2A 20p
 Toggle with ON/OFF plate DPST 250V 1.5A 25p

RED OUTPUT SLIDE SWITCH
 Marks the end of the old-fashioned thumb-wheel switch. With 7-segment type read-out. Full details in our catalogue. £1.38

● PLUGS & SOCKETS

| DIN | PLUG | CHASSIS SOCKET |
|----------------|------|----------------|
| 2-pin | 8p | 6p |
| 3-pin | 9p | 7p |
| 3-pin A (180°) | 10p | 7p |
| 3-pin B (240°) | 10p | 7p |
| 5-pin B | 10p | 9p |

JACK PLUGS

| | |
|---------------------------------|-----|
| 1in. Std. Mono Plastic Barrel | 13p |
| 1in. Std. Mono Metal Barrel | 24p |
| 1in. Std. Stereo Plastic Barrel | 18p |
| 1in. Std. Stereo Metal Barrel | 30p |
| 2.5mm Plastic Barrel | 8p |
| 2.5mm Metal Barrel | 15p |
| 3.5mm Plastic Barrel | 8p |
| 3.5mm Metal Barrel | 15p |

JACK CHASSIS SOCKETS
 2.5mm Open-type metal 8p
 3.5mm Open-type metal 8p
 1" Std. Mono Open-type metal 10p
 1" Std. Mono Moulded with 2 Leah contacts 14p
 1" Std. Stereo Open-type metal 14p
 1" Std. Stereo Moulded with 3 break contacts 18p

PHONO

| | |
|-----------------------|-----|
| Plastic-topped Plug | 5p |
| Screened Plug | 12p |
| Chassis Socket Single | 4p |
| Chassis Socket Twin | 6p |

● TRANSFORMERS

| | |
|--|-------|
| LT700 min. output. Pri. 1kV; Sec. 0-220mW | 50p |
| Sub-min. mains 0-0.6V 100mA | 95p |
| 12-0-12V 50mA (Size both approx. 30 x 27 x 26mm) | |
| Min. mains | |
| 0-6V 500mA, 0-6V 500mA | £1.20 |
| 0-12V 250mA, 0-12V 250mA | £1.30 |
| 0-20V 150mA, 0-20V 150mA | £1.35 |
| 0-24V 125mA, 0-24V 125mA | £1.35 |
| Mains MTSAT: Sec: 12-15-20-24-30V 2A | £3.60 |
| Mains MT20AT: Sec: 0-15-20V 1A, 0-15-20V 1A | £3.65 |

● ORGAN CONSTRUCTION

A Full Scale Electronic Organ that you can Build to Your Own Specification.

FULL CONSTRUCTIONAL DETAILS IN OUR LEAFLETS

Leaflet MES 51: Price 15p. Describes a fully polyphonic basic organ which can later be used as the basis of a large sophisticated instrument.
 Leaflet MES 52: Price 5p. Contains the description of the MES 55 series organs and shows you how to add a second keyboard with lots more steps.



● THE AMAZING DMO2

A ready-built, tested and guaranteed digital master oscillator. Accurately generates the top 13 notes for your organ system and reduces the complete tuning of your organ to ONE SIMPLE adjustment. New design gives selectable C to C output ranges of (approx.): 4k to 8k (highest) or 2k to 4k or 1k to 2k, etc. right down to 16Hz to 22Hz! And this new compatible design is even smaller—only 3.5in x 3.7in including gold-plated edge connexion.
 DMO2T includes built in variable depth and rate frequency shift (tremulant).
 DMO2 £12.25 DMO2T £14.25
 SAJ 110: 7-stage frequency divider in 14-pin DIL package. Sine or square wave input. Square wave output may be converted to saw-tooth. £1.80 each or 6 for £9.94 or 12 for £18.10.
 Keyboards high quality, fully sprung.
 Flat-front 48-note F to E £16.95
 Sliding-front 48-note C to C £15.95
 Sliding-front 61-note C to C £20.44
 Swell pedal with 10k top, pot £5.93
 *Spring Line Unit (Short) £3.05
 *Spring Line Unit (Long) £7.69
 *Reverberation Driver Module £5.84

* R.A.F. please for full details: leaflet MES 24. Gold-lead phosphor-bronze wire 30p per yd. Palladium earth bar 15p per centimetre length. Contact Blocks 2-make (TO2) 25p
 Stop Tags rocker type not engraved (white, red, grey or black) with DPDT switch 45p

SPECIAL OFFER

5W Audio Amp 1C TBA 810S with Data and Circuits Price £1.00.

"ELECTRONICS TODAY INTERNATIONAL" 4600 SYNTHESISER

We stock all parts for this brilliantly designed synthesiser. This includes all the P.C.B.s, metal-work and drilled and printed front panel giving a truly professional finish. Authoritative opinions agree the E.T.I. International Synthesiser is technically superior to most of today's models. Complete constructional details in our booklet, available shortly. R.A.F. please for price list and specification.

We also stock all parts for the P.E. Synthesiser and Minisonic.



P.O. BOX 3, RAYLEIGH, ESSEX. Tel.: Southend-on-Sea (0702)44101

VAT Please add 8% to the final total. Post and packing FREE in U.K. (15p handling charge on orders under £1).

First-class post pre-paid envelope supplied free with every order.

THE NEW NELSON-JONES FM TUNER

PUSH-BUTTON VARICAP DIODE TUNING (6 Position)

(WW' JUNE '73)

Exclusive Designer Approved Kits



What are the important features to look for in an FM tuner kit? Naturally it must have an attractive appearance when built, but it must also embody the latest and best in circuit design such as:-

- MOSFET** front end for excellent cross modulation performance and low noise.
- 3 GANG** tuning for high selectivity.
- VARICAP** tuning diodes in back to back configuration for low distortion.
- CERAMIC** filters for defined IF response.
- INTEGRATED** circuit IF amplifiers for reliability and excellent limiting/AM rejection.

- PHASE LOCKED** Stereo decoder with Stereo mute, see below
- LED** fine tuning indicators.
- PUSH BUTTON** tuning (with AFC disable) over the FM band (88-104)
- IC STABILISED** and 5/C protected power supply.
- CABINET** double veneered anti-rattle warp.

The Nelson-Jones Tuner has all of these features and many more, and more importantly the design is fully proven not just with a few prototypes but with many thousands of working tuners spread across the world.

Typ. Spec'n: 20 dB Quieting 0-75uV, Image rejection -70dB.I.F. Rejection -85 dB.


Basic tuner module prices start as low as £12-31, with complete kits starting at £25-95 (mono) + P.P. 65p, and of course all components are available separately.

Our low cost alignment service is available to customers without access to a signal generator. Please send large SAE for our latest price lists which details all of the many options and special low prices for complete kits. All our other products remain available.

PORTUS AND HAYWOOD PHASE LOCKED DECODER (W.W. Sept. '70). Still the lowest distortion P.L. decoder available, THD typically 0-05% (at Nelson-Jones Tuner O/P level) Supplied complete with Red LED.

PRICE £7-02 when bought with a complete N-J tuner kit or £8-29 if bought separately (P.P. 21p). **PLEASE NOTE.** Existing tuners are readily convertible and kits/parts are available for this purpose.

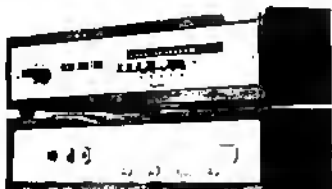TEXAN AMPLIFIER. We have designed the tuner case and metwork to match the Texan amplifier (see photograph). Complete designer approved Texan kits are available at £30-78 plus P.P. 65p including Teak Sleeve.



NEW LOW COST STEREO TUNER

Available as basic or complete kits

Basic stereo tuner £15 post free.
Basic mono tuner £12 post free,
6 position push button units with
integral pots £2-92.

No alignment required. Mullard LP1186 front end module used with Ceramic IF and IC amplifier. Push button tuning (6 position) with Interstation Mute, restricted range AFC, single LED tuning indicator, phase locked IC decoder, and complete metwork and veneered cabinet. Complete with IC regulated PSU and full assembly instructions. (Mechanically identical to N-J Tuner.)

TYP. SPECIFICATION
2uV for 30dB S/N
Image rejection 40dB
IF rejection 65dB

VAT at 8% is included in all prices

PRICE Complete stereo kit £28-42
Complete mono kit £24-19
P. & P. 65p

INTEGREX LIMITED, P.O. Box 45, Derby, DE1 1TW Phone Swadlincote (028387) 5432 Telex 377106

Fully guaranteed Individually packed VALVES

| | | | | | | | |
|------------|-------|-------|-------|--------|-------|----------|-------|
| A1065 | £1-85 | ECL80 | 55p | 6Z34 | 70c | PY80 | 40p |
| A88 | 55p | ECL82 | 35p | 6Z37 | £1-00 | PY41 | 40p |
| ATP4 | 50p | ECL83 | 70p | KT66 | £2-60 | PY92 | 40p |
| B12H | £3-00 | ECL86 | 50p | KT88 | £2-00 | PY83 | 40p |
| CY31 | 50p | EP28 | 85p | MH4 | 75p | PY38 | 45p |
| DAF56 | 55p | EP37A | | ML4 | 85p | PY900 | £1-00 |
| DF96 | 55p | EP40 | £1-50 | OA2 | 45p | PY800 | 45p |
| DK98 | 70p | EP40 | 75p | OC2 | 45p | PY301 | 50p |
| DL92 | 40p | EP41 | 85p | PAB30 | 40p | QQV03-10 | |
| DL96 | 60p | EP80 | 30p | PC97 | 50p | AD 161 | £1-40 |
| DY88/87 | | EP83 | £1-25 | PC900 | 50p | AD 182 | £2-00 |
| | 40p | EP85 | 35p | PC884 | 40p | AD 211 | 40p |
| DY802 | 45p | EP86 | 35p | PC885 | 40p | AD 212 | 40p |
| EBAC701 | | EP89 | 30p | PC888 | 50p | AD 214 | 40p |
| | £1-20 | EP81 | 45p | PC829 | 50p | AD 118 | 40p |
| E180CC 70p | | EP82 | 30p | PC189 | 60p | AD 117 | 40p |
| E182CC | | EP84 | 40p | PCF80 | 40p | AD 116 | 40p |
| | £1-25 | EP188 | 35p | PCF82 | 40p | AD 115 | 40p |
| EA50 | 40p | EP184 | 35p | PCF83 | 40p | AD 114 | 40p |
| EAB30 | 40p | EP190 | 75p | PCF86 | 60p | AD 113 | 40p |
| EA742 | 75p | EL32 | £2-30 | PCF90 | 75p | AD 112 | 40p |
| EB81 | 30p | EL34 | 70p | PCF201 | 75p | AD 111 | 40p |
| EB83 | £1-00 | EL36 | 80p | PCF801 | 55p | AD 110 | 40p |
| EB84 | 75p | EL37 | £1-80 | PCF802 | 50p | AD 109 | 40p |
| EB85 | 40p | EL41 | 30p | PCF805 | 75p | AD 108 | 40p |
| EB86 | 40p | EL41 | 30p | PCF806 | 75p | AD 107 | 40p |
| EB87 | 40p | EL42 | 30p | PCF808 | 90p | AD 106 | 40p |
| EC82 | 35p | EL84 | 30p | PCH100 | 80p | AD 105 | 40p |
| EC83 | 40p | EL86 | 60p | PCL81 | 55p | AD 104 | 40p |
| EC84 | 35p | EL88 | 45p | PCL82 | 45p | AD 103 | 40p |
| EC85 | 35p | EL90 | 45p | PCL83 | 45p | AD 102 | 40p |
| EC86 | 35p | EL94 | 60p | PCL84 | 45p | AD 101 | 40p |
| EC88 | 40p | EM31 | 65p | PCL85 | 55p | AD 100 | 40p |
| EC89 | 40p | EM34 | 65p | PCL86 | 60p | AD 99 | 40p |
| EC90 | 40p | EM38 | 40p | PL1200 | 70p | AD 98 | 40p |
| EC91 | 40p | EM40 | 40p | PL36 | 60p | AD 97 | 40p |
| EC92 | 40p | EM47 | £1-00 | PL36 | 60p | AD 96 | 40p |
| EC93 | 40p | EM41 | 45p | PL81 | 50p | AD 95 | 40p |
| EC94 | 40p | EM42 | 45p | PL82 | 45p | AD 94 | 40p |
| EC95 | 40p | EM43 | 45p | PL83 | 45p | AD 93 | 40p |
| EC96 | 40p | EM44 | 45p | PL84 | 45p | AD 92 | 40p |
| EC97 | 40p | EM45 | 45p | PL85 | 45p | AD 91 | 40p |
| EC98 | 40p | EM46 | 45p | PL86 | 45p | AD 90 | 40p |
| EC99 | 40p | EM47 | 45p | PL87 | 45p | AD 89 | 40p |
| EC100 | 40p | EM48 | 45p | PL88 | 45p | AD 88 | 40p |
| EC101 | 40p | EM49 | 45p | PL89 | 45p | AD 87 | 40p |
| EC102 | 40p | EM50 | 45p | PL90 | 45p | AD 86 | 40p |
| EC103 | 40p | EM51 | 45p | PL91 | 45p | AD 85 | 40p |
| EC104 | 40p | EM52 | 45p | PL92 | 45p | AD 84 | 40p |
| EC105 | 40p | EM53 | 45p | PL93 | 45p | AD 83 | 40p |
| EC106 | 40p | EM54 | 45p | PL94 | 45p | AD 82 | 40p |
| EC107 | 40p | EM55 | 45p | PL95 | 45p | AD 81 | 40p |
| EC108 | 40p | EM56 | 45p | PL96 | 45p | AD 80 | 40p |
| EC109 | 40p | EM57 | 45p | PL97 | 45p | AD 79 | 40p |
| EC110 | 40p | EM58 | 45p | PL98 | 45p | AD 78 | 40p |
| EC111 | 40p | EM59 | 45p | PL99 | 45p | AD 77 | 40p |
| EC112 | 40p | EM60 | 45p | PL100 | 45p | AD 76 | 40p |

TRANSISTORS, DIODES etc.

| | | | | | |
|--------|--------|---------|---------|--------|---------|
| AC 112 | AF 139 | BSY 27 | OA 202 | OC 200 | SN 3053 |
| AC 126 | AF 178 | BSY 36 | OAZ 200 | OC 204 | SN 3054 |
| AC 127 | AF 185 | BSY 56A | OC 22 | OC 206 | SN 3055 |
| AC 128 | AF 192 | BR7 16 | OC 25 | OC 208 | SN 3056 |
| AC 175 | AF 226 | CR8 110 | OC 28 | OC 210 | SN 3057 |
| AC 176 | AF 23 | CR8 120 | OC 29 | OC 212 | SN 3058 |
| AC 177 | AF 28 | CR8 130 | OC 30 | OC 214 | SN 3059 |
| AC 178 | AF 28 | CR8 140 | OC 31 | OC 216 | SN 3060 |
| AC 179 | AF 28 | CR8 150 | OC 32 | OC 218 | SN 3061 |
| AC 180 | AF 28 | CR8 160 | OC 33 | OC 220 | SN 3062 |
| AC 181 | AF 28 | CR8 170 | OC 34 | OC 222 | SN 3063 |
| AC 182 | AF 28 | CR8 180 | OC 35 | OC 224 | SN 3064 |
| AC 183 | AF 28 | CR8 190 | OC 36 | OC 226 | SN 3065 |
| AC 184 | AF 28 | CR8 200 | OC 37 | OC 228 | SN 3066 |
| AC 185 | AF 28 | CR8 210 | OC 38 | OC 230 | SN 3067 |
| AC 186 | AF 28 | CR8 220 | OC 39 | OC 232 | SN 3068 |
| AC 187 | AF 28 | CR8 230 | OC 40 | OC 234 | SN 3069 |
| AC 188 | AF 28 | CR8 240 | OC 41 | OC 236 | SN 3070 |
| AC 189 | AF 28 | CR8 250 | OC 42 | OC 238 | SN 3071 |
| AC 190 | AF 28 | CR8 260 | OC 43 | OC 240 | SN 3072 |
| AC 191 | AF 28 | CR8 270 | OC 44 | OC 242 | SN 3073 |
| AC 192 | AF 28 | CR8 280 | OC 45 | OC 244 | SN 3074 |
| AC 193 | AF 28 | CR8 290 | OC 46 | OC 246 | SN 3075 |
| AC 194 | AF 28 | CR8 300 | OC 47 | OC 248 | SN 3076 |
| AC 195 | AF 28 | CR8 310 | OC 48 | OC 250 | SN 3077 |
| AC 196 | AF 28 | CR8 320 | OC 49 | OC 252 | SN 3078 |
| AC 197 | AF 28 | CR8 330 | OC 50 | OC 254 | SN 3079 |
| AC 198 | AF 28 | CR8 340 | OC 51 | OC 256 | SN 3080 |
| AC 199 | AF 28 | CR8 350 | OC 52 | OC 258 | SN 3081 |
| AC 200 | AF 28 | CR8 360 | OC 53 | OC 260 | SN 3082 |
| AC 201 | AF 28 | CR8 370 | OC 54 | OC 262 | SN 3083 |
| AC 202 | AF 28 | CR8 380 | OC 55 | OC 264 | SN 3084 |
| AC 203 | AF 28 | CR8 390 | OC 56 | OC 266 | SN 3085 |
| AC 204 | AF 28 | CR8 400 | OC 57 | OC 268 | SN 3086 |
| AC 205 | AF 28 | CR8 410 | OC 58 | OC 270 | SN 3087 |
| AC 206 | AF 28 | CR8 420 | OC 59 | OC 272 | SN 3088 |
| AC 207 | AF 28 | CR8 430 | OC 60 | OC 274 | SN 3089 |
| AC 208 | AF 28 | CR8 440 | OC 61 | OC 276 | SN 3090 |
| AC 209 | AF 28 | CR8 450 | OC 62 | OC 278 | SN 3091 |
| AC 210 | AF 28 | CR8 460 | OC 63 | OC 280 | SN 3092 |
| AC 211 | AF 28 | CR8 470 | OC 64 | OC 282 | SN 3093 |
| AC 212 | AF 28 | CR8 480 | OC 65 | OC 284 | SN 3094 |
| AC 213 | AF 28 | CR8 490 | OC 66 | OC 286 | SN 3095 |
| AC 214 | AF 28 | CR8 500 | OC 67 | OC 288 | SN 3096 |
| AC 215 | AF 28 | CR8 510 | OC 68 | OC 290 | SN 3097 |
| AC 216 | AF 28 | CR8 520 | OC 69 | OC 292 | SN 3098 |
| AC 217 | AF 28 | CR8 530 | OC 70 | OC 294 | SN 3099 |
| AC 218 | AF 28 | CR8 540 | OC 71 | OC 296 | SN 3100 |
| AC 219 | AF 28 | CR8 550 | OC 72 | OC 298 | SN 3101 |
| AC 220 | AF 28 | CR8 560 | OC 73 | OC 300 | SN 3102 |
| AC 221 | AF 28 | CR8 570 | OC 74 | OC 302 | SN 3103 |
| AC 222 | AF 28 | CR8 580 | OC 75 | OC 304 | SN 3104 |
| AC 223 | AF 28 | CR8 590 | OC 76 | OC 306 | SN 3105 |
| AC 224 | AF 28 | CR8 600 | OC 77 | OC 308 | SN 3106 |
| AC 225 | AF 28 | CR8 610 | OC 78 | OC 310 | SN 3107 |
| AC 226 | AF 28 | CR8 620 | OC 79 | OC 312 | SN 3108 |
| AC 227 | AF 28 | CR8 630 | OC 80 | OC 314 | SN 3109 |
| AC 228 | AF 28 | CR8 640 | OC 81 | OC 316 | SN 3110 |
| AC 229 | AF 28 | CR8 650 | OC 82 | OC 318 | SN 3111 |
| AC 230 | AF 28 | CR8 660 | OC 83 | OC 320 | SN 3112 |
| AC 231 | AF 28 | CR8 670 | OC 84 | OC 322 | SN 3113 |
| AC 232 | AF 28 | CR8 680 | OC 85 | OC 324 | SN 3114 |
| AC 233 | AF 28 | CR8 690 | OC 86 | OC 326 | SN 3115 |
| AC 234 | AF 28 | CR8 700 | OC 87 | OC 328 | SN 3116 |
| AC 235 | AF 28 | CR8 710 | OC 88 | OC 330 | SN 3117 |
| AC 236 | AF 28 | CR8 720 | OC 89 | OC 332 | SN 3118 |
| AC 237 | AF 28 | CR8 730 | OC 90 | OC 334 | SN 3119 |
| AC 238 | AF 28 | CR8 740 | OC 91 | OC 336 | SN 3120 |
| AC 239 | AF 28 | CR8 750 | OC 92 | OC 338 | SN 3121 |
| AC 240 | AF 28 | CR8 760 | OC 93 | OC 340 | SN 3122 |
| AC 241 | AF 28 | CR8 770 | OC 94 | OC 342 | SN 3123 |
| AC 242 | AF 28 | CR8 780 | OC 95 | OC 344 | SN 3124 |
| AC 243 | AF 28 | CR8 790 | OC 96 | OC 346 | SN 3125 |
| AC 244 | AF 28 | CR8 800 | OC 97 | OC 348 | SN 3126 |
| AC 245 | AF 28 | CR8 810 | OC 98 | OC 350 | SN 3127 |
| AC 246 | AF 28 | CR8 820 | OC 99 | OC 352 | SN 3128 |
| AC 247 | AF 28 | CR8 830 | OC 100 | OC 354 | SN 3129 |
| AC 248 | AF 28 | CR8 840 | OC 101 | OC 356 | SN 3130 |
| AC 249 | AF 28 | CR8 850 | OC 102 | OC 358 | SN 3131 |
| AC 250 | AF 28 | CR8 860 | OC 103 | OC 360 | SN 3132 |
| AC 251 | AF 28 | CR8 870 | OC 104 | OC 362 | SN 3133 |
| AC 252 | AF 28 | CR8 880 | OC 105 | OC 364 | SN 3134 |
| AC 253 | AF 28 | CR8 890 | OC 106 | OC 366 | SN 3135 |
| AC 254 | AF 28 | CR8 900 | OC 107 | OC 368 | SN 3136 |
| AC 255 | AF 28 | CR8 910 | OC 108 | OC 370 | SN 3137 |
| AC 256 | AF 28 | CR8 920 | OC 109 | OC 372 | SN 3138 |
| AC 257 | AF 28 | CR8 930 | OC 110 | OC 374 | SN 3139 |
| AC 258 | AF 28 | CR8 940 | OC 111 | OC 376 | SN 3140 |
| AC 259 | AF 28 | CR8 950 | OC 112 | OC 378 | SN 3141 |
| AC 260 | AF 28 | CR8 960 | OC 113 | OC | |



GIRO NO. 331 7056. Access accepted.
C.V.A. only, P. & F. 10% on orders below £5
Discounts £10-10%, £10-15% (except note items)
Export Order enquiries welcome (VAT free)
Official Orders accepted from
Educational & Government Departments
ALL PRICES INCLUDE VAT AT 8%

SPECIAL RESISTOR KITS (Prices include post & packing)
10E12 1/2W KIT: 10 of each E12 value, 22 ohms—1M, a total of 570 (CARBON FILM 5%), £3.58 net
10E12 1/4W KIT: 10 of each E12 value, 22 ohms—1M, a total of 570 (CARBON FILM 5%), £3.77 net
25E12 1/2W KIT: 25 of each E12 value, 22 ohms—1M, a total of 1425 (CARBON FILM 5%), £8.19 net
25E12 1/4W KIT: 25 of each E12 value, 22 ohms—1M, a total of 1425 (CARBON FILM 5%), £8.28 net
5E12 1/2W KIT: 5 of each E12 value, 10 ohms—1M, a total of 305 (METAL FILM 5%), £2.80 net
Due to current world shortages, resistor kits may contain some high and value substitutions.

MULLARD POLYESTER CAPACITORS C280 SERIES
250V P.C. Mounting: 0-01µF, 0-015µF, 0-022µF, 0-033µF, 0-047µF, 3p, 0-068µF, 12p, 1µF, 4p, 0-15µF, 4p, 0-22µF, 5p, 0-33µF, 8p, 0-47µF, 9p, 0-68µF, 12p, 1µF, 15p, 1-5µF, 23p, 2-2µF, 26p.

MULLARD POLYESTER CAPACITORS C296 SERIES
400V: 0-001µF, 0-0015µF, 0-0022µF, 0-0033µF, 0-0047µF, 2p, 0-0068µF, 0-01µF, 0-015µF, 0-022µF, 0-033µF, 3p, 0-047µF, 0-068µF, 0-1µF, 4p, 0-15µF, 6p, 0-22µF, 8p, 0-33µF, 12p, 0-47µF, 14p.
160V: 0-01µF, 0-015µF, 0-022µF, 0-033µF, 0-047µF, 0-068µF, 3p, 0-1µF, 4p, 0-15µF, 5p, 0-22µF, 5p, 0-33µF, 6p, 0-47µF, 8p, 0-68µF, 12p, 1µF, 14p.

MINIATURE CERAMIC PLATE CAPACITORS
50V: (pF) 22, 27, 33, 39, 47, 56, 68, 82, 100, 120, 150, 180, 220, 270, 330, 390, 470, 560, 680, 820, 1K, 1K5, 2K2, 3K3, 4K7, 6K8, (µF) 0-01, 0-015, 0-022, 0-033, 0-047, 2p, each. 0-1, 30V, 5p.

POLYSTYRENE CAPACITORS 160V 5%
(pF) 10, 15, 22, 33, 47, 68, 100, 150, 220, 330, 470, 680, 1000, 1500, 2200, 3300, 4700, 6800, 10000, 4p.

RESISTORS

CF—High Stag Carbon Film, 5% MF—High Stag Metal Film, 5%.

| | | | | | |
|---------------|------|---------|---------|-------|----------|
| W. Type Range | 1-99 | 100-499 | 500-999 | 1000+ | Size mm |
| 1/4 CF 22-1M | 1 | 0-75 | 0-60 | 0-55 | 2-4x7-5 |
| 1/4 CF 22-2M2 | 1 | 0-75 | 0-60 | 0-55 | 3-9x10-5 |
| 1/4 CF 22-1M | 1 | 0-75 | 0-60 | 0-55 | 5-5x16 |
| 1/4 MF 10-2M7 | 2 | 1-54 | 1-32 | 1-1 | 3x7 |
| 1/4 MF 10-2M2 | 2 | 1-43 | 1-21 | 0-99 | 4-2x10-8 |
| 1/4 MF 10-10M | 3 | 1-98 | 1-81 | 1-65 | 6-6x13 |
| 2 MF 10-10M | 4-5 | 3-52 | 3-08 | 2-75 | 8x17-5 |

For value mixing prices, please refer to our catalogue. (price in pence each).
VALUES AVAILABLE—E12 Series only. (Net prices above 100.)

PRESET SKELETON POTENTIOMETERS
MINIATURE 0-25W Vertical or horizontal 6p each 1K, 2K2, 4K7, 10K, etc. up to 1M Ω
SUB-MIN 0-05W Vertical, 100 Ω to 220K Ω 5p each.

B. H. COMPONENT FACTORS LTD. (P.W.) 61 CHEDDINGTON ROAD, PITSTONE N.R. LEIGHTON BUZZARD, BEDS., LU7 9AD
Tel.: Cheddington 688446 (Std. Code 0296)
CATALOGUE No. 3 20p

Miniature Mullard Electrolytics

| | | | |
|-----------|----|-------------|-----|
| 1-0µF 63V | 6p | 68µF 16V | 6p |
| 1-5µF 63V | 6p | 68µF 63V | 12p |
| 2-2µF 63V | 6p | 100µF 10V | 6p |
| 3-3µF 63V | 6p | 100µF 25V | 6p |
| 4-0µF 63V | 6p | 100µF 15V | 14p |
| 4-7µF 63V | 6p | 150µF 63V | 6p |
| 6-8µF 63V | 6p | 150µF 15V | 15p |
| 8-0µF 63V | 6p | 220µF 6-4V | 6p |
| 10µF 16V | 6p | 220µF 10V | 6p |
| 10µF 25V | 6p | 220µF 16V | 8p |
| 10µF 33V | 6p | 220µF 63V | 21p |
| 15µF 16V | 6p | 330µF 63V | 25p |
| 15µF 25V | 6p | 330µF 15V | 25p |
| 16µF 40V | 6p | 470µF 6-4 | 9p |
| 22µF 25V | 6p | 470µF 40V | 20p |
| 22µF 63V | 6p | 680µF 16V | 15p |
| 32µF 10V | 6p | 680µF 40V | 25p |
| 33µF 16V | 6p | 1000µF 16V | 20p |
| 33µF 40V | 6p | 1000µF 25V | 25p |
| 33µF 63V | 6p | 1500µF 6-4V | 15p |
| 47µF 10V | 6p | 1500µF 16V | 25p |
| 47µF 25V | 6p | 2200µF 10V | 25p |
| 47µF 63V | 8p | 3300µF 6-4V | 26p |

VEROBOARD 0-1 0-15

| | | |
|------------------------|-----|-----|
| 2 1/2 x 5" | 36p | 36p |
| 2 1/2 x 3 1/2" | 33p | 25p |
| 3 1/2 x 3 1/2" | 42p | 46p |
| 3 1/2 x 3" | 36p | 36p |
| 2 1/2 x 1 1/2" | — | — |
| 2 1/2 x 5" (Plain) | — | 19p |
| 2 1/2 x 3 1/2" (Plain) | — | 16p |
| 5 x 3 1/2" (Plain) | — | 29p |
| Insertion tool | 73p | 73p |
| Track Cutter | 56p | 56p |
| Pins, Pkt. 25 | 22p | 22p |

POTENTIOMETERS
Carbon Track 5K Ω to 2M Ω, log or lin (and 1K lin). Single, 16p Duaf. Gang 46p. Log single with switch 26p. Slider Pots, 10K, 100K, 500K, semi log 30mm, 34p. 45mm, 47p, 60mm, 55p.

DIODES

| | | |
|------------|------------|-----|
| IN4001 6p | DIN 2 Pin | 12p |
| IN4002 6p | 3 Pin | 13p |
| IN4002 7p | 3 Pin | 13p |
| IN4003 9p | 5 Pin 180° | 16p |
| IN4004 9p | Std. Jack | 20p |
| IN4005 13p | 2.5mm Jack | 13p |
| IN4006 14p | Phone | 6p |
| IN914 7p | SOCKETS | |
| IN916 7p | DIN 2 Pin | 10p |
| OA100 10p | 3 Pin | 10p |
| OA5 42p | 6 Pin 180° | 12p |
| OA47 9p | Std. Jack | 15p |
| OAB1 1p | 2.5mm Jack | 13p |
| OA200 8p | Phone | 6p |

ELECTROLYTIC CAPACITORS. Tubular & Large Cans
(µF/V): 1/25, 2/25, 4/25, 4/710, 5/25, 8/25, 10/10, 10/50, 16/25, 22/63, 25/25, 25/50, 32/25, 50/25, 100/10, 100/25, 6p, 50/50, 8p, 100/50, 200/25, 11p, 250/50, 18p, 500/10, 11p, 500/25, 15p, 500/50, 18p, 1000/10, 15p, 1000/25, 22p, 1000/50, 20p, 2000/10, 20p, 1000/100, 88p, 2000/25, 30p, 2000/100, 93p, 2500/25, 30p, 2500/50, 61p, 5000/25, 65p, 5000/50, 61-08.
HI-VOLT: 4/350, 14p, 6/350, 19p, 100/100 20p, 16/350, 22p, 16/450, 23p, 32/350, 33p, 50/250, 20p, 100/250, 30p.
METALLISED PAPER CAPACITORS
250V: 0-05µF, 0-1µF, 6p, 0-25, 6p, 0-5µF, 7p, 1µF, 9p, 500V: 0-025, 0-05, 6p, 0-1, 6p, 0-25, 7p, 0-5, 9p, 1000V: 0-01, 11p, 0-022, 13p, 0-047, 0-1, 15p, 0-22, 23p, 0-47, 34p.

STOP PRESS
Our Retail Shop should now be open at 59 North St., Leighton Buzzard

| | | |
|-------------------------------------|-----------|-----------------------|
| Screened Wire, Metre | 6p | NEW KIT |
| Twin Screened Wire, Metre | 12p | 5E12 1W Metal Film, |
| Screened Screened Wire, Metre | 12p | 5 each value 10 Ω-1M, |
| Connecting Wire, All colours, Metre | 24p | total of 305 |
| Neon Bulb, 90V Wire Ended | 5 for 24p | £3.25 |
| Panel Neon, 240V Red, Amber, Clear | 20p | |

MULTIMETER U4323
22 Ranges plus AF/IF Oscillator 20,000 Ω/Volt.
Vdc—0-5-1000V in 7 ranges
Vac—2-5-1000V in 6 ranges
Idc—0-05-1000mA in 5 ranges
Resistance—50 Ω—1M Ω in 4 ranges.
Accuracy—5% of F.S.D.
OSCILLATOR—1 KHz and 465 KHz (A.M.) at approx. 1 Volt.
Size—160 x 97 x 40mm.
Supplied complete with carrying case, test leads and battery.
PRICE £48.30 net p & p 25p.



U4323

MULTIMETER U4341
27 Ranges plus Transistor Tester, 16,700 Ω/Volt. Overload protected, Vdc—0-3-300V in 8 ranges.
Vac—1-5-750V in 6 ranges.
Idc—0-06-600mA in 5 ranges.
Iac—0-3-300mA in 4 ranges.
Resistance—2K Ω—2M Ω in 4 ranges.
Accuracy—dc—2 1/2%, ac—4% of F.S.D.
Ifr—10-350 in 2 ranges.
Size—115 x 215 x 90mm.
Complete with steel carrying case, test leads, and battery.
PRICE £11.30 net p & p 30p.



U4341

NEW CAPACITOR KITS
C280 Kit—PC Mounting polyester 250V. 5 of each value: 0-01 0-022, 0-047, 0-1, 0-22µF. 2 of 0-47, 1µF. £1.30 net.
C296 Kit—Tubular polyester, 400V. 5 of each value: 0-01, 0-022, 0-047, 0-1, 0-22µF. 2 of 0-47µF. £1.30 net.
Ceramic Kit—square planquette 50V. 5 of each value: 22, 33, 47, 100, 220, 330, 470, 1000pF, 2200, 4700pF, 0-01µF, £1.30 net.
250V Paper kit—Tubular metal case. 3 of each value: 0-05, 0-1, 0-25, 0-5, 1µF. 90p net.
500V Paper Kit—Tubular metal case, 3 of each value: 0-025, 0-05, 0-1, 0-25, 0-5µF. 90p net.
1000V Paper Kit—Tubular metal case. 3 each value: 0-01, 0-025, 0-05, 0-1µF. £1.10 net.

S-DC

| | |
|----------|-------|
| S-DeC | £2-14 |
| T-DeC | £3-92 |
| µDeC "A" | £4-30 |
| µDeC "B" | £7-53 |
| 2 DeC | £4-72 |

ANTEX

| | |
|-------|-------|
| CN240 | £2-43 |
| CN240 | £2-01 |
| X25 | £2-01 |

PANEL METERS

| | | |
|----------|-------|-------|
| 2" scale | 100µA | £1-95 |
| 100µA | 500µA | £1-95 |
| 1mA | All | £1-95 |
| 5mA | at | £1-95 |
| 10mA | £3-75 | £1-95 |
| 50mA | | £1-95 |
| 100mA | | £1-95 |
| 500mA | | £1-95 |
| 1A | | £1-95 |

Dalo Pen 98p
"expert" solder gun £6.95
Wire pack 5 x 5mtrs. 27p
Diode pack (Ge) 50 for 25p
Jackson "00" 365pF 98p
C804, 5pF, 10pF, 15pF 83p
20pF, 25pF, 50pF 89p
60pF, 75pF, 100pF 91p
Dilecon 100, 300pF 91p
500pF
LED, TIL 209 5 for 61
Panel holder 4 colours 23p
R/r y Sw'ch's, IP12V, 2P6V, 3P4V, 4P3V 6P2V 30p

COMPLETE NEW RANGE

We have a new range of low cost frequency counters and frequency standards, not to mention our instrument cases, metal boxes and Eurithmic Loudspeaker systems.
We supply calculators from £11.00 up + Books, Digital Clocks, Hi-Fi Components, Quadraphonic Records and Kits, Dolby units and Uher Tape recorders. Our lists are free but postage would be appreciated.


Studio Electronics
P.O. BOX 18 HARLOW CM18 6SH ESSEX
TEL: HARLOW (STD 0279) 25457

VHF MODULATOR

Which enables the use of a standard TV as a monitor for CCTV and Video games (TV Tennis). Operates from 8V-12 VDC. Tuneable over VHF Channels 27-40. Input—Standard 1V p.p. Video. Output—7.5mV into 75ohm at 600 MHz. Dimensions 2 1/2" x 2" x 1 1/2"—8" Coax.
Price—Fully Assembled and Tested £6.50 inc. VAT and postage.

Please send cheque or P.O. with order to:
STRONG ELECTRONICS LIMITED
Bourne Works, Whyteleafe, Surrey CR3 0YD

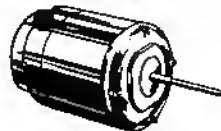"SLO-SYN" 3-LEAD SYNCHRONOUS STEPPING MOTOR



Type SS1S. These fine motors are easily reversed, starting and stepping in less than 50 without electrical or mechanical braking. Simple relay circuit can be applied to give DC... to winding for a maximum holding torque of 300oz/in with 35v at 0.35 amps through windings. For AC (synchronous) operation at 120v., 50Hz, Speed 60 rpm at 60Hz., 72 rpm. STEPPING. Holding torque at 50 steps per second—1000 oz/in. Can be wired to give 100 or 200 steps per revolution with accuracy of 0.1° per step non-cumulative. Torque characteristics can be modified by simple R.C. circuits. Dimensions: dia. 4", body length 4 1/2", spindle length 2 1/2" x 3/8" dia. Weight 6 1/2 lbs. BRAND NEW in maker's packing. Offered at less than 1/2 maker's price. **OUR PRICE ONLY £15**

NORPLEX


Fibro-glass copper-clad laminate. Finest quality epoxy resin base. Heat resistant, ideal for P.C.B. Sizes: 12" x 12"; 24" x 12"; 24" x 24"; FULL SHEET 43" x 37" (11 sq ft). Single-sided Copper with thickness of 1/32", 3/64", 3/32". Also double-sided 1/16", 1/8", 3/32". £1 per sq ft. Cut sizes (1-10 sq. ft.) 25p. P. & P. Full Sheet £8 each. Carr. £1 for 1st sheet plus 25p each additional sheet.

SMITHS RINGER-TIMER

Reliable 15 minute times, spring wound (concurrent with time setting) 15 x 1min divisions, approximately 1/2" between divisions. Panel mounting with chrome bezel 3 1/2" dia. £1.40. 15p P. & P.

KNOWLE (U.S.A.) MINIATURE MICROPHONE CAPSULES

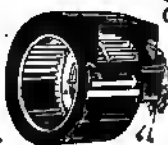Impedance approx. 200Ω, output 60 or 80 DB at 1 Kc. As used in deaf aids, bugging devices, etc. Size (60 DB) 7/32" x 5/32" x 3/4"; (80 DB) 2 1/8" x 5/32" x 1/2". Equipment, all tested. £1.20 each. P. & P. FREE.



Ultra PRECISION CENTRIFUGAL BLOWER

by Air Control Ltd.
30 segments individually balanced in heavy cast alloy case. 2,300 r.p.m. 240 A.C. Very powerful and silent running. 5 1/2" dia. 3" inlet dia. Outlet flange 3" x 2 1/2". **LIMITED NUMBER ONLY**
£4.95. P & P 40p.

MAINS SOLENOID

This little unit gives vertical lift of approximately 1" through hinged 'f e l b o w'. Bracket incorporates 2 fixing screws. Length of arm, 2 1/2". 240V A.C. Pull at coil is approximately 1lb. £1. **FREE P. & P.** Special quotes for quantities.

SOLENOIDS by WESTOOL

240AC type MM6. 3lb. pull, 2 1/2" x 1 1/2" x 1 1/2". Travel 1". 90p. each. P. & P. 10p.
240AC type MM4. 2lb. pull, 1 1/2" x 1 1/2" x 1". Travel 3/8". 70p each. P. & P. 10p. Quantity discounts: 10-50 10%, 50 upwards 25%.

OPEN FRAME shaded pole GEARED MOTORS


(Dural gear case)
240 A.C., 28rpm, NEW HIGH TORQUE, approx. overall size: 3 1/2" x 3 1/2" x 2 1/2" x spindle 2" dia. as illustrated. £2.70. P. & P. 30p. Similar to above, 19rpm. £2.70. P. & P. 30p. 110rpm with pressed steel gear case (similar to above but slightly smaller). £2.70. P. & P. 30p.

SILVANIA MAGNETIC SWITCH

Now complete with reference magnet!

A magnetically activated switch, vacuum sealed in a glass envelope. Silver contacts, normally closed. Rated 5amp at 120v. 1amp at 240v. Size: (approx.) 1 1/2" long x 1/2" dia. Ideal for burglar alarms, security systems etc., and wherever non-mechanical switching is required. 10 for £2.10; P. & P. 15p. 50 for £8.60; 100 for £15.50. **FREE P. & P.** over 10.

AMPEX 7.5v. D.C. MOTOR

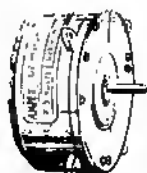

An ultra precision tape motor designed for use in the A230 portable recorder. Torque 450GM/CM. Stall load at 500ma. Draws 60ma on run, 600rpm ± speed adjustment. Internal A.F.R.F. suppression, 1" dia. x 1 1/2" spindle, motor 3" dia. x 1 1/2". Original cost £18.50. **OUR PRICE £3.30.** P. & P. 25p. Quantity available. Mu-metal enclosure available 75p each. **FREE P. & P.**

ALL PRICES INCLUDE V.A.T.

Whilst we welcome official orders from established companies and Educational Departments, it is no longer practical to invoice goods under £5. Therefore, please remit cash with orders below this amount.

315/317, EDGWARE ROAD, LONDON, W2.
Tel: 01-723 5667 01-402 5580

ELECTRO-TECH COMPONENTS LTD.

YOUR CAREER in RADIO & ELECTRONICS ?

Big opportunities and big money await the qualified man in every field of Electronics today—both in the U.K. and throughout the world. We offer the finest home study training for all subjects in radio, television, etc., especially for the CITY & GUILDS EXAMS (Technicians' Certificates); the Grad. Brit. I.E.R. Exam; the RADIO AMATEUR'S LICENCE; P.M.G. Certificates; the R.T.E.B. Servicing Certificates; etc. Also courses in Television; Transistors; Radar; Computers; Servo-mechanisms; Mathematics and Practical Transistor Radio course with equipment. We have OVER 20 YEARS' experience in teaching radio subjects and an unbroken record of exam. successes. We are the only privately run British home study College specialising in electronics subjects only. Full details will be gladly sent without any obligation.

To: British National Radio & Electronics School, Dept W.C. 25 P.O. Box 156, Jersey, C.I.

Please send FREE BROCHURE to

NAME Block

ADDRESS Caps.

..... Please

BRITISH NATIONAL RADIO AND ELECTRONICS SCHOOL

ULTRON COMPONENTS

35 PARK AVENUE, POTTERS BAR, HERTS. 01-882 4355

MAIL ORDER ONLY

CASH WITH ORDER, OR PHONE US

DISCOUNTS:—15% off for 12+
20% off for 50+
25% off for 100+

COMPARE THESE PRICES—
ALL INCLUSIVE OF V.A.T.

Add 10p p & p for orders under £2.00

ALL TOP BRANDED MAKES, AND GUARANTEED

| | | | | | | | | | |
|--------|-----|---------|-------|---------|-----|---------|-------|--------|-------|
| AC126 | 18p | BCY43 | 25p | 2N1303 | 18p | 2N2507A | 18p | 2N3866 | 70p |
| AC127 | 18p | BCY38 | 16p | 2N1308 | 25p | 2N2925 | 14p | 2N3803 | 14p |
| AC128 | 18p | BCY39 | 16p | 2N1306 | 25p | 2N2928 | 9p | 2N3806 | 14p |
| AC187 | 12p | BP164 | 16p | 2N1307 | 25p | 2N2933 | 18p | 2N3903 | 15p |
| AC188 | 12p | BY127 | 11p | 2N1308 | 27p | 2N2954 | 42p | 2N4061 | 12p |
| AD149 | 45p | MJ480 | 75p | 2N1309 | 27p | 2N2956 | 44p | 2N4062 | 13p |
| AD181 | 85p | MJ481 | 95p | 2N1371 | 90p | 2N2958 | 86p | OC29 | £1.00 |
| AD182 | 85p | MJ490 | 85p | 2N1371A | 95p | 2N2959 | 89p | OC28 | 88p |
| AF123 | 24p | MJE371 | 40p | 2N1371B | £1 | 2N2961 | 80p | OC29 | 80p |
| AF178 | 40p | MJE2861 | £1.15 | 2N2927 | 31p | 2N2962 | 89p | OC35 | 45p |
| BC107 | 10p | MJE2865 | £1.00 | 2N2928 | 30p | 2N2963 | 12p | OC36 | 60p |
| BC107B | 10p | MJE3005 | 95p | 2N2929 | 18p | 2N2972 | 10p | OC83 | 20p |
| BC108 | 10p | 2N698 | 28p | 2N2927 | 27p | 2N2973 | 10p | OC71 | 75p |
| BC109 | 10p | 2N699 | 30p | 2N2933 | 75p | 2N2974 | 11p | | |
| BC109B | 11p | 2N706A | 11p | 2N2959 | 13p | 2N2975 | 10p | R.C.A. | |
| BC113 | 13p | 2N706 | 13p | 2N2969A | 13p | 2N2977 | 10p | 40309 | 30p |
| BC114 | 14p | 2N914 | 16p | 2N2411 | 50p | 2N2979 | 7p | 40310 | 35p |
| BC118 | 10p | 2N915 | 24p | 2N2646 | 44p | 2N3710 | 11p | 40311 | 42p |
| BC136 | 16p | 2N918 | 30p | 2N2846 | 70p | 2N3711 | 11p | 40313 | 50p |
| BC187 | 16p | 2N920 | 45p | 2N2894 | 85p | 2N3730 | 90p | 40314 | 32p |
| BC193 | 17p | 2N921 | 50p | 2N2904A | 45p | 2N3771 | £1.10 | 40315 | 32p |
| BC194 | 17p | 2N922 | 50p | 2N2906 | 22p | 2N3773 | £2.26 | 40316 | 35p |
| BC183L | 10p | 2N1131 | 20p | 2N2908 | 14p | 2N3791 | £2.26 | 40319 | 89p |
| BCY42 | 27p | 2N1132 | 20p | 2N2909A | 16p | 2N3810 | 25p | 40320 | 89p |

| 6 amp stud diodes | 741 | 35p | 8C40D | £1.05 | 16/400 | 80p | Bridge Rectifiers |
|--|------|-------|-------|-------|--------|-------|-------------------|
| 15 amp stud diodes <td>1310</td> <td>£2.40</td> <td>8C45D</td> <td>£1.80</td> <td>16/600</td> <td>£1.20</td> <td>1A 60V 24p</td> | 1310 | £2.40 | 8C45D | £1.80 | 16/600 | £1.20 | 1A 60V 24p |
| | | | 8C46E | £1.45 | 1/05 | 30p | 2A 600V 45p |
| | | | 8C30D | £1.50 | 1/10 | 35p | 4A 200V 85p |

AND MANY, MANY MORE

SINCLAIR CALCULATORS


Sinclair Scientific £22.45 (£2-05)
Cambridge Assembled £15.95 (£1-55)
Cambridge Memory £20.95 (£1-95)

FERRANTI ZN414

IC radio chip with data £1-20 (22p). Also available kit of extra parts to complete a radio £2-50 (43p). Send see for free leaflet.

SINCLAIR PROJECT 80

AFU £5-36 (73p)
Z40 £5-12 (63p)
Z60 £5-38 (73p)
Q16 £7-21 (80p)
P25 £5-11 (63p)
P26 £7-79 (84p)
P28 £7-36 (80p)
Decoder £7-75 (84p). Trans for P28 £3-85 (50p).
Tuner £11-62 (£1-37). Stereo 80 £11-62 (£1-37).
Project 80S £29-95 (£2-90).
Project 80SQ £33-95 (£3-10).
Project 80 SQ Quad Decoder £15-95 (£1-18)



ECONOMICAL QUADRAPHONICS

Introducing the Napolex QA10 self contained matrix quadraphonic synthesizer. Just feed the output of any stereo system (including Project 80 or 80) into it and hook on 4 speakers to obtain the latest experience in sound. Send see for free leaflet. Only £10-15 (£1-10).



SINCLAIR SUPER IC12

6well IC power amp and preamp. With 44 page booklet and printed circuit £1-80 (40p).



NEW SINCLAIR IC20

High power IC audio amplifier £8-45 (£1-05).

DELUXE KIT FOR THE IC12

Includes all parts for the printed circuit and volume, bass and treble controls needed to complete the mono version £1-75 (27p). Stereo model with balance control £3-80 (44p).

IC12 POWER KIT

Supplies 28V 0.5 Amps £2-99 (57p).

LOUDSPEAKERS FOR THE IC12

5" x 8 ohm £1-35 (35p). 5" x 8" x 8 ohm £1-75 (47p).

PREAMP KITS FOR THE IC12

Type 1 for magnetic pickups, mics and tuners Mono model £1-45 (28p). Stereo model £2-80 (35p). Type 2 for ceramic or crystal pickups. Mono 75p (20p). Stereo £1-30 (25p).

SEND SAE FOR FREE LEAFLET ON KITS

BATTERY ELIMINATOR

BARGAINS

The most versatile battery eliminator ever offered. Switched output of 3, 4.5, 6, 7.5, 9 and 12V at 500 mA £3-90 (57p).



Other eliminators stocked:—

250mA:—3 way switched model

giving 6, 7.5 and

9V £2-50 (58p).

50mA:— 4.5V £2-40 (40p). 6V £2-40 (40p). 9V

£2-40 (40p). 7.5V cassette type £2-80

(50p). Double 4.5V + 4.5V £2-95 (50p).

6V + 6V £2-95 (50p). 9V + 9V £2-95

(50p).

500mA:— Heavy duty deluxe models 6V £2-78

(55p). 7.5V £2-78 (55p). 9V £2-78 (55p).

S-DECS AND T-DECS

S-DeC £1-99 (31p)

T-DeC £2-63 (47p)

U-DeC A £3-99 (51p)

U-DeC B £8-99 (81p)

IC carriers:—

16 dils plain 81p (15p)

with socket £1-77 (25p)

10 TO5: plain 75p (15p). With socket £1-88 (24p).

Experiment guides:—A £1-50 (36p). B £1-77 (36p).

C 90p (28p). D £2-40 (45p). E £2-20 (63p).



SWANLEY ELECTRONICS

PO BOX 68, SWANLEY,
KENT BR8 8TQ.

Please add the sum shown in brackets after the price to cover the cost of post and new VAT. Official credit orders from schools etc. welcome. No VAT charged on overseas orders.

CENTURION

INSTRUMENT



CASES

Model Nos. 119 and 121 two part aluminum construction base front and back unit finished in white gloss, hooded cover finished in blue hammer stove enamel.

Model D W H

119 152mm 127mm 89mm £1-60 ea

121 152mm 203mm 76mm £2-00 ea

Model Nos. 221F and 222F flat packs. Front & Rear panels aluminium case mild steel front panel finished in white gloss other parts finished in blue hammer stove enamel.

221F 152mm 203mm 152mm £2-80 ea

222F 197mm 254mm 159mm £3-40 ea

Prices include P & P U.K.
Add 8% V.A.T. U.K. only.
Send S.A.E. for full range brochure.

Manufactured by


Arbore Electronics Limited

Unit 13 East Hanningfield Ind. Est.
Nr. Chelmsford, Essex CM3 5BG
Tel. Chelmsford (0245) 400700.

Sheet metal work wiring assembly service available

H.A.C. SHORT-WAVE KITS

WORLD-WIDE RECEPTION

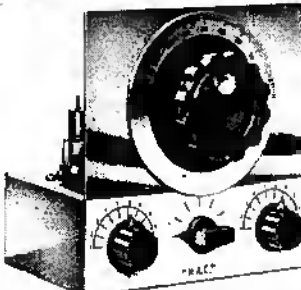

Famous for over 25 years for Short-Wave Equipment of quality. "H.A.C." were the Original suppliers of Short-Wave Receiver Kits for the amateur constructor. Over 10,000 satisfied customers—including Technical Colleges, Hospitals, Public Schools, R.A.F. Army, Hants, etc.

1974 "DX" RECEIVER

Complete kit—Price £4-90 incl. p. & p. & V.A.T. Customer writes: "Australia, India and America at loud volume."—"I have now heard over 300 stations including many Amateurs. I have received 32 Q.S.L. verified reports—from all continents. An amazing one-valve."

This kit contains all genuine short-wave components, built to precise, valve, accessories and full instructions. Ready to assemble, and of course, as all our products—fully guaranteed. Full range of other S.W. kits, including the famous model "K plus" (illustrated above). All orders despatched by return. Send now for free descriptive catalogue of kits and components. Test Report available. EXCITING COMPETITION for Short-Wave listeners. Send stamped envelope for details.

"H.A.C." SHORT-WAVE PRODUCTS
P.O. BOX NO. 16, EAST GRINSTEAD,
SUSSEX RH11 3SN

ambit INTERNATIONAL

LINEAR Price Logic Price

| LINEAR | Price | Logic | Price |
|-----------|-------|--------|-------|
| CT 7001 | 9.80 | 7400 | 0.20 |
| LM 380 | 1.00 | 74S00 | 0.74 |
| LM 381 | 1.85 | 7402 | 0.23 |
| TBA 810s | 1.50 | 7404 | 0.23 |
| LM 3900 | 0.68 | 7413 | 0.38 |
| TBA 120A/ | | 7446 | 1.20 |
| SN 76660N | 1.00 | 7447 | 1.20 |
| CA 3089e/ | | 7448 | 1.25 |
| TDA 1200 | 1.94 | 7473 | 0.31 |
| CA 3053 | 0.52 | 7474 | 0.31 |
| ua 753 | 0.99 | 7490 | 0.71 |
| TBA 651 | 1.81 | 7493 | 0.71 |
| CA 3123E | 1.40 | 74S112 | 2.30 |
| MC 1310 | 2.80 | 74121 | 0.38 |
| CA 3090Q | 2.80 | 74192 | 1.57 |
| CA 3090AQ | 3.75 | | |
| ua 7805UC | 1.75 | | |
| ua 7805KC | 2.05 | | |
| NE 550A | 0.80 | | |
| ua 753 | 0.80 | | |
| ua 710 | 0.55 | | |
| ua 733 | 1.80 | | |
| ua 741CV | 0.40 | | |
| NE 560B | 3.19 | | |
| NE 561B | 3.19 | | |
| NE 562B | 3.19 | | |
| NE 565A | 2.75 | | |
| NE 566V | 2.55 | | |
| NE 567V | 2.75 | | |
| NE 555V | 0.78 | | |
| ICL 8038 | | | |
| CC | 3.10 | | |
| LM 1496 | 1.02 | | |

Transistors

| | |
|----------|------|
| BFY 51 | 0.25 |
| BC 109 | 0.12 |
| BC 183L | 0.14 |
| BC 212 | 0.14 |
| BF 256LB | 0.34 |
| MEM 615 | 0.38 |
| MEM 616 | 0.50 |
| 2N 3702 | 0.14 |
| 2N 3704 | 0.14 |
| TIP 2955 | 0.99 |
| TIP 3055 | 0.60 |
| 1N 4004 | 0.10 |
| 1N 4148 | 0.07 |

TOKO Coils and filters

| | |
|-------------------------------------|------|
| 4KHZ 455KHz Mechanical filter | 1.35 |
| 7KHZ 455KHz Mechanical filter | 1.35 |
| 8KHZ 455KHz Ceramic filter | 0.45 |
| 6KHZ 455KHz Ceramic filter | 0.45 |
| 6KHZ 470KHz Ceramic filter | 0.50 |
| 6KHZ 470KHz Ceramic filter | 0.45 |
| 200KHz 10.7MHz Ceramic filter | 0.40 |
| 22uH choke for CA 3089E | 0.15 |
| Quadrature coil for CA 3089E | 0.30 |
| Double quadrature coil | 0.55 |
| CA 3090Q | 0.30 |
| 19 and 38KHz notch filter | 1.50 |
| 455KHz 1st IF transformer | 0.27 |
| 455KHz 2nd IF transformer | 0.27 |
| 455KHz 3rd IF transformer | 0.27 |
| LW oscillator coil | 0.27 |
| LW antenna loading coil | 0.27 |
| HW osc coil (TBA 651) | 0.27 |
| MW osc coil (CA 3123E) | 0.27 |
| 10.7MHz IF Transformer | 0.50 |
| 43mH Choke | 0.27 |
| 5.1mH Choke | 0.27 |
| 265+265pF plastic variable cap 0.55 | |

8319

Larsen NEW MOSFET tunerhead. The much awaited new varicap tunerhead. 7.74

FM 1185

Ambit FM IF amplifier and demod. with AFC, tuning meter and field strength meter outputs. Uses CA 3089E and ceramic filter plus TOKO coils. 4.25

FM 1185

Ambit FM IF amplifier and demod. with AFC, tuning meter and field strength meter outputs. Uses CA 3089E and ceramic filter plus TOKO coils. 4.25

FM 1185

Ambit FM IF amplifier and demod. with AFC, tuning meter and field strength meter outputs. Uses CA 3089E and ceramic filter plus TOKO coils. 4.25

Ambit FM IF amplifier and demod. with AFC, tuning meter and field strength meter outputs. Uses CA 3089E and ceramic filter plus TOKO coils. 4.25

Ambit FM IF amplifier and demod. with AFC, tuning meter and field strength meter outputs. Uses CA 3089E and ceramic filter plus TOKO coils. 4.25

Ambit FM IF amplifier and demod. with AFC, tuning meter and field strength meter outputs. Uses CA 3089E and ceramic filter plus TOKO coils. 4.25

Ambit FM IF amplifier and demod. with AFC, tuning meter and field strength meter outputs. Uses CA 3089E and ceramic filter plus TOKO coils. 4.25

Ambit FM IF amplifier and demod. with AFC, tuning meter and field strength meter outputs. Uses CA 3089E and ceramic filter plus TOKO coils. 4.25

Ambit FM IF amplifier and demod. with AFC, tuning meter and field strength meter outputs. Uses CA 3089E and ceramic filter plus TOKO coils. 4.25

Ambit FM IF amplifier and demod. with AFC, tuning meter and field strength meter outputs. Uses CA 3089E and ceramic filter plus TOKO coils. 4.25

Ambit FM IF amplifier and demod. with AFC, tuning meter and field strength meter outputs. Uses CA 3089E and ceramic filter plus TOKO coils. 4.25

Ambit FM IF amplifier and demod. with AFC, tuning meter and field strength meter outputs. Uses CA 3089E and ceramic filter plus TOKO coils. 4.25

Ambit FM IF amplifier and demod. with AFC, tuning meter and field strength meter outputs. Uses CA 3089E and ceramic filter plus TOKO coils. 4.25

Ambit FM IF amplifier and demod. with AFC, tuning meter and field strength meter outputs. Uses CA 3089E and ceramic filter plus TOKO coils. 4.25

Ambit FM IF amplifier and demod. with AFC, tuning meter and field strength meter outputs. Uses CA 3089E and ceramic filter plus TOKO coils. 4.25

Ambit FM IF amplifier and demod. with AFC, tuning meter and field strength meter outputs. Uses CA 3089E and ceramic filter plus TOKO coils. 4.25

Ambit FM IF amplifier and demod. with AFC, tuning meter and field strength meter outputs. Uses CA 3089E and ceramic filter plus TOKO coils. 4.25

Ambit FM IF amplifier and demod. with AFC, tuning meter and field strength meter outputs. Uses CA 3089E and ceramic filter plus TOKO coils. 4.25

Ambit FM IF amplifier and demod. with AFC, tuning meter and field strength meter outputs. Uses CA 3089E and ceramic filter plus TOKO coils. 4.25

Ambit FM IF amplifier and demod. with AFC, tuning meter and field strength meter outputs. Uses CA 3089E and ceramic filter plus TOKO coils. 4.25

Ambit FM IF amplifier and demod. with AFC, tuning meter and field strength meter outputs. Uses CA 3089E and ceramic filter plus TOKO coils. 4.25

Ambit FM IF amplifier and demod. with AFC, tuning meter and field strength meter outputs. Uses CA 3089E and ceramic filter plus TOKO coils. 4.25

Ambit FM IF amplifier and demod. with AFC, tuning meter and field strength meter outputs. Uses CA 3089E and ceramic filter plus TOKO coils. 4.25

Ambit FM IF amplifier and demod. with AFC, tuning meter and field strength meter outputs. Uses CA 3089E and ceramic filter plus TOKO coils. 4.25

Ambit FM IF amplifier and demod. with AFC, tuning meter and field strength meter outputs. Uses CA 3089E and ceramic filter plus TOKO coils. 4.25

Ambit FM IF amplifier and demod. with AFC, tuning meter and field strength meter outputs. Uses CA 3089E and ceramic filter plus TOKO coils. 4.25

Ambit FM IF amplifier and demod. with AFC, tuning meter and field strength meter outputs. Uses CA 3089E and ceramic filter plus TOKO coils. 4.25

Ambit FM IF amplifier and demod. with AFC, tuning meter and field strength meter outputs. Uses CA 3089E and ceramic filter plus TOKO coils. 4.25

CA3090AQ decoder kit
+ MPX filter £5.40
Built & tested £6.60

Catalogue 25p

ALL PRICES EXCLUDE VAT.
PLEASE ADD 8% TO ALL UK ORDERS.
POST AND PACKING 15p

37a HIGH STREET
BRENTWOOD
ESSEX CM14 4RH

Telephone: (0277) 216029 Telex: 996194

BI-PRE-PAK

INTRODUCE

Sterling Sound Audio Modules




| | |
|-----------------------------------|-------|
| SS.203 Stereo Decoder | £5.62 |
| SS.202 I.F. Stage (Pre-tuned) | £5.25 |
| SS.201 Front end (Variable tuned) | £6.25 |

Stereo Decoder, ready for connecting to the IF stages of existing FM Radio or Tuner. The very latest 2nd Generation coil-less integrated circuit design, operating on this phase locked loop system, offering even better stereo separation. LED stereo indicator lights available.

SS.103 3W R.M.S. I.C. AMP

on P.C. Board with all components built and tested **£1.75**

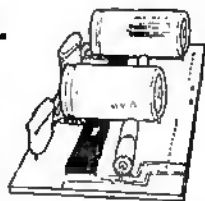SS.103-3 Two I.C. stereo version **£3.25**



These amps. are supplied with a free booklet on connecting up, specifications and easy to build projects.

5W & 10W POWER AMPS



SS.105 5W **£1.95**

SS.110 10W **£2.40**

These matchbox size amplifiers have an exceptionally good tone and quality for the price. They are only 2 1/2" x 1 1/2". The 5W amp will run from a 12V car battery making it very suitable for portable voice reinforcement such as public functions. Two amplifiers are ideal for stereo. Complete connection details and treble, bass, volume and balance control circuit diagrams are supplied with each unit. Discounts available for quantity orders.

Other Sterling Sound Modules

Pre-assembled printed circuit boards 2" x 3" available in stereo only, will fit -15 edge connector.

Stereo Pre-Amp SS.101 is for use with crystal or ceramic cartridges. **£1.60**

Stereo Pre-Amp SS.102 for use with low output magnetic cartridges. **£2.25**

Stereo Tone Control SS.10C active tone control board will give bass and treble boost and cut. Pots. extra. **£1.60**

Instruction leaflet supplied with all units. VAT at 8% must be added to total value of order. Postage and packing—add 15p (U.K. orders)

To BI-PRE-PAK LTD., 224 West Road Westcliffe-on-sea Essex SS0 8DF.

Please send SS Modules

I enclose £..... Inc. V.A.T.

Name

Address

- ★ ELECTRONIC PIANO KIT
- ★ SYNTHESISER KIT
- ★ ELECTRONIC ORGAN KITS



There are five superb Electronic Organ kits specially designed for the D-I-Y enthusiast. With the extreme flexibility allowed in design, you can build an organ to your requirements, which will compare with an organ commercially built costing double the price.

★ Portable organ with 4 octave keyboard, £145.29. ★ Console organ with 5 octave keyboard, £269.90. ★ Console organ with 2 x 4 octave keyboards and 13 note pedal board. £470.65. ★ Console organ with 2 x 5 octave keyboards and 32 note pedal board. £655. ★ Console organ with 3 x 5 octave keyboards and 32 note pedal board. £770. ★ W/W Sound Synthesiser Kit. £130. ★ W/W Touch Sensitive Electronic Piano. £100.

All components can be purchased separately, i.e., semi-conductor devices, M.O.S. master oscillators, coils, keyboards, pedal boards, stop tabs, draw bars, key-contacts, etc.

Send 50p for catalogue which includes 5 x 10p vouchers or send your own parts list, enclosing S.A.E. for quotation.

ELVINS

ELECTRONIC MUSICAL INSTRUMENTS

Designers and component suppliers to the musical industry
12 Brett Road, Hackney, London, E8 1JP. Tel. 01-986 8455

Tele-Tennis

As described in Practical Wireless

Play the game that's sweeping the nation. You've seen it in pubs, clubs and arcades—now you can play it in the comfort of your own home.

Plugs into the aerial of your U.H.F. 625 Black & White or Colour television. No internal connections to your T.V. set. Does not interfere with other T.V. programmes. Built from 6 neat sub-sections, purchase a complete kit or sub-section at a time.

All parts available separately including P. C. boards, case and ready punched and slotted fascia panel.

S.A.E. for full details.

DABAR ELECTRONIC PRODUCTS


98 LICHFIELD STREET
WALSALL, Staffs WS1 1UZ



CHROMASONIC electronics


Dept 1.
56, Fortus Green Road, London, N10 3HN
telephone 01 883 3705

OPTOELECTRONICS




Monsanto

Common Anode
MAN 72
MAN 52
MAN 82



Xcitron

Common Cathode
MAN 74
MAN 54
MAN 84



litronix

DL 707
DL 701
DL 747
DL 746

OUR PRICE £2.59 £1.83 £2.65

LIGHT EMITTING DIODES

Free snap-on plastic resistor

| | 0.125" dia | 0.2" dia |
|-----------|-----------------------------|------------------------|
| | TIL209 size | MLED650 size |
| | Our Usual price | Our Usual price |
| | Special Peck Price | Special Peck Price |
| 10 RED | £2.40 £2.99 | £2.40 £2.39 |
| 10 GREEN | £2.40 £3.49 | £2.40 £3.99 |
| 10 YELLOW | £2.40 £2.99 | £2.40 £3.99 |
| 10 WHITE | £2.40 £3.39 | |
| 10 ORANGE | £3.10 | £4.90 |
| 10 RED | 0.175" dia T092 size | £2.40 £1.39 |

LINEAR I.C.'s

| | | | | | |
|-------------------|-------|----------|--------|----------|--------|
| 709 (8 pin dip) | 33p | LM377 | £2.91 | LM414 | £1.725 |
| 709 (TO-99) | 39p | LM380 | £1.08 | LM415 | £2.24 |
| 709 (14 pin dip) | 34p | LM381 | £2.28 | LM440 | £2.84 |
| 710 (8 pin dip) | 34p | LM382 | £2.19 | SN75491 | £1.43 |
| 710 (TO-99) | 39p | LM390 | 73p | SN75492 | £1.60 |
| 710 (14 pin dip) | 38p | | | TA423 | 80p |
| 711 (TO-99) | 44p | MC1303L | £1.85 | TA430 | £1.76 |
| 711 (14 pin dip) | 38p | MC1208P | 54p | TA4310 | £1.34 |
| 723 (TO-99) | 94p | MC1310 | £2.45 | TA4320 | 97p |
| 722 (14 pin dip) | 64p | | | TA4350 | £2.31 |
| 741 (8 pin dip) | 31p | MC 1312 | £2.42 | TA4370 | £5.05 |
| 741 (TO-99) | 44p | MC 1314 | £4.05 | TA4500 | 90p |
| 741 (14 pin dip) | 42p | MC 1315 | £5.37 | TA4570 | £1.67 |
| 747 (14 pin dip) | 90p | | | TA4700 | £3.56 |
| 748 (8 pin dip) | 41p | MC1330P | 86p | TA0100 | £1.33 |
| 748 (TO-99) | 44p | MC1339P | £1.26 | TBA231 | 88p |
| 748 (14 pin dip) | 42p | MC1350 | £1.26 | TBA500 | £2.85 |
| | | MC1351 | £1.08 | TBA520 | £2.66 |
| AY-1-0212 | £5.99 | MC1352 | £1.08 | TBA530 | £1.94 |
| AY-5-1024 | £4.59 | MC1357 | £1.56 | TBA560C | £3.96 |
| AY-5-3507 | £7.45 | MC1358 | £1.65 | TBA675A | £1.03 |
| AY-5-3510 | £6.92 | MC1375 | £1.38 | TBA625B | £1.03 |
| | | MC1456CG | £1.71 | TBA625C | £1.03 |
| | | MC1458CI | £2.37 | TBA651 | £1.62 |
| SHADA2 | £3.87 | MC1468G | £2.47 | TBA800 | 90p |
| | | MC1475 | £3.54 | TBA810S | £1.07 |
| CA304A | 93p | MC1490G | £1.46 | TBA810AS | £2.92 |
| CA306A | £1.53 | MC3302 | £1.30 | TBA820 | 74p |
| CA307A | £1.62 | MC3401 | 75p | TCA940 | £1.94 |
| CA308A | £1.61 | MFC4000B | 40p | IDA1200 | £2.10 |
| CA308Z | £1.62 | MFC4060A | 76p | IDA1405 | 97p |
| | | MFC603DA | £1.89 | IDA1412 | 97p |
| 100ST1 | £1.45 | MFC6040 | £1.00 | IDA1415 | 97p |
| 1036T1 | £1.45 | | | ULN2111A | 1.56 |
| 1037T1 | £1.45 | | | 2N402E | 1.94 |
| 1129 | £1.39 | MM5314 | 7.76 | 2N414 | 1.29 |
| 1130 | £1.39 | MM5316 | £16.17 | | |
| 1131 | £1.39 | | | | |
| LM301 (TO-99) | 59p | MVE3V | £1.62 | | |
| LM301 (8 pin dip) | 52p | MVR17V | £1.42 | | |
| LM307 (TO-99) | 59p | MVR15V | £1.62 | | |
| LM307 (8 pin dip) | 52p | | | | |
| LM308HTO-99 | £1.26 | NE540 | £1.29 | | |
| LM308 (8 pin dip) | 97p | NE555 | 85p | | |
| LM309C | £2.36 | NE560 | £1.62 | | |
| LM339 | £3.68 | NE561B | £3.45 | | |
| LM371 | £2.04 | NE562 | £3.45 | | |
| LM372 | £2.43 | NE563 | £2.39 | | |
| LM373 | £3.04 | NE580 | £1.75 | | |
| | | NE597 | £2.39 | | |

Back in stock again!

HC244R


The Stabilized Power supply for which demand always exceeds supply switched 2, 6, 7, & 9 volts up to 400 mA. Polarity reversal switch, Neon Mains Indicator, on/off switch, 4/6 Lead Multi-Way output plug adaptor, Metal Case, Rubber Feet. £4.89 + p & p 10p

74 SERIES TTL

1st GRADE BRANDED PRODUCTS

| | | | | | |
|------|-----|-------|------|-------|------|
| 7400 | 17p | 7442 | 90p | 7490 | 69p |
| 7401 | 17p | 7445 | 1.20 | 7491 | 1.10 |
| 7402 | 17p | 7447 | 1.15 | 7492 | 80p |
| 7403 | 17p | 7447A | 1.76 | 7493 | 70p |
| 7404 | 17p | 7448 | 1.47 | 74100 | 2.32 |
| 7406 | 25p | 7470 | 32p | 74121 | 30p |
| 7409 | 29p | 7473 | 33p | 74122 | 85p |
| 7410 | 17p | 7474 | 48p | 74141 | 1.07 |
| 7413 | 29p | 7475 | 63p | 74154 | 1.76 |
| 7420 | 17p | 7476 | 42p | 74192 | 2.11 |
| 7430 | 17p | 7486 | 35p | 74193 | 2.45 |
| 7441 | 90p | 7489 | 4.65 | 74196 | 1.70 |

F.M. STEREO TUNERS

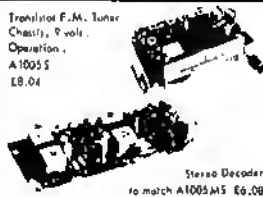

Transistor F.M. Tuner Chassis, 9 volts Operation, A1005 S £8.04



New Mini F.M. Tuner * 12 volt supply £6.76 Matching Stereo Decoder £4.86

Stereo Decoder to match A1005MS £6.09

SIEMENS LCD's

20:59

LIQUID CRYSTAL DISPLAY complete with socket and removable reflective backing. Ref AN4132R 13mm character height. Can be directly driven by National Semiconductor Alarm Clock chip MM5316.


OUR PRICE £13.99

24 HOUR DESPATCH NOW IN OPERATION

AT LAST

We can now supply the complete set of I.C.'s for the Full Logic version of the CES 50 Decoder. The MC1312, MC1314 & MC1315. Under CES licensing arrangements these can only be sold as a kit inclusive of associated components. Please ask for free price list.

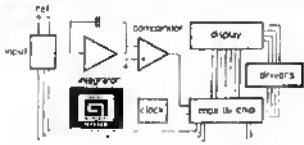3 1/2 DECADE DIGITAL VOLTMETER INTEGRATED CIRCUIT




This state-of-the-art MOS LSI chip contains all the logic necessary for a 3 1/2 decade, dual slope integrating, automatic polarity detecting DVM. Supplied with free data and circuit booklet. AY-5-3507

OUR PRICE ONLY £7.46


(booklets alone 20p)

PHOTO-DARLINGTON

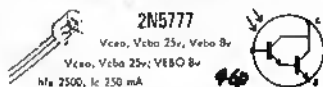

2N5777
Vceo, Vcbo 25v, Vcbo 8v
Vceo, Vcbo 25v, VEBO 8v
Ic 2500, Ic 250 mA

MINITRON

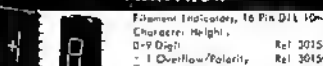

Fluorescent Indicators, 16 Pin DIL 10mm Character Height. Ref 3015P Ref 3015G
- 1 Overflow/Polarity

NEW PRICE £1.26



LP1186 Diode - tuned From End £4.65
LP1185 F. M. I. F. Amplifier £3.58
LP1400 Stereo Multiplex Decoder £4.86

This trio make one of the most fabulous F. M. tuners of all time. Typical channel separation 50 db.

SPECIAL OFFERS

Left Hand Decimal Point
All Common Anodes,
Character Height 0.3"

4 for £5.99
5 for £7.95
6 for £8.93

RED (Led 7)
GREEN (Led 18)
YELLOW (Led 21)



VAT INCLUDED AT 8%

OVERSEAS CUSTOMERS DEDUCT 2 1/2%
VAT INVOICES ON REQUEST
P&P On UK Orders min 15p

CALLERS WELCOME

Marshall's

A. Marshall & Son (London) Limited Dept. PW
42 Cricklewood Broadway London NW2 3HD Tel: 01-452 0161
& 85 West Regent Street Glasgow G22 0D Tel: 041-332 4133

Everything you need is in our new 1975 catalogue. Available now price 25p

Trade and export enquiries welcome

PW TELE TENNIS

As featured in PRACTICAL WIRELESS July - November 1974.
Also on BBC Nationwide and in the Daily Mail October 2nd 1974.

This exciting new game is now available in kit form. Due to popular demand we are now able to offer a fantastic saving on list prices. Ideal game for whole family. No need to modify your TV set, just plugs in to aerial socket. Parts list as follows:

| | | | | | |
|----------------------|-----|-----|-----|-----|----------------|
| A Resistor Pack | ... | ... | ... | ... | £1.00 p.p. 20p |
| B Potentiometer Pack | ... | ... | ... | ... | £1.25 p.p. 20p |
| C Capacitor Pack | ... | ... | ... | ... | £1.45 p.p. 20p |
| D Semiconductor Pack | ... | ... | ... | ... | £4.00 p.p. 20p |
| E IC Sockets | ... | ... | ... | ... | £1.15 p.p. 25p |
| F Transformer | ... | ... | ... | ... | £7.50 p.p. 20p |
| G PCB's | ... | ... | ... | ... | £4.50 p.p. 20p |
| H Switches | ... | ... | ... | ... | £7.20 p.p. 20p |
| I UHF Modulator Kit | ... | ... | ... | ... | £7.20 p.p. 20p |

Special Prices—complete kit (excluding case) £42.00 p.p. 50p Sections A-F incl. £23.50 plus 30p. Assembly instructions with complete kit of 75p on request.

| | | | | | | | |
|----------|-----|--------|-------|--------|-------|---------|-------|
| SN7400 | 16p | SN7420 | 16p | SN7453 | 16p | SN7491 | £1.10 |
| SN7401 | 16p | SN7423 | 37p | SN7454 | 16p | SN7492 | 75p |
| SN7401AN | 38p | SN7425 | 37p | SN7460 | 16p | SN7493 | 65p |
| SN7402 | 16p | SN7427 | 45p | SN7470 | 30p | SN7494 | 85p |
| SN7403 | 16p | SN7430 | 16p | SN7471 | 30p | SN7495 | 85p |
| SN7404 | 24p | SN7432 | 45p | SN7472 | 44p | SN7496 | £1.00 |
| SN7405 | 24p | SN7437 | 35p | SN7474 | 48p | SN74100 | £2.16 |
| SN7406 | 45p | SN7438 | 35p | SN7475 | 59p | SN74107 | 43p |
| SN7407 | 45p | SN7440 | 16p | SN7476 | 45p | SN74118 | £1.00 |
| SN7408 | 25p | SN7441 | 85p | SN7480 | 75p | SN74119 | £1.92 |
| SN7409 | 33p | SN7442 | 85p | SN7481 | £1.25 | SN74121 | 57p |
| SN7410 | 16p | SN7445 | £1.59 | SN7482 | 87p | SN74122 | 80p |
| SN7411 | 25p | SN7446 | £2.00 | SN7483 | £1.20 | SN74123 | 72p |
| SN7412 | 28p | SN7447 | £1.30 | SN7484 | 95p | SN74141 | £1.00 |
| SN7413 | 50p | SN7448 | £1.50 | SN7485 | £1.58 | SN74150 | £1.44 |
| SN7416 | 45p | SN7450 | 16p | SN7486 | 45p | SN74190 | £1.95 |
| SN7417 | 30p | SN7451 | 16p | SN7490 | 65p | | |

TRY OUR NEW GLASGOW SHOP

Prices correct at October 1974, but all exclusive of V.A.T. Post and Package 20p postage and package charges

Popular Semi-conductors

| | | | | | | | | | |
|---------|-------|--------|-------|--------|-----|---------|-------|----------|-------|
| 2N696 | 22p | 2N3707 | 13p | AD142 | 59p | 3C309 | 10p | LM709 | 48p |
| 2N697 | 16p | 2N3708 | 70p | AD143 | 45p | BC137 | 21p | TO99 | 38p |
| 2N698 | 40p | 2N3715 | £1.50 | AD161 | 45p | BC138 | 19p | 8D1L | 33p |
| 2N699 | 45p | 2N3716 | £1.80 | AD162 | 45p | BCY70 | 17p | 14D1L | 40p |
| 2N1302 | 19p | 2N3771 | £2.20 | AD161 | pr | BCY21 | 22p | LM723C | 90p |
| 2N1303 | 19p | 2N3772 | £1.80 | AD161 | pr | BCY72 | 13p | LM741 | 13p |
| 2N1304 | 24p | 2N3773 | £2.65 | AF109R | 40p | BD123 | 32p | TO99 | 40p |
| 2N1305 | 24p | 2N3819 | 37p | AF115 | 24p | DB131 | 40p | 8D1L | 70p |
| 2N1306 | 31p | 2N3870 | 39p | AF124 | 30p | DB132 | 30p | 8D1L | 30p |
| 2N1307 | 23p | 2N3823 | £1.10 | AF125 | 39p | BD135 | 45p | LM747 | £1.00 |
| 2N1308 | 25p | 2N3904 | 27p | AF126 | 28p | BD136 | 49p | LM7805 | £2.00 |
| 2N1309 | 36p | 2N3905 | 24p | AF127 | 28p | BD137 | 55p | MC1310 | £2.92 |
| 2N1671 | £1.44 | 2N4036 | 63p | AF139 | 39p | BD138 | 63p | M1480 | 90p |
| 2N1671A | £1.54 | 2N4037 | 42p | AF170 | 55p | BD139 | 71p | M1481 | £1.14 |
| 2N1671B | £1.72 | 2N4216 | 20p | AF179 | 65p | BD140 | 82p | M149C | 98p |
| 2N1671C | £4.32 | 2N4299 | 36p | AF180 | 36p | BF115 | 50p | M1491 | £1.38 |
| 2N2102 | 76p | 2N4921 | 73p | AF179 | 51p | BF116 | 23p | MJE340 | 45p |
| 2N2147 | 78p | 2N4922 | 84p | AF240 | 73p | BF117 | 43p | MJE2955 | £1.12 |
| 2N2148 | 94p | 2N4923 | 83p | AF279 | 54p | BF154 | 16p | MJE3055 | 68p |
| 2N2160 | 60p | 2N5190 | 92p | AF280 | 54p | BF163 | 32p | MFC4000B | 40p |
| 2N2218A | 22p | 2N5191 | 95p | 8C107 | 16p | BF180 | 35p | MFC4010A | 49p |
| 2N2219 | 24p | 2N5192 | £1.24 | BC108 | 15p | BF181 | 34p | MFC4060 | 54p |
| 2N2219A | 26p | 2N5195 | £1.46 | BC109 | 19p | BF184 | 30p | MFC6040 | 91p |
| 2N2221 | 18p | 2N5202 | 45p | BC124 | 75p | BF194 | 12p | NE560D | £4.48 |
| 2N2221A | 21p | 2N5457 | 49p | BC148 | 13p | BF195 | 13p | NE531 | £4.48 |
| 2N2222 | 20p | 2N5458 | 45p | BC149 | 13p | BF196 | 13p | NE565A | £4.48 |
| 2N2222A | 25p | 2N5459 | 49p | BC167B | 13p | BF197 | 15p | OC28 | 76p |
| 2N2646 | 55p | 40361 | 44p | BC168B | 13p | BF198 | 18p | OC42 | 50p |
| 2N2904 | 22p | 40362 | 50p | BC168C | 11p | BF200 | 40p | OC71 | 17p |
| 2N2904A | 24p | 40363 | 80p | BC169B | 13p | BF237 | 22p | OC71B | 17p |
| 2N2905 | 24p | 40407 | 44p | BC124 | 75p | BF238 | 22p | OC71C | 17p |
| 2N2905A | 26p | 40408 | 50p | BC182 | 13p | BFX29 | 20p | SL414A | £1.80 |
| 2N2906 | 18p | 40408 | 50p | BC182L | 12p | BFX30 | 27p | TAA263 | £1.80 |
| 2N2906A | 21p | 40409 | 52p | BC183 | 12p | BFX64 | 24p | TBA800 | £1.50 |
| 2N2907 | 22p | 40410 | 52p | BC183L | 12p | BFX85 | 30p | TBA810 | £1.50 |
| 2N2907A | 24p | 40411 | £1.25 | BC184 | 13p | BFX87 | 28p | TIP29A | 49p |
| 2N2926 | 11p | 40602 | 46p | BC184L | 13p | BFX88 | 25p | TIP30A | 58p |
| 2N3053 | 25p | 40604 | 56p | BC212K | 16p | BFX89 | 45p | TIP31A | 62p |
| 2N3054 | 26p | 40605 | 49p | BC212L | 16p | BFX19 | 65p | TIP32B | 62p |
| 2N3055 | 75p | AC117 | 20p | BC214L | 21p | BFY51 | 21p | TIP33A | £1.01 |
| 2N3441 | 97p | AC126 | 20p | BC237 | 13p | BFY52 | 21p | TIP34A | £1.51 |
| 2N3442 | £1.69 | AC127 | 20p | BC238 | 13p | BFY90 | 75p | TIP35A | £2.90 |
| 2N3415 | 10p | AC128 | 20p | BC239 | 13p | BRY39 | 48p | TIP36A | £3.70 |
| 2N3416 | 15p | AC151V | 25p | BC257 | 14p | CI060 | 65p | TIP41A | 79p |
| 2N3417 | 21p | AC152A | 17p | BC258 | 13p | CA3020A | 1.80 | TIP42A | 90p |
| 2N3702 | 11p | AC132K | 35p | BC124 | 75p | CA3046 | 1.80 | TIP295 | 90p |
| 2N3703 | 12p | AC176 | 18p | BC300 | 36p | CA3048 | £2.11 | TIP3055 | 60p |
| 2N3704 | 14p | AC176K | 25p | BC301 | 34p | CA3089E | £1.96 | ZTX300 | 13p |
| 2N3705 | 12p | AC187K | 23p | BC307 | 11p | CA30900 | £4.23 | ZTX302 | 20p |
| 2N3706 | 9p | AC188K | 14p | BC308 | 12p | LM1301A | 46p | ZTX500 | 15p |

TRANSFORMERS

SAFETY MAINS ISOLATING TRANSFORMERS

Err. 120/240 V Sec. 120/240 V Centre Tapped and Screened

| Ref. No. | VA (Watts) | Weight lb oz | Size cm. | £ P & P |
|----------|------------|--------------|--------------------|----------|
| 07 | 20 | 1 | 7-0 x 6-0 x 6-0 | 2.55 38 |
| 149 | 60 | 3 | 9-9 x 7-7 x 8-6 | 3.98 45 |
| 150 | 100 | 5 | 9-9 x 8-9 x 8-6 | 4.45 45 |
| 151 | 200 | 8 | 12-1 x 9-3 x 10-2 | 7.39 53 |
| 152 | 350 | 13 | 12-1 x 11-8 x 10-2 | 8.93 73 |
| 153 | 350 | 15 | 14-0 x 10-8 x 11-8 | 10.80 73 |
| 154 | 500 | 19 | 14-0 x 13-4 x 11-8 | 12-41 91 |
| 155 | 750 | 29 | 17-2 x 14-0 x 14-0 | 18.65 .. |
| 156 | 1000 | 38 | 17-2 x 16-6 x 14-0 | 26.50 .. |
| 157 | 1500 | 46 | 21-6 x 13-4 x 18-1 | 30.23 .. |
| 158 | 2000 | 60 | 21-6 x 15-3 x 18-1 | 33.70 .. |

AUTO TRANSFORMERS

| Ref. No. | VA (Watts) | Weight lb oz | Size cm. | Auto Taps | £ P & P |
|----------|------------|--------------|--------------------|-------------------|----------|
| 113 | 20 | 1 | 5-8 x 5-1 x 4-5 | 0-115-210-240 | 1.52 30 |
| 64 | 75 | 2 | 7-4 x 6-7 x 6-1 | 0-115-210-240 | 1.64 30 |
| 4 | 150 | 3 | 8-9 x 7-7 x 7-7 | 0-115-200-220-240 | 3.75 45 |
| 66 | 300 | 6 | 9-9 x 9-6 x 8-6 | .. | 5.29 53 |
| 67 | 500 | 12 | 12-1 x 11-2 x 10-2 | .. | 8.02 67 |
| 84 | 1000 | 19 | 14-0 x 13-4 x 14-3 | .. | 12.49 91 |
| 93 | 1500 | 30 | 14-0 x 15-9 x 14-3 | .. | 16.65 .. |
| 95 | 2000 | 32 | 17-2 x 16-6 x 14-0 | .. | 22.00 .. |
| 73 | 3000 | 40 | 21-6 x 13-4 x 18-1 | .. | 31.90 .. |

CASED AUTO TRANSFORMERS

115V mains lead input and U.S.A. 2-pin outlets. 20VA £2.85 pp 38p
500VA £9.50 pp 80p 1000VA £15.92 via B.R.S.

TRANSFORMERS

PRIMARY 140-250 VOLTS 12 AND OR 24 VOLT RANGE

| Ref. No. | Ampr. | Weight lb oz | Size cm. | Secondary Windings | £ P & P |
|----------|-------|--------------|-------------------------|--------------------|----------|
| 111 | 0.5 | 0.25 | 8 4-8 x 2-9 x 3.5 | 0-12V at 0.25A x2 | 1.34 23 |
| 213 | 1.0 | 0.5 | 1 4 6-1 x 5-8 x 4-8 | 0-12V at 0.5A x2 | 1.58 30 |
| 17 | 1 | 1 | 1 12 7-0 x 6-4 x 6-1 | 0-12V at 1A x2 | 2.09 38 |
| 110 | 4 | 2 | 12 8-3 x 7-7 x 7-0 | 0-12V at 2A x2 | 2.69 38 |
| 70 | 6 | 3 | 8 8-9 x 8-0 x 7-7 | 0-12V at 3A x2 | 2.75 45 |
| 108 | 8 | 4 | 5 8 8-9 x 8-9 x 8-6 | 0-12V at 4A x2 | 4.15 45 |
| 72 | 10 | 5 | 6 4 9-9 x 9-6 x 8-6 | 0-12V at 5A x2 | 4.67 53 |
| 116 | 12 | 6 | 6 12 9-9 x 10-2 x 8-6 | 0-12V at 5A x2 | 5.02 53 |
| 17 | 16 | 8 | 8 12 12-1 x 9-9 x 10-2 | 0-12V at 8A x2 | 6.62 60 |
| 115 | 20 | 10 | 11 8 14-0 x 9-6 x 11-8 | 0-12V at 10A x2 | 12.43 73 |
| 126 | 30 | 15 | 15 8 14-0 x 12-1 x 11-8 | 0-12V at 15A x2 | 12.99 85 |
| 132 | 60 | 30 | 32 0 17-2 x 15-3 x 14-0 | 0-12V at 30A x2 | 15.30 .. |

30 VOLT RANGE

| Ref. No. | Ampr. | Weight lb oz | Size cm. | Secondary Taps | £ P & P |
|----------|-------|--------------|-----------------------|-------------------|---------|
| 112 | 0.5 | 1 | 4 6-1 x 5-8 x 4-8 | 0-12-15-20-24-30V | 1.65 30 |
| 79 | 1.0 | 2 | 4 7-0 x 6-7 x 6-1 | .. | 2.18 38 |
| 3 | 2.0 | 3 | 4 8-9 x 7-7 x 7-7 | .. | 3.18 38 |
| 20 | 3.0 | 4 | 8 9-9 x 8-3 x 8-6 | .. | 4.12 45 |
| 21 | 4.0 | 6 | 4 9-9 x 9-6 x 8-6 | .. | 4.67 53 |
| 51 | 5.0 | 6 | 12 11-8 x 8-6 x 10-2 | .. | 5.83 53 |
| 117 | 6.0 | 8 | 0 12-1 x 9-3 x 10-2 | .. | 6.51 60 |
| 88 | 8.0 | 12 | 0 12-1 x 11-8 x 10-2 | .. | 9.00 67 |
| 89 | 10.0 | 13 | 12 14-0 x 10-2 x 11-8 | .. | 9.97 73 |

50 VOLT RANGE

| Ref. No. | Ampr. | Weight lb oz | Size cm. | Secondary Taps | £ P & P |
|----------|-------|--------------|--------------------|-------------------|---------|
| 102 | 0.5 | 1 | 12 7-0 x 6-4 x 6-1 | 0-19-25-33-40-50V | 2.35 30 |
| 103 | 1.0 | 2 | 12 8-3 x 7-4 x 7-0 | .. | 3.06 38 |
| 104 | 2.0 | 5 | 8 9-9 x 8-9 x 8-6 | .. | 4.26 45 |
| 105 | 3.0 | 6 | 12 9-9 x | | |

Practical Wireless Classified Advertisements

The pre-paid rate for classified advertisements is 12p per word (minimum 12 words), box number 30p extra. Semi-displayed setting £10.00 per single column inch. All cheques, postal orders, etc., to be made payable to PRACTICAL WIRELESS and crossed "Lloyds Bank Ltd." Treasury notes should always be sent registered post. Advertisements, together with remittance, should be sent to the Classified Advertisement Manager, PRACTICAL WIRELESS, IPC Magazines Ltd. Fleetway House, Farringdon Street, London, EC4A 4AD for insertion in the next available issue.

Receivers and Components



CRATA F.M. TUNER

- Pack 1. Resistors **36p**
 2. Capacitors **£1.70**
 3. Semi Conductors **£5.85**
 4. Inductors & filters **£7.00**
 5. Chassis & hardware **£5.00**
 6/7. A.M. Parts **£3.65**

TEXAN 20 + 20W AMP.

- Pack 1. Resistors **80p**
 2/3. Capacitors **£3.65**
 5. Switches **£1.00**
 6. Potentiometers **£1.45**
 7. Semi Conductors **£8.25**
 8. Transformer **£6.95**
 9. Printed Circuit **£2.50**
 10. Chassis **£3.00**
 11. Cables **40p**

V.A.T. EXTRA

add 20p p/p etc. except transformer (35p)

S.A.E. for lists

TERERADIO ELECTRONICS,
 325-7 Fore Street, Edmonton,
 London N9 0PE 01-807-3719
 Closed Thursdays

PW TENNIS KITS. Post free inclusive. Semic conductors, £12.75. So kits £3.50. Order both, £18. Island Devices, PO Box 11, Margate, Kent.

ALLRAD ELECTRONICS

Branded Components—Full Specification

| TRANSISTORS | Price ea. | SCR'S | Price ea. | DIODES | Price ea. |
|-------------|-----------|---------|-----------|--------------|-----------|
| A1125B/178 | 0.13 | CR81100 | 0.30 | LN814/1N4148 | 0.05 |
| A1140/140 | 0.48 | CR81110 | 0.50 | LN4001/8 | 0.08 |
| A1161/162 | 0.35 | CR81120 | 0.60 | | |
| A1143/167 | 0.14 | CR81130 | 0.45 | | |
| AP18 | 0.35 | CR81140 | 0.55 | | |
| BC107/80 | 0.08 | | | | |
| BC147/80 | 0.10 | | | | |
| BC182/104 | 0.10 | | | | |
| BC212/104 | 0.11 | | | | |
| BC107/172 | 0.12 | | | | |
| BC113/132 | 0.35 | | | | |
| BC184/104 | 0.10 | | | | |
| BF550/1163 | 0.10 | | | | |
| BY127 | 0.25 | | | | |
| MJ3570 | 0.62 | | | | |
| MJ3571 | 0.73 | | | | |
| 2N2218 | 0.18 | | | | |
| 2N2906 | 0.13 | | | | |
| 2N2906 all | 0.11 | | | | |
| 2N2907 | 0.15 | | | | |
| 2N3054 | 0.42 | | | | |
| 2N3055 | 0.44 | | | | |
| 2N3702/3/4 | 0.10 | | | | |
| 2N3703/5 | 0.10 | | | | |
| 2N3707/8 | 0.08 | | | | |
| 2N3712 | 0.28 | | | | |
| TL1220 754 | 0.20 | | | | |
| PACK OF | | | | | |
| TEX | 1.75 | | | | |

299/301 BALLARDS LANE

LONDON N11 8NP 01-445-5188

MAIL ORDER ONLY. Cash with order

Orders under £3 plus 15p P & F. Add VAT to total

Precision Polycarbonate Capacitors

All High Stability—Extremely Low Leakage

| 440V AC (±10%) | 50pF | 63V Range | ±1% | ±2% | ±5% |
|-------------------|------|-----------|------|------|------|
| 0.1µF (11" × 1") | 50p | 0.47µF | 50p | 40p | 30p |
| 0.22µF (11" × 1") | 50p | 1.0µF | 60p | 50p | 40p |
| 0.33µF (11" × 1") | 62p | 2.2µF | 80p | 65p | 50p |
| 0.47µF (11" × 1") | 71p | 3.3µF | 100p | 80p | 65p |
| 0.68µF (11" × 1") | 75p | 4.7µF | 130p | 105p | 85p |
| 0.90µF (11" × 1") | 80p | 6.8µF | 160p | 130p | 100p |
| 1.0µF (11" × 1") | 81p | 10.0µF | 200p | 160p | 130p |
| 2.0µF (11" × 1") | 112p | 15.0µF | 250p | 200p | 160p |

TANTALUM BEAD CAPACITORS—Values available: 0.1, 0.22, 0.47, 1.0, 2.2, 4.7, 6.8µF at 15V/25V or 50V; 10.0µF at 10V/20V or 25V; 22.0µF at 5V/10V or 15V; 33.0µF at 4V or 10V/4.7µF at 4V or 5V; 100.0µF at 3V. ALL at 10p each, 10 for 85p, 80 for 44.

TRANSISTORS: BC108/180L 11p BFY50 20p BC107/9 8p BC182/104 11p BFY51 20p BC114 12p BC212/104 14p BFY52 20p BC147/80 10p BC547/58A 12p AF178 30p BC188/178 12p BF154 12p OC71 12p BC182/182L 11p BF197 12p 2N3055 50p

POPULAR DIODES—1N914 8p, 5 for 45p, 18 for 80p; 1N4001 8p, 5 for 45p, 14 for 80p; 1N4002 8p, 5 for 45p, 14 for 80p; 1N4003 8p, 5 for 45p, 14 for 80p; 1N4004 8p, 5 for 45p, 14 for 80p; 1N4287 8p, 5 for 45p, 14 for

BETA DEVICES

FOR BETTER PRICES

| TRANSISTORS | DIODES & RECT. | BRIDGE RECT. |
|------------------|-------------------------|------------------|
| AC189/8 FR 0-40 | 1N914 0-04 | 1A 100v 0-20 |
| BC107/8/9 0-08 | 1N4148 0-04 | 1A 200v 0-22 |
| BC109C 0-11 | BY127 0-14 | 1A 500v 0-30 |
| BC147/8 0-10 | 1N4001/2 0-05 | 25A 200v £2.00 |
| BCV70/71/72/0 13 | 1N4003/4/5 0-06 | ZENERES |
| BFX88 0-20 | 1N4007/7 0-08 | BZY88c 3-3- |
| BFY50 0-18 | 1N5401 0-11 | 23v 5% 0-09 |
| BPY11/52 0-12 | | 1 watt 0-5- |
| 2N1182 0-05 | 7 SEG DISPLAYS | 200v 5% 0-15 |
| 2N1711 0-25 | 3015F £1.00 | L.E.D. |
| 2N2646 0-30 | DL707-LEDE1-70 | 209-RED 0-17 |
| 2N2905A 0-21 | DL747-LEDE2-45 | LED CLIP 0-02 |
| 2N3053 0-14 | | OP. AMP. 10's |
| 2N3056 0-33 | D.I.L. SOCKETS | 70C TO99 0-80 |
| TIP28A 0-49 | | 708C D.I.L. 0-30 |
| TIP30A 0-57 | 14 Pin 0-19 | 741C TO99 0-85 |
| TIP31A 0-81 | 16 Pin 0-34 | 741C D.I.L. 0-36 |
| TIP32A 0-74 | | 728C D.I.L. 0-80 |
| TIP41A 0-74 | V.A.T. INC. | 747C D.I.L. 0-85 |
| TIP42A 0-80 | | 748C D.I.L. 0-80 |
| 7400N 0-16 | 74 SERIES T.T.L. | 7474N 0-37 |
| 7401N 0-18 | 7400N 0-18 | 7400N 0-23 |
| 7402N 0-18 | 7427N 0-28 | 7402N 0-23 |
| 7404N 0-19 | 7400N 0-18 | 7403N 0-22 |
| 7408N 0-22 | 7400N 0-18 | 7412N 0-20 |
| 7410N 0-18 | 7447N £1.00 | 74123N £1-25 |
| 7418N 0-39 | 7472N 0-32 | 74141N £1-13 |

C.W.O. PLUS P.P. 10p TO BETA DEVICES, 26J THE RIDGEWAY, ENFIELD, MIDDX.

MULLARD 10W RMS AMPLIFIER MODULES. Absolutely complete. £2-65 inclusive. LTE, 46 Minehead Road, South Harrow, Middx.

For Sale

COPPER CLAD LAMINATE FOR PRINTED CIRCUITS

Single sided 1/16" paper base—1-0p/sq. inch.
Single sided 1/16" glass-epoxy—1-5p/sq. inch.
Any rectangular sizes cut to your requirements.
Please send cash with order.
Price includes postage and packing.
From: **SIMTECH ENGINEERING LTD**
VOLUNTARY PLACE
WANSTEAD
LONDON E.11. 01-530-4240.

MICROPHONES: AKG D109, £12-65; AKG D202E1, £45-45; AKG D190C, £18-70; AKG D190E, £20; AKG D224 £53; Sennheiser MD211N, £49-50; Sennheiser MD413N, £29-70. All brand new and boxed. Send CWO to J. J. Francis, (Wood Green) Ltd., Manwood House, Matching Green, Harlow, Essex. Tel: Matching 476.

VALVES, VALVES & MORE VALVES. Large stocks 1930-1974, many obsolete. Also available many types of transistors and styls. Price lists available, 15p. Cox Radio, The Parade, East Wittering, Sussex. West Wittering 2023.

SOUND TO LIGHT CONVERTORS 3-channel, 1-5 kW £18, 3 kW £25, single channel £9; Sequencer £93; Strobes from £19; Projectors from £24; etc. Call or mail Aarvak Electronics, 98A West Green Road (Side Door), London N15 5NS. 01-800 8656.

1932 PYE WIRELESS wooden case still in working order no new parts original receipt. Offers Box 121.

HRO nine coils, power pack. Handbook, £50. Tel: 01-437 5281.

MICROPHONES: Two Pioneer DM-3A. Brand new. Unobtainable in Europe. £25 each, £45 the pair. CWO to Highway Associates, Aynho, Banbury, Oxon. Tel. Croughton 750.

Situations Vacant

ELECTRONIC CRAFTSMEN

Is your present job routine and uninteresting ?

We are a research establishment and our craftsmen are engaged on a wide variety of work in the fields of prototype and small batch wiring and assembly, test and inspection, maintenance fault finding and repair. Why not join us and enjoy working in first class conditions in the country.

You can expect gross earnings including overtime of £45 per week, and we can offer good housing at low rental (for applicants who reside outside the radius of our Assisted Travel Area) together with 3 weeks paid holiday with holiday bonus, free pension and excellent sick benefit scheme.

Applicants who should have served a recognised apprenticeship or have had equivalent training together with experience in one of the fields detailed should 'phone Tadley 4111 (STD 073.56.4111) Ext. 5230, or write to:

Industrial Recruitment Officer
(PA/56/PW) Procurement Executive
Ministry of Defence
AWRE Aldermaston
Reading, Berks
RG7 4PR

MEN! £70p.w. can be yours

Jobs galore? Tens of thousands of new computer personnel needed over the next few years alone. With our revolutionary, direct-from-America, course, you train as a Computer Operator in only 4 weeks! Pay prospects? £3500 + p.a.
London Computer Operators Training Centre subscribes to the British Government backed National Computing Centre code of practice for Computer Training Schools so you know your training will be second to none.

After training, our executive appointments bureau—one of the world's leaders of its kind—introduces you FREE to world-wide opportunities. Write or 'phone TODAY, without obligation.

London Computer Operators Training Centre
Y20, Oxford Hse.,
9-15 Oxford St. W.1. Tel: 01-734 2874

RADIO AND AUDIO ENGINEER required for service company. City and Guilds and experience. Will be rewarded with a good salary. Tel: D. Williams. 01-593 4895. B and C Electronic Services Ltd.

RADIO AND AUDIO SUPERVISOR required for young expanding service company. This is a senior position for a man with City and Guilds servicing and experience. The successful applicant shall be responsible for the smooth running of an audio repair section. Good salary and incentives. Tel: D. Williams. 01-593 4895. B and C Electronic Services Ltd.

Educational

TELEVISION TRAINING

16 MONTHS' full-time practical and theoretical training course in Radio and TV Servicing (Mono and Colour) for beginners.

13 WEEKS' full-time Colour TV Servicing course (including Mono revision) for men with a good electronics background.

Next session commences on April 16th.

Prospectus from: **London Electronics College, Department A4, 20 Penywern Road, London SW5 9SU. Tel. 01-373 8721.**

GO TO SEA as a Radio Officer. Write: Principal, Nautical College, Broadwater, Fleetwood FY7 8JZ.

Ladders

LADDERS, timber and aluminium. Tel: Telford 586644 for brochure.

Aerials

GENUINE FULL SIZE
18 element TV aerial
 as used by leading
 TV companies.

FOR ONLY
£2.20
 inc. VAT

+43P CMT



ITV, BBC1, BBC2, BBC4 & Colour Guaranteed Perfect Pictures. Serv. E.E. We supply this genuine I.H.F. aerial for only £2.20, can be fitted outside or inside. Quality made technically advanced design. Precision grid reflector eliminates ghosting. Complete with clamp, instructions advice. Money Back Refund. Wall/Catavan Bracket 25p. Best Cable 12P per yard. Plug 10P & FREE with bracket maps & channel reference of Radio & TV Transmitters. SEND COUPON TO DEPT. PW10 219 Mansfield Rd. Nottingham.

IMPERIAL TRADING (AERIALS) LTD.
 the quality Aerial Specialists

Jaybeam Multibeams
 MBM 28 £3-00, MBM 48 £4-00, MBM 70 £12-00,
 Loopstick LBM 2 £7-00
 Stereobeams
 SBM 3 £5-00, SBM 4 £5-50, SBM 6 £8-00, FM9S
 £19-00,
 UHF Masthead Amplifiers £11-00
 Low Loss co-ax 12p/m
 We stock a good range of AMTRON KITS and
 BIG HI-FI ACCESSORIES.
 The shop has a good range of components and
 is open Tues.-Sat. 0900-1700.
ELECTRONIC SUPPLIES LTD
 78 Chatsworth Road, Chesterfield S40 2AP

Service Sheets

LARGE SUPPLIER OF SERVICE SHEETS

(T.V., RADIO, TAPE RECORDERS,
 RECORD PLAYERS, TRANSISTORS,
 STEREOGRAMS, RADIOGRAMS,
 CAR RADIOS)
 ALL AT 50p EACH

**"PLEASE ENCLOSE LARGE S.A.E
 WITH ALL ENQUIRIES & ORDERS"**

Otherwise cannot be attended to
 (Uncrossed P.O.'s please, original
 returned if service sheets not available.)

PLEASE NOTE

We operate a "by return of post" service. Any
 claims for non-delivery should be made within
 7-days of posting your order.

C. CARANNA

71 BEAUFORT PARK
 LONDON, N.W.11 6BX

We have the largest supplies of Service
 Sheets (strictly by return of post). Please
 state make and model number alternative.

Free TV fault tracing chart or TV list on
 request with order.

Mail order or phone 01-458 4882

SERVICE SHEETS for over 6,000
 models of Televisions, Radios, Transistors,
 Stereo, Tape Recorders, Record
 Players, etc., at only 30p plus SAE
 with free Fault-Finding Guide. Over
 50,000 sheets in stock for 10,000
 models. SAE enquiries. Catalogue 20p
 plus SAE. Hamilton Road, 47 Bohemia
 Road, St. Leonards, Sussex. Telephone
 Hastings 429066.

SERVICE SHEETS. Radio, TV etc.,
 8,000 models. Catalogue 20p. S.A.E.
 enquiries. Telray, 11 Maudland Bank,
 Preston.

BELL'S TELEVISION SERVICES for
 Service Sheets, Manuals, Books on
 Radios, TVs, etc. Service Sheets 40p
 plus s.a.e. Free booklists on request.
 Back issues of PW, PE, EE, TV avail-
 able 25p plus 7p post. S.a.e. with en-
 quiries.—B.T.S. (Mail Order Dept.),
 190 Kings Road, Harrogate, Yorks.
 Telephone (0423) 55885.

Wanted

TOP PRICES PAID for NEW VALVES
 and TRANSISTORS

popular T.V. and Radio types.

KENSINGTON SUPPLIES (C).
 367 Kensington Street, Bradford 8,
 Yorkshire.

WE BUY New Valves, Transistors and
 clean new components, large or small
 quantities, all details, quotation by
 return. **WALTON'S**, 55 Worcester
 Street, Wolverhampton.

EARLY WIRELESS receivers, com-
 ponents and magazines, details to
 Johnson Raffles, Haverbreaks, Lancas-
 ter.

AVO. 7 & 8 any condition. Any quan-
 tity. Huggett's, 2 Pawns Road, W.
 Croydon.

Books and Publications

Technical Books - Radio & Electronics

| | |
|--|-------|
| World's Radio & TV Stations (International Edit) | £0.60 |
| Audio Amplifiers | £0.53 |
| Boys Book of Crystal Sets & Simple Circuits | £0.25 |
| Television Timebase Circuits | £1.00 |
| Radio TV and Industrial Tube & Valve Equip | £0.60 |
| How to get the best out of your Tape Recorder | £1.50 |
| Modern Electronic Troubleshooting | £1.30 |
| Jack Darr's Service Clinic | £1.35 |
| Transistor Circuits for Modern Test Equipment | £0.60 |
| Red & Elect Colour Codes and Data Chart | £0.15 |
| Handbook of Transistor Equiv & Substitutes | £0.40 |
| Hi Fi, PA & Disco Amplifier Design Hdbk. | £0.75 |
| Radio Servicing Problems | £0.60 |
| Electronic Circuits for the Amat Photographer | £0.60 |
| Handbook of Simple Transistor Circuits | £0.35 |
| How to build Solid State Audio Circuits | £1.75 |
| Sound and Loudspeaker Manual | £0.50 |
| TV Technicians Bench Manual | £2.50 |
| Radio Amateur Operator's Handbook | £0.70 |
| Television Servicing Vol. No. 1 | £0.85 |
| Television Servicing Vol. No. 2 | £1.10 |
| Television Servicing Vol. No. 3 | £0.60 |
| Television Servicing Vol. No. 4 | £0.85 |
| Radio Technicians Bench Manual | £3.00 |
| Servicing Transistor Radio Receivers | £0.75 |
| 1st Book of Hi Fi Loudspeaker Enclosures | £0.50 |
| 2nd Book of Hi Fi Loudspeaker Enclosures | £0.60 |
| Manual of Electronic Circuits for the Home | £0.50 |
| Modern Crystal Set Circuits for Beginners | £0.35 |
| Electronic Novelties for the Motorist | £0.50 |
| 2nd Book of Transistor Equiv & Substitutes | £0.95 |
| Handbook of Electronic Musical Novelties | £0.50 |
| Transistorised Novelties for Hi Fi Enthusiast | £0.35 |
| Fault Location Exercises in Rad & TV Vol.1 | £0.80 |
| Fault Location Exercises in Rad & TV Vol.2 | £1.35 |
| Colour TV Picture Faults | £2.50 |
| Practical Transistor Novelty Circuits | £0.40 |
| Boys Book of Practical Radio & Electronics | £0.60 |
| Radio Receiver Construction using ICs & Transis. | £0.50 |
| ICs & Transistor Gadgets Construction Handbk. | £0.50 |
| Integrated Circuits Equiv & Substitutes Hbk. | £0.75 |

FREE! *****
 * A 'Resistor Colour Code Disc Calculator' *
 * (Invaluable to the keen radio constructor!) *
 * OFFERED FREE ON REQUEST FOR ORDERS £3 AND OVER *
 * PLEASE ADD 10% FOR POSTAGE & PACKING *
RADIO BOOK SERVICE
 40 Elwill Way, Beckenhelm BR3 2RZ

Electronics

—an elementary
 introduction
 for beginners
 by L. W. Owers

This new book contains an easy-to-
 understand introduction to the basic
 concepts of electronics including
 radio, t.v., transistors, integrated
 circuits, etc., etc.
 120 pages, softback £1.45 (inc. p. & p.)
 from Publication Mailing Services
 P.O. Box 6, Crawley, Sussex
 RH10 6LH

ELECTRONICS MEN. You are worth
 more than a measly £40 or £50 a week.
 Last year I earned £3,600 for six
 months' work, the other six I had off.
 You could do similar, my booklet
 explains how. It's 65p from Alben, 3
 Church Street, Diss IP22 3DD.

UFO CHARTS: Wave Prediction 54p;
 Daily Flight Pattern, 50p; Map, 50p;
 TV UFO Detection, 2 Optical Circuits,
 63p; Propulsion Theory, 55p; "Anti-
 Gravity" 55p. Circuits: Transistor
 Optical Detector, 66p; Radiation/Optical,
 44p; Microdetectors, memory,
 auto-record, 80p. Sighting Recorder,
 55p. R. & E. Highlands, Needham,
 Suffolk.

Miscellaneous

MINI ACCUMULATORS

2 volt MULTI-USE
 Sealed Lead Acid Re-
 chargeable Cells,
 Size GA50—1.4" x 1.1"
 x .44" 3 for £1.85
 inc. P. & P.
 Size GA2—1.7" x 1.3"
 x .57" 3 for £2.35
 inc. P. & P.
**GARFIELDS, 288 Rye
 Lane, London, S.E.11**

BUILD THE
TREASURE TRACER
MK III Metal Locator

- Varicap tuning
- Britain's best selling metal locator kit
- Weighs only 22oz.
- Speaker and earphone operation
- Knocks down to only 17in.
- Prebuilt search coil assembly
- Ministry approved design
- As seen on BBC1 and BBC2 TV
- You only need soldering iron, screwdriver, pliers and snips
- Five transistor circuit

Sand s.a.e. for leaflet

Complete Kit £9.80 Built, tested and guaranteed £13.75
 P & P 45p + 78p VAT P & P 45p + £1.10 VAT
**MINIKITS ELECTRONICS, 35a LANGLEY DRIVE,
 (Mail Order Only) LONDON E11 2LN**

AUDIOSCAN, the "do-it-yourself"
 speaker mail-order specialists. High
 fidelity speaker kits, chassis units,
 sound absorbent, grille fabric and
 much more. Send 7p in stamps for
 bargain list to: Audioscan, Dept. PW-9,
 4 Princes Square, Harrogate, Yorks.

VALVES. Huge stocks of rare and
 obsolete types. SAE for list. White-
 side's, 35 Central Road, Manchester 20.

FANTASTIC NEW MICROTEST 80

MEASURES
ONLY

90x70x18 mm



Fantastic value at **£11.95**

8 fields of measurement
and 40 ranges

Volts D.C. 6 ranges: 100mV - 2V, - 10V, - 50V, - 200V, - 1000V. (20k Ω/V)

Volts A.C. 5 ranges: 1.5V, - 10V, - 50V, - 250V, - 1000V. (4kΩ/V)

Amp. D.C. 5 ranges: 50μA - 500μA - 5mA - 50mA - 500mA - 5A

Amp. A.C. 5 ranges: 250μA - 2.5mA - 25mA - 250mA - 2.5A

Ohms 4 ranges: Low Ω - Ω x 1 - Ω x 10 - Ω x 100 (da 1/10 of Ω fino a 5 Mega Ω)

V Output 5 ranges: 1.5V, - 10V, - 50V, - 250V, - 1000V

Decibels 5 ranges: + 6dB, + 22dB, + 36dB, + 50dB, + 62dB

Capacity 4 ranges: 25μF - 250μF - 2500μF - 25,000μF




SUPRETESTER 680R ICE
20,000 Ohm per Volt/sensitivity • Fully screened against external magnetic fields • Scale width and small case dimensions (128 x 95 x 32mm) • Accuracy and stability (1% in D.C., 2% in A.C.) of indicated reading • Simplicity and ease of use and readability • Full ranges of accessories • 1000 times overload • Printed circuit board is removable without de-soldering • More ranges than any other meter. Ask for free catalogue **£18.50**

Accessories (extra) available to convert Microtest 80 & Supertester 680R into following: SIGNAL INJECTOR, GAUSS METER, ELECTRONIC VOLT/METER, AMPERCLAMP, TRANSISTOR TESTER, TEMPERATURE PROBE, PHASE SEQUENCE INDICATOR—Send for details.

MORE RANGES FOR LESS MONEY!

AC/DC Multimeter type U4324

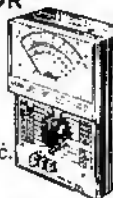A-DC 0-06-3A - 6 Ranges.
A-AC 0-3-3A - 5 Ranges.
V-DC 0-6-1200V - 9 Ranges.
V-AC 3-900V - 8 Ranges.
Freq.: In the range of 45 to 20kHz.
Resistance: 500 Ohm to 5 MΩ
5 Ranges. Decibel: -10 to +12dB.
Accuracy: ± 2.5% DC, ± 4% AC.
Dimensions: 181 x 95 x 63 mm.



Only **£8.85**

ALPHANUMERIC NIXIE TUBES B7971

The Alphnumeric NIXIE tube has the ability to display all the letters of the alphabet, numerals 0 thru 9 and special characters in a single tube. From the standpoint of both readability and electrical characteristics, the Alphnumeric NIXIE tube provides many unique benefits including: 17v-21mA • All d.c. operation • Uniform, continuous line characters of equal height • Memory with simple solid state drive circuits • Readability in high ambient light... 200 lumen/berts brightness • Long life with no loss of brightness • Character height 2 1/2 in.

Price only **99p** each plus 16p P/P.
Bases for above 60p each.

JUST ARRIVED!!

NUMERIC INDICATOR TUBES

Ultra-long life, high quality, 0-9 and 2 independent decimal points. Supply voltage 200V D.C. Current 14mA. Pulse duration 100μs. Character height 0-51, overall size 1 1/4". Brand new, guaranteed. Surplus to manufacturer's requirements. Type B5853st
1-25 £1.00 25+ 90p 100+ 80p

1000+ price on application
Add 8% VAT to all items + 35p P & P

ELECTRONIC BROKERS LTD.
49-53 Pancras Road, London NW1 2QB
Tel: 01-837 7781

12 VOLT 21" 13 Watt Fluorescent Lighting
(by Thorn/AE) with diffuser & on/off switch. Ideal caravan, boat, emergency lighting, etc. Guaranteed.



£5.50 inc. VAT & Post. List price £7.02 inc. VAT
SALOP ELECTRONICS 21 Wyle Cop,
Shrewsbury, Shropshire Tel. 53204

HEADPHONES: 8 ohms. Suitable communications receivers, £3-39. Partridge Electronics Ltd., Broadstairs, Kent.

BUILD THE STEREO FM TUNER

P.W. SANDOWN LOOK

- PCB & Cmpnts Inc. TR & BOX _ £26.32
- Push Button Unit. 6 Position _ £ 2.97
- METERS, Tuning & Level _ each £ 1.50
- Subminiature Switches _ set of 4 £ 2.62
- Cabinets & Front Panels _ _ to order
- VAT INCLUSIVE PRICES P & P 25p

S.A.E. for further details

P.W. ELECTRONICS, 40 TUDENHAM RD,
IPSWICH, SUFFOLK IP4 2SL. Mail Order only

HARDWARE. Comprehensive range of screws, nuts, washers, etc. in small quantities, and many useful Constructors' items. Sheet aluminium to individual requirements, punched, drilled, etc. Fascia panels, dials, nameplates in etched aluminium. Printed circuit boards for this magazine and other individual requirements, one-offs and small runs. Machine engraving in metals and plastics, contour milling. Send 2 x 4 1/2p stamps for catalogue. Ramar Constructor Services, Masons Road, Stratford on Avon, Warwicks., CV37 9NF.

FLUORESCENT LIGHT KIT

12v
8w

You can build this superbly priced light for use in homes, garages, workshops, for example, or emergency lighting. Everything is supplied, the tube, whole assembled equipment, first quality components, P.C.B.s, instructions, etc.

Price only **£3-19** inc. VAT
Ready built **£3-78** POST & packing
Diffuser only 59p extra

ALUMINIUM BOXES

Prices include tax, VAT, and P & P.
Post and packing 30p extra on all orders.

| | | | | | | | |
|----|----|----|----|--------|--------|------|-----|
| 7 | 6" | 6" | 6" | 2 1/2" | 1 1/2" | hull | 29p |
| 8 | 6" | 6" | 6" | 2 1/2" | 1 1/2" | hull | 29p |
| 9 | 6" | 6" | 6" | 2 1/2" | 1 1/2" | hull | 29p |
| 10 | 6" | 6" | 6" | 2 1/2" | 1 1/2" | hull | 29p |
| 11 | 6" | 6" | 6" | 2 1/2" | 1 1/2" | hull | 29p |
| 12 | 6" | 6" | 6" | 2 1/2" | 1 1/2" | hull | 29p |
| 13 | 6" | 6" | 6" | 2 1/2" | 1 1/2" | hull | 29p |
| 14 | 6" | 6" | 6" | 2 1/2" | 1 1/2" | hull | 29p |
| 15 | 6" | 6" | 6" | 2 1/2" | 1 1/2" | hull | 29p |

Order info to —

ELECTRONICS DESIGN ASSOCIATES
DEPT. PW
82 Bath St., Walsall, WS1 3DE. Phone 33692

DON'T LOOK

unless you can resist the temptation to get these super 'attention-getters':

★ Pocket-sized **MAXI-VOLT** Big 1/2 inch Spark Generator (instant 15,000 volts!). Ready-made, needs no batteries. Carry it around anywhere. Only weighs about 3 oz. (89g.) send **£1.90** for your Maxi-Volt now!

★ Unique **TRANSMITTER/RECEIVER** Kit. No licence examinations or tests required to operate this transistorised equipment. Easy to build. Get transmitting. Send **£6.90** for yours now!

★ Psychedelic **MINI-STROBE** Kit. Take a pocket-sized lightning storm to Disco's & parties. 'Brain-freeze' 'em with vari-speed stop-motion flashes. Includes super case too. Send **£2.90** now!
(all prices include V.A.T., packing & postage.)

Send remittance to:

BOFFIN PROJECTS,
4 CUNLIFF ROAD,
STONELEIGH, EWELL, SURREY
(Mail order U.K. only)
Or for more details, send 20p for lists

HAVE YOU HAD YOUR CHIPS?
AY-5-1224 Digital Clock chip now **£3.95** inc. VAT, post free. Circuit and details s.a.c. **GREENBANK ELECTRONICS** (Dept. 322), 94 New Chester Road, Wirral, Merseyside L62 5AG.

Synthesiser "Sounds Supreme"

by **Dewtron** (VA extra.)

Famous kits, e.g. waa-waa complete kit **£3.50**; Fuzz kit **£5.50**. P & P 25p under **£10**. Ring Modulator modules **£3**. "Mister Bassman" Bass Pedal Units and whole range of synthesiser modules, musical novelties, etc. Catalogue 15p from **D.E.W. Ltd.**, 254 Ringwood Road, Ferndown, Dorset.

PRINTED CIRCUIT BOARDS. PCB from your patterns **£1** plus 5p per square inch. From published patterns in this magazine 50p per board. Add VAT, 5p p&p per PCB. Mail order only, T.E.C. 241 Burnt-oak Broadway, Middlesex.

**SIMPLE TO FORM
NON-MAGNETIC RUST PROOF
MILL FINISH**

ALUMINIUM

FLAT MINI SHEETS

10ins. x 14ins. 20 swg (0.90mm.)

6 sheets for £2 incl P&P

OTHER SIZES AVAILABLE

For general car repairs,
trims, kick plates, etc.

**BAYKIN
ENGINEERING LTD.**
GREVILLE ROAD, BEDMINSTER,
BRISTOL, BS3 1LL

LOW COST I.C. MOUNTING. Lengths of 100 I.C. pin sockets, 60p (p & p 5p). Quantity rates, SAE details & sample. L.E.D. (MLED500), 20p each. (post paid). P.K.G. Electronics, "Oak Lodge", Tansley, Derbyshire.

INTRODUCING our **NEW PEAK** reading V.U. Meter system which offers a high standard of monitoring at reasonable cost. Full details on above and our range of **AUDIO MIXERS** and sub-assemblies available in kit form or fully assembled ready to use.

Consult:—

PARTRIDGE ELECTRONICS

Ref. P.W.

21-25 Hart Road, Benfleet
Essex. Established 23 years.

PRINTED CIRCUIT MANUFACTURERS OFFER. PCBs for All PE and PW projects published after June '74, at one price, 70p each. Any 5, £2.85. PCB sets for: PW Tele-tennis, £3.50. Sandown Tuner with screens, £2.20. PE CCTV, £1.45. Power Slaves, £1.55; Scorpio Ignition, 'WW' Ferret Metal Locator, 65p each. CWO Prices inclusive. **PRODUCTION SPACE AVAILABLE FOR:** PCB production, PCB and electronic design, electroplating, silk-screening, roller tinning, photography and all artwork. Estimates by return post or phone. WKF Electronics Wellbeck Street, Whitwell, Worksop, Notts. Tel: 695.

AERIAL WIRE. High quality PVC covered multi-strand copper, 50ft 60p (10p); 75ft 87p (13p); 100ft £1.20 (15p); 150ft £1.80 (24p); 200ft £2.39 (26p); 250ft £2.96 (28p); 300ft £3.54 (31p). P & P in brackets. Longer lengths available. SAE all enquiries. Al Radio Components, 14 The Borough, Canterbury, Kent CT1 2DR.

FIBRE OPTIC SUPPLIERS

We stock a wide range of Fibre Optic products—glass and plastic light conduit, plastic mono-fibre, Male's Tails (decorative effects) and accessories—plus lasers, retroreflectors, red/yellow/green/infrared emitting diodes, photo-detectors, polarising filters, ultrasonic transducers.

Send S.A.E. for short form list to:—
FIBRE OPTIC SUPPLIERS (PW)
P.O. Box 702, London W10 6SL.

ANTIQUÉ WIRELESS ENTHUSIASTS. For all your requirements in radio, pre-1945, contact Tudor Rees's Antiqué Wireless Service. Retail shop now open at 64 Broad Street, Staple Hill, Bristol. Tel: 0272 565472.

SUPERB INSTRUMENT CASE by Bazelli, manufactured from heavy duty PVC faced steel. Hundreds of Radio, Electronics and Hi-Fi enthusiasts are choosing the case they require from our range of over 200 models. Generous trade discount. Fast despatch. Free literature, Bazelli, Department No. 25, St. Wilfrids, Foundry Lane, Halton, Lancaster LA2 6LT.

LOWEST COST IC SOCKETS. Use Soldercon IC socket pins for 8 to 40 pin DILs. Make 8 pin sockets for 4p, 14 pin for 7p (at 300 pin price). In strips of 100 pins: 100+ pins 70p, 300+ 50p, 1,000+ 40p. Instructions supplied. 10p P&P for orders under £2. Add 8% VAT. Send SAE for sample. Sintel, 53n Aston Street, Oxford. Tel: 0865 43203.

AERIAL BOOSTERS £3-30

We make three types of Aerial Boosters: 845-UHF 62S, B12-VHF 40S, B11-VHF. RADIO

VALVE BARGAINS

Any 5—50p, 10—75p, 50—£1.30:—
ECC82, ECL80, EB91, EB789, EF80, EF85, EF183, EF184, EY86, PCC84, PCC89, PCC189, PC97, PCF80, PCF86, PCF805, PCF808, PCL62, PCL83, PCL84, PCL85, PFL200, PL36, PL81, PL504, PY33, PY82, PY800, PY801, 30L15, EH90, P 88, PC86.

TV COLOUR VALVES

PL508, PL509, PY5001A, 25p EACH.
Press Button U.H.F. Tuners—£2.50.
Rotary U.H.F. Tuners—£2.00.

PLUG SOCKETS (Price per item, in brackets for ten)

CO-AX PLUGS 6p (50p) Socket surface 7p (60), Connectors 4p (35p).

D.I.N. PLUGS. 2 pin, 3 pin and 5 pin 20p (£1.65).

JACK PLUGS. Standard 18p (£1.50), 3.5 mm 10p (80p), 2.5 mm 10p (80p).

All prices include V.A.T. P. and p, 10p per order. Money back refund. S.A.E. for leaflet.

ELECTRONIC MAILORDER (BURY) LTD.
62 Bridge Street, Ramsbottom, Bury,
Lancs. Tel: Rams. 3836

TRANSISTORS (p. & p. 10p.)

All new and full spec.

BC107/8/9, BC147/8/9, BC157/8/9 all 9p
BF180 25p, BF182/3 40p, BF184 17p,
BF187 13p, BFW10 55p, 741 8DIL 34p,
BF336 35p, 2N3771 £1.10, 2N3441 50p,
BD131 40p.

EX COMPUTER PC PANELS

4 x 2in packed with semiconductors and top quality resistors, capacitors, diodes etc. Guaranteed min. 35 transistors, plus data 25 boards £1 (30p)

DURAL EXTRUDED HEATSINKS, 10D outline, black anodised, drilled for 4 x TO3 transistors 5 x 4 x 1 1/4 40p (15p) Sim. to above but for 8 x TO3 5 x 8 x 1 1/4 70p (27p)

ELECTROLYTICS

| | |
|-------------------------------|-----------|
| 15,000µ 30v, 68,000µ 16v | 65p (22p) |
| 30,000µ 25v | 65p (22p) |
| 4,000µ 70v, 3,800µ 40v 4 x 2" | 55p (15p) |
| 5,000µ 35v | 40p (12p) |
| 20A 100 pV SI recs. 4 for | £1 (12p) |
| 3A 100 pV SI recs 4 for | 50p (8p) |
| 250 mixed resistors | 60p (13p) |
| 250 mixed capacitors | 60p (11p) |
| 150 mixed HI-STABS | 60p (11p) |
| 200 SI planar diodes | 60p (8p) |
| QH bulbs 12v 55w | 50p (7p) |
| 2N3055 EQUIV 4 for | £1 (10p) |


Postage and packing shown in brackets
ADD 8% VAT TO TOTAL

KEYTRONICS

(Mail Order only)

44 EARLS COURT ROAD
LONDON W8. 01-478 8499

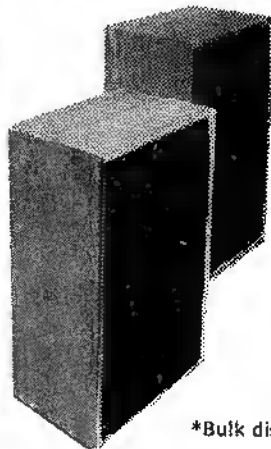Quality Loudspeaker Systems less than half price



Direct from manufacturer as supplied by us to the trade.

Finished in natural Teak veneer 15 watt 8ohm bass reflex speaker system containing Goodmans 8" bass and H.F. tweeter.

Frequency response 50 Hz - 19000 Hz. Complete with leads and DIN plug. Cabinet size 17" x 10" x 7" deep.

Price only £16.00/pair including VAT plus £1.90 packing, carriage and insurance (U.K. mainland).

Please send cash with order direct to: Forward Marketing, 30 Ridgeway, Stanground, Peterborough.

*Bulk discounts available for trade enquiries.

NEW YEAR BONANZA!

B.B. SUPPLIES offer:-
LEVER key switch, 4-pole, lock-off-lock, in black plastic stackable case app. 120mm x 120mm x 25mm. Brand new. **75p**
PUSH button switching unit, 3 two-pole c/o units, one cancel others, room for one more unit. App. 75mm x 60mm x 35mm. Brand new (wired and numbered) **80p**
RELAY, 24 volt, 3000 ohms, 4 c/o contacts. Size: 40mm x 35mm x 15mm (wired and covered). Brand new **60p**
LAMP fitting, 5 volt-contained in hammer finished, grey steel box on wood pinth. Ideal case for small projects. Size app. 75mm x 75mm x 70mm. Brand new **50p**
SPECIAL price until 31-3-75 for all 4 above items + useful accessory. **£2.90**
4T S energising arspices (salvaged) **25p**
 All prices include VAT and p. & p. Many other Govt. surplus, new and hand items at bargain prices. S.A.E. for New Year Catalogue of electronic parts to:
34 HEATHWOOD GARDENS, SWANLEY KENT BR1 7HN

If you have difficulty in obtaining

PRACTICAL WIRELESS

Please place a regular order with your newsagent or send 1 year's subscription (£3.25) to:-

Subscription Department,
 Practical Wireless,
 Tower House, Southampton Street,
 London, WC2E 9QX

WATFORD ELECTRONICS

35 CARDIFF ROAD, WATFORD, HERTS, ENGLAND
 MAIL ORDER. CALLERS SATURDAYS ONLY

C.W.O. Please P. & P. add 15p to orders under £3. Prices exclusive of VAT

All components brand new and fully guaranteed

| TRANSISTORS (less 10% for 25+ of one type) | | TTL 74 SERIES | |
|--|------------|---------------|-------------|
| AC107 10p | BC102 11p | OC38 12p | ZTX350 11p |
| AC125 13p | BC133 11p | OC41 35p | 2N706 11p |
| AC138 13p | BC184 11p | OC42 35p | 2N708 11p |
| AC127 13p | BC212 13p | OC44 12p | 2N131 20p |
| AC128 13p | BC213 13p | OC45 12p | 2N132 20p |
| AC175 14p | BC214 13p | OC70 12p | 2N130 20p |
| AC187 13p | BCY39 80p | OC71 12p | 2N1302 20p |
| AC188 13p | BCY40 80p | OC72 12p | 2N1303 20p |
| AC177 35p | BCY42 25p | OC74 20p | 2N1304 24p |
| ACY10 25p | BCY43 25p | OC78 12p | 2N1305 24p |
| ACY20 24p | BCY58 18p | OC82 15p | 2N1306 24p |
| ACY21 24p | BCY59 18p | OC83 20p | 2N1307 24p |
| ACY22 18p | BCY70 15p | OC140 105p | 2N1893 30p |
| AD140 48p | BCY71 18p | OC201 70p | 2N1990 45p |
| AD149 48p | BCY72 12p | OC202 80p | 2N211 23p |
| AD181 35p | BD131 40p | TIP29 43p | 2N2303 25p |
| AD182 35p | BD132 40p | TIP29A 43p | 2N2483 35p |
| AF114 14p | BD133 40p | TIP30 48p | 2N2894 30p |
| AF115 14p | BD145 35p | TIP30A 54p | 2N2905 15p |
| AF116 14p | BDY11 115p | TIP31 48p | 2N2907 15p |
| AF117 14p | BDY17 135p | TIP32 64p | 2N2926 9p |
| AF118 40p | BDY18 125p | TIP33 93p | 2N3053 18p |
| AF121 35p | BDY19 195p | TIP34 130p | 2N3054 42p |
| AF124 32p | BDY81 50p | TIP41 85p | 2N3055 45p |
| AF125 32p | BF194 10p | TIP41A 85p | 2N3814 85p |
| AF126 32p | BF195 10p | TIP42 70p | 2N3816 85p |
| AF127 32p | BF196 12p | TIP42A 74p | 2N3702 52p |
| AF128 32p | BF197 12p | TIS43 28p | 2N3703 12p |
| AF129 32p | BF198 12p | TIS44 17p | 2N3704 12p |
| AF188 50p | BFX84 24p | TIS45 50p | 2N3705 12p |
| AF239 38p | BFX85 24p | TIS46 20p | 2N3706 12p |
| BC107 8p | BFX88 28p | TIS48 20p | 2N3707 12p |
| BC108 8p | BFY50 16p | TIS60 16p | 2N3708 8p |
| BC109 8p | BFY51 16p | TIS61 19p | 2N3709 8p |
| BC147 10p | BFY52 16p | TIS62 28p | 2N3713 120p |
| BC148 10p | BFY53 17p | TIS63 28p | 2N3715 120p |
| BC149 10p | BFY54 17p | TIS64 28p | 2N3716 120p |
| BC157 13p | BFX39 35p | ZTX107 10p | 2N3717 150p |
| BC158 11p | BFX30 30p | ZTX108 10p | 2N3711 140p |
| BC159 13p | MJE370 65p | ZTX109 12p | 2N3712 160p |
| BC167 12p | MJE371 78p | ZTX300 12p | 2N3713 240p |
| BC168 12p | MJE372 82p | ZTX301 14p | 2N3819 20p |
| BC169 12p | MPE102 30p | ZTX302 18p | 2N3820 8p |
| BC170 11p | MPE103 30p | ZTX303 22p | 2N3823 8p |
| BC171 11p | MPE104 28p | ZTX304 18p | 2N3903 15p |
| BC172 11p | MPE105 36p | ZTX500 15p | 2N3905 17p |
| BC177 10p | OC28 40p | ZTX502 18p | 2N3906 17p |
| BC178 10p | OC28 50p | ZTX504 42p | 2N4037 35p |
| BC179 10p | OC35 48p | ZTX501 23p | 2N4082 12p |

| LINEAR IC'S | DIODES | BRIDGE RECTIFIERS | TRIACS |
|--------------------|--------------------|-------------------|---------------|
| 709C DIL/T099 32p | MC1304P 160p | AA120 10p | 400V 3A 85p |
| 723C DIL/T099 70p | MC1710CG 275p | BY100 8p | 500V 3A 120p |
| 741C 8pin DIL 30p | NE525 85p | BY140 35p | 500V 6A 150p |
| 10 14pin DIL | NE525 FM 53p | BY211 25p | 20p 100A 145p |
| T099 38p | PA263 150p | OA5 38p | 500V 10A 140p |
| 747C 14pin DIL 75p | PA283 445p | OA9 9p | DIAC 5T2 25p |
| 748C 8pin DIL 35p | LA6032 150p | OA78 19p | ZENER |
| 4L910 35p | LA6032 150p | OA81 6p | DIODES |
| 7805 (T03) 1.40 | TAD100 AM 150p | OA85 10p | 3.3V-330V |
| CA3015 140p | TZA300 135p | OA90 6p | 400mV 9p |
| CA3035 135p | ZN414 116p | OA91 6p | 1-3W 17p |
| CA3038 80p | Less 15% 15 + mix | DA200 8p | ALUM. BOXES |
| CA3048 70p | OPTO ELECTRONICS | QA201 6p | 22x31x1 45p |
| CA3058 210p | Min/Rev 3015P | PL4001 6p | 4x4x1 45p |
| CA3062 135p | LED display 118p | PL4004 8p | 4x2x1 45p |
| CA3081 150p | OCPT70 40p | PL4007 12p | 4x5x1 48p |
| CA3089E 195p | OCPT71 65p | PL4010 12p | 4x2x2 50p |
| CA3090G 345p | ORP21 58p | IN914 5p | 3x2x1 38p |
| LM3090 T099 170p | ORP61 45p | IN4001/2 5p | 7x5x2 78p |
| LM304 T099 170p | ORP60 45p | IN4003 6p | 3A 100V 45p |
| LM305 T099 170p | LED TIL 208p (Red) | IN4004/5 6p | 3A 100V 75p |
| MC724P 50p | with cut | IN4005/7 7p | 10x7x3 118p |
| MC7303L 130p | 2N5777 49p | 1N4148 5p | 10x4x3 99p |
| | | | 12x3x3 125p |
| | | | 12x8x3 150p |

POLYESTER CAPACITORS: Axial lead type. (Values are in μ F).
 40V: 0-001, 0-0012, 0-0015, 0-0018, 0-0022, 0-0033, 21p; 0-0047, 0-0068, 0-01, 0-015, 0-022, 3p; 0-047, 0-068, 0-1, 4p; 0-15, 0-22, 7p; 0-33, 10p; 0-47 13p; 100V: 0-1, 0-15, 4p; 0-22 5p; 0-33 6p; 0-47 8p; 0-68 10p; 1-0 13p. 250V: 0-22 6p; 0-33 8p; 0-68 12p; 0-47 1p; 2-2 11p.

RADIAL LEAD P.C. TYPE (Values are in μ F).
 250V: 0-01, 0-015, 0-022, 3p; 0-033, 0-047, 0-068 3p; 0-1 4p; 0-15 4p; 0-22, 0-33 5p; 0-47 7p; 0-68 10p; 1-0 11p; 1-5 20p; 2-2 22p.

ELECTROLYTIC CAPACITORS: Axial lead type (Values are in μ F)
 63V: 1-0, 1.5, 2-2, 3-3, 4, 4-7, 6-8, 10, 15, 20, 22, 47, 68 μ each, 100 12p. 40V: 100, 6p. 30V: 3500, 35p. 25V: 88, 6p; 150, 6p; 220, 11p; 470, 13p. 25V: 680, 18p; 1000, 24p; 2200, 34p; 3000, 38p. 16V: 40, 125, 250, 8p. 18V: 1000, 1500, 18p. 10V: 4, 100 5p; 640, 10p; 1000, 14p; 2200, 18p.

CERAMIC CAPACITORS
 50V d.c. Plequette body 25mm leads.
 Range: 5p-10,000pf price 2p each.
 0-015 μ F, 0-022 μ F, 0-033 μ F, 0-047 μ F 3p

POTENTIOMETERS (AB) Carbon
 Track, 0-25W Log & 0-5W Linear values
 1K Ω -2M Ω single gang 14p
 5K Ω -2M Ω single gang D/P switch 28p
 2K Ω -2M Ω dual gang stereo 42p

SLIDER POTENTIOMETERS
 0-25W log and linear values
 5K Ω -500K Ω single gang 35p
 10K-500Kohm Dual gang 50p
KNobs for above Black or Silvered 8p

MYLAR FILM CAPACITORS
 100V: 0-001 μ F, 0-002 μ F, 0-005 μ F, 3p.
 0-01 μ F, 0-015 μ F, 0-02 μ F, 0-04 μ F, 0-05 μ F 4p.
 0-1 μ F, 0-15 μ F, 0-2 μ F. 30V: 0-47 μ F 6p.

PRESET POTENTIOMETERS
 0-25W: 100 Ω -1M Horizontal 6p
 1K-1M Vertical 4p
 0-1W: 50 Ω -1M Vertical 6p

RESISTORS High Stability Low noise
 Type C Tol. Range Val. 1-49 50+
 1W C 5% 2-20-10M E24 8p -5p
 1W C 5% 2-20-10M E12 1p -5p
 1W C 5% 2-20-10M E12 2-5p 2p
 1W WW 10% 1 Ω -100 Ω E12 8p -

| JACK PLUGS | SOCKETS | | PANEL METERS |
|---------------------|-----------------|-----------------------------|--|
| | Screened chrome | Open metal | |
| 2-5mm 10p | 4p | Moulded with break contacts | Size 2 1/2" x 1 1/2" requires 1 1/2" diam. hole. |
| 3-5mm 14p | 4p | | ME5-50 μ A |
| Standard mono 17p | 13p | | ME7-100 μ A |
| Standard stereo 30p | 13p | | ME8-500 μ A |
| | 18p | | ME9-1m/A |
| | | | ME10-5m/A |

| DIN | PLUGS | SCKTS. | INLINE SCKTS. | OIL SOCKETS LOW PROFILE |
|-------------------------------|-------|------------------------|---------------|-------------------------|
| 2, 3, 4, 5 (180°, 240°) 6 pin | 12p | 6p | 15p | 6 Pin 14p |
| CO-AXIAL (TV) | 10p | 6p | 13p (I.I.) | 14 Pin 15p |
| PHONO assorted colours | 8p | 5p (spl.) 10p (I.I.P.) | 8p | 15 Pin 16p |
| BANANA 8p | 5p | - | - | ME11-10m/A |
| | | | | ME12-80m/A |
| | | | | ME13-100m/A |
| | | | | ME14-500m/A |
| | | | | ME15-1 AMP |
| | | | | ME15-30V AC |
| | | | | ME17-300V AC |
| | | | | ME18-"S" METER |
| | | | | ME19-"VU" METER |

| TOGGLE: SPST | DPDT | PUSH BUTTON: Miniature push to make or break nonlocking |
|----------------------|---------------|--|
| 18p | 22p | 15p |
| SUB-MINIATURE TOGGLE | SP changeover | ROCKER (white): 5A 250V SP changeover |
| 35p | 35p | 25p |
| SPST on/off | DPDT | ROCKER SWITCH (White) 3A 250V Illuminated neon switch |
| 84p | 19p | 50p |
| SLIDE: 1A DP 250V | 1A DP 250V | ROTARY WAFER: 1 pole/12 way, 2p/6w, 2p/2w, 2p/4w, 3p/2w, 3p/4w, 4p/2w, 4p/3w |
| 8p | 8p | 24p |

| TRANSFORMERS | Mains | LAMP HOLDERS/LAMPS |
|-------------------|------------|--|
| Primary 220V-240V | 100mA 90p | LES HOLDERS Dome top, Red, Blue, Green/Yellow/White, 1" hole 14p |
| 6-0-6 (miniature) | 100mA 80p | Les Bulbs 6v and 12v 8p |
| 6-0-9 " | 100mA 80p | MES HOLDER, Heavy duty, round top Red and Amber requires 1 1/2" hole 25p |
| 12-0-12 " | 100mA 80p | NEON, 240V Red round top 1 1/2" hole 25p |
| 18-0-18 also 24V | 100mA 80p | NEON, A as above but with 1" square Red or Green top 25p |
| 24-0-24 | 500mA 220p | LAMPS LES 6v, 12v, MES 3-5v, 24v All 6p each |
| 30-24-20-15-12-0 | 1A 230p | |
| 5-0 | 2A 110p | |

| VEROBOARD | Pitch (copper clad) | 0-15 (plate) | 0-15 (plate) |
|--------------------|---------------------|--------------|--------------|
| 2 1/2x3 1/2" | 30p | 23p | 14p |
| 2 1/2x3" | 32p | 32p | 15p |
| 3 1/2x3" | 35p | 32p | 15p |
| 3 1/2x2 1/2" | 38p | 38p | 25p |
| 2 1/2x1 1/2" | 88p | 75p | 55p |
| 3 1/2x1 1/2" | 130p | 105p | 75p |
| 4 1/2x1 1/2" | 173p | - | 105p |
| Pin of 35 pins | 20p | | |
| Spot face cutter | 49p | | |
| Pin insertion tool | 69p | | |

TWO NEW ADDITIONS TO FANE 'POP' RANGE LOUDSPEAKERS

POP 70 15" 70 Watt

Impedance
8 ohms or
15 ohms
Gauss 17,000
Voice Coil
Diam. 2"
70 watt RMS
Range
45-8,000 Hz



£19.95 Rec. Retail Price inc. VAT

Also for those who can
afford the very best
For Instrument Reproduction

Two Super Sensitive Models
CRESCENDO '12' B
Ideal for Lead Guitar etc.
12" 75 Watt 2" Pole Diam. Gauss 20,000
CRESCENDO '15/100A'
General Purpose
15" 100 Watt 2" Pole Diam. Gauss 20,000



Rec. Retail Price
£39.95 CRESCENDO '12' B
£46.59 CRESCENDO '15/100A'

There is also a 12" Crescendo
Speaker for General Purpose
Public Address, and a 12" and 15"
for Bass Guitar etc.

Please send S.A.E. for leaflet on HORN
UNITS & 'POP' or 'CRESCENDO' Range
of Loudspeakers

POP 55 12" 60 Watt

Impedance
8-15 ohms
Gauss 15,000
Voice Coil
Diam. 2"
Range 50-9,000 Hz
AN ALL PURPOSE
UNIT OF HIGH
SENSITIVITY
Rec. Retail Price
inc. VAT



£15.99

BRIEF DETAILS OF 'POP' RANGE
NOW AVAILABLE IN 8 ohms or 15
ohms

| | | | Rec. Retail |
|-----------|-----|------------|-------------|
| POP '15' | 12" | 15 Watt | £6.30 |
| | 1" | Voice Coil | inc. VAT |
| POP '25T' | 12" | 25 Watt | £8.99 |
| | 1" | Voice Coil | inc. VAT |
| POP '50' | 12" | 50 Watt | £12.95 |
| | 2" | Voice Coil | inc. VAT |
| POP '60' | 15" | 60 Watt | £16.95 |
| | 2" | Voice Coil | inc. VAT |
| POP '100' | 18" | 100 Watt | £31.00 |
| | 3" | Voice Coil | inc. VAT |

HIGH FREQUENCY HORN UNITS

MODEL 910
Rating 50
watts with
recommended
filter

£15.95 inc. VAT
MODEL 920 Mk II (as illust.)
SIGNIFICANTLY
INCREASED SENSITIVITY.
UNCHANGED PRICE. Rating with
recommended filter
100 watts
£39.95 inc. VAT
Filters for either model available if required



Distributors to Wholesale and Retail Traders—**LINEAR PRODUCTS LTD., ELECTRON WORKS, ARMLEY, LEEDS.**
Manufacturers enquiries to—**FANE ACOUSTICS LTD., 286 BRADFORD ROAD, BATLEY, YORKS**
Prices shown correct at Dec 11, 1974

INDEX TO ADVERTISERS

A.H. Supplies ... 874
Allard Electronics ... 957
Ambic International ... 953
Arbour Electronics ... 953
A.S.P. Ltd. ... 880

B.B. Supplies ... 962
Barrie Electronics ... 956
Baykin Engineering Ltd. ... 960
Bentley Acoustics ... 940
Beta Devices ... 958
B.H. Component Factors Ltd. ... 951
Bi-Pak Semiconductors ... 888-889
Bi-Pre-Pak Ltd. ... 943, 954
Bib Hi-Fi Accessories Ltd. ... 912
Boffin Projects ... 960
Bochwell ... 908
British Institute of Engineering
Technology ... 872, 948, cover iii
British National Radio & Electronics
School ... 911, 940, 952
J. Bull (Electrical) Ltd. ... 936
Bywood ... 885

C. Caranna ... 959
Chiltmead Ltd. ... 872
Chromasonic Electronics
C.J.L. Ltd. ... 908
Codar ... 886
Colomor (Electronics) Ltd. ... 950
Crescent Radio Ltd. ... 873
Crofton Electronics ... 886
C.T. Electronics ... 935
Custom Cabinets ... 885

Dabar Electronic Products
D.E.W. Ltd. ... 948, 954
Doram Electronics Ltd. ... 960
Doram Electronics Ltd. ... 903

Electronics Brokers ... 960
Electronic Design Associates ... 884, 960
Electronic Mail Order Ltd. ... 961
Electronic Supplies Ltd. ... 959

Electrospares ... 944
Electro-Tech ... 952
Electrovalue Ltd. ... 887
Elvins ... 954

Folstead Electronics ... 880
Fibre Optics Supplies ... 960
F.W. Electronics ... 960

Galleon Trading ... 957
Garfields ... 959
Goldring ... 908
Greenweld Electronics ... 948
Group Three ... 961

H.A.C. (Shortwave) Products ... 953
Harverson Surplus Co. Ltd. ... 939
Heath (Gloucester) Ltd. ... 899
Henry's Radio Ltd. ... cover iv

I.L.P. (Electronics) Ltd. ... 879
Imperial Trading ... 959
Integrex Ltd. ... 884
Intertext (I.C.S.) ... 884

Jones J. C. ... 957

Kensington Supplies ... 959
Keytronics ... 961

Laskys ... 875, 876, 877
Lewis Radio ... 874
Linear Products Ltd. ... 963
Logic Leisure Ltd. ... 878
London Computer Operators Training
Centre ... 958
London Electronics College ... 958

Maplin Electronic Supplies ... 949
Marco Trading ... 957
Marshall, A. ... 956
Milward, G. F. ... 912
Minikits Electronics ... 959
Ministry of Defence ... 958

Newmart Electronics ... 900
Newnes-Butterworths ... 872

Partridge Electronics Ltd. ... 878, 961
Phoenix ... 884
Publication Mailing Services ... 959

Radio Book Services ... 959
Radio Components Specialists ... 946, 947
Radio Exchange Ltd. ... cover ii
R.C.S. Products Ltd. ... 886
R.D.I. ... 957
R.S.C. (Hi-Fi) Centre Ltd. ... 870-871
R.S.T. Valve Mail Order Co. ... 881
R. & T.V. Components Ltd. ... 882-883
Rivlin Instruments Ltd. ... 874
Riversdale Electronics ... 944

Salop Electronics ... 960
Saxon Entertainments Ltd. ... 907
Simtech Engineering Ltd. ... 958
Sound Systems of Suffolk ... 957
Strong Electronics Ltd. ... 951
Studio Electronics ... 951
Suprelectronics ... 904
Swanley Electronics ... 953

Technomatic Ltd. ... 878
Teleradio ... 957
Trampus Electronics Ltd. ... 964

Ulton Components ... 952

Vero Electronics ... 886

Watford Electronics ... 962
Wilmslow Audio ... 904

Xeroza Radio ... 880

Z & I Aero Services ... 964

Head Office and Warehouse
44A WESTBOURNE GROVE
LONDON W2 5SF
Tel: 727 5641/2/3

Z & I AERO SERVICES LTD.

Please send all correspondence and Mail-Orders to Head Office
When sending cash with order, please include 0.15 in £ for postage and handling
MINIMUM CHARGE 15p. No C.O.D. orders accepted

Retail Shop
85 TOTTENHAM COURT ROAD
LONDON W1
Tel: 580 8403
Open all day Saturday

AC/DC MULTIMETER TYPE U4324



33 ranges up to
3 Amps AC/DC;
1200V DC, 900V
AC, 500kΩ, +12
db.

Sensitivity:
20kΩ/V DC;
4kΩ/V AC

Accuracy:
±2.5% DC;
±4% AC


Movement is protected by silicon diodes.

Dimensions 167x98x63 mm. Weight: 1.5lb.

PRICE: complete with test leads, instruction manual and fibre-board storage case £9.25. Packing & carriage £0.50.

MULTIMETER TYPE U4323

Sensitivity: 20,000Ω/V.

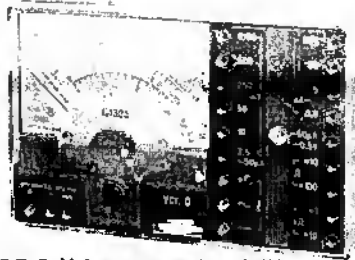


7 D.C. Voltage ranges 0.5-1000V
8 A.C. Voltage ranges 2.5-1000V
5 D.C. Current ranges 0.05-500mA

4 Resistance ranges 1kΩ-1mΩ
Built-in oscillator providing AF output of 1kHz and I.F. output of 465kHz with an amplitude of 1 volt minimum.

Dimensions: 140x87x40 mm. Weight 0.5kg

PRICE complete with leads and plastic storage case £7.70. Packing & postage £0.50

AC/DC MULTIMETER TYPE U4313

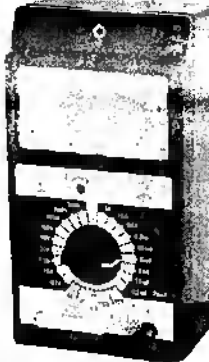

39 ranges:
600μA to 1.5A
AC
60μA to 1.5A DC
75mV to 600V
DC
1.5V to 600V AC
1MΩ, 0.5μF, 12db

Accuracy: 1.5%
DC; 2.5% AC

Sensitivity: 20k
Ω/V DC; 2kΩ/V
AC

Mirror scale 86mm long.

Dimensions: 115x215x90 mm, Weight 3.3lb.

PRICE, complete with test leads, service manual and steel carrying case £12.50. Packing & carriage £0.50.

**ALL THE ABOVE INSTRUMENTS FEATURE TAUT SUSPENSION MOVEMENTS
PRICES ARE EXCLUSIVE OF V.A.T.**



TRAMPUS ELECTRONICS LTD

58-60 GROVE ROAD,
WINDSOR, BERKS.


FAST SERVICE.

SEND C.M.O. ADD VAT TO ALL PRICES IN U.K. 76P 15P. EUROPE 25P. OVERSEAS 65P.

MONEY BACK IF NOT SATISFIED.
LARGE STOCKS. LOW PRICES.
ALL BRAND NEW TOP GRADE FULL
SPEC DEVICES. CALLERS WELCOME.

CATALOGUE/LIST FREE SEND S.A.E.

Digital Displays

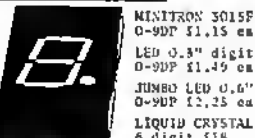

MINITRON 3015F
0-9DP £1.15 ea
LED 0.3" digit
0-9DP £1.45 ea
JUNBO LED 0.6"
0-9DP £2.25 ea
LIQUID CRYSTAL
6 digit £18

LEDS 14P.

NINI PIN SOURCE OR RED DIFFUSE
LEDS. 209 STYLE. NO CLIP. 14P ea
TIL209 RED LED & CLIP 17P ea
RIG 1" RED LED & CLIP 18P ea
ORANGE & GREEN LEDS:
NINI 25P ea. BIG & CLIP 33P ea
INFRA RED LED £1.25/777 5P.
PS12 PHOTO IC/amp/switch £1.
DIGITAL CLOCK
SOS INTEGRATED CIRCUITS.
AY51224 4 DIGIT CLOCK supplied
with 14pin socket & data £4.25
25X5114/1 4 DIGIT CLOCK with
28 pin socket & data 17.50
3 DIGIT DVM AY35502
LOGIC CONVERTER DRIVER

CASSETTE mechanics

STEREO CASSETTE MECHANISM.
As used in imported types
costing £100. Only requires
a case & electronics. Leads
supplied. Send for data 15p.

702 OPA 69p
703 BF/IF 29p
709 T099 21p
709 BIL 14 29p
710 DIL 14 35p
720 Radio £1.38
725 Regulator 67p
741 T099 29p
741 DIL8 31p
741 DIL14 31p
747 Dual 741 89p
748 DIL 8 59p
1535 IC 50p
74101 14pin 14p
74102 14pin 14p
74103 14pin 14p
74729 14pin 14p

FREE!

Over 150 ways to engineer a better future

HIGHER PAY **A BETTER JOB**

SECURITY

find out how in just 2 minutes

That's how long it will take you to fill in the coupon. Mail it today and we'll send you full details and a free book. We have successfully trained thousands of men at home—equipped them for higher pay and better, more interesting jobs. We can do as much for YOU. A low-cost home study course gets results fast—makes learning easier and something to look forward to. There are no books to buy and you can pay-as-you-learn.

Why not do the thing that really interests you? Without losing a day's pay, you could quietly turn yourself into something of an expert. Complete the coupon (or write if you prefer not to cut the page). No obligation and nobody will call in on you... but it could be the best thing you ever did.

Others have done it, so can you

"Yesterday I received a letter from the Institution informing that my application for Associate Membership had been approved. I can honestly say that this has been the best value for money I have ever obtained, a view echoed by two colleagues who recently commenced the course". Student D.I.B., Yorks.

"Completing your course, meant going from a job I detested to a job that I love, with unlimited prospects"—Student J.A.O. Dublin.

"My training quickly changed my earning capacity and, in the next few years, my earnings increased fourfold". Student C.C.P., Bucks.

FIND OUT FOR YOURSELF

These letters and there are many more on file at Aldermaston College, speak of the rewards that come to the man who has given himself the specialised know-how employers seek. There's no surer way of getting ahead or of opening up new opportunities for yourself. It will cost you a stamp to find out how we can help you. Write to


ALDERMASTON COLLEGE

Dept. RPW02, Reading RG7 4PF.

HOME OF BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Practical Radio & Electronics Certificate course includes a learn while you build **3 transistor radio kit.**

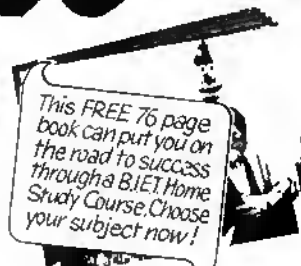Everything you need to know about **Radio & Electronics** maintenance and repairs for a **spare time income** and a **career** for a better future.



CUT OUT THIS COUPON
Tick or state subject of interest.
Post to address below.

| | | |
|--|--|---|
| MECHANICAL | DRUGHTSMANSHIP | Construction Surveyors Institute L.C.S.I. |
| Society of Engineers—A.M.S.E. (Elect) | Institute of Engineering Designers (A.M.I.E.D.) | City & Guilds General Building (all branches) |
| Institute of Engineer & Technicians (A.M.I.E.) | General Draughtsmanship | Heating & Vent. |
| CITY & GUILDS | Elect. Draughtsmanship | Inst. Clerk of Works |
| Gen. Mech. Eng. Maintenance Eng. Welding | Architectural Draughtsmanship | Health Engineering |
| Gen. Diesel Eng. Sheet Metal Work | Technical Drawing | Road Construction Quantities |
| Eng. Inspection Eng. Metallurgy | | Estimates Hydraulics Structural Eng. |
| ELECTRICAL & ELECTRONIC | RADIO & TELECOMMUNICATIONS | GENERAL |
| CITY & GUILDS | City & Guilds Telecoms. | Agricultural Eng. Council of Eng. |
| Gen. Electrical Engineering Electrical | Gen. Radio & TV Eng. | Institutions Farm Science Plastics |
| Electrical Maths Computer Electronics | Radio Amateurs' Society | Supplementary courses for Nat. Certificates. |
| Electronic Eng. Practical Radio & Electronics (with kit) | Radio Servicing | |
| MANAGEMENT & PRODUCTION | AUTOMOBILE & AERONAUTICAL | |
| Institute of Cost & Management Accountants | Institute of the Motor Industry A.M.I.I. | |
| Computer Programming Works Management Work Study | MAAJMI City & Guilds Auto Eng. | |
| Gen. Production Eng. Estimating & Planning | Gen. Auto Eng. Motor Mechanics Auto Diesel Eng. Garage Management A.E.U. Aero Engineering Exams Gen. Aero Eng. | |
| Storekeeping Management Skills Quality Control | CONSTRUCTIONAL | |
| | Institute of Building I.T.O.B. A.H.T. Clerk of Works | Coaching for many exams, including G.C.E. |

G.C.E.
—choose from 58 'O' & 'A' level subjects

POST TODAY FOR A BETTER TOMORROW

To Aldermaston College,
Dept. RPW02, Reading RG7 4PF.

NAME.....
Block capitals please
ADDRESS.....
.....
..... POSTCODE.....
OTHER SUBJECTS.....
..... AGE.....

Accredited by C.A.C.C.

Member of A.B.C.C.

Henry's

LARGEST SELECTION OF ELECTRONIC COMPONENTS AND EQUIPMENT. LOW PRICES—MEAN LESS VAT.



You can build the Texan and Stereo FM Tuner

TEXAN 20 + 20 WATT IC STEREO AMPLIFIERS

Features glass fibre PCB board, Gardners low field transformer, 6-IC's, 10-transistors plus diodes, etc. Designed by Texas Instruments engineers for Henry's and P.W. 1972. Supplied with full chassis work, detailed construction handbook and all necessary parts. Full input and control facilities. Stabilised supply. Overall size 15 1/2" x 22" x 6 1/2" mains operated. Free teak sleeve with every kit.



£31-00 (Carriage 50p).

(also built and tested £37-50)



HENELEC Stereo FM Tuner Features capacity diode tuning, lead and tuning meter indicators, stabilised power supply—mains operated. High performance and sensitivity with unique station indication IC stereo decoder. Overall size in teak sleeve 8" x 22" x 6 1/2". Complete kit with teak sleeve £21-00 (Carriage 50p).

(also built and tested £24-95)

JOIN THE LARGE BAND OF HAPPY CONSTRUCTORS!

TRANSISTORISED MODULES

Tuners - Power Supplies - Amplifiers

AMPLIFIERS (All single channel unless stated)

| | | £ p |
|--------|----------------------------|-------|
| 4-300 | 9 volt 300 MW | 1-75 |
| 2004 | 9 volt 250 MW | 2-70 |
| 104 | 9 volt 1 watt | 3-10 |
| 304 | 9 volt 3 watt | 3-95 |
| 555 | 12 volt 3 watt | 4-10 |
| 555ST | 12 volt 1 1/2 + 1 1/2 watt | 4-95 |
| E1208 | 12 volt 5 watt | 5-10 |
| 608 | 24 volt 10 watt | 4-95 |
| 410 | 28 volt 10 watt | 4-95 |
| 620 | 45 volt 30 watt | 9-95 |
| Z40 | 30/35 volt 15 watt | 5-45 |
| Z60 | 45/50 volt 25 watt | 6-95 |
| SA8817 | 24 volt 6 + 6 | 10-20 |

Amplifiers with controls

| | | |
|-------|------------------------------------|-------|
| E1210 | 12 volt 2 1/2 + 2 1/2 watts 6 ohms | 8-25 |
| R500 | Mains 5 watts 4-16 ohms | 6-30 |
| SAC14 | Mains 7 + 7 watts 8 ohms | 11-75 |
| SAC30 | Mains 15 + 15 watts 8 ohms | 14-95 |
| CA038 | 12 volt 1 1/2 + 1 1/2 watts 8 ohms | 6-95 |
| CA088 | 12 volt 3 + 3 watts 8 ohms | 10-50 |

FM Modules

| | |
|---|------|
| Mulfard LP 1185 FM tuner (front end) with data | 4-85 |
| Mulfard LP 1185 10.7 MHz IF unit with data | 4-50 |
| Garler Permeability FM tuner (front end) 10.7 MHz O/P | 4-20 |

FM and AM Tuners and Decoders

| | |
|--|-------|
| FM5231 (tu 2) 6 volt fm tuner | 7-95 |
| TU3 12 volt version (FM use with Decoder) | 7-95 |
| SD4912 Stereo Decoder for Tu 3-12 volt | 7-95 |
| SP62H 6 volt stereo FM tuner | 14-80 |
| A1067 9 volt MW-AM | 4-95 |
| Sinclair 12/45 volt FM tuner stereo recorder for above | 7-45 |
| A1018 9 volt FM tuner in cabinet | 13-95 |
| A1005M (S) 8-12 volt Stereo decoder FM for above | 7-50 |
| 106Z 12 volt Stereo decoder general purpose | 6-50 |

Preamplifiers

| | |
|--|------|
| Sinclair Stereo 50 Preamplifier | 6-75 |
| E1300 Car/Tape Mic inputs 9 volt | 2-85 |
| E1310 Stereo 3-30 mV mal cart 9 volt | 4-75 |
| FF3 Stereo 3 mV tape head 9 volt | 4-95 |
| 3402 Stereo 5-20 mV Mag. cart. mains | 5-95 |
| EQ25 Mono 3-250 mV Tape/Cart/Play 9 volt | 1-95 |

Power Supplies Mains Input

| | |
|--------------------------------------|-------|
| (chassis-riser case) | |
| 470C674/9V 300 MA with ad/s | 2-25 |
| P500 9 volt 500 MA | 3-20 |
| HCC244R 3.6/7.5/9V 400 MA stabilised | 3-20 |
| *P11 2v, 1 amp, 3-30 | 3-30 |
| *P15 28V, 1/2 amp | 3-30 |
| *P1080 12V 1 A 4.70 | 4-70 |
| *P1081 45V 0.9 A | 4-70 |
| P12 45-12V, 0.4-1 amp | 7-15 |
| SE1015 8.6/9/12V, 1 amp stabilised | 12-75 |
| P1076 3/4/8/12/18V, 1 amp | 4-20 |
| SE800A 1-15 VOLT 0-1A stabilised | 17-50 |

ALL PRICES SUBJECT TO VAT

EMI SPEAKERS SPECIAL PURCHASE

13 In. x 8 In. chassis speakers (Carriage 50p each of 50p per pair) £2-20
 150 TC 10 watts 8 ohm twin cone £2-20
 *450 10 watts 4, 8, 15 ohm with twin tweeters and crossover £3-85 each
 UR 15 watt 8 ohms with tweeter £5-25
 300 20 watt 8, 15 ohm with tweeter £7-80 each
 *Polished wood cabinet £4-80 carr., etc. 35p each or 50p pair.



UHF TV TUNERS

625 line receiver UHF transistorised tuners UK operation. Brand new. (Post/packing 25p. each).
 TYPE C variable tuning £2-50
 TYPE B 4-button push-button (adjustable) £3-50

PA-DISCOTHEQUE LIGHTING EQUIPMENT



Without doubt U.K.'s best range of modular and complete equipment. Lighting, mixing, microphones, accessories, speakers, amplifiers, lenses, etc., etc.

FREE stock lists (Ref. No. 18) on request CALL IN AND SEE FOR YOURSELF at HENRY'S DISCO CENTRE, 309 EDGWARE ROAD, TEL. 01-723 6963

125W-WATT LIGHT DIMMER £3-50 pp 20p

Manufactured by Ultra Ltd. Supplied with plate knob & Inst.

DENSHI BOARD KITS

| | |
|---------------------|--------|
| SR-2A 16 Projects | £ 7-70 |
| SR-3A 100 Projects | 14-95 |
| ST-45 45 Projects | 10-50 |
| ST-100 100 Projects | 13-20 |

TURNER KITS

| | |
|---------------------|----------|
| X20 10 Projects | Kit 6-80 |
| 50 in 150 Projects | 15-45 |
| 150 in 150 Projects | 23-65 |

RADIONIC KITS

| | |
|-----------------|-------|
| X20 20 Projects | £5-70 |
| X40 40 Projects | 12-75 |
| X40A ADD-ON | 10-45 |

TEST EQUIPMENT MULTIMETERS

| Carriage 50p | £ p |
|---|-------|
| J4324 20kΩ/V | 15-50 |
| J4325 20kΩ/V with case | 16-50 |
| J4313 20kΩ/V with steel case | 6-75 |
| J4313 20kΩ/V with steel case | 12-50 |
| J4317 20kΩ/V with case | 16-50 |
| J4341 33kΩ/V plus transistor steel case | 10-50 |
| D8323 20kΩ/V plus 1kHz OSC with case | 7-70 |
| ITI-2 20kΩ/V slim type | 5-85 |
| TML33D (L33DX) 2kΩ/V | 7-50 |
| Robust | |
| TP55N 20kΩ/V (Case £2) | 8-25 |
| TI05 20kΩ/V | 6-25 |
| TW20S 20kΩ/V | 10-00 |
| TW50K 50kΩ/V | 11-25 |
| EP10K 10kΩ/V | 9-95 |
| AF105 50kΩ/V Deluxe | 12-50 |
| (Carriage £1-90) | |
| S100TR 100kΩ/V plus transistor tester | 22-50 |



NEW REVOLUTIONARY SUPERTESTER 680R

| £ p | |
|---|-------|
| 680R Multi-tester | 18-50 |
| ITE40 AC Multimeter | 19-75 |
| ITE15 Grid dip meter | 19-50 |
| 440kΩ-28MHz | 19-50 |
| ITE65 23 Range valve | 22-50 |
| ITE20D RF Generator | 18-95 |
| 120kΩ-500MHz | 18-95 |
| ITE22D AF Generator | 19-95 |
| 20Hz-200kHz | |
| *HM350 in circuit transformer tester | 19-50 |
| *C3025 Deluxe meter 1-300MHz | 6-95 |
| *TT145 Compact transistor tester | 14-75 |
| TC3-30 R/C osc. 20Hz-200kHz | 19-75 |
| *C3042 SWR Meter | 5-75 |
| *SE350A De-Jux signal tracer | 12-95 |
| *SE400 Mini-lab all in one tester | 15-50 |
| Ci Scope 500,000kHz (Carriage £9) | 43-00 |
| *C3043 5 CH F/A meter 1-300MHz | 5-75 |
| R'stance sub box | 2-40 |
| Capacitor 1/2 20p | 2-10 |
| 2 amp variable transformer (carr. £1) | 6-55 |
| Radio actively counter 0-10r (carr. £1) | 9-97 |
| Mains unit for above (carr. 50p) | 3-75 |

TAPE HEADS

| | |
|---|------|
| Marlot XRPS/17 1/2 Track High | 2-50 |
| Marlot XRPS/18 1/2 Track Med. | 3-50 |
| Marlot XRPS/35 1/2 Track Med. | 5-00 |
| Marlot XRPS/63 3/4 Track High | 1-75 |
| Marlot Erase Heads for XRSP 17/18/35 (XES11) | 75p |
| Marlot BX12E 343 1/2 Track Erase | 75p |
| RRP 'S'igle Trk Rec/Play | 45p |
| Bogen Type UL280 Erase Miniature Stereo Cassette Rec/Play | 2-25 |

EXCLUSIVE 5 WATT IC AMPLIFIERS

| | |
|---|------|
| Special purchase 5 watt output 8-16 ohm load, 30 volt max. DC operation, complete with data. Price £4-50 each or 2 for £2-85. | |
| Printed Circuit Panels 50p. | |
| BD131 | 0-42 |
| BD135 | 0-20 |
| BF180 | 0-36 |
| BF194 | 0-28 |
| BF213 | 0-36 |
| BF234 | 0-28 |
| BF238 | 0-24 |
| BF250 | 0-21 |
| BF251 | 0-20 |
| BF264 | 0-35 |
| BF290 | 0-31 |

INTEGRATED CIRCUITS 74 SERIES & LINEAR

EXTRA DISCOUNTS

Semiconductors—Any one type or mixed SN74 Series '1C, 12—extra 10%; 25—extra 15%; 100—extra 20%.

| £ p | £ p | £ p | |
|----------|------|-----------|------|
| SN7400N | 0-16 | SN7485N | 1-83 |
| SN7401N | 0-16 | SN7486N | 0-47 |
| SN7402N | 0-16 | SN7489N | 3-87 |
| SN7403N | 0-16 | SN7490N | 0-55 |
| SN7404N | 0-26 | SN7491AN | 1-00 |
| SN7405N | 0-22 | SN7492N | 0-70 |
| SN7406N | 0-42 | SN7493N | 0-70 |
| SN7407N | 0-42 | SN7494N | 0-80 |
| SN7408N | 0-28 | SN7495N | 0-80 |
| SN7409N | 0-28 | SN7498N | 0-95 |
| SN7410N | 0-16 | SN7497A | 3-87 |
| SN7411N | 0-25 | SN74100N | 1-89 |
| SN7412N | 0-30 | SN74104N | 0-58 |
| SN7413N | 0-36 | SN74105N | 0-53 |
| SN7414N | 0-72 | SN74107N | 0-45 |
| SN7418N | 0-36 | SN74107N | 0-58 |
| SN7417N | 0-38 | SN74111N | 0-86 |
| SN7420N | 0-15 | SN74116N | 0-89 |
| SN7418N | 0-33 | SN74118N | 0-90 |
| SN7422N | 0-25 | SN74119N | 1-68 |
| SN7423N | 0-37 | SN74120N | 0-95 |
| SN7425N | 0-37 | SN74121N | 0-50 |
| SN7426N | 0-32 | SN74122N | 0-70 |
| SN7427N | 0-37 | SN74123N | 0-60 |
| SN7428N | 0-49 | SN74125N | 0-75 |
| SN7430N | 0-16 | SN74132N | 0-62 |
| SN7432N | 0-37 | SN74141N | 0-90 |
| SN7433N | 0-37 | SN74145N | 1-26 |
| SN7437N | 0-37 | SN74150N | 1-75 |
| SN7438N | 0-37 | SN74151N | 1-00 |
| SN7440N | 0-22 | SN74152N | 0-75 |
| SN7441AN | 0-92 | SN74154N | 2-00 |
| SN7442N | 0-79 | SN74155N | 1-00 |
| SN7443N | 1-27 | SN74158N | 1-00 |
| SN7444N | 1-27 | SN74157N | 0-85 |
| SN7445N | 1-60 | SN74160N | 1-38 |
| SN7446N | 1-85 | SN74161N | 1-38 |
| SN7447AN | 1-60 | SN74162N | 1-38 |
| SN7448N | 1-27 | SN74163N | 1-38 |
| SN7450N | 0-16 | SN74164AN | 1-76 |
| SN7451N | 0-16 | SN74165N | 1-76 |
| SN7453N | 0-15 | SN74166N | 1-60 |
| SN7454N | 0-16 | SN74167N | 3-08 |
| SN7460N | 0-16 | SN74170N | 0-82 |
| SN7470N | 0-36 | SN74173N | 1-66 |
| SN7472N | 0-38 | SN74174N | 1-57 |
| SN7473N | 0-41 | SN74175N | 1-10 |
| SN7474N | 0-42 | SN74176N | 1-26 |
| SN7475N | 0-59 | SN74177N | 1-26 |
| SN7476N | 0-45 | SN74178N | 0-78 |
| SN7480N | 0-60 | SN74181N | 3-95 |
| SN7481N | 1-10 | SN74182N | 1-26 |
| SN7482N | 0-67 | SN74184N | 1-80 |
| SN7483N | 1-10 | SN74185N | 1-80 |
| SN7484N | 1-00 | SN74190N | 2-00 |

| £ p | £ p | £ p | |
|-----------|------|----------|------|
| SN74191N | 2-00 | CA3012 | 1-32 |
| SN74192N | 2-00 | CA3014 | 1-80 |
| SN74193N | 2-00 | CA3016 | 1-02 |
| SN74194N | 1-30 | CA3019 | 1-12 |
| SN74195N | 1-10 | CA3020 | 1-80 |
| SN74196P | 1-20 | CA3026A | 1-03 |
| SN74197N | 1-20 | CA3036 | 1-08 |
| SN74198N | 2-77 | CA3046 | 0-70 |
| SN74199N | 2-52 | CA3048 | 1-15 |
| CA3081 | 1-80 | CA3075 | 1-21 |
| CA3085E | 2-94 | CA3088 | 1-80 |
| CA30900 | 4-23 | CA3091 | 1-80 |
| Signetics | | NE555 | 0-65 |
| NE555 | 0-65 | NE580B | 4-50 |
| NE580B | 4-50 | NE581B | 4-50 |
| NE582B | 4-50 | NE587B | 2-65 |
| NE587B | 2-65 | MC1301P | 1-42 |
| MC1301P | 1-42 | MC1304P | 1-79 |
| MC1304P | 1-79 | MC1310P | 0-97 |
| MC1310P | 0-97 | MC1358CF | 2-21 |
| MC1358CF | 2-21 | MC1410C | 0-80 |
| MC1410C | 0-80 | MC1410P | 0-85 |
| MC1410P | 0-85 | MFC4010P | 0-55 |
| MFC4010P | 0-55 | MFC6040P | 1-00 |
| MFC6040P | 1-00 | Others | |
| Others | | TBA800 | 1-50 |
| TBA800 | 1-50 | SN76003N | 1-50 |
| SN76003N | 1-50 | SN7617A | 0-60 |
| SN7617A | 0-60 | SN7618P | 0-61 |
| SN7618P | 0-61 | 708C | 0-75 |
| 708C | 0-75 | 729C | 0-30 |
| 729C | 0-30 | 789C | 0-39 |
| 789C | 0-39 | 792C | 0-65 |
| 792C | 0-65 | 747C | 0-45 |
| 747C | 0-45 | 748C | 0-61 |
| 748C | 0-61 | LM30 | |