

JUNE  
1978

# practical WIRELESS

Australia 85c  
New Zealand 85c  
South Africa 80c  
Malaysia \$2.25

45p



ALSO:- SIMPLE DARKROOM TIMER  
STATESIDE CALLING

## BOVINGTON

### TANK BATTLE GAME



## T.T.L. 74 I.C.s by TEXAS, NATIONAL, I.T.T., FAIRCHILD Etc

7400 14p	7413 30p	7437 25p	7460 15p	7481 75p	74121 30p	74139 100p	74155 75p	74173 150p	74188 350p
7401 14p	7414 30p	7438 25p	7470 30p	7482 45p	74122 40p	74141 60p	74156 70p	74174 100p	74189 350p
7402 14p	7416 30p	7440 15p	7472 25p	7483 40p	74153 60p	74142 27p	74157 70p	74175 75p	74190 140p
7403 14p	7417 30p	7441 65p	7473 30p	7485 60p	74125 50p	74143 27p	74160 90p	74176 100p	74191 140p
7404 14p	7420 15p	7442 65p	7474 30p	7486 70p	74126 50p	74144 27p	74181 90p	74177 100p	74192 120p
7405 14p	7422 20p	7445 80p	7475 30p	74100 35p	74130 130p	74145 75p	74162 90p	74178 140p	74193 120p
7406 40p	7423 25p	7446 85p	7476 30p	74184 40p	74131 100p	74147 230p	74183 90p	74179 140p	74194 100p
7407 40p	7424 25p	7447 75p	7477 30p	74105 40p	74132 85p	74148 100p	74184 125p	74180 100p	74195 100p
7408 20p	7426 25p	7448 70p	7483 70p	74107 30p	74135 100p	74150 120p	74185 125p	74181 200p	74196 100p
7409 20p	7427 25p	7450 15p	7485 100p	74108 50p	74136 80p	74151 65p	74186 125p	74182 75p	74197 100p
7410 15p	7428 40p	7451 15p	7486 30p	74110 50p	74137 100p	74152 65p	74187 325p	74183 150p	74198 185p
7411 20p	7430 15p	7453 15p	7489 250p	74118 50p	74138 125p	74153 120p	74188 200p	74184 150p	74199 185p
7412 20p	7432 25p	7454 15p	7490 35p						

## SEMICONDUCTORS by MULLARD, TEXAS, MOTOROLA, SIEMENS, I.T.T., R.C.A.

10 for AD161 350p	10 for BC183L 160p	10 for BC547B 100p	10 for BD135 350p	10 for BF199 220p	10 for E430 1150p	10 for TIP23B 380p	10 for TIP34A 720p	10 for 1N4005 45p	10 for 2N3705 90p
AD162 350p	BC184 80p	BC548 90p	BD136 350p	BF200 280p	MPSA65 250p	TIP23C 465p	TIP34B 800p	1N4006 50p	2N3706 90p
BC107 90p	BC184L 160p	BC549 120p	BD137 350p	BF204 150p	MPSA66 250p	TIP30 350p	TIP34C 2000p	1N4007 60p	BYX94 70p
BC108 90p	BC212 90p	BC549C 100p	BD139 350p	BF205 150p	MPSA67 250p	TIP30A 380p	TIP34D 580p	1N4008 70p	SCR PUTS ETC.
BC109 90p	BC212L 100p	BC549C 120p	BD140 350p	BF244B 300p	MJE340 440p	TIP30B 425p	TIP41B 630p	2N3709 150p	2N2546 450p
BC147 90p	BC213L 100p	BC556 100p	BF180 280p	BF257 150p	TIP29A 350p	TIP31A 380p	TIP42A 790p	2N3830 150p	2N6072 450p
BC148 90p	BC214 90p	BC557 120p	BF181 280p	BF258 250p		TIP31B 435p	TIP42B 770p	2N2906 150p	BR101 300p
BC149 90p	BC214L 100p	BC557B 140p	BF182 280p	BF259 280p		TIP32 500p	TIP2955 700p	2N2907 180p	BRV39 380p
BC157 90p	BC237 90p	BCV70 130p	BF183 280p	E100 400p	ARE FOR ANY TYPE OR MIX OF 10 AND INCLUDE POST AND VAT	TIP32A 550p	TIP3055 550p	2N3053 200p	BRV58 320p
BC158 90p	BC328 100p	BCV71 125p	BF184 90p	E204 430p		TIP32B 750p	1N4001 40p	2N3055 550p	BT101 1250p
BC159 90p	BC338 100p	BCV72 140p	BF195 90p	E300 450p		TIP32C 800p	1N4002 40p	2N3702 90p	BT106 1250p
BC182 90p	BC516 450p	BD131 330p	BF196 90p	E310 500p		TIP33A 620p	1N4003 40p	2N3703 90p	GT107 1250p
BC182L 100p	BC517 450p	BD132 350p	BF197 90p	E420 1140p		TIP33B 720p	1N4004 40p	2N3704 90p	TS88A 230p
BC183 90p	BC547 90p	BD133 450p	BF198 220p						

### LINEAR I.C.s

CA3130 100p
CA3140 100p
CA3076 200p
CA3085 85p
CA3088 190p
CA3089 210p
CA3090A Q 400p
CA3130 100p
LM300T D5 170p
LM301AN 85p
LM307N 85p
LM308T D5 130p
LM308DIL 130p
LM309K 100p
LM310T D5 160p
LM311T D5 260p
LM317K 325p
LM324 150p
LM348N 200p
LM350N 110p
LM351 180p
LM555 25p
LM710T D5 60
LM710DIL 65p
LM723T D5 75p
LM793DIL 75p
LM733 180p
LM748 45p
LM1303N 155p
LM1458 100p
LM3900N 90p
MC1310P 185p
ML741 14 Pin 30p
MM5514 430p
MM5518 550p
NE5200 150p
NE555 25p
NE556 100p
NE552B 400p
Mullard BTY87 100R 100V 8-5A 3817 DFC Clock £1 00
Chp £6 50
SN75003N 180p
SN75013N 180p
SN75013ND 125p
SN75023N 180p
SN75023ND 125p
SN75027N 180p
SN75028N 180p
SN75066N 100p
TAA300 150p
TAA350 190p
TA A550 50p
TA A851B 140p
TA A700 350p
TAD100 160p
TAD110 130p
TBA120S 80p
TGA120T 125p
TBA350 240p
TBA390Q 215p
TBA340 230p
TBA340Q 240p
TBA550Q 335p
TBA550C 335p
TBA841A12 250p
TBA720 250p
TBA800 110p
TBA810S 110p
TBA820 180p
TBA990 280p
TCA270Q 250p
TCA270S 250p
XR2206 675p
XR2207 450p
XR2216 850p
ZN414 120p
7805 140p
7812 140p
7815 140p
7818 140p
7824 150p

### DECODER BOARD CONTAINS

18 x 74158 £4.80  
2 x 74153 each  
1 x 74180 No technical details  
1 x 74150 details  
1 x TIP32 available

### EDGE CONNECTORS

### RESISTORS

E 12 SERIES  
J WATT  
100 OFF ANY  
ONE VALUE £1 00

### WIRE WOUND RESISTORS

BY V.T.M.  
5K 9 Watts  
10 for £1.00  
100 for £8.00  
1000 for £50.00  
10,000 for £400.00

### MULLARD MODULES

LP1152 200p  
LP1153  
LP1165  
LP1166 400p  
LP1168 each  
LP1181  
LP1173 400p

### FND 500

7 SEGMENT COMMON CATHODE DISPLAYS  
£1 30 each 4 for £5 00

### RCA

2N3668 S.C.R. 100V 12-5 AMP TO3 £2.00

### SPECIAL SCOOP OFFER

Leds 0-125 OR 0-2"  
RED ONLY. 100 for £8.00  
1000/£60.00

### ELEKTORNAADO AMPLIFIER

WRITE/PHONE FOR DETAILS

### UNENCODED HEXADECHIMAL

18 KEYBOARD  
1-10. ABCDEF.  
2 OPTIONAL KEYS.  
SHIFT KEY £15.00.

### BRIDGE RECTIFIERS

1A 50V 25p  
1A 100V 30p  
1A 200V 36p  
1A 400V 35p  
1A 600V 40p  
2A 50V 35p  
2A 100V 50p  
2A 200V 55p  
2A 400V 60p

### ELECTROLYTIC CAPACITORS

uF/V	5p	uF/V	15p
47/25	5p	330/25	15p
1/16	5p	330/35	16p
1/25	5p	330/50	18p
1/50	5p	470/10	12p
2-2/25	5p	470/25	16p
2 2/35	5p	470/35	18p
3-3/25	5p	470/50	22p
4-7/10	5p	1000/16	25p
4-7/16	5p	1000/35	26p
4-7/25	5p	2200/10	28p
4-7-50	5p	2200/16	35p
6-8/25	5p	2200/63	75p
10/10	5p	2200/100	120p
10/16	5p	3300/16	40p
10/25	5p	3300/25	42p
10/35	5p	3300/63	80p
10/50	5p	4700/25	45p
22/6V3	5p	4700/40	50p
22/10	5p	4700/63	120p
22/16	5p		
22-25	5p		
22/35	5p		
22/50	5p		
33/6V3	5p		
33/16	6p		
33/25	6p		
33/40	6p		
33/50	7p		
47/10	6p		
47/16	6p		
47/25	6p		
47/35	6p		
47/50	7p		
100/10	6p		
100/16	6p		
100/25	6p		
100/50	6p		
100/63	10p		
125/15	6p		
200/10	6p		
280/25	12p		
220/50	12p		

### POLYESTER CAPACITORS

Mullard or Erie	uF/V	5p
	-001	5p
	-0022	5p
	-0033	5p
	-0047	5p
	-0068	5p
	-01	5p
	-022	5p
	-033	5p
	-047	5p
	-1	6p
	-22	7p
	-33	9p
	-47	12p
	-1-0	20p
	-2-2	25p
	-4-7	35p
	-6-8	40p

### MURATA ULTRASONIC TRANSDUCERS MA40 L1R

£2 50 each. 2 for £4 00.

1200 uF 63V	2 for £1 00
2200 uF 63V	2 for £1 50
3300 uF 63V	2 for £1 60

### T.T.L. OFFERS

7410 10 for 100p
7412 10 for 150p
7420 10 for 100p
7430 10 for 100p
7440 10 for 250p
7474 10 for 200p
7476 10 for 250p
7483 10 for 700p
7486 10 for 450p
74107 10 for 350p
74121 10 for 250p
74153 10 for 400p
74161 10 for 800p

MM2102 AN-4L  
1024 x 1 BIT. 450n sec  
STATIC RAM  
£1.60 each  
4/£6.00. 8/£11.60

8218 8 BIT IN/OUT PORT £3.00 each  
PHONE FOR QUANTITY PRICE

AYS-1013 UAR/T £8 00

FUTABA 5LT02 DISPLAY £5 50

BD144 165p
B 2018B 250p
BU 205 220p
GDJ 32 250p
AU 100 180p
R 2008B 210p

### LEDS

RED .125 15p
GREEN .125 25p
YELLOW .125 25p
RED .2 15p
GREEN .2 25p
YELLOW .2 25p
DL 747 Display 280p

### CMOS

4000 14p	4030 55p
4001 14p	4082 95p
4002 14p	4083 120p
4006 90p	4047 100p
4007 16p	4048 55p
4009 55p	4049 40p
4011 14p	4050 40p
4012 14p	4054 120p
4013 50p	4055 140p
4015 90p	4056 135p
4016 40p	4060 120p
4017 90p	4066 55p
4018 90p	4069 20p
4020 100p	4071 16p
4022 90p	4072 16p
4023 16p	4081 18p
4024 65p	4082 18p
4025 16p	4510 150p
4026 16p	4511 120p
4027 50p	4516 110p
4028 30p	4518 130p
4029 110p	4528 100p

### TEXAS

T15 88A  
V.H.F. FET  
10 for £2-30  
100 for £20 00

555 TIMER  
10 for £2-50p

741 OP. AMP.  
10 for £2-00

### BYX 94

DIODES  
1250 PIV 1 Amp  
100 for £8 00

### BOB07/608

COMP. POWER  
£1 50 pair

### DIL SOCKETS

8 Pin 13p
14 Pin 14p
16 Pin 15p

### LIMITED OFFER

BC237  
100 for £3 00

### SPECIAL OFFERS

BC147  
BC148  
BC149 100  
BC157 FOR ASSORTED £8 50

### POTENTIOMETERS

1K LIN-2M LIN  
5

# practical WIRELESS

ISSUE 856

JUNE 1978 · VOLUME 54 · NUMBER 2

**BRITAIN'S LEADING JOURNAL FOR THE RADIO & ELECTRONIC CONSTRUCTOR**

Published by IPC Magazines Ltd., Westover House, West Quay Rd., POOLE, Dorset BH15 1JG

## News and Views

- 18 **EDITORIAL**—Crystal Gazing
- 19 **NEWS . . . NEWS . . . NEWS**
- 19 **KINDLY NOTE**—Radio 2 Tuner, July 1977.  
"Shoot", August 1977. IC of the Month, ULN-3006T, March 1978.  
Multi-Range Test Meters, March 1978.  
Experimenter's Corner, LED Light Display, April 1978.
- 26 **HOTLINES**—Recent developments in electronics .....Ginsberg
- 31 **PRACTICAL WIRELESS**—Preview of our next issue
- 48 **PRODUCTION LINES**—Information on the latest products .....Alan Martin
- 61 **ON THE AIR**—Amateur Bands .....Eric Dowdeswell G4AR  
VHF Bands, including What do the VHF's have to offer? .....Ron Ham BR515744  
SW Broadcast Bands .....Charles Molloy G8BUS  
MW Broadcast Bands .....Charles Molloy G8BUS
- 68 **PW READER'S PCB SERVICE**—Prices and details of the PCBs available

## For our Constructors

- 20 **AUDIO DISTORTION METER—2** .....E. A. Rule  
Constructional details
- 27 **PW PURBECK OSCILLOSCOPE—3** .....Ian Hickman  
Front panel and power supply wiring
- 38 **PW BOVINGTON TANK GAME** .....David Coultts  
Full constructional details of this exciting TV game
- 49 **DARKROOM TIMER** .....A. P. Donleavy  
A simple controller for your enlarger

## General Interest

- 32 **STATESIDE CALLING** .....Joe Kasser G3ZCZJ W3  
A broad look at the hobbyist radio scene in the USA
- 52 **SO YOU WANT TO PASS THE RAE?—10** .. John Thornton-Lawrence GW3JGA and Ken McCoy GW8CMY  
Aerials, feeders and matching. Overcoming interference. The examination.

## Extra

- 39 **INDEX TO VOLUME 53**  
Contents of our issues dated May 1977 to April 1978.

### COPYRIGHT

© IPC Magazines Limited 1978. Copyright in all drawings, photographs and articles published in 'Practical Wireless' is fully protected and reproduction or imitation in whole or in part is expressly forbidden. All reasonable precautions are taken by 'Practical Wireless' to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it and we cannot accept legal responsibility for it. Prices are those current as we go to press.



# The latest kit innovation!

from **Sparkrite**

the quickest fitting  
**CLIP ON**  
 capacitive discharge  
 electronic ignition  
 in KIT FORM

Introductory  
**SPECIAL OFFER**  
 £2 OFF Kit



- Smoother running
- Instant all-weather starting
- Continual peak performance
- Longer coil/battery/plug life
- Improved acceleration/top speeds
- Optimum fuel consumption

Sparkrite X4 is a high performance, high quality capacitive discharge, electronic ignition system in kit form. Tried, tested, proven, reliable and complete. It can be assembled in two or three hours and fitted in 1/3 mins. Because of the superb design of the Sparkrite circuit it completely eliminates problems of the contact breaker. There is no misfire due to contact breaker bounce which is eliminated electronically by a pulse suppression circuit which prevents the unit firing if the points bounce open at high R.P.M. Contact breaker burn is eliminated by reducing the current to about 1/50th of the norm. It will perform equally well with new, old, or even badly pitted points and is not dependent upon the dwell time of the contact breakers for recharging the system. Sparkrite incorporates a short circuit protected inverter which eliminates the problems of SCR lock on and, therefore, eliminates the possibility of blowing the transistors of the SCR. (Most capacitive discharge ignitions are not completely foolproof in this respect). The circuit incorporates a voltage regulated output for greatly improved cold starting. The circuit includes built in static timing light, systems function light, and security changeover switch. All kits fit vehicles with coil/distributor ignition up to 8 cylinders.

**THE KIT COMPRISES EVERYTHING NEEDED**  
 Die pressed epoxy coated case. Ready drilled, aluminium extruded base and heat sink, coil mounting clips, and accessories. Top quality 5 year guaranteed transformer and components, cables, connectors, P.C.B., nuts, bolts and silicon grease. Full instructions to assemble kit neg. or pos. earth and fully illustrated installation instructions

NOTE—Vehicles with current impulse tachometers (Smiths code on dial RV1) will require a tachometer pulse slave unit. Price £3.95 inc. VAT, post & packing.

Electronics Design Associates (Dept. PW6),  
 82 Bath Street, Walsall WS1 3DE.

Electronics Design Associates, Dept. PW 6  
 82 Bath Street, Walsall, WS1 3DE. Phone: (0922) 614791

Name \_\_\_\_\_  
 Address \_\_\_\_\_

Phone your order with Access or Barclaycard

inc. V.A.T. and P.P.

QUANTITY REQD.

X4 KIT	£14.95	£12.95
TACHS PULSE SLAVE UNIT	£3.95	
Access or Barclaycard no.		

I enclose cheque/PO's for

£ \_\_\_\_\_  
 Cheque No \_\_\_\_\_

Send SAE if brochure only required.

## The MIGHTY MIDGETS



# MINIATURE SOLDERING IRONS AND ACCESSORIES



	RETAIL PRICE each inc. v.a.t.	POSTAGE extra.
18 WATT IRON inc. No.20 BIT	£3.78	22p
SPARE BITS	44p	—
STANDS	£3.25	65p
SOLDER: SAVBIT 20'	52p	9p
" 10'	26p	4p
LOWMELT 10'	65p	9p
I.C. DESOLDERING BIT	88p	9p
BIT SIZES:	No.19 (1.5 mm) No.21 (4.5 mm)	No.20 (3 mm) No.22 (6 mm)

From your Local Dealer or Direct from Manufacturers

## S & R. BREWSTER LTD

86-88 Union St. Plymouth PL1 3HG  
 Tel: 0752-65011 TRADE ENQUIRIES WELCOME

## TECHNICAL TRAINING IN ELECTRONICS TELEVISION AND RADIO SERVICING

ICS can provide the technical knowledge that is so essential to your success, knowledge that will enable you to take advantage of the many opportunities open to the trained person. You study in your own home, in your own time and at your own pace and if you are studying for an examination ICS guarantee coaching until you are successful.

- City & Guilds Certificates:**  
 Telecommunications Technicians  
 Radio, TV, Electronics Technicians  
 Technical Communications  
 Radio Servicing Theory  
 Radio Amateurs  
 Electrical Installation Work  
 MPT Radio Communications Certificate

- Diploma Courses:**  
 Colour TV Servicing  
 Electronic Engineering and Maintenance  
 Computer Engineering and Programming  
 Radio, TV, Audio Engineering and Servicing  
 Electrical Engineering, Installation  
 and Contracting

POST OR PHONE TODAY FOR FREE BOOKLET.

## ICS To: International Correspondence Schools

Dept. No. 276V, Intertext House, LONDON  
 SW8 4UJ or telephone 622 9911

Subject of Interest \_\_\_\_\_

Name \_\_\_\_\_

Address \_\_\_\_\_

Tel: \_\_\_\_\_

## THERMOSTATS



Refrigeration as illustrated with 36" capillary £1-62.  
**Limpet Stat** must be mounted in close calibrated 90°-190°F 15 amp contact £1-62.  
**Appliance Stat** fix like a volume control—15 amp contact 30°-80°F 85p.  
 ditto but for high temps £1-25.  
**Oven Stat**—with sensor and capillary 85p.

## MAINS OPERATED SOLENOIDS



Model TT2—small but powerful 1 1/2 in. pull—approx. size 1 1/2 x 1 1/2 in. £2-00.

Model 4001—1 1/2 in. pull. Size 2 1/2 x 2 x 1 1/2 in. £2-50.

Model TT10—1 1/2 in. pull. Size 3 x 2 1/2 x 2 in. £4-50.

Prices include VAT & postage.




## DELAY SWITCH


Mains operated—delay can be accurately set with pointers knob for periods of up to 2 1/2 hrs. 2 contacts suitable to switch 10 amps—second contact opens few minutes after 1st contact 95p.
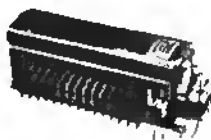
## MOTORISED DISCO SWITCH

With 10 amp change-over switches. Multi adjustable switches are rated at 10 amps. This would provide a magnificent display. For mains operating. 2 switch model £3-25. 10 switch model £5-75. 12 switch model £6-75.



## SMITHS CENTRAL HEATING CONTROLLER

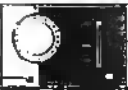

Push button gives 10 variations as follows: (1) continuous hot water and continuous central heating (2) continuous hot water but central heating off at night (3) continuous hot water but central heating on only for 2 periods during the day (4) hot water and central heating only for 2 periods during the day (5) hot water all day but central heating only for 2 periods during the day (6) hot water and central heating on for 2 periods during the day time only—then for summer time use with central heating off (7) hot water continuous (8) hot water day time only (9) hot water twice daily (10) everything off. A handsome looking unit with 24 hour movement and the switches and other parts necessary to select the desired programme of heating. Supplied complete with wiring diagram. Originally sold we believe at over £15. We offer these while stocks last at £6-95 each INCLUDING VAT and Postage.

## LOW R.P.M. MOTORS



Made by Crauzet-Smiths—SAIWA—Vanner and similar famous companies—all supplied ready for 230/240v 50hz mains working at £2-75 each. Following speeds in stock when preparing this advert.


1 rev per day 6 rev per day  
 1 rev per hour 12 revs per hour  
 1 rev per min  
 2 rpm 1 1/2 rpm  
 4 rpm 15 rpm 15 rpm 25 rpm 30 rpm

## TRACTOR FAN



Ex computers—made by Woods of Colchester. Ideal for fixing through panel—reasonably quiet running—very powerful 2500 rpm. Choice of two sizes 5" or 6 1/2" dia. £5 and £8.

## FLUORESCENT TUBE INVERTOR

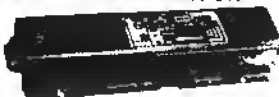

For camping—car repairing—emergency lighting from a 12v battery you can't beat fluorescent lighting. It will offer plenty of well distributed light and is economical. We offer inverter for 21" and 33 watt miniature tube for only £3-75 with tube and tube holders as well.

## MINI-MULTI TESTER



Amazing, deluxe pocket size precision moving coil instrument—jewelled bearings—10000cps—11 instant ranges measure: DC volts 10, 50, 250, 10000. AC volts 10, 50, 1000. DC amps 0-1 mA and 0-100 mA. Continuity and resistance 0-150K ohms.

Complete with insulated probes, leads, battery, circuit diagram and instructions. Unbelievable value only £8-90

## FREE

Amps ranges kit enable you to read DC current from 0-10 amps directly on the 0-10 scale. It's free if you purchase quickly but if you already own a mini tester and would like one send £1-50.

## MULLARD UNILEX

A mains operated 4+4 stereo system. Rated one of the finest performers in the stereo field this would make a wonderful gift for almost anyone in easy-to-assemble modular form and complete with a pair of Finest speakers this should sell at about £30—but due to a special bulk buy and as an incentive for you to buy this month we offer the system complete at only £15 including VAT and postage.



## UNISELECTORS

These are pulse operated switches as used in automatic telephone switchboards etc. The pulse moves the switch arm through one position. Except where indicated the selectors are 25 position types and 50v Coil is standard. 24v or 12v operation extra at £2 per switch.



3 pole £4-00  
 6 pole £7-02  
 10 pole £10-50  
 3 pole 50 way £10-50

4 pole £5-94  
 8 pole £8-72  
 12 pole £12-95  
 4 pole 50 way £12-74

## 24 HOUR TIMERS

The one illustrated is 'E' controls this uses the Smiths mechanism as in their autoset. 2 on/off's per 24 hours 13 amp contacts. override switch £8-50. Smiths 100 amp model one on/off per 24 hours £10-50, extra contacts £1-00 per set. AEG 50 amp model with clockwork standby, one on/off per 24 hours £8-50, extra contacts £1-00 per set.



## INDUCTION MOTORS

One illustrated is our reference MM11 made for ITT 3" stack 1 1/2" spindle £2-25. 1" stack model £1-75. 1" stack £2-75. 1 1/2" stack £3-25.



## MAINS TRANSFORMERS

5v 1 amp £1-00. 12v 1 amp £1-00.  
 20v 1 amp 20w auto 25v £1-00.  
 18v 1/2 amp £1-75. 6-3v 2 amp £1-75.  
 25v 1 1/2 amp £2-25. 24v 3 amp £2-50.  
 50v 2 amp £4-50. 9v 1 amp £1-50.  
 3-5v-0-8 5v 1/2 amp £1-50. 100w auto 230-115v £2-00. 8-5v £3-50.



Many more, send for list.

## MULLARD AUDIO AMPLIFIERS

All in module form, each ready built complete with heat sinks and connection tags, data supplied. Model 1933 500mW power output £1-00 including Post & VAT.  
 Model 1172 1W power output £1-85 including Post & VAT.  
 Model EP0000 4 watt power output £2-00 including Post & VAT. EP 6001 twin channel or stereo pre-amp £2-00 including Post & VAT.



## THIS MONTH'S SNIP

Japanese made FM tuner and matching decoder. Two items for less than average price of the tuner only £1-20 the two. Don't miss this, stocks will not last long. Wooden case with glass dial £15-50.



## RELAYS

12 volts two 10 amp changeover plus in 15p. 12v three 10 amp changeover plus in £1-25. 12v two changeover miniature wire ended 95p. 12 volt open single screw fixing two 10 amp changeovers £1-25. 12 volt open three 10 amp changeovers £1-25. Latching relay mains operated 2 c/o contacts £2-11. Mains operated three 10 amp changeovers open type one screw fixing £1-25. Many other types with different coil voltages and contact arrangements are in stock, enquiries invited.



## MICRO SWITCH BARGAINS

Rated at 5 amps 250 volts. Ideal to make a switch panel for a calculator and for dozens of other applications. Parcel of 10 for £1-00. VAT and post paid.



## 25A ELECTRIC PROGRAMMER

Learn in your sleep. Have radio playing and kettle boiling as you wake—switch on lights to ward of intruders—have a warm house to come home to. All these and many other things you can do if you invest in an electrical programmer. Clock by famous maker, with 15 amp on/off switch. Switch-on time can be set anywhere to stay on up to 6 hours. Independent 60 minute memory logger. A beautiful unit. Price £2-85. VAT and postage 80p, or with glass front, chrome bezel £1-50 extra.



Terms. Prices include Post & VAT. But orders under £8-00 please add 50p to offset packing. Bulk enquiries—Please Phone for Generous Discounts 688 1533.

**J. BULL (ELECTRICAL) LTD**  
 (Dept. P.W.), 103 TAMWORTH RD.  
 CROYDON CR9 1SG

## IT'S FREE!

Our monthly Advance Advertising Bargains List gives details of bargains arriving or just arrived—often bargains which sell out before our advertisement can appear.—It's an interesting list and it's free—just send S.A.E. Below are a few of the Bargains still available from previous lists.

## MAINS TRANSFORMERS

All these have 230/240v 50Hz Primary			
VOLTAGE	CURRENT	REF.	PRICE
5v	2 amp	TM 1	£1-04
2-4v	5 amp	TM 2	£1-02
4v	7 amp	TM 30	£2-70
6v	1 amp	TM 3	£1-05
6-5v	1/2 amp	TM 37	85p
6-5v	200 ma	TM 31	£1-02
6-5v-0-6 5v	100mA	TM 21	£1-02
6-5v-0-6 5v	100mA	TM 7	£2-10
6-5v-0-6 5v	100mA	TM 33	£1-02
6-5v	2 amp	TM 4	£1-09
6-5v	1 amp	TM 12	£1-02
8-5v + 8-5v sep winding	1/2 amp	TM 12	£1-02
9v	1 amp	TM 5	£1-02
9v	1 amp 'c' core	TM 8	£1-06
9v	3/4 amp	TM 11	£2-70
9v	5 amp	TM 38	£3-24
10v	25 amp	TM 15	£4-00
10v-0-10v	12 1/2 amp	TM 15	£4-00
12v-0-12v	4 amp	TM 27	£4-32
12v	1/2 amp	TM 9	£1-05
12v	1/2 amp	TM 7	£2-10
12v	1/2 amp	TM 10	£1-09
12v-0-12v	30mA	TM 19	£1-02
14v-0-12v	1 amp	TM 41	£3-24
18v tapped 9v	2 amp	TM 11	£2-70
18v	7 amp	TM 27	£4-32
18v-0-15v	3 1/2 amp	TM 27	£4-32
18v-0-15v	3 1/2 amp	TM 38	£4-00
17v	1/2 amp	TM 12	£1-02
18v	1/2 amp	TM 13	£1-00
20v	1/2 amp	TM 14	£1-02
20v	5 amp	TM 27	£4-32
20v	12 1/2 amp	TM 16	£4-00
20v-0-20v	8 amp	TM 16	£4-00
13v	100mA	TM 1	£1-02
24v	1 1/2 amp	TM 16	£2-12
24v	2 amp	TM 17	£2-70
24v + 2v 7 amp	2 amp	TM 39	£2-87
24v	4 amp	TM 40	£3-70
25v	1 1/2 amp	TM 18	£2-43
25v	1/2 amp	TM 29	£2-86
25v	1/2 amp	TM 27	£4-32
25v tapped 24, 20, 15 & 12	3 1/2 amp	TM 27	£4-32
30v	8 amp	TM 15	£4-00
32v	37 amp	TM 34	£31-80
40v tapped at 30v, 20v & 10v	6 amp	TM 15	£4-00
50v-2 amp with 6-3v shrouded	5 amp	TM 22	£4-00
50v	8 amp	TM 29	£11-85
50v	5 amp	TM 29	£11-85
75v-3 amp with 6-3v shrouded	5 amp	TM 23	£4-00
75v	4 1/2 amp	TM 24	£7-02
80v tapped 60v & 75v	4 amp	TM 24	£7-02
100v	1 amp	TM 25	£7-02
100v-0-100v	1/2 amp	TM 25	£7-02
130v tapped 120v	1/2 amp	TM 25	£3-78
320v	1 amp	TM 35	£7-02
250v-0-250v with 6-3v 2A	50 mA	TM 36	£2-70
250v	100 mA	TM 36	£2-70
500v	50mA	TM 38	£2-70

350mA 6 Volt Mains Unit. Ideal for power 6 volt equipment, cassettes, tape recorder or amplifier or other appliances requiring more than the average amount of current. This is a really well made unit in plastic case made for Crown Radio intended originally to clip into position, this has external battery type contacts but it is a simple matter to solder leads straight onto these contacts and this unit employs full wave rectification and is recommended in every way. Price £4-30

Calculators. By famous makers like Texas. Intended originally to be sold at quite high prices new and unused. Type 1. Basic functions—add, subtract, multiply, divide etc. Price £5-15. Type 2.—again basic functions but with rechargeable nickel batteries. Price £7-02. Battery Chargers for same £2-70. Type 3.—basic functions but with memory £3-10. Type 4.—basic functions, memory and rechargeable batteries. Price £11-34 + 84p.

AM/FM Radio. Complete chassis, has tuning scale with pointer, volume control, on/off etc. Controls have edgewise knobs. These radios can be mounted on or just inside extension speaker, then you have a first class 'musical while you work' receiver. Reception on both AM/FM is better than average and even in areas where FM is notorious bad, good results have been obtained. The output also is above average, the speaker power is probably around 1 1/2 watts. They can be powered by 6v batteries or 6v power supply. In fact the Crown Radio one mentioned above is ideal, would no doubt function as an AM/FM Tuner—real bargain at £5-50 + 84p.

UV Tubes (Philips Atomic). Useful for bringing out water marks in stamps and special colours in rocks, similar specimens. We have these in two sizes 9" 6v price £1-50 + 12p. Post 50p + 4p. 2 1/2 20 watt £2-00 + 15p. Post 75p + 6p. 4 Pole 15 Way Switch. For digital displays the 10 positions being evenly spaced through the 360 turn, and there is no stop. Silver plated contacts are rated at 5 amps, normally an expensive switch but offered at 85p each.


Morse Key. This is well designed, fully adjustable key, suitable for beginners. Our Ref. MK1. Price £1-15. Professional Morse Key. Heavy cast base of metal construction, this is high speed key with fine adjustments. Price £3-35. Our Ref. MK2. Terminals. Very good quality, British made, screw down type, top accepts a 4mm plug. The screw down section also has a hole through which solid wire may be passed, with insulators for metal panel mounting, 5 popular colours. Price 15p each, Ref. TS1, or 10 in bag for £1-30. Ref. TS1/10. Spring Trigger Terminals. Red and black terminals mounted on insulated panel approximate size 2 1/2" x 1". These terminals grip like a vice but connection in the first place is quick and simple. Hold back the trigger—push in wire—let go of trigger, definitely a time saver. Price 54p the pair. Shrouded Plug-Stat. Miniature size 2-2k, 10 for £1-00 + 12p. Relay Base. 14 pin standard for many plug-in relays 54p + 4p. AC Mains Relay. Plug in to standard base, three 10 amp changeover contacts. Price £1-00 + 14p. but 2 x 10 amp c/o contacts £1-25, bases 35p extra. Heavy Duty 15v Relay. This has 3 pairs of changeover contacts which are rather bigger than usual and look capable of dealing with 15 amp loads. Ditto but 4 Volt Coil. Price £2-16 + 16p.





# LOOK! Here's how you master electronics.



...the practical way.

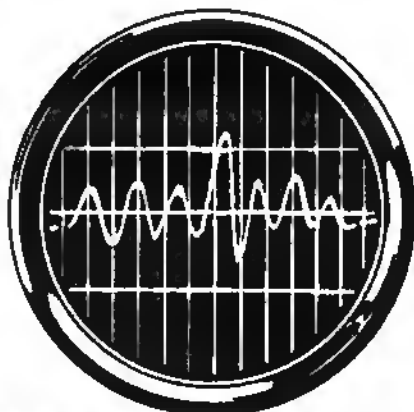

This new style course will enable anyone to have a real understanding of electronics by a modern, practical and visual method. No previous knowledge is required, no maths, and an absolute minimum of theory.

You learn the practical way in easy steps mastering all the essentials of your hobby or to further your career in electronics or as a self-employed electronics engineer.

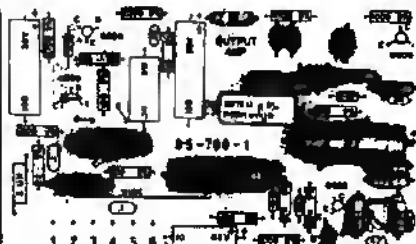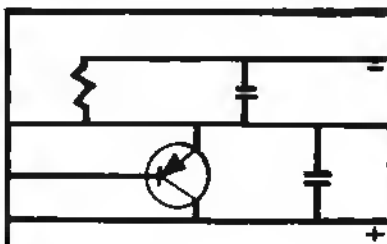All the training can be carried out in the comfort of your own home and at your own pace. A tutor is available to whom you can write, at any time, for advice or help during your work. A Certificate is given at the end of every course.



## 1 Build an oscilloscope.

As the first stage of your training, you actually build your own Cathode ray oscilloscope! This is no toy, but a test instrument that you will need not only for the course's practical experiments, but also later if you decide to develop your knowledge and enter the profession. It remains your property and represents a very large saving over buying a similar piece of essential equipment.


## 2 Read, draw and understand circuit diagrams.

In a short time you will be able to read and draw circuit diagrams understand the very fundamentals of television, radio, computers and countless other electronic devices and their servicing procedures.

## 3 Carry out over 40 experiments on basic circuits.

We show you how to conduct experiments on a wide variety of different circuits and turn the information gained into a working knowledge of testing, servicing and maintaining all types of electronic equipment, radio, t.v etc.

**FREE GIFT**

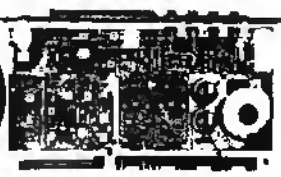

All students enrolling in our courses receive a free circuit board originating from a computer and containing many different components that can be used in experiments and provide an excellent example of current electronic practice.

**Free!**

To find out more about how to learn electronics in a new, exciting and absorbing way, just clip the coupon for a free colour brochure and full details of enrolment.

**British National Radio & Electronic School**

P.O. Box 156, Jersey, Channel Islands.

NAME \_\_\_\_\_

WB 6 ADDRESS \_\_\_\_\_

Block caps please



# GREENWELD

443 Millbrook Road Southampton  
SO1 0HX Tel: (0703) 772501

All prices quoted include VAT. Add 25p UK/BFPO postage. Most orders despatched on day of receipt. SAE with enquiries please. **MINIMUM ORDER VALUE £1.** Official orders accepted

from schools, etc. (Minimum Invoice charge £5). Export/Wholesale enquiries welcome. Wholesale list now available for bona-fide traders. Surplus components always wanted.

## BUY A COMPLETE RANGE OF COMPONENTS AND THESE PACKS WILL HELP YOU

- ★ **SAVE ON TIME**—No delays in waiting for parts to come or shops to open!
- ★ **SAVE ON MONEY**—Bulk buying means lowest prices—just compare with others!
- ★ **HAVE THE RIGHT PART**—No guesswork or substitution necessary!

All packs contain full spec. BRAND NEW, MARKED DEVICES—SENT BY RETURN OF POST. VAT INCLUSIVE PRICES.

**KM1** 50V ceramic plate capacitors, 5%, 10 of each value 22pF to 1000pF. Total 210, £2.35

**KM2** Extended range, 22pF to 0.1µF, 330 values £4.90

**KM3** Polyester capacitors, 10 each of these values: 0.01, 0.015, 0.022, 0.033, 0.047, 0.068, 0.1, 0.15, 0.22, 0.33, 0.47µF. 110 altogether for £4.75

**KM4** Mylar capacitors, min 100V type, 10 each all values from 1000pF to 10,000pF. Total 130 for £3.75

**KM5** Polystyrene capacitors, 10 each value from 10pF to 10,000pF, E12 series 5% 180V. Total 370 for £12.30

**KM6** Tantalum bead capacitors, 10 each of the following: 0.1, 0.15, 0.22, 0.33, 0.47, 0.68, 1, 2.2, 3.3, 4.7, 6.8, all 38V; 10/25 15/15 22/16 33/10 47/6 100/3. Total 170 tanks for £14.20

**KM7** Electrolytic capacitors 25V working, small physical size, 10 each of these popular values: 1, 2.2, 4.7, 10, 22, 47, 100µF. Total 70 for £3.50

**KM8** Extended range, as above, also including 220, 470 and 1000µF. Total 100 for £5.90

**KM9** Miniature carbon film 5% resistors, CR25 or similar, 10 of each value from 10R to 1M, E12 series. Total 610 resistors, £4.90

**KM10** Extended range, total 550 resistors from 1R to 10M £8.30

**KM11** Zener diodes, 400mW 5% BZY88, etc. 10 of each value from 27V to 38V, E24 series. Total 250 for £18.30

**KM12** As above but 5 of each value £8.70

### EDGE CONNECTORS

Special purchase of these 0.1" pitch double-sided gold-plated connectors enables us to offer them at less than one-third their original list price! 18 way 47p; 21 way 47p; 32 way 72p; 40 way 90p.

### SOLAR CELLS

As used on space labs, etc., these tiny cells give 50µA @ 0.5V in sunlight. Ideal for powering small CMOS projects, etc. Can be banked together for greater power output. Size 19 x 8.5mm, 3 for £1; 10 for £3; 25 for £7; 100 for £25.

### POWER PACK

Wood grained metal case 90 x 80 x 75mm containing mains transformer giving 4V @ 200mA, 12 co-ax sockets, PC board with 1½ fuseholder R's C's, etc. Only 75p.

### S-DECS & T-DECS

S-DEC Breadboard £2.25

T-DEC Breadboard £2.95

### SIRENS

Work off 4 x HP7 batteries, emit very loud noise. Overall size 110 x 75 x 90mm. Use as Burglar Alarm in car, house, workshop, etc ONLY £1.95.

### PC ETCHING KIT MK III

Now contains 200 sq. ins. copper clad board, 1lb. Ferric Chloride, DIALO etch-resistant pan, abrasive cleaner, two miniature drill bits, etching dish and instructions. £3.30

SEND 45p FOR OUR 1977/8 CATALOGUE. CONTAINS 50p DISCOUNT VOUCHERS. AMENDMENT SHEET No. 2 GIVES DETAILS OF OVER 100 ITEMS SLASHED 50%!!! (Send SAE if you've already got cat.)

Our latest Bargain Sheet is FREE, send SAE for your copy.

### VEROCASES

Plastic top and bottom ally panels front and back

1237	154x85x40	£2.53
1238	154x85x60	£2.79
1239	154x85x80	£3.22
3007	180x120x40	£3.30
3008	180x120x55	£3.50
3009	180x120x90	£3.74
1410	205x140x40	£3.51
1411	205x140x75	£4.05
1412	205x140x110	£4.12

### VERO PLASTIC BOXES

Professional quality two tone grey polystyrene with threaded inserts for mounting PC boards

2518	120x65x40	£2.17
2520	150x80x50	£2.45
2522	188x110x60	£3.23

### SLOPING FRONT BOXES

1798	171x121x75/37-5	£4.19
2528	220x174x100/53	£5.95

Painting box. 71 x 49 x 24mm black or white 40p

Hand controller box 94 x 61 x 23mm White 84p

### VEROBOARD

Our packs of vero offcuts are one of our biggest sellers—and no wonder, they are amazing value! Each pack contains 7 or 8 pieces to make up a total area of 100 sq. ins. All packs are the same price, £1.30 each and are available as follows:

Pack A all 0.1" pitch

Pack B all 0.15" pitch

Pack C mixed 0.1 & 0.15"

Pack D all 0.1" plain

Also available by weight 1lb £3.95 10lbs £32.50

Regular size vero

17x31x0.1" £2.90, 10 strips £15

17x31x0.15" £1.70, 0.1" plain £1.63

DIP Breadboard size 8, 15x4.5", can accommodate 20x14 pin ICs £2.35

VQ Board, size 148 x 75mm 0.1" pitch. Copper strips in rows of 4 to facilitate construction with IC's. Layout sheet provided 85p

### VERO PINS AND TOOL

Spot face cutter for 0.1 or 0.15 pitch VQ

0.1" pins single sided 30p/100

0.15" pins single sided 30p/100

0.15" pins double sheets 35p/100

### CALCULATOR CHIP

Type C500 by GI. 4 function + constant. 8 digit. Multiplied output for simple keyboard interfacing 24 pin DIL. With comprehensive data + socket £1.50.

### DARLINGTON COMP PAIR

BD695A and BD695A—45V 8A 70W plastic power gain 750 @ 4A. PNP-NPN pair £1.50.

### RESISTOR OFFER. Miniature 1W

5% carbon film, but the leads, although full length have been preformed for vertical mounting. Now in the following values only: 68R, 150R, 330R, 390R, 470R, 1k, 1k2, 2k, 3k, 5k, 10k, 22k, 27k, 33k, 68k, 100k, 470k, 820k, 1M—18 values altogether. 100 off each value, total 1900 resistors for £6. Or 1000 off each value, total 1900 resistors for £45 (this works out at 0.2360p per resistor!)

## SPECIAL TRANSISTOR OFFERS

Plastic versions of these popular types.

BC108-9, BCY70-71-72 at very low prices.

PN108 (BC108) ..... 12 for £1

PN70 (BCY70) ..... 14 for £1

PN71 (BCY71) ..... 15 for £1

PN109 (BC109) ..... 16 for £1

PN71 (BCY71) ..... 14 for £1

Complementary Power Pair. BD525 & BD526. Motorola plastic power, 80V 2A devices, normally 94p pair. Special offer price 34p pair.

Small signal PNP transistors, like 2N3702 (Marked MSPS1218) 20 for £1.

TANT BEAD CAPS—4µF 50V, normally 14p each. Our special offer price 12 for £1.

## FANTASTIC HALF PRICE OFFER

### TANK BATTLE T.V. GAME AVAILABLE NOW



TANK BATTLE AY-3-87 10 I.C. (Normal Price) £21.50 OUR PRICE £10.90

TANK BATTLE PRINTED CIRCUIT BOARD Application and assembly notes £4.90 OUR PRICE £2.90

TANK BATTLE BASIC KIT (Just add 11 pushbuttons and cases) £27.90 OUR PRICE £19.90

TANK BATTLE CASES with printed fascia plate and hand controls OUR PRICE £4.95

SOUND AND VISION MODULATORS Built, Tested, Guaranteed £5.50 OUR PRICE £4.90

- ★ Hide behind barricades and avoid being hit
- ★ Dodge the enemy's mines
- ★ Force you opponent into deserting the battlefield
- ★ Three forward and reverse tank speeds
- ★ Tank firing range is two-thirds of the battlefield
- ★ On-screen scoring
- ★ 32 rotational angles
- ★ Shells travel in an authentic curved trajectory
- ★ Sound direct from the TV
- ★ Realistic battle sounds derived from a synthesiser
- ★ Tanks move and fire in all directions
- ★ Black and white kit available NOW
- ★ Budget-priced colour add-on unit available shortly.

All Components Guaranteed

PRICES INCLUDE VAT and Post/Packing

Make all cheques or postal orders payable to Teleplay

ACCESS · phone your order · BARCLAY

Retail Shop and Demonstrations—14 Station Road, New Barnet, Herts.

For further Details and Technical Help—phone 01-441 2922

For extra speed phone your order on Barclay or Access Cards

Shop hours 10 a.m.-7 p.m.

teleplay

## GLOUGESTER INDUSTRIAL SALES AND AUCTIONS LTD

Eastington Trading Estate, Nr. Stonehouse Gloucester

Tel: STONEHOUSE 4118

(M.5. MOTORWAY-EXIT No. 13)

We hold regular monthly Auction Sales of mostly New Electronic and Electrical Goods consisting of Transistors, Triacs, Integrated Circuits, Diodes, Capacitors and Resistors, together with Fractional Motors, Transformers, Power Packs, etc. etc. Phone or write to be put on our Auction Mailing List.

Why not get in touch with our Mr. Jack Bailey and enquire about our terms for the disposal of your surplus stocks etc. through our Auctions.





# Marshall's

Come and get a great deal

Call in and see us 9-5.30 Mon-Fri 9-5.00 Sat  
Express Mail Order Tel orders on credit cards £10 min.  
Trade and export enquiries welcome


A. Marshall (London) Ltd, Dept: PW London: 40-42 Cricklewood Broadway, NW2 3ET Tel: 01-452 0161 Telex: 21492 & 325 Edgware Road, W2 Tel: 01-723 4242. Glasgow: 85 West Regent Str, G2 2QD Tel: 041-332 4133. Bristol: 1 Straits Parade, Fishponds Road, BS16 2LX Tel: 0272 654201

2N929	0-37	2N3417	0-25	2N4082	0-20	2N9245	0-37	AF108	0-89	BC182L	0-15
2N930	0-37	2N3439	0-25	2N4121	0-21	2N9246	0-44	AF109	0-82	BC183A	0-12
2N1101	0-32	2N3441	0-22	2N4122	0-21	2N9247	0-44	AF114	0-78	BC183LA	0-13
2N1303	0-86	2N3442	0-45	2N4123	0-19	2N9248	0-44	AF115	0-70	BC184	0-12
2N1105	0-80	2N3455	0-25	2N4124	0-19	2N9401	0-44	AF118	0-70	BC184L	0-13
2M1801	0-35	2N3566	0-25	2N4225	0-19	2N5418	1-05	AF124	0-70	BC205	0-15
2N1613	0-35	2N3587	0-25	2N4226	0-19	2N5447	0-16	AF139	0-75	BC212A	0-17
2N1637	0-72	2N3588	0-17	2N4235	1-35	2N5448	0-16	AF200	0-70	BC212LA	0-18
2N1890	0-29	2N3589	0-30	2N4236	1-85	2N5449	0-38	AF201	1-30	BC213B	0-16
2N1883	0-34	2N3627	0-40	2N4237	1-85	2N5457	0-31	AF239	0-70	BC213LA	0-17
2N1991	1-10	2N3682	0-25	2N4240	1-70	2N5458	0-35	AF240	1-25	BC214	0-17
2N1893	0-30	2N3683	0-29	2N4250	0-20	2N5553	0-63	AF279	0-88	BC234L	0-18
2N194	0-42	2N3702	0-14	2N4260	0-32	2N5890	0-55	AF280	0-85	BC237B	0-15
2N2217	0-55	2N3703	0-14	2N4264	0-32	2N6122	0-44	AF281	1-35	BC238B	0-13
2N2218	0-25	2N3704	0-14	2N4268	0-32	2N6123	0-48	AF282	1-35	BC239C	0-17
2N2219	0-36	2N3705	0-14	2N4269	0-32	2N6124	0-45	AF283	1-35	BC239E	0-17
2N2221	0-23	2N3707	0-14	2N4287	0-32	2N6125	0-47	BC108	0-16	BC237A	0-18
2N2222	0-23	2N3707	0-14	2N4288	0-32	2N6126	0-45	BC109	0-16	BC238B	0-24
2N2270	0-45	2N3708	0-12	2N4302	0-31	2N6127	0-30	BC115	0-22	BC239B	0-18
2N2398	0-27	2N3709	0-12	2N4303	0-33	2N7303	3-85	BC114	0-22	BC281A	0-25
2N2399	0-27	2N3710	0-12	2N4342	0-60	40232	0-80	BC115	0-22	BC282B	0-25
2N2483	0-36	2N3711	0-12	2N4401	0-20	40311	0-55	BC118	0-22	BC283B	0-25
2N2484	0-36	2N3712	0-12	2N4402	0-20	40312	0-55	BC135	0-22	BC284B	0-18
2N2485	0-36	2N3714	1-35	2N4403	0-20	40383	1-43	BC135	0-22	BC287B	0-18
2N2486	1-10	2N3716	1-70	2N4403	0-20	40389	0-70	BC138	0-21	BC288B	0-18
2N2904	0-31	2N3794	0-21	2N4822	0-83	40408	0-82	BC137	0-22	BC290C	0-19
2N2905	0-31	2N3819	0-36	2N4870	0-59	40440	0-78	BC138	0-44	BC297	0-22
2N2906	0-25	2N3820	0-39	2N4871	1-58	40912	1-70	BC140	0-39	BC328	0-29
2N2907	0-23	2N3821	0-35	2N4901	1-85	40994	0-80	BC141	0-35	BC337	0-29
2N2923	0-17	2N3827	0-27	2N4902	1-85	40995	0-80	BC142	0-35	BC414	0-17
2N2924	0-17	2N3854A	0-30	2N4902	1-85	40973	0-30	BC147	0-32	BC415	0-16
2N2925	0-19	2N3855	0-30	2N4903	1-75	AC120	0-48	BC148	0-15	BC416	0-17
2N3011	0-37	2N3856A	0-19	2N4904	1-85	AC127	0-48	BC149	0-15	BC417A	0-13
2N3020	0-25	2N3858A	0-20	2N4905	2-40	AC128	0-48	BC153	0-39	BC447B	0-13
2N3063	0-76	2N3859A	0-22	2N4921	1-40	AC131	0-45	BC154	0-39	BC448	0-13
2N3064	0-72	2N3860	0-18	2N4922	1-40	AC132	0-48	BC157A	0-16	BC449	0-14
2N3065	0-76	2N3861	1-85	2N5087	0-30	AC133	0-58	BC158B	0-17	BC450	0-13
2N3108	0-76	2N3901	0-30	2N5088	0-30	AC135K	0-58	BC159B	0-15	BC459	0-15
2N3133	0-56	2N3904	0-18	2N5089	0-30	AC176	0-54	BC180	0-38	BCY54	2-40
2N3242	0-68	2N3905	0-18	2N5129	0-42	AC176K	0-90	BC187B	0-13	BCY58	0-27
2N3290	0-25	2N3906	0-16	2N5130	0-22	AC187	0-59	BC188B	0-13	BCY70	0-21
2N3301	0-49	2N3982	0-85	2N5131	0-22	AC187K	0-85	BC199B	0-13	BCY71	0-21
2N3302	0-39	2N4031	0-65	2N5137	0-22	AC188	0-54	BC170B	0-18	BCY72	0-21
2N3392	0-17	2N4002	0-30	2N5143	0-22	AC188K	0-85	BC171B	0-17	BCY78	0-42
2N3394	0-17	2N4033	0-85	2N5190	0-58	ACV17	1-80	BC172C	0-15	BD121	2-20
2N3397	0-19	2N4036	0-72	2N5190	0-85	ACV22	0-85	BC173C	0-17	BD131	0-33

AY-3-8900	0-50	CA3082	3-75	LM341P248-80	LM923	0-50	LM78L05CZ	SN78018KE	1-80
CA3000	3-30	CA3085	1-10	LM348N	0-95	LM1303N	1-15	SN78033N1	1-80
CA3001	4-25	CA3088	3-80	LM358N	0-60	LM1304N	1-32	SN78033N2	1-80
CA3002	3-30	CA3070	1-90	LM360N	3-00	LM1305N	1-32	SN78033N3	1-30
CA3003	2-50	CA3071	1-90	LM370N	3-00	LM1307N	1-22	SN78033N4	1-30
CA3006	4-80	CA3072	1-90	LM371M	2-35	LM1310N	2-10	SN78033N5	1-30
CA3007	4-15	CA3075	1-70	LM350K	0-45	LM1351N	1-30	SN78033N6	1-30
CA3008	2-35	CA3076	1-12	LM373N	3-35	LM1458N	0-45	SN78033N7	1-30
CA3019	1-85	CA3080	1-85	LM374N	3-35	LM1498N	1-87	SN78033N8	1-30
CA3021	1-85	CA3082A	1-10	LM375N	2-40	LM1499N	1-84	SN78033N9	1-30
CA3014	2-20	CA3086	0-50	LM378A	4-25	LM1812N	0-20	SN78033N10	1-30
CA3018	0-75	CA3088F	1-87	LM380NS	0-90	LM1829N	1-15	SN78033N11	1-30
CA3018A	1-10	CA3089E	2-99	LM380N141	0-80	LM1829N	1-15	SN78033N12	1-30
CA3020	2-50	CA3090A	4-40	LM381AN	2-70	LM1829N	1-15	SN78033N13	1-30
CA3021	2-50	CA3130	1-86	LM381N	1-80	LM1841N	1-80	SN78033N14	1-30
CA3022	2-50	LOBST1	2-25	LM382N	1-37	LM1841N	1-80	SN78033N15	1-30
CA3023	2-20	LM114H	2-75	LM384N	1-35	LM1849N	1-90	SN78033N16	1-30
CA3026	0-90	LM301AH	5-0	LM388N	4-90	LM1889N	4-90	SN78033N17	1-30
CA3028A	0-90	LM301B	5-0	LM387N	1-18	LM2907N	0-80	SN78033N18	1-30
CA3028B	0-90	LM301C	5-0	LM388N	1-18	MC1495L	5-10	SN78033N19	1-30
CA3029B	1-25	LM304	2-80	LM389N	1-90	MC1495L	5-10	SN78033N20	1-30
CA3029A	0-80	LM308H	1-20	LM389N	1-90	MC1495L	5-10	SN78033N21	1-30
CA3033	1-50	LM308N	0-45	LM389N	1-90	MC1495L	5-10	SN78033N22	1-30
CA3030A	2-20	LM309KC	1-95	LM389N	1-90	MC1495L	5-10	SN78033N23	1-30
CA3033	3-75	LM317K	3-35	LM389N	1-90	MC1495L	5-10	SN78033N24	1-30
CA3034	2-70	LM318N	2-15	LM389N	1-90	MC1495L	5-10	SN78033N25	1-30
CA3035	1-95	LM320T	2-15	LM389N	1-90	MC1495L	5-10	SN78033N26	1-30
CA3036	1-25	LM320T12	1-15	LM389N	1-90	MC1495L	5-10	SN78033N27	1-30
CA3038	2-60	LM320T12	1-15	LM389N	1-90	MC1495L	5-10	SN78033N28	1-30
CA3038A	0-70	LM320T24	1-15	LM389N	1-90	MC1495L	5-10	SN78033N29	1-30
CA3039	4-11	LM300MP	5-0	LM389N	1-90	MC1495L	5-10	SN78033N30	1-30
CA3040	3-75	LM320P	2-15	LM389N	1-90	MC1495L	5-10	SN78033N31	1-30
CA3041	1-85	LM320P12	1-15	LM389N	1-90	MC1495L	5-10	SN78033N32	1-30
CA3042	1-85	LM320P15	1-15	LM389N	1-90	MC1495L	5-10	SN78033N33	1-30
CA3043	2-20	LM320MP15	1-15	LM389N	1-90	MC1495L	5-10	SN78033N34	1-30
CA3045	1-50	LM320MP24	1-15	LM389N	1-90	MC1495L	5-10	SN78033N35	1-30
CA3046	0-70	LM320P	2-15	LM389N	1-90	MC1495L	5-10	SN78033N36	1-30
CA3047	2-20	LM320P	2-15	LM389N	1-90	MC1495L	5-10	SN78033N37	1-30
CA3047A	3-70	LM320K	0-95	LM389N	1-90	MC1495L	5-10	SN78033N38	1-30
CA3048	2-48	LM320K	0-95	LM389N	1-90	MC1495L	5-10	SN78033N39	1-30
CA3049	1-85	LM340T	5-88	LM389N	1-90	MC1495L	5-10	SN78033N40	1-30
CA3050	2-86	LM340T120	88	LM389N	1-90	MC1495L	5-10	SN78033N41	1-30
CA3051	1-83	LM340T150	88	LM389N	1-90	MC1495L	5-10	SN78033N42	1-30
CA3052	1-78	LM340T240	88	LM389N	1-90	MC1495L	5-10	SN78033N43	1-30
CA3053	0-77	LM341P5	8-80	LM389N	1-90	MC1495L	5-10	SN78033N44	1-30
CA3054	1-10	LM341P10	8-80	LM389N	1-90	MC1495L	5-10	SN78033N45	1-30
CA3059	2-18	LM341P150	88	LM389N	1-90	MC1495L	5-10	SN78033N46	1-30

OUR NEW 1978 CATALOGUE IS AVAILABLE NOW!  
LOTS OF NEW PRODUCTS AND IDEAS.  
PRICE 45p POST PAID OR 35p TO CALLERS.

Prices correct as at March 1978. All prices include VAT, p & p 40p.



**TRAMPUS ELECTRONICS LTD., 58-60 GROVE ROAD, WINDSOR, BERKS. SL4 1NS. TELEPHONE WINDSOR (07535) 3425.**

Cash and cheque orders over £5 post free. Credit cards by post or phone £5 min. Post & packing 20p. C.W.O. add VAT to prices marked \* 8%, others 12½%. Free price list of our full range send addressed envelope. Quote this Ad, as prices may change. All devices to makers specifications.

Normally 24 hour turn around on orders for ex stock product.

<b>FULL SPEC PAKS £1</b>	
PAK A: 12 red LEDs	£1*
B: 5 x 741 B PIN	£1*
C: 4 x 2N3055 TO3	£1*
PAK D: 12 x BC109	£1*
PAK E: 7 x BFY51	£1*
H: 7 x 2N3695FET	£1*
K: 40 x 2N4140	£1*
M: 4 x 2N412A NPN/PNP	£1*
PAK P: 50 x CA81/91	£1*
PAK R: 20 x P/BC109	£1*
PAK S: 14 x BC107	£1*
PAK T: 14 x BC108	£1*
T: 10 x BD135 Type	£1*
V: 50 x 5 mfd 50V	£1*
X: 4 x 555 Timer	£1*
Z: 20 x PNP 7302 Type	£1*

Y: 4 x LM301/14P	£1*
U: 4 x 1A 50V SCR	£1
<b>NEW PAK O: 50 x 220 mfd 5V</b>	£5
electrolytic	£1

**DEVELOPMENT PARCELS All £5.**

SET 1: 250 x 50V ceramics 0% 10 each	£5
--------------------------------------	----




### EASY BUILD SPEAKER DIY KITS

Specially designed by RT VC for cost conscious hi fi enthusiasts, these kits incorporate two leak simulate enclosures, two 8" 13" x 8" (approx.) woofers, two tweeters and a pair of matching crossovers. Supplied complete with an easy to follow circuit diagram and crossover components.

**£2800**  
STEREO PAIR Input 15 watts rms, 30 watts peak each unit. Cabinet size 20" x 11" x 9 1/2" (approx.).  
SPEAKERS AVAILABLE WITHOUT CABINETS.

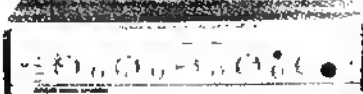It is the units which we supply with the enclosures illustrated. Size 13" x 8" (approx.) woofer. (LMI 2 1/2 app) **£1700** per tweeter, and matching crossover components. stereo pair Power handling 15 watts rms, 30 watts peak. + p & p £3.40



### 20 x 20 WATT STEREO AMPLIFIER

Superb Viscount IV unit in leak finished cabinet. Silver fascia with aluminium rotary controls and push buttons, red mains indicator and stereo jack socket. Function switch for mic, magnetic and crystal pick ups, tape, tuner, and auxiliary Rear panel features two mains outlets, DIN speaker and input sockets, plus fuse. 20 + 20 watts rms, 40 + 40 watts peak.

**£2900**  
p & p £2.50

### 30 x 30 WATT AMPLIFIER KIT

**SPECIAL OFFER:** package price with 30 x 30 kit Specially designed by RT VC for the experienced constructor complete in every detail. Same facilities as Viscount IV amplifier. 60 + 60 peak supplied with 2 GOODMANS COMPACT 12" Bass woofers with crossed alders, 14,000 Gauss magnet, 30 watts R.M.S. handling +3dB approx. tweeters and crossovers p & p £4.00

**NOW AVAILABLE** fully built and tested **£3900** p & p Output 30 + 30 watts rms, 60 + 60 peak. £2.50

### 45 WATT MONO DISCO AMP

**£3500** p & p £2.50  
Size approx. 13 1/2" x 5 1/2" x 6 1/2"  
45 watts rms, 90 watts peak output. Big features include two disc inputs, both low ceramic cartridges, tape input and microphone input, Level mixing controls fitted with integral push pull switches. Independent bass and treble controls and master volume.

### 70 & 100 WATT MONO DISCO AMP

Size approx. 14" x 4" x 10"  
Brushed aluminium fascia and rotary controls.  
Five vertical slide controls: master volume, tape level, mic level, deck level, PLUS INTER DECK FADER for perfect graduated change from record deck No. 1 to No. 2, or vice versa. Pre-fade level control. 70 watt (PFL) lets YOU hear next disc before fading. 100 watt in. VU meter monitors output level.  
Output 100 watts RMS 200 watts peak. 100 watt **£65**

### COMPACT FOR TOP VALUE

These infinite ballie enclosures come to you ready mixed and professionally finished. Each cabinet measures approx. per stereo pair 12" x 9" x 5" deep, and is in wood simulate.

Complete with two 8" (approx.) speakers for maximum power handling of 7 watts. 8Ω. + p & p £2.20

**£850**

SPEAKERS Two models. Duo IIb, teak veneer, 12 watts rms, 24 watts peak, 18 1/2" x 12 1/2" x 7 1/2" (approx.) Duo III, 20 watts rms, 40 watts peak, 27" x 13" x 11 1/2" approx. PER PAIR **£17** Duo III **£52** p & p £7.50

### DECCA 20 WATTS STEREO SPEAKER

stereo pair This matching loudspeaker system is hand made. kit comprises of two 8" diameter approx. base drive unit, with heavy die cast chassis laminated cones with rolled P.V.C surrounds, two 3 1/2" diameter approx. domed tweeters complete with crossover network. 8Ω. £4.00 p & p **£20.00**

### ADD ON STEREO CASSETTE TAPE DECK KIT

Designed for the experienced D.I.Y. man. This kit comprises of a tape transport mechanism, ready built and tested record replay electronics with twin V.U. meters and level control for mating with mechanism. Specifications: Sensitivity Mic, 0.85 mV ± 20K OHMS Din, 40mV ± 400K OHMS Output 300mV RMS per channel, 1KHz from 2K OHMS source. Cross Talk - 30db. Tape Counter - 3 Digit, Resetttable. Frequency Response 40Hz 8KHz ± 6db. Deck Motor 9 Volt DC with electronic speed regulations. Key Functions - Record, Rewind, Fast Forward, Play, Stop & Eject. Opt. extras: Mains transformer to suite **£2.50** + £1 p & p. **£19.95** p & p £2.50

### CHASSIS RECORD PLAYER DECK

Record changer with cue, stereo ceramic cartridge. p & p **£2.00**

BSR MP60 TYPE Single play record deck. less cartridge. p & p **£2.55**

Cartridges to suit above:  
Acos, magnetic stereo **£4.95**  
Ceramic stereo **£1.95**  
BSR automatic record player deck ceramic device and stereo ceramic head, p & p **£9.95**

BSR MP 60 type, complete with magnetic cartridge, diamond stylus, and deluxe plinth and cover. p & p **£4.50**

Home 8 Track cartridge player. This unit will match with the Viscount IV 9" x 8" x 3 1/2"; p & p **£2.50** **£16.50**

### PERSONAL SHOPPERS

STEREO CASSETTE record/replay fully built P.C. board. Used without guarantee (Ex Equipment). **£195**

AM. FR. TUNER P.C.B. with Mullard L.P. 1185. **£9.50**

100K Multiturn Varicap tuning pots, 6 for **£1.00**

MUSIC CENTRE CABINET with hinged smoke acrylic top, finished in natural teak veneers. Size 30 1/2" x 14 1/2" x 7 1/2" approx. **£5.95**

FERGUSON, 3-speed, 7" Hi-Fi tape transport mechanism, complete with top covers. **£15.95**

MULLARD, Bullt power supply. **£3.50**

### RTVC

Order by giving credit card number ONLY.

323 EDGWARE ROAD, LONDON W2  
210 HIGH STREET ACTON W3 6NS  
ALL PRICES INCLUDE VAT AT 12 1/2%  
All items subject to availability. Price correct at 1.3.78 and subject to change without notice.

Personal Shoppers EDGWARE ROAD LONDON W2 Tel: 01-723 8432. 9.30am-5.30pm. Half day Thursday. ACTON Mail Order only. No callers. GOODS NOT DESPATCHED OUTSIDE UK

# You'll learn a lot from the free Heathkit catalogue.




NEW Computer Systems  
Send for a special 16 page brochure.



NEW Bi-directional RF Wattmeter



NEW De-luxe Coin-tracking Metal Locator

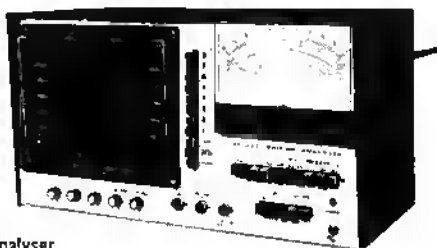

NEW De-luxe 12" CRT Ignition Analyser

The Heathkit catalogue is packed with scores of top quality electronic kits. Educational, practical and fascinating items which you can build yourself.

Send for the catalogue now.

To Heath (Gloucester) Limited,  
Department PW68, Bristol Road,  
Gloucester, GL2 6EE.

Name .....

Address .....

Please tick the literature you want and enclose the appropriate amount in postage stamps.

Heathkit catalogue only  (enclose 11p to cover postage) 16 page computer brochure only  (enclose 20p to cover postage and part costs). N.B. If you are already on the Heathkit mailing list you will automatically receive a copy of the latest catalogue without having to use this coupon.

Soldering iron offer FREE

When you receive your catalogue you'll get details of this free offer worth approximately £4.75.

HEATH  
Schlumberger  
The world's biggest producers of electronic kits.

ACCESS AND BARCLAYCARD WELCOMED


There are Heathkit Electronics Centres at 233 Tottenham Court Road, London (01-636 7349) and at Bristol Road, Gloucester (Gloucester 29451).





# RADIO EXCHANGE LTD.

## NEW ELECTRONIC MASTER KIT

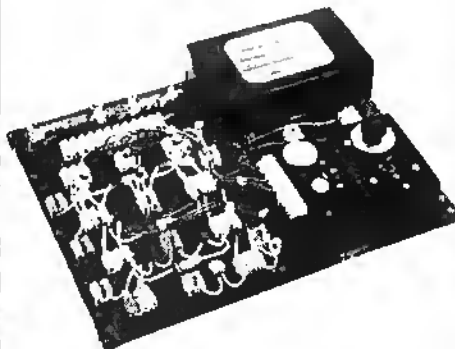

WITH SPECIAL V.H.F. TUNER MODULE TO CONSTRUCT. A completely Solderless Electronic Construction Kit, with ready drilled Bakelite Panels, Nuts, Bolts, Wood Screws etc. Also in the kit: Transistors, Capacitors, Resistors, Pots, Switches, Wire, Sleeving, Knobs, Dials, 5" x 3" Loudspeaker and Speaker Case, Crystal Earpiece, etc. Also ready wound Coils and Ferrite Rod Aerial. These are the Projects you can build with the components supplied with the kit, together with comprehensive Instruction Manual Pictorial and Circuit Diagrams.

**PROJECTS:** V.H.F. Tuner Module ★ A.M. Tuner Module ★ M.W. L.W. Diode Radio ★ Six Transistor V.H.F. Earpiece Radio ★ One Transistor M.W. L.W. Radio ★ Two Transistor Metronome with variable beat control ★ Three Transistor and Diode Radio M.W. L.W. ★ Four Transistor Push Pull Amplifier ★ Eight Transistor V.H.F. Loudspeaker Receiver ★ Variable A.F. Oscillator ★ Jiffy MultiTester ★ Four Transistor and Diode M.W. L.W. Radio ★ A.F. R.F. Signal Injector ★ Five Transistor Push Pull Amplifier ★ Sensitive Hearing Aid Amplifier ★ Three Transistor and Diode Short Wave Radio ★ Signal Tracer ★ Three Transistor Push Pull Amplifier ★ One Transistor Class A Output Stage to drive Loudspeaker ★ Sensitive Transistor Pre-Amp ★ Transistor Tester ★ Sensitive Three Transistor Regenerative Radio ★ Four Transistor M.W. L.W. and Diode Tuner ★ Five Transistor M.W. L.W. Trawler Band Regenerative Radio ★ Five Transistor V.H.F. Tuner ★ Three Transistor Code Practice Oscillator ★ Five Transistor Regenerative Short Wave Radio ★ Four Transistor and two Diodes M.W. L.W. Loudspeaker Radio ★ Seven Transistor M.W. L.W. Radio with Loudspeaker Push Pull output ★ One Transistor Home Broadcaster.

**£14.99 + P & P £1.10**


## NEW ROAMER TEN MODEL R.K.3

MULTIBAND V.H.F. AND A.M. RECEIVER.

13 TRANSISTORS AND SIX DIODES. QUALITY 4" ROUND LOUDSPEAKER.


WITH Multiband V.H.F. section covering Mobiles, Aircraft, T.V. Sound, Public Service Band, Local V.H.F. Stations, etc. and Multiband A.M. section with Airspaced Tuning Capacitor for easier and accurate tuning, covering M.W.1, M.W.2, L.W. Three Short Wave Bands S.W.1, S.W.2, S.W.3 and Trawler Band. Built-in Ferrite Rod Aerial for Medium Wave, Long Wave and Trawler Band, etc., Chrome Plated 7 section Telescopic Aerial, angled and rotatable for peak Short Wave and V.H.F. reception. Push-Pull output using 600mV Transistors. Gain, Wave-Change and Tone Controls. Plus two Slider Switches. Powered by P.P.9—9 volt Battery.

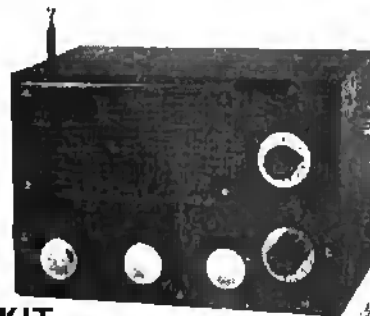Complete kit of parts including carrying strap. Building Instructions and operating Manuals. **£14.79 + P & P £1.10**


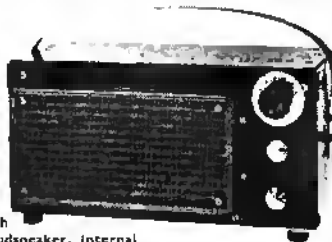
## NEW MODEL R.K.1

Multiband A.M. Receiver. M. W. L. W. Trawler Band and Three Short Wave Bands Seven Transistors and Four Diodes. Push Pull Output stage. 5" x 3" Loudspeaker. Internal Ferrite Rod Aerial. Kit includes all parts to build it up including Carrying Strap, Rubber Feet and ready-drilled Panels. Comprehensive Instruction Manual for stage by stage construction. Uses P.P.9 Nine Volt Battery.




**£8.99 + P & P 90p**
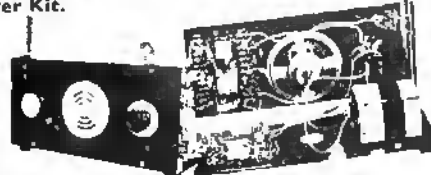
## ELECTRONIC CONSTRUCTION KIT

E.C.K. 2 Self Contained Multi-Band V.H.F. Receiver Kit.


8 transistors and 3 diodes. Push pull output. 3in. loudspeaker, gain control, 7 section chrome plated telescopic aerial V.H.F. tuning capacitor, resistors, capacitors, transistors, etc. Will receive T.V. sound, public service band, aircraft, V.H.F. local stations, etc. Operates from a 9 volt P.P. 7 battery (not supplied with kit)



Complete kit of parts **£7.95 + P & P and Ins. 90p**
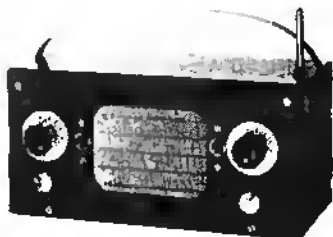
## NEW MODEL R.K.2

MW, LW and Air Band Receiver. Eight Transistors and Four Diodes, 3" Loudspeaker, Telescopic Aerial, Internal Ferrite Rod Aerial. Complete with Carrying Strap, and ready-drilled Panels and all components necessary for construction. A sensitive Receiver with the additional luxury of an Air Band section to pick up Aircraft from many miles away. Full Instruction Manual enables stage by stage construction. Uses P.P.9 and P.P.3 Nine Volt Batteries.



**£9.99 + P & P £1.10**

## EDU-KIT MAJOR COMPLETELY SOLDERLESS ELECTRONIC CONSTRUCTION KIT BUILD THESE PROJECTS WITHOUT SOLDERING IRON OR SOLDER




Complete kit of parts including construction plans Total building costs

**£9.99 + P & P and Ins. £1.10**

- 4 Transistor Earpiece Radio
- Signal Tracer
- Signal Injector
- Transistor Tester NPN—PNP
- 4 Transistor Push Pull Amplifier
- 24 Resistors
- Earpiece
- 2 Slider Switches
- MW/LW/SW Coils
- 21 Capacitors
- 10 Transistors
- 3 12-way Connectors
- 1 Tuning Condenser
- 3 Knobs
- Ready Wound Ferrite Rod
- 6 1/2 yards of wire
- 1 yard of sleeving, etc.
- Batteryless Crystal Radio
- One Transistor Radio
- 2 Transistor Regenerative Radio
- 3 Transistor Regenerative Radio
- Audible Continuity Tester
- Sensitive Pre-Amplifier
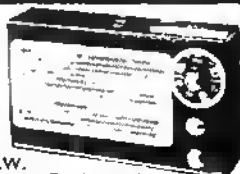
## E.V.6. PLUS ONE

Build this exciting new design. Now with 7 Transistors and 4 diodes. MW/LW. Powered by 9V battery. Ferrite rod aerial, tuning condenser, volume control, and now with 3in. loudspeaker. Attractive case with red speaker grille. Size 9in. x 5 1/2in. x 2 1/2in. approx. All parts including Case and Plans.



Total Building Costs **£6.95 + P & P and Ins. 90p**

## V.H.F. AIR CONVERTER KIT

Build this converter kit and receive the aircraft band by placing it by the side of a radio tuned to medium wave or the VHF band and operating as shown in the instructions supplied free with all parts. Uses a retractable chrome plated telescopic aerial, gain control, V.H.F. tuning capacitor, transistor, etc. All parts including case and plans



**£4.95 + P & P and Ins. 60p**

## TO: RADIO EXCHANGE LTD 61A High Street, Bedford MK40 1SA

Tel.: 0234 52367 REG NO. 768372

● Callers side entrance "Lavelis" Shop.  
● Open 10-1, 2.30-4.30 Mon.-Fri. 9-12 Sat.

I enclose £..... for.....

Name .....

Address .....

..... PW578

**ALL PRICES INCLUDE VAT**

# What did Flemming say to Edison about Antennas in 1912?

We're not sure, but we can be sure that they couldn't have been discussing the merits of the Joystick VFA (Variable Frequency Antenna, 5-30 Mhz). That had to come later. . . so that now, you can have a versatile antenna system that acts as a ground plane right through the six lower amateur bands and on all frequencies in between. Short wave listener and transmitting amateur alike will benefit from a VFA—if you can't hear 'em, you can't work 'em.

**SYSTEM "A" £36.00**

250 w. p.e.p. OR for the SWL.

**SYSTEM "J" £42.60**

500 w. p.e.p. (improved 'Q' on receive).

## PARTRIDGE SUPER PACKAGES

### COMPLETE RADIO STATIONS FOR ANY LOCATION

All Packages feature the World Record Joystick Aerial (System 'A'), with 8ft. feeder, all necessary cables, matching communication headphones. Deliv. Secured our risk. **ASSEMBLED IN SECONDS! BIG CASH SAVINGS!**

**PACKAGE No. 1 £210.55**

As above with R.300 RX. SAVE £17.28!

**PACKAGE No. 2 £195.00**

Is offered with the FRG7 RX. SAVE £12.21!

**PACKAGE No. 3 £177.00**

Here is a lower-price, high-quality package featuring the LOWE SRX30, with all the Partridge extras. SAVE £12.21!

**RECEIVERS ONLY, inclusive delivery, etc.**  
R.300 £184.50 FRG7 £162.00 SRX30 £146.25

All prices are correct at time of going to press and include VAT at 12½% and carriage.



just telephone your card number  
Phone 0843 62535 (ext. 5)  
(or 62839 after office hours)



or write for details, send 9p stamp



5, Partridge House, Prospect Road, Broadstairs, CT10-1LD. (Callers by appointment).

**Random FLASHER UNIT**  
Wired ready for use. Complete with three 100 watt coloured lamps that flash independently at random. **£19.95**

**TWIN BANK 6 LIGHT UNIT**  
(less lamps) LENGTH 14½ inches  
BC Fitting **£11.35**  
E.S. **£11.35**  
Fitting EACH

**Sound to Light MASTER UNIT**  
600 WATTS PER CHANNEL  
**£30.95**  
INCLUDING CHANNEL OUTPUT PLUGS AND MAINS 13V SOCKET

**TYPE A SPOT**  
(less lamp)  
BC Fitting | E.S. Fitting  
**£2.30** EACH **£2.30** EACH

**TYPE B 3 BANK UNIT**  
(Less Lamps)  
BC **£7.99** Fitting EACH | E.S. **£7.99** Fitting EACH

**TWIN BANK 12 LIGHT UNIT**  
Length 31½  
(less lamps)  
BC **£18.50** Fitting EACH | E.S. **£18.50** Fitting EACH

**100 WATT SPOT LAMPS**  
RED, YELLOW, GREEN, BLUE, CLEAR  
3 lamps each **£4.50**  
E.C. or E.S. Fitting

ALL PRICES INCLUDE V.A.T. and POST & PACKING (these prices apply to the United Kingdom only)

**ALBEN ENGINEERING CO. LTD.**  
DEPT. PW THE CRESCENT, WORSTHORNE, BURNLEY, LANCS. Tel: Burnley 20940

Send 20p for illustrated leaflet & price list

THE COMMUNICATIONS RECEIVER THAT HAS IT ALL . . .



# FRG-7

The finest general-coverage synthesised communications receiver on the market

## £173.00 inc. VAT

Also available from us with special 2m converter, all for just an extra £15.00



Phone for details of current stocks, both new and secondhand



**AMATEUR RADIO EXCHANGE**

2 Northfield Road, Ealing, London, W.13.

Tel: 01-579 5311

Easy terms up to 3 years

Credit Card Sales by Telephone

Closed all day Wednesday



# Mini-priced breadboards for maxi-sized projects.


**Experimenter**® low-cost solderless breadboards are the first in the world specially designed for 0.3" and 0.6" pitch DIP's.

They clip together by an exclusive interlocking system in any configuration, (just like dominoes), so you arrange the breadboards to suit your circuit, not vice-versa.


They are precision moulded from durable, flame-retardant plastic, and feature alphanumeric coding for easy circuit building, and non-corrosive, pre-stressed nickel-silver alloy contacts—reliable for well over 10,000 insertions.



EXCLUSIVE INTERLOCKING SYSTEM.

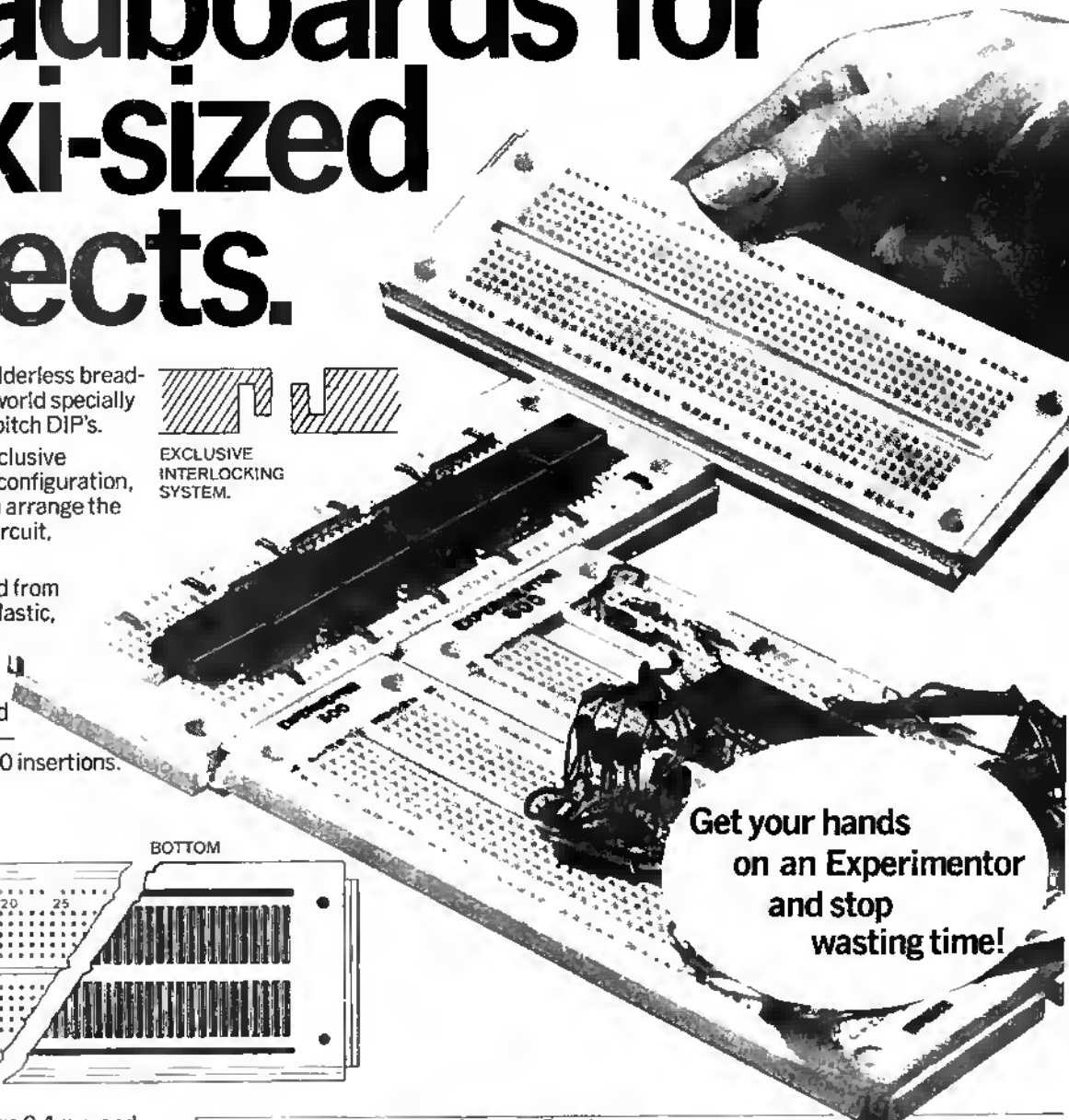

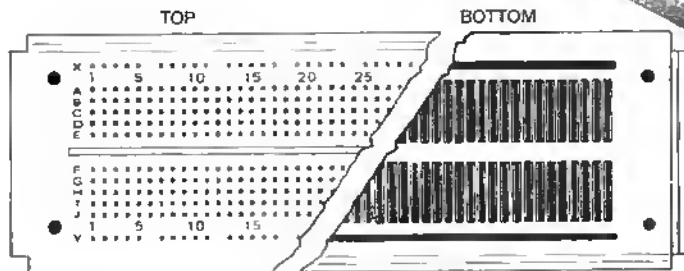Get your hands on an Experimenter and stop wasting time!



Contact resistance is a mere 0.4 mΩ and interterminal capacitance is typically less than 5 pF. The **Experimenter** is usable to over 100 MHz.

**Experimenter 600** and **650** models are ideal for RAM's ROM's and PROM's (0.6" centre IC's) while the **300** and **350** models are for smaller DIP's (0.3" centres). All four models, of course, also take all standard components, the 0.1" grid being compatible with transistors, diodes, LED's, capacitors, resistors, pots—in fact any component with lead sizes between 0.015" and 0.032"



A useful quad bus strip (EXP4B) further

Model	Length"	Width"	Centre channel"	5-way tie points	Bus	Price	All units are 0.330" deep. Prices include VAT (8%) and p & p f UK Orders. Add 5% to all orders outside UK. All prices and specifications correct at the time of going to press.
EXP300	6.0	2.1	0.3	94(470)	2(80)	£7.29	
EXP350	3.6	2.1	0.3	46(230)	2(40)	£4.21	
EXP600	6.0	2.4	0.6	94(470)	2(80)	£7.88	
EXP650	3.6	2.4	0.6	46(230)	2(40)	£4.89	
EXP4B	6.0	1.0	N/A	N/A	4(160)	£3.29	

expands the versatility of the system for the MPU user.

**Experimenter** breadboards can be used alone or mounted on any convenient flat surface, thanks to moulded-in mounting holes and vinyl insulation backing that prevents short circuits. Mount them from the front with 4-40 flathead screws or from the rear with 6-32 self tapping screws.

But however you use them, **Experimenter** breadboards are the quickest and easiest way to build and test circuits.

If you're working on IC's, MPU's, memories,

displays or any other circuits, buy the breadboards that are designed for you.

Ring us (01-890 0762) with your Access, Barclaycard or American Express number and your order will be in the post that ni

Alternatively, send a cheque, or postal order (don't send credit cards!) and it still only takes a few days. Otherwise ask for our complete catalogu



## FANTASTIC SPEAKER OFFER

### TWIN 12" SPEAKER CABINET PLUS PAIR 12" SPEAKERS

of Robust vibration-proof construction. Fitted protective corner pieces. Removable Vynair covered front with silver effect trim. Sunken jack socket with esuchicon at the rear. Pair 12" 20w speakers for wiring in series and front mounting in above supplied to complete the 40 watt unit for lead guitar or P.A.

White stocks last  
Three items  
**£19-95**



Carr. £2 50

## 50 WATT AMPLIFIER SACRIFICE

### Limited stocks of TITAN TA/50A

to be cleared to make way for a re-styled model.

Solid state, 3 sep. controlled inputs plus Master control. Bass, Treble & Presence Controls. Vynide covered cab. with corner protectives. Value £60. Terms: Dep. £7-95 & 8 monthly payments £4-72 (Total £45 71). Matching Cabinets 1 x 12" £29 95, 2 12" £49 95



**£39-95**

## FANE CRESCENDO/12

SUPER 100w SPKR.  
HALF PRICE  
WHILE STOCKS  
LAST



MODEL 12L  
This is basically the 12A with the addition of Linen cone surround. State impedance when ordering

**£29-95** Carr. £1 50

## RSC 100 WATT DISCO SYSTEM



Consisting of  
(1) TWIN T/TABLE CONSOLE with PRE-AMP, and POWER OUTPUT STAGES (2) & (3) PAIR 50 WATT LOUDSPEAKERS including 12" UNITS

AT A FANTASTIC LOW PRICE

Also MONITORING FACILITIES, plus Treble and Bass Controls. Separate Input for 'mike' with vol. control. Black Vynide covered Cabinet with lid. Or Dep £16-49 & 18 monthly pmts. £6-75 (Total £137-99)

**TD23 STEREO VERSION OF ABOVE £125-00** Carr. £3-00

## ALL RSC PRICES INCLUDE VAT

- \* DISCO MAJOR POWER DISCO CONSOLE with integral Power Amplifier.
- \* TWIN FULL SIZE BSR turntables with cueing device.
- \* CARTRIDGES with Diamond Styl.
- \* 3 SEPARATE VOLUME CONTROLS for each turntable and Mic.
- \* CONSOLE COMPLETE WITH LID. FULL HEADPHONE MONITORING FACILITIES

Terms: Deposit £30-00 and 18 fortnightly pmts. £9-80 (Total £206-40) Carr. £4-00

**£169-95**

Also available **200 WATT SYSTEM £199-95** Carr. £4-75

**TD1 DISCO CONSOLE** Incorporating twin BSR type turntables & Sonotone or Acos Cartridges with diamond styl. Separate Vol. controls for each turntable. Also MONITORING FACILITIES, plus Treble and Bass Controls. Separate Input for 'mike' with vol. control. Black Vynide covered Cabinet with lid.

**£119-95**

New Branches at  
**LEEDS, HANLEY and WOLVERHAMPTON**



Barclaycard & Access  
FROM 2 ORDERS quoting  
CARD NUMBER accepted

MAIL ORDERS & EXPORT ENQUIRIES TO:-  
AUDIO BOULE, HENSGOFFER LANE, LEEDS, 18.  
TEL: 0658 877881.

MAIL ORDERS MUST NOT BE SENT TO SHOPS  
TERMS C.O.D. or C.O.D. No. C.O.D. order £3. POSTAGE 80p PER  
ORDER OR AS QUOTED. Phone or Write for FREE CATALOGUE

OPEN ALL DAY SATS (5 Day Week)

Prices correct at 17.3.78 E. & O.E. All items subject to availability

**BRADFORD** 10 North Parade (Closed Wed.). Tel. 25349  
**BIRMINGHAM** 30/31 Great Western Arcade.

**CARLISLE** 8 English Street (Closed Thurs.). Tel. 38744  
**COVENTRY** 71 Shelton St., The Precinct. Tel. 25983  
**DERBY** 97 St. Peter's Street (Closed Wed.). Tel. 41301  
**DARLINGTON** 19 Northgate (Closed Wed.). Tel. 88043  
**DEWBURY** 9/11 Kingsway (Closed Tues.) Tel. 488058  
**DONCASTER** 3 Queensgate, Waterdale Centre. (Closed Thurs.). Tel. 63069  
**EDINBURGH** 101 Lothian Rd. (Closed Wed.). Tel. 229 8501  
**GLASGOW** 326 Argyle St. (Closed Tues.). Tel. 041-248 4158

**HANLEY** Stoke-on-Trent, 44 Piccadilly Tel. 207764

**MULL** 7 Whitefriargate (Closed Thurs.). Tel. 20505

**LEICESTER** 32 High Street (Closed Thurs.). Tel. 58480

\* **LEEDS** 16-18 County (Mecca) Arcade, Briggate (Closed Wed.). Tel. 440609

**LIVERPOOL** TEMPORARILY INOPERATIVE due to serious fire

**LONDON** 238 Edgware Road, W.2 (Closed Thurs.). Tel. 723 1029

\* **MANCHESTER** 60A Oldham Street (Closed Wed.). Tel. 238 2778

**MIDDLESBROUGH** 108 Linthorpe Rd. (Cl. Wed.) Tel. 247095  
**NEWCASTLE UPON TYNE** 59 Grainger St. (Closed Wed.). Tel. 21469

**NOTTINGHAM** 19/19A Market Street (Closed Thurs.). Tel. 48068

**SHEFFIELD** 13 Exchange Street (Castle Mkt. Bldg.) (Closed Thurs.). Tel. 20716

**WOLVERHAMPTON** 6 Wulfrun Way (Closed Thurs.). Tel. 26612

\* **MUSICAL INSTRUMENTS & ACCESSORIES** in stock at these branches.

## J. BIRKETT

### Radio Component Suppliers

25 The Strait, Lincoln LN2 1JF Tel: 20787

**ILLUMINATED EDGEWISE SIGNAL LEVER METERS** at £1.35 each  
**100-0-100uA TUNING METERS** 1 1/2" x 1 1/2" at 90p each.  
**TRANSFORMERS** 240 volt, 24v tapped at 14 volt 1 amp at £1.25 (25p P&P).  
**TRANSFORMERS** 20 volt, 1 amp twice, 10 volt 1 amp twice @ £4.50 (95p P&P).

**AUDIBLE ALARM SYSTEM** with Transistors and I.C. Made for Car Seat Belts No Details at 75p.

**GENERAL PURPOSE P CHANNEL FETs** with circuits 10 for 75p.

**ITT CAPACITORS PNT-2R.** 1uf 100v.w. at 20p doz.  
**20 PHOTO TRANSISTOR AND DARLINGTONS** Assorted untested for £1.

**SMALL R.T. TELESCOPIC AERIALS** for 60p.  
**DUAL 100K LIN WIRE WOUND POTENTIOMETERS** at 50p.  
**COMPRESSION TRIMMERS** 10pf, 30pf, 50pf, 500pf, 1000pf. All at 10p each.

**30S PRE-AMPLIFIER I.C. TYPE TAA 350** with circuit @ 35p.  
**50 BC 107-8-9 TRANSISTORS** Assorted untested for 57p.  
**100 MULLARD C280 CAPACITORS** Assorted for 57p.

**6 LIFT TELESCOPIC AERIALS** at 60p each.  
**LARGE FLANGE SOLDER-IN FEED THRU'S** at 6 for 18p.

**AUDIO I.C. LM 380** with circuits at 80p.  
**5-5 MHz CERAMIC FILTERS** at 27p each.  
**MINIATURE CERAMIC TRIMMERS** 2.5 to 6pf, 0 to 8pf, 3 to 10pf, 4-7 to 20pf, 0 to 30pf. All at 10p each.

**200 ASSORTED 1/4, 1/2 RESISTORS** for 75p.  
**ERIE REDCAP SUB-MINIATURE 0-01uf 100v.w. CAPACITORS** @ 5p each.

**T.V. S.A.W. FILTERS** Untested 3 for 35p.  
**CLOCK P.C. BOARDS** with Buzzer, Bridge Rectifier, Mercury Switch Transistors etc. No data Brand New @ £1.

**BAW61 HIGH SPEED DIODES** at 12 for 35p.  
**SUB-MINIATURE 4-7uf 10v.w. TANTALUM CAPACITORS** 5p ea. 6 for 25p.

**12 VHF BRANDED FETs** Assorted for £1.  
**COIL FORMERS** 3/16" dia. with core at 5p ea. 6 for 25p.  
**COIL FORMERS** 3/16" less core, 100 for £1.

**AUDIO PRE-AMPLIFIER I.C. TAA 435** with circuit @ 45p.  
**1 GHz STRIPLINE NPN TRANSISTORS** at £1 each.  
**MCMURDO 8 PIN PLUG** @ 20p, **8 PIN SOCKET** @ 20p, **COVERS** @ 15p.

**RCA VERSION OF BFY 96 TRANSISTORS** @ 55p each.  
**VERNITRON FM4 10-7 MHz CERAMIC FILTER** @ 50p.  
**MULLARD ELECTROLYTICS** 2240uf 40v.w. @ 40p, 4500uf 25v.w. @ 40p, 5000uf 10v.w. @ 15p, 6400uf 16v.w. @ 25p, 8000uf 10v.w. @ 25p

Please add 20p for post and packing, unless otherwise stated, on UK orders under £2. Overseas orders at cost.

## BARGAIN PARCELS SAVE POUNDS

Huge quantities of electronic components must be cleared as space required. 1000's of capacitors, resistors, transistors. Ex equipment panels etc. covered in valuable components. No time to sort. Must sell by weight 7 lbs-£4-95; 14lbs-£7-95; 28lbs-£12-95; 56lbs-£29-95; 112 lbs-£39-95.

**Handy Packs**

4 aluminium boxes 123 x 44 x 38 mm ideal for signal meters, etc. £1.00.

Miniature Edgewise Panel Meters

200: A FSD. £1.20

100 miniature reed switches ideal for burglar alarms, model railways, etc. £3-30.

6 x 6 gold 12 volt reed relays on board £2-45.

High quality computer panels encased in top grade components 5 lbs £4-75. 10 lbs £8-95.

**DE LUXE FIBRE GLASS PRINTED CIRCUIT ETCHING KITS**

Includes 150 sq. ins. copper clad 1/8 board, 1 lb ferric chloride, 1 Dalo etch resist pen, abrasive cleaner, 2 mini drill bits, etch tray and instructions only £5-30.

150 sq. in. fibre glass board £2-00

Dalo pen. 90p.

1 lb ferric chloride to mill spec. £1-25.

5 lbs ferric chloride to mill spec. £5-00.

Instruction sheet 20p

Miniature mains transformers, fully shrouded. 240V. In 5-0-6V at 100ma out.

Ex new equipment. Complete with mains lead and plug on input and short leads on output 90p.

**Semiconductor Bargains**

TH2 Thermistors 10 for £1.

100 new & marked silicon and germanium transistors including BC148, BF184, BC183, etc. £3-95.

200 new & marked transistors including 2N3055, AC128, BFY50, BD131, etc. £6-85

100 mixed diodes IN4148, etc. £1-50.

100 mixed diodes including zener, power and bridge types £3-50.

Bridge rectifier 100v 2.5 amp 4 for £1.

Brand new ITT 25 kv triplers for Decca Bradford chassis £2-50. 5 for £10.

50 Germanium diodes, ideal for crystal sets, etc. £1.

Miniature Vernitron FM4 10-7 MHz Ceramic Filter 50p each 3 for £1.

New U.M.F. transistor TV tuners 4 push-button type £3-50

Hardware Packs each containing 100's of items including BA nuts and bolts, Nylon, Self-tapping, Palsdriye, "pin" clips, Cable clamps, Fuse holders, Spire nuts etc., £1 per pound.

Aluminium TV coax plugs 10 for £1-00

Miniature 5K log pots with s/p switch 4 for £1.

**DON'T LET YOUR ENVIRONMENT DEHYDRATE YOU OR YOUR POSSESSIONS.** Buy a Honeywell Humidity Controller. Compact (3 1/2" x 1 1/2" x 1 1/2"), wide range of control, adjustable by 1/2" spindle with flat. Contact Rating 3-75A @ 240VAC, 7-5A @ 120VAC. Ideal for Greenhouses, Centrally Heated Homes, Offices, etc. Build your own Humidifiers or Dehydration Alarms. £4-50 ea. 4 for £2.

New Miniature FM Frontends BS-108MHz, 10-7MHz. I.F. or with Integral Tuning-gang £2-50.

BR101 full spec. 5 for £1-00.

TBA 120A 50p each

SN 75115N £1 each.

20 mm anti-surge fuses your selection

600MA to 3-15A. 12 for £1-00

**Component Bargains**

300 mixed resistors 1/4 & 1/2 watt £1-50

300 modern mixed caps most types £1-30

125 mixed resistors mostly 1/2 & 2 watt. £1.

100 mixed polyester caps £2-20.

100 mixed modern miniature and ceramic plate caps £1-00.

100 mixed wirewounds £2-20.

300 printed circuit resistors £1-00.

25 mixed pots & presets £1-50.

100 High wattage resistors, wirewound etc. £2-20.

Modern Vertical Presets with slotted knobs, 220Q, 470K, 500K, 1 MEG, 25 for £1, 4 Packs £2-50.

Small 5Q wirewound Horiz. Convergence Preset with Knob. 10 for £1.

Microtrols 1 watt Audio I.C. MFC 8010 complete with circuits and data £1-10 each, 3 for £4.

100K Stereo Slider Pots Modern, slim type. 50p each, 3 for £1.

Double Gang A.M. Tuning Condensars with integral 100K pot. For varicap tuning on VHF as used in modern Thorn music centres. £1.

40p P & P ON ALL ABOVE ITEMS. SEND CHEQUE OR POSTAL ORDER WITH ORDER TO SENTINEL SUPPLY, DEPT PW

149A BROOKMILL ROAD, DEPTFORD, SE8

CALLERS BY APPOINTMENT ONLY



# 15-240 Watts!

## HY5 Preamplifier

The HY5 is a mono hybrid amplifier ideally suited for all applications. All common input functions (mag Cartridge, tuner, etc) are catered for internally. The desired function is achieved either by a multi-way switch or direct connection to the appropriate pins. The internal volume and tone circuits merely require connecting to external potentiometers (not included). The HY5 is compatible with all I.L.P. power amplifiers and power supplies. To ease construction and mounting a P.C. connector is supplied with each pre-amplifier.

**FEATURES:** Complete pre-amplifier in single pack—Multi-function equalization—Low noise—Low distortion—High overload—Two simply combined for stereo.

**APPLICATIONS:** Hi-Fi—Mixers—Disco—Guitar and Organ—Public address

**SPECIFICATIONS:**

**INPUTS:** Magnetic Pick-up 3mV; Ceramic Pick-up 30mV; Tuner 100mV; Microphone 10mV;

**Auxiliary** 3-100mV; input impedance 4.7k $\Omega$  at 1kHz;


**OUTPUTS:** Tape 100mV; Main output 500mV R.M.S.

**ACTIVE TONE CONTROLS:** Treble  $\pm$  12dB at 10kHz; Bass  $\pm$  at 100Hz.

**DISTORTION:** 0.1% at 1kHz. Signal/Noise Ratio 65dB.

**OVERLOAD:** 30dB on Magnetic Pick-up. **SUPPLY VOLTAGE**  $\pm$  18-30V.

**Price** £5.22 + 65p VAT P&P free.

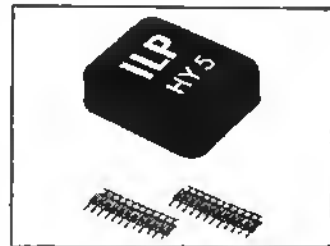

## HY30 15 Watts into 8 $\Omega$

The HY30 is an exciting New kit from I.L.P. It features a virtually indestructible I.C. with short circuit and thermal protection. The kit consists of I.C., heatsink, P.C. Board, 4 resistors, 6 capacitors, mounting kit, together with easy to follow construction and operating instructions. This amplifier is ideally suited to the beginner in audio who wishes to use the most up-to-date technology available.

**FEATURES:** Complete Kit—Low Distortion—Short, Open and Thermal Protection—Easy to Build.

**APPLICATIONS:** Updating audio equipment—Guitar practice amplifier—Test amplifier—audio oscillator.

**SPECIFICATIONS:**

**OUTPUT POWER** 16W R.M.S. into 8 $\Omega$ ; **DISTORTION** 0.1% at 1.5W.

**INPUT SENSITIVITY** 500mV. **FREQUENCY RESPONSE** 10Hz-10kHz—3dB.

**SUPPLY VOLTAGE**  $\pm$  18V.

**Price** £5.22 + 65p VAT P&P free.



## HY50 25 Watts into 8 $\Omega$

The HY50 leads I.L.P.'s total integration approach to power amplifier design. The amplifier features an integral heatsink together with the simplicity of no external components. During the past three years the amplifier has been refined to the extent that it must be one of the most reliable and robust High Fidelity modules in the World.

**FEATURES:** Low Distortion—Integral Heatsink—Only five connections—7 amp output transistors—No external components

**APPLICATIONS:** Medium Power Hi-Fi systems—Low power disco—Guitar amplifier

**SPECIFICATIONS:** **INPUT SENSITIVITY** 500mV


**OUTPUT POWER** 25W RMS into 8 $\Omega$  **LOAD IMPEDANCE** 4-16 $\Omega$  **DISTORTION** 0.04% at 25W

at 1kHz

**SIGNAL/NOISE RATIO** 75dB **FREQUENCY RESPONSE** 10Hz-45kHz—3dB

**SUPPLY VOLTAGE**  $\pm$  25V **SIZE** 105 80 25mm

**Price** £6.82 + 65p VAT P&P free.

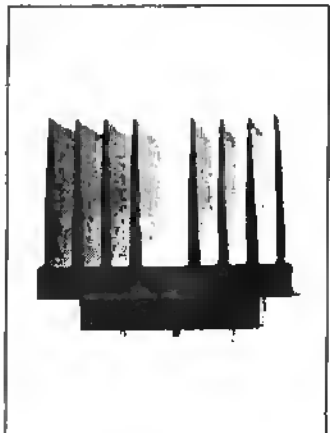

## HY120 60 Watts into 8 $\Omega$

The HY120 is the baby of I.L.P.'s new high power range. Designed to meet the most exacting requirements including load line and thermal protection this amplifier sets a new standard in modular design.

**FEATURES:** Very low distortion—Integral heatsink—Load line protection—Thermal protection—Five connections—No external components

**APPLICATIONS:** Hi-Fi—High quality disco—Public address—Monitor amplifier—Guitar and organ

**SPECIFICATIONS:**

**INPUT SENSITIVITY** 500mV.

**OUTPUT POWER** 60W RMS into 8 $\Omega$  **LOAD IMPEDANCE** 4-16 $\Omega$  **DISTORTION** 0.04% at 60W


at 1kHz

**SIGNAL/NOISE RATIO** 90dB **FREQUENCY RESPONSE** 10Hz-45kHz—3dB

**SUPPLY VOLTAGE**  $\pm$  35V

**SIZE** 114 50 85mm

**Price** £15.84 + £1.27 VAT P&P free.

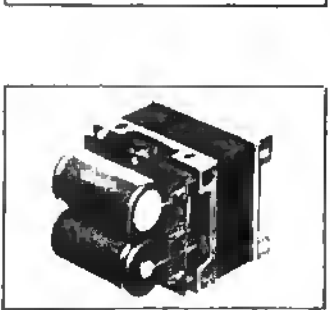

## HY200 120 Watts into 8 $\Omega$

The HY200 now improved to give an output of 120 Watts has been designed to stand the most rugged conditions such as disco or group while still retaining true Hi-Fi performance.

**FEATURES:** Thermal shutdown—Very low distortion—Load line protection—Integral heatsink—No external components

**APPLICATIONS:** Hi-Fi—Disco—Monitor—Power slave—Industrial—Public Address

**SPECIFICATIONS:**

**INPUT SENSITIVITY** 500mV

**OUTPUT POWER** 120W RMS into 8 $\Omega$  **LOAD IMPEDANCE** 4-16 $\Omega$  **DISTORTION** 0.08% at 100W

at 1kHz

**SIGNAL/NOISE RATIO** 90dB **FREQUENCY RESPONSE** 10Hz-45kHz—3dB

**SUPPLY VOLTAGE**  $\pm$  35V

**SIZE** 114 50 85mm

**Price** £23.32 + £1.67 VAT P&P free.

## HY400 240 Watts into 4 $\Omega$

The HY400 is I.L.P.'s "Big Daddy" of the range producing 240W into 4 $\Omega$ ! It has been designed for high power disco address applications. If the amplifier is to be used at continuous high power levels a cooling fan is recommended. The amplifier includes all the qualities of the rest of the family to lead the market as a true high power hi-fidelity power module.

**FEATURES:** Thermal shutdown—Very low distortion—Load line protection—No external components.

**APPLICATIONS:** Public address—Disco—Power slave—Industrial

**SPECIFICATIONS:**

**OUTPUT POWER** 240W RMS into 4 $\Omega$  **LOAD IMPEDANCE** 4-16 $\Omega$  **DISTORTION** 0.1% at 240W

at 1kHz

**SIGNAL NOISE RATIO** 94dB **FREQUENCY RESPONSE** 10Hz-45kHz—3dB

**SUPPLY VOLTAGE**  $\pm$  35V

**INPUT SENSITIVITY** 500mV **SIZE** 114 100 85mm

**Price** £32.17 + £2.37 VAT P&P free.

## POWER SUPPLIES

PSU58 suitable for two HY30's £5.22 plus 65p VAT. P/P free.

PSU59 suitable for two HY50's £6.82 plus 65p VAT. P/P free.

PSU70 suitable for two HY120's £15.75 plus £1.19 VAT. P/P free.

PSU90 suitable for one HY200 £12.95 plus £1.61 VAT. P/P free.

PSU180 £23.18 + £1.85 VAT.

B1 £0.48 + £0.06 VAT.

TWO YEARS' GUARANTEE ON ALL OUR PRODUCTS

I.L.P. ELECTRONICS LTD., GROSSLAND HOUSE, NACKINGTON, CANTERBURY, KENT, CT4 7AD.

**I.L.P. ELECTRONICS LTD.,**  
GROSSLAND HOUSE, NACKINGTON,  
CANTERBURY, KENT, CT4 7AD.

Please Supply \_\_\_\_\_  
Total Purchase Price \_\_\_\_\_  
I Enclose Cheque  Postal Orders  Money Order   
Please debit my Access account  Barclaycard account   
Account number \_\_\_\_\_  
Name and Address \_\_\_\_\_  
Signature \_\_\_\_\_

# BOOKS AND COMPONENTS

## BOOKS BY BABANI

Purchase books to the value of £5.00 from the list below and choose any 80p pack from this page FREE.

BP2 Handbook of Radio, TV & Industrial & Transmuting Tube & Valve Equivalents 60p†

BP3 Handbook of Tested Transistor Circuits 40p†

BP6 Engineers and Machinists Reference Tables 40p†

BP7 Radio & Electronic Colour Codes and Data 15p†

BP10 Modern Crystal and Transistor Set Circuits for beginners 95p†

BP15 Constructors Manual of Electronic Circuits for the Home 60p†

BP16 Handbook of Electronic Circuits for the Amateur Photographer 60p†

BP18 Boys and Beginners Book of Practical Radio and Electronics 80p†

BP22 79 Electronic Novelty Circuits 75p†

BP23 First book of Practical Electronic Projects 75p†

BP24 52 Projects Using IC741 (or equivalents) 75p†

BP26 Radio Antenna Handbook for Long Distance Reception and Transmission 85p†

BP27 Giant Chart of Radio Electronic Semiconductor and Logic Symbols 80p†

BP29 Major Solid State Audio Hi-Fi Construction Projects 85p†

BP32 How to Build Your Own Metal & Treasure Locators 85p†

BP34 Practical Repair & Renovation of Colour TVs 95p†

BP35 Handbook of IC Audio Pre-amplifier & Power Amplifier Construction 95p†

BP36 50 Circuits Using Germanium, Silicon & Zener Diodes 75p†

BP37 50 Projects Using Relays, SCR's and TRIACS 95p†

BP39 50 (FET) Field Effect Transistor Projects 95p†

129 Universal Gram-motor Speed Indicator 80p†

160 Coil Design and Construction Manual 75p†

161 Radio, TV and Electronics Data Book 60p†

196 AF-RF Reactance—Frequency Chart for Constructors 15p†

202 Handbook of Integrated Circuits (ICs) Equivalents and Substitutes 75p†

205 First Book of Hi-Fi Loudspeaker Enclosures 75p†

213 Electronic Circuits for Model Railways 85p†

214 Audio Enthusiasts Handbook 85p†

216 Electronic Gadgets and Games 85p†

217 Solid State Power Supply Handbook 85p†

219 Solid State Novelty Projects 85p†

220 Build Your Own Solid State Hi-Fi and Audio Accessories 85p†

222 Solid State Short Wave Receivers for Beginners 95p†

223 50 Projects Using IC CA3130 95p†

224 50 CMOS IC Projects 95p†

225 A Practical Introduction to Digital IC's 95p†

226 How to Build Advanced Short Wave Receivers 95p†

RCC Resistor Colour Code Disc Calculator 10p†

## BOOKS BY NEWNES

No. 229 Beginners Guide to Electronics Price £2.25†

No. 230 Beginners Guide to Television Price £2.25†

No. 231 Beginners Guide to Transistors Price £2.25†

No. 233 Beginners Guide to Radio Price £2.75†

No. 234 Beginners Guide to Colour Television Price £2.25†

No. 235 Electronic Diagrams Price £1.80†

No. 236 Electronic Components Price £1.06†

No. 237 Printed Circuit Assembly Price £1.06†

No. 238 Transistor Pocket Book Price £3.90†

No. 225 110 Thyristor Projects Using SCRs & Triacs Price £2.50†

No. 227 110 COS/MOS Digital IC Projects For the Home Constructor Price £2.25†

No. 226 110 Operational Amplifier Projects for the Home Constructor Price £2.50†

No. 242 Electronics Pocket Book Price £3.75†

No. 239 30 Photoelectric Circuits & Systems Price £1.80†

## NUTS AND BOLTS

BA BOLTS - packs of BA threaded cadmium plated screws slotted cheese head. Supplied in multiples of 50

Type	No.	Price	Type	No.	Price
1in OBA	839	£1.20	3/4in 4BA	848	£0.22
1in OBA	840	£0.75	3/4in 4BA	847	£0.25
1in 2BA	842	£0.65	3/4in 6BA	848	£0.40
1in 2BA	843	£0.45	3/4in 6BA	849	£0.21
1in 2BA	844	£0.52	3/4in 6BA	850	£0.26
1in 4BA	845	£0.44			

BA NUTS - packs of cadmium plated full nuts in multiples of 50

Type	No.	Price	Type	No.	Price
OBA	856	£0.72	4BA	857	£0.30
ZBA	856	£0.48	6BA	858	£0.24

BA WASHERS - flat cadmium plated plain stamped washers supplied in multiples of 50

Type	No.	Price	Type	No.	Price
OBA	859	£0.14	4BA	861	£0.12
ZBA	860	£0.12	6BA	862	£0.12

SOLDER TAGS - hot tinned supplied in multiples of 50.

Type	No.	Price	Type	No.	Price
OBA	851	£0.40	4BA	853	£0.22
ZBA	852	£0.28	6BA	854	£0.22

## SWITCHES

Description	No.	Price
DPDT miniature slide	1973	£0.11*
DPDT standard slide	1974	£0.14*
Toggle switch SPST 1 amp 250V a.c.	1975	£0.33*
Toggle switch DPDT 1 amp 250V a.c.	1976	£0.42*
Rotary on-off mains switch	1977	£0.50*
Push switch - Push to make	1978	£0.13*
Push switch - Push to break	1979	£0.18*

**ROCKER SWITCH**  
A range of rocker switches SPST - moulded in high insulation. Material available in a choice of colours ideal for small apparatus

Colour	No.	Price
RED	1980	£0.22*
BLACK	1981	£0.22*
WHITE	1982	£0.22*
BLUE	1983	£0.22*
YELLOW	1984	£0.22*
LUMINOUS	1985	£0.22*

Description	No.	Price
Miniature SPST toggle, 2 amp 250V a.c.	1958	£0.50*
Miniature SPST toggle, 2 amp 250V a.c.	1959	£0.55*
Miniature DPDT toggle, 2 amp 250V a.c.	1960	£0.65*
Miniature DPDT toggle, centre off, 2 amp 250V a.c.	1961	£0.85*
Push button SPST, 2 amp 250V a.c.	1962	£0.65*
Push button SPST, 2 amp 250V a.c.	1963	£0.68*
Push button DPDT 2 amp 250V a.c.	1964	£0.80*

**MIDGET WAFER SWITCHES**  
Single-bank wafer type - suitable for switching at 250V a.c. 100mA or 150V d.c. in non-reactive loads make before-break contacts. These switches have a spindle 0.25in dia. and 30° indexing

Description	Order No.	Price
1 pole 12 way	1985	£0.48*
2 pole 6 way	1966	£0.48*
3 pole 4 way	1967	£0.48*
4 pole 3 way	1968	£0.48*

**MICRO SWITCHES**  
Plastic button gives simple on-off action. Rating 10 amp 250V a.c. Button gives 1 pole change over action. Rating 10 amp 250V a.c.

Description	Order No.	Price
	1969	£0.20
	1970	£0.25

## FUSE HOLDERS AND FUSES

Description	Order No.	Price
20mm x 5mm chassis mounting	508	£0.07*
1 1/2in x 1/2in chassis mounting	507	£0.12*
1 1/2in car inline type	508	£0.15*
Panel mounting 20mm	509	£0.20
Panel mounting 1 1/2in	510	£0.30

**QUICK BLOW 20mm**

Type	No.	Type	No.	Type	No.
150mA	611	1A	615	3A	619
250mA	612	1.5A	616	4A	620
500mA	613	2A	617	5A	621
800mA	614	2.5A	618	All 5p each	

**ANTI-SURGE 20mm**

Type	No.	Type	No.	Type	No.
100mA	622	1A	625	2.5A	628
250mA	623	2A	626	3.15A	629
500mA	624	1.6A	627	5A	630
All 7p each					

**QUICK BLOW 1 1/2in**

Type	No.	Type	No.	Type	No.
250mA	631	500mA	632	800mA	634
All 7p each					

Type	No.	Type	No.	Type	No.
1A	635	2.5A	638	4A	641
1.6A	636	3A	639	5A	642
2A	637	All 5p each			

## CASES AND BOXES

**INSTRUMENT CASES.** In two sections vinyl covered top and sides, aluminium bottom, front and back.

No.	Length	Width	Height	Price
155	8in	5 1/2in	3in	£1.52*
156	11in	6in	3in	£2.12*
157	8in	4 1/2in	1 1/2in	£1.30*
158	8in	5 1/2in	2 1/2in	£1.76*

**ALUMINIUM BOXES.** Made from bright all., folded construction each box complete with half inch deep lid and screws.

No.	Length	Width	Height	Price
159	5 1/2in	2 1/2in	1 1/2in	62p*
160	4in	4in	1 1/2in	62p*
161	4in	2 1/2in	1 1/2in	62p*
162	5 1/2in	4in	1 1/2in	74p*
163	4in	2 1/2in	2in	64p*
164	3in	2 1/2in	1in	44p*
165	7in	5in	2 1/2in	£1.04*
166	8in	6in	3in	£1.32*
167	6in	4in	2in	86p*

**MIDGET WAFER SWITCHES**

Description	Price
1965 - 1 pole 12 way	40p*
1966 - 2 pole 6 way	40p*
1967 - 3 pole 4 way	40p*
1968 - 4 pole 3 way	40p*

## TRANSFORMERS

**MINIATURE MAINS Primary 240V**

No.	Secondary	Price
2021	6V-0-6V 100mA	80p*
2022	9V-0-9V 100mA	90p*
2023	12V-0-12V 100mA	95p*

**MINIATURE MAINS Primary 240V with two independent secondary windings**

No.	Type	Price
2024	MT280-0-6V, 0-6V RMS	£1.50*
2025	MT150-0-12V, 0-12V RMS	£1.50*

**1 AMP MAINS Primary 240V**

No.	Secondary	Price	P. & P.
2025	6V-0-6V 1 amp	£2.50*	P. & P. 45p
2027	9V-0-9V 1 amp	£2.00*	P. & P. 45p
2028	12V-0-12V 1 amp	£2.80*	P. & P. 55p
2029	15V-0-15V 1 amp	£2.75*	P. & P. 66p
2030	30V-0-30V 1 amp	£3.45*	P. & P. 86p

**STANDARD MAINS Primary 240V**  
Multi-tapped secondary mains transformers available in 4 amp 1 amp and 2 amp current rating. Secondary taps are 0-1R 25 33-40-50V

Volts available by use of taps:  
4, 7, 8, 10, 14, 15, 17, 19, 25, 31, 33, 40, 25 0-25V.

No.	Rating	Price	P. & P.
2031	1 amp	£5.50*	P. & P. 86p
2032	1 amp	£6.60*	P. & P. 86p
2033	2 amp	£8.90*	P. & P. £1 10

## AUDIO LEADS

107	FM Indoor Ribbon Aerial	
113	3.5mm Jack plug to 3.5mm jack plug Length 1.5m	£0.75*
114	5 pin DIN plug to 3.5mm. Jack connected to pins 3&5. Length 1.5m	£0.85*
115	5 pin DIN plug to 3.5mm. Jack connected to pins 1&4. Length 1.5m	£0.85*
116	Car aerial extension. Screened insulated lead fitted plug & ski.	£1 10*
117	AC mains connecting lead for cassette recorders & radios. 2 metres	£0.68*
118	5 pin DIN phono plug to stereo headphone jack socket	£1 05*
119	2+2 pin DIN plug to stereo jack socket with attenuation network for stereo headphones. Length 0.2m	£0 80*
120	Car stereo connector. Variable geometry plug to fit most car cassette. 8 track cartridge & combination units. Supplied with inline fused power lead and instructions.	£0 80*
123	6.6m Coiled Guitar Lead Mono Jack Plug to Mono Jack Plug BLACK	£1 50*
124	3 pin DIN plug to 3 pin DIN plug. Length 1.5m	£0.75*
125	5 pin DIN plug to 5 pin DIN plug. Length 1.5m	£0.75*
126	5 pin DIN plug to Tinned open end. Length 1.5m	£0.75*
127	5 pin Din plug to 4 Phono Plugs. All colour coded. Length 1.5m	£1 30*
128	5 pin DIN plug to 5 pin DIN socket. Length 1.5m	£1 06*
129	5 pin DIN plug to 5 pin DIN plug mirror image. Length 1.5m	£1 05*
130	2 pin DIN plug to 2 pin DIN inline socket Length 5m	£0.68*
131	5 pin DIN plug to 3 pin DIN plug. 1&4 and 3&5. Length 1.5m	£0.83*
132	2 pin DIN plug to 2 pin DIN socket. Length 10m	£0.98*
133	5 pin DIN plug to 2 phono plugs. Connected pins 3&5. Length 1.5m	£0.78*
134	5 pin DIN plug to 2 phono sockets. Connected pins 3&5. Length 23cm	£0.68*
135	5 pin DIN socket to 2 phono plugs. Connected pins 3&5. Length 23cm	£0.68*
136	Coiled stereo headphone extension lead. Black. Length 6m	£1.75*
178	AC mains lead for calculators etc.	£0.68*

## AVDEL BOND CYANOACRYLATE G2

The wonder adhesive which works in seconds. Bonds plastic rubber transformer components, permanently - immediately! O/D143 ONLY 70p\* for a 2gm phial

## BI-PAK CATALOGUE

**NEW EDITION NOW AVAILABLE**  
Send for your copy of our revised catalogue and price list NOW! It contains 127 pages packed with literally hundreds of semiconductor, components and our famous range of BI-KITS audio modules. **ONLY 65p POST FREE**

**ORDERING** Do not forget to state order number and your name and address.  
V.A.T. Add 12 1/2% to prices marked\* 8% to those unmarked. Items marked are zero rated.  
P&P. 35p unless otherwise shown

# BI-PAK

DEPT. PW6, P.O. Box 6, Ware, Herts  
COMPONENTS SHOP: 18 BALDOCK STREET, WARE, HERTS.



# High quality audio modules for Stereo and mono

## \$450

**STEREO FM TUNER**  
Fitted with phase lock-loop  
**£22.30**  
+ 40p p&p  
+ 12½% VAT



FREQUENCY RANGE	88-108 Mhz
SENSITIVITY	3.0 µV
BANDWIDTH	250 kHz
SPURIOUS REJECTION	50 dB
SELECTIVITY ± 400 kHz	55 dB
AUDIO OUTPUT (22.5 kHz deviation)	100 mV
STEREO SEPARATION	30 dB
SUPPLY REQUIREMENTS	90 to 30V (90mA max)
AERIAL IMPEDANCE	75 ohms
DIMENSIONS	240mm x 110mm x 32mm

The 450 Tuner provides instant programme selection at the touch of a button ensuring accurate tuning of 4 pre-selected stations, any of which may be altered as often as you choose, simply by changing the settings of the pre-set controls. Features include FET input stage, Vari-Cap diode tuning, Switched AFC LED Stereo Indicator.

## Stereo 30

**COMPLETE AUDIO CHASSIS**  
**£18.95**  
+ 40 p&p  
+ 12½% VAT



OUTPUT POWER	7 Watts RMS
LOAD IMPEDANCE	8 ohms
TOTAL HARMONIC DISTORTION	Less than .5% (Typically .3%)
FREQUENCY RESPONSE	50 Hz to 20 kHz ± 3dB
STONE CONTROL RANGE	± 22 dB at 100Hz and 10kHz
SENSITIVITY	190 mV for full output
INPUT IMPEDANCE	1 M ohms
TRANSFORMER REQUIREMENTS	22 V.A.C. rated at 1A
DIMENSIONS (Less controls and panel)	290mm x 130mm x 33mm

The Stereo 30 comprises a complete stereo pre-amplifier, power amplifier and power supply. This, with only the addition of a transformer or overwind will produce a high quality audio unit suitable for use with a wide range of inputs i.e. high quality ceramic pick-up, stereo tuner, stereo tape deck etc. Simple to install, capable of producing really first class results, this unit is supplied with full instructions, black front panel, knobs, main switch, fuse and fuse holder and universal mounting brackets.

## AL60

**AUDIO AMPLIFIER MODULE**  
25 Watts RMS  
**£4.55** + 25p p&p  
+ 12½% VAT



OUTPUT POWER	25 Watts RMS
SUPPLY	30-50 V
LOAD IMPEDANCE	8-16 ohms
TOTAL HARMONIC DISTORTION	Less than .1% (Typically .06%)
FREQUENCY RESPONSE	20 Hz to 30 kHz x 2 dB
SENSITIVITY	280 mV for full output
MAX. HEAT SINK TEMPERATURE	90°C
DIMENSIONS	103mm x 64mm x 15mm

This high quality audio amplifier module is for use in audio equipment and stereo amplifiers and provides output powers up to 25 RMS with distortion levels below 0.1%.

## AL80

**AUDIO AMPLIFIER MODULE**  
35 Watts RMS  
**£7.15\*** + 25p p&p  
+ 12½% VAT




OUTPUT POWER	35 Watts RMS
SUPPLY	40-60 V
LOAD IMPEDANCE	8-16 ohms
TOTAL HARMONIC DISTORTION	Less than .1% (Typically .06%)
FREQUENCY RESPONSE	20 Hz to 30 kHz x 2 dB
SENSITIVITY	280 mV for full output
MAX. HEAT SINK TEMPERATURE	90°C
DIMENSIONS	103mm x 64mm x 15mm

The AL80 is similar in design to the AL60 above and is of the same high quality but provides output powers up to 35W with distortion levels below 0.1%.
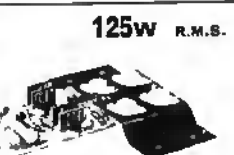
## AL250

**POWER AMPLIFIER**  
**£17.25\*** + 40p p&p + 8% VAT



OUTPUT POWER	125 Watts RMS continuous
OPERATING VOLTAGE	50-80 V
LOADS	4-16 ohms
FREQUENCY RESPONSE	25 Hz to 20 kHz measured at 100 Watts
SENSITIVITY FOR 100 WATTS O/P AT 1 kHz	450 mV
INPUT IMPEDANCE	33 K ohms
TOTAL HARMONIC DISTORTION	0-1% into 4 ohms 0-06% into 8 ohms

This unit, designated AL250, is a power amplifier providing an output of up to 125W RMS, into a 4 ohm load.

## AL30A

**AUDIO AMPLIFIER MODULES**  
**£3.75** + 8p p&p  
+ 12½% VAT



MAXIMUM SUPPLY VOLTAGE	30 V
POWER OUTPUT for 2% THD	10 Watts RMS
TOTAL HARMONIC DISTORTION	Less than .25%
LOAD IMPEDANCE	8-16 ohms
INPUT IMPEDANCE	100 K ohms
FREQUENCY RESPONSE	30 Hz-25 kHz ± 3 dB
SENSITIVITY	75 mV for full output
DIMENSIONS	74mm x 63mm x 28mm

These low cost 8 and 10 watt modules offer the utmost in reliability and performance, whilst being compact in size.

## SPM80

**STABILISED POWER SUPPLY**  
**£4.25** + 12½% VAT  
+ 12½% VAT



INPUT A.C. VOLTAGE	85-45V
OUTPUT D.C. VOLTAGE	35 V nominal
OUTPUT CURRENT	10 mA-1.8 amps
OVERLOAD CURRENT	1.7 amps approx.
DIMENSIONS	108mm x 63mm 30mm

Designed to power two AL60s at 15 Watts per channel simultaneously. Circuit Techniques include full short circuit protection.

## PA100

**STEREO PRE-AMPLIFIER**  
**£15.80**  
+ 40p p&p  
+ 12½% VAT



FREQUENCY RESPONSE	20 Hz to 20 kHz x 1 dB
TOTAL HARMONIC DISTORTION	Less than .1% (Typically .07%)
SENSITIVITY	1. TAPE 100 mV/100 K ohms 2. RADIO TUNER 100 mV/100 K ohms 3. MAGNETIC P.U. 3-8 mV/60 K ohms
EQUALISATION	75 mV for full output Within ± 1 dB from 20 Hz to 20 kHz
BASS CONTROL RANGE	± 15 dB at 75 Hz
TREBLE CONTROL RANGE	+ 10-20 dB at 15 kHz
SIGNAL/NOISE RATIO	Better than 65 dB (All inputs)
INPUT OVERLOAD	Better than 26 dB (All inputs)
SUPPLY	20 to 40 V
DIMENSIONS	300 x 90 x 33mm (less controls)

A top quality stereo pre-amplifier and tone control unit, the PA100 provides a comprehensive solution to the front end requirements of stereo amplifiers or audio units. The six push button selector switch gives a choice of inputs together with two filters for high and low frequencies.

## MPA30

**MAGNETIC CARTRIDGE PRE-AMPLIFIER**

Enjoy the quality of a magnetic cartridge with your existing ceramic equipment using the MPA 30 which is a high quality pre-amplifier enabling magnetic cartridges to be used where facilities exist for the use of ceramic cartridges only.  
**£2.95**  
+ 25p p&p  
+ 12½% VAT

SENSITIVITY	3-5 mV for 100 mV output
EQUALISATION	Within ± 1 dB from 20 Hz to 20 kHz
INPUT IMPEDANCE	50 K ohms
SUPPLY	18 to 30 V—earth
DIMENSIONS	110 x 50 x 25mm (inc DIN socket)

## PA12

**STEREO PRE-AMPLIFIER**

The PA12 Stereo Pre-Amplifier chassis is designed and recommended for use with the AL 20/30 Audio Amplifier Modules, the PS12 power supply and the T638 Transformer. Features include on/off volume, Balance, Bass and Treble controls. Complete with tape output.  
**£7.10**  
+ 30p p&p  
+ 12½% VAT

FREQUENCY RESPONSE	20 Hz-20 kHz (-3dB)
BASS CONTROL	± 12 dB at 60 Hz
TREBLE CONTROL	± 14 dB at 10 kHz
INPUT IMPEDANCE	1 Meg. ohm
INPUT SENSITIVITY	300 mV
CROSSTALK	-60 dB
SIGNAL/NOISE RATIO	-45 dB
OVERLOAD FACTOR	± 20 dB
TAPE OUTPUT IMPEDANCE	25 K ohms
DIMENSIONS	152mm x 54mm x 25mm

## PS12 POWER SUPPLY

Designed for use with the AL30A S.450 and MPA30 in conjunction with transformer T538.  
**£1.30**  
+ 25p p&p  
+ 12½% VAT

INPUT VOLTAGE	17-20V AC
OUTPUT VOLTAGE	27-30V DC
OUTPUT CURRENT	800mA
SIZE	60mm 43mm x 25mm

## GE 100 NINE CHANNEL MONO-GRAPHIC EQUALIZER

The GE100 has nine 1 octave adjustments using integrated circuit active filters. Boost and Cut limits are ± 12dB. Max Voltage handling 2 V RMS, T.H.D., 0.05%, input impedance 100K. Output impedance less than 10 K. Frequency response 20 Hz-20 kHz (±3dB). The nine gain controls are centre at 50, 100, 200, 400, 800, 1,600, 3,200, 6,400 and 12,800 Hz. The suggested gain controls are 10 K LIN sliders (not supplied with the module) See Paks S31 and 16192.  
**£22.00**  
+ 25p p&p  
+ 12½% VAT

**SG30 POWER SUPPLY BOARD** for GE100 15-0-15 VOLT **£3.50** + 12½% VAT + 25p p&p

## SIREN ALARM MODULE

American Police siren powered from any 12 volt supply into 4 or 8 ohm speaker. Ideal for car burglar alarm, freezer breakdown and other security purposes. Order No. S15, No. BP124.  
Only **£3.50** + 8% VAT + 25p p&p

## MA60 HI-FI AMPLIFIER KIT

Build you own top quality amplifier, save yourself pounds. The MA60 kit comprises the following Bi-Pak modules, 2 x AL60 amps, 1 x PA100 pre-amp, 1 x SPM80 stab. power supply, 1 x BM780 trans. giving 17 watts RMS per channel STEREO. All modules covered by the Bi-Pak satisfaction or money back guarantee. Details of the above modules are in this ad.  
Price **£32.50** + 12½% VAT + 60p p&p

## TC60 KIT

A beautifully designed genuine TEAK WOOD veneered cabinet to put the professional touches to your home built amplifier. Full set of parts incl. Front & Back Panels, Knobs, Chassis, Fuses, Sockets, Neon, etc. Ideal for the MA60, Size. 425mm x 900mm x 95mm  
Price **£19.95** + 12½% VAT + 80p p&p

## TRANSFORMERS

T536 For use with S.450 AL30A MPA30  
Order No. 2038 Price: **£3.30** + 8p p&p + 12½% VAT  
T638 For use with Stereo 30  
Order No. 2039 Price: **£3.20** + 8p p&p + 12½% VAT  
BM780 For use with AL60 SPM80  
Order No. 2034 Price: **£5.40** + 8p p&p + 12½% VAT  
BM7250 For use with AL250  
Order No. 2035 Price: **£1.35** + **£1.10** p&p + 12½% VAT

**BI-PAK**  
DEPT. PW6, P.O. Box 6, Ware, Herts

# Crystal Gazing

## EDITOR

Geoffrey C. Arnold

## ASSISTANT EDITOR

Dick Ganderton, C. Eng., MIERE

## ART EDITOR

Peter Metallf

## TECHNICAL EDITOR

Ted Parratt, BA

## NEWS & PRODUCTION EDITOR

Alan Martin

## TECHNICAL SUB-EDITOR

Peter Preston

## TECHNICAL ARTIST

Rob Mackie

## SECRETARIAL

Sylvia Barrett  
Debbie Chapman

## EDITORIAL OFFICES

Westover House, West Quay Road,  
POOLE, Dorset BH15 1JG  
Telephone: Poole 71191

## ADVERTISEMENT MANAGER

01-261 6671 Roy Smith

## CLASSIFIED ADVERTISEMENTS

01-261 5762 Colin R. Brown

## ADVERTISEMENT OFFICES

King's Reach Tower, Stamford Street,  
London SE1 9LS

## BINDERS

Binders, for either the old or the new format, are £2.85 and indexes are 45p (Inc VAT) and can be obtained from the Post Sales Department, IPC Magazines Ltd., Lavington House, Lavington Street, London SE1 0PF. Remittances with overseas orders for binders should include 60p to cover despatch and postage.

## BACK NUMBERS

We are very glad to announce the re-establishment of a PW Back Numbers Service for our readers. In future back numbers dated from June 1977 only will be available from our Post Sales Department for 65p, which includes postage and packing. Cheques and Postal Orders should be made payable to IPC Magazines Ltd.

Send your orders to:- Post Sales Department, IPC Magazines Ltd., Lavington House, Lavington Street, London SE1 0PF.

In a recent lecture entitled "Tomorrow's Broadcasting—The Technical Possibilities", Dr. Boris Townsend, head of the Engineering Information Service of the Independent Broadcasting Authority, highlighted some examples of the pitfalls in trying to forecast future developments in engineering. In 1924 for example, Campbell Swinton, talking to the RSGB, dismissed the topic of television (or as he called it then, seeing at a distance) as "... probably scarcely worth anybody's while to pursue". In more recent times, a well-known television engineer swore an affidavit to the FCC in America, that the shadow-mask colour display tube could not be mass-produced!

In making his forecasts, Dr. Townsend saw the biggest advances in broadcasting coming from the ever-widening use of sophisticated microcircuits. Their use in signal-processing circuitry would allow good quality TV pictures to be produced from scenes with low lighting levels, and reproduced from small, cheap videotape recorders. The adoption of microprocessor-based control systems has already allowed the IBA to operate and maintain 400 transmitters with the same number of staff as were needed for only 40 transmitters some dozen years ago. The introduction of similar systems into studios is also having far-reaching effects.

Sticking my own neck out, I foresee that the domestic TV receiver itself is likely to undergo a change of use over the coming years. The growing popularity of TV games, such as the Tank Battle which we feature in this issue, is the first step in this process. The broadcast Teletext services, Oracle from the IBA and Ceefax from the BBC, are already established and hopefully we will soon see a reduction in the price of receivers fitted with the necessary decoders. Also on the data front, the Post Office has recently announced that their Viewdata service is to be made available to the public from January 1979. All this will mean that the TV set will be used less as a source of broadcast entertainment and more as a source of information and participative entertainment. The adoption of microcircuits should also allow the domestic videotape recorder to be reduced in mechanical complexity and hence in cost, so that we may be able to view our favourite TV programmes when it suits us, rather than when the planners deem that we should.

Geoffrey C. Arnold

## PLEASE NOTE—CORRESPONDENCE

We do not operate a Technical Query Service except on matters concerning constructional articles published in PW. We do not supply service sheets or information on commercial radios, TV's or electronic equipment.

All queries must be accompanied by a stamped self-addressed envelope otherwise a reply cannot be guaranteed.



**Rally date**

'The Northern Mobile Rally 1978', organised by the Otley Radio & Electronics Society (G8JTD, G3XNO) is to be held at The Victoria Park Hall, Keighley on Sunday 21 May between 11.30 and 17.30.

Talk in stations on 2m f.m. S22 and 70cm f.m. SU8. There will be trade stands, films for the children, bar, refreshments and many other attractions. Further details from:

J. E. Annakin, G8DFZ, Rally Manager,  
25 Ashfield Place, Otley, W. Yorks  
LS21 3JN.

**Revival '78**

The Martlesham and Ipswich Radio Club and The Ipswich Area Civil Service Sports Association (I.A.C.-S.S.A.) are again organising an outdoor event for the Radio Amateur and his family, to be held on Sunday, 14 May 1978, at the I.A.C.S.S.A. Sports Ground, Straight Road, Bucklesham (NGR TM 222 421). Special attractions include; A v.h.f./u.h.f./s.h.f. aerial gain competition and demonstration, measurement of transmitter and receiver performance, bring and buy stands, Ad-hoc trading tables at £1 per hour for visitors and home-brew equipment competition.

The South Anglian Repeater Group, West Suffolk f.m. Group and Raynet

will be well represented and a 2m (R3 S22, 70cm) (RB4 SU8) and h.f. bands talk-in station will be in operation, probably using the call sign GB3 SWR. Further attractions include; Big name traders, demonstrations of Viewdata tv and microprocessor games, vintage wireless displays, raffle, pistol and archery ranges, flying display of radio controlled aircraft, plus many other family entertainments.

The event will start at 11.00am, admission 40p (accompanied children free). A licensed bar will be open from midday and there will be snacks, teas etc., throughout the day.

Further information can be obtained by sending a SAE to: C.P. Ransom G8LBS, 79 Camden Road, Ipswich, Suffolk IP3 8JN.

**First show**

The Dept. of Electrical Engineering Science at the University of Essex is organising the 1st Essex Electronics Exhibition on 18/19 April 1978.

Admission is by free ticket issued by either the companies exhibiting or by the Department. Further details from:

E. P. Strudwick, Dept. Electrical Engineering Science, University of Essex, Wivenhoe Park, Colchester, Essex.  
Tel: 0206 44144 Ext. 2248.

**Hi-Fi Seminar**

Latest developments in turntables and pickups, amplifiers, loudspeakers, tuners and tape recorders will be reviewed in a one day seminar being organised by the Society of Electronic and Radio Technicians. Speakers include such famous names from the audio field as James Moir, James Linsley Hood, John Borwick, Angus McKenzie and Basil Lane. The lectures will be followed by demonstrations.

The seminar will be held at the Institute of Marine Engineers, Mark Lane, London EC3 on Wednesday, 7 June 1978, commencing at 10.00 am. Fees are £15 (£10 to SERT members) and this includes a copy of the papers, coffee, lunch and afternoon tea.

Further details from: SERT, 8-10 Charing Cross Road, London WC2H 0HP.

**Can I help you!**

Are you the secretary, organiser or general dog's body of your local radio club or any other group whose functions may interest readers of *PW*. If so, let me know and I will endeavour to publicise your rally, get-together, whatever, through this column. Remember though, we compile the magazine some time ahead of publication day (e.g. this note was written in mid-March), so, the earlier I can have details, the better. Alan Martin

**KINDLY NOTE!****Radio 2 Tuner, July 1977**

On p 213, C7 is incorrectly shown as 3·3pF. This should be 3·3µF as shown in the components list.

**"Shoot", August 1977**

Certain errors in the circuit diagram on p.283 have been noted. The PCB is correct, however, VR4 should be 22k preset, and not 2·2k. Pin 14 of IC3A should be connected to +8V line as should pin 14 of IC4A and pin 3 of IC2B. Pins 1, 2, 5, 6 and 7 of IC3C should be connected to 0V line, as should pin 7 of IC4B. Under the heading "Connection" on p.282, it is claimed that the sync. output is taken from pin 16 of IC1 of "Tele-Games" unit. This should read "pin 15".

**IC of the Month, Sprague ULN-3006T Hall Effect Switch, March 1978** *PW* the second paragraph

following the heading "The Hall Effect", p. 845, and commencing "The current carriers..." is somewhat ambiguous, and should read "The current carriers in the silicon (which may be electrons or "holes") are both deflected to one side of the material, depending upon direction of current flow and magnetic field, in accordance with Fleming's Left Hand Rule."

**"Multi-Range Test Meters," March 1978**

Page 839, the paragraph commencing "The minimum measurable..." should read:

The minimum total circuit resistance necessary, if full-scale deflection is not to be exceeded, is therefore 1500 ohms. This will be made up of the meter movement resistance plus a series current-limiting resistor, both of which are internal to the instrument. External readings are from zero upwards.

**Experimenter's Corner, p. 910 April 1978.** In the circuit diagram and text for "LED Light Display", the pnp transistors are incorrectly shown as AC176 (npn). These should of course be AC128 in every case.



# AUDIO DISTORTION METER

E. A. RULE

PART 2

## Construction

In general the construction is not critical and the prototype built by the author used plain Vero matrix board as shown in the photographs. However a complete set of p.c.bs is available and the various drawings show these and the associated component placements.

Leads from the front panel controls to the boards should be of screened wire, and the millivoltmeter circuit board should have a tinfoil screen fitted around it as detailed in Fig. 8. It can be made from tinfoil cut from a cocoa tin and is held in position by two paper clips soldered to it as shown. The better the screening of boards and components, the lower the final distortion measurement limit will be.

## Initial Setting Up of the Meter

Set all pre-sets to halfway. After carefully checking that no mistakes have been made in the construction, switch on. At first the meter will swing about for a few moments and then settle down.

Allow about one minute before setting up the distortion meter as follows:—

Disconnect the bridge output lead to the millivolt meter attenuator and then connect an audio generator directly to the millivolt meter attenuator. (The point originally connected to the bridge.)

Set the output of the generator at 1kHz to give full scale deflection of the meter with the millivolt meter range switch on the 1V range. Switch to the 10V range, meter should fall to 10% of full scale. If not, adjust the pre-set 3 for more feedback and repeat test. Only the minimum amount of feedback required to obtain a linear scale should be used. When the reading drops to 10% of full scale, pre-set 2 should be adjusted so that a 5V input gives full scale on the 10V range, and 0.5V input gives full scale on the 1V range, etc.

Switch millivolt meter attenuator back to 10V range and transfer generator to the input socket. Reconnect output lead of bridge. Set/Read switch to Set. Adjust generator output for 10V and distortion meter input attenuator to maximum. Adjust VR7 in bridge circuit for full scale on meter. (If your

generator does not have 10V output, use 1V and switch millivolt meter attenuator to 1V range.)

Turn input attenuator to minimum. The residual reading on meter should be less than 0.4mV on the 1mV range with all screens etc., in place. The authors instrument has a residual noise 0.24mV on the 1mV range. This represents a 93dB measuring range for signals above 10V, i.e., down to 0.003%. Set generator to 1V output at 1kHz. Set distortion meter to 1V range and adjust input attenuator for a convenient reading about two thirds of full scale. Switch generator to 1V output at 100kHz. Adjust trimmer TC1 for the same reading on meter as before. This adjusts the frequency response of the meter for a flat response to 100kHz.

Switch generator back to 1kHz and set its output to 10V (or 1V if the higher output is not available).

After adjusting the input attenuator for full scale deflection, switch Read/Set switch to Read. Adjust bridge frequency and balance controls to obtain lowest possible reading on meter, reducing the voltage range switch as the meter readings reduce. The final lowest reading obtained is the Total Harmonic content of the Test Signal.


## Operation

A typical set up is shown in Fig. 13. When measuring very low values of distortion, it is very important to avoid multiple earth connections. Only the amplifier under test should be earthed. The other test equipment must have its normal mains earth removed and connected only via its connecting lead to the earth of the amplifier. Care should be taken that all test equipment is safe and fitted with mains isolation transformers or battery operated. Multiple earths can cause very high distortion readings and could be very misleading.

Before commencing a measurement, connect your generator directly to the distortion meter and measure its distortion. The figure you get from this test will set the minimum distortion you can measure. This minimum should be restricted to at least twice the direct reading obtained if reasonable accuracy is to be maintained.

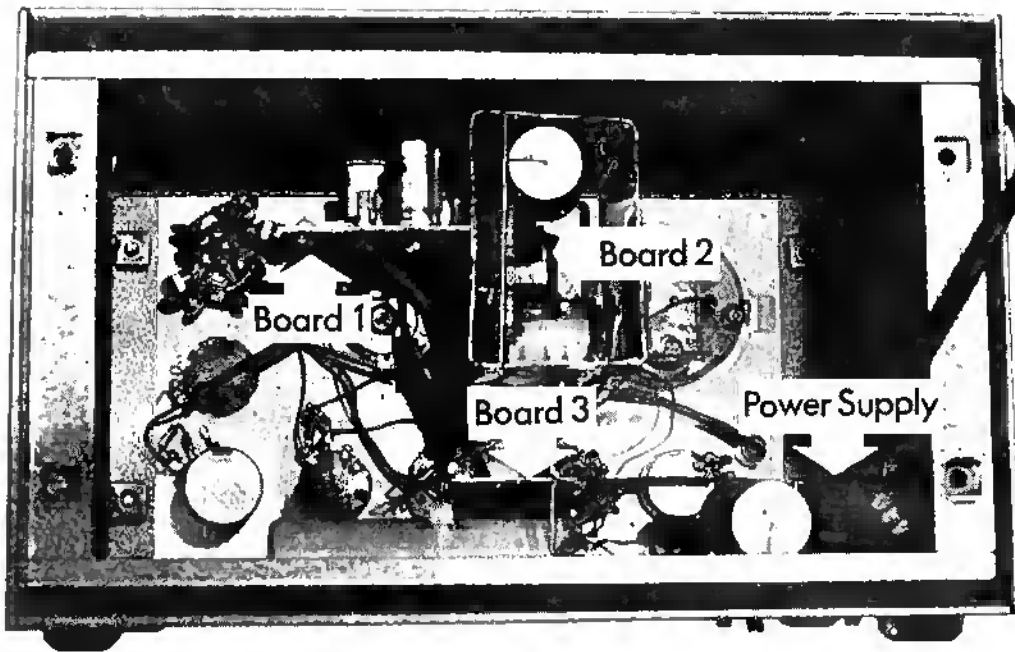To make a measurement, adjust the input signal of the amplifier under test to provide the required





Inside view of the completed instrument showing the layout of the p.c.bs and the controls mounted on the front panel. The power supply is fitted to the cabinet base and is the only board not mounted onto the front panel

output into a dummy load. Set the distortion meter millivolt switch to a suitable voltage range. Adjust the input attenuator for full scale reading (100%). Switch to "Read" and null out the fundamental signal. As the optimum bridge balance is obtained, the millivolt meter range will have to be switched to the next lower range. Read off the distortion direct from the meter when no further reduction in level is possible. Note that the frequency and balance controls are interdependent.

With an oscilloscope connected to the socket provided on the distortion meter the harmonic content of the signal can be examined. A scope sensitivity of approximately 10mV/cm is required. With inputs


below 10V the minimum distortion readable will be reduced.

(Note: For inputs of less than 10V set the millivolt meter voltage switch to the range which will allow full scale deflection to be obtained. This range then becomes [for purpose of measurement] the 100% range and all other ranges move down by the same factor. For example, with 1V input, switch meter to 1V range, this is then 100% distortion full scale, the 0.1V range becomes 10% full scale etc.)

For accurate measurements the limits are shown in Table 1. However measurements of distortion to lower levels can be made, but with decreasing accuracy.

Nearly all pre-amplifier and tape recorders have

This view shows the components and boards mounted onto the back of the front panel. This is the prototype unit using matrix boards instead of p.c.bs

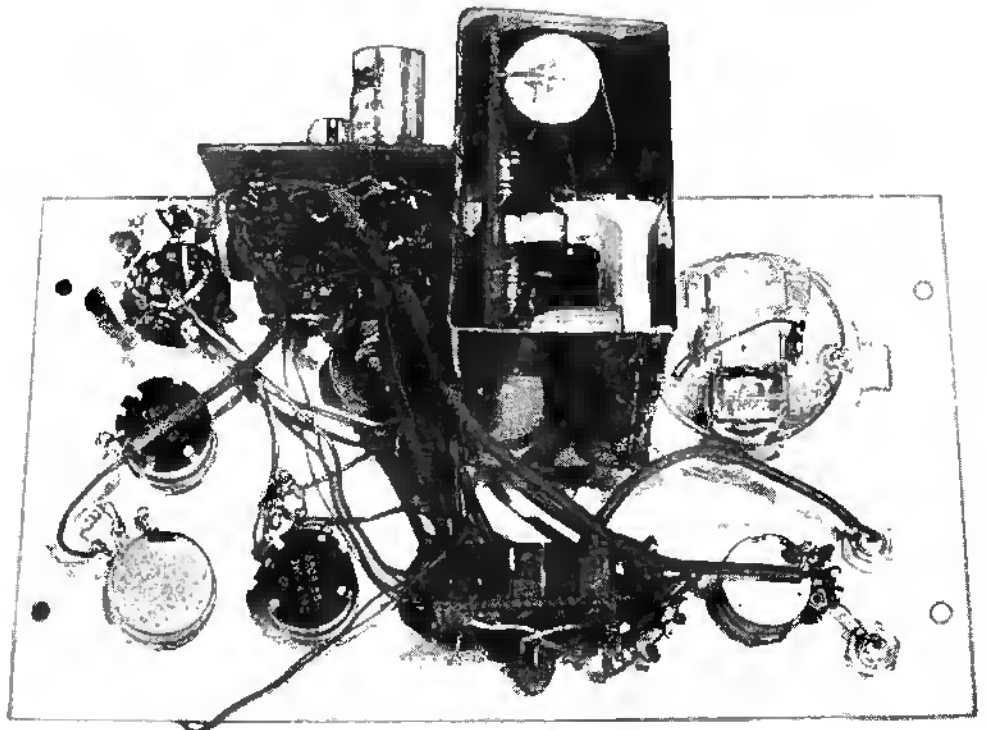

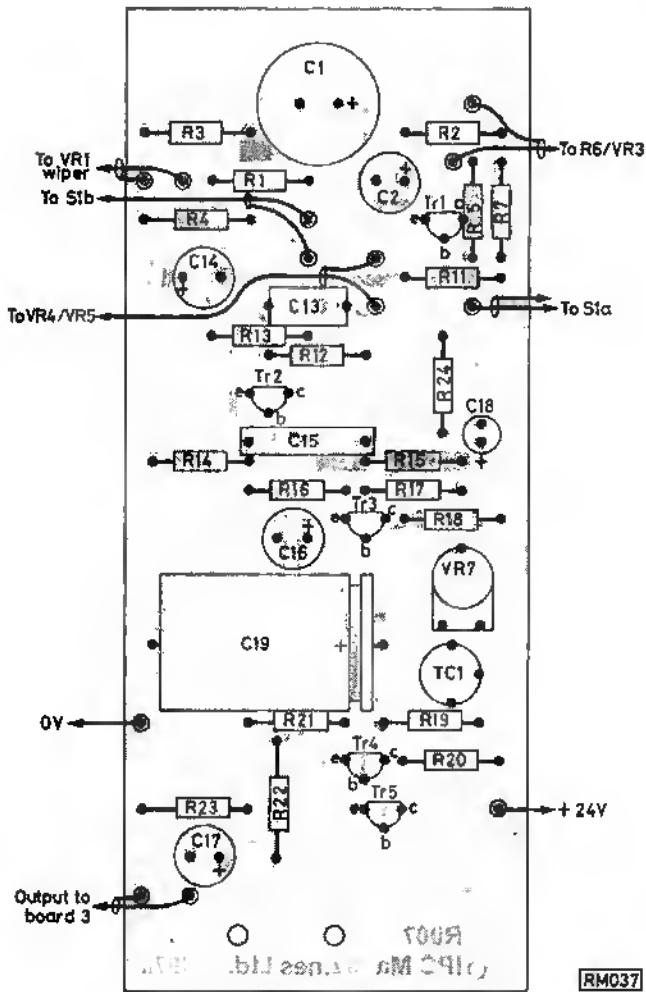


Fig. 5: Component placement drawing for the Bridge Circuit p.c.b. (Board 1)



Fig. 6: Copper track layout for Board 1. Ready drilled boards for this instrument are available from Reader's PCB Services (See page 68)

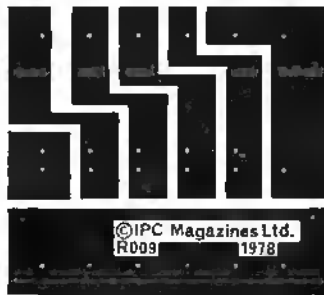


Fig. 7: Copper track layout for Board 3. Fig. 8: (Below) Component placement drawing for Board 3


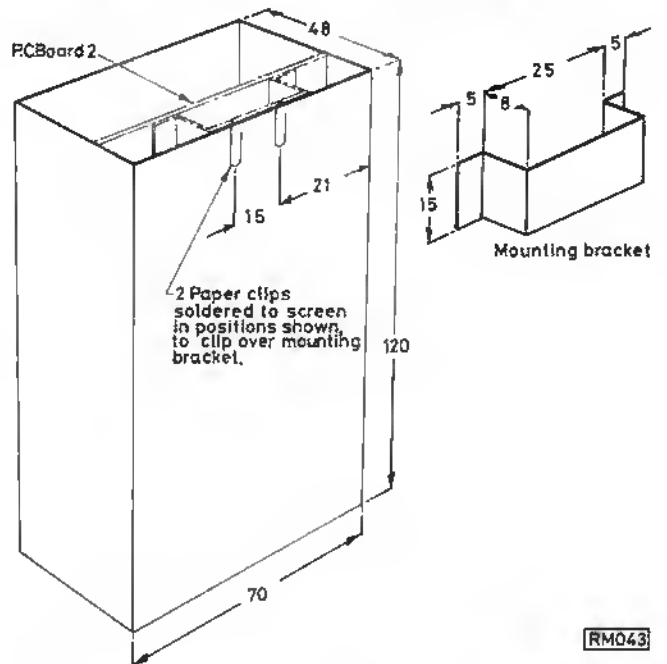


Fig. 8: Details of the tinplate screen for Board 2. The small bracket is soldered to the copper earth tracks at the top of Board 2

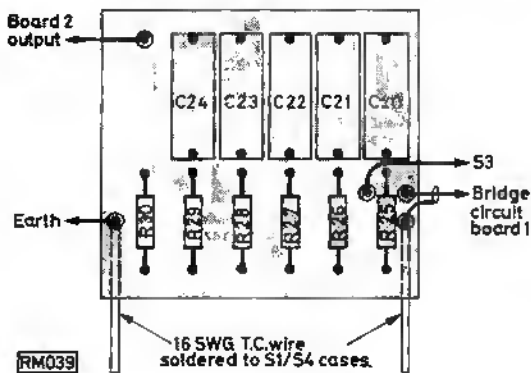

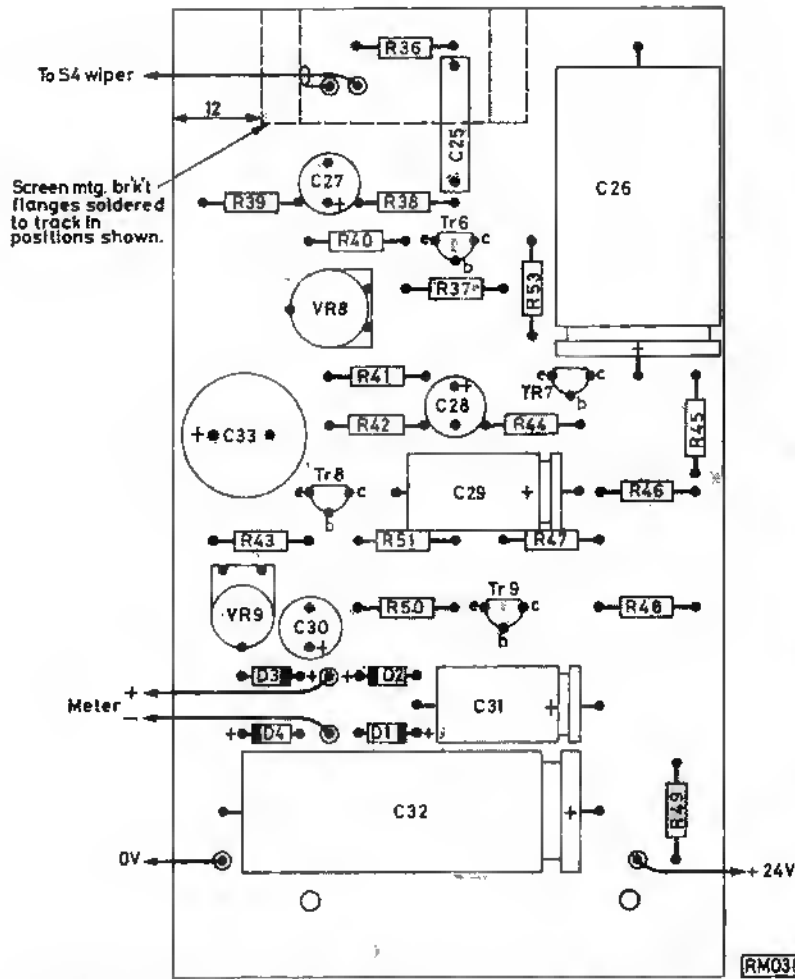


Fig. 9: Component placement drawing for the Meter Circuit p.c.b. (Board 2). Note the small finplate bracket soldered to the earth track


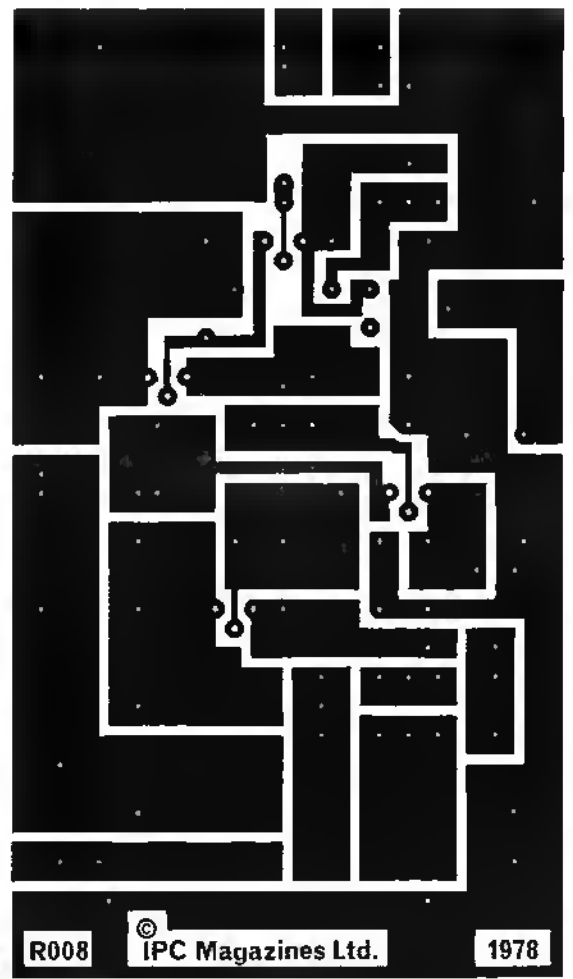


Fig. 10: Copper track layout for Board 2

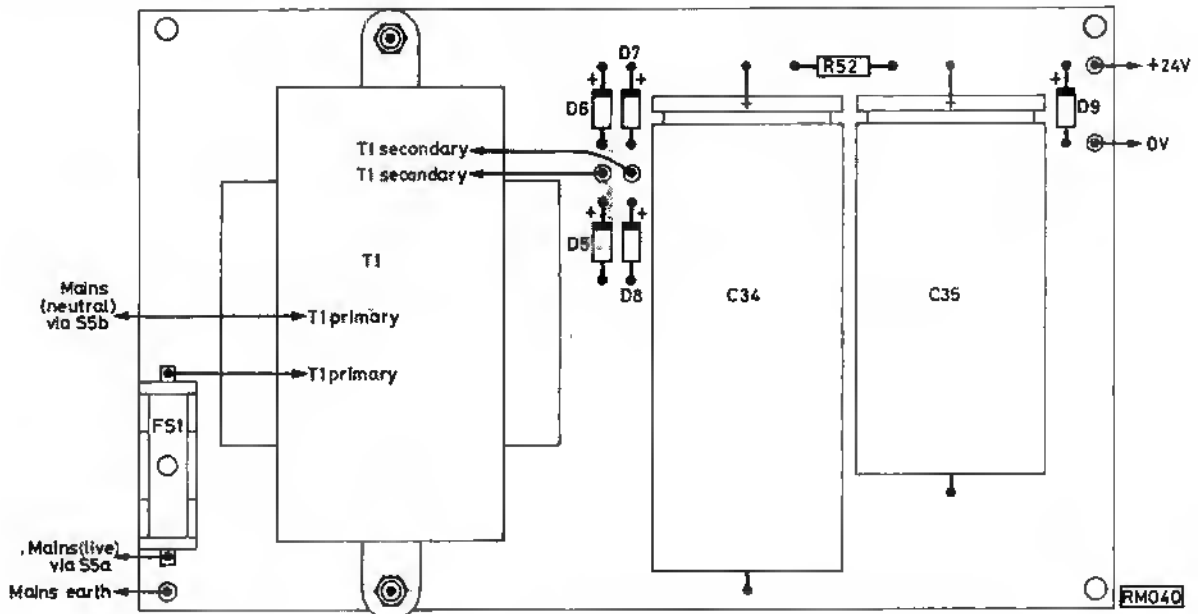

Component placement drawing for the Power Supply p.c.b. (Board 4)

outputs in excess of 1V and power amplifiers of the hi-fi type will have more than 10V output. So the t.h.d. meter should enable the hi-fi amplifiers to be checked down to below 0.01% with reasonable


accuracy. Do not be surprised if your amplifier does not reach the lowest figures at the extremes of the audio band and do not maintain the highest frequency for longer than it takes to make a measurement.

**Fig. 11: Copper track layout for Board 4. A ready drilled set of boards for this instrument is available from Reader's PCB Service (see page 88)**




© IPC Magazines Ltd.  
R010 1978

**Fig. 12: Details of the components mounted directly onto S2 wafer tags. The drawing shows the components opened out for clarity; they should be arranged along the axis of the switch mechanism in a cylindrical fashion**

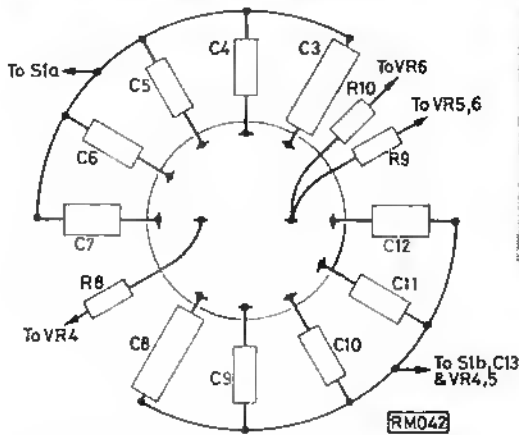

**Fig. 13: A typical set up for testing an audio amplifier using the Audio Distortion Meter**

AM 010

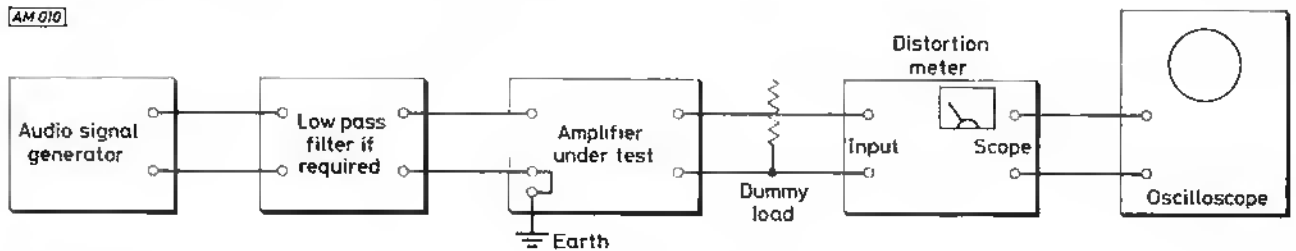

The following procedure is to assist the operator when using the distortion measuring meter for the first time. It is confined to measuring the distortion of a 1kHz signal, and should help the operator to become familiar with the basic operation.

- The controls should be set as follows:—
- Meter Range Switch on 1V range.
  - Frequency Range Switch on range 3.
  - Filter Out
  - Set/Read switch on Set
  - Input Attenuator at Zero
  - All other controls Midway

Connect a sine wave signal of 1kHz, 1V RMS to the input socket. Advance the input attenuator until meter reads 1V, i.e., full scale. Switch the set/read switch to the read position and rotate the frequency dial for minimum reading on meter. Adjust balance control to reduce meter reading further. Switch the volt meter range switch to next lower range as the signal is reduced by adjustment of the frequency and balance controls.

When no further improvement (reductions) can be obtained the distortion can be read directly from the

Minimum Input	Accurate Measurement
10V	0.01%
1V	0.1%
100mV	1%
10mV	10%
1mV	—

**Table 1.**



## ★ components

### Resistors

#### $\frac{1}{4}$ W 5% metal oxide

33 $\Omega$	1	R43
100 $\Omega$	3	R7, 49, 52
560 $\Omega$	1	R6
1k $\Omega$	1	R50
1.2k $\Omega$	1	R4
2.2k $\Omega$	3	R5, 8, 23
2.7k $\Omega$	1	R9
4.7k $\Omega$	2	R10, 45
10k $\Omega$	9	R14, 15, 16, 18, 20, 21, 36, 40, 48
12k $\Omega$	3	R3, 42, 51
22k $\Omega$	2	R40, 53
27k $\Omega$	1	R41
33k $\Omega$	5	R26, 27, 28, 29, 30
39k $\Omega$	1	R2
47k $\Omega$	3	R1, 19, 24
100k $\Omega$	5	R11, 12, 13, 25, 47
150k $\Omega$	1	R38
180k $\Omega$	1	R17
220k $\Omega$	1	R22
270k $\Omega$	1	R39
330k $\Omega$	1	R44
470k $\Omega$	1	R37

#### $\frac{1}{4}$ W 2% metal oxide

1 $\Omega$	1	R35
10 $\Omega$	1	R34
100 $\Omega$	1	R33
1k $\Omega$	1	R32
10k $\Omega$	1	R31

### Potentiometers

#### $\frac{1}{2}$ inch diameter spindles

100 $\Omega$	1	VR9
1k $\Omega$ lin.	2	VR2, 6
10k $\Omega$ lin.	1	VR8
10k $\Omega$ + 10k $\Omega$ lin.	1	VR4, 5
20k $\Omega$ lin.	1	VR3
100k $\Omega$ log.	1	VR1

#### Miniature horiz. skeleton preset

100k $\Omega$	1	VR7
---------------	---	-----

### Semiconductors

#### Diodes

OA202	4	D1, 2, 3, 4
1N4001	4	D5, 6, 7, 8
BZY88C24	1	D9

#### Transistors

BC413B	9	TR1, 2, 3, 4, 5, 6, 7, 8, 9
--------	---	-----------------------------

### Capacitors

#### Polyester

2.2nF	2	C7, 12
0.01 $\mu$ F	2	C6, 11
0.047 $\mu$ F	2	C5, 10
0.1 $\mu$ F	1	C25
0.22 $\mu$ F	8	C4, 9, 13, 20, 21, 22, 23, 24
0.68 $\mu$ F	1	C15
1 $\mu$ F	2	C3, 8

#### Electrolytic Printed circuit board mounting

2.2 $\mu$ F	63V	3	C14, 18, 27
10 $\mu$ F	63V	6	C2, 16, 17, 28, 29, 31
100 $\mu$ F	63V	1	C30
220 $\mu$ F	63V	1	C1
470 $\mu$ F	63V	1	C33

#### Electrolytic Axial leads

470 $\mu$ F	63V	2	C19, 32
1000 $\mu$ F	63V	2	C26, 34
4700 $\mu$ F	25V	1	C35

#### Ceramic trimmer

3-35pF	1	TC1
--------	---	-----

### Switches

Min. toggle s.p.d.t.	1	S3
2p. 6w. midget wafer	2	S1, 4
2p. 6w. miniature rotary switch	1	S2
Mains switch assy to fit S2 mech.	1	S5

### Miscellaneous

Transformer 24V 20VA Miniature  
Case RS 509-888  
Printed circuit boards (Four in set) Readers PCB Service.  
24V indicator lamp  
Knobs Sifam collet fixing type 15mm diameter  
W151 wing knob (3)  
K150 plain knob (3)  
K151 plain knob with line pointer (2)  
N150 nut covers (6)  
C150 caps (8)  
Figure dial for 15mm knobs with pointer (1)  
numbered 1-10 (1)  
Meter 1mA f.s.d. 90  $\times$  74mm approx.  
BNC 50 $\Omega$  sockets (2)  
Tinplate sheet for screen (cut from used cocoa tin or similar)  
PW Front panel overlay (Obtainable from PW Editorial Office)

meter and voltage switch.

That is, if initial full scale (100%) was 1V and final reading was (say) 6mV, then distortion is 0.6%. The low frequency filter can be switched in for measuring frequencies above 1kHz if hum is affecting the measurement.

## Other uses of the Meter

With the input attenuator at maximum, the meter can be used as a normal AC millivoltmeter with full scale range of 10 and 1V, 100, 10 and 1mV. This would make it possible for example to measure the

output of a magnetic pick-up directly.

It can also be used for measuring Hum and Noise in an amplifier. By adjusting the input attenuator for full scale on a test signal from an amplifier and then removing the test signal and shorting the test amplifier input to earth. The meter will then indicate the residue Hum and Noise of the test amplifier, for example: if full scale was obtained on 10V range with the test signal and then after removing it the reading was (say) 6mV, this represents a ratio of 1666:1, approximately 64dB.

Many other uses can be found and a few hours spent using the meter will be very rewarding. ●

# HOTLINES

## A REVIEW OF RECENT DEVELOPMENTS

*In general, the author does not have any more information on products than appears in the article*

### I spy Strangers

Some kind soul sent me a whole heap of papers from the recent International Solid State Circuits Conference and there seems to be some real goodies on the way (not available yet). One which took my eye is a single 14-pin dual-in-line package which houses a complete motion detector. It is intended for application in electronic toys. This little beastly can be made to keep an eye on a 2ft. diameter area at 8ft. The photodiode itself is actually integrated as part of the chip. An external loudspeaker is required and when connected up, the unit will emit a whooping noise whenever it senses motion within its "sight" area. It carries on making this din for a set period of time, then it goes back to sleep and waits for the next "something" to move within its sighting area. It would seem to offer great possibilities as a burglar alarm, etc.

A further nice feature of this little i.c. is that it has another mode of operation. To change it to this you need only add a single connection.

In its new mode it will "search". It does this by flashing an external bulb at some 3Hz. At the same time, it croaks out a random series of squeaks and grunts (the paper offers the more sophisticated description, "emits audible notes"). When the "thing" detects its own reflection it immediately sounds an alarm and simultaneously increases the bulb flashing rate to 25-30Hz. The chip uses two technologies; linear bipolar, and I<sup>2</sup>L.

### Hi-digi-fi

A recent report from Japan details feverish activity among audio equipment manufacturers—in the digital field. It is now virtually certain that the hi-fi systems of the future will be digital.

To date it seems that the only "standard" to emerge is a wide acceptance of a 30cm disc as the norm. Interestingly, though, the early professional systems will use tape before moving over to disc, and it is expected that the consumer scene will also follow this pattern.

But don't get too enthusiastic about digital audio. The world consensus of opinion is that it will be some four years before professional digital audio

systems really catch on, and a further six years after that the consumer market will blossom. It could therefore be some ten years before you see these systems advertised. The main hold up will be price. Initially, systems will be expensive and the first few years will be needed to gradually bring the prices down.

Why go digital anyway? It seems that analogue hi-fi has now gone about as far as it can, whereas digital is in its infancy. In terms of improvements digital technology has much to offer the audio buffs. To start with, frequency response and dynamic range are both independent of the characteristics of the tapes or discs used. It is also claimed that there is no crosstalk problem between channels. From all the specifications on systems that I've read, the responses are flat (very, very flat) right up to 20kHz, and dynamic range, even at this early stage is well over 80dB—some 20dB better than most analogue systems I read about these days.

Another advantage of the digital approach is wow and flutter—there isn't any! This is because all the signals are retimed so accurately during playback.

Various individual technologies are to be employed initially, including a laser/disc system. But the comforting thing is that despite the very different techniques, the final product, be it tape or disc is compatible in that one can convert material from tape to disc and vice versa.

Perhaps we'll all end up with a home computer to play our gramophone records on. Wonder what that dog, squinting down that trumpet/horn thinks about it all?

### Useful Chips

Another chip which could be very useful for the home constructor (when it becomes available) is a new level detector i.c. Onto the chip the manufacturers have managed (somehow) to cram five comparators, a voltage regulator, five output driver transistors, five scaling resistors and an input buffer stage with a high input impedance. By connecting five i.e.d.s (plus usual limiting resistors), each i.e.d. can be made to light as the input voltage increases in steps of 200mV, i.e. for each 200mV input,

the next i.e.d. illuminates. The open-collector outputs on the chip can handle currents up to 80mA and voltages up to 18V. In practical terms this means versatility because the ratings allow not only i.e.d.s to be used as indicators, but also filament lamps. By using suitable circuitry, the device can be made to flash the first lamp or i.e.d. continuously when the input level falls below the 200mV threshold level.

### Charge!

Charge those c.c.d. (charge-coupled devices) are in the news again—well worth keeping an eye on. This time it's a Japanese company that is using c.c.d.s in an experimental colour television camera. Each of the three c.c.d. chips (one for each primary colour has an array of 111,192 separate little sensing elements in an area 10.3mm × 9.1mm. If small is beau iful, then these devices must be fantastic.

The colour television camera, when it comes on the market (probably late next year if all goes well) will come complete with zoom lens, built-in camera control circuitry, and electronic viewfinder. Price is set at around the £500—£600 mark. Weight will be less than 2kg.


### Programmer

Microprocessors are here to stay and many are available to home constructors. One of the problems is learning how to programme these clever little electronic beasties. An answer is offered by a German manufacturer. He's marketing a little "black box" which can be used in conjunction with a black and white TV receiver. The black box has a light pen and the TV receiver is used as both input and output terminal. The box comes with a 230-page manual and costs around £280. For a further £140 (approximately) the purchaser can add a cassette control Interface for writing (and reading) memory data on standard, commercially available tape. The reading/writing rate is some 1 kilobyte in 90 seconds.

*Ginsberg*





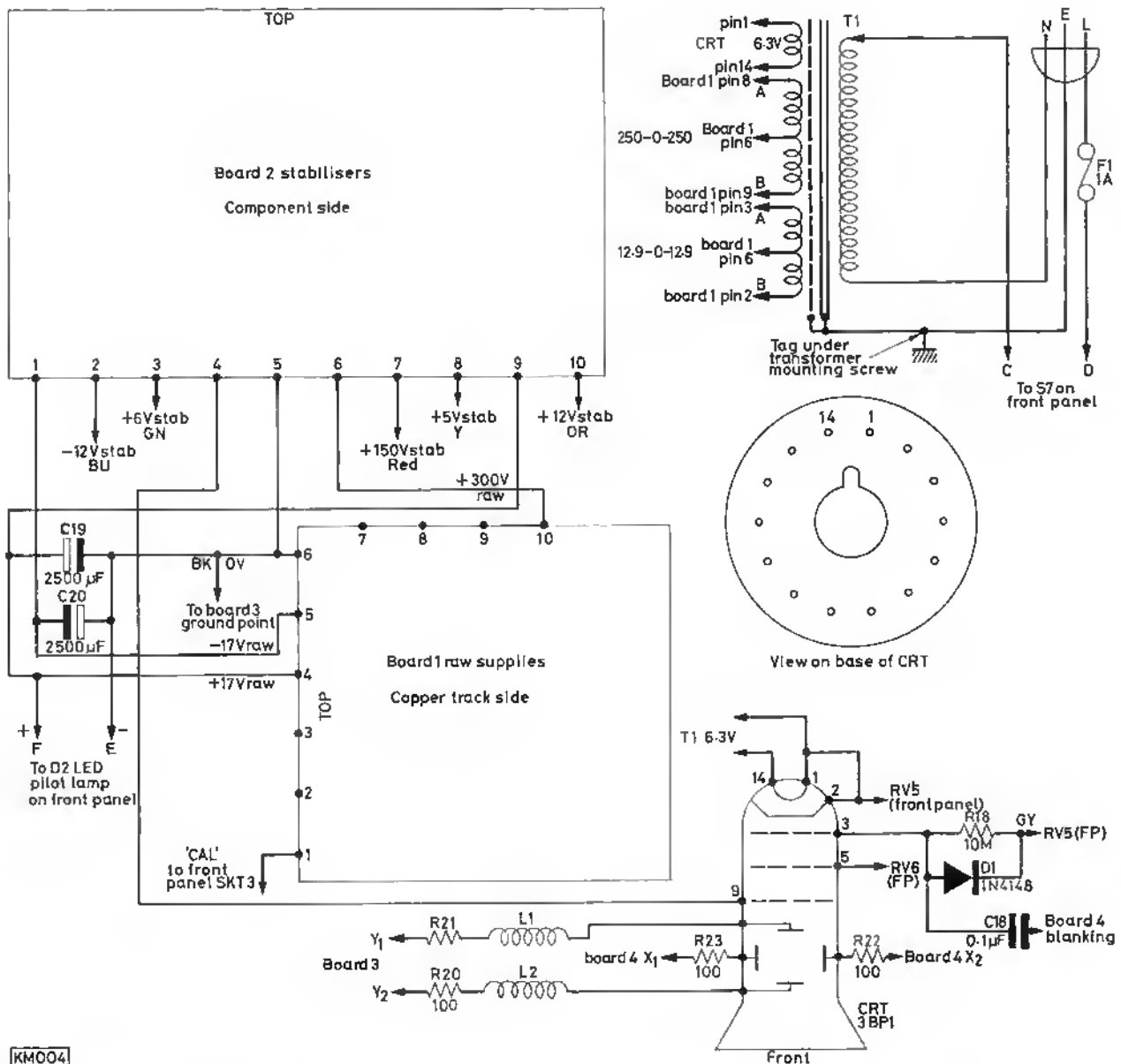

KMOQ4

Fig. 1: Power supply interwiring diagram and c.r.t. base connections. This drawing should be read in conjunction with Fig. 2 Front Panel wiring diagram. Please note that RV5 and RV6 should be read as VR5 and VR6

solder tag under the edge connector mounting screws.

Thus Board 4 ground plane, when plugged in, is earthed to the base of the mainframe via the edge connector mounting bracket and to the front panel via the 4BA pillar. Board 3, whilst similarly earthed, picks up the Black wire from the ribbon cable, at a point on the 16 s.w.g. earthwire adjacent to the Input Low contact and from the same point an earthwire runs to the earth point on S3 and thence to a solder tag under SKT 1 mounting screw.

This earthing arrangement is essential to avoid instability, ensure a flat Y amplifier frequency response and avoid ringing on square waves.

When making the connections between the front panel and mainframe, lay the panel down in front of the mainframe as though it were hinged at its lower edge. (This is why Fig. 2 Front Panel Wiring has been drawn the way it has.) Dress the wires from


**WARNING**  
Extra care must be taken when working on any part of this instrument while power is switched on. 1100 volts can kill. When delving into the insides of the scope for any reason with power on keep one hand in your pocket

the front panel along towards the "hinge" and thence off to their destinations. This will ensure that when the front panel is offered up and secured in position, there is adequate but not excessive lead length.

Having rechecked the wiring and removed the temporary link from Board 1 pin 6 to chassis, plug in briefly and check straight away that all the stabilised voltages are correct, indicating no shorts anywhere. Check that the slider of VR5 covers the range -750V to -800V approximately and that of VR6 -350V to -600V approximately. The c.r.t. base wiring can now be completed, except for C18 and the deflection plates.

In fact, the c.r.t. and mu-metal screen can now be fitted and a simple check carried out if desired. To do this, temporarily connect one end of a 47kΩ resistor to +150V stabilised and the other end via a 100kΩ resistor to chassis.



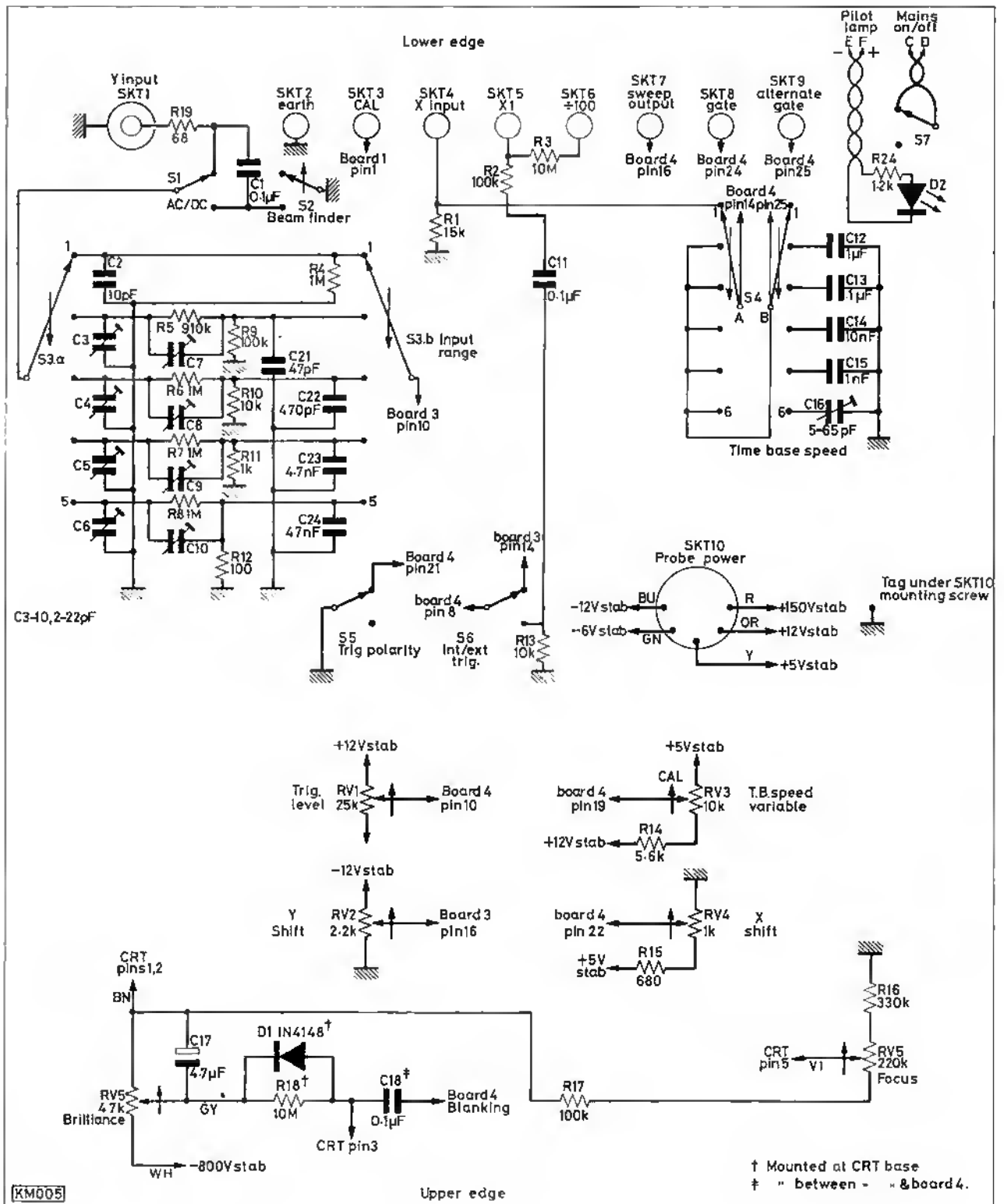

**Fig. 2: Front panel back wiring.** This diagram has been drawn with the top edge of the front panel at the bottom so as to correspond with its orientation when placed on the bench for the purpose of wiring. Connecting wires from the front panel to other parts of the instrument should be long enough to allow the panel to be lowered to the bench in front of the mainframe. This makes for easier working conditions. Please note that potentiometers labelled RV1 to 5 should be read as VR1 to 5 and also that the 220kΩ Focus potentiometer at the bottom righthand corner of the diagram labelled RV5 should be VR6. This drawing should be used with Fig. 1 the power supplies interwiring diagram

# ★ components

## FRONT PANEL AND MAIN FRAME

### Resistors

(Unless otherwise specified 5% 1/4W carbon film)

R1 15kΩ	R13 10kΩ
R2 100kΩ	R14 5-6kΩ
R3 10MΩ 10%	R15 680Ω
R4 1MΩ 1%	R16 330kΩ
R5 910 kΩ 1%	R17 100kΩ
R6 1MΩ 1%	R18 10MΩ 10%
R7 1MΩ 1%	R19 68Ω
R8 1MΩ 1%	R20 100Ω
R9 100kΩ 1%	R21 100Ω
R10 10kΩ 1%	R22 100Ω
R11 1kΩ 1%	R23 100Ω
R12 100Ω 1%	R24 1-2kΩ

### Capacitors

C1 0.1μF 350V	C13 0.1μF 1% 63V
C2 10pF Ceramic	C14 10nF 1% 63V
C3 2-22pF	C15 1nF 1% 63V
C4 2-22pF	C16 5-65pF
C5 2-22pF	C17 4.7μF 100V
C6 2-22pF	C18 0.1μF 1000V
C7 2-22pF	C19 2500μF 25V
C8 2-22pF	C20 2500μF 25V
C9 2-22pF	C21 47pF Ceramic
C10 2-22pF	C22 470pF Ceramic
C11 0.1μF 350V	C23 4.7nF met. film
C12 1μF 1% 63V	C24 47nF met. film

### Potentiometers

20% lin. 1/4W 1/2 inch shafts

VR1 25kΩ	VR4 1kΩ
VR2 2-2kΩ	VR5 47kΩ
VR3 10kΩ	VR6 220kΩ

### Inductors

L1 See Text	L2 See Text
-------------	-------------

### Diodes


D1 1N4148	D2 Hi brightness i.e.d.
-----------	-------------------------

### Transformer

T1 250-0-250V, 6-3V, 12-9-0-12-9V, Transformer Type 7559 (Barrie Electronics)
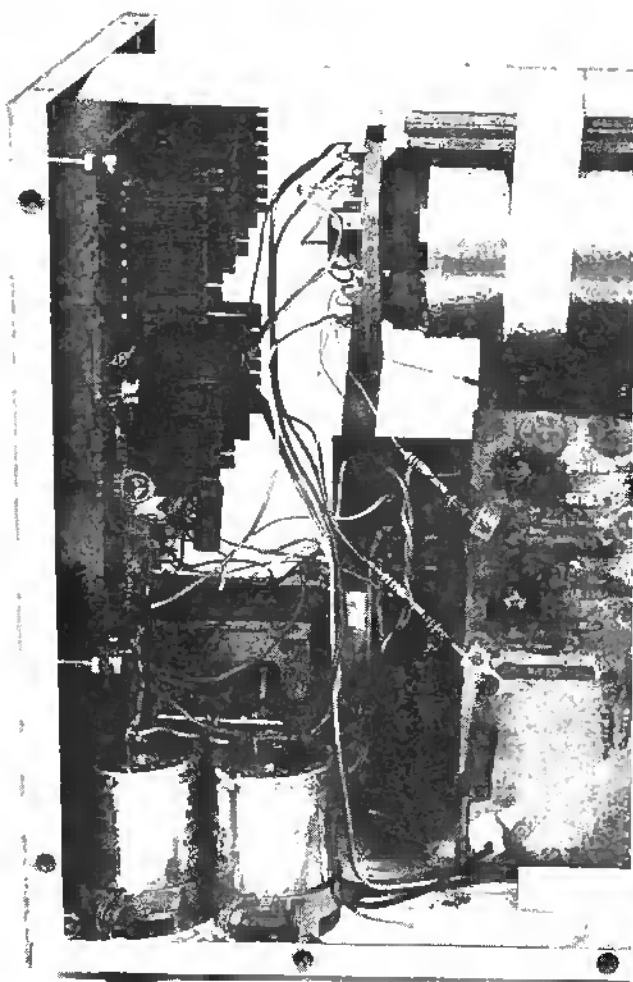
### Miscellaneous

- F1 1/2 inch x 1/2 inch, 1A fuse and holder
- S1 Miniature s.p.c.o. toggle switch
- S2 Miniature push button p.o.
- S3 2p 5w 2 wafer (Maka-switch)
- S4 2p 6w 1 wafer
- S5 Miniature s.p.c.o. toggle switch
- S6, 7 Miniature s.p.c.o. toggle switch
- SKT1 BNC socket, round 50Ω (UG1094/U)
- SKT2 4mm socket, black
- SKT3 4mm socket, blue
- SKT4 4mm socket, white
- SKT5, 6 4mm socket, green
- SKT7 4mm socket, yellow
- SKT8, 9 4mm socket, red
- SKT10 5 pin DIN-180° (A)
- CRT 3BP1 plus base
- Case mounting clips (vert) for C19, 20
- Edge connector 0.1 inch pitch 36 way 2 off
- Knobs Sifam 15mm collet fixing with nut covers and caps.
- K150 plain 2 off
- K151 line pointer 4 off
- W151 wing and line pointer 6 off



Connect all four deflection plates to the junction of the two resistors, i.e. approximately +100V. With VR5, VR6 and VR201 all set to midtravel, switch on and allow a few seconds for the tube heater to warm up.

Adjusting VR5 should produce a spot on the end of the tube and VR6 should enable it to be focused to a small diameter. If at either side of this setting it looks elliptical, wider or taller as VR6 is adjusted, VR201 (astigmatism) should enable this to be corrected. Mind where you put your hand when adjusting VR201, it's not far from the e.h.t. on Board 1! It should be possible to focus the spot down to a pinpoint, provided the brilliance control is not advanced too far, though of course VR201 will need resetting when Boards 3 and 4 are fitted.

In fact Board 3, the Y amplifier is the next step and full details of this will be published in next month's instalment.

Several readers have enquired about the possibilities of using alternative tubes for Purbeck. We cannot advise anyone as to the suitability of components other than those specified. Not only will the mechanical construction need alteration, but revised amplifiers and e.h.t. supplies will also be required.



NEXT MONTH IN...

# practical WIRELESS

ON SALE 2ND. JUNE


## Get on the Air

A 2m f.m. transmitter of nominal 10 watts output, having six crystal-controlled frequencies and provision for an external v.f.o.

Easily constructed on four simple printed circuit boards, the transmitter is housed in a quality instrument case and provided with a novel frequency readout.

The completed unit is both modern and professional in appearance.

## WITH THE PW 'AVON' 2m FM Transmitter

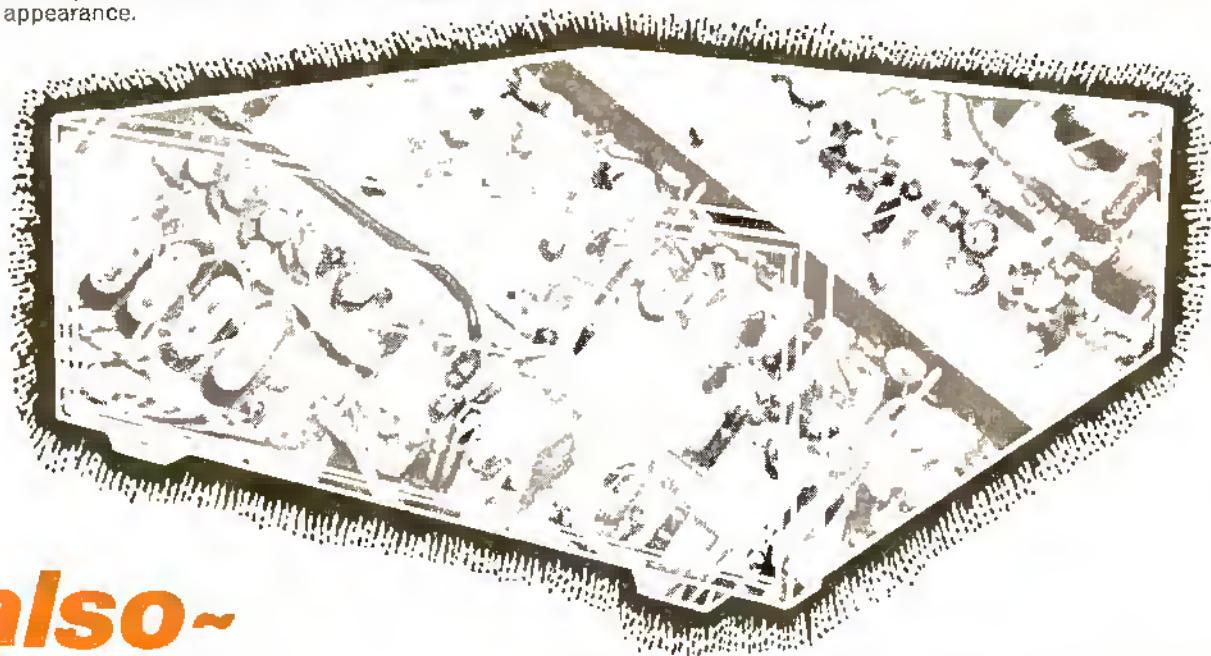

**also~**

### Introducing **DIGITAL LOGIC**




Beginning a primer in logic, which will cover gates, flip-flops and counters, characteristics of TTL and CMOS and design techniques.

### **Phase~ Locked Calibrator**

A simple circuit design which provides an accurate 200kHz output signal, phase-locked to the BBC's Droitwich transmitter, useful for calibration of receivers and digital frequency meters.

# STATESIDE CALLING

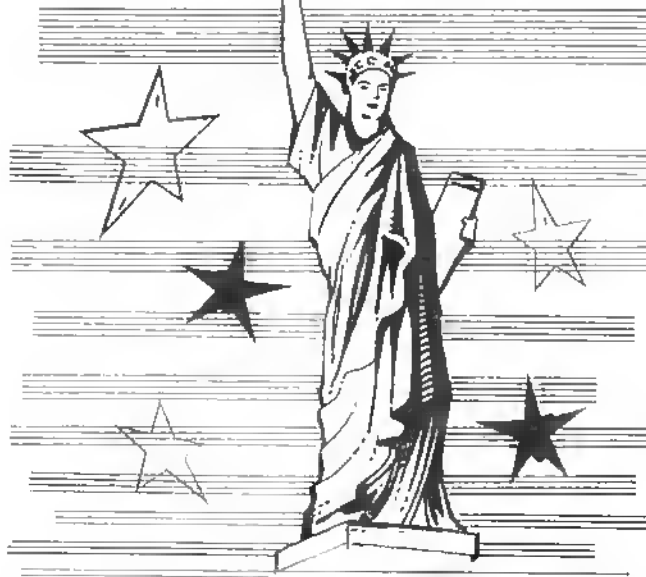

JOE KASSER G3ZCZ/W3

When one thinks of people in another part of the world, one usually imagines that their life style is almost identical to one's own. The fallacy of this concept is only obvious when one travels and is exposed to another way of life. Contrary to popular belief, radio amateurs are no different to other people and although the hobby is international, it takes on different forms in different countries. This article is an introduction to amateur radio in the United States of America.

## The Transmitting Licence

It is much easier to become a radio amateur in the USA than in the UK. There are several classes of Licence, each having different examination standards and frequency privileges, as shown in the table. In general, Novices have to pass an examination in elementary theory and a 5 w.p.m. Morse test. The examination is administered by a radio amateur volunteer on behalf of the licensing authority (which in the USA, is the Federal Communications Commission).

The Novice licence is valid for two years and until recently was distinguished by the WN prefix. It allows its owner c.w. only privileges in the 10, 15, 40 and 80 metre bands with a maximum power input of up to 250 watts.

The Technician class of licence requires slightly more technical knowledge than a Novice, and allows operating privileges similar to our Class B licence on segments of the 6 metre band and higher frequencies. The General, Advanced and Extra class licences are all allowed all-band, all-mode operation, but each class of licence (except Extra) is limited to segments of the band. The test for the General requires 13 w.p.m. c.w. and the test for the Extra requires 20 w.p.m. Increasing levels of technical knowledge are required for up-grading from one class to the next.

The licences are free and except for the Novice, are valid for five years. Separate mobile or TV licences are not required. The segments of the bands available to the different classes of licence are summarised in Fig. 1.

The band split between phone and c.w. is decided by the FCC for the amateurs, and not by the amateurs themselves as in most other parts of the world. In general the input power limits are 1kW input d.c. or 2kW input p.e.p. except on Top Band, which is segmented in both frequency and power depending on geographical location as shown in Fig. 2.

## The HF Bands

Operation on the h.f. bands is very different to that in Europe. The vast majority of the stations appear to be using the full legal limit and beam antennas. Thus the bands are crowded with strong signals all originating from the states, and it is difficult to hear non-stateside signals at times. The USA is so large that in general, any foreign station is DX.

The bands are so crowded that if you want to work the states from outside, you should get up into the General parts of the bands when they are open to the USA. You may then be giving the stations you work, their first G contact. If they want your QSL they will probably offer to QSL direct and even send you IRCs. There are many more of them than there are Gs, so if they are not in a rare state such as Utah or Delaware, let them QSL first. If they want your card, they will. If you operate in the Extra or Advanced segments of the bands the chances are greater that you will be working someone for his umpteenth G contact.

The 3-5MHz band is so wide (3.5-4.0MHz) that the c.w. part is called 80 metres, but the phone part is called 75 metres. At this point of the solar cycle, it

TABLE: US Amateur Radio Classes

Class	Morse Requirements	Technical Knowledge Required	Operating Privileges
Novice	5 w.p.m.	Hardly any	10, 15, 40 and 80m
Technician	5 w.p.m.	About RAE level	6m and higher
General	13 w.p.m.	About RAE level	All bands, some frequencies
Advanced	13 w.p.m.	A little more than RAE level	All bands, more frequencies
Extra	20 w.p.m.	As Advanced	All bands, all frequencies



offers cross continent contacts late at night. The 40 metre band has similar characteristics but is little used at night due to the vast amount of broadcast station interference. Sectors of the band allocated to broadcast stations in Europe are allocated to amateurs in the Americas and those broadcast stations come in loud and clear in the USA. The 20, 15 and 10 metre bands are pretty much the same as in Europe, in terms of distance worked, but are generally without the language barrier, because the common language in the states is English (more or less). There is thus very very little incentive for the American amateur to learn a foreign language.

## Traffic Handling

American radio amateurs have third-party traffic handling privileges. This means that they can pass messages for people other than radio amateurs. For example, a station in New York can contact a station in Los Angeles and ask that station to pass on a message to a non-amateur. He can even have him connect his radio to the telephone line via a phone patch and make a radiotelephone call, thus saving on his long distance telephone bill. There is a number of countries that have reciprocal agreements with the USA about third-party traffic; in other words they allow traffic to be passed between their country and the states. Thus on all bands one can hear a number of nets passing traffic messages. Once a year the American Radio Relay League (ARRL) organises a traffic handling contest (called Sweepstakes), in which the information exchanged simulates message traffic.

## The VHF Bands

At v.h.f. there is no 4 metre band, but there are operating privileges at 50MHz (6 metres) and 220MHz (1 $\frac{1}{4}$  metres). Six metres opens up to sporadic E much more often than 4 metres, and thus a lot of the activity is on c.w. and s.s.b. It has

properties very similar to 10 metres in terms of ground-wave communications capabilities, but DX is of course much more scarce on 6 than on 10.

The 2 metre band is 4MHz wide (144-148MHz). The top two megahertz are filled with f.m. repeaters and simplex channels spaced 30kHz apart. Small segments of localised s.s.b./c.w. activity exist close to 144 and 145MHz, but in the main the lower two megahertz comprise the wide open spaces. At the time of writing, the FCC is proposing to open some of it up for repeaters. There is OSCAR-related activity at about 145.9MHz. Thus apart from narrow and sparse areas of activity at 144, 145 and 145.9MHz the lower two megahertz is an uncharted wilderness at this time. Local s.s.b. or c.w. activity on a nation-wide basis is rare.

In most big cities, tuning the low end of the band by day will be very unrewarding with little to be heard. Even in the evenings you would be lucky to hear more than three simultaneous contacts taking place in the low half of the band, but during a contest a tremendous number of stations suddenly crawl out of somewhere and fill up the one or two hundred kilohertz. However, in the major cities the f.m. channels will be crowded. In most big cities all the repeater channels between 146 and 147MHz are in use as well as some of the 147-148MHz ones. There is no f.m. calling channel as such, just find a repeater and use it seems to be the rule.

In the states, the pioneers on v.h.f. set up repeaters to extend the range of their converted taxicab f.m. mobile equipment. As newcomers came on the band, they found the repeaters in existence and joined in. If people did not like a particular machine they were free to build and use their own on an adjacent frequency. In some parts of the country there were even repeater "wars" over choice frequencies between two repeater groups, each trying to force the other group to change frequency (this was before the days of synthesisers, when everyone was crystal controlled). Eventually voluntary frequency control was established by area-wide organisations. In the main how-


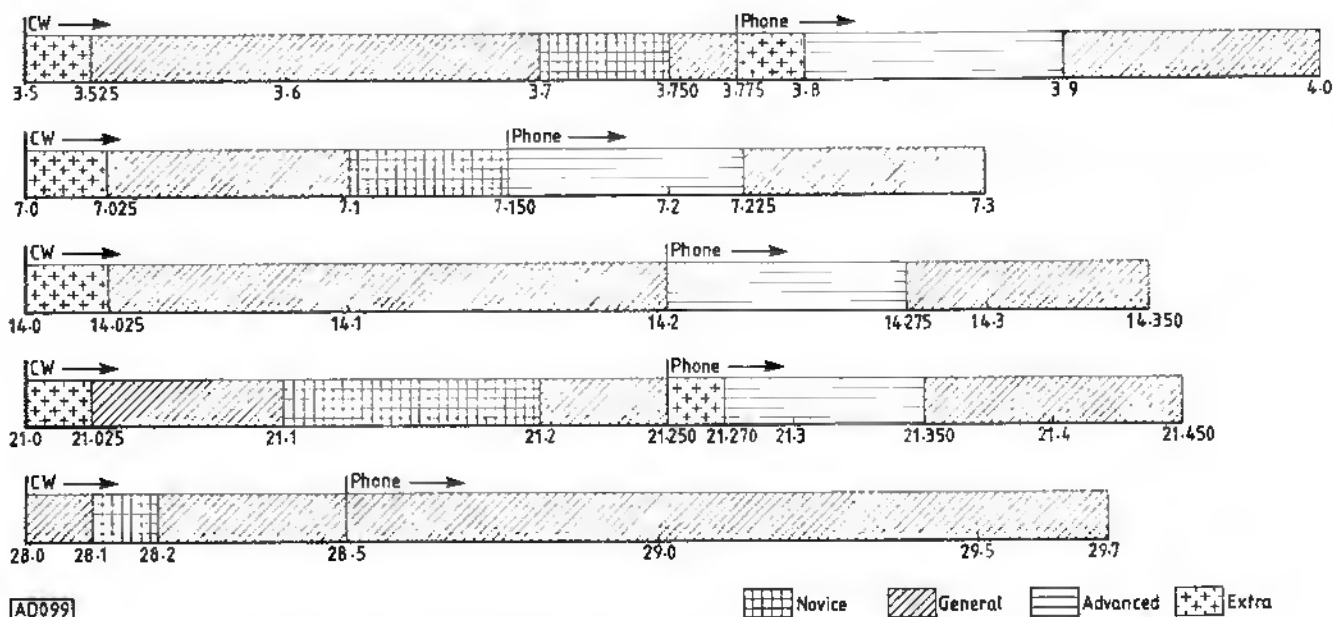


Fig. 1: HF Frequency Assignments in the USA. Note that higher class licenses have privileges in lower class segments, the table shows the lowest class allowed in each segment

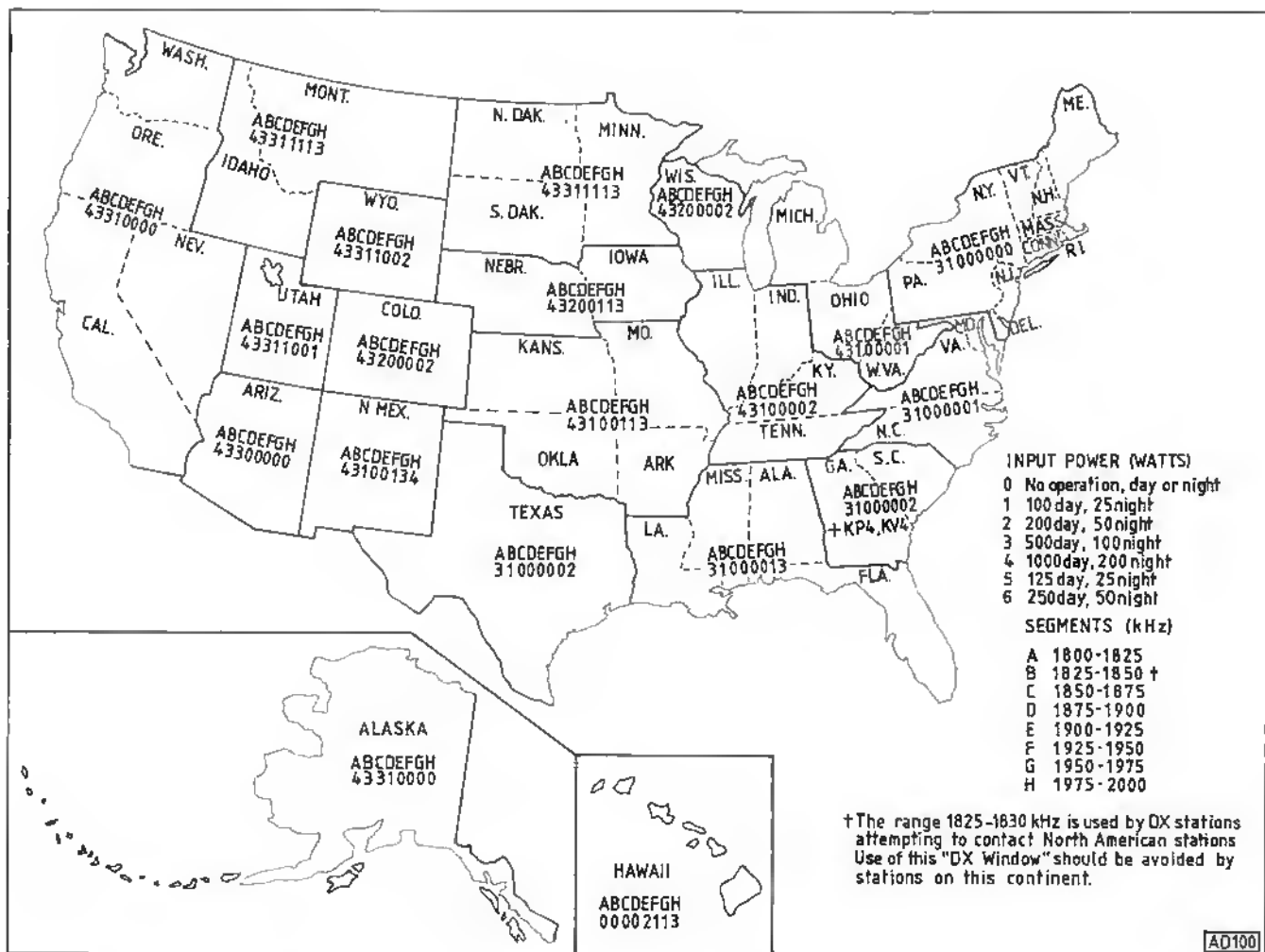

**Fig. 2: Top Band frequency allocations in the USA**

ever there have been few cases of deliberate interference with repeaters, because the newcomers to v.h.f., especially to 2m, generally only used f.m. and soon learned the advantages of the extended range and continuous monitoring of the repeaters.

In the UK the situation is different, the bands were in use before the advent of the repeaters. Also the 2m band is only two megahertz wide and everyone has to fit into it. Hopefully it will take just a short while for everyone to find out the advantages of repeaters and common sense will then prevail.

The 220MHz band is similar in characteristics to 2m. There is little in the way of s.s.b./c.w. commercial equipment for the band, and hence most of the activity is f.m. The same applies to 70cm. Here, most of the activity is f.m. between 440 and 450MHz, i.e. right at the top of the band, so that conversion of surplus equipment involves the minimum of changes. The 70cm band is also used for remote control of lower band repeaters and for inter-repeater links. Activity on higher frequencies is at par with Europe, namely very rare and due to only a few individuals.

## Using Repeaters

Many f.m. repeaters are connected to telephone lines. This allows for "auto patch" facilities, whereby amateurs can actually access the telephone network via the repeater and dial calls using the tones. They can report accidents to the police, call home and ask

the wife if they should stop off at the local supermarket and pick up some groceries, or do as one radio amateur did over one of the local machines here in Washington DC; while sitting in the garden by the side of the pool, he used his walkie talkie equipped with a touch-tone pad to dial his house phone and ask his wife to bring him out another can of beer!

The number of repeaters is constantly growing. The ARRL publishes an annual directory that is free for the asking to members. The frequencies are based on a 600kHz split with a spacing of 30kHz between channels. They are known by the kilohertz values, i.e. a repeater on 146.25MHz (in), 146.85MHz (out) is commonly known as the 25/85 machine. In the 146/147MHz region the input frequency is the lower one, whilst in the 147/148MHz region the reverse is true and the higher frequency is the input channel. This was carefully arranged this way so that receivers could be peaked up at 147MHz and work with the whole range of channels. These frequencies are of course not allocated to the amateur radio service in Europe, and on my last trip to the UK, I found that some of the American repeater output channels that I had in my rig were in use by the police.

Apart from f.m. the majority of activity on 2m and 70cm seems to involve OSCAR. Project Oscar started the whole thing in California with the launch of the OSCAR I satellite in 1961, and AMSAT took over in 1969. The ARRL puts out a lot of free



# MK14-the only low-cost keyboard-addressable microcomputer!

## The new Science of Cambridge MK14 Microcomputer kit

The MK14 National Semiconductor Scamp based Microcomputer Kit gives you the power and performance of a professional keyboard-addressable unit—for less than half the normal price. It has a specification that makes it perfect for the engineer who needs to keep up to date with digital systems or for use in school science departments. It's ideal for hobbyists and amateur electronics enthusiasts, too.

But the MK14 isn't just a training aid. It's been designed for practical performance, so you can use it as a working component of, even the heart of, larger electronic systems and equipment.

### MK14 Specification

- ★ Hexadecimal keyboard
- ★ 8 digit, 7-segment LED display
- ★ 512 x 8 Prom, containing monitor program and interface instructions
- ★ 256 bytes of RAM
- ★ 4MHz crystal
- ★ 5V stabiliser
- ★ Single 6V power supply
- ★ Space available for extra 256 byte RAM and 16 port I/O
- ★ Edge connector access to all data lines and I/O ports

### Free Manual

Every MK14 Microcomputer kit includes a free Training Manual. It contains



operational instructions and examples for training applications, and numerous programs including math routines (square root, etc) digital alarm clock, single-step music box, mastermind and moon landing games, self-replication, general purpose sequencing, etc.

### Designed for fast, easy assembly

Each 31-piece kit includes everything you need to make a full-scale working microprocessor, from 14 chips, a 4-part keyboard, display interface components, to PCB, switch and fixings. Further software packages, including serial interface to TTY and cassette, are available, and are regularly supplemented.

The MK14 can be assembled by anyone with a fine-tip soldering iron and a few hours' spare time, using the illustrated step-by-step instructions provided.

### Tomorrow's technology – today!

*"It is not unreasonable to assume that within the next five years . . . there will be hardly any companies engaged in electronics that are not using micro-processors in one area or another."*

Phil Pittman, Wireless World, Nov. 1977.



Just  
**£39.95**  
(+ £3.20 VAT, and p&p)

The low-cost computing power of the microprocessor is already being used to replace other forms of digital, analogue, electro-mechanical, even purely mechanical forms of control systems.

The Science of Cambridge MK14 Standard Microcomputer Kit allows you to learn more about this exciting and rapidly advancing area of technology. It allows you to use your own microcomputer in practical applications of your own design. And it allows you to do it at a fraction of the price you'd have to pay elsewhere.

Getting your MK14 Kit is easy. Just fill in the coupon below, and post it to us today, with a cheque or PO made payable to Science of Cambridge. And, of course, it comes to you with a comprehensive guarantee. If for any reason, you're not completely satisfied with your MK14, return it to us within 14 days for a full cash refund.

**Science of Cambridge Ltd,**  
6 Kings Parade,  
Cambridge,  
Cambs., CB2 1SN.  
Telephone: Cambridge (0223) 311488

Regd No. 213817088.

To Science of Cambridge Ltd,  
6 Kings Parade, Cambridge,  
Cambs., CB2 1SN.

Please send me an MK14 Standard  
Microcomputer Kit. I enclose cheque/  
Money order/PO for £43.55 (£39.95  
+ 8% VAT and 40p p&p).  
Allow 21 days for delivery.

Name \_\_\_\_\_

Address (please print) \_\_\_\_\_

\_\_\_\_\_  
\_\_\_\_\_  
\_\_\_\_\_

# Science of Cambridge

PW6

# TRANSFORMERS

ALL EX-STOCK—SAME DAY DESPATCH. VAT 8%

## 12 AND 24 VOLT OR 12-0-12V PRIMARY 220-240 VOLTS

Ref	12V	24V	£	P & P
111	0-5	0-25	2.28	0.45
213	1-0	0-5	2.84	0.78
71	2	1	3.51	0.78
18	4	2	4.43	0.95
70	6	3	5.35	0.95
108	8	4	6.26	1.14
72	10	5	7.17	1.14
116	12	6	8.09	1.32
57	16	8	10.39	1.32
115	20	10	13.18	2.08
187	30	15	17.95	2.08
226	80	30	28.32	O.A.

## 30 VOLT RANGE

Prim 220/240V Sec 0-12-15-20-24-30V  
12V-0-12V or 15V-0-15V available by connection to appropriate taps.

Ref	Amps	£	P & P
112	0-5	2.64	0.78
79	1-0	3.37	0.96
3	2-0	4.27	0.96
80	3-0	5.20	1.14
21	4-0	7.44	1.14
51	5-0	8.37	1.32
117	6-0	9.29	1.45
85	8-0	11.73	1.64
89	10-0	13.33	1.84

## 60 VOLT RANGE

Prim 220/240V Sec 0-24-30-40-48-60V  
24V-0-24V or 30V-0-30V available by connection to appropriate taps.

Ref	Amps	£	P & P
124	0-5	3.88	0.96
125	1-0	4.58	0.96
127	2-0	7.49	1.14
125	3-0	10.84	1.32
123	4-0	12.33	1.84
40	5-0	13.95	1.84
120	6-0	15.86	1.84
121	8-0	28.15	O.A.
122	10-0	24.93	O.A.
189	12-0	27.13	O.A.

## MAINS ISOLATING (SCREENED)

PRIM 120/240 SEC 120/240 CT

Ref	VA (Watts)	£	P & P
*97	20	4.40	0.79
149	50	6.28	0.95
150	100	7.18	1.14
151	200	11.38	1.50
152	250	12.78	1.84
153	350	16.28	1.84
154	500	19.35	2.15
155	750	29.96	O.A.
156	1000	37.50	O.A.
157	1500	45.00	O.A.
158	2000	54.00	O.A.
159	3000	79.05	O.A.

\*State Volts required 115V or 240V.

## HIGH VOLTAGE MAINS ISOLATING

Prim 200/220V or 400/440V  
Sec 100/120V or 200/240V

Vs	Ref	£	P & P
80	243	5.89	1.32
350	267	14.11	1.84
1000	250	41.76	O.A.
2000	252	54.25	O.A.

Our wide range of transformers are too numerous to list, please call (open 9am-5pm Mon-Fri) or send your requirements. Electroil & semiconductor stockists. Panel, Multi Meters, Audio accessories, send 15p stamps for lists.

## SCREENED MINIATURES

Ref	mA	Volts	£	P & P
238	200	3-0-3	1.99	0.55
21	1A, 1A	0-5-0-5	2.25	0.78
11	100	0-0-0	2.14	0.38
235	330, 330	0-0, 0-0	1.89	0.38
207	500, 500	0-8-8, 0-8-8	2.59	0.71
208	1A, 1A	0-8-0, 0-8-0	3.53	0.78
236	200, 200	0-15, 0-15	1.89	0.38
214	300, 300	0-20, 0-20	2.50	0.78
221	700 (DC)	20-12-0-12-20	3.41	0.78
208	1A, 1A	0-15-20-0-15-20	4.03	0.96
203	500, 500	0-15-27-0-15-27	3.99	0.96
204	1A, 1A	0-15-27-0-15-27	5.38	0.96
239	50	12-0-12	1.89	0.38
S112	500	12-15-20-24-30	2.84	0.78

## COMPONENT PAKS

50 High Quality Metal Oxide  
2 x 5% 1/4 + 1/4 W resistors.  
150 Mixed Value Capacitors.  
10 Reed Switches.  
30 Wire Wound Resistors mixed.  
25 Assorted presets.  
30 3 tag terminal strips.  
Hardware pack nuts, bolts, washers, insulators  
70p. P & P 40p. VAT 12 1/2%

## BRIDGE RECTIFIERS

200V 2A £1.45  
400V 2A £0.55  
200V 4A £0.05  
400V 4A £0.00  
400V 6A £1.05  
500V 10A\* £2.35  
VAT 12 1/2% \*VAT 8% P & P 15p.  
AVO cases and accessories  
Magnetic to Ceramic Cartridge Converter (MFA 30) operating Voltages 20-45 £3.50 VAT 12 1/2%, p & p 35p.

## MINI-MULTIMETER

DC-1000V AC-1000V DC-100mA Res-150kΩ  
1000Ω/V Bargain £5.86. VAT 8% P & P 52p.  
30,000 ohm/V Multi-meter—mirror scale  
Ranges AC/DC to 1000V DC current to 250mA  
Resistance to 3 Mohms.  
5" x 3 1/2" x 1 1/2". £11.09. P & P £1.05. VAT 8%

## Special offer Avo Meter (107)

Mk IV style. Ranges DC to 1000V current to 1 amp AC to 1000V 3 ohmic ranges to 10M ohms. 10,000V D.C. 1000 AC safety cut-out £45.00 PP £1.15. VAT 8%

## 12 way Grelco heavy black plastic terminal block

39p. 15p p&p. Panel fuse holder 1 1/2" completely enclosed pull-out type 25p, 15p p&p. 2 x Fuse boards 2 open 1 1/2" fuse holders 2 1/2" x 3 1/2" p & p 15p. VAT 8%.

## TEST METERS

AVO 8 Mk5	£21.00	AVO MM5	£24.00
AVO 71	£23.00	Wee Megger	£58.00
ACO 73	£30.00		
AVO T169	In circuit Transistor Tester	£30.00	
U435	Budget Meter 20kΩ/VDC, 2kV/VAC 1000V AC/DC, 2 1/2 A AC/DC		

## Plug in Save Batteries!

3300 fits into 13A socket 6-7 5-9V  
300mA multiplug outlet £3.30  
Stabilised 3-6-7 5-9V/400mA multiplug outlet £6.81  
VAT 12 1/2% P & P 55p

## TRANSFORMERS SPECIAL OFFER

BE1 Prim 0-120, 0-120V (120 or 240V) Sec 24V 10A £3.99 P & P £1.56  
BE7 0-110-120-220V Pk1, 240V, Sec 20V 1A £1.75, 35p p&p  
BE3 100V line to 4Ω 7 1/2W £2.05 P & P 68p  
BE4 Prim 120 or 240V 9-0-9 1A £1.88 P & P 0-38  
BE5 15W matching trans. sec 15Ω 15V £1.59 £1.35 P & P 30p, Ref. 30  
240-240 Isolator 200VA £4.20 P & P  
BE6 Pri: 0-220V sec 4500V 10MA £4.50 P & P £1.00  
30p, Ref 62 240-240 Isolator 250VA £3.20 P & P 96p.

## ELECTRONIC CONSTRUCTION KIT

10 projects (including electronic organ). No soldering needed £7.29. VAT 8% P & P 70p

## NEW RANGE HIGH QUALITY TRANSFORMERS

Sec 45-38-0-39-45 Sec to give 36-0-36, 36-0-36, 45-0-45V, 72V or 90V.

VA	£	P & P
2A	£1.89	£1.38
3A	£1.47	£1.48
4A	£1.90	£1.84
5A	£1.74	£2.15
6A	£20.77	£2.38

## PANEL METERS

2" 0-50µA	£5.50	4" 0-50µA	£6.70
0-500µA	£5.50	0-500µA	£8.70
0-1mA	£5.50	0-1mA	£8.50
0-50V	£5.50	0-50V	£8.48

## ISOLATOR—1 KVA 240V to 240V enclosed style terminal connection. Special offer at

£18.78. Carriage £2.75. Ref. BE7.

## I MILLION ELECTROSIL RESISTORS EX STOCK

Prices correct 27-11-77. Please add VAT after P & P.

## DECS SOLDERLESS BREAD-BOARDING

S Dec 70 contacts £1.99  
T Dec 208 contacts £3.63  
U Dec "A" for I.C.s etc £3.99  
U Dec "B" for I.C.s etc £6.99  
VAT 8% P & P 40p

## ANTEX SOLDERING IRONS

15W £3.75 18W £3.75  
25W £5.75 Stand £1.40  
VAT 8% P & P 46p

## Audio kit 25W + 25W. Complete with instructions £35.50. Yeak:

Cab-mounting hardware £14.50. P & P £1.78. VAT 12 1/2%

## Stereo FM Tuner with Phase Lock Loop. 4 pre-selected stations varicap tuning switched. A.F.C. LED Beacon £20.45. VAT 12 1/2% P & P 40p

Barrie Electronics Ltd. 3, THE MINORITIES, LONDON EC3N 7JF TELEPHONE: 01-483 3316/7/8 NEAREST TUBE STATIONS: ALDGATE & LIVERPOOL ST



# Wilmslow Audio

THE firm for speakers!

SEND 15P STAMP FOR THE WORLD'S BEST CATALOGUE OF SPEAKERS, DRIVE UNITS, KITS, CROSSOVERS ETC. AND DISCOUNT PRICE LIST.

- ATC • AUDAX • BAKER • BOWERS & WILKINS • CASTLE • CELESTION • CHARTWELL COLES • DALESFORD • DECCA • EMI • EAGLE • ELAC • FANE • GAUSS • GOODMAN • HELME • I.M.F. • ISOPHON • JR • JORDAN WATTS • KEF • LEAK • LOWTHER MCKENZIE • MONITOR AUDIO • PEERLESS • RADFORD • RAM • RICHARD ALLAN • SEAS • TANNOY • VIDEOTONE • WHARFEDALE

## WILMSLOW AUDIO (Dept. P.W.)

SWAN WORKS, BANK SQUARE, WILMSLOW, CHESHIRE SK9 1HF

Discount HiFi Etc. at 5 Swan Street and 10 Swan Street  
TEL: WILMSLOW 29599 FOR SPEAKERS  
WILMSLOW 28213 FOR HiFi

## MAIL ORDER DEPT:-

# CRESCENT RADIO LTD

1 ST. MICHAELS TERRACE, WOOD GREEN, LONDON, N22 4SJ

TELEPHONE: 888-4474

## 3 KILOWATT PSYCHEDELIC LIGHT CONTROL UNIT

1000 WATT PER CHANNEL.  
Three channel: Bass, Middle, Treble.  
The input of this unit is connected to the loudspeaker terminals of an amplifier and the required lighting is connected to the output terminals of the unit thus enabling you to produce a fascinating sound to light display.  
Full instructions supplied or S.A.F. for details.  
Fantastic Value at £20.00 + 8% VAT.

## LOUDSPEAKER SELECTION

+ 12 1/2% VAT  
2 1/2" 8, 40 and 75 ohm at £1.30 (Please state which impedance is required)  
5" 8 ohm CERAMIC at £1.70  
8" GOODMAN'S 'Audiom 8PA' 8 ohm 16w at £5.86  
10" 'ELAC' Dual Cone 8 ohm 10 watt at £4.75

## POWER SUPPLY UNITS + 8% VAT

PP1—Switched 3, 4, 6, 7 1/2, 8, 12v at 600mA with on/off switch and pilot light. Approx size: 130 x 55 x 75mm. ONLY £2.80  
PP2—Heavy duty 12 volt power supply. 1.5A at 12 volt DC. Approx. size: 155 x 90 x 95mm. ONLY £5.00.

## BARGAIN TRANSFORMERS

240v primary, 12-0-12v 500mA secondary. Approx size: 60 x 40 x 60mm. Fixing centres 75mm. PRICE: £1.80 + 8% VAT. Also available Mains transformer with 18V 600mA sec. Price and size same as above.

## EAGLE TRANSFORMERS

LT44 Miniature driver transformer  
PRIM. 20K Ω. SEC. 1K Ω.  
LT700 Miniature output transformer, 200W.  
PRIM. 1-2K Ω. SEC. 9-2 Ω.  
PRICE: EITHER OF THE ABOVE 21p + 12 1/2% VAT.

## MAINS TRANSFORMERS

MT6 240v PRIM. 6/0/6v 100mA SEC.  
MT12 240v PRIM. 12/0/12v 50mA SEC.  
PRICE: MT6, MT12 £1.17 + 8% VAT.  
MAINS TRANSFORMERS WITH TWO INDEPENDENT SECONDARY WINDINGS.  
MT100. PRIM. 240v. SEC. 0-24v, 0-36v @ 100mA.  
MT150. PRIM. 240v. SEC. 0-12v, 0-12v @ 150mA.  
MT280. PRIM. 240v. SEC. 0-6v, 0-6v @ 280mA.  
PRICE: MT100, MT150, MT280 £2.62 + 8% VAT.

## MAINS TRANSFORMERS

MT40. PRIM. 240v. SEC. 20/0/20v @ 1A. PRICE: £3.16 + 8% VAT.  
MT10, MT15, MT20 100 volt line transformers.  
PRICE: MT10, MT15 £2.25 + 8% VAT. MT20 £2.98 + 8% VAT.  
INPUTS ON THESE: 8 or 16 OHMS. S.A.F. for details on these or any of the above.  
Please add 26p p&p to all orders for Eagle Transformers.

## PIEZO ELECTRIC HORN UNITS 100 watt

New High Quality, High Power Tweeter. No Kover required. Freq. Response: 3-8KHz to 28KHz. Spec. Sheet sent on receipt of S.A.F.  
OUR PRICE: £9.50 each + 8% VAT.

ACCESS AND BARCLAYCARD ACCEPTED—PHONE ORDERS WELCOMED  
ALL PRICES INCLUDE POSTAGE UNLESS OTHERWISE STATED—PLEASE ADD V.A.T. AS SHOWN—B.A.E. WITH ALL ENQUIRIES PLEASE.  
Personal callers welcome at: 21 GREEN LANE, PALMERS GREEN, W13. Phone: 888-3266 and 13 SOUTH MALL, EDMONSTON W9 Phone: 808-1655



educational stuff about the OSCAR satellite programme, which by-the-way is available to anyone worldwide, for the asking. Worked All States via OSCAR is just possible for Eastern stations and is well within the capabilities of anyone in the continental United States west of the Mississippi river.

## Equipment

Salaries in the states are generally at between two and four times the level of the equivalent salary for the same job in the UK. Thus on a basis of hours worked, equipment is much cheaper over here. The large number of amateurs support a few manufacturers so that there is quite a variety of domestic gear available as well as the ubiquitous Japanese black boxes.

Parts for the homebrewer are also readily available by "mail". Many suppliers advertise in the various magazines, and their wares can be ordered by post, or by telephone quoting credit card numbers.

Crystals for 2m transceivers are available over the counter in most major cities and the prospective visitor can wait until he arrives in the USA to purchase the bulk of his crystals. If he is lucky the store may even have facilities for tuning the rig frequency. If you are interested in operating in the USA when visiting this country you can obtain detailed information from the RSGB, or write to the FCC, Washington DC, 20554 for an application form (Form 610A). Make sure that you send in your application at least three months before your trip, because it will take them that long to reply.

## Listening and Viewing

The receiving side of the hobby is also somewhat different. The medium waves, f.m. and v.h.f. TV bands are filled in most major urban areas. Medium wave DX-ing is a little easier than in Europe, because most of the stations broadcast in English. Stations are spaced 10kHz apart, which enables the inter-continental DX to creep in between the cracks. The majority of stations are east of the Mississippi. The FCC recognise the sky-wave effect at night and regulate the band occupancy such that many local stations are required to close down at local sunset. This allows clear-channel stations to be heard over continental distances at night. It is thus for example possible to drive through downtown Los Angeles in the evening, tune the car radio a little and listen to broadcasts from Denver, Oklahoma and Iowa, or to drive around in Washington DC and listen to stations in Montreal, Chicago and New Orleans.

The v.h.f. TV bands are also full in most cities with some additional channels in the u.h.f. bands in use. All transmissions in the Americas are 525-line 30-fields, thus there are no modifications necessary to the TV sets for their use in TV DX-ing. The f.m. band is 20MHz wide in the range 88-108MHz, with 88-92MHz being reserved for public broadcasting stations. These stations, usually run by universities or local authorities, broadcast educational programmes, classical music and selected shows from the BBC (including the *Goon Show*) as opposed to the popular music or news churned out by the commercial stations. There are three major networks in the states that broadcast commercial programmes, and each city usually has a local outlet of each as well as one or more independent stations and the public station. This allocation applies to television as well as radio. Recent broadcasts on public television have included, *I Claudius* and *Upstairs-Downstairs*.

Many of the independent TV stations broadcast old films and TV shows including *UFO*, *The Saint*, *The Prisoner*, *The Avengers* and *Danger Man*. The f.m. stations usually broadcast in stereo. Both medium wave and f.m. stations usually churn out popular music, each specialising in a particular type, and there may be one or two stations that continually broadcast news. The u.h.f. TV band is relatively sparsely populated, its growth being curtailed by cable television systems.

## Citizen's Band

Closely related to amateur radio is Citizen's Band Radio. The Citizen's Band is a small allocation of spectrum space at about 27MHz. It seems to have been originally allocated for personal communications between a fixed base station and a mobile (so that for example, a husband could talk to his wife on the way home from work) or between mobiles, so that the drivers of two cars travelling together can communicate.

Licences are now available free for the asking, with no tests involved. Power input is limited to 5 watts d.c. a.m. and equipment is cheap. A forty-channel transceiver can be purchased for about \$50. There are estimated to be millions of CB stations in service, the majority of them being unlicensed.

Homo sapiens is a creature of invention. The American branch of that species, perhaps more inventive than other branches, has devised new uses for the Citizen's Band. Lorry drivers use it to warn each other of impending police radar speed traps. Prostitutes have been known to solicit customers via CB radio. Hobby operation including QSL'ing abounds and most stations use self-given "handles" rather than their official call signs, always assuming that they have an original call sign.


Illegal power amplifiers are often used and some operators are even equipped with amateur band equipment such as Yaesu FT101s. In the cities the channels are overcrowded and communication ranges are limited by the numbers of conversations taking place on the frequency. One channel has been set aside for emergency use (ch 9) and one is used as a calling channel (ch 19). Almost everyone monitors channel 19 when on the road unless they have QSYd for a particular reason to another channel, and contribute traffic and police location information. Hitchhikers also solicit rides over channel 19. One neighbour of mine estimated that in two weeks of use he recouped the cost of the equipment due to the timely warning he received about the locations of police radar speed traps that would otherwise have caught him. Citizen's Band is a boon if used correctly, but if abused is a mess.
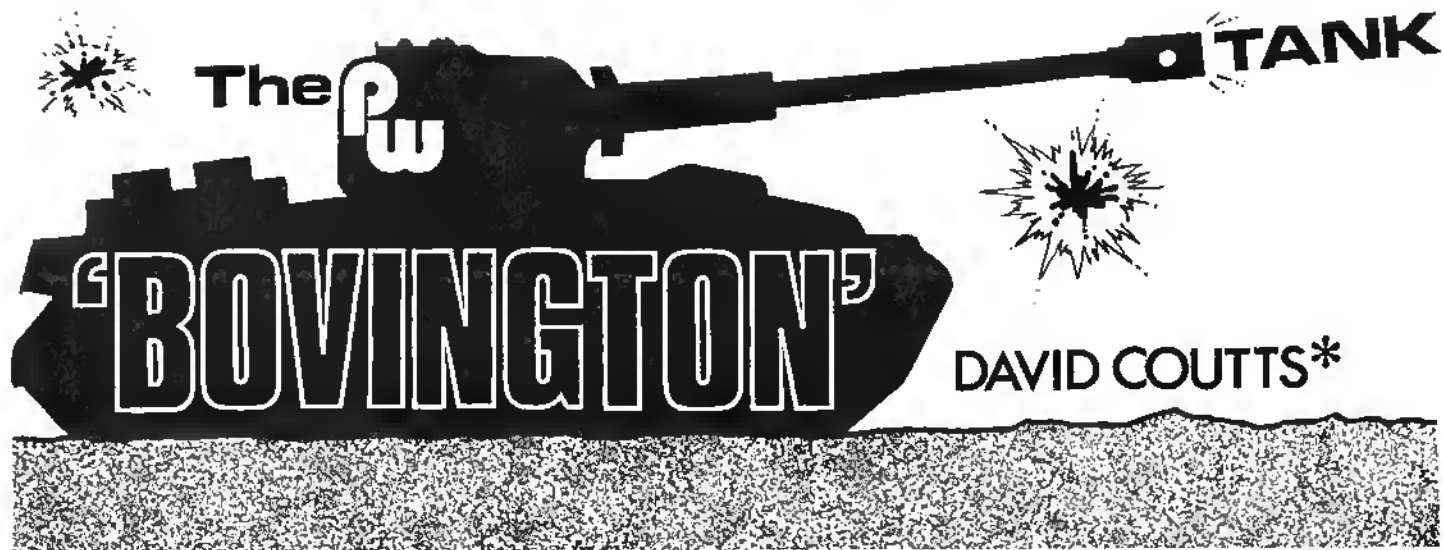
## Microprocessors

The latest arrival on the electronics hobby scene is the home computer based on the microprocessor. Thousands have been sold and clubs are forming all over the country. Microcomputers can be the subject of many articles in themselves, but suffice it to say for now that their use is invading the home as well as the amateur radio shack. It is estimated that within five years the vast majority of homes in the US will contain at least one microprocessor.

This article has been an introduction to amateur radio and the electronics scene in the United States. Future articles will go into more detail about the various aspects of the hobby. ●





The General Instrument AY-38710 integrated circuit is a 625 line interlaced "TV Tank Battle Game" for two players. The "battleground" consists of white barriers and a series of black mines. There is one white and one black tank, each controlled by two single pole double throw paddle switches biased to centre off. A push button for each player controls gun firing and a push button allows the battle to be reset. Pin 22 of the i.c. is switched to control the tank traps. In the open position the tanks can drive through these barriers, in the other position (grounded) the tanks halt when they collide with them. Motor sounds are provided for each tank as well as gun fire and shell explosions, and the score is coded to each tank. The tanks are driven like real tracked vehicles, pushing both switches forward causes the tank to go forward. If the switches are held the tank automatically speeds up after a few seconds. If the switches are released the tank continues at the speed reached at the time of release. Pulling both switches back causes the tank to reverse, while holding one switch back and one forward causes the tank to rotate. To stop the tank when it is going forward momentary selection of reverse is required. The shell has a range of about two thirds of the screen and after firing there is a reload period before you can fire again. The shell can be steered during its flight by rotating the tank. The shell will pass over the mines but will explode on hitting barriers. A hit on your opponent counts one point, while running over a mine counts one against you. When one player reaches 16 hits the scores flash to show that the game has ended.

## Circuit Description

The circuit diagram is shown in Fig. 3. T1 provides 12-0-12 volts which is full wave rectified by D1 and D2 and smoothed by C1. IC1 regulates the supply VP to approximately 6.5 volts, VR1 adjusting the voltage and C2, 3 and 4 providing decoupling. IC4 a and b provide the 4 MHz clock to the AY-38710, L1 being adjustable to allow the oscillator to be set to the correct frequency. IC3 a and b, with their

associated Rs and Cs, provide the shaping for the fire and explosion sounds. IC3c does the same for the motor sounds which are all fed via IC3d to the output transistors TR1 and TR2. Switches S4, 5 and 6 control the left tank and S7, 8 and 9 control the right tank. S3 is the game reset and S2 is the tank trap switch. R2 to R4 mix the video signals and the composite video is buffered by the emitter follower TR3 and fed to the modulator.

TR4 and its associated components act as the modulator which runs at a frequency of approximately 160-170MHz, with harmonics extending into the u.h.f. band.

## Construction

Construction is relatively straightforward, most of the components being mounted on the p.c.b. It is, however, advisable to use sockets for IC2, 3 and 4. The component layout is shown in Fig. 7. Drill 6BA clearance holes for board fixing, FS1, T1 and IC1, and a 6mm hole for L1. Drill other holes to suit the component leads. Before mounting any components on the board place the p.c.b. in the box with a modulator at the front right, and the p.c.b. about 10mm from the right side of the case. Drill 4 fixing holes in the bottom of the case using the p.c.b. as a template. Also drill a 6mm hole in the bottom to line up with L1 core. Put the p.c.b. to one side and drill the box and front panel as shown in Fig. 1. Also drill a few 6mm holes in the base and rear of the case for ventilation. Stick a small piece of speaker cloth over the rear of the speaker hole on the front panel, fix the speaker in place with epoxy adhesive and mount the switches S1, 2 and 3. The sound output is controlled by VR3 which is mounted on the front panel.

Assemble the p.c.b. using the layout Fig. 7 and parts list as a guide but do not fit IC2, 3 or 4 into their sockets yet. R9 can be either a 20M $\Omega$  resistor or two 10M $\Omega$  resistors (R9a and R9b). Fit a TO5 heatsink to TR2, cut and bend a piece of aluminium sheet 60mm x 35mm as a heatsink for TR1 as shown in Fig. 4, drilling through the p.c.b., and retaining IC1 and the heatsink with a 6BA screw. Cut and bend

\*An Engineer with General Instrument Microelectronics, Glenrothes

**PULL-OUT**

# practical **WIRELESS**

**INDEX TO**

## **Volume 53**

**MAY 1977 TO APRIL 1978**

*Pages*

1—84  
85—164  
165—244  
245—316  
317—388  
389—468  
469—544  
545—632  
633—712  
713—792  
793—872  
873—952

*Issue*

May 1977  
June 1977  
.. July 1977  
August 1977  
September 1977  
October 1977  
November 1977  
December 1977  
January 1978  
February 1978  
March 1978  
April 1978

The format of Practical Wireless was increased in size beginning with the issue dated September 1977

**IPC Magazines Ltd,  
Westover House,  
West Quay Road,  
POOLE,  
Dorset, BH15 1JG.**

# INDEX

Volume 53

May 1977 to April 1978

## CONSTRUCTIONAL—Audio

Active Tone Control by F. G. Canning ...	814
Audio Level Indicator by W. Pleass ...	442
'Europa' Stereo Amplifier by C. Toms Part 1	832
Part 2	912
'Jubilee' Electronic Organ by M. J. Hughes	
Part 1 352, Part 2 426, Part 3 505, Part 4	
581, Part 5 665. Kindly Note 677, 755, 837,	938
Multivib 'Musico' by R. H. Longden ...	732
Portable PA Amplifier by S. H. Davies ...	566
Reverberation Amplifier by S. C. Parsons	104
2-Way Intercom by S. Davies ...	22
20W IC Audio Amplifier by F. G. Rayer	182

## CONSTRUCTIONAL—Receiving

All-Band SW Converter by F. G. Rayer Part 1	490
Part 2	598
Atomic Time Receiver by N. C. Helsby	288
Kindly Note	454, 518
CW Filter Unit by A. Langton ...	134
Direct Conversion Receiver by M. Tooley ...	652
Kindly Note	837
General Purpose SW Receiver by F. G. Rayer	
Part 1	337
Part 2	425
LED Tuning Indicator by J. P. Macaulay ...	577
Narrow Band FM Demodulator by W. Bond ...	277
Radio 2 Tuner for your Hi-Fi by R. A. Pentold	213

## CONSTRUCTIONAL—Test Equipment

Aerial Performance Test Set by F. C. Judd	678
Audio Dummy Load by F. G. Rayer	745
A 741 Signal Tracer by W. Mooney ...	193
Kindly Note	305
Audio Visual Logic Probe by P. Pond ...	842
Extender for PW Transistor Tester (July-Aug	
76) by I. Hickman ...	136
Heatsink Thermometer by I. Hickman ...	750
Low Distortion Sine-Square Wave Generator	
by M. Tooley ...	412
Kindly Note	574
Multirange Testmeters by D. Jones ...	838
Oscilloscope Viewing Hoods by M. Allenden ...	760
'Purbeck' Oscilloscope by I. Hickman Part 1	892
RF Resonance Indicator by D. H. E. King	497

Versatile AF Generator by C. Toms	108
VHF Wavemeter by M. Tooley ...	920
Wide Range Voltmeter by M. Tooley	486

## CONSTRUCTIONAL—General

Battery State Indicator by W. Mooney	849
Compact 2-metre Beam Aerials by F. C. Judd	57
Design Your Own Projects by T. Bailey and R. Whitaker	
1. Light Trigger ...	358
2. Cassette Recorder Power Supply	436
3. Car Courtesy Light ...	512
4. Impedance Matching Amplifier	602
5. Continuity Tester	685
6. TTL Interface Circuit ...	896
Economy Timing Strobe by B. Harvey ...	752
Extra Data	919
Electronic Car Voltage Regulator by C. Grayson	363
Handi-Mini Power Supply by I. Hickman ...	260
Laboratory Power Supply by J. Thornton-Lawrence ...	588
Morse Tutor by D. J. Edwards	263
Mystery Train Tour by E. A. Parr ...	822
Kindly Note	938
Proportional Power Controller by C. Toms	672
Kindly Note	837
Protected Battery Charger by G. O. H. Sjogren	50
S-DeCnology by D. Gibson	
No. 6. The Ohm Gnome ...	39
No. 7 Medium Wave Receiver	121
No. 8 Ultra-Simple Audio Amplifier	188
No. 9 Light-to-Frequency Converter	294
No. 10 Record Player Amplifier	345
No. 11 Automatic Courtesy Light	595
No. 12 The Might Light	756
u-DeCnology by D. Gibson	
1. Simple Light Modulator	826
2. The Grip'n Grow ...	917
'Seekit' Metal Locator by W. Opel Part 1	42
Part 2	117
'Slim Jim' 2-metre Aerial by F. C. Judd	899
'Solo Supermind' by A. Willcox ...	408
Kindly Note	574
'Tele-Games' by D. S. Coutts ...	124
Kindly Note	305
'Tele-Games' Add-on Module 'Shoot'	
by D. S. Coutts ...	280
Traffic Light Controller by P. Chambers ...	584
Kindly Note	837
24-Hour Digital Clock by J. Miller-Kirkpatrick	204



## EXPERIMENTER'S CORNER

Basic 9V Stabiliser by R. N. Soar ... ..	762
LED Light Display by A. Cooper ... ..	910
Simple Low-Z Pre-amplifier by D. L. Jones ...	762
Transistor Gain Indicator by S. Lamb ... ..	910

## IC of the MONTH by B. Dance

No. 62 SGS-ATES TBA820LV Audio Amplifier	34
No. 63 RCA CA3140 Operational Amplifier ...	216
No. 64 Ferranti ZN1034E Timer ... ..	516
Kindly Note ... ..	574
No. 65 Thompson-CSF TCA900/910 Speed Regulator ... ..	604
No. 66 Thompson-CSF ESM1601 Proximity Detector ... ..	738
No. 67 Sprague ULN3006T Half-Effect Switch	845
No. 68 2N5777 Photo-Darlington Sensor ...	905

## KINDLY NOTE

<i>Points arising from articles in the previous volume</i>	
Gas/Smoke Sensor Alarm April 1977 ... ..	106, 755
Tug 'o' War Game April 1977 ... ..	38, 222

## MISCELLANY—Technical

Circuits for Audio Amplifiers by F. G. Rayer (Part 1 March 1977, Part 2 April 1977)	
Part 3 ... ..	47
Part 4 ... ..	141
FM Front Ends by B. Dance ... ..	269
Hotlines (recent developments in electronics) by Ginsburg 30, 111, 202, 286, 367, 440, 586, 670, 749, 829, 927	
Improved Etching of PCBs by J. A. Kennedy ...	33
Lambda Circuits by B. Dance ... ..	936
Measuring with Operational Amplifiers by A. Sharpe ... ..	186
Monolithic Voltage Regulators by B. Dance	
Part 1 Fixed Regulators ... ..	26
Part 2 Variable Regulators ... ..	112
So You Want To Pass The RAE by J. Thornton-Lawrence and K. McCoy	
No. 1 Arithmetic (Kindly Note 454) ... ..	334
No. 2 Ohm's Law and all that ... ..	416
No. 3 Electro-Magnetism ... ..	501
No. 4 AC—Inductance—Transformers ... ..	570
No. 5 Capacitance—Impedance—Resonance (Kindly Note 837)	659
No. 6 Diagrams—Valves—Semiconductors	764
No. 7 Transistors—Transmitters ... ..	816
No. 8 FM—PM—Transmitter Measurements	922
The Forceful Mr. Fleming—a look at a prob- lem posed by readers of our RAE series ...	770
Special Product Report—Chromasonics	
'Chroma-Chime' Kit ... ..	578
'Stray Signals' by "Point Contact" ... ..	676
The 5-metre Story by R. Ham Part 1 ... ..	740
Part 2 ... ..	830
Part 3 ... ..	902

## ON THE AIR

Amateur Bands by E. Dowdeswell 65, 145, 225, 298, 368, 446, 519, 609, 693, 773, 850, 928	
SW Broadcast Bands by D. Bell 69, 149, 229, 302, 370	
SW Broadcast Bands by C. Molloy 450, 520, 610, 694, 774, 853, 929	
MW Broadcast Bands by C. Molloy 66, 146, 226, 301, 369, 449, 522, 610, 694, 774, 854, 930	
VHF Bands by R. Ham 70, 150, 230, 302, 373, 453, 522, 613, 697, 777, 855, 933	
VHF Personalities by R. Ham	
Alan Baker G8LQG ... ..	856
Henry Hatfield ... ..	934

## PRODUCTION LINES

Abrasive Tools—Tension Files ... ..	435
Raspawl and Abrafile ... ..	758
ADE (Security) Maxi-Guard Burglar Alarm ...	514
Alcon Instruments—Miselco Multimeter ...	55
Multimeter Master 20 ... ..	515
Ambit International—AM Tuner Module 7122 ...	434
BASF—Record and Cassette Care Kits ... ..	601
BFI Electronics—IC Sockets ... ..	212
Bi-Pak Semiconductors—10W Amplifier Module	212
Boss Industrial Mouldings—Instrument Cases	350
ABS Boxes ... ..	837
Bywood Electronics—'Scrumpli' Microproces- sor Kit ... ..	515
Clock Module LT601 ... ..	837
Cannon—Tidy Tray ... ..	285
Chekits—Audio Amplifier Module Kits ... ..	133
Concept Electronics—IC Adhesive Labels ...	514
Continental Specialists—Protoboard PB6 ...	435
Distronic—Crystal Oscillators ... ..	54
Doram Electronics—New Kits ... ..	211
Eagle International—Catalogue ... ..	285
Eraser International—E105 Contact Cleaner ...	837
Gen. Instruments Microelectronics—IC AY- 1-1320 ... ..	210
Gould Advance—Data Book of Instruments ...	435
Greenwood Electronics—Oryx 9 Soldering Iron	350
Vice—Oryx 1B Iron ... ..	600
GSPK—Torch 'Search Lite' ... ..	601
Home Radio—Engineer's Resistor Pack ... ..	435
H. R. Holmes—'Versa-Vice' ... ..	132
Industrial Science—Elecolit 340 Conducting Paint ... ..	434
ITT Instrument Service—Fluke 8020A Multimeter	349
Jermyn—3-Terminal Voltage Regulator ... ..	132
Lascar Electronics—Waveform Generator Module ... ..	284
3½-Digit Panel Meter ... ..	601
Transformers ... ..	759
Linstead Electronic Instruments—Signal Generator ... ..	55
Maplin Electronics—Catalogue ... ..	54
Mogul Electronics—Op. Amplifier TL080-4 ...	212
Op. Amplifier CA3160 ... ..	285
National Semiconductors—Plug-in Resistor Networks ... ..	350
50W Amplifier- Optocouplers ... ..	600
PB Electronics—Blob Board ... ..	133
Platignum—Tidy-Tubs ... ..	350

Philips Electrical—Clock Radio AS460 ...	211
Language Trainer AAC4000	284
Plessey—IC's SL664 SL665 ... ..	211
Plustronics—Music Centre CTA200 ... ..	133
Aiko Stereo Cassette Recorder	
ATP711 ... ..	349
Precision Inst. Labs—Signal Injector ... ..	132
Rastra Electronics—Logic Test Probe ... ..	54
Waveform Generator IC	
ICL8038 ... ..	54
Audio Power Modules	
SI1010/20/50 ... ..	212
Rawplug—25W Soldering Iron ... ..	434
Rhopoint—Klip-Blok Patchboards ... ..	909
RTVC—Disco Amplifiers ... ..	55
SGS-ATES—Voltage Regulator L200 ... ..	54
Sinclair Radionics—Digital Clock Microquartz	514
Digital Multimeter PDM35	758
SST Distributors—Philips Electronic Kits ... ..	600
Tangent Electronics—Universal (Mains) Control Module ... ..	515
Tempus—Casio Digital Clocks/Calculators ... ..	909
Tye Security—Lightsticks ... ..	210
Vessco Vision—Nordemende 'Globetrotter' 800	759
Verospeed Service—Etching Kit-Audio Warning Device ... ..	284
Walmore Electronics—IC Test Clip ... ..	349
Miniature Crystals ... ..	909
Watford Electronics—Stereo Cassette Deck TCD68 ... ..	758

## SHOW REPORTS

High Fidelity '77 by R. Schofield ... ..	219
RSGB Convention '77 by R. Ham ... ..	306
The Paris Show by D. Gibson ... ..	198

## LEADERS

A Logical Step? ... ..	650
A Time Of Change ... ..	730
Band-Switch ... ..	890
Calling All Constructors ... ..	564
Comment Impossible! ... ..	102
I Spy! ... ..	406
Morse Code—The PW Way ... ..	258
Our Face-lift ... ..	332
Perseverance ... ..	484
Something For Nothing ... ..	180
You Lucky People! ... ..	20

## BOOK REVIEWS/NEW BOOKS

Practical Introduction to Digital ICs—D. W. Easterling ... ..	593
Electronics Fault Diagnosis—I. R. Sinclair ... ..	593
How to Build Advanced SW Receivers—R. A. Penfold ... ..	759
Modern Electronics Made Simple—G. H. Olsen ... ..	773
The Radio, TV and Audio Technical Reference Book—S. W. Amos ... ..	432

## MISCELLANEOUS

A Mere 20 Years (since Sputnik 1) by R. Ham	594
Binders for PW ... ..	20, 848
Cover Price Increase—Note ... ..	484
CQ-CQ-CQ readers ads. ... ..	222
Early Wireless Collection by R. Ham ... ..	333
Letters to the Editor ... ..	56, 200
Lionel Howes G3AYA—Note ... ..	258
News—News—News 20, 103, 180, 258, 333, 407, 485, 565, 651, 731, 812, 891	
Obituary—Frank Hennig G3GSW by R. Ham	433
Potential Bread—writing for PW ... ..	690
PW Back Numbers ... ..	181
Readers PCB Service 25, 131, 190, 287, 362, 415, 511, 593, 658, 739, 825, 904,	
Reporting BBC's 500th World Radio Club by R. Ham ... ..	107
RNARS Morse Proficiency Transmissions ... ..	222
'Special Offer' a la 1933! ... ..	494

## SUPPLEMENTS ETC

Component Source Directory ... ..	November 1977
Guide To Aerials ... ..	March 1978
Index to Volume 52, May 1976 to April 1977	May 1977
Information Card—Semiconductor Characteristics ... ..	May 1977

## Special Offer

Soldering Iron Kits	569
---------------------	-----

## Gift

Pocket Magnifier	October 1977
------------------	--------------

## LIST OF AUTHORS

Allenden M.	Lamb S.
Bailey T.	Langton A.
Bell D.	Longden R. H.
Bond P.	Macaulay J. P.
Bond W. G3XGP	McCoy K. GW8CMY
Canning F. G.	Molloy C. G8BUS
Cooper A.	Mooney W. G3VZU
Coutts D. S.	Opel W.
Dance M. MSc	Parr E. A.
Davies S.	Parsons S. C.
Dowdeswell E. G4AR	Penfold R. A.
Edwards D. J.	Pleass W. BA BSc AMIEE
Gibson D. G3JDG	Rayer F. G. G3OGR
Grayson C. BSc	Schofield R.
Ham R. FRAS BRS15744	Sharpe A.
Harvey B.	Sjogren G. O. H.
Helsby N. C. MIEE	Soar R. N.
Hickman I.	Thornton-Lawrence J.
Hughes M. J. MA C.Eng. T.Eng (CEI) FSERT	
	MIERE GW3JGA
Jones D.	Toms C. BSc
Jones D. L.	Tooley M. BA G8CKT
Judd F. C. G2BCX	Whitaker R.
King D. H. E. G3TQN	Willcox A.


# BATTLE GAME



a piece of tinfoil (cocoa tin) as shown in Fig. 5 to form a box for the modulator screening, fit the sides and bottom by soldering to four Veropins as shown in the drawing but leave the top plate off until the

unit is working and displaying a picture on the television screen.

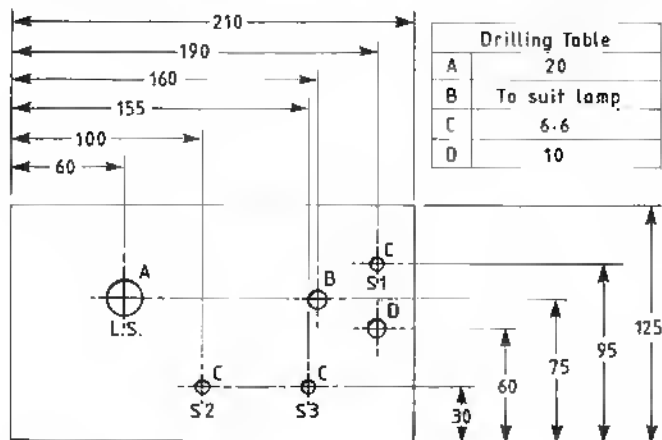
Carefully check the p.c.b. for correct assembly and freedom from inadvertent shorts such as solder



Dimensions in mm.

AD094


▲ Fig. 1: Front panel drilling diagram

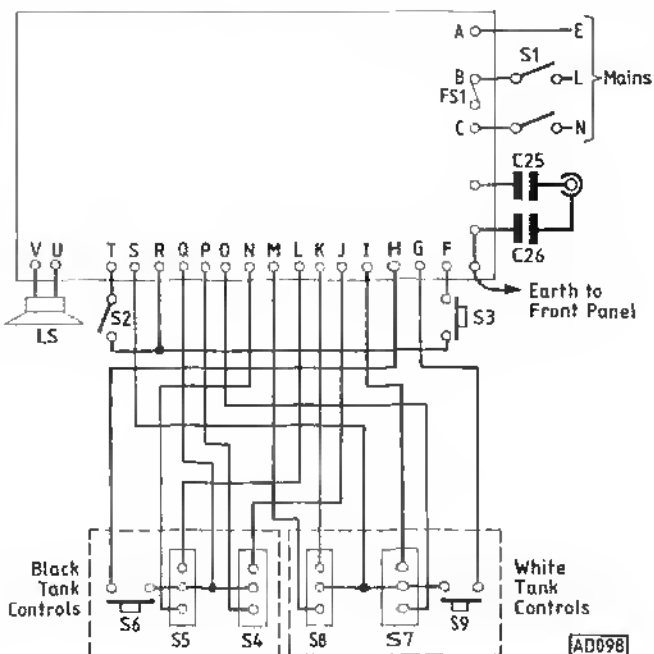

AD098

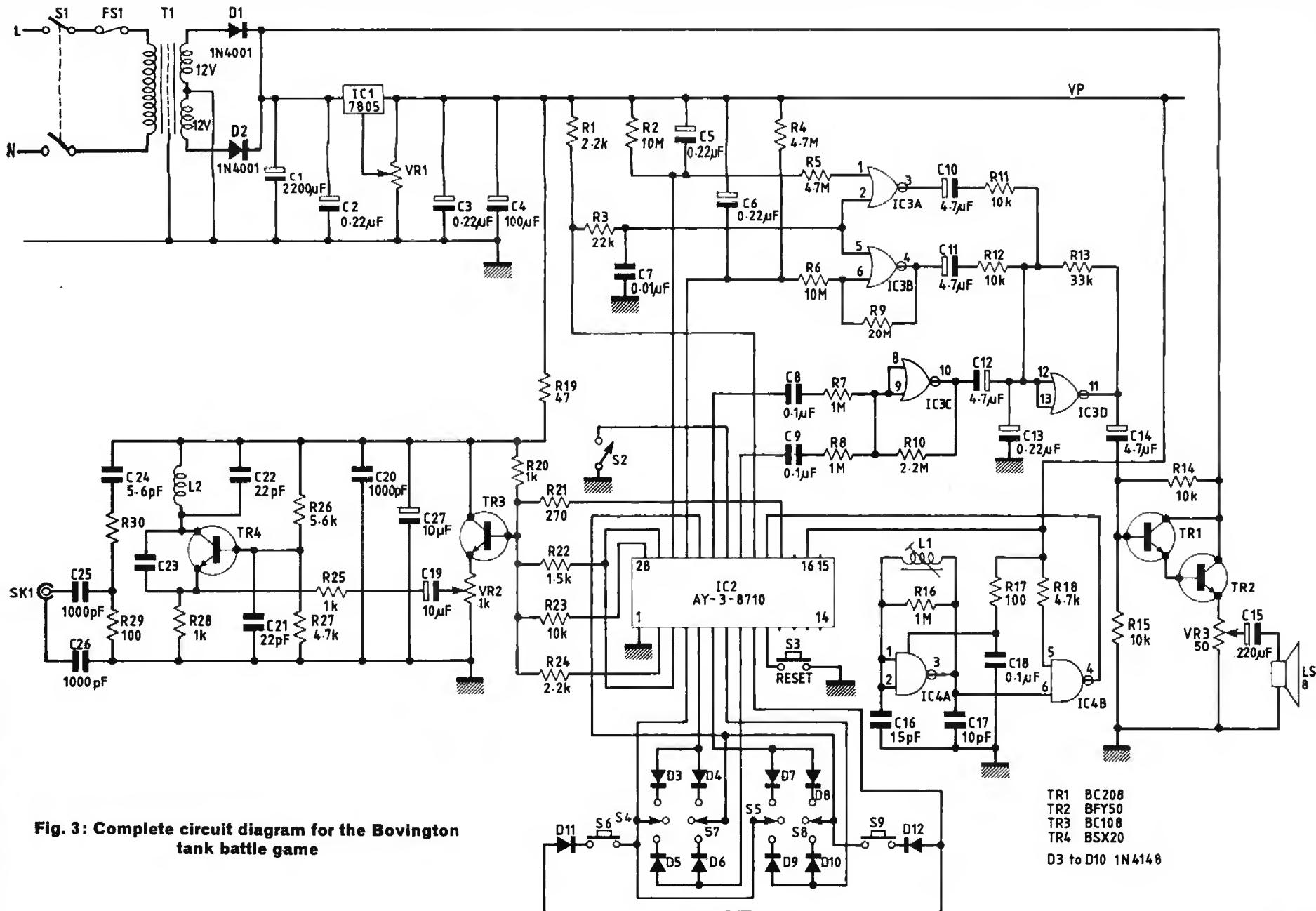▶ Fig. 2: Main printed circuit board connections






- TR1 BC208
- TR2 BFY50
- TR3 BC108
- TR4 BSX20
- D3 to D10 1N4148


**Fig. 3: Complete circuit diagram for the Bovington tank battle game**

Tank Cct. Diagram Fig.1

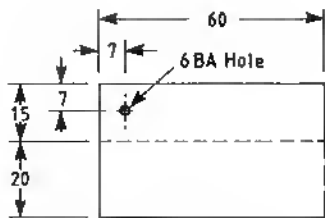


Dimensions in mm.  
Material: 16 SWG Aluminium

▲ Fig. 4: Heat sink for IC1

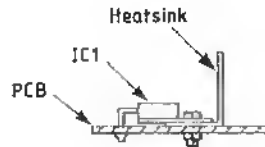


AD096


Fig. 5: Details of modulator screen ►

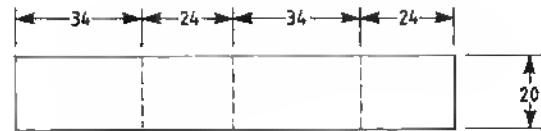

1 off

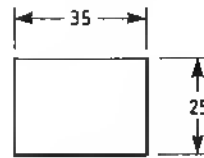

2 off

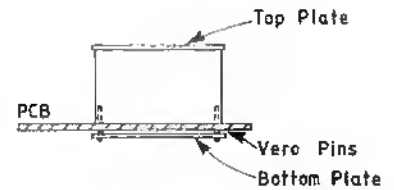

Dimensions in mm.  
Material: Tinplate.

AD097

bridges, set VR1 fully clockwise and VR2 to midrange and fit the unit in the case with 6BA screws through the fixing holes. Wire the unit up as shown in Fig. 2. Fix two 6 pin DIN sockets in the front of case connected to points G-Q & S on the p.c.b. to feed the hand controllers. These sockets may be omitted and the multicore wires fed through suitable holes fitted

with grommets. The hand controllers can be assembled in any convenient small plastic boxes.

Switch the power on, monitor the voltage VP across C4 and adjust VR1 to obtain 6.5 volts. If you have a scope or counter fit IC4, power up and adjust L1 for 4MHz. If not, set the top of the core of L1 approximately 6mm into the former. Fit the remaining inte-

## ★ components

### Resistors

All  $\frac{1}{4}$ W 5%

47 $\Omega$	1	R19
100 $\Omega$	3	R17, 29, 30
270 $\Omega$	1	R21
1k $\Omega$	3	R20, 25, 28
1.5k $\Omega$	1	R22
2.2k $\Omega$	2	R1, 24
4.7k $\Omega$	2	R18, 27
5.6k $\Omega$	1	R26
10k $\Omega$	5	R11, 12, 14, 15, 23
22k $\Omega$	1	R3
33k $\Omega$	1	R13
1M $\Omega$	3	R7, 8, 16
2.2M $\Omega$	1	R10
4.7M $\Omega$	2	R4, 5
10M $\Omega$	4	R2, 6, 9a, 9b

### Capacitors

Plate Ceramic

3-3pF	1	C23
5-6pF	1	C24
10pF	1	C17
15pF	1	C16
22pF	2	C21, 22

Disc Ceramic

1000pF	3	C20, 25, 26
0.01 $\mu$ F	1	C7
0.1 $\mu$ F	3	C8, 9, 18

Polyester

0.22 $\mu$ F	2	C2, 3
--------------	---	-------

Tantalum

0.22 $\mu$ F 10V	3	C5, 6, 13
4.7 $\mu$ F 10V	4	C10, 11, 12, 14
10 $\mu$ F 10V	2	C19, 27
100 $\mu$ F 10V	1	C4

Electrolytic

220 $\mu$ F 25V	1	C15
2200 $\mu$ F 25V	1	C1

### Potentiometers

1k $\Omega$ Horizontal preset	1	VR2
4.7k $\Omega$ Horizontal preset	1	VR1
50 $\Omega$ Wirewound.	1	VR3

### Semiconductors

Diodes

1N4001	2	D1, 2
--------	---	-------

Integrated circuits

4001A	1	IC3
4011A	1	IC4
7805 regulator	1	IC1
AY-3-8710	1	IC2

Transistors


BC108	1	TR3
BC208	1	TR1
BFY50	1	TR2
BSX20	1	TR4

### Switches

Paddle s.p.d.t. (Arrow CPM3 Black)	2	S4, 5 (Biased to centre off)
Paddle s.p.d.t. (Arrow CPM3 White)	2	S7, 8 (Biased to centre off)
Push-button s.p.	3	S3, 6, 9
Toggle s.p.d.t.	1	S2
Toggle d.p.s.t. (Mains)	1	S1

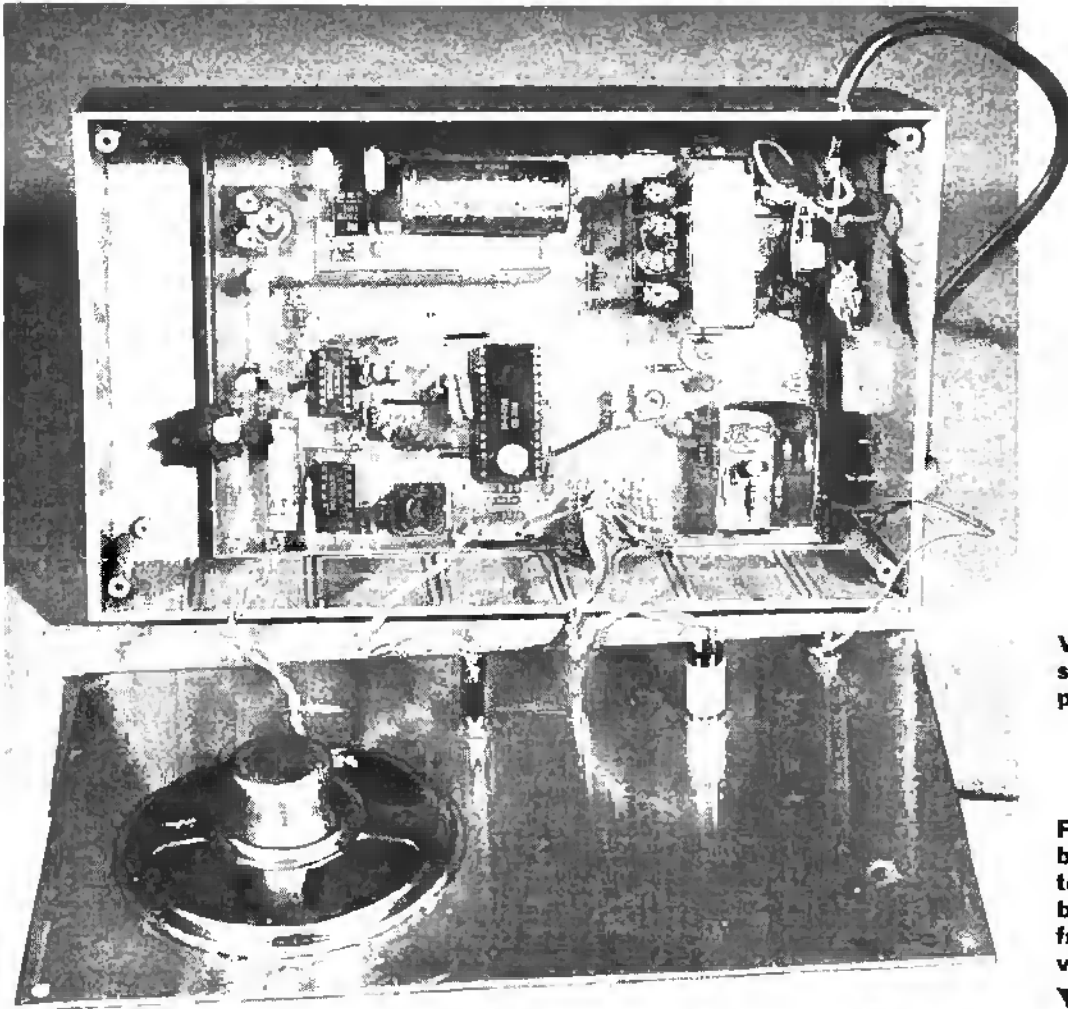
### Miscellaneous

Transformer 12V, 12V 250mA MT12 (Marshall's)
Loudspeaker 2 $\frac{1}{2}$ inch 8 $\Omega$
Case RS Type 509-608
Hand control boxes (2) RS Type 509-298
350mA fuse and holder
Miniature multicore cable (9-way) 4metres
Miniature mains cable
Indicator lamp 12V
Knob for volume control
6-way DIN plug and socket (2) Optional for hand control leads.
TO5 heat sink
Co-axial TV socket surface mounting type.
28-way d.i.l. socket (1)
14-way d.i.l. socket (2)



View of the internal construction of the main p.c.b. and case

Fig. 6: Printed circuit board copper track pattern. Ready drilled boards are available from Readers PCB Services (see page 68)

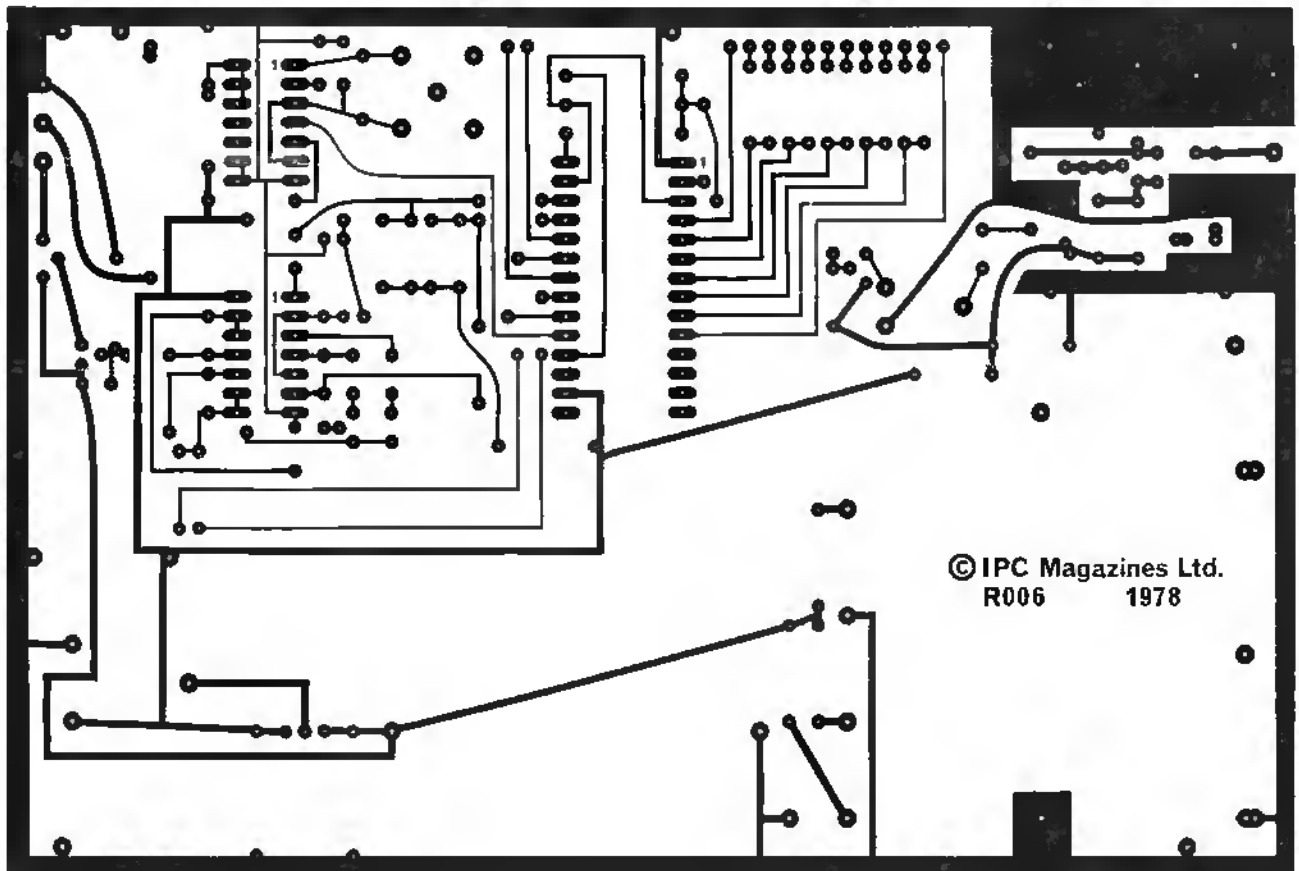

© IPC Magazines Ltd.  
R006 1978



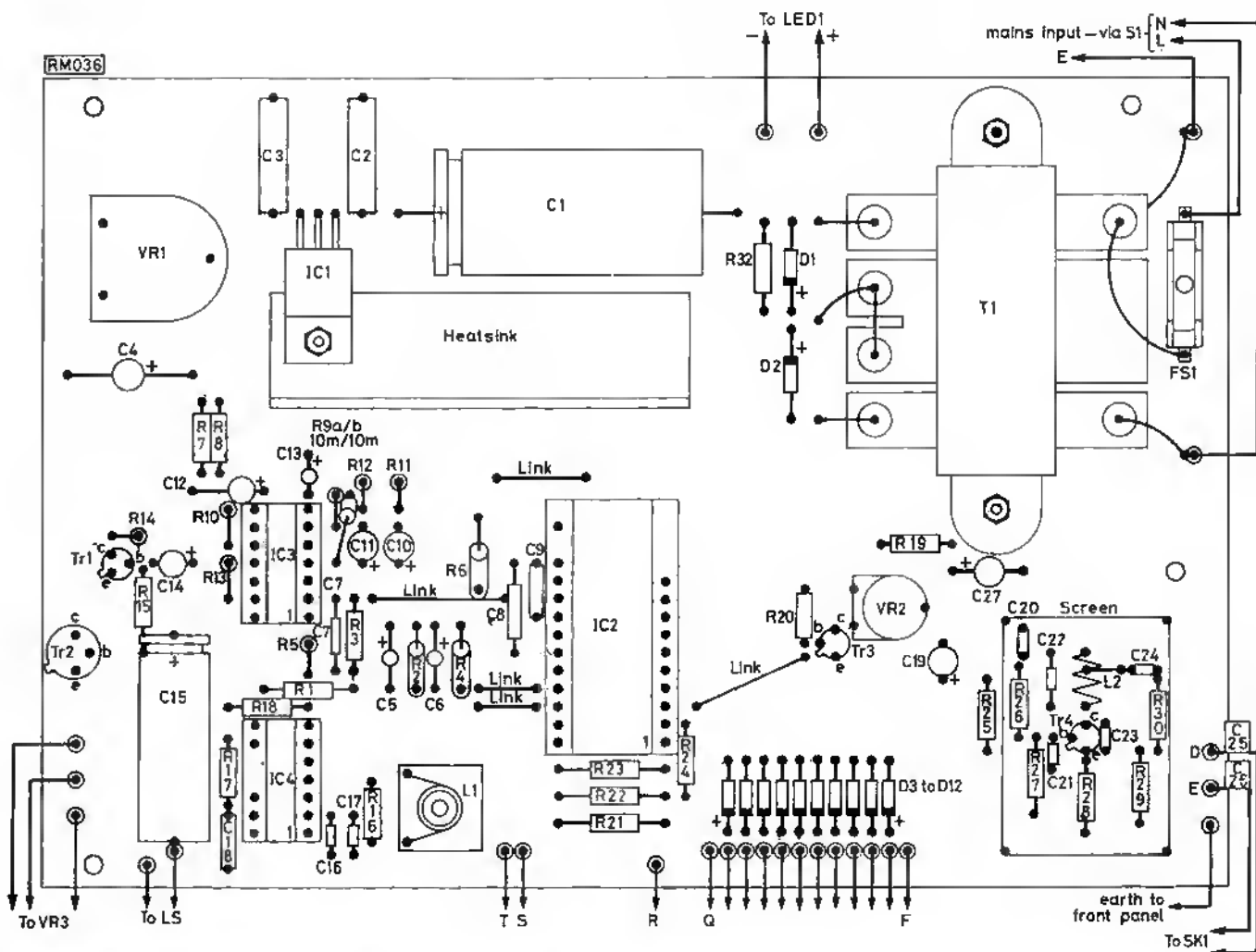


Fig. 7: Main printed circuit board component placement drawing

grated circuits, connect to the aerial input of the television and switch on. Push the reset button, release it and tune the television until a signal from the games unit is found. Several signals may be found, if so choose the best one. L1 may need to be slightly adjusted. When a good picture has been obtained adjust VR2 for the optimum picture, and fit the top cover to the modulator. Check that all the switches function as required and fit the front panel.

## Fault Finding

If the unit fails to function check all your construction carefully, then:—

1. Check that the voltage across C4 is 6.5 volts.
2. Vary VP over the range 6 to 7 volts by means of VR1, if this does not help reset it to 6.5 volts.

3. Check with a scope that pin 19 of IC2 has a 4MHz clock input and pin 16 is at 6.5 volts.
4. Check that composite sync is appearing at IC2 pin 18, pushing and releasing the reset.
5. Check for composite video at TR3 base and again at VR2 wiper. If it is appearing at VR2 wiper try again to tune the television to the game signal. If you still cannot get a picture, substitute a new transistor for TR4.
6. If the tanks only go forward under control of the switches you will probably find that one pair of wires to the switches are crossed.

## Four Players

Extra excitement and skill can be introduced into the game by splitting the tank controls between four players, two to each tank. The steering controls are operated by the "drivers" while the tank commanders have control of the firing buttons.

The modifications needed to make this a four-player game are very simple, especially if DIN plugs and sockets are used for connecting the control boxes to the main unit. The commander's firing control can be fitted into a simple box wired into the DIN plug. If a duplicate set of controls is not desirable then a permanently fitted "commander's" control can be wired into the game unit with a switch arranged to select either the firing button on the "driver's" box or the button on the "commander's" box.

### IC2 Pin Functions

1	Ground
2, 3, 18, 27, 28	Video outputs
4, 5, 6, 7, 8, 9, 24	Control inputs
10	Reset
16	VP (+6.5V)
19	4MHz clock input
20, 21, 23, 25, 26	Sound output
22	Tank trap select
11, 12, 13, 14, 15, 17	Do not connect

# PRODUCTION LINES

alan martin

## Pssst wanna watch?

When l.e.d. and l.c.d. watches first came onto the British market, they cost between £50 and £100 and any available in the £20 range were either advertised on 'Police Five' or came off the back of that proverbial lorry.

We are informed by W.K.F. Electronics, that they have a selection of watches available at very reasonable prices.

First, an l.e.d. watch (left in photograph) that features a rather novel touch sensitive operating pad to display hours and minutes, seconds, day and date, also day and month. Price £10.75 plus VAT.

Second, the standard l.c.d. watch (centre in photograph), which displays hours and minutes continuously,

press the button for day and month, press again for seconds. The watch also has a separate back-light function. Price £10.50 plus VAT.

Finally the chronograph l.c.d. watch (right in photograph) whilst possessing the standard watch functions of hours, minutes, seconds, day, date and month, also features a lap and continuous stop watch facility, with timing to 100th of a second. Price £18.95 plus VAT.

All the watches are supplied with an adjustable stainless steel bracelet and the two l.c.d. watches are powered by batteries costing only 42p (retail) with an estimated life of twelve months.

*W.K.F. Electronics, Fleet House, Welbeck Street, Whitwell, Workshop, Notts. Tel: 0909 720-695.*



## Vero interesting

Vero Electronics Ltd. introduce a new range of cases with their 'Series II Boxes AB 010'.

These boxes are moulded in light grey high-impact polystyrene in two parts. The anodised aluminium front panel supplied with the box is retained between the two halves, avoiding the need for fixing screws. Slots and bosses are moulded into the interior of the box, so that a choice of mounting positions, either horizontal or vertical, is available for p.c.b.'s

or component decks.

Many of the boxes have a battery compartment which is accessible without dismantling the box.

The standard range consists of fifteen boxes varying from 110mm x 68mm x 33mm to 190mm x 138mm x 91mm, and other sizes are available to special order at a minimum quantity of 100.

Further details from: *Vero Electronics Ltd., Industrial Estate, Chandler's Ford, Eastleigh, Hampshire S05 3ZR. Tel: 042 15 69911.*



## No lick TAC-1

The Polycal TAC-1 is a pocket size, liquid crystal display, travel alarm clock. Measuring 65mm x 32mm x 11.5mm, it weighs only 45g with batteries. The 3V d.c. power input is provided by two silver oxide or manganese alkaline batteries (type GS-14, A-76 or equivalent). Power consumption is 3mW max. (with the alarm sounding). Accuracy is claimed to be ±30 seconds per month at 20°C (68°F). With a separate back-light, the multi-digit liquid crystal displays hours, minutes, clock-working sign and am/pm indication.


Priced at £22.50, which includes VAT and p & p, the TAC-1 is available from: *Tempus, Dept. P.W., 19/21 Fitzroy Street, Cambridge CB1 1EH. Tel: 0223 312866.*

## Rechargeable iron

A new version of the Engel B.50 Rechargeable Soldering Iron is now available from Kelgray Products Ltd. and is complete with charger unit. The iron now incorporates a built-in spotlight to illuminate the working area and uses long-life rechargeable nickel-cadmium batteries. Providing up to 100 intermittent operations (300 continuous use) without recharging, which can be achieved in about 8 hours (overcharging is impossible). A safety switch is fitted to the trigger-switch to prevent accidental operation. The iron heats up to an operating temperature of approx 350°C in about 7 seconds; a variety of bits are available.

Designed for recharging from a.c. mains, the B50 comes complete with cleaning pad, protective cover, 2 lighting fittings and screwdriver. A particular advantage of this iron is that no stray eddy currents which might damage a sensitive i.c. are generated when the iron is being used.

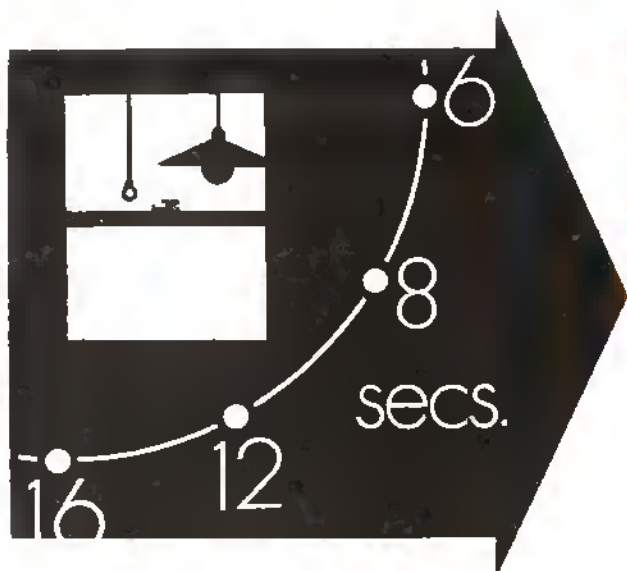Priced at £16.50 which includes p&p and VAT, the B50 is obtainable from: *Kelgray Products Ltd., Kelgray House, Sandy Lane, Crawley Down, West Sussex RH10 4HS. Tel: 0342 715066.*



# SIMPLE DARKROOM TIMER

A.P. DONLEAVY

This article describes a simple timer which switches an enlarger on and off for predetermined periods. The instrument can handle exposures up to 32 seconds although this can be easily increased as will be described. The accuracy is better than 10% which is adequate for black and white printing.

The instrument uses a switch which enables the exposure time to be set by feel rather than by having to peer at some dimly lit switch setting.

## Circuit

The circuit is shown in Fig. 2. The 555 i.c. is connected as a monostable multivibrator and on application of a negative pulse to pin 2 a positive pulse emerges at pin 3. The duration of this pulse is determined by the R-C values of R1 to R8 and C1, and also by the voltage on pin 5. This pulse is applied to the gate of the s.c.r. which causes it to conduct for the duration of the pulse. The s.c.r. is essentially being used as a mains switch. If the mains were applied directly to the s.c.r. it would only conduct on the positive-going part of the cycle and the light would only have about one third of its normal intensity. A bridge rectifier is used to rectify the mains supply and thus overcomes this problem.

SW2 applies the pulse to start the timing. Pin 2 is tied to Vcc via R9 to prevent unwanted triggering. Application of a negative pulse via SW1 will prematurely terminate any timing interval.

The length of the timing pulse is proportional to the value of the resistance at pins 6 and 7. The values R1 to R8 are chosen to give sequence times of 2, 4, 6, 8, 12, 16, 24 and 32 seconds, within 10% but the values can be altered to suit the needs of the individual constructor. Every 27kΩ added to the resistor chain will give an extra two seconds time. Hence if a 48 second timing period is required, an extra 8 x 27kΩ or 216kΩ resistor would be needed to be added in series with R1 to R8. In practice a 220kΩ resistor would suffice. The final calibration is made by adjusting VR1.

The unit should consume no more than 8mA, so the power supply uses a miniature mains transformer, with a full wave rectifying circuit.



The timer is built into a small instrument case with all the controls on the front panel

## Components

Any 555 timer i.c. can be used, e.g. LM555, SN72555 NE555, and any s.c.r. and bridge rectifier that can handle at least 400V at 500mA can be used for SCR1 and D1.



SW3 is made up from a Doram Mini-Maka switch. The minimum requirement is one pole eight way. The prototype had an open position at one end of the scale, which gives a timing pulse of almost indefinite length. This is used for leaving the enlarger permanently switched on. The mains transformer need only be capable of supplying between 6V and 15V at 50mA at the secondary.
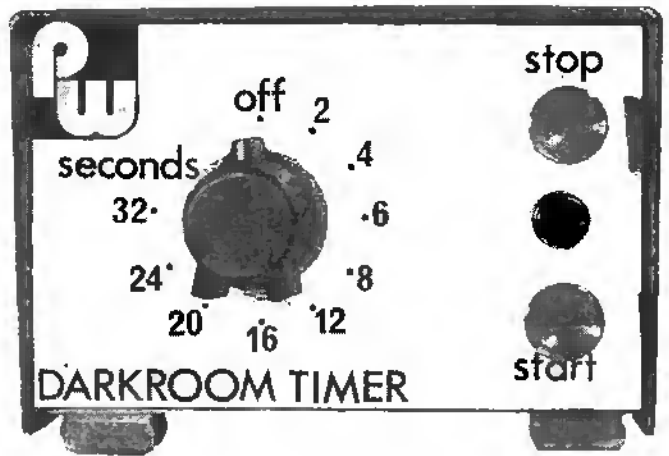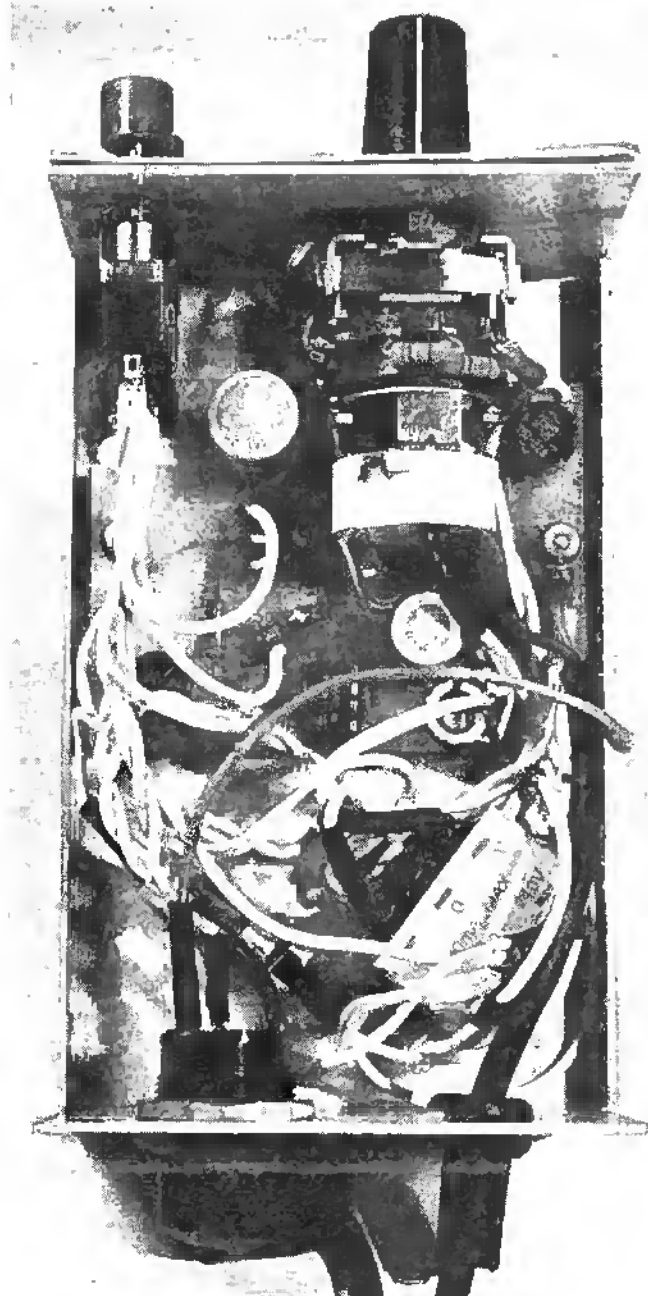
## Construction

The unit is built on a printed circuit board 105mm x 57mm. The layout of the copper tracks is shown in Fig. 4 and the component layout in Fig. 3. The unit is housed in a metal instrument case and to complete the front panel a PW overlay is available.

The p.c.b. is supported by two short 4BA screws with a nut between the board and case bottom. Remember that some of the copper tracks carry live






▲ Front panel layout of the darkroom timer. A transparent overlay is available from the PW Editorial Offices which will enable readers to achieve a professional finish to their equipment. The overlay is cut out and placed over the front panel, being held in place by the switch nuts and washers. A coloured background can be used behind the overlay if desired

▲ Inside view of the complete unit showing the positioning of the transformer, p.c.b. and switch

Fig. 1: Pin connections for the 555 timer i.c. and the C106D thyristor

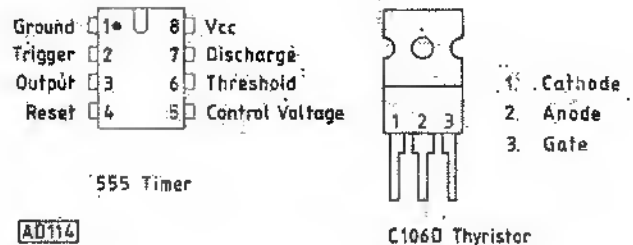

## ★ components

### Resistors

All  $\frac{1}{2}W$  2%

R1	27k $\Omega$	R6	56k $\Omega$
R2	27k $\Omega$	R7	120k $\Omega$
R3	27k $\Omega$	R8	100k $\Omega$
R4	27k $\Omega$	R9	4.7k $\Omega$
R5	56k $\Omega$	R10	68k $\Omega$

### Potentiometers

VR1 10k $\Omega$  min. horizontal skeleton

### Capacitors

C1	47pF 16V
C2	100pF 16V

### Semiconductors

IC1	555 timer
SCR1	TIC 106D or similar 400V working
D1, D2	1A bridge rectifier 400V working

### Miscellaneous

Transformer	3-0-3V 1.2VA Sub-miniature
SW3	1 pole 12 way miniature wafer switch
SW4	Mains switch to fit SW3 mechanism
SW1 and 2	Miniature push-button push to make. Lamp output plug and socket (RS components 488-567 and 488-593). Fuse and holder 2A
Printed circuit board	Reader's PCB Services
Case	RS components. 509-715
Knob	15mm Sifam W15 collet fixing with nut cover and cap
PW Front Panel Overlay	


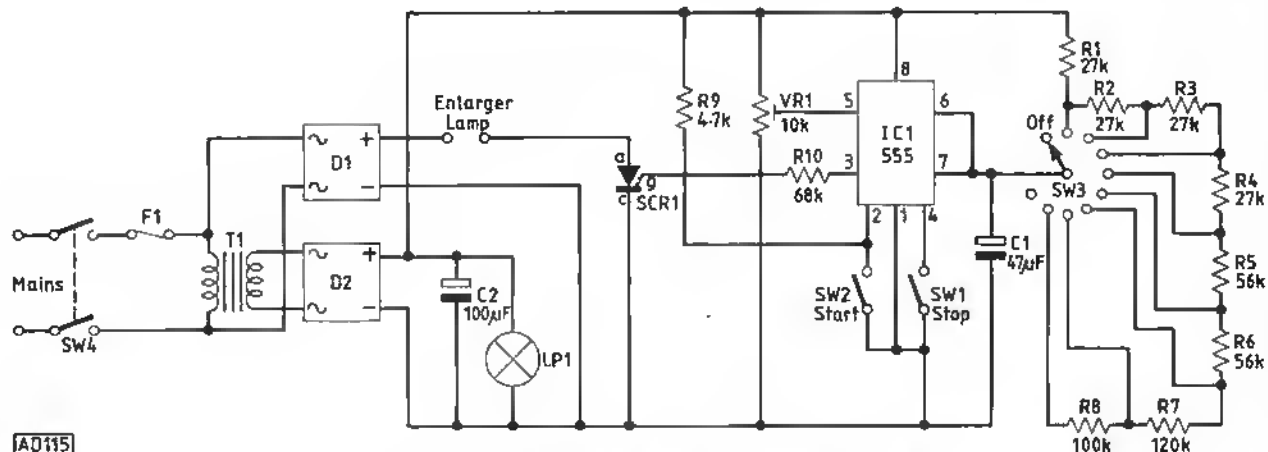
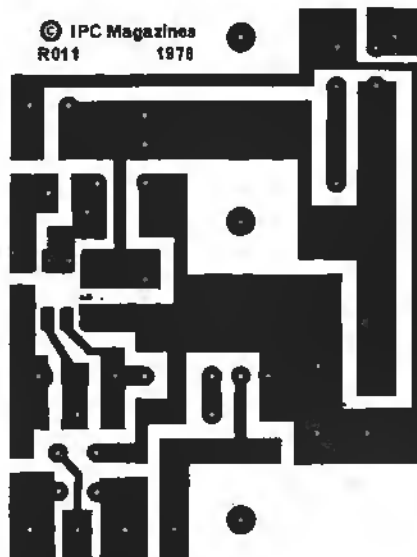


Fig. 2: Circuit diagram of the darkroom timer

**Fig. 3: Component layout diagram.** Care must be taken to avoid solder bridges or other forms of short circuits between tracks or components as mains voltages appear at several points on the board. A piece of self adhesive plastic sheet should be placed on the metal base of the case underneath the p.c.b. to avoid any possibility of component leads shorting to chassis

**Fig. 4: Copper track pattern for the darkroom timer p.c.b.** Ready drilled boards are available from Reader's PCB Service. (see page 68)

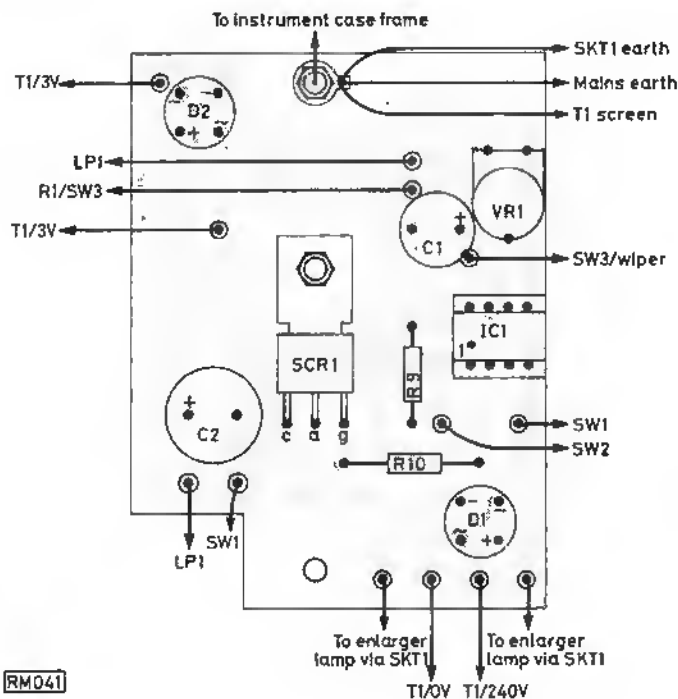

mains voltages and that these should be kept well clear of the supporting bolts.

A shielded miniature mains plug and socket are used to connect the enlarger lamp to the unit and this is fitted into the back of the case. If desired the fuse can be a panel mounting type and also fitted into the back. A mains switch is fitted to the end of

the wafer switch. Resistors R1 to R8 are soldered directly on SW3.

Switch to the maximum time period of 32 seconds, then depress SW2 and measure the period. Adjust VR1 until a 32 second period is obtained and your darkroom is calibrated. ●

# So you want to pass the R.A.E. (Radio Amateurs' Examination)?

No. 10

John Thornton Lawrence GW3JGA & Ken McCoy GW8CMY


Here is the final section of this series and this month we are to consider aerials, feeders, matching and also interference. At the conclusion, we give some hints on actually sitting the examination.

## AERIALS, TRANSMISSION LINES AND MATCHING

The subject of aerials is a complex one and in the space available we will be confining our attention to basic essentials. For further information please refer to the appropriate section in the RSGB *Radio Communication Handbook* or the *Radio Amateurs' Examination Manual*.

The fundamental aerial is a length of wire which is half a wavelength long; this is known as the **half-wave dipole** and is shown in Fig. 85. The aerial is said to be resonant at a specific frequency which is determined by its length, and the distribution of voltage and current along the wire is known as **standing waves**.

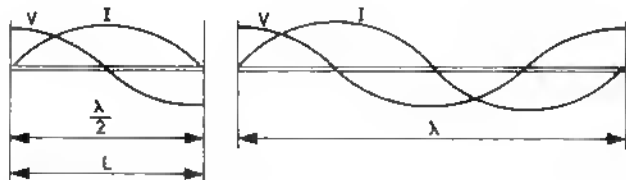The ratio of voltage to current varies along the conductor, but at the centre of a resonant half-wave dipole it gives a convenient impedance of approximately 70 ohms. If the aerial is broken here, the r.f. power can be fed into the dipole at its resonant point.



Half-wavelength

Full-wavelength


Feed Point Impedance  
Approx. 70 Ohms

Feed Point Impedance  
Approx. 5000 Ohms



Half-wave Dipole

Radiation Pattern  
Plan View

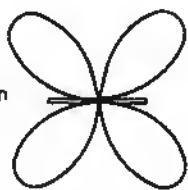

Full-wave Dipole

AD101

Fig. 85: Dipole characteristics

The full-wave resonant aerial has, as might be expected, a standing-wave pattern similar to two half-wave aerials joined end-to-end. The centre impedance in this instance is very high; inconveniently so in fact and special matching arrangements are called for, as we shall see later.

The radiation pattern of a half-wave dipole is in the form of a "doughnut" shape which in section becomes the characteristic figure "8" shape, as shown in Fig. 85.

With a full-wave resonant aerial, the radiation patterns of the two half-wave sections affect one another, producing the four-lobe shape shown.

## Dipole Length

The length of a half-wavelength in free space is given by:

$$L = \frac{300 \times 0.5}{\text{Frequency (MHz)}} \text{ metres}$$

However in practical application, due to (a) capacitance effects at the ends, (b) the velocity of the radio wave being slower in the wire than in free space and (c) the effect of the wire diameter, it has been found that the actual aerial dimensions are about 5 per cent shorter than the calculated free-space length. (Free-space length  $\times 0.95$ .)

For example, the length of a practical, resonant, half-wave dipole for 3.6MHz would be given by:

$$L = \frac{300 \times 0.5 \times 0.95}{3.6 \text{ MHz}} = \frac{142.5}{3.6} = 39.6 \text{ metres}$$

## The Vertical Aerial (Quarter wave $\lambda/4$ )

When looking at the radiation characteristics of a quarter-wave vertical aerial, it is necessary to take into consideration the reflective properties of the ground. If we consider the ground as a mirror to the radiation from an aerial, it will be seen that the vertical aerial AB, in Fig. 86 has an image BC in the ground mirror (just as in optics).

Thus, radiation leaving the aerial from point D will travel by two paths in the direction E: one direct from D and the other from the ground reflection. (The position F is a mirror-image of the aerial in the ground). The radiation pattern is similar to the half-wave dipole but being in the vertical plane it is omnidirectional in the horizontal or plan view.

Vertical aerials fitted on the roofs of vehicles for v.h.f. and u.h.f. utilise the excellent reflective properties of the metal as ground.

## Directional Aerials

The pattern and direction of the maximum radiation of an aerial can be modified by the addition of extra elements, which may be driven by feeding



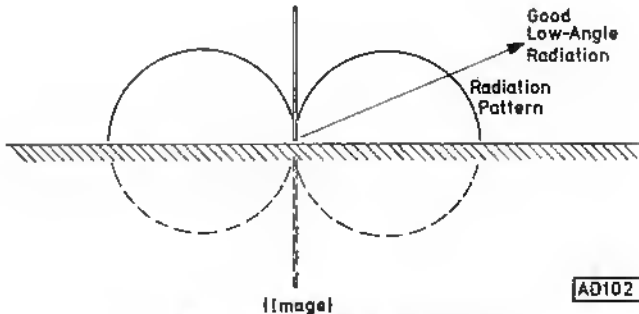
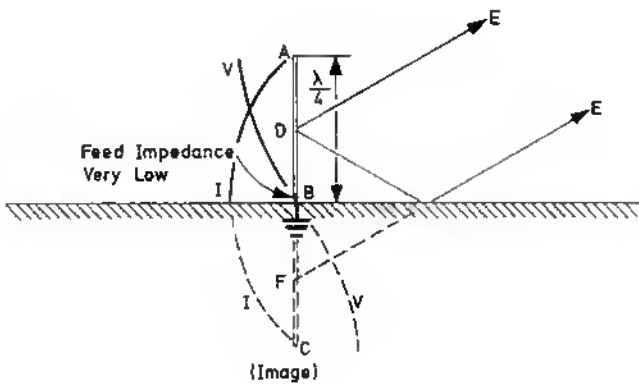


Fig. 86: The  $\frac{1}{4}$ -wave vertical aerial

power to them or parasitic, where no direct electrical connection is made.

The "Yagi" array shown in Fig. 87 has a half-wave dipole with parasitic director and reflector elements. The lengths and spacings are chosen to give increased "gain" in the forward direction and reduced gain in the reverse direction (as compared with a plain dipole).

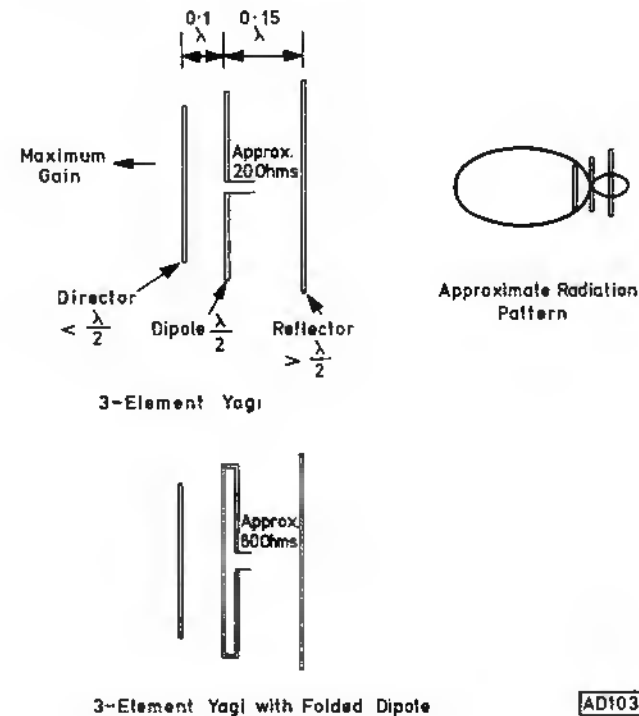


Fig. 87: Simple directional aerial arrays

One of the consequences of adding parasitic elements is that the dipole impedance becomes inconveniently low (about 20 ohms) and to overcome this a folded dipole is often used. This has the effect of transforming the impedance up by a factor of four to give a value of around 80 ohms.

## Transmission Lines and Feeders

The source of r.f. power is quite often not the place of utilisation. For convenience we need to have the transmitter indoors, but the aerial has to be outside, as high and far away from buildings as possible. In some instances it may be possible to bring the aerial directly to the transmitter but in most cases a transmission line or feeder cable is required.

## Impedance Matching

For maximum power transfer from one circuit to another the input impedance of the circuit receiving power must equal the output impedance of the circuit delivering it. The output impedance of a valve-type transmitter final amplifier is in the order of a few thousand ohms and a transistorised version would present about five ohms or less. The aerial impedance required can therefore vary between about twenty ohms and several thousand ohms, depending on the type and the point of connection.

The impedance of the transmission line or coaxial feed cable connecting the transmitter to the aerial is defined by its physical construction. Usual values for coaxial cables are 50 or 75 ohms and for twin transmission lines, 70 to 600 ohms, depending on the method of manufacture.

Some form of matching arrangement is therefore required between the various sections of the system which convey r.f. power from transmitter output stage to aerial. A typical example is shown in Fig. 88.

- There are three basic types of lines or feeders.
- Single wire feeder (which carries a true travelling wave.)
  - Coaxial feeder.
  - Parallel wire line.

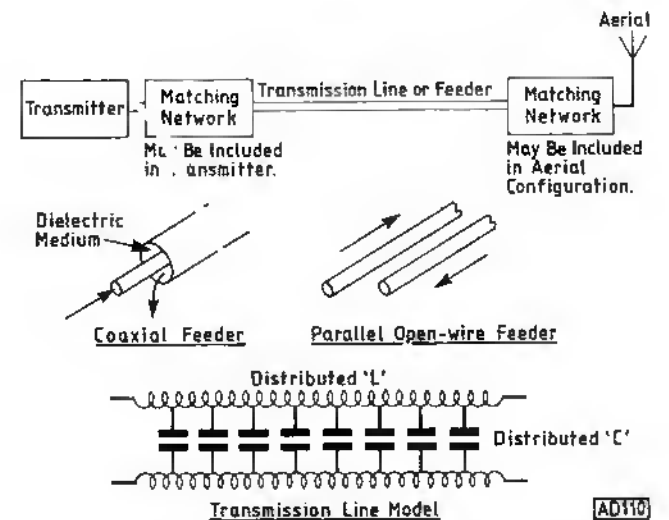


Fig. 88: Transmission lines

Single feeders (a) are not commonly used because they tend to act as radiators themselves. In the coaxial type (b) the r.f. field is restricted to the inside of the structure, whilst in parallel wires the field is confined to the immediate vicinity of the conductors.

### Characteristic Impedance ( $Z_0$ )

A transmission line or feeder may be considered as consisting of a distributed inductance with associated distributed capacitance, as shown in Fig. 88. It is the relative value of inductance and capacitance which gives the transmission line a property known as characteristic impedance ( $Z_0$ ). When a transmission line is connected to, or terminated with, a pure resistance which is equal to the characteristic impedance, a current travelling along it does not see any change in conditions when it meets the load. In other words, a short transmission line terminated in a purely resistive load equal to the characteristic impedance of the line, acts as though it were of infinite length. Such a line is said to be matched, and here power travels outwards from the r.f. source until it reaches the load, where it is completely absorbed. Let us look at what happens if the transmission line is terminated by its characteristic impedance and then by an impedance other than  $Z_0$ . This is shown diagrammatically in Fig. 89.

Where the line is terminated in its characteristic impedance ( $Z_0$ ) the voltage or current will have the same value at any point along it. (a) If however it is terminated with (b) an open circuit or (c) a short circuit, then standing waves are produced along the feeder as shown. This is because the power is not being absorbed at the end of the line but is being reflected: the reflected wave adds to the incoming wave and produces a standing-wave pattern along the line. These examples are extreme cases, but any mismatch produces a resultant standing-wave pattern.

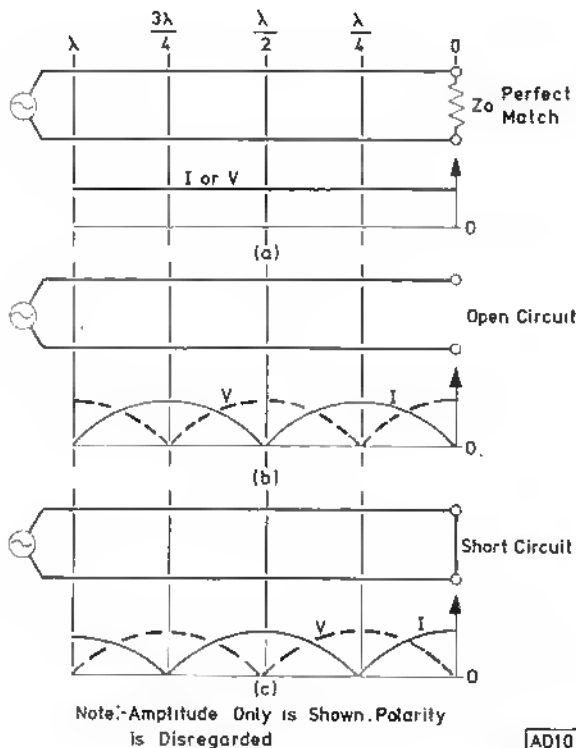


Fig. 89: Transmission line terminations

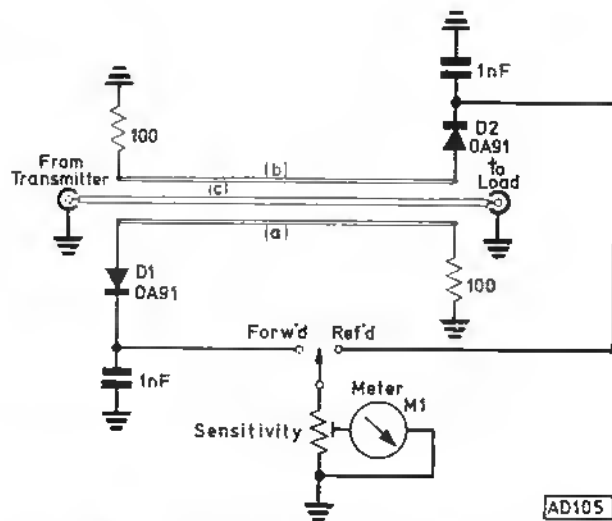


Fig. 90: A simple standing wave ratio meter

The ratio of the maximum value of the standing-wave to the minimum is known as the standing-wave ratio (s.w.r.). Values will vary from unity (matched condition) to infinity (complete mis-termination).

### Standing Wave Ratio Meter

A useful device for looking at the s.w.r. in a coaxial feeder cable is shown in Fig. 90. Loops of wire, (a) and (b), sample forward and reverse power passing through the centre conductor (c). The voltages developed in the coupling loops are rectified by D1 and D2 and the resulting d.c. output deflects the meter M1, thereby giving an indication of the forward and reverse (reflected) power.

The s.w.r. meter is particularly useful when making adjustments to aerial matching and tuning. Constructional details for a v.h.f. unit were carried in the May 1978 issue of PW.

### Matching

Most transmitter and aerial matching circuits are of the resonant type and are tuned to the operating frequency. We have already described the "Pi" matching network for a valve output stage (PW March 1978, p. 821), shown again in Fig. 91(a); an "L" type network for transistorised output stages is shown in Fig. 91(b). This configuration allows for more convenient component values when working at the low output impedances encountered.

In both circuits the impedance transformation is adjusted by the relative capacitances of C1 and C2, whilst maintaining resonance at the operating frequency. It is usual in this instance to arrange for the transmitter network to provide an output impedance which matches the characteristic impedance of a readily available type of coaxial cable, e.g. 50 ohms or 75 ohms.

When the coaxial cable is operated with a low s.w.r., losses within it are also low, so it is very convenient to fit any filters necessary here.

Some aerials, such as the dipole, have a characteristic impedance at the feed point which will match directly the characteristic impedance of the feeder cable and an aerial matching network is therefore unnecessary. However, if a symmetrical or balanced aerial such as the dipole is fed by coaxial cable, a

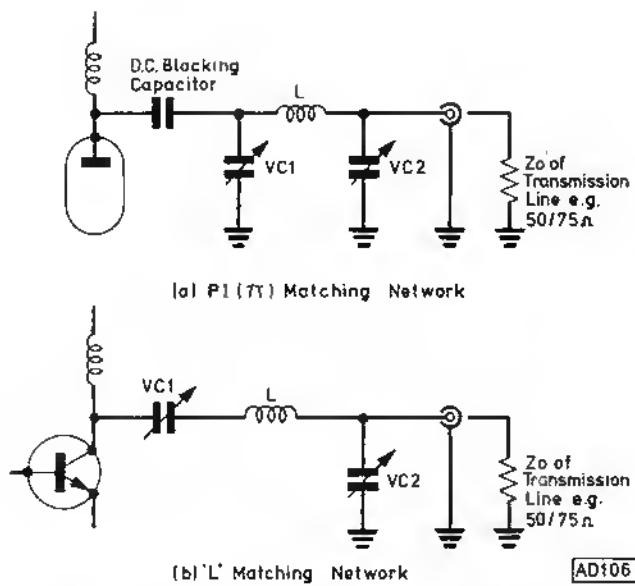


Fig. 91: Transmitter output matching networks

state of imbalance will exist, because one arm of the dipole is connected to the centre conductor whilst the other is connected to the outer shield. The currents flowing in the shield cannot be cancelled by those in the centre conductor which it surrounds.

### Balance to Imbalance Transformer (Balun)

Diagrams of balun transformers are shown in Fig. 92. In (a) a quarter-wavelength coaxial sleeve surrounds the coaxial cable and in (b) a quarter-wavelength of rod, forming a "stub", balances the output to the aerial. For low frequencies, it is more convenient to wind the balun transformer on a ferrite ring. This type is less frequency-conscious and may be used over a wide range.

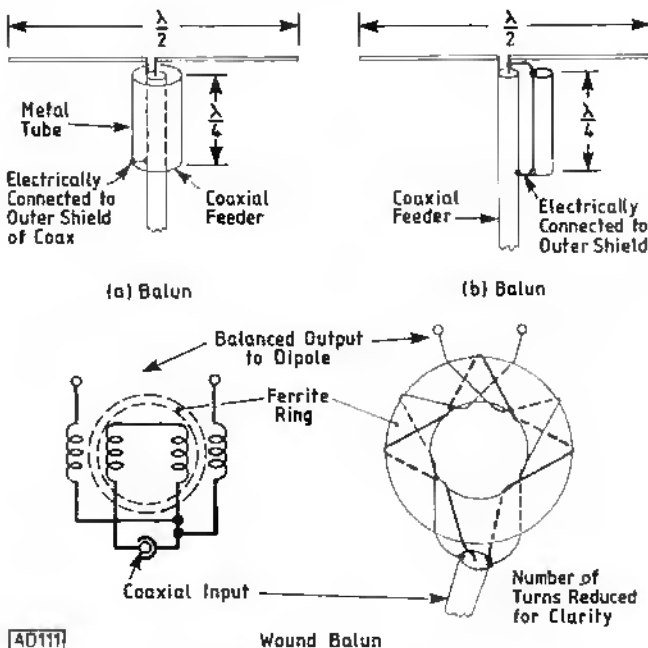


Fig. 92: Balun transformers

### Quarter Wave Transformer

Where it is necessary to transform an aerial impedance to match a particular feeder cable, use can be made of a quarter wave "stub" as shown in Fig. 93. Here, a full-wave aerial is to be fed in the centre (where the impedance is around 5,000 ohms) with twin feeder whose characteristic impedance is 72 ohms. If the quarter-wave stub is made to have the correct characteristic impedance then the aerial impedance is transformed down by the stub to match that of the feeder.

$$Z_m (\text{matching stub}) = \sqrt{Z_{\text{aerial}} \times Z_{\text{line}}}$$

$$= \sqrt{5000 \times 72}$$

$$= 600 \text{ ohms}$$

(An open-wire line of 16 s.w.g. conductors spaced 112mm (4 1/2 in) apart would have a Zo of 600 ohms).

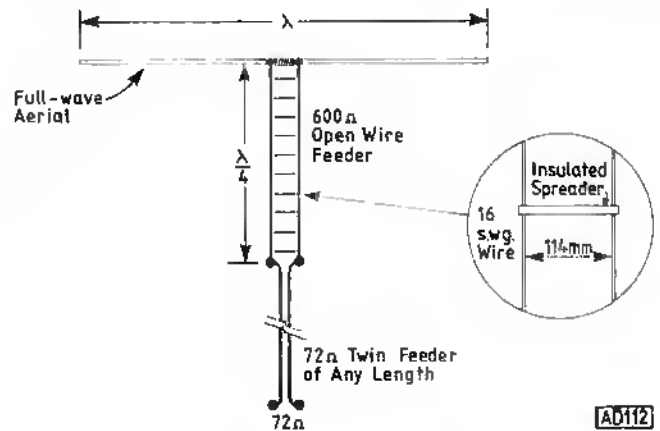


Fig. 93: A 1/4-wave transformer

### Interference

Non-interference with other radio users, whether they be military, commercial, amateur or domestic, is a condition of the Licence.

An understanding of the way in which interference is caused and how it can be avoided or cured is needed, not only for the RAE, but later on, when you obtain your licence; you will then be in a position to maintain a good clean transmission and live in peace with your neighbours (and the Home Office Inspector).

No practical transmitter is absolutely perfect and in addition to its correct output, is bound to radiate some spurious signals, however small. If these are not kept to a very low level, interference with receivers (TV or radio) operating nearby may result.

Similarly, no practical receiver is absolutely perfect, so when it is tuned to a particular frequency it may be subjected to interference by strong signals on other frequencies, as may be the case if it is situated in close proximity to a radio transmitter.

Interference can also be caused to audio systems, etc., when subjected to strong r.f. fields. Here, the signal enters the equipment and is then rectified or amplitude demodulated, usually by the emitter-base junction of a transistor in the audio pre-amplifier stages, resulting in breakthrough. An increasing number of hi-fi systems employing transistors are prone to interference of this nature.



## TVI, BCI, AND AFI

Interference can usually be separated into three main categories: television (t.v.i.), radio broadcast (b.c.i.), and audio (a.f.i.).

Television and radio broadcasting are "protected" services and the Post Office may be called upon to investigate cases of interference with these and other authorised transmissions. Audio amplifiers, on the other hand, are not intended to be radio receivers and so will not be afforded the same facilities.

In general, all interference results either from deficiencies in the transmitter or the apparatus being interfered with. Let us look initially at the transmitting end.

## DEFICIENCIES AT THE TRANSMITTER

### Design and Construction

It is important that the various r.f. signals present within the transmitter are not allowed to radiate directly. Efficient screening is essential, as is the filtering of h.t. and other power supplies, particularly the mains input. A suitable mains filter is shown in Fig. 94. Decoupling and bypass capacitors should be of mica or ceramic, having low inductance properties. (See section on capacitors.) Wiring should be short and direct to minimise stray inductance and capacitance.

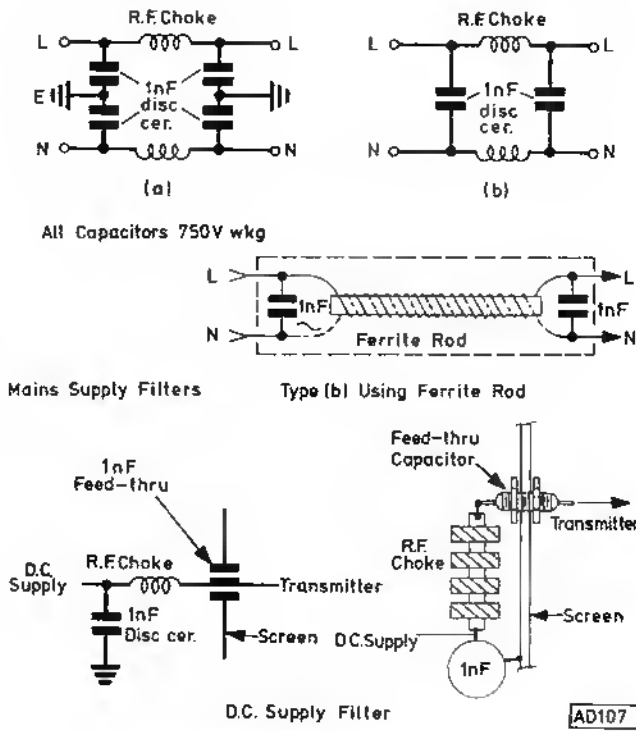


Fig. 94: Power supply filters

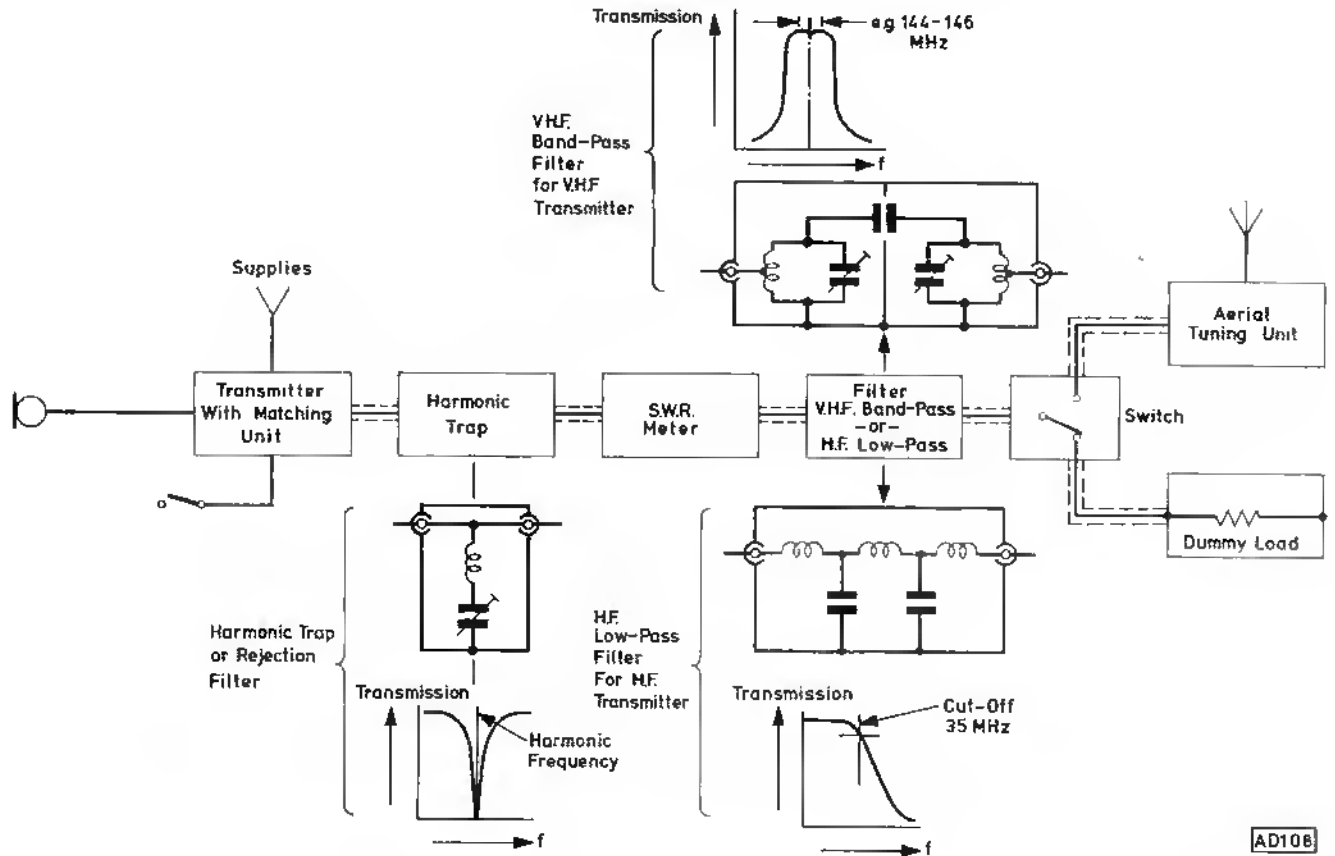


Fig. 95: Block diagram of a well-screened transmitting station

Tuning capacitor spindles protruding through front panels are often a source of spurious signals and should therefore be of an insulated material or have an insulated coupling.

The cut-out for a panel meter can often cause problems and a screening can over the rear of the meter is desirable. In general, try to ensure that the case of the transmitter is radiation-proof. Commercially made transmitters, including those for the amateur market, already incorporate most of these features and the maker's data sheet usually quotes the level of spurious emissions one may expect.

The block diagram of a well-screened transmitting station is shown in Fig. 95. The transmitter is well protected and its supply leads filtered, ensuring negligible direct radiation. The output passes via a coaxial cable to a harmonic trap, which usually consists of a series-resonant circuit, housed in a screened box and tuned to the particular harmonic likely to cause interference. For example, it might be tuned to 42MHz, attenuating the 3rd harmonic of 14MHz which could be the source of t.v.i. in a Channel 1 reception area. The output then passes via a coaxial cable to the standing-wave ratio (s.w.r.) bridge, which indicates relative forward and reflected power levels.

From here it is fed through a filter, again housed in a screened box which, in the case of a transmitter operating on bands up to 30MHz, would be of the low-pass type, attenuating spurious signals above this frequency. For a v.h.f. (2m) transmitter, a band-pass filter attenuating spurious signals either side of the pass-band frequencies, would be used.

In practice, the transmitter tuning would first be adjusted into a dummy load. The output would then be switched to an aerial tuning unit which is used to provide optimum matching to the aerial with the minimum of reflected power (indicated on the s.w.r. bridge).

Note: All interconnecting coaxial cables and terminations should be well soldered.

## Aerial and Feeder

The aerial should be sited as high as possible away from neighbouring buildings, TV and radio aeri- als, etc.

A vertical transmitting aerial is more likely to induce strong fields into nearby equipment than a horizontal one. This is due to the fact that it relies on a ground connection which can cause interfering currents in nearby conductors. In addition, vertically polarised signals are much more likely to be picked up by vertical down-leads, such as those used for television aeri- als.

It is important that all the transmitter power should be radiated by the aerial proper and that no emission should take place from the feeder cable itself. This means that the currents in each conductor of the feeder should be equal and opposite.

Where a dipole aerial is fed by an unbalanced coaxial cable, there is significant imbalance in the current distribution and some radiation from the feeder results. The feeder, usually being vertical, readily causes interfering currents to be induced into nearby television down-leads. To overcome this problem, a balance-to-unbalance transformer (balun) is connected at the centre of the dipole, as shown in Fig. 92. In other types of aeri- als and feeders, correct adjustment of the tuning unit is all-important in reducing feeder radiation to a minimum.

## Operation

Excessive drive in any of the transmitter stages will increase the level of harmonics, so power should be kept to the minimum consistent with efficient operation.

Tuning of the final power amplifier and adjustment of the aerial tuning unit will have a considerable effect on the amount of spurious signals radiated. When tuning the transmitter power amplifier into a dummy load, increase the coupling only until the correct power level is obtained. Do not overcouple the transmitter or the Q of the p.a. tank circuit will be reduced, with a consequent increase of spurious emissions. This also applies when adjusting the aerial tuning unit.

An abrupt keying characteristic causes excessive side frequencies, so check each side of your transmission for key clicks (see page 819).

Overmodulation produces excessively wide sidebands and causes splatter; always monitor the modulation level and ensure that overmodulation does not occur (see page 925).

The audio bandwidth necessary for good speech communication is about 3kHz. The modulation circuit of the transmitter should therefore have a rapidly falling response above 3kHz in order to avoid the radiation of excessive and unnecessary sidebands.

## Summary

Let us summarise the requirements for keeping deficiencies at the transmitter to a minimum:

1. Use correct components in the transmitter, well laid out.


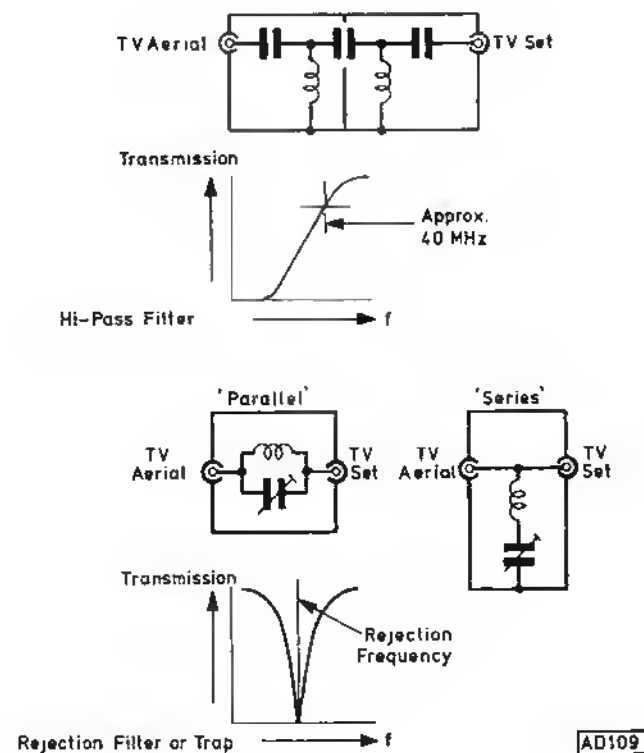


Fig. 96: TV interference rejection filters

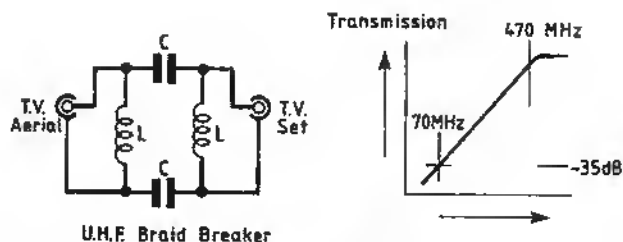2. Prevent direct radiation from the transmitter and associated leads by screening and filtering.
  3. Use appropriate filters in the transmitter output.
  4. Use a dummy load for tuning up and a suitable aerial tuning unit. Do not overcouple.
  5. Keep aerials in the clear and avoid radiation from the feeder cable (balun transformer).
  6. Tune up carefully: do not overdrive or overmodulate.
- Check your transmission regularly.



## DEFICIENCIES AT THE RECEIVER

The latest statistics (for 1976) indicate a dramatic fall in the number of complaints regarding transmitter interference. However, the greater proportion of those made were attributed to deficiencies in receiver design.

In many instances, interference is the result of a receiving installation of poor standard; e.g. indoor aerial, aerial incorrect type for area, downlead incorrectly installed, receiver incorrectly installed, excessively long mains leads or speaker leads, etc. etc.

Considering the problem of t.v.i., strong signals can enter the receiver via the aerial and cause interference by cross-modulation in the r.f. or subsequent stages. A high-pass or rejection filter for the frequency concerned must be fitted in the aerial lead, as shown in Fig. 96: the series-tuned filter being generally more effective.

Masthead amplifiers are a notorious cause of interference as they have broadband input characteristics, some extending from 10MHz to 1,000MHz. Cross-modulation and swamp effects are common. A high-pass filter should be fitted between the aerial and the input to the amplifier, but in practice difficulties arise here because the aerial has to be taken down and the filter made weatherproof.


However, the most common method by which r.f. will enter the receiver is by the presence of "braid" currents in the aerial downlead. These r.f. currents flow through earthy parts of the receiver causing r.f. voltages to be produced in susceptible parts of the circuit.

A "braid breaker", suitable for u.h.f. television, is shown in Fig. 97. The reactance of the series capacitors is high at frequencies up to 30MHz, effectively "breaking" the downlead, but at u.h.f. it is low, resulting in negligible attenuation of the television signal.

Where "braid currents" in the downlead cause interference at h.f. and v.h.f., an alternative circuit can be used. Here a short length of the coaxial downlead cable is wound on a ferrite ring, increasing the inductive reactance of the outside braid without affecting the signals within. An alternative to the ferrite ring, and almost as effective, is to wind the co-ax around a ferrite aerial rod.

If the interference is entering the receiver by way of the mains lead, a mains filter as shown in Fig. 94 should be installed. In the case of hi-fi systems, it can also be picked up on speaker leads, so decoupling these with a disc ceramic capacitor of 1nF to 10nF is often effective. A ferrite ring may be required in addition, if the problem is really severe.

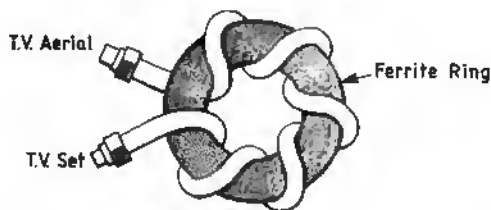It is unwise to incorporate modifications inside the receiver, as you may invalidate its warranty and be held responsible for any subsequent malfunction. In difficult cases it would be wise to consult the dealer or manufacturer.



Ferrite Ring Filter  
(The tv. feeder is made into a coaxial choke)  
Also useful on mains & loudspeaker leads

AD133

Fig. 97: "Braid-breakers" for u.h.f. and h.f./v.h.f.

## Summary

1. Check that the receiving installation is of adequate standard for the reception area.
2. If the interference is entering via the aerial lead, fit a high-pass or rejection filter.
3. If cross-modulation occurs in a mast-head amplifier, fit a high-pass filter in the aerial feed to it.
4. If the interference is entering via the downlead braid, fit a ferrite ring or capacitive braid-breaker.
5. If the interference is entering via the mains lead or other cables, fit a mains filter or ferrite ring.
6. If the problems are caused by direct radiation, try repositioning the aerials, feeders, etc. Wherever possible, avoid making internal modifications to receivers or audio systems. In difficult cases, refer to manufacturer.

## Note:

An excellent series of articles on interference appeared in *Radio Communication*, May 1975. Some back-issues are available from the Radio Society of Great Britain, 35 Doughty Street, London WC1N 2AE. Alternatively your local Radio Club or a nearby radio amateur may be able to help with a copy.

## SITTING THE R.A.E.

It is a good plan to set yourself regular revision two or three nights a week prior to the examination. Allocate specific subjects each night so that everything is covered in good time and practice answering specimen questions in writing and time yourself.

It is best to leave the night before the exam relatively free from commitments. This is a good time for collecting together the things you need, including your thoughts!

Take with you, two pencils and a pencil sharpener, two pens (in case one runs out), ruler, symbol stencil (if you have one), eraser and your examination card. Calculators are permitted provided they are of the electronic, battery-operated type. There are no restrictions on the functions the machine will perform.

You should receive your card at least a week before the examination. If not, contact the Examination Centre/Night School immediately and confirm that you are, in fact, registered.



When going to the Examination Centre, allow plenty of time; your bus may be delayed, you may have difficulty in parking your car. Aim to be in the building at least 30 minutes before the start. Locate the examination room, and be seated well before the examination commences.

When appropriate, your invigilator will distribute the papers: do not look at them until he gives the signal. Timing will begin from the point at which you are allowed to turn the paper over—don't panic! Give yourself at least ten minutes to read things through carefully and note any special instructions.

If, through no fault of your own, you arrive late, apologise to the invigilator then settle into your place quietly and attempt as many of the questions as you are able in the period remaining.

Remember, the paper is divided into two parts; Part 1 has two compulsory questions on licensing conditions (15 marks) and interference (15 marks). Part 2 requires six questions from a choice of eight to be answered (10 marks each). Failure in either section will regretfully result in failure of the examination as a whole.

Give yourself about twenty minutes for each of the eight questions and this will allow a little time at the end to look through your answers. The answers should not be over-elaborate or padded out: make your point as quickly and as clearly as possible, there is no time to waste. It is probably best to tackle the compulsory questions in Part 1 first and then move on to Part 2 where you have a choice. Here you can answer the easiest first and so gain a little extra time.

With answers containing calculations, it is a good idea to set out all the steps in detail. Then if a slip is made in the arithmetic, the examiner will see the correct formulae and methods have been used, and will mark accordingly.

Hints and tips on the drawing of diagrams were given earlier in this series (February 1978, page 764), but remember drawings take time, so keep them simple. You are not being examined in grammar or indeed spelling but neatness and cleanliness are relatively important, if only to avoid ambiguity. The examiner will not be impressed by illegible writing, scribbled diagrams, etc. If you make a mistake, cross it out with a single ruled line; it will then be ignored and you will not lose marks.

A few minutes before the end, stop, read through your answers and correct any minor omissions. Make sure all are numbered and lettered correctly and that your examination reference is quoted.

We wish you every success and hope to meet some of you on the air in the near future.

73 de GW3JGA es GW8CMY.

## NOTE

The syllabus and examination pattern for the R.A.E. are changing in 1979. We plan to publish a follow-up article to update this series

TRAN-SISTORS		11p BC114		13p BD135		14p BF273		14p OC72		45p 7447A		16 Pin DIL:		ZENER DIODES:		PRECISION POLY-CARBONATE CAPACITORS	
AC107	30p BC110	11p BC184	13p BD136	14p BF338	14p OC75	45p 7450	20p 1+	22p 400mW + - 5% 3V-33V	All High Stability—extremely Low Leakage		440V Value (µF)	A.C. RANGE Dimensions (mm)	Price each				
AC117	32p BC125	11p BC188	13p BD139	14p BF357	14p OC77	45p 7453	20p 10+	1W 10p each: 10/80p	L D		0.1	27	12.7	£1.34			
AC128	32p BC128	11p BC187	13p BD140	14p BF458	14p OC81	45p 7460	20p 50+	3V3-200V 16p each: 10/41.75	SKELETON PRESETS:		0.15	27	12.7	£1.52			
AC127	32p BC132	11p BC186	13p BD141	14p BF459	14p OC82	45p 7470	20p 100+	100 ohm to 1M—7p each: \$0 for 63 50p, 100 for £5 50p	(Vertical or Horizontal)		0.22	33	15	£1.66			
AC125	32p BC134	11p BC185	13p BD142	14p BF458	14p OC81	45p 7473	20p 100+	100 ohm to 1M—7p each: \$0 for 63 50p, 100 for £5 50p	18 Pin DIL:		0.25	33	16	£1.78			
AC126K	32p BC135	11p BC182	13p BD143	14p BF459	14p OC82	45p 7474	20p 100+	100 ohm to 1M—7p each: \$0 for 63 50p, 100 for £5 50p	4 Pin:		0.33	33	16	£1.92			
AC141K	44p BC137	11p BC212L	14p BD182	14p BF431	14p TIP29	54p 7475	20p 100+	100 ohm to 1M—7p each: \$0 for 63 50p, 100 for £5 50p	4 Pin:		0.47	33	19	£2.04			
AC142	44p BC138	11p BC213	14p BD187	14p BF431	14p TIP31A	55p 7476	20p 100+	100 ohm to 1M—7p each: \$0 for 63 50p, 100 for £5 50p	4 Pin:		0.6	33	19	£2.24			
AC142K	44p BC139	11p BC214	14p BD188	14p BF431	14p TIP32A	57p 7482	20p 100+	100 ohm to 1M—7p each: \$0 for 63 50p, 100 for £5 50p	4 Pin:		0.68	50-8	22	£2.48			
AC153K	44p BC140	11p BC214	14p BD188	14p BF431	14p TIP33	59p 7490	20p 100+	100 ohm to 1M—7p each: \$0 for 63 50p, 100 for £5 50p	4 Pin:		1.0	50-8	22	£2.64			
AC163	44p BC142	11p BC214B	14p BD188	14p BF431	14p TIP33	59p 7490	20p 100+	100 ohm to 1M—7p each: \$0 for 63 50p, 100 for £5 50p	4 Pin:		1.5	50-8	23.4	£3.14			
AC178	35p BC143	11p BC214L	14p BD188	14p BF431	14p TIP33	59p 7490	20p 100+	100 ohm to 1M—7p each: \$0 for 63 50p, 100 for £5 50p	4 Pin:		2.0	50-8	23.4	£3.74			
AC178	44p BC147	11p BC235	17p BF111	14p BF431	14p TIP33	59p 7490	20p 100+	100 ohm to 1M—7p each: \$0 for 63 50p, 100 for £5 50p	4 Pin:		0.1	27	12.7	£1.34			
AC178	44p BC147A	11p BC235	17p BF111	14p BF431	14p TIP33	59p 7490	20p 100+	100 ohm to 1M—7p each: \$0 for 63 50p, 100 for £5 50p	4 Pin:		0.15	27	12.7	£1.52			
AC178	44p BC147B	11p BC235	17p BF111	14p BF431	14p TIP33	59p 7490	20p 100+	100 ohm to 1M—7p each: \$0 for 63 50p, 100 for £5 50p	4 Pin:		0.22	33	15	£1.66			
AC187K	42p BC148	11p BC232C	17p BF117	14p BF431	14p TIP33	59p 7490	20p 100+	100 ohm to 1M—7p each: \$0 for 63 50p, 100 for £5 50p	4 Pin:		0.25	33	16	£1.78			
AC187	42p BC148	11p BC232C	17p BF117	14p BF431	14p TIP33	59p 7490	20p 100+	100 ohm to 1M—7p each: \$0 for 63 50p, 100 for £5 50p	4 Pin:		0.33	33	16	£1.92			
AC188K	42p BC149	11p BC232C	17p BF117	14p BF431	14p TIP33	59p 7490	20p 100+	100 ohm to 1M—7p each: \$0 for 63 50p, 100 for £5 50p	4 Pin:		0.47	33	19	£2.04			
AC193K	41p BC149B	11p BC231A	17p BF121	14p BF431	14p TIP33	59p 7490	20p 100+	100 ohm to 1M—7p each: \$0 for 63 50p, 100 for £5 50p	4 Pin:		0.6	33	19	£2.24			
AC194K	41p BC149C	11p BC231A	17p BF121	14p BF431	14p TIP33	59p 7490	20p 100+	100 ohm to 1M—7p each: \$0 for 63 50p, 100 for £5 50p	4 Pin:		0.68	50-8	22	£2.48			
AC194K	41p BC149C	11p BC231A	17p BF121	14p BF431	14p TIP33	59p 7490	20p 100+	100 ohm to 1M—7p each: \$0 for 63 50p, 100 for £5 50p	4 Pin:		1.0	50-8	22	£2.64			
AC194K	41p BC149C	11p BC231A	17p BF121	14p BF431	14p TIP33	59p 7490	20p 100+	100 ohm to 1M—7p each: \$0 for 63 50p, 100 for £5 50p	4 Pin:		1.5	50-8	23.4	£3.14			
AC194K	41p BC149C	11p BC231A	17p BF121	14p BF431	14p TIP33	59p 7490	20p 100+	100 ohm to 1M—7p each: \$0 for 63 50p, 100 for £5 50p	4 Pin:		2.0	50-8	23.4	£3.74			
AD140	84p BC153	11p BC232A	17p BF122	14p BF431	14p TIP33	59p 7490	20p 100+	100 ohm to 1M—7p each: \$0 for 63 50p, 100 for £5 50p	4 Pin:		0.1	27	12.7	£1.34			
AD142	84p BC153	11p BC232A	17p BF122	14p BF431	14p TIP33	59p 7490	20p 100+	100 ohm to 1M—7p each: \$0 for 63 50p, 100 for £5 50p	4 Pin:		0.15	27	12.7	£1.52			
AD143	83p BC157	11p BC232C	17p BF122	14p BF431	14p TIP33	59p 7490	20p 100+	100 ohm to 1M—7p each: \$0 for 63 50p, 100 for £5 50p	4 Pin:		0.22	33	15	£1.66			
AD149	80p BC157A	11p BC232C	17p BF122	14p BF431	14p TIP33	59p 7490	20p 100+	100 ohm to 1M—7p each: \$0 for 63 50p, 100 for £5 50p	4 Pin:		0.25	33	16	£1.78			
AD161	85p BC159	11p BC232C	17p BF122	14p BF431	14p TIP33	59p 7490	20p 100+	100 ohm to 1M—7p each: \$0 for 63 50p, 100 for £5 50p	4 Pin:		0.33	33	16	£1.92			
AD162	84p BC159B	11p BC232C	17p BF122	14p BF431	14p TIP33	59p 7490	20p 100+	100 ohm to 1M—7p each: \$0 for 63 50p, 100 for £5 50p	4 Pin:		0.47	33	19	£2.04			
AF114	32p BC159	11p BC232C	17p BF122	14p BF431	14p TIP33	59p 7490	20p 100+	100 ohm to 1M—7p each: \$0 for 63 50p, 100 for £5 50p	4 Pin:		0.6	33	19	£2.24			
AF115	32p BC159B	11p BC232C	17p BF122	14p BF431	14p TIP33	59p 7490	20p 100+	100 ohm to 1M—7p each: \$0 for 63 50p, 100 for £5 50p	4 Pin:		0.68	50-8	22	£2.48			
AF116	32p BC159C	11p BC232C	17p BF122	14p BF431	14p TIP33	59p 7490	20p 100+	100 ohm to 1M—7p each: \$0 for 63 50p, 100 for £5 50p	4 Pin:		1.0	50-8	22	£2.64			
AF117	32p BC161	11p BC232C	17p BF122	14p BF431	14p TIP33	59p 7490	20p 100+	100 ohm to 1M—7p each: \$0 for 63 50p, 100 for £5 50p	4 Pin:		1.5	50-8	23.4	£3.14			
AF118	30p BC167B	11p BC232C	17p BF122	14p BF431	14p TIP33	59p 7490	20p 100+	100 ohm to 1M—7p each: \$0 for 63 50p, 100 for £5 50p	4 Pin:		2.0	50-8	23.4	£3.74			
AF121	30p BC168A	11p BC232C	17p BF122	14p BF431	14p TIP33	59p 7490	20p 100+	100 ohm to 1M—7p each: \$0 for 63 50p, 100 for £5 50p	4 Pin:		0.1	27	12.7	£1.34			
AF124	34p BC168B	11p BC232C	17p BF122	14p BF431	14p TIP33	59p 7490	20p 100+	100 ohm to 1M—7p each: \$0 for 63 50p, 100 for £5 50p	4 Pin:		0.15	27	12.7	£1.52			
AF128	34p BC168C	11p BC232C	17p BF122	14p BF431	14p TIP33	59p 7490	20p 100+	100 ohm to 1M—7p each: \$0 for 63 50p, 100 for £5 50p	4 Pin:		0.22	33	15	£1.66			
AF127	38p BC170	11p BC232C	17p BF122	14p BF431	14p TIP33	59p 7490	20p 100+	100 ohm to 1M—7p each: \$0 for 63 50p, 100 for £5 50p	4 Pin:		0.25	33	16	£1.78			
AF139	45p BC170B	11p BC232C	17p BF122	14p BF431	14p TIP33	59p 7490	20p 100+	100 ohm to 1M—7p each: \$0 for 63 50p, 100 for £5 50p	4 Pin:		0.33	33	16	£1.92			
AF174	84p BC170C	11p BC232C	17p BF122	14p BF431	14p TIP33	59p 7490	20p 100+	100 ohm to 1M—7p each: \$0 for 63 50p, 100 for £5 50p	4 Pin:		0.47	33	19	£2.04			
AF179	74p BC171	11p BC232C	17p BF122	14p BF431	14p TIP33	59p 7490	20p 100+	100 ohm to 1M—7p each: \$0 for 63 50p, 100 for £5 50p	4 Pin:		0.6	33	19	£2.24			
AF179	74p BC171A	11p BC232C	17p BF122	14p BF431	14p TIP33	59p 7490	20p 100+	100 ohm to 1M—7p each: \$0 for 63 50p, 100 for £5 50p	4 Pin:		0.68	50-8	22	£2.48			
AF181	75p BC171B	11p BC232C	17p BF122	14p BF431	14p TIP33	59p 7490	20p 100+	100 ohm to 1M—7p each: \$0 for 63 50p, 100 for £5 50p	4 Pin:		1.0	50-8	22	£2.64			
AF182	36p BC172	11p BC232C	17p BF122	14p BF431	14p TIP33	59p 7490	20p 100+	100 ohm to 1M—7p each: \$0 for 63 50p, 100 for £5 50p	4 Pin:		1.5	50-8	23.4	£3.14			
AF239	45p BC172B	11p BC232C	17p BF122	14p BF431	14p TIP33	59p 7490	20p 100+	100 ohm to 1M—7p each: \$0 for 63 50p, 100 for £5 50p	4 Pin:		2.0	50-8	23.4	£3.74			
AF279	80p BC172C	11p BC232C	17p BF122	14p BF431	14p TIP33	59p 7490	20p 100+	100 ohm to 1M—7p each: \$0 for 63 50p, 100 for £5 50p	4 Pin:		0.1	27	12.7	£1.34			
ASV67	61p BC173	11p BC232C	17p BF122	14p BF431	14p TIP33	59p 7490	20p 100+	100 ohm to 1M—7p each: \$0 for 63 50p, 100 for £5 50p	4 Pin:		0.15	27	12.7	£1.52			
AU110	61p BC173B	11p BC232C	17p BF122	14p BF431	14p TIP33	59p 7490	20p 100+	100 ohm to 1M—7p each: \$0 for 63 50p, 100 for £5 50p	4 Pin:		0.22	33	15	£1.66			
AU113	48p BC176	11p BC232C	17p BF122	14p BF431	14p TIP33	59p 7490	20p 100+	100 ohm to 1M—7p each: \$0 for 63 50p, 100 for £5 50p	4 Pin:		0.25	33	16	£1.78			
BC107	12p BC117	11p BCY31	13p BF195	14p BF431	14p TIP33	59p 7490	20p 100+	100 ohm to 1M—7p each: \$0 for 63 50p, 100 for £5 50p	4 Pin:		0.33	33	16	£1.92			
BC107A	14p BC177A	11p BCY38	13p BF199	14p BF431	14p TIP33	59p 7490	20p 100+	100 ohm to 1M—7p each: \$0 for 63 50p, 100 for £5 50p	4 Pin:		0.47	33	19	£2.04			
BC107B	14p BC178	11p BCY42	13p BF199	14p BF431	14p TIP33	59p 7490	20p 100+	100 ohm to 1M—7p each: \$0 for 63 50p, 100 for £5 50p	4 Pin:		0.6	33	19	£2.24			
BC108	12p BC178A	11p BCY70	13p BF200	14p BF431	14p TIP33	59p 7490	20p 100+	100 ohm to 1M—7p each: \$0 for 63 50p, 100 for £5 50p	4 Pin:		0.68	50-8	22	£2.48			
BC108A	14p BC178B	11p BCY71	13p BF204	14p BF431	14p TIP33	59p 7490	20p 100+	100 ohm to 1M—7p each: \$0 for 63 50p, 100 for £5 50p	4 Pin:		1.0	50-8	22	£2.64			
BC108C	14p BC178A	11p BCY72	13p BF224	14p BF431	14p TIP33	59p 7490	20p 100+	100 ohm to 1M—7p each: \$0 for 63 50p, 100 for £5 50p	4 Pin:		1.5	50-8	23.4	£3.14			
BC109C	14p BC179B	11p BCZ11	13p BF240	14p BF431	14p TIP33	59p 7490	20p 100+	100 ohm to 1M—7p each: \$0 for 63 50p, 100 for £5 50p	4 Pin:		2.0	50-8	23.4	£3.74			

# Portable Calculating Power -at the flick of your wrist!

"Over 22,000 sold to date."

AVAILABLE ONLY AS A KIT.



A wrist calculator—the ultimate in common-sense portable calculating power. Goes where you go, ready for action at a flick of your wrist.

By virtue of its size, a wrist calculator is different to a pocket calculator. And now this wrist-machine has another difference. It has even more power than some much larger pocket calculators!

And what's more, because it's a kit, supplied to you direct from the manufacturer, it costs just £9.95 (plus 8% VAT, P&P). And for that you get a calculator with extra power, and all the satisfaction of building it yourself!

## Put real calculating power up your sleeve.

The Science of Cambridge wrist calculator gives you the full range of arithmetic functions (+, -, ×, =). It uses ordinary algebraic logic, which means you enter calculations as you would write them. It has a % key, the convenience functions  $\sqrt{x}$ ,  $1/x$ ,  $x^2$  and a full 5-function memory.

And incredibly, it has a clear-last-entry key, pi, brackets, and  $\div$ . It even has an automatic linear metric conversion function!

Very few ordinary calculators have the same functions for the same sort of money.

## Now 10 keys can do the work of 32.

All those functions, from just 10 keys? In such a small calculator? The secret lies in the special four-level keyboard. Each level has a different set of functions. Simple two-way switching system allows you to select any keyboard level quickly and easily. Each set of functions is carefully grouped, to let you whisk through calculations with the minimum of switching.

And the answers come up bright and clear, too. The display uses 8 full-size red LED digits. It has wide-angle magnification, and is easily visible under any light conditions.

## More battery power, too!

With the Science of Cambridge wrist-calculator, you'll get up to 30 hours use between battery changes (that's a lot of calculating!).

## Assembling the Science of Cambridge wrist calculator.

The wrist calculator comes as finished components, ready for assembly. All you need is two or three hours, and a fine-tip soldering iron.

If anything goes wrong, we'll replace damaged components free. We want you to enjoy building the kit, and to end up with a valuable, useful, powerful calculator.

## Contents.

Acrylic/ABS case and display window parts. Two-part stitched strap and spring bar clips. PCB. Special direct-drive chip (no interface chip required). Display. Keyboard components. Batteries.

Each of the 34 components is contained in a plastic box; and neatly shrink-wrapped, accompanied by full instructions for assembling and using the calculator. All components are fully guaranteed.

**KIT ONLY**  
**£9.95**  
Plus VAT, P&P

The wrist calculator kit is available only direct from Science of Cambridge. If, for any reason, you're not completely satisfied with your wrist calculator, return it to us within 10 days for a full cash refund. Send the coupon today!

# Science of Cambridge Ltd.

(Previously Sinclair Instrument Ltd)

6 Kings Parade, Cambridge, Cambs. CB2 1SN.

Regd No. 213817088.

To: Science of Cambridge Ltd., 6 Kings Parade, Cambridge, Cambs. CB2 1SN.

\*Please send me.....(qty) Science of Cambridge wrist calculators kits, at £9.95 plus 80p Vat and 25p P&P (total £11) each.

Overseas orders may be subject to postal surcharge

\*I enclose cheque/PO/money order for £.....

NAME.....

ADDRESS.....

\*Complete as appropriate

PW6

(please print)



# ON THE AIR

## AMATEUR BANDS

by Eric Dowdeswell G4AR

Our SSTV expert Paul Barker of Sunderland has now become G8OVD and soon will be able to look back at the other chaps! Paul studied at home for the RAE and had only the RSGB's RAE manual and a few library books to see him through. He managed to "copy" three VKs on 20m SSTV so completing his SAC! Best of luck on the air OM. Likewise John Overton did the trick in Milngavie, Glasgow and so sports GM4GUA now, having already passed the code test. He's using an HW32A on 20m s.s.b. for the time being but a KW2000B is on the way.

Brian Smith is well away in Barry, Glam, with his new FRG7. Having been disgusted with what he has heard of the CB band just below 28MHz he says he'll get stuck into the RAE studies and get a proper ticket! After a spell of ten years away from the amateur bands Ken Proctor of 35 Hertford Close, Eastfield, Scarborough, Yorks, is active again and would like to hear from old friends including Bernard Hughes BRS25901 who contributes to this column. Ken has a Trio 9R59DS and 90ft of wire and covers all the bands.

The note on David Greenhalgh in the February column resulted in G3SHW of Stockport coming up with a Lafayette HA350 for him which illustrates a little of the fine spirit of amateur radio. David, in Poynton, Cheshire is delighted and hopefully he'll be contributing to the column in future.

After using a domestic portable for a while J. Goodier of Marple, near Stockport, acquired an FRG7 and really found out what the amateur bands are all about. He wants a good prefix list and so, as ever, the answer is Geoff Watts of 62 Belmore Road, Norwich who will deliver the goods for just 40p. From Newport, Gwent comes a first report from Martin Llezers and a note on his local ARS, reported later. He has 250ft of wire on his Realistic DX160 and an 8ft rod aerial for "the h.f. bands". I've suggested that he try the long wire on those bands too!

Now here is an interesting letter from Bill Land BRS34761, 7 Wellbrook Road, Bishops Clare, Cheltenham, Glos, who admits to being 72 years young and an addict of RTTY for which he has a Creed 7B printer running from his Eddystone 750 and Trio 9R59DS. Bill wants to hear from others using this mode and can help with a list of parts for the 7B. Another old-timer is John Whiting of Fareham, Hants, who started with crystal sets in 1922 but now sports an FRG7, listening mainly on 10m for the moment. He can cope with the code test so is contemplating studying for the RAE.

Fame at last! Bob Griffiths writes for the first time to say we have a keen young reader on the Isle of Wight! He, too, has had a lay-off of 14 years but is now back in the swim again but with a lot of pertinent remarks on the plethora of UA stations! Must come as a shock after the relative hush of the bands in days gone by. Bob uses an EA12, AR88D plus converters for 2m and 70cm. His aerial farm consists of 132ft wire, 20m ground-plane, 20m V-dipole and a vertical for 80m.

From Morpeth, Northumberland comes John Hodgson again with DX heard on his Realistic DX160 and long wire. He has received QSL cards from CB'ers in Sweden and Norway! John is keen on RTTY so suggest he writes to Bill Land mentioned above. Bob Bell of 5 Byron Avenue, Blyth, Northumberland can't be too far from John just quoted above and they ought to get together since Bob would like to start a club in the area. Bob is yet another FRG7 owner, having been SWLing for some 25 years and worked his way through a number of sets.

**CLUB NEWS** Geoff Cole G4EMN, secretary of the Wessex ARG, oft mentioned here, had applications for membership from a couple of readers situated a long way from Wessex. Although flattered, he says that this is not quite the ideal! So, anyone who wants to join a club, try to locate your local group or write to the RSGB, 35 Doughty Street, London WC1 for the address. Geoff rightly says that every reader of this column ought to belong to a club.

**Blackwood and District ARS** GW8GW meets every Friday 1930hrs at Oakdale Community College, near Blackwood, Gwent. On May 12th GW8LJJ talks on *Practical Construction* and the 19th is film night, *Printed Circuit Manufacture*. Write to Steve Cole GW4BLE, 10 Llanthewy Road, Newport.

**Mid-Warwickshire ARS** first and third Mondays 2000hrs at 61 Emscote Road, Warwick with G3UDN on the air. They'd like to see PW readers, particularly Nick Smith A9050 and C. J. Roe of this column.



Contact Norman Read G8CXL, 86 Telford Avenue, Leamington Spa.

**Bury RS G3BRS**, every Tuesday at Mosses Centre, Bury at 1930hrs with RAE courses, code training, local c.w. nets, new local repeater GB3MA on 70cm. Whew! It's all go! Hon. Sec. is Eric Thirkell G4FQE, Mosses Community Centre, Cecil Street, Bury.

**Stevenage and District ARS** get together at 2015hrs on first and third Thursdays at Staff Canteen, Hawker Siddeley Dynamics. Morse classes and RAE course at local college by G3SJR. May 18th is the date for a lecture by members of London UKFM Group, while on June 1st G3AGP talks on *Electronics in Medicine*. Contact Trevor Tugwell G8KMV, 11 The Dell, Stevenage, Herts.

**Silverthorn RC** produces a ten-page newsletter "Spurious" so they're pretty active, meeting every Friday 1930hrs at Friday Hill House, Simmons Lane, Chingford, London E4. Contact C. J. Hoare, Hon. Sec., at this QTH.

**Newport ARS** meets Mondays 1930hrs at Brynglas House Community Centre, Newport with RAE and code classes coming up. Write to Martin Liezers, 32 Barrack Hill, Newport.

## Log extracts

**B. Smith:**—80m C5ABC (Gambia) 4U1ITU 20m C5AAF FC9UC JY5HH ZL2AM 15m CE3BPC C31LU

**K. Proctor:**—80m EA8QJ ZB2G PJ8CO KL7AVX ZL3BX CO7RS 9Y4NP 40m CO4DC HP1XYA ZL1BAQ ZL2BDP ZL3RD 20m VP8PT HP3XKB HL1JI HK0BBF 15m FP8DX KL7JEJ JA9IWN 10m FG7BA

**J. Hodgson:**—80m J3AAG OY5NS PJ8CO 8P6FV 40m TG4NX YV5APF 20m FM7WV HK1NR VE8RCF VK7AE VP2DAW 15m HK0QA KL7GRP ZS2MI (Marion Is) ZB2G 10m EA9FL HH2MC VU2DK.

**J. Whiting:**—10m CT2AX EA8BS SV1HX.  
**B. Land:**—RTTY 20m DK6RY EA3ABU IT9BWT JY5KR K6XP OE2KO SM6HUG YU2BOR W2WIX.

**M. Liezers:**—80m KZ5JM ZB2G 5B4DI 20m HK0QA KM6FC YB0HH 15m KL7GRP VP1AB 10m C5ABC EP2RL.

**J. Goodier:**—20m CT4YN FC9UC.

All s.s.b. except where stated otherwise.

## VHF BANDS

by Ron Ham BRS15744

**Richard Staples**, G8MME, Lymn, Cheshire, is active on both 2m and 70cm s.s.b. On 2m he runs 400 watts from a pair of 4-250A valves to a couple of 10-element parabees, at 40ft a.g.l., and on 70cm, his 2m exciter, TS700G, drives a Microwave Modules Transverter and a home-brew 4CX250B amplifier producing 250 watts to a 48-element multibeam, mounted above his 2m array. Richard is looking for s.s.b. skeds on 70cm and will be reporting on future activity in the north-west of England. **Vic Hartopp**, G8COB, Northampton, uses an IC201 transceiver for all modes on 2m and has

Reports on the various bands are welcome and should be sent direct, by the 15th of the month, to:

**AMATEUR BANDS** Eric Dowdeswell G4AR, Silver Firs, Leatherhead Road, Ashted, Surrey KT21 2TW. Logs by bands, each in alphabetical order.

**MEDIUM and SW BANDS** Charles Molloy G8BUS, 132 Segars Lane, Southport, PR8 3JG. Reports for both bands must be kept separate.

**VHF BANDS** Ron Ham BRS15744, Faraday, Greytlars, Storrington, Sussex RH20 4HE.

recently been enjoying himself rebuilding a Mohican receiver, and listening to the American CBers on his HRO.

A couple of newcomers to v.h.f., **Henry Hatch**, G2CBB, South Croydon, using an IC215 is working through the repeaters and **Robin Bellerby**, G3ZYE, Hove, Sussex, taking part in his first 2m opening, did not realise there could be such pile-ups of stations on the repeaters. In Littlehampton, Sussex, **Norman Langridge**, using the v.h.f. section of his Yaesu FR400-Super DX receiver with a 3-element home-brew, loft mounted beam can always hear traffic through GB3SN, but, during the opening on March 7th he heard GW mobiles working through GB3BC which has encouraged Norman to modify his aerial system. Along the coast to Worthing where **David Wakefield**, BRS39756, uses the receiver of a Pye Vanguard on 2m, with a roof mounted dipole, and CR100 and R1475 receivers, fed by a long wire aerial, on the h.f. bands. David's interest in radio is further stimulated through his activities as a Cadet Wireless Operator in the Air Training Corps.

Despite the poor conditions and the low atmospheric pressure, 29.3in, **Alan Baker**, G4GNX, Newhaven, had a 59 contact on 2m s.s.b. at 1800 on February 26th with F1ENH/P, Boulogne, both running 15 watts, and at 1730 on March 2nd, in thick fog, on Beachy Head, near Brighton, Alan heard signals from repeaters ON0HT and ON0OV and a Buckingham station working through the Kent repeater, GB3KR, R4.

The atmospheric pressure remained around 29.5in from midnight on February 27th to midnight on March 2nd when it took off and climbed to 30.4in by noon on the 6th, and, true to form, the v.h.f.s opened up as the high pressure began to fall. During the evening of the 6th, **John Kuipers**, G4GUX, Brighton, worked G8LY, in Hampshire, on 70cm, first via GB3AW, Ashmansworth, Berks, RB10, and then through GB3BR, Brighton, RB6, and GB3PH, Portsmouth, RB2. Later he heard signals through GB3BK, Upper Basildon, RB6, GB3SD, Weymouth, RB14, had a c.w. contact with ON4VN and heard 2m signals through GB3BC, R6, GB3MH, on its new channel, R3, GB3WW, Carmel, Dyfed, R7 and FZ3THF, R4.

Around 1945 on the 6th, **Ken Smith**, BRS 20001, Horsham, received several French broadcast stations in Band II and patterning on u.h.f. TV channels, and earlier, **Graham Laucht**, G8OQM, Birmingham, worked G8KSN, Ramsgate, Kent first via GB3PI, Cambridge, R6, and then direct. Like Graham, **Brian Fenwick**, G8BTC, Brighton, heard a variety of repeater signals on 2m, including Cornwall, GB3NC, R5; Brian noticed that signals were often stronger on the input frequency than from the repeater. Frequently, on the

6th and 7th, I received a good picture from Lichfield, Ch 8, 189MHz, Continental f.m. stations in Band II and strong signals from GB3BC, BM and KR, with only dipoles feeding the respective receivers. At 0125 on the 7th, I heard two Portsmouth stations, G8NUI and G8OQN/M in contact via the London repeater, GB3LO, R7, and at 2152, another pair, G4GUX and **Martin Newell**, G8KOE, both in Brighton carried out a similar test on 70cm and had a QSO via the Portsmouth repeater.

At 0900 on the 7th, G4GNX/M using his new IC-240 to a  $\frac{5}{8}$  whip aerial, heard strong signals through GB3BC, from a low point in Brighton, F1EBE, Rouen, via GB3LO, and at midday on the 6th, he received signals from the Malvern Hills, GB3MH, R3, and Paris repeaters. At 2206, from Newhaven, Alan had a c.w. contact with ON6FT and at 0011 on the 7th he worked F1EVM/P, Caen, on 2m s.s.b.

The atmospheric pressure continued falling until 1800 on the 8th when it began rising rapidly, reaching 30.4in by midday on the 10th, and then fell back to 30.0in by noon on the 12th which, as expected, caused a tropospheric opening.

At 2230 on the 8th, newly licensed G8OQM/M, using a FT227R to a  $\frac{5}{8}$  whip aerial, travelled down to Beachy Head, Sussex, and heard GB3BM, his home repeater and then had QSOs through GB3BC. From Brighton's Race Hill, at 1900 on the 9th, G4GNX/M worked F1BBZ and F3KT via FZ8THF, Vichy, R0, a distance of 320 miles. **Roy Bannister**, G4GPX, Lancing, Sussex, succeeded in accessing the Vichy repeater but owing to UK traffic on R0 he could not complete a QSO. Both Alan and Roy heard the Ghent, ON0ON, R4, and Paris, R6, repeaters and during the evening of the 10th, **Clive Penna**, G3POI, Orpington, Kent, worked EA1AB on 2m c.w. and **Mike Rowe**, G8JVE, East Preston, Sussex, heard an EA1 and worked into France and Wales on 2m s.s.b. Around 2330 on that evening, **Alan Belfield**, G4GLN, Streatham, contacted an EA on 70cm c.w.

**John Branegan**, now licensed GM8OXQ, Saline, Fife, worked his first three countries, G3GZX, G18JTS, and GW4GTE during the 2m contest weekend, March 4th and 5th. John said "there was a definite lift on March 4th, and by 2200, GI signals into Scotland were very good and they could hear the Central Scotland repeater in GI".

Throughout the period, 9th to 12th there was frequent co-channel interference in Band II and u.h.f.-TV and at 0914 on the 11th I received a 599 signal from the Emley Moor beacon, GB3EM, on 70cm with only a dipole feeding the receiver.

The 10m band has been open almost daily from February 20th to March 15th with a familiar pattern of strong signals from Russian amateurs in the morning and from north-American amateur and CB stations during the afternoon and early evening. I heard VKs during the early mornings of February 26th and March 7th and JAs on March 5th and 11th working into Europe. On most days signals averaging 539 were heard from the Cyprus beacon, 5B4CY and the project TESSA beacon, ZE2JV. During the afternoons of March 1st and 2nd, **Don Butterworth**, G3IKO, Redhill, Surrey, heard the Bermuda beacon VP9BA and I logged the Bahrain beacon, A9XC, during the afternoons of the 5th and 6th.

February 26th was a good day on 10m for **Gordon Goodyer**, BRS 37345, Petworth, Sussex, who heard both A9XC and VP9BA in the morning as well as signals from amateurs in 22 countries. Although

signals were very strong throughout the day Gordon reports a drop off in strength around midday and a quiet band from 1430 to 1515. **Roger Bunney**, DX TV columnist, using his Hallicrafters 5-10 receiver logged transatlantic signals up to 37MHz on the 26th. **Nigel Golds**, BRS 36910, West Chiltington, Sussex, noted the powerful American stations around 1730 on March 11th and the Russians during the afternoon of the 12th.

The exceptional 10m conditions observed by Gordon and Roger on February 26th were followed by ionospheric disturbances, reported by the BBC World Service, on the 27th and 28th which may well have been caused by the solar storm recorded by **Cmdr Henry Hatfield**, Sevenoaks, Kent, **John Smith**, Rudgwick, Sussex, and myself from February 21st to 26th. What's more **John Branegan**, reported auroral activity, with plenty of 2m c.w. from EI, GW and LA, from 1830 to 1912 on February 27th and from 1657 to 1912 on March 1st. John has built a projection box attachment for his 2in telescope so that he can record the number of sunspots and since 2048 on March 5th he has been monitoring the telemetry signals from the new amateur radio satellite, OSCAR-8.

Despite frequent overcast skies, **Henry Hatfield** got a glimpse of the sun through his spectrohelioscope on March 6th when, in addition to sunspots, he saw several filaments and a ribbon flare, on the 10th he counted some 15 spots in four main groups, and on the 15th he noted a bright plage on the east limb. **Henry**, **John Smith** and myself recorded solar noise at 136 and 142MHz on March 2nd, and then daily from the 6th to the 13th with noise storm conditions on days 6th, 8th, 10th and 15th.

According to comments heard both on and off the air by **Alan Baker** and myself the "Slim Jim" 2m aerial described in our April issue works well and is very popular.

Let's hope that conditions will be good to provide plenty of DX for the RSGB's HF National Field Day on June 3rd and 4th and VHF NFD and SWL contest on July 1st and 2nd. Thanks again for all your reports, and good luck if you compete in the contests.

## What do the VHF's have to offer?

The accepted part of the radio frequency spectrum known as Very High Frequency ranges from 30 to 300MHz, (10-1 metres), and is generally used for communications by aircraft (108-136MHz), amateur radio (4m, 70.05-70.7 and 2m 144-146MHz), private and business mobile radio (71-88 and 165-174MHz), shipping (156-165MHz), satellites (136-137MHz), military, various emergency services and broadcasting by f.m. radio, Band II (88-108MHz) and television, Band I (41-67MHz) and Band III (176-215MHz).

The effective range of a v.h.f. signal is naturally limited by the terrain beneath its path and the prevailing atmospheric conditions. Broadly speaking, the propagation of signals between 30-80MHz is governed by the E region of the ionosphere, and above 80MHz, by conditions in the troposphere. These bands are therefore a challenge to both the listener and the transmitting amateur, to be ready for sudden sporadic-E disturbances between April and August and at any time, for a tropospheric opening, when the weather



is fine and the atmospheric pressure is high. These v.h.f. openings are exciting, because the signals travel more than ten times their normal range and as the v.h.f. bands are shared throughout Europe, there is a mine of DX, both sound and vision, to be found among the mix-up of continental signals while the event lasts.

During sporadic-E events, very strong signals are heard in the UK from east-European broadcast stations between 65-73MHz and even stronger signals, from a variety of continental mobiles, interfere with the Band I television channels. There are two beacons in the 4m band to listen for, GB3SU, 70·695MHz and GB3SX, 70·685MHz.

The 2m band is full of surprises throughout a tropospheric opening; and like most v.h.f. enthusiasts, our readers have heard and worked amateur stations, using all modes, over a wide area from Scandinavia to the Mediterranean Sea, and all parts of the UK.

First indications of an opening can come from any of the chain of 2m beacons ranging from Cornwall, GB3CTC, 144·915MHz, to Angus, GB3ANG, 144·975MHz, and northern Ireland, GB3GI, 144·137MHz, to Wrotham, Kent, 144·150MHz. Having decided, from the number of UK beacons heard, the extent and predominant direction of the prevailing lift, it is worth looking for the continental beacons such as; DL0PR, 144·910MHz, EA3URE, 144·042MHz, FX3THF, 144·905MHz, LA1VHF, 144·860MHz, OH6VHF, 144·900MHz, OK0EB, 144·970MHz, ON4VHF, 145·990, OZ7IGY, 144·930MHz, PA0JTA, 144·148MHz, SK4MPI, 144·960MHz, SP2VHF, 144·980MHz, and YU1VHF, 145·990 to name a few. A beacon's signal is a continuous note, frequently interrupted with its call-sign.

Another good propagation indicator is the 2m repeater network, using f.m., which now provides considerable coverage of the UK and is rapidly spreading through Europe. Each repeater shares a carefully planned channel numbered from R0 through R9, covering a series of input frequencies from 145·000MHz, in 25kHz steps, to 145·225MHz. The range of output frequencies, also in 25kHz steps, is 600kHz higher, from 145·600 to 145·825MHz. In addition to handling the amateur radio traffic, these unmanned, automatic duplex transceivers periodically identify themselves by transmitting their official call-signs.

At some time during a tropospheric opening, continental f.m. broadcast stations will be heard in Band II, often stronger than the "local" BBC stations, and Band III television will suffer from co-channel interference.

Space enthusiasts can use the AMSAT-OSCAR 7 satellite which has two repeaters (transponders) aboard, 2m to 10m and 70cm to 2m. Signals received by the satellite between 145·85 and 145·95MHz are re-radiated between 29·4 and 29·5MHz and signals going in between 432·125 and 432·175MHz come out, inverted, between 145·975 and 145·925MHz. The satellite's telemetry beacon can be heard on 145·980MHz.

Every year, the RSGB, in conjunction with the IARU, arrange a number of contests, on 4m and 2m, for licensed amateurs and SWLs. These events are interesting because they are well supported by individual and group entries operating from their home QTH, or from portable or mobile locations. Should a contest coincide with an atmospheric disturbance then there is plenty of DX about.

Sections of the 2m band are used for Slow Scan TV, RTTY, the Radio Amateurs Emergency Network (Raynet), and scientifically, for moon-bounce experiments, meteor scatter and the study of auroral propagation.

I suggest that readers who are interested in v.h.f. should obtain a copy of the RSGB *VHF/UHF Manual* and talk to the v.h.f. operators in their local radio club.

## BROADCAST BANDS

### SHORT WAVE BROADCASTS

by Charles Molloy G8BUS

Harmonics, though familiar enough to the radio amateur, may well be an unknown phenomenon to the broadcast band DXer. A harmonic in this context is a spurious transmission on twice or three times the frequency of a broadcasting station. The basic frequency is called the fundamental, twice that frequency is the second harmonic, three times the frequency is the third harmonic and so on. Harmonics occur naturally inside a radio transmitter but great efforts are made to suppress them so that they do not reach the aerial and radiate. High power transmitters are now commonplace and when connected to a directional array the effective radiated power (e.r.p.) may easily be in megawatts. Under these circumstances it is easy for a few watts of the second or third harmonic to be radiated along with the fundamental. Normally, this is not a problem as the s.w. broadcaster ought to be transmitting near to the maximum usable frequency (m.u.f.) to obtain optimum results. Harmonics would then be above the critical frequency and will penetrate the ionosphere and not come back to the earth.

Now that the higher frequencies are opening up again after the recent sunspot minimum, reception of harmonics should occur more often. Radio amateurs make world-wide contact on 10 metres using only a few watts, and reception of harmonics in the range 23 to 30MHz should occur over a similar range. Harmonic DXing is the broadcast band DXer's equivalent of QRP (low power) and as such has a challenge and fascination all its own. One snag though. Be sure you are listening to a genuine harmonic and not to a spurious signal generated within your receiver. A check for the fundamental or a check of conditions on 10 metres is a help.

From Guernsey in the Channel Islands comes a letter from George Le Couteur who heard Radio Moscow when he was tuning through the 10m band. The exact frequency was 28·350MHz which is three times 9·450 in the 31m band and sure enough he "found them putting out their usual huge signal on the frequency". The second harmonic is 18·900 and George found them on this out-of-band frequency as well. Other DX heard, on fundamental this time, is Radio New Zealand regularly around 0830 on 11820kHz, faint but clear of QRM.



# WITH UNIT THREE WE INTRODUCE OUR

Stirling Sound

# Audio Plan®

## MONEY SAVING, VERSATILE

with a new module every constructor  
is going to welcome

Audio Plan lets you build it your way! Using the vast experience gained from selling direct to thousands of constructors, we have put together from our streamlined range of constructor modules the three hi-fi assemblies most wanted for power, performance and price (see below). Each features our unique Unit Three stereo push-button selector/filter module for ceramic p.u., mag. p.u., radio, tape record/replay and high cut and low cut filters. Connections are via three 5-pin Din sockets mounted at rear. **UNLIKE ANY OTHER MODULES, YOU CAN EXTEND OR SHORTEN UNIT 3 TO MAKE IT FIT ANY CABINET SIZE BY SIMPLY CUTTING ACROSS THE P.C.B. AND POSITIONING TWO SECTIONS AS REQUIRED.** These are then connected to each other again. Simple! Sensible! and so very useful to anyone wanting his assembly to have that extra professional appearance. Note—Unit 3 may also be used with other than Stirling Sound modules if you aren't changing to Audio Plan just yet.

It's  
"telescopic"!

Audio Plan Unit Three stereo push-button selector/filter unit with front panel facets. Size: 240 x 105mm.

£6.75

POST FREE & INC TAX

### POWER AMPLIFIERS

Outputs quoted in watts R.M.S. into 4 ohms  $\pm 10\%$ . Figures in brackets indicate the appropriate Stirling Sound power supply. For full range, see our new catalogue.

### UNIT TWO PRE-AMP AND CONTROL UNIT

Provides treble cut/boost  $\pm 15$  dB at 10kHz; bass  $\pm 15$  dB at 30Hz; volume control; stereo balance control. Input sensitivity 1-5 mV. R.I.A.A. compensated. S/N ratio 75dB for 5mV in. Output 200 mV to 1 volt according to input voltage. Black front panel, white titles. 220 x 80 x 50mm. Supply voltage 10-16 V.D.C.

£12.43 POST FREE & inc. V.A.T.

SS.103	1.C. amp. 3 watts R.M.S. (SS.318)	£2.85
SS.103-3	Stereo version of above 2 I.C.s	£5.00
SS.105	5 watts R.M.S. into 3 $\Omega$ (Car Batt.)	£3.95
SS.110	10 watts R.M.S. 3 $\frac{1}{2}$ " x 2" x 1" (SS.324)	£4.85
SS.120	20 watts R.M.S. (SS.334)	£9.00
SS.140	40 watts R.M.S. Distortion typically 0-1%. 5" x 3 $\frac{1}{2}$ " x 1 $\frac{1}{2}$ " (SS.345)	£8.50
SS.160	64 watts R.M.S. Distortion typically 0-1%. 5" x 3 $\frac{1}{2}$ " x 1 $\frac{1}{2}$ " (SS.360)	£8.50
SS.1100	100 watts R.M.S. Distortion at half-power, typically 0-1%. 5" x 3 $\frac{1}{2}$ " x 1 $\frac{1}{2}$ " (SS.360)	£10.50
HS.100	Heatink for SS.140 or SS.160	75p
HS.1100	Ditto for SS.1100	£1.50

Power Units have low volt. D.C. take-off point.

ASSEMBLY	POWER AMPS.	CONTROL	SELECTOR	POWER SUPPLY	PRICE POST FREE & inc. V.A.T.
AUDIO PLAN A	2 x 60 W. r.m.s.	Unit 2	Unit 3	60V	£49.95
AUDIO PLAN B	2 x 40 W. r.m.s.	Unit 2	Unit 3	45V	£44.95
AUDIO PLAN C	2 x 20 W. r.m.s.	Unit 2	Unit 3	34V	£38.95

## \* THE STIRLING SOUND DISCO/PA PROGRAMME

Modular D.I.Y. assemblies for great economy: Control/Mixer Consoles; Sound-light Units including the cable-free Spectra-sonic; Mixers; Amps; Speakers; 'Ampower' amplified speakers, etc. Mention 'Disco' when sending for new catalogue as below.

ALL PRICES INC. V.A.T. & POST FREE ★ ACCESS OR BARCLAYCARD—JUST GIVE YOUR NUMBER

**Stirling**  
Sound

**TO ORDER** Cash (cheque/money order) with order or your Access/Barclaycard No. Goods (except heavy discs) post free in U.K. All prices incl. V.A.T. Prices subject to alteration without prior notice.

**New Stirling Sound Catalogue**

**READY NOW** with full product ranges, prices, technical information, etc. Send 20p in stamps for your copy by return.

Dept. PW6,  
37 VANGUARD WAY, SHOEBURYNNESS, ESSEX  
Tel: (03708) 5543

SHOP AND SHOWROOM

220-224 West Road, Westcliff-on-Sea. Telephone: Southend (0702) 351048.

TO STIRLING SOUND, 37 VANGUARD WAY, SHOEBURYNNESS, ESSEX

PLEASE SEND .....

..... (or as list attached) & CATALOGUE for

which I enclose £..... + 20p for Post.

Name.....

Address .....

..... PW.6

**Harold Brodribb**, St Leonards-on-Sea has also picked up harmonics of Radio Moscow, on 23·920MHz (2×11960), 24·110 (2×12055) on 29·1 (?) and 29·8 (?). Harold is now using a home-made converter with his CR100 which gives very much better results in the range 25-30MHz and he reports increased activity in the 11m broadcast band (25605 to 26095kHz) with reception of Tel Aviv on 25605 at midday and of the Voice of America (location unknown) on 26000kHz at 1800.

Short-wave crystal sets are in the news again with a report from **Rod Hunt** of Darlington who pulled in Radio Canada, Finland, Norway, Sweden, Austria and a number of others, using a home-brew crystal set and a 50ft outdoor aerial. Rod says that one definitely needs patience and persistence and it is only a matter of time until Australia is caught!

Radio Australia has attracted the attention of **George Norris** of Stowmarket (FRG7 and Windom Antenna) who says that propagation on this path at the moment seems to favour the morning between 0700 and 1000. "Try 11740kHz (25m) first and then 21680 and 21570 (13m). The former seems to hold up well most of the day with QRM at times". **William Stevenson** (Manchester) has a Vega 206 which he uses with a folded dipole in the loft for the 19m band and a 45ft Zepp with a.t.u. for the rest of the bands. His log included Radio Australia on 11705kHz at 1500 SIO 434. Fifteen-year-old **Robert Pound** of Cambourne in Cornwall is a regular listener to Radio Australia on 11740 but has been trying without success on 4920 for the 10kW VLM4 which relays the Domestic s.w. Service between 1930 and 1400. Has anyone logged this station? Robert, who uses an ex-WD receiver (type unknown) and an end-fed aerial situated in the loft, has been trying to pick up Radio Kaduna, Nigeria on 3396kHz in order to hear the talking drum interval signal. The NBC international service is also using this interval signal. **Chris Howles** of Lichfield (Vega 206 and 50ft long wire) reports hearing Lagos signing on at 1800 on 15120kHz in the 19m band and according to the *World Radio and TV Handbook* the interval signal precedes signing-on.

to listen to it until 0400. Subsequent night listening between 0100 and 0330 produced WHN New York on 1050, CHUM Toronto 1050, CFRB Toronto 1010, CHNS Halifax 960, CJYQ St John's 930, WCAU Philadelphia 1210, WOWO Fort Wayne Indiana 1190, CJCH Halifax 920. Mike now intends to obtain one of the new Yaesu Musen digital receivers and he also plans to construct a loop. A number of points arise out of Mike's letter.

Reception of North American m.w. stations is not limited to the winter. DXing is possible throughout the year. All that is required is a path of darkness between transmitter and receiver and this occurs some five hours after local sunset in the UK. Even on the longest day, sunrise occurs seven hours after sunset at this QTH though this period may vary according to location in the UK. At my QTH this means about 1½ hours DXing of NA before dawn on June 21st and much longer periods during April, May, July and August. Only stations on the eastern seaboard of North America will be heard in June but on the other hand European QRM is light as Central and Eastern Europe will be in daylight. DXing North America in summer can be rewarding. I once logged the 40 watt relay at Glovertown in Newfoundland on 1090kHz during the month of July.

Mike noticed that fade-outs lasting for periods of several days are common on the North American path and he wonders if there is any set pattern for good reception. Fade-outs do recur sometimes after 28 days, which is the period that a disturbance or spot on the surface of the sun takes to rotate and face the earth again—that is if it lasts that long. Reception is often at its best just before a fade-out so it might be possible to predict such a peak. Matters are not so simple, though, as the ionosphere is a complex medium and long range propagation on the medium waves has not been studied to any degree. After all the band is intended for local broadcasting! In any event the medium waves are never dead, there is always some DX to be heard. If North America cannot be heard at all then South America will be at its best. If you hear an American voice during a fadeout then listen carefully for it may be something special such as Puerto Rico or perhaps the American Virgin Islands. I shall give up medium wave DXing if it ever becomes possible to predict what can be heard as most of the fun will then have disappeared.

Finally, Mike offers a tip to QSL hunters. International Reply Coupons cost 25p in the UK but stamp dealers can supply unused postage stamps for most foreign countries. These are more convenient for the recipient to use and, a lot cheaper to buy (for Canada in Mike's experience). A very good idea if you know what value of stamps to obtain for a return letter.

Central and South America are often heard well during the summer. **D. R. Mayhew** (Littlehampton), who uses a Philips receiver and the PW 40in loop reports hearing Radio Managua, Nicaragua on 620kHz, La Voz de Mexico on 730, Radio Cadena el Salvador on 760, 'ROK 80' in Juarez Mexico on 800, Radio Sutatenza Colombia 810 and Radio la Versatil El Salvador on 1300kHz. More Latin American DX is reported by **Steve Whitt** (Cambridge) who used an Eddystone 940 with a 2ft square loop and the PW balanced amplifier to pull in Radio Margarita 1020 and Radio Coro 1210, both in Venezuela. "It was very interesting to receive my first South American DX, I don't know how I missed it before," writes Steve. It is very easy to pass over Latin Americans, especially during a North American fade-out, and class

## BROADCAST BANDS

### MEDIUM WAVE DX

by **Charles Molloy G8BUS**

A long interesting letter, just bursting with enthusiasm from **Mike Kuske** of Folkestone describes how he heard his first North American m.w. station. His National Panasonic GX600M had been purchased for short wave listening but after reading PW he decided to try the medium waves for, although interested in North American domestic radio, he never thought it could be heard in the UK. With 100ft of wire wound around the loft for an aerial he pulled in WINS in New York City on 1010kHz at 0045 and he continued



# HERE IS THE NEWS.....

One of the major problems confronting today's electronics designer/enthusiast is the incessant stream of new types of ICs and components. So, where radio is concerned, our new catalogue is a revelation to the circuit user. The new Ambit catalogue contains all that is new and worthwhile, plus feature articles describing applications work, providing ideas and suggestions - and some radio theory basics - like tuned circuits and impedance matching - that cut through the flannel to give you essential practical details to help you with your own design work. We also invite customers/readers to submit their own features for our radio magazine supplement on modern RF circuitry and techniques.

Featured in our catalogue/magazine supplement:

- CA3189E** The new RCA FM IF system described in detail, with an 'ultimate hi-fi' application in our reference series FM IF unit based on linear phase filters
- ULN2204/ TDA1803** The new AM/FM/Audio combination IC that has revolutionized portable radio design. 2 to 12v voltage range 10-14mA total standby.
- TDA1082** LF/HF/VHF oscillator, balanced mixer, RF stage and pin diode age drive - a versatile RF processing device that deserves a much wider audience.
- HA11219** Impulse noise blanker for mobile and fixed radio/audio. It can even 'clean' noisy signal otherwise inaudible! Destined for a big future.
- TDA1220** SGS' entry into the AM/FM radio IC battle with a promising approach that separates AM and FM functions into separate blocks
- CFM2/LFY MA1023** The worlds smallest ceramic ladder and mechanical filters from TOKO Switched 12/24 hour 0.77" LED display alarm clock module with no RF!
- The chances are that our catalogue will be the first place many of you will see these new products. Backed with our extensive R&D, we aim to provide a regular summary of new products in the radio and associated fields of electronics - and we invite all submissions for consideration.
- In the theory section this issue:
- Tuned circuit impedances and matching - tracking and bandwidth - a novel approach to 100kHz to 30MHz continuously tuned radio - and the discriminating metal locator, save your money before you buy one, and see how they're made!
- In a world of electronics that constantly expands and diversifies into an increasing number of specialities, we offer you a refuge where we stick to one main theme, and keep you informed to a standard not possible in publications without direct every-day involvement in project research, development and evaluation.

Much of the satisfaction in our new approach to specialized features, is the fact that you will also be able to obtain all the necessary parts for your circuit from us, at prices that are so competitive that we've been number one in coils/filters since we started trading:


TOKO coils and filters:	Radio IC's	Power regs	Ferrite rods:
A bigger than ever range of IFs for 455-470kHz, 9.0-11 MHz in 7mm & 10mm square styles. Now including TV video and sound IFs from 30-33p.	CA3189E 2.75	723CN 0.80	14x9.5cm 0.30
Coils for Shortwave, coils for VHF, coils for LW/MW - with 800,000 in stock!	NA1137W 2.20	NE550B 0.80	18x9.5 0.38
MF1455 2.4kHz SSB filter 9.95	TBA1205 1.00	TAAS60 0.50	17.5x9.5 0.39
CFM2 miniature mechanical filter 0.65	uA720 1.40	L200 1.95	20x9.6 0.51
LFY455 Alignment ladder filter 1.25	TBA651 1.81	PLL & misc	mw coil 0.27
CFSE107 ceramic FM IF filter 0.50	HA11917 1.40	8638CC 4.50	LW coil 0.20
BRF3132A 6pole linear phase FM 2.25	MC1350P 1.20	NE555V 0.55	coupling 0.30
BRF3125 4pole linear phase FM 1.30	MC1330 1.35	NE568V 2.50	clips 0.05
BLF3107N 18/58kHz stereo filter 1.90	uA753 1.80	NE568 3.50	fx1115 0.12
Ratio discriminators for 12.7MHz 0.65	MC1496 1.25	NE562B 3.50	H balun 0.25
Ratio discriminators for 455-470kHz 1.35	TDA1082 1.95	NE565K 2.50	Trimmer Cs
<b>NOTE:</b> We have the most unique stock of RF signal coils/chokes in the world - and offer a full custom part service for "specials"	TDA1083 1.95	11C90 14.00	1.5-6pF 0.18
<b>TOKO chokes:</b>	ULN2204 1.05	SP8629 4.20	1.5-10 0.18
Stock values from 1uH to 120mH in three types:	TDA1220 1.75	Vericap diodes	2-22 0.19
7Ba 1-1000uH: 18p one-off	TDA1090 3.35	PIH diodes etc	2 1310ml 0.37
8RB 100uH - 33mH: 18p one-off	<b>Decoders for MPX</b>	BA102 0.30	5-6-60 0.24
10RB 4.7 - 120mH: 33p one off	MC1310P 2.20	BA121 0.32	5-30cer. 0.18
Also tuneable high value inductors, with over 50% adjustment ranges from nom. values.	CA3090AC 3.75	IT7210 0.30	7.36cer. 0.19
<b>TOKO tunerheads:</b>	HA1196 4.35	BB105B 0.40	<b>MODUL. ES....</b>
EF6800 Rensco vericap/Mosfet 12.95	KB4400 2.20	BB104B 0.45	12oz/24 hrs 45 +
EC3302 'premium' tet/vericap 7.50	<b>Audio</b>	MVA42 1.48	transfo. 1.60"
AT/NT3302 Combined tuner/am prog. 8.25	LM380N 1.00	NV8m115 1.05	MA1023
Reference series tuner modules for FM	LM381N 1.81	NV8m125 1.05	7" display
As well as all those previously advertised....	2P93 1.00	BA479 0.35	vnt alarm etc
EF6853 3 MOSFET very high gain low noise	TBA810AS 1.08	1d1061 0.95	BA182 0.21
BB 108 6 stage vericap tuner with	TCA940E 1.80	OA91 0.08	12/24hr 11 26"
amplified/buffered oscillator output	TDA2002 1.75	<b>Resistors/Caps</b>	transfo 1.65"
Spectrum analyzer aligned 19.75	TDA2020 2.99	A new range in	an/fm tuner
7130 3x8pole IF filters, 2 AGC MOSFET	<b>Op amps</b>	our cat/pice	modules as
IF preamps, CA3189E All tuner	LM301N 0.39	list	previously adv.
functions etc. mtrs, meters etc.	uA741 0.34	<b>Misc</b>	EF5400 9.75
Spectrum analyzer aligned 16.25	CA3130 0.85	Min edge with	EF5801 17.45
91195B MPX decoder+2w af monitor 18.45	LM3900N 0.68	variety of scales	7020 6.95
	<b>Power regulators:</b>	illum. 2.50"	7030 10.95
	7805UC 1.55	30x50 std face	complete kits
	TDA1412 0.95	with variety of	for tuners/af,
	7815UC 1.55	scales 2.75	metal locators
	78M20 1.20	Amazing value	see price list
	78M24 1.20	40x55 face illum	or new cat.
		series 3.75	

# AMBIT INTERNATIONAL

2 Gresham Road, Brentwood, Essex. CM14 4HN

CWD please  
PP 25p  
VAT extra  
\*8%  
phone 02771  
216029

## Why use half a system?

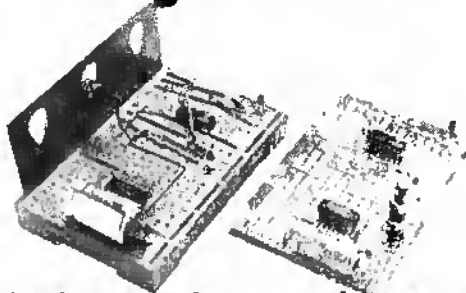

When for the same price you can have a complete system

PB Breadboards and Blob-Boards are the only Bread board system in the world which enable you to

Design, Test Develop, Prove the Circuit working and produce a professional printed circuit board.

- |         |                                       |       |
|---------|---------------------------------------|-------|
| S-DeC   | matching Blob-Board + Project Booklet | £3.50 |
| T-DeC   | matching IC Blob-Board + Project Book | £4.50 |
| U-DeC A | matching IC Blob-Board + Project Book | £4.65 |
| U-DeC B | matching IC Blob-Board + Project Book | £8.99 |




DeC-IT and Blob-IT  
P.B. Electronics (Scotland) Ltd.,  
9 Radwinter Road,  
Saffron Walden, Essex CB11 3HU
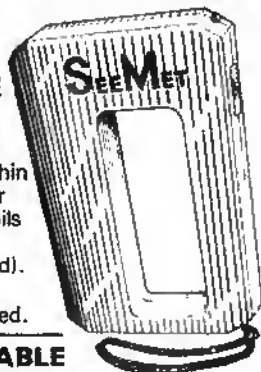
## AT LAST! AVAILABLE IN KIT FORM SEEMET

THE FAMOUS POCKETSIZE METAL DETECTOR

Seemet readily detects concealed ferrous and non-ferrous metals within range of its detector field. Ideal for finding concealed pipes, wires, nails etc. One-handed operation, uses standard PP3 Battery (not supplied). **ONLY £3.25 plus p. & p. 25p.** (inc. VAT), full instructions supplied.



## UNBEATABLE DIMMER OFFER

from Britain's largest Dimmer Makers.

Complete Kit of Parts for our VCL 500M, 500W Dimmer Switch. **Only £2.00, plus p. & p. 25p.** (inc. VAT) full instructions supplied.

Send coupon below with your remittance.

Please supply: — **PW2** NAME \_\_\_\_\_  
 SEEMET KITS at £3.50 incl. of p. & p. ADDRESS \_\_\_\_\_  
 DIMMER KITS at £2.25 inc. of p. & p. \_\_\_\_\_

I enclose cheque/P.O. POSTCODE \_\_\_\_\_  
 for £ \_\_\_\_\_ BLOCK CAPS PLEASE

## Fotherby, Willis Electronics Ltd.

GLADSTONE TERRACE, STANNINGLEY, LEEDS, LS28 6NE.  
Telephone: Leeds (STD 0532) 563373 Telex 557111

GLYNWED



# PW READERS PCB SERVICE

## To:- READERS PCB SERVICES LTD, PO BOX 11, WORKSOP, NOTTS

Please supply PCB's as indicated by tick/s in box/es.....

Issue	Project	Ref	Price P/P	
Dec 75	Sound-To-Light Display	DN0798	1-15+12	<input type="checkbox"/>
Dec 75	Disco System, Amp. (2 req'd) each	AM0421	4-40+22	<input type="checkbox"/>
Dec 75	Disco System, Light Modulator	AM0423	3-50+22	<input type="checkbox"/>
Mar 76	CMOS Crystal Calibrator	AM0438	1-18+12	<input type="checkbox"/>
July 76	Disco Preamplifier	A003	0-85+12	<input type="checkbox"/>
Aug 76	Cassette Player Power Supply	A001	0-85+12	<input type="checkbox"/>
Oct 76	Digital Car Clock (set)	A011/012/013	2-58+12	<input type="checkbox"/>
Oct 76	Interwipe	DN8JM	0-80+12	<input type="checkbox"/>
Oct 76	Video-Writer (set)	D002/3/4/6 A007	21-44+50	<input type="checkbox"/>
Nov 76	Cirtest Probe	A018	0-48+12	<input type="checkbox"/>
Nov 76	Burglar Alarm	A019	0-50+12	<input type="checkbox"/>
Dec 76	Chromachase	A021	5-70+22	<input type="checkbox"/>
Jan 77	Oscilloscope Calibrator	A023	1-25+12	<input type="checkbox"/>
Apr 77	Gas/Smoke Sensor Alarm	A028	0-85+12	<input type="checkbox"/>
May 77	2-Way Intercom	D019	1-28+12	<input type="checkbox"/>
May 77	Protected Battery Charger	A027	2-38+12	<input type="checkbox"/>
May 77	Seekit Metal Locator	A031	3-38+12	<input type="checkbox"/>
June 77	Reverberation Amplifier	A032	2-38+12	<input type="checkbox"/>
June 77	Versatile AF Generator	A033	2-38+12	<input type="checkbox"/>
June 77	Tele-Games	D029	3-22+18	<input type="checkbox"/>
July 77	20W IC Amplifier	A034	1-38+12	<input type="checkbox"/>
July 77	Radio 2 Tuner	A035	1-88+12	<input type="checkbox"/>
July 77	Digital Clock Timer	A036	3-28+12	<input type="checkbox"/>
Aug 77	Shoot (Telegames)	D035	1-55+15	<input type="checkbox"/>
Aug 77	Atomic Time Receiver	D036	2-65+15	<input type="checkbox"/>
Aug 77	Morse Code Tutor Cards (SRBP)	A037	4-75+15	<input type="checkbox"/>
Sept 77	Jubilee Electronic Organ	A038	19-00+75	<input type="checkbox"/>
Sept 77	Electronic Car Voltage Regulator	D037	1-25+12	<input type="checkbox"/>
Oct 77	Audio Level Indicator	D039	0-98+12	<input type="checkbox"/>
Oct 77	Sine-Square Wave Generator	D040	2-35+15	<input type="checkbox"/>
Nov 77	Laboratory Power Supply	A039	3-50+12	<input type="checkbox"/>
Jan 78	Direct Conversion Receiver	D043	1-85+15	<input type="checkbox"/>
Jan 78	Proportional Power Controller	DN9JM	0-78+12	<input type="checkbox"/>
Mar 78	Audio/Visual Logic Probe	R001	1-40+15	<input type="checkbox"/>
Apr 78	Europa Stereo Amplifier	R002	9-55+45	<input type="checkbox"/>
May 78	DX'ers Audio Filter	D001	2-35+15	<input type="checkbox"/>
June 78	Bovington Tank Game	R006	3-80+20	<input type="checkbox"/>
June 78	Audio Distortion Meter (set)	R007/8/9/10	6-75+25	<input type="checkbox"/>
June 78	Darkroom Timer	R011	1-55+15	<input type="checkbox"/>

Post and packing is for one board or set of boards. Prices include VAT. Remittances with overseas orders must be sufficient to cover despatch by sea or air mail as required.

I enclose Postal Order/Cheque ACCESS welcome.  
Send card number only.

No.....

for £..... made payable to READERS PCB SERVICES LTD

NAME .....

ADDRESS .....

Post Code.....

Any correspondence concerning this service must be addressed to READERS PCB SERVICES and not to the Editorial offices.

them, as one newcomer to this column did, as unidentified Spaniards. At this time of year listen for Latin Americans after midnight, the peak occurring just before sunrise. There are very strong signals to be heard at times.

Steve asks what type of equipment is in use at my QTH. The main receiver is a GEC BRT400, a valved communications type that was designed some 25 years ago for broadcast band monitoring. Also in service is an Eddystone EC10 which is very useful as a second receiver if it is necessary to check two channels. A 90ft long wire with a.t.u., a 40in loop, crystal calibrator, audio notch filter, portable tape recorder and a home-made switching unit to switch aerials and calibrator, completes the set-up.


Another DXer who continues to use valved equipment is J. Gaines of Surbiton who has a Marconi CR100/8 which is giving splendid service. I used a CR100 for m.w. DXing for a number of years and it is a really first-class receiver on this band, though its performance on the short waves leaves a lot to be desired. One "mod" carried out by J. Gaines was to split the r.f. and i.f. gain controls.

This is a feature of the BRT400 that appeals to me as the r.f. gain control on many receivers controls both r.f. and i.f. gain at the same time. With the BRT400 the two are separate and there is an advantage to be gained at times by adjusting them separately. Overloading and cross-modulation occur at, or before the mixer and it is often necessary to reduce r.f. gain to eliminate this, with of course a reduction in i.f. gain as well when a common control is in use. It is in the mixer stage that the bulk of receiver noise is generated and in order to obtain a good signal-to-noise ratio, the r.f. gain should be as great as possible. Backing off the i.f. gain is the way to follow signal strength in this case, especially with the a.g.c. switched off, which should be normal practice when DXing on the medium waves. I set the r.f. gain as high as it will go without giving trouble and then I control signal strength with the i.f. gain control.

A good substitute for an r.f. gain control, if none is fitted, is an external attenuator. The simplest is a potentiometer of about 1000 ohms. The lead from the aerial goes to the central tag. One of the outer tags goes to the receiver aerial socket and the other outer tag goes to the receiver earth socket. Overloading and cross-modulation can be controlled very easily by this method.

From Farum in Denmark comes a letter from Mick Evans who describes himself as a London guy who has gone to live and work in Denmark. Mike says that PW is very expensive in DK land, working out at well over £1 a copy. Why not take out an annual subscription? This service has recently been re-introduced at £10-60 per annum to any UK or overseas address. Mike's main trouble though is a buzz spread over a portion of the medium wave band and he asks if a mains filter would help. If the buzz is being radiated by the house wiring, as seems the case, then it would be necessary to filter the whole mains supply to the house. Contact the Danish Shortwave Club International, Greve Strandvej 144, DK2670 Greve Strand, Denmark, who should know the correct body to complain to. The DSWCI incidentally, is international, it publishes a bulletin in English called Short Wave News, which contains a medium wave section, in spite of the name. Enquiries in the UK should go to Noel Green, together with a stamped addressed envelope. Noel's address is 14 Marsden Road, Blackpool FY4 3BZ.

**HF 7948 FRONT END**

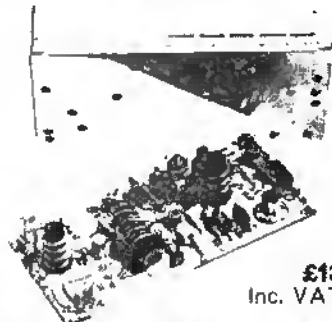

**£13.12**  
Inc. VAT, P&P


**TECHNICAL CHARACTERISTICS:**  
Output terminal for digital frequency meter;  
Antenna impedance—75 to 300 Ohms;  
Frequency ranges 87.5 to 104MHz or to 108MHz; Sensitivity—0.9uV 26dB signal to noise ratio  $\pm$ 75kHz deviation; Intermodulation 80dB Image rejection—60dB; Tuning voltage—1V to 11V; Total gain—33dB; Intermediate frequency—10.7MHz; Power supply voltage +15V; Power consumption 15mA; Dimensions 104 x 50mm.

**TECHNOLOGY:**

Double sided epoxy printed circuit board with plated through holes; Dual gate effect transistors; Silvered coils.

**FI 2846**

**IF AMP AND DECODER**

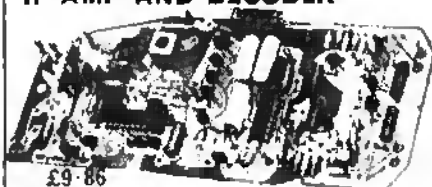

**£9.86**  
Inc. VAT, P&P

**TECHNICAL CHARACTERISTICS:**  
Intermediate frequency—10.7MHz; IF Bandwidth—280kHz; Signal to noise ratio—70dB with 1mV input; Distortion—mono 0.1%, stereo 0.3%; Sensitivity—30uV up to the 3dB limit; Channel separation—40dB at 1kHz; Pass band—20 to 15,000Hz; Rejection at 38kHz greater than 55dB; Am rejection—45dB; De-emphasis—50 to 75uS. Pilot capture at 19kHz +4%; Channel matching within less than 0.3dB; Output impedance—100 Ohms; Output voltage—500mV; Phase locked loop stereo decoder; Output for LED VU-meter; Null indicator; Outputs for AGC, AFC and inter-station muting; Consumption—55mA LEDs extinguished, 100mA LEDs illuminated; Power supply—15V; Dimensions 195 x 76mm.

**CIRCUIT TECHNOLOGY:**

Epoxy printed circuit board. Monolithic integrated circuits, ceramic filter.

**ALS 1500**

**STABILISED POWER SUPPLY**



**£2.53**  
Inc. VAT, P&P

**TECHNICAL CHARACTERISTICS:**


Output voltage—15V; Max. output current—500mA; Thermal coefficient less than 1mV/C; 15V power supply for modules HF 7948 and FI 2846; Supply protected against short circuit (power and current protection); Dimensions—65 x 55mm.

**TECHNOLOGY:**


Double sided epoxy circuit board; Monolithic integrated circuit.

**OPTOELECTRONIC OPTIONS**

**£8.06**  
Inc. VAT, P&P

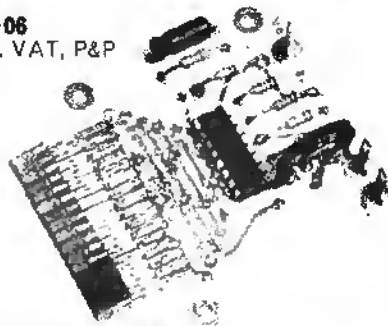


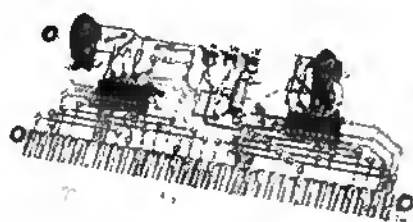**LED VU-METER**  
Station strength indicator



**£13.50**  
Inc. VAT, P&P


**ILLUMINATED POINTER**  
Station finder

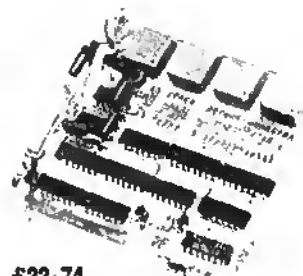


**£22.74**  
Inc. VAT, P&P

**FREQUENCY METER**  
Digital display of received station frequency

**£8.77**  
Inc. VAT, P&P

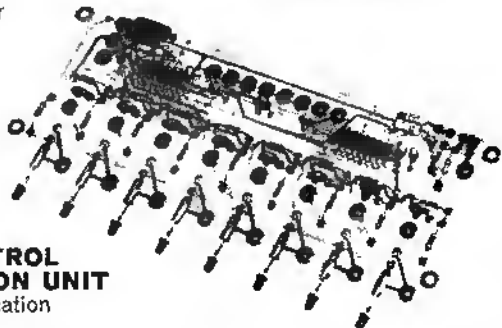

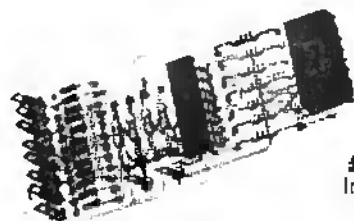**TOUCH CONTROL  
PRE-SELECTION UNIT**  
LED channel indication



**£4.35**  
Inc. VAT, P&P

**NUMERICAL DISPLAY**  
Pre-selected channel number

**CROSSLAND HOUSE · NACKINGTON · CANTERBURY · KENT**  
Telephone (0227) 63218 Telex 965780







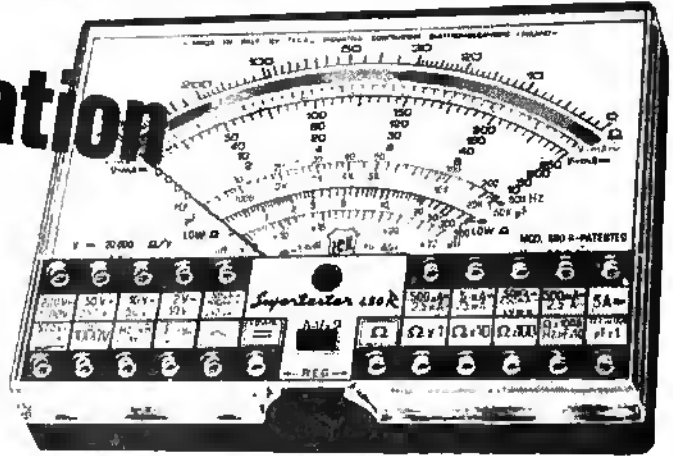
## I.C.E. MULTIMETERS

**TWICE the information  
in HALF the size**

The I.C.E. range of multimeters provide an unrivalled combination of maximum performance within minimum dimensions, at a truly low cost. Plus, a complete range of add-on accessories for more ranges, more functions.



### SuperTester 680R (illustrated)

- \* 20kΩ/V, ±1% fsd on d.c.
- 4kΩ/V, ±2% fsd on a.c.
- \* 80 Ranges – 10 Functions
- \* 140 × 105 × 55mm

**£25.25 + VAT**

(For Mail Order add 80p P&P)

### SuperTester 680G

- \* 20kΩ/V, ±2% fsd on d.c.
- 4kΩ/V, ±2% fsd on a.c.
- \* 48 Ranges – 10 Functions
- \* 109 × 113 × 37mm

**£19.95 + VAT**

(For Mail Order add 80p P&P)

### Microtest 80

- \* 20kΩ/V, ± 2% fsd on d.c.
- 4kΩ/V, ±2% fsd on a.c.
- \* 40 Ranges – 8 Functions
- \* Complete with case – only 93 × 95 × 23mm

**£14.95 + VAT**

(For Mail Order add 80p P&P)

All I.C.E. multimeters are supplied complete with unbreakable plastic carrying case, test leads, etc. and a 50-plus page, fully detailed and illustrated Operating and Maintenance Manual.

Now available from selected stockists. Write or phone for list, or for details of direct mail-order service.



Electronic Brokers Ltd.  
49-53 Pancras Road, London NW1 2QB  
Tel: 01-837 7781



**DELTA**

**ALARM:** Auto Brightness, Pulsed Tone, 9 min snooze

Electronics only kit: Non Alarm **£10.00** Alarm **£13.00**  
Complete with case: Non Alarm **£13.00** Alarm **£16.00**  
Ready Built Tested Working: add **£ 1.00**

**Timer Facility:** Display Seconds Stopwatch use, Sleep Delay: 50p extra  
**DISPLAYS:** 7 Red LED FND500 **£1.20** each, 8 for **£6.48**, NSB5430 1/2" red LED. Stick of 4 **£4.32**, 5LTO2 stick of 4 Green **£5.40**.

**CLOCK CHIPS:** MK50253 Alarm 12/24hr 4.6 digit **£5.40**, MM5385 **£4.32**, MK50362N calendar **£7.56**, 6 digit counter 50395/6/7 **£9.18**.

**MICRO PROCESSOR:** Z80 CPU **£21.60**, CTC & PIO **£15.12**, MK4096N 300ns 4KX1 0un RAM **£6.75**, 1702A UV PROM 450ns **£10.80**

**BATTERY RECHARGER:** Mains Adaptor with 4 way Plug, 4XAA (1.2v) Ni Cads plus holder **£8.64**, AA Ni Cads separately **£1.20**

**BARON(PW)**, 6 Gower Road, Royston, Herts. (0763) 43695.

Use Barclaycard or Access

### DIGITAL CLOCK KITS

... thousands sold

TEAK or PERSPEX cases

1/2" Red LEDs, 4 digit 12hr display PM indicator. Mains frequency accuracy Complete instructions. Power cut flasher. Real wood or Perspex: White, Black, Red Green, Blue. 6" x 2 1/2" x 3"

## Your career in Electronics?

Enrol in the BNR & E School and you'll have an entertaining and fascinating hobby. Stick with it and the opportunities and the big money await you, if qualified, in every field of Electronics today. We offer the finest home study training for all subjects in radio, television, etc., especially for the CITY AND GUILDS EXAMS (Technicians' Certificates); the Grad. Brit. I.E.R. Exam; the RADIO AMATEUR'S LICENCE; P.M.G. Certificates; the R.T.E.B. Servicing Certificates; etc. Also courses in Television; Transistors; Radar; Computers; Servo-mechanisms; Mathematics and Practical Transistor Radio course with equipment. We have OVER 20 YEARS' experience in teaching radio subjects and an unbroken record of exam successes. We are the only privately run British home study College specialising in electronics subjects only. Fullest details will be gladly sent without any obligation.

### PRACTICAL WIRELESS T.V. SOUND TUNER

(Nov. 78 article by A. C. Alnatie) Copy of original article supplied on request

- IF Sub-Assembly (G8) **£6.80**. P & P 75p.
- Mullard ELC1043 V'cap UHF Tuner **£4.50**. P & P 35p.
- 3-way Station Control Unit **£1.20**. P & P 25p.
- 6-way Station Control Unit (Special Offer) **£1.00**.
- Power Supply Prtd Circuit Board **£1.00**. P & P 30p.
- Res, Caps, Semiconds, etc. for above **£5.80**.
- Mains Transformer for above **£2.50**. P & P 30p.

Add 12 1/2% VAT to price of goods. P & P all items 85p.

Callers welcome at shop premises.

**MANOR SUPPLIES**

172 WEST END LANE, LONDON NW6

(Near W. Hampstead Tube Stn.) Tel. 01-794 8751

BRITISH NATIONAL RADIO & ELECTRONICS  
SCHOOL,

P.O. Box 156, Jersey, Channel Islands.

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

WD 6 \_\_\_\_\_ (Block caps please)

**WATCH BATTERIES 65p**  
Ray-O-Vac long life. Most types.

**DIY KIT 35p.**

(with battery order)

Case opening tool, fits most watches. Tweezers, Equiv. chart, Instructions.

**NEW FROM CASIO NEW**

**F-100 SPORTS WATCH**

Chronograph with up to 25 functions including net times, lap times and 1st & 2nd place times to 1/100 second. Water resistant (100ft) and shock resistant plastic case & strap.



**£19-95**

RRP £24-95

**52QS-14B**

Metal encased version of F-100 with stainless steel bracelet RRP £44-95.

**£34-95**



**31QR-16B**

This new watch is really well styled. 7 + 2 functions plus stopwatch from one second to 13 hours 7 45mm thick.

**£34-95**

RRP £44-95

**31QR-17B**

As above but 8-4mm.

**£29-95**

RRP £35-95.

**ALARM WATCH (illustrated above)**

At last they have arrived! Six digit display, Hrs, Mins, Secs plus Day or Hrs, Mins, Date plus Day. Month and date on demand. Loud 24 hour alarm with on/off indicator.

25CR-16B. Round faced watch. RRP £64-95.

**£49-95**

25CS-16B. Superbly styled square faced watch. Slim case. RRP £74-95.

**£59-95**

**29CS-11B**

**WORLD TIME**

Times and dates in ten world areas plus optional time. One touch summertime adjustment. Second display. ± 10 seconds/month. 15 months battery. 9-6mm thick.



**£59-95**

RRP £74-95.

Unless otherwise stated **CASIO** watches have a constant LCD display of hours, minutes, seconds, am/pm with day, date and month on demand. With night light, automatic 28, 30, 31 day calendar, mineral glass face and all stainless steel cases, they are water resistant to 100 feet. One battery lasts approximately 12 months. Accurate to less than ± 15 seconds/month



**IBICO 075**

Clock/calendar displays Hours, Minutes, Date and Day. STOPWATCH measures Net and Lap times from 1/10 second to 10 hours with rollover. Full access Memory. Percentage. ✓ 5000 hrs batteries. Leatherette wallet. (6mm x 64mm x 115mm)

**£23-50**

**CASIO**

AQ10M £19-95. BT-1 £21-95. MQ-2 £34-95.

**CASIO SCIENTIFICS**


Digital: FX31 £11-95. FX39 £15-95. FX144 £17-95. FX126 £19-95.

LCD: FX2200 £13-95. FX3004 £25-95. LC822 £10-95. LC78 £16-95.

Send 25p for our illustrated catalogue. Prices include VAT and P&P. Send cheque. P.O. or phone your credit card number to—

**TEMPUS** Dept PW  
15-21 Fitzroy Street  
Cambridge CB1 1EM  
Telephone (0223) 312346

**GOOD NEWS FOR DX-ERS!**

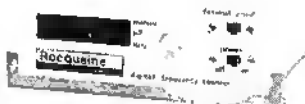

Now you really can afford a frequency Counter. We proudly announce our model RQ-3, a thoroughly reliable no-nonsense design, available to the home constructor in kit form. The RQ-3 is equally at home in the DX-er's shack, school science lab, or servicing workshop. It will display FREQUENCY, PERIOD, and WAVELENGTH. Coupled to the local oscillator of your Rx, it will accurately measure the receiver tuning.

**ABRIDGED SPECIFICATION**

- Operation up to 50MHz.
- Power requirement: 240V AC.
- Movable decimal point: 6 digit accuracy.
- Switch to select frequency, period, or wavelength.
- ± .001 % accuracy.
- High input impedance and sensitivity.

Send Now. Complete KIT £44-95 + 8% VAT.



Also available: Crystal Calibrator model RQ-1. A novel design which gives CW or amplitude modulated harmonics of 1MHz, 100 KHz, 10KHz. Kit at unbeatable price £12-72 + 8% VAT. Send for details—our aim is your complete satisfaction.

**ROCQUAINE ELECTRONICS,**  
Aldebaran, Le Coudre, St. Peters,  
GUERNSEY, CHANNEL ISLES.

**ETCH RESIST TRANSFER-KIT SIZE 1 : 1**

Complete kit 13 sheets 6in x 4 1/2 in £2-50 with all symbols for direct application to P.C. Board. Individual sheets 25p each. (1) Mixed symbols (2) Lines 0-05 (3) Pads (4) Fish plates and connectors (5) 4 lead and 3 lead pads (6) DILs (7) Bends 90° and 130° (8) B-10-12 T.O.S. cans (9) Edge connectors 0-15 (10) Edge connectors 0-1 (11) Lines 0-02 (12) Bends 0-02 (13) Quad in line

**CIRCUIT LAYOUT TRANSFERS SIZE 2 : 1**

One sheet 12 in x 9 in giving all transfers as in etch resist from No. 3 to No. 10 inclusive makes circuit layout easy. Black only. Price £1. Also lines and bends. Price £1.

**FRONT AND REAR PANEL TRANSFER SIGNS**

All standard symbols and wording. Over 250 symbols, signs and words. Also available in reverse for perspex etc. Choice of colours red, blue, black or white. Size of sheet 12 in x 9 in. Price £1.

**GRAPHIC TRANSFERS WITH SPACER ACCESSORIES**

Available also in reverse lettering. Colours red, blue, black or white. Each sheet 12 in x 9 in contains capitals, lower case and numerals. 1/2 in kit or 1/2 in £1 complete. State size required.

**ALL ORDERS DISPATCHED PROMPTLY. ALL POST AND VAT PAID.**

Ex. U.K. add 50p for air mail. Shop and trade enquiries welcome.

**E. R. NICHOLLS**  
P.C.B. Transfers Dept., PW,  
44 Lowfield Road, Stockport, Ches.  
061-480 2179

**WHAT'S NEW?**

**ME, semiconductor teaching kit**



The most MODERN, RAPID ECONOMIC way to master space age electronics. Starting even from ZERO by performing over

**100 EXPERIMENTS**

creating more than 20 practical applications

You learn all about the most up to date electronic circuits; how to calculate, repair, and design them, while pursuing your favourite hobby. Start from scratch, or improve your present knowledge, train and earn money in your spare time, turn your pastime into valuable job opportunities. Compare our prices: you receive the entire course, "mini laboratory" and components for LESS than the price of the components alone.

**COMPLETE KIT: nothing else to buy\***

**You get:**

- Instruction manual: over 200 pages of detailed step-by-step instructions. Start from scratch, explains basic laws and physics of Electricity, semiconductor principles and operation electronic circuits; form diodes (including diac, zener) transistors, triacs to integrated circuits (C.MOS, operational amplifiers) etc. . .
- Over 200 Electronic components: aerospace technology. Printed circuit experiment board, photo-transistor, triac, thyristor (C.S. transistors (including FET, MOSFET) LEDs plus resistors, capacitors, milliammeter, potentiometers, variable capacitor, etc. . . etc. . . etc. . .
- measuring instruments (you assemble yourself from among components furnished in kit)
- ELECTRONIC VOLTMETERS, LOW FREQUENCY MEASURING AMPLIFIER, LOGIC INDICATORS, REGULATED POWER SUPPLY, MULTIAMTHER.


**You perform:**

Over 100 different experiments: from the most basic voltage measurements to radio transmitter circuits and including HI FI, Flip Flops, IC applications, Triac use etc. . . etc. . . etc. . .

**You construct:**

More than 20 complete functional systems: light modulator, high fidelity amplifier, radio control set, radio receiver and transmitter, electronic gadgets and games and many, many more.

\*Hand tools not furnished.

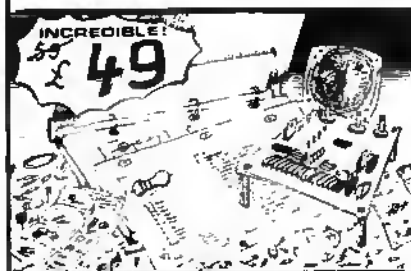

**SAVE £10 - mail coupon today - SAVE £10**

**saga** P.O. Box 401, Kingsmead, Kings Lane, Chipperfield, Nr. Kings Langley, Herts WD4 9PB.

Please send me — (QTY) [K2 KIT(S)]  
I enclose cheque (money order) for

£ \_\_\_\_\_

Name \_\_\_\_\_

Address \_\_\_\_\_

A.



**JONES SUPPLIES**

TTL				CMOS			
	P	P		P	P		P
7400	— 13	7447	— 30	4001	— 17	4047	— 95
7401	— 13	7451	— 16	4002	— 17	4048	— 48
7402	— 16	7470	— 30	4011	— 19	4050	— 53
7403	— 16	7472	— 28	4013	— 45	4070	— 53
7404	— 19	7473	— 30	4014	— 35	4502	— 95
7406	— 36	7474	— 30	4015	— 35	4508	— £2 90
7407	— 36	7475	— 40	4016	— 52	4510	— £1 51
7408	— 19	7476	— 35	4017	— 35	4511	— £1 75
7410	— 14	7486	— 35	4018	— 35	4514	— £2 05
7413	— 36	7479	— 35	4023	— 19	4518	— £1 80
7414	— 74	7493	— 35	4027	— 52	4518	— £1 20
7416	— 36	7496	— 32	4028	— 97	4528	— £1 20
7420	— 16	74107	— 32	4042	— 35	4536	— £5 00
7442	— 35	74141	— 70	4048	—		— £1 40

**BARREL KITS**  
**GUARANTEED 100% GOOD COMPONENTS**  
 99p Each Line.

15. TO3 NPN Silicon Power  
 5. TO-220 Plastic Power 6 Amp  
 20. Assorted Voltage 400mW Zeners  
 5. IM340T Voltage Regulators. Assorted Voltages  
 25. PNP/NPN TO18, TO92 Transistors  
 80. 400 PIV 500mA. Silicon Diodes  
 10. Low Noise 2N930.  
 2. 240V 12/0/12 100mA. Transformer plus PCB

**MISCELLANEOUS**  
 U2 size Ni CAD Batts. £2-65  
 8 pin 741 op. amp. .18  
 Scope Probs. x 1 x 10 £14-90  
 BNC Termination. 30p P & P  
 BNC 50 ohm Socket. .90  
 Signal Injector: AF/RF. £5-20  
 30p P & P  
 Multimeter 1,000 OPV £6-25  
 11 Ranges P & P 50p.  
 Telephone Pick-Up Coll .65  
 240V 12/0/12 1 amp £2-03  
 shrouded trans. 60p P & P  
 240V 15/0/15 1 amp £2-70  
 shrouded trans. 60p P & P  
 240V 30/0/30 1 amp £3-18  
 shrouded trans. 60p P & P  
 240V 30, 24, 20, 15, 12, 2 amp  
 unshrouded trans. £5-40  
 60p P & P.

Prices. Please Add 8% VAT. P & P. 10p. except where shown

## Jones Supplies

586 Ashton Road, Hathershaw, Oldham, Lancs. 01-652-9879.

## FANE NEW "POP" RANGE SPEAKERS

Improved appearance — higher sensitivity



	Rec. Price
12" 'POP' 40 Dual 45w Cone	£14-95
12" 'POP' 50H 50w	£16-99
12" 'POP' 75 75w	£22-95
15" 'POP' 65 70w	£25-95
15" 'POP' 80 80w	£29-95
18" 'POP' 100 100w	£49-95
18" 'POP' 150 150w	£55-00

**SPECIALIST RANGE**

	Rec. Price
12" DISCO/80 80w Fitted large Tweeter Cone	£29-95
12" DISCO/100 100w	£31-95
12" GUITAR/80L 80w For Lead Guitar	£27-95
12" GUITAR/80B " For Bass Guitar	£28-95
12" PA/80 80w Dual Cone. For general purpose P.A.	£27-95
15" BASS/85 85w For Bass Guitar	£39-95
15" BASS/100 100w	£42-00

Each designed to produce the individual sound requirement for its purpose. Robust Cast Aluminium Chassis.  
 ●Linen Cone surround

**HIGH FREQUENCY HORNS**

**J44** Range: 2-5KHz-15KHz Power: 50w with HPX2R Imp: 8 ohms Size approx 3 1/2" x 3 1/2" x 3" **£7-95**

**J73** Range: 2-5KHz-20KHz Power: 50w with HPX 1R Imp: 8 ohms Size approx: 7 1/2" x 3" x 6 1/2" **Rec Price £11-75**

**J104** Range: 2KHz-15KHz Power: 50watt with HPX1R 70 watt with HPX2R Imp: 8 ohms Size approx 10 1/2" x 3 1/2" x 7 1/2" **£16-95**

**920/2** Range: 1 KHz-18KHz Power: 100w with HPX1. Imp: 8 ohms Size approx 14" x 9" x 15" **Rec. £59-95**

**HIGH POWER "CROSS-OVERS"**  
 HPX1R (3-5KHz) **£3-25**  
 HPX2R (5KHz)  
 Impedance or total impedance of Bass Drivers not to exceed 8Ω. Otherwise use series Horns or attenuation provided with HPX1R and HPX2R.

**FANE SPEAKERS—SUPPLIED TO MOST LEADING U.K. MANUFACTURERS OF GROUP & DISCO EQUIPMENT**  
 2 years guarantee on speakers & Horns  
 Distributors (Wholesale & Retail)  
 Rec. prices shown correct at 23/3/77

**LINEAR PRODUCTS LTD, ELECTRON WORKS, ARMLEY, LEEDS**  
 Manufacturers & Export enquiries to:  
**FANE ACOUSTICS LTD, 286 BRADFORD ROAD, BATLEY, YORKS**

**MAINS INTERCOM**

**NO BATTERIES NO WIRES ONLY**  
**£29-99 PER PAIR + VAT £9-78**

The modern way of instant 2-way communications. Supplied with 8-core wire. Just plug into power socket. Ready for use. Crystal clear communications from room to room. Range 1-mile on the same mains phase. On/off switch. Volume control. Useful as inter-office intercom, between office and warehouse in surgery and in homes. P. & P. 99p.

**4-STATION INTERCOM**

**£19-95 + V.A.T. £1 60**

Solve your communication problems with this 4-Station Transistor Intercom system (1 master and 3 Subs), in robust plastic cabinets for desk or wall mounting. Call/talk/listen from Master to Subs and Subs to Master. Ideally suitable for Business, Surgery, Schools, Hospitals and Offices. Operates on one 9V battery. On/off switch. Volume control. Complete with 3 connecting wires each 66ft. A Battery and other accessories. P. & P. 60p.

**NEW! AMERICAN TYPE CRADLE TELEPHONE AMPLIFIER**

**ONLY £15-95 + VAT £1-28**

Latest transistorized Telephone Amplifier with detached plug-in speaker. Placing the receiver on to the cradle activates a switch for immediate two-way conversation without holding the handset. Many people can listen at a time. Increase efficiency in office, shop, workshop. Perfect for "conference" calls: leaves the user's hands free to make notes, consult files. No long waiting, saves time with long-distance calls. On/off switch, volume control, conversation recording model at £17-95 + VAT £1-44. P. & P. 89p.  
 10-day price refund guarantee on all items  
**WEST LONDON DIRECT SUPPLIES (FWO)**  
 166 KENNINGTON HIGH STREET, LONDON, W8  
 01-887 5548

Please mention Practical Wireless when replying to Advertisements

## H.A.C. SHORT-WAVE KITS

WORLD-WIDE RECEPTION



'H.A.C.' well known by amateur constructors for its Short Wave receivers, now offers a complete range of kits and accessories to suit the novice and the expert.

£9-00 inclusive—the ever popular and easy to construct DX receiver Mark III; containing all genuine short wave components, drilled chassis, valve, accessories and full instructions.

NEW T Twin transistor receiver, selective, sensitive and with fantastic reception, yet needing only a single PP3 battery. Special introductory offer at £9-70 inclusive—can only be held at this price while stocks last.

Lastly the K and K plus (illustrated above) for the more advanced constructor. This receiver has recently been re-designed for even better reception. All orders despatched within 7 days. Send stamped and addressed envelope now for free descriptive catalogue of kits and accessories.

SORRY, NO CATALOGUES WITHOUT S.A.E.

**"H.A.C." SHORT-WAVE PRODUCTS**  
 P.O. Box No. 16, 10 Windmill Lane  
 Lewes Road, East Grinstead, West  
 Sussex RH19 3SZ





### NOTICE TO READERS

When replying to Classified Advertisements please ensure:

- That you have clearly stated your requirements.
- That you have enclosed the right remittance.
- That your name and address is written in block capitals, and
- That your letter is correctly addressed to the advertiser.

This will assist advertisers in processing and despatching orders with the minimum of delay.

### Receivers and Components

**COMPONENTS FOR P.W. PROJECTS.** Components lists with prices available for P.W. projects from October 1977 onwards. Send SAE stating project and month of publication (maximum four projects per SAE). Lists sent by return together with ACE order form/catalogue. ACE MAILTRONIX, Tootal Street, Wakefield, W. Yorks WF1 5JR.

**NOVELTY COLLECTING**

## VINTAGE RADIO

**1920 to 1950**

Receivers, valves, components, service data, historical research, books, magazines, repairs and restorations. A complete service for the collector and enthusiast of vintage radio.

S.a.e. with enquiries and for monthly newsheet. Full 1977 catalogue, 70p post paid.

**TUDOR REES (Vintage Services), 14, Broad Street, Staple Hill, Bristol, BS16 5NL. Tel. Bristol 365472.**

**TIRRO ELECTRONICS** the mail order division of **RIFRO ELECTRONICS UK** offers a wide range of components for the amateur enthusiast. Large SAE or 20p brings list. **GRENELL PLACE, MAIDENHEAD, BERKS SL6 1HL.**

## VALVES

Radio - T.V. - Industrial - Transmitting and Projector Lamps

We Dispatch Valves to all parts of the world by return of post. Air or Sea mail, 2700 Types in stock, 1930 to 1976. Obsolete types a speciality. List 20p. Quotation S.A.E. Open to callers Monday to Saturday 9.30 to 5.00 closed Wednesday 1.00. We wish to purchase all types of new and boxed Valves and Projector Lamps.

**COX RADIO (SUSSEX) LTD.**

Dept. P.W. The Parade, East Wittering, Sussex PO20 8BN  
West Wittering 202J (STD Code 024366)

**BARGAINS GALORE:** LM555CN 35p. 4148 3p. Log Pots 5K 16p. Chassis Sockets 11p. 914 3p. Carbon Film Resistors 1/2 W 100 for 80p. Veroboard 3 1/2 in x 5 in 40p. Send now for complete list. Only extra 15p postage.

**CLEVELAND SUPPLIES, P.O. Box 20, Howard Drive, Redcar, Cleveland.**

# SMALL ADS

The prepaid rate for classified advertisements is 20 pence per word (minimum 12 words), box number 60p extra. Semi-display setting £6.80 per single column centimetre (minimum 2.5 cms). All cheques, postal orders etc., to be made payable to Practical Wireless and crossed "Lloyds Bank Ltd". Treasury notes should always be sent registered post. Advertisements, together with remittance, should be sent to the Classified Advertisement Manager, Practical Wireless, Room 2337, IPC Magazines Limited, King's Reach Tower, Stamford St., London, SE1 9LS. (Telephone 01-261 5846)

### CONDITIONS OF ACCEPTANCE OF CLASSIFIED ADVERTISEMENTS

- Advertisements are accepted subject to the conditions appearing on our current advertisement rate card and on the express understanding that the Advertiser warrants that the advertisement does not contravene any Act of Parliament nor is it an infringement of the British Code of Advertising Practice.
- The publishers reserve the right to refuse or withdraw any advertisement.
- Although every care is taken, the Publishers shall not be liable for clerical or printers' errors or their consequences.

### 24 HR. CLOCK/APPLIANCE TIMER KIT

Switches any appliance of up to 1kW on and off at preset times once a day. KIT contains: AY-3-1230 Clock/Appliance Timer I.C., 0.5" LED display, mains supply, display drivers, switches LEDs, triac, PCBs and full instructions. ONLY £13.75

White box 50x131x71mm with red Acrylic window £2.20  
White box as above drilled ready for KIT £2.60

- DLT77 Dual 0-9° 7 seg. LED Display £1.80  
AY-3-1230 Clock Appliance Timer I.C. £4.85  
LM3911 Thermometer/Temperature Control I.C. £1.00  
555 Timer I.C. 8 pin dip 26p (3 for £1.00)  
741 Op Amp I.C. 8 pin dip 24p (5 for £1.00)

400V TRIACS Plastic		MINI MAINS TRANSFORMERS	
3A	63p	0-6V 100mA	85p
8.5A	78p	12-0-12V 100mA	95p
12A	88p	LEDs 0-9° Green	21p
18A	105p	Red 90p (11 for £1)	
*Isolated tab			

QUANTITY DISCOUNTS ON REQUEST  
ADD 8% VAT + 29p P&P. MAIL ORDER ONLY TO:  
**T. K. ELECTRONICS (PW)**  
108 STUDLEY GRANGE ROAD, LONDON. W7 2LX.

LED's. Mixed bags of 4 different sizes and 4 different colours. 50 at £5.25, 100 at £9.25 including VAT and post and packing. CWO. Michael Williams Electronics, 47 Vicarage Avenue, Cheddle Hulme, Cheshire, SK8 7JP.

### BRAND NEW COMPONENTS BY RETURN.

Electrolytic Capacitors 16V, 25V, 50V.  
0.47, 1.0, 2.2, 4.7 & 10 mfd.—3p, 22, 47—3 1/2p.  
(50V—6p), 100—7p, (50V—8p), 220—8p, (50V—10p), 470—11p, (50V—16p), 1000/15V—15p, 1000/25V—18p, 1000/50V—22p.

Subminiature bead tantalum electrolytics.  
0.1, 0.22, 0.47, 1.0 & 35V, 4.7 @ 6.3V—8p, 2.2/35V & 4.7/25V—9p, 10/25V, 15/16V—12p, 22/16V, 33/10V, 47/6V, 68 & 100 @ 3V—14p.

Mullard Miniature Ceramic E12 Series 63V 2%, 10 pf. to 47 pf.—3p, 56 pf. to 330 pf.—4p.

Vertical Mounting Ceramic Plate Caps. 50V, E12 22 pf.—1000 pf. E6 1500 pf.—47000 pf.—2p

Polystyrene E12 Series 63V. Hor. Mounting. 10 pf. to 1000 pf.—3p, 1200 pf. to 10000 pf.—4p.

Mullard Polyester 250V Vert. Mfg. E6 Series. .01 to .1—4p, .15, .22—5p, .33, .47—8p, .68—11p, 1.0—14p, 1.5—20p, 2.2—24p.

Mylar (Polyester) Film 100V. Vertical Mfg. .001, .002, .005—3p, .01, .02—4p, .04, .05—5p.

Miniature Film Resistors Highstab. E12 5%, 0-125 watt 10Ω to 2MΩ ..... 1p  
0-250 watt 1Ω to 10MΩ. (10% over 1M) ..... 1p  
0-500 watt 10Ω to 10MΩ. .... 2p  
1-000 watt 10Ω to 10MΩ. .... 2p

IN4148—3p, IN4002—5p, IN4006—7p, IN4007—8p  
BC107/B9, BC147/B9, BC157/B9, BF194 & 7—9p.  
20mm. fuses .15, .25, .5, 1.0, 2.0, 3.0 & 5A—3p.  
Printed Circuit Holders for 20mm. fuses—3p.  
Post 10p (Free over £4). Prices VAT inclusive.

**THE C. R. SUPPLY CO.**  
127, Chesterfield Road, Sheffield S8 0RN

S'CONDUCT'S	BU 208 £1.99	CAPACITORS
BC 107 8p	BY 127 10p	0.1/800V 5p
BC 132 16p	TIP 29 35p	25/25V 3p
BC 147 8p	1N 645 11p	
BC 204B 5p	1S 940 4p	W/W RESIST'S
BC 351 11p	INT'G'D C'C'TS	2-5W Axial 12p
BD 131 34p	LM 741 8P DIL 15p	5W Radial 8p
BD 138 37p	LM 741 8P DIL 15p	10W Axial 8p
BT 106 £1.10	M252 81 A 27-00	15W Radial 11p
BU 205 £1.80	(Rhythm Gen.)	
BRIDGE RECT. 1S 805 (1A 50V) 16p	Min Order £2. p&P 25p. Prices include VAT	SAE FOR LISTS
	Export and Wholesale enquiries welcome	
	<b>K &amp; A DISTRIBUTORS, 32 BARBY ROAD, SYSTON, LEICESTER. TEL. 0533 609391</b>	

**ELECTRONIC COMPONENTS** Since 1966. Price List and 50 Mixed Resistors FREE on request. J. R. Hartley, 78B High Street, Bridgnorth, Salop WV16 4DY.

## DIGITAL BONANZA

Latest stock allows even bigger bargains!!

**PACK M1 (100% Good)** 2 Calculator keyboards. £1.00

**PACK M2 (100% Good)** 1 x 2102L-1, 1024 bit static RAM. Low power requirement version of 2102. With data. £1.50

**PACK M3 (100% Good)** 1 x MM5725 4 function calculator I.C. (Not designed for use with Pack M1). With data. £1.00

**PACK E1 (80% Guaranteed Good)** 5 x MAN3 7 segment 0.27" LED displays. £1.00

**PACK E2 (100% Good)** 1 x 8 digit 0.33" high 7 segment calculator style Liquid Crystal display. With data. £2.95

**PACK E3 (100% Good)** 1 x 8 digit 0.5" high 7 segment calculator style Liquid Crystal display. With data. £4.25

**PACK T1 (100% Good)** 1 x digital wristwatch I.C. Directly drives L.C.D. watch display (see Pack T2). Designed for a wristwatch but could be used to build a clock. With data. £1.00

**PACK T2 (100% Good)** 1 x 3 1/2 digit wristwatch Liquid Crystal display with centre colon. With data. £1.00

**PACK L1 20** Assorted op-amps. Marked and unmarked devices you identify and test. Excellent value for £1.00

**PACK L2 20** LM709 op-amps. (Untested). Another bargain at £1.25

**PACK D1 (80% Guaranteed Good)** 15 x DTL logic I.C.'s. Mainly dual J-K flip flops. Replaces those costly TTL flip flops in most projects. Saves £££'s. £1.00

**PACK D2 25 x SN7400** type I.C.'s. 100 two 1/2 NAND gates. We guarantee at least 50 good. A giveaway at only £1.00

Minimum percentage guaranteed good is shown alongside Pack number. Where no guaranteed minimum is stated, we'll guarantee that after testing, the yield from these packs will prove to be much cheaper than buying at average mail order prices. Satisfaction guaranteed or return complete pack for a replacement or refund.

MAIL ORDER ONLY—  
NO CALLERS PLEASE  
Postage and Packing please add 20p

**CODESPEED**  
P.O. Box 23, 34 Seaford Road,  
Copparr, Portsmouth, Hants. PO3 5BJ

**TRANSISTORS, RESISTORS, CAPS, POTS, Plugs & Sockets, Zeners, TTL, Cable, Boxes.** All at very good prices. 65 Railway Road, Leigh, Lancs. Telephone Leigh 679575.

## Radio Receivers

**SHORTWAVE 3-2.12 MHz+M.W.** Small Portables (Superhet+INT.Speaker) £10.95, headphones for use with this set £4.95. VHF/Airband 88-135 MHz+M.W. Pocket Sets (Superhet+Int Spur.) £9.95 available without Air (108-135 MHz) Band at £8.45. Mains-Battery MW+VHF+Air (108-174 MHz) Portables £13.55. Prices include P & P, Accs & VAT. Noble Electronics, 26 Lloyd Street, Atrincham, Cheshire WA14 2DE. Tel: 061-941 4510.

## Electrical

**LIST NO. 28** now ready—Styli illustrated equivalents also cartridges, leads, etc., free for long SAE. Felstead Electronics (PW), Longley Lane, Gatley, Cheddle, Cheshire SK8 4EE.

## Educational

GO TO SEA as a Radio Officer. Write: Principal, Nautical College, Broadwater, Fleetwood FY7 8JZ.

# TELEVISION TRAINING

15 MONTHS full-time course for beginners. Short course can be arranged if you have previous electronics knowledge.

- 13 WEEKS ELECTRONIC FUNDAMENTALS
- 13 WEEKS MONOCHROME TELEVISION
- 13 WEEKS COLOUR TELEVISION
- 13 WEEKS CLOSED CIRCUIT TV & VCR

The training incorporates a high percentage of practical work.

Next session starts on September 11th.

Prospectus from:

## LONDON ELECTRONICS COLLEGE

Dept. B6, 20 Penywern Road, London SW5 9SU. Tel. 01-373 8721

## Courses

**MICROPROCESSOR PROGRAMMING.** Correspondence courses including personal tuition for various machines. Also basic microprocessor course and BASIC and FORTRAN courses. Contract programming undertaken. Details from: Micro Productions, "Greenfields," Llantwit Fardre, Pontypridd.

## Wanted

**COLLECTOR WANTS** 30's Art Deco/40's and early 50's Bakelite radios and TVs. Cheap please. Non-working OK. 01-552 0014.

**"RADIO AND TELEVISION SERVICING"** books wanted from 1964-65 edition up to date. £3.00 plus postage paid per copy by return of post. Bell's Television Services, 190 Kings Road, Harrogate, N. Yorks. Tel: (0423) 65885.

**WANTED.** "Practical Wireless" "Apollo" F.M.-Tuner abandoned kit parts. "Murree" Watling Street, Hinckley, Leicester. Tel: 35087.

## Ladders

**LADDERS.** Varnished 20ft 9in extd., £29-72, carr. £2-40. Leaflets. Also alloy ext. up to 62ft 6in. Ladder Centre (WLS2), Halesfield (1) Telford. Tel: 586644. Callers welcome.

*Practical Wireless, June 1978*

## Situations Vacant

# Radio Technicians

Government Communications Headquarters has vacancies for Radio Technicians. Applicants should be 19 or over.

**STANDARDS** required call for a sound knowledge of the principles of electricity and radio, together with 2 years experience of using and maintaining radio and electronic test gear.

**DUTIES** cover highly skilled telecommunications/electronic work, including the construction, installation, maintenance and testing of radio and radar telecommunications equipment and advanced computer and analytic machinery.

**QUALIFICATIONS:** Candidates must hold either the City and Guilds Telecommunications Part 1 (Intermediate) Certificate or equivalent HM Forces qualification.

**SALARY** (inc. supps.) from £2,673 at 19 to £3,379 at 25 (higher pay on entry) rising to £3,883 with opportunity for advancement to higher grades up to £4,297 with a few posts carrying still higher salaries.

Opportunities for service overseas.

Further particulars and application forms available from:

## GCHQ

Recruitment Officer,  
GCHQ, Oakley,  
Priors Road, Cheltenham, GL52 5AJ.  
Cheltenham (0242) 21491 Ext 2270



## Books and Publications

**SIMPLIFIED TV REPAIRS.** Full repair instructions individual British sets £4-50, request free circuit diagram. Stamp brings details unique. TV Publications (Ause PW), 76 Church Street, Larkhall, Lanarkshire.

### HOW TO DEAL SUCCESSFULLY IN USED COLOUR TELEVISIONS

Exciting new business guide reveals how anyone with average intelligence can make a high spare-time CASH INCOME selling used colour TV's from home. Written mainly for the non-technical, but with immediate applications for the engineer, this comprehensive publication describes: how to start — where and what to buy — which sets to avoid — reconditioning — how, where and when to advertise — presentation — how to expand — comprehensive sections on general business formalities, guarantees, manufacturers, spares, and monochrome sets. PLUS MUCH MORE! This unique guide presents a sound, reputable and very profitable home business which can be started for less than £20!

Send just £25 £5 today for fast delivery. Includes FREE advice and FREE up-dating service.

**CITY PUBLISHING (P.W.)**  
2 Nottingham Rd., Spondon, Derby DE2 7NH.

**HOW TO START A BUSINESS.** By popular demand a fully illustrated manual has now been produced, showing, in easy, step by step, stages, how to rewind ARMATURES & FIELD COILS as used in Vacuum Cleaners, Drills and Portable Tools. Chapters on taking data, materials required, test instruments required, rewind instructions, charts, etc. How to cost instruction manual £4-00 plus 30p P & P. CWO. COPPER SUPPLIES, 102 Parnwood Road, Withington, Manchester 20. Dept. PWA.

### THE DALESFORD SPEAKER BOOK

by R. F. C. Stephens.

This book is a must for the keen home constructor. Latest technology DIY speaker designs. Contains full plans for infinite baffle and reflex designs for 10-100 watts, also unusual centre-base system for those who want hi-fi to be "Heard and not seen". £1.95 (£2.20 post paid. \$3 Overseas).

**VAN KAREN PUBLISHING**  
3 SWAN STREET  
WILMSLOW  
CHESHIRE

## Service Sheets

**SERVICE SHEETS** for Radio, Television, Tape Recorders, Stereo, etc. With free fault-finding guide, from 50p and SAE. Catalogue 25p and SAE. HAMILTON RADIO, 47 Bohemia Road, St. Leonards, Sussex.

**LARGE SUPPLIER OF SERVICE SHEETS**  
All models at 75p PO/Cheques plus s.a.e. Except Colour and Car Radios. Free TV fault finding chart or TV list. Strictly by return.

**C. CARANNA**  
71 Beaufort Park, London NW11 6BX  
01-458 4882

**SERVICE SHEETS,** Radio TV, etc., 10,000 models. Catalogue, 24p, plus SAE with orders, enquiries. Telray, 154 Brook Street, Preston PR1 7HP.



## SERVICE SHEETS — COLOUR TV SERVICE MANUALS

Service Sheets for Mono TV, Radios, Record Players and Tape Recorders 75p. Please send large Stamped Addressed Envelopes. We can supply manuals for most makes of Colour Television Receivers by return of post.

**B.R.C. PYE ECKO PHILIPS ITC/KE SONY G.E.C. HITACHI BAIRD ULTRA INVICTA FERGUSON H.M.V. MARCONI AND MANY MORE**

Let us quote you. Please send a Stamped Addressed Envelope for a prompt reply. Also comprehensive T.V. repair manuals by J. M. Court. S.A.E. for details. MAIL ORDER ONLY

**G. T. TECHNICAL INFORMATION SERVICE**  
10 DRYDEN CHAMBERS, 119 OXFORD ST., LONDON W1R 1PA

**BELL'S TELEVISION SERVICES** for Service Sheets on Radio, TV, etc., 75p plus S.A.E. Colour TV Service Manuals on request. S.A.E. with enquiries to B.T.S., 190 King's Road, Harrogate, N Yorkshire. Tel: (0423) 55885.

## Aerials

### ANTI-TVI TRAP DIPOLES

CUT OUT TVI TX-ing and SWL-ing.  
MODELS— SWL £26.00; 500 Watt or SWL £41.00.  
Aerial Matching Unit, 500 Watt & SWL 10-150 metres inc. Shipping Band, £16.25.  
Inc. VAT and P & P. Send 10" x 7" 12½p s.e.e. and 3 x 9p stamps for details, aerial article, test reports, testimonials G2DYM.

LAMBDA, WHITEBALL, WELLINGTON, SOMERSET

## For Sale

**COMPUTERISED CHESS Challenger** Three Levels of skill normally £200, our price only £124.95. Mail Order only. JAGBERRY LTD., 95b Ardwell Avenue, Barkingside, Ilford, Essex.

**NEW BACK ISSUES OF "PRACTICAL WIRELESS"** available 65p each post free. Open P.O./Cheque returned if not in stock—Bell's Television Services, 190 Kings Road, Harrogate, N. Yorks. Tel: (0423) 55885.

**SEEN WHISTONS CAT?** 5000 odds and ends. Mechanical/Electrical Cat free. WHISTON (Dept. PW), New Mills, Stockport.

**LOGIC PROBE**, suitable TTL/CMOS 5-16V indicates Logic states and Trigger Pulses £12 inc. C. Marshall, 22 Oakfield Road, Croydon, Surrey CR0 2UA.

**S.W.L.s** are you missing dx? Then try our aerial system complete with tuner. £26 inc. CWO. MDH Radiotelephones, Munster House, Priory Road, Milford Haven, Dyfed.

**MARCONI SIGNAL GENERATOR**, TF601 D/1. 10MHz to 470MHz. Xtal Calib. Excellent condition £120 ono. Tel: Henlow Camp 695.

**"VDU, "Practical Wireless"** design, just needs 5V and keyboard, suit microprocessor. Bargain at £40 ono. Tel: Newbury 47071.

## Miscellaneous

### MORE DX?

**RARE DX** under QRM? DIG IT OUT from whistles and CW with a Tunable Audio Notch Filter, speaker amplifier, bypassed when off, only £7-99. **NO LONG WAVE?** 100-600K Hz Converter feeds your 3-5.4 MHz receiver, only £8-60. **SPOT RARE DX** with a Calibrator, 1 MHz, 100, 25 KHz markers to VHF, only £13-60. **EXPLORE VLF**, 10-150 KHz Receiver only £9-70. **SIG. GEN.** 10-200 Hz, sine/square, only £9-80. **SEND OFF NOW.** Each easy-assembly kit includes all parts, printed circuit, case, connectors etc, instructions, postage and money back assurance.

CAMBRIDGE KITS

45 (PF) Old School Lane, Milton, Cambridge.

**OUTSTANDING 2200 HI-FI FM TUNER.** Latest silicon superhet design, Varicap Tuning, Full Coverage 88-102 MHz. Ideal for Push button/Manual tuning. Supplied Built & Tested with full instructions only £9-95 (P&P 50p). GREGG ELECTRONICS, 86-88 Parchmore Rd, Thornton Heath, Burrey.

ENAMELLED COPPER WIRE				
SWG	1 lb	Box	4oz	2oz
14-19	2-49	1-29	-69	-59
20-29	2-45	1-69	-82	-89
30-34	2-99	1-79	-89	-64
35-40	2-95	1-99	1-84	-75

Inclusive of p&p and VAT.  
SAE brings Catalogue of copper and resistance wires in all coverings.  
**THE SCIENTIFIC WIRE COMPANY**  
PO Box 36, London E4 8BW  
Reg. Office: 12 Coningsby Gardens.

### PRINTED CIRCUITS and HARDWARE

Readily available supplies of Constructors' Hardware. Printed circuit boards, top quality for individual designs. Prompt service. Send 25p for catalogue from:

**RAMAR CONSTRUCTOR SERVICES**  
Masons Road, Stratford-on-Avon, Warwick  
Tel: 4378

### BUILD THE TREASURE TRACER MK III Metal Locator



- Varicap tuning
- Britain's best selling metal locator kit!
- Fitted with Faraday shield.
- Speaker and earphone operation
- 4,000 already sold
- Knocks down to only 17in.
- Practical search coil assembly
- Thoroughly professional finish
- As seen on BBC1 and BBC2 TV
- You only need soldering iron, screwdriver, pliers and snips
- Five transistor circuit

Send stamped, addressed envelope for leaflet

Complete £15.95 Built & tested £20.95  
Post £1.26 + £1.37 VAT Post £1.26 + £1.77 VAT

**MINIKITS ELECTRONICS,**  
4 CLEVELAND ROAD,  
LONDON, E11 2AN (Mail order only)

**SCOPE CALIBRATOR**, portable, battery operated. SAE details, Ramar Constructor Services, Masons Road, Stratford-on-Avon, Warwick.

### GOVERNMENT SURPLUS SUPER PACK 36 PLUS

2 BCY30, 2 BFX65, 2 Varley Relays, 4 5 D.F. toggle switches, 2 72" multicores, PVC covered cables, 2 4T Microphone/Speakers, 8 microswitches, 1 magnet, 1 Buzzer, 1 app. 25 yd gingle or multistrand wire PLUS. Send £2-50 + 50p PP to

**B.B. Supplies, Dept. P.W., 125 Hight Street, Deal, Kent.**

4T Inserts 1½ x ½ 20 ohm DC. Ideal for microphone or speaker use. 50p each incl. P & P Quantity discounts available.

We would like you to know that we make—

- ★ BEC Cabinets
- ★ Special cabinets
- ★ Prototype printed circuits
- ★ Instrument panels

We also have a quantity 683/AT Cabinet punching service, and undertake artwork.

**H. M. ELECTRONICS**  
275a Fullwood Rd; Sheffeld S16 3SD  
Tel: (0742) 699678  
Send 15p (Refundable) for leaflets

### ARMATURE & COIL WINDING ENAMELLED COPPER WIRE

Only top quality materials supplied. All orders dispatched within 24 hrs.

S.W.G.	1 lb reel	½ lb reel
16 to 18	£2-85	£1-80
19 to 23	£3-15	£1-80
24 to 28	£3-45	£1-80
29 to 40	£3-95	£2-10

All prices are inclusive of P. & P. in U.K.  
**COPPER SUPPLIES, 182 Parrwood Road, Withington, Manchester 20. Tel: 061-445 8783**

### 100 WATT GUITAR/PA/MUSIC AMPLIFIER

With superb treble, bass, Overdrive, airtline, 12 months guarantee. Unbeatable offer at £39. Also twin channel with separate treble/bass per channel £48. Money returned if not absolutely delighted within 7 days. Also fuzz boxes great sound, robust construction £4-99. Also 100 watt 12 in. speakers £22-50.

All inclusive of P.P. Send cheque or P.O. to:  
**WILLIAMSON AMPLIFICATION**  
62 THORNCLIFFE AVENUE, DUKINFIELD, CHESHIRE. TEL: 061-344 9007

**CUSTOM METER Scales** £2-00. Send original scale (returnable) with requirements. Mellor, 1 Orchard Road, Fairfield, Stockton, Cleveland.

### alfac SYSTEM

ALFAC ETCH RESIST Dry Transfer Electronic symbols can be used to make P.C.B.'s by transferring directly on to copper clad boards or tracing paper. Almost 100 different symbols for easy, accurate and quick results.

We invite bonafide retailers and wholesalers to distribute the Alfac range. Generous trade discounts are offered, together with fully illustrated support brochures for distribution. A free catalogue, sample and trade terms are available from us on receipt of your official company's request. Please write to Pelitech Ltd., 6 Church Green, Witney, Nr. Oxford.

### SPECIAL OFFER



Magnetic Contacts for Burglar Alarms, etc. 105 flush 4 wire 58p. 104 surface 5 terminal 89p. 106 flush 2 terminal 55p. Prices fully inclusive.

Send crossed cheque, P.O. to: **CWAS ALARM**, 11 Denbrook Walk, Bradford BD4 8QS, W. Yorks. or S.A.E. for complete Price List of Professional Alarm Equipment.

**SUPERB INSTRUMENT CASES** by Hazell, manufactured from P.V.C. faced steel. Hundreds of people and industrial users are choosing the cases they require from our vast range. Competitive prices start at a low 90p, chassis punching facilities at very competitive prices. 400 models to choose from, free literature (stamp would be appreciated). **BAZELLI**, Dept No 25, St. Wilfrid's, Foundry Lane, Halton, Lancaster LA2 6LT.

### EX MINISTRY EQUIPMENT

Aerial Rotation Motor units, complete with Remote Position Indicator connectors and Data. Transistor Curve Tracers. DC Motors. 5V DC Stabilised Power Supplies. Thumb Wheel Switches. Ten Turn Potentiometers. DC Milliamperes. Lever Switches. Seven Segment Gas Displays. Terminal Blocks. 12 Way Cable. 100 Way Cable. 240V Solenoids. Push Buttons. Odd Items of Test Equipment. Aircraft Instruments and Equipment. Lots of Items in Stock. 9" x 3" S.A.E. For List. Mail Order Only. Eldon Electronics, 31 Alexander Drive, Timperley, Cheshire, WA15 6NF.

## NOTICE TO READERS

Whilst prices of goods shown in classified advertisements are correct at the time of closing for press, readers are advised to check with the advertiser both prices and availability of goods before ordering from non-current issues of the magazine.



TTLs by TEXAS		74L's		4001		OP. AMPS.		MEMORY I.C.s		MPS A12		DIODES		OA202	
7400	14p	7407	20p	74L300	30p	4001	20p	NE531V	140p	MPSA12	82p	2N2907/A	25p	8Y121	12p
7401	14p	74100	140p	74L302	30p	4002	20p	RC4136	130p	MPSA35	48p	2N2908/B	9p	IN118	7p
7402	16p	74104	75p	74L304	30p	4003	20p	700	40p	MPS003	72p	2N2920/CG	11p	OA47	8p
7403	16p	74105	75p	74L308	30p	4009	20p	CA3180	120p	MPS006	72p	2N3053	22p	OA81	15p
7404	24p	74107	35p	74L310	32p	4010	20p	LM301A	48p	MPS008	80p	2N3054	45p	OA83	15p
7405	25p	74109	40p	74L313	35p	4011	20p	LM318N	175p	MPS008	80p	2N3055	48p	OAB9	9p
7406	44p	74110	75p	74L320	35p	4012	20p	LM324N	130p	MPS008	80p	2N3056	48p	OA91	9p
7407	44p	74111	75p	74L322	34p	4013	20p	LM341N	148p	MPS008	80p	2N3057	48p	OA93	9p
7408	22p	74116	210p	74L327	43p	4014	20p	MC1488P	75p	OC29	140p	2N3442	131p	OA99	9p
7409	22p	74118	180p	74L347	150p	4015	20p			OC35	140p	2N3543	140p	OA99	9p
7410	16p	74119	225p	74L348	150p	4016	20p			OC71	32p	2N3944	34p	OA200	9p
7411	26p	74120	130p	74L373	60p	4017	100p			R2088	125p	2N3702/3	14p		
7412	25p	74121	32p	74L374	70p	4018	110p			R2010	225p	2N2704/5	14p		
7413	40p	74122	85p	74L374	70p	4019	52p			TIP26A	90p	2N3706/7	14p	1A 30V	25p
7414	83p	74123	75p	74L375	75p	4020	120p			TIP29C	62p	2N3708/9	14p	1A 100V	27p
7415	40p	74125	70p	74L383	120p	4021	115p			TIP30A	90p	2N3713	320p	1A 400V	47p
7416	40p	74126	70p	74L385	140p	4022	100p			TIP30C	12p	2N3819	27p	8A 50V	40p
7417	40p	74128	45p	74L388	55p	4023	22p			TIP31A	68p	2N3820	50p	2A 100V	45p
7418	18p	74128	82p	74L390	80p	4024	80p			TIP31C	68p	2N3823	78p	3A 200V	70p
7419	43p	74132	61p	74L393	80p	4025	22p			TIP32A	78p	2N3886	87p	3A 600V	80p
7422	25p	74136	81p	74L395	140p	4026	170p			TIP33A	97p	2N3900/8	22p	4A 100V	90p
7423	38p	74141	85p	74L397	55p	4028	170p			TIP33C	120p	2N4053	11p	1A 400V	85p
7425	33p	74142	300p	74L399	110p	4027	65p			TIP34A	124p	2N4193/A	25p	6A 500V	147p
7426	43p	74145	95p	74L399	140p	4029	120p			TIP34A	143p	2N4193/B	25p	6A 500V	120p
7427	44p	74147	205p	74L399	140p	4029	120p			TIP35A	240p	2N4401/3	34p	10A 100V	140p
7428	40p	74148	180p	74L399	140p	4029	120p			TIP35A	240p	2N4401/3	34p	10A 100V	140p
7430	37p	74151	81p	74L399	140p	4029	120p			TIP35A	240p	2N4401/3	34p	10A 100V	140p
7432	37p	74151	81p	74L399	140p	4029	120p			TIP35A	240p	2N4401/3	34p	10A 100V	140p
7433	43p	74153	110p	74L399	140p	4029	120p			TIP35A	240p	2N4401/3	34p	10A 100V	140p
7437	37p	74154	100p	74L399	140p	4029	120p			TIP35A	240p	2N4401/3	34p	10A 100V	140p
7438	37p	74155	97p	74L399	140p	4029	120p			TIP35A	240p	2N4401/3	34p	10A 100V	140p
7440	18p	74156	97p	74L399	140p	4029	120p			TIP35A	240p	2N4401/3	34p	10A 100V	140p
7441	85p	74157	77p	74L399	140p	4029	120p			TIP35A	240p	2N4401/3	34p	10A 100V	140p
7442	75p	74159	290p	74L399	140p	4029	120p			TIP35A	240p	2N4401/3	34p	10A 100V	140p
7443	120p	74160	180p	74L399	140p	4029	120p			TIP35A	240p	2N4401/3	34p	10A 100V	140p
7444	120p	74161	180p	74L399	140p	4029	120p			TIP35A	240p	2N4401/3	34p	10A 100V	140p
7445	97p	74162	180p	74L399	140p	4029	120p			TIP35A	240p	2N4401/3	34p	10A 100V	140p
7448	100p	74163	180p	74L399	140p	4029	120p			TIP35A	240p	2N4401/3	34p	10A 100V	140p
7447	75p	74164	120p	74L399	140p	4029	120p			TIP35A	240p	2N4401/3	34p	10A 100V	140p
7448	85p	74165	65p	74L399	140p	4029	120p			TIP35A	240p	2N4401/3	34p	10A 100V	140p
7450	18p	74165	180p	74L399	140p	4029	120p			TIP35A	240p	2N4401/3	34p	10A 100V	140p
7451	16p	74167	320p	74L399	140p	4029	120p			TIP35A	240p	2N4401/3	34p	10A 100V	140p
7453	18p	74170	280p	74L399	140p	4029	120p			TIP35A	240p	2N4401/3	34p	10A 100V	140p
7454	18p	74172	750p	74L399	140p	4029	120p			TIP35A	240p	2N4401/3	34p	10A 100V	140p
7460	18p	74173	100p	74L399	140p	4029	120p			TIP35A	240p	2N4401/3	34p	10A 100V	140p
7470	38p	74174	120p	74L399	140p	4029	120p			TIP35A	240p	2N4401/3	34p	10A 100V	140p
7472	32p	74175	120p	74L399	140p	4029	120p			TIP35A	240p	2N4401/3	34p	10A 100V	140p
7473	38p	74178	130p	74L399	140p	4029	120p			TIP35A	240p	2N4401/3	34p	10A 100V	140p
7474	37p	74177	120p	74L399	140p	4029	120p			TIP35A	240p	2N4401/3	34p	10A 100V	140p
7475	43p	74180	120p	74L399	140p	4029	120p			TIP35A	240p	2N4401/3	34p	10A 100V	140p
7476	37p	74181	324p	74L399	140p	4029	120p			TIP35A	240p	2N4401/3	34p	10A 100V	140p
7480	54p	74182	190p	74L399	140p	4029	120p			TIP35A	240p	2N4401/3	34p	10A 100V	140p
7481	100p	74184	250p	74L399	140p	4029	120p			TIP35A	240p	2N4401/3	34p	10A 100V	140p
7482	90p	74185	190p	74L399	140p	4029	120p			TIP35A	240p	2N4401/3	34p	10A 100V	140p
7483	85p	74186	90p	74L399	140p	4029	120p			TIP35A	240p	2N4401/3	34p	10A 100V	140p
7484	100p	74190	120p	74L399	140p	4029	120p			TIP35A	240p	2N4401/3	34p	10A 100V	140p
7485	120p	74191	120p	74L399	140p	4029	120p			TIP35A	240p	2N4401/3	34p	10A 100V	140p
7486	38p	74192	100p	74L399	140p	4029	120p			TIP35A	240p	2N4401/3	34p	10A 100V	140p
7489	240p	74193	60p	74L399	140p	4029	120p			TIP35A	240p	2N4401/3	34p	10A 100V	140p
7490	35p	74193	60p	74L399	140p	4029	120p			TIP35A	240p	2N4401/3	34p	10A 100V	140p
7491	90p	74195	110p	74L399	140p	4029	120p			TIP35A	240p	2N4401/3	34p	10A 100V	140p
7492	54p	74196	180p	74L399	140p	4029	120p			TIP35A	240p	2N4401/3	34p	10A 100V	140p
7493	34p	74197	130p	74L399	140p	4029	120p			TIP35A	240p	2N4401/3	34p	10A 100V	140p
7494	90p	74198	250p	74L399	140p	4029	120p			TIP35A	240p	2N4401/3	34p	10A 100V	140p
7495	75p	74199	250p	74L399	140p	4029	120p			TIP35A	240p	2N4401/3	34p	10A 100V	140p
7499	90p	74221	175p	74L399	140p	4029	120p			TIP35A	240p	2N4401/3	34p	10A 100V	140p

**SEMICONDUCTORS, ALL FULL SPEC.** BC212, BC182, BC217, BCY71, 8F197 BC159 all 8p each. RCA 2015 TO3 POWER TRANSISTORS (SIM, 2N3055) 35p. MRD 3051 PHOTO TRANSISTORS 35p. FETS SIMILAR TO 2N 3819 17p. MOSFET SIMILAR 40073 35p. 3N140 MOSFETS 30p. M203 DUAL MATCHED PAIR MOSFETS, SINGLE GATE PER TUBE 40p. 5L301 DUAL MATCHED PAIR 5L1, 5L2 TRANSISTORS Fe, 100MHZ 30p. INTL. C.1103 102A, 102B, 102C, 102D, 102E, 102F, 102G, 102H, 102I, 102J, 102K, 102L, 102M, 102N, 102O, 102P, 102Q, 102R, 102S, 102T, 102U, 102V, 102W, 102X, 102Y, 102Z. DIODES 35p. MC1310 STEREO DECODER IC-120p. TA8000 IC; 90p. CD4001 IC; 50p. 7418 PIN IC's 23p. DIODES; IN4002 4p, IN4005 7p, RED LED's 0.2" x 0.125" 12p, NE555 TIMER IC's 34p. LM 381 95p.

**MICROPHONES;** GRUNDIG ELECTRET MICROPHONE INSERTS WITH FET PREAMP £1.50p. CRYSTAL MIKE INSERTS 37mm 45p. ELECTRET CONDENSER MIKES, IK IMP. WITH STANDARD JACK PLUG £2.85. EM506 CONDENSER MIKES, UNIDIRECTIONAL, FET AMP DUAL IMPEDANCE 50K/600 OHMS ON/OFF SWITCH 30-18KHZ £11.00. EM100 MIN. TIE CLIP CONDENSER MIKES, OHMI, IK IMP. USES DEAF AID BATTERY (SUPPLIED) £4.95.

**MORSE KEYS;** ALL METAL HI-SPEED TYPE £2.25.

**TIL 305 ALPHA-NUMERICAL DISPLAYS,** 0.38" FIG. SIZE, WITH DATA SHEET, £2.75.

**SWR/POWER METER TYPE SWR50** SWR 1.2-1: 1, POWER 0-1KW, 3-5 TO 150MHZ, 52 OHMS IMPED. £12.75. SWR AND F.S. METER 3-15 OHMZ, 50 OHMS IMPED., £9.50. FX2000 CRYSTAL MARKER GENERATOR 100KHZ TO 50MHZ (LESS XTAL) £7.90.

**SOLDER SUCKERS** PLUNGER TYPE, REPLACEABLE NOZZLE, EYE PROTECTION SHIELD, HIGH SUCTION £4.95.

**CRYSTALS,** 300KHZ 40p, 4.43MHZ CTV XTAL 45p.

**EDGE CONNECTORS** 0-1 MATRIX 64 WAY 65p, 34 WAY 40p, 0.2" 18 WAY 15p. RELAYS MIN SEALED TYPE 4 POLE CHANGEOVER 36 OHM (WITH BASE) 45p, MIN. SEALED 240V AC 2 POLE COIL RELAYS 40p, 4 POLE REED RELAYS, 12 VOLTS 30p, MIN. REED RELAY, N.O.PEN, 30mm/m x 10mm/m 3-6VDC, 22p.

**MOTORS;** 5 TO 6 VDC MODEL MOTORS 20p, SUB. MIN. 'BIG INCH' 115 VAC 3 RPM MOTORS 30p.

**BOXES;** BLACK ABS PLASTIC PROJECT BOXES, BRASS INSERTS AND LID: 75 x 56 x 35mm 44p, 95 x 71 x 35mm 52p, 115 x 95 x 36mm 60p.

**TRANSFORMERS;** 6-0-6V 100MA, 9-0-9 75MA, 12-0-12F 50MA ALL 75p EACH, 12-0-12V 100MA 95p, 12 VOLT 500MA 95p, 1:1 TRIAC/XENON PULSE TRANSFORMERS 30p, 6MH 3 AMP CHOKES 30p.

**BUZZERS,** GPO TYPE 6-12 VOLTS 30p, 12 VOLT LARGE PLASTIC DOMED BUZZERS (50mm) LOUD NOTE 50p, MIN. SOLID STATE BUZZERS, 6-9-12 OR 24 VOLT, ALL 15MA., 75p each, 6-12V ALL-METAL BUZZER, 30mm, HIGH PITCH, 25p. U.H.F. TUNERS, PUSH BUTTON T.V. TYPE (NOT VARIAC) NEW AND BOXED £2.50.

**TAPE HEADS;** STEREO CASSETTE £3.00. MIN330 DUAL IMPED. RP HALF TRACK HEADS 30p. SRP90 1 TRACK RP HEADS £1.95. STANDARD 8 TRACK STEREO £1.75. TD10 DUAL HEAD ASSEMBLIES 2 HEADS, BOTH 1/2 TRACK RP WITH BUILT IN ERASE, MOUNTED ON BRACKET £1.20p.

**SPECIAL OFFER, ZN414 RADJO CHIPS** 75p. LM380 80p. METERS; 200 MICRO AMP MIN. LEVEL METERS 75p, GRUNDIG IMA BATT. LEVEL METERS 40 x 40mm £1.10p, STEREO TUNING METERS 100 MICROAMP PER MOVEMENT £2.75. 30 TURNS DIAL MECHANISMS WITH LOCKING ARM, ALUMINIUM DIAL SCALED 0-100, WINDOW SCALED £2.30, 32mm DIAMETER, 1/2 SPINDLE NEW £1.75p.

**TRANSUDERS,** ULTRASONIC MADE BY MURATA 40KHZ £2.95 pair. (15mm DIAM).


**SWITCHES;** MIN TOGGLE, SPST 8 x 5 x 7mm 45p, DPDT 8 x 7 x 7mm 50p. DPDT CENTRE OFF 12 x 11 x 9mm 75p. MIN. PUSH TO MAKE OR PUSH TO MAKE OR PUSH TO BREAK 16 x 6mm 15p EACH TYPE, 10 AMP ROCKER SWITCHES SPST 12p, SLIDER SWITCHES; DPDT MIN. 12p, DPDT COFF 30p, 4P2W 30p.

**MICRO SWITCHES;** STANDARD SIZE ROLLER ACTION 15p, MIN. 13 x 10 x 4mm 20p. PLESSLEY WINKLER SWITCHES, 1 POLE 30 WAY 2 BANK ADJUSTABLE STOP 75p.

**TERMS:** CASH WITH ORDER (OR OFFICIAL ORDER FROM COLLEGES ETC.). POSTAGE 30p. OVERSEAS POST AT COST. V.A.T. INCLUDED IN ALL PRICES. S.A.E. FOR LISTS.

**ORDER ADDRESS**  
PROGRESSIVE RADIO, 31, CHEAPSIDE, LIVERPOOL. 2 Tel: 051 236 0982

**THIS is the Catalogue you need to solve your component buying problems!**



- The finest components catalogue yet published.
- Over 200 A-4-size pages.



# WATFORD ELECTRONICS

33/35, CARDIFF ROAD, WATFORD, HERTS, ENGLAND  
MAIL ORDER, CALLERS WELCOME. Tel. Watford 40588/9

**ALL DEVICES BRAND NEW, FULL SPEC. AND FULLY GUARANTEED. ORDERS DESPATCHED BY RETURN OF POST. TERMS OF BUSINESS: CASH/CHEQUE/P.O. OR BANKERS DRAFT WITH ORDER. GOVERNMENT AND EDUCATIONAL INSTITUTIONS OFFICIAL ORDERS ACCEPTED. TRADE AND EXPORT INQUIRY WELCOME. P. & P. ADD 50p TO ALL ORDERS UNDER £10.00. OVERSEAS ORDERS POSTAGE AT COST.**

**VAT** Export orders no VAT. Applicable to U.K. Customers only. Unless stated otherwise, all prices are exclusive of VAT. Please add 8% to devices marked \*. To the rest add 12.1%.

We stock many more items, it pays to visit us. We are situated behind Watford Football Ground, nearest Underground/Br. Rail Station, Watford High Street. Open Monday to Saturday 9 a.m.-8 p.m. Ample Free Car Parking space available.

**POLYESTER CAPACITORS:** Axial lead type. (Values are in  $\mu$ F).  
0.001, 0.0015, 0.0022, 0.0033  $\mu$ F; 0.0047, 0.0058, 0.01, 0.015  $\mu$ F; 0.022, 0.033, 0.047, 0.068, 0.1  $\mu$ F; 0.15, 0.22, 0.33, 0.47, 0.58, 0.75, 1.0  $\mu$ F; 1.5, 2.2, 3.3, 4.7, 5.8, 7.5, 10, 15, 22, 33, 47, 58, 75, 100, 150, 220, 330, 470, 580, 750, 1000, 1500, 2200, 3300, 4700, 5800, 7500, 10000, 15000, 22000, 33000, 47000, 58000, 75000, 100000, 150000, 220000, 330000, 470000, 580000, 750000, 1000000, 1500000, 2200000, 3300000, 4700000, 5800000, 7500000, 10000000, 15000000, 22000000, 33000000, 47000000, 58000000, 75000000, 100000000, 150000000, 220000000, 330000000, 470000000, 580000000, 750000000, 1000000000, 1500000000, 2200000000, 3300000000, 4700000000, 5800000000, 7500000000, 10000000000, 15000000000, 22000000000, 33000000000, 47000000000, 58000000000, 75000000000, 100000000000, 150000000000, 220000000000, 330000000000, 470000000000, 580000000000, 750000000000, 1000000000000, 1500000000000, 2200000000000, 3300000000000, 4700000000000, 5800000000000, 7500000000000, 10000000000000, 15000000000000, 22000000000000, 33000000000000, 47000000000000, 58000000000000, 75000000000000, 100000000000000, 150000000000000, 220000000000000, 330000000000000, 470000000000000, 580000000000000, 750000000000000, 1000000000000000, 1500000000000000, 2200000000000000, 3300000000000000, 4700000000000000, 5800000000000000, 7500000000000000, 10000000000000000, 15000000000000000, 22000000000000000, 33000000000000000, 47000000000000000, 58000000000000000, 75000000000000000, 100000000000000000, 150000000000000000, 220000000000000000, 330000000000000000, 470000000000000000, 580000000000000000, 750000000000000000, 1000000000000000000, 1500000000000000000, 2200000000000000000, 3300000000000000000, 4700000000000000000, 5800000000000000000, 7500000000000000000, 10000000000000000000, 15000000000000000000, 22000000000000000000, 33000000000000000000, 47000000000000000000, 58000000000000000000, 75000000000000000000, 100000000000000000000, 150000000000000000000, 220000000000000000000, 330000000000000000000, 470000000000000000000, 580000000000000000000, 750000000000000000000, 1000000000000000000000, 1500000000000000000000, 2200000000000000000000, 3300000000000000000000, 4700000000000000000000, 5800000000000000000000, 7500000000000000000000, 10000000000000000000000, 15000000000000000000000, 22000000000000000000000, 33000000000000000000000, 47000000000000000000000, 58000000000000000000000, 75000000000000000000000, 100000000000000000000000, 150000000000000000000000, 220000000000000000000000, 330000000000000000000000, 470000000000000000000000, 580000000000000000000000, 750000000000000000000000, 1000000000000000000000000, 1500000000000000000000000, 2200000000000000000000000, 3300000000000000000000000, 4700000000000000000000000, 5800000000000000000000000, 7500000000000000000000000, 10000000000000000000000000, 15000000000000000000000000, 22000000000000000000000000, 33000000000000000000000000, 47000000000000000000000000, 58000000000000000000000000, 75000000000000000000000000, 100000000000000000000000000, 150000000000000000000000000, 220000000000000000000000000, 330000000000000000000000000, 470000000000000000000000000, 580000000000000000000000000, 750000000000000000000000000, 1000000000000000000000000000, 1500000000000000000000000000, 2200000000000000000000000000, 3300000000000000000000000000, 4700000000000000000000000000, 5800000000000000000000000000, 7500000000000000000000000000, 10000000000000000000000000000, 15000000000000000000000000000, 22000000000000000000000000000, 33000000000000000000000000000, 47000000000000000000000000000, 58000000000000000000000000000, 75000000000000000000000000000, 100000000000000000000000000000, 150000000000000000000000000000, 220000000000000000000000000000, 330000000000000000000000000000, 470000000000000000000000000000, 580000000000000000000000000000, 750000000000000000000000000000, 1000000000000000000000000000000, 1500000000000000000000000000000, 2200000000000000000000000000000, 3300000000000000000000000000000, 4700000000000000000000000000000, 5800000000000000000000000000000, 7500000000000000000000000000000, 10000000000000000000000000000000, 15000000000000000000000000000000, 22000000000000000000000000000000, 33000000000000000000000000000000, 47000000000000000000000000000000, 58000000000000000000000000000000, 75000000000000000000000000000000, 100000000000000000000000000000000, 150000000000000000000000000000000, 220000000000000000000000000000000, 330000000000000000000000000000000, 470000000000000000000000000000000, 580000000000000000000000000000000, 750000000000000000000000000000000, 1000000000000000000000000000000000, 1500000000000000000000000000000000, 2200000000000000000000000000000000, 3300000000000000000000000000000000, 4700000000000000000000000000000000, 5800000000000000000000000000000000, 7500000000000000000000000000000000, 10000000000000000000000000000000000, 15000000000000000000000000000000000, 22000000000000000000000000000000000, 33000000000000000000000000000000000, 47000000000000000000000000000000000, 58000000000000000000000000000000000, 75000000000000000000000000000000000, 100000000000000000000000000000000000, 150000000000000000000000000000000000, 220000000000000000000000000000000000, 330000000000000000000000000000000000, 470000000000000000000000000000000000, 580000000000000000000000000000000000, 750000000000000000000000000000000000, 1000000000000000000000000000000000000, 1500000000000000000000000000000000000, 2200000000000000000000000000000000000, 3300000000000000000000000000000000000, 4700000000000000000000000000000000000, 5800000000000000000000000000000000000, 7500000000000000000000000000000000000, 10000000000000000000000000000000000000, 15000000000000000000000000000000000000, 22000000000000000000000000000000000000, 33000000000000000000000000000000000000, 47000000000000000000000000000000000000, 58000000000000000000000000000000000000, 75000000000000000000000000000000000000, 100000000000000000000000000000000000000, 150000000000000000000000000000000000000, 220000000000000000000000000000000000000, 330000000000000000000000000000000000000, 470000000000000000000000000000000000000, 580000000000000000000000000000000000000, 750000000000000000000000000000000000000, 1000000000000000000000000000000000000000, 1500000000000000000000000000000000000000, 2200000000000000000000000000000000000000, 3300000000000000000000000000000000000000, 4700000000000000000000000000000000000000, 5800000000000000000000000000000000000000, 7500000000000000000000000000000000000000, 100, 15000000000000000000000000000000000000000, 22000000000000000000000000000000000000000, 33000000000000000000000000000000000000000, 47000000000000000000000000000000000000000, 58000000000000000000000000000000000000000, 75000000000000000000000000000000000000000, 1000, 1500, 2200, 3300, 4700, 5800, 7500, 100, 15000, 22000, 33000, 47000, 58000, 75000, 1000, 1500, 2200, 3300, 4700, 5800, 7500, 100, 15000, 22000, 33000, 47000, 58000, 75000, 1000, 1500, 2200, 3300, 4700, 5800, 7500, 100, 15000, 22000, 33000, 47000, 58000, 75000, 1000, 1500, 2200, 3300, 4700, 5800, 7500, 100, 15000, 22000, 33000, 47000, 58000, 75000, 1000, 1500, 2200, 3300, 4700, 5800, 7500, 100, 15000, 22000, 33000, 47000, 58000, 75000, 1000, 1500, 2200, 3300, 4700, 5800, 7500, 100, 15000, 22000, 33000, 47000, 58000, 75000, 1000, 1500, 2200, 3300, 4700, 5800, 7500, 100, 15000, 22000, 33000, 47000, 58000, 75000, 1000, 1500, 2200, 3300000000





Head Office and Warehouse  
44A WESTBOURNE GROVE  
LONDON W2 5SF  
Tel: 727 5641/2/3

# Z & I AERO SERVICES LTD.


Retail Shop  
85 TOTTENHAM COURT ROAD  
LONDON W1  
Tel: 580 8403  
Open all day Saturday

Please send all correspondence and Mail-Orders to Head Office

## A SELECTION FROM OUR STOCKS OF FULLY GUARANTEED FIRST QUALITY VALVES

1B3GT 0.45	6AK6 0.75	6CW4 3.75	12BA6 0.45	ECL80 0.40	EZ80 0.50	PCL805 0.75
1R4 0.50	6AK7 0.85	6CY5 1.00	12BE6 0.80	ECL81 0.75	GY501 0.90	PD510 3.35
1R5 0.50	6AL5 0.40	6CY7 1.00	12BH7A 0.75	ECL82 0.40	GZ300 0.45	PL36 1.10
1S4 0.40	6AM6 0.70	6DQ6B 1.45	12BY7A 0.80	ECL83 1.15	GZ32 0.45	PL81 0.80
1S5 0.40	6AM8 0.70	6DT6 0.80	35W4 0.70	ECL84 0.70	KT66 4.50	PL83 0.55
1T4 0.40	6AN5 2.50	6GH8A 0.80	50C5 1.00	ECL85 0.45	KT88 5.80	PL84 0.75
1U4 0.70	6AN6 0.85	6GK5 0.70	*75C1 0.80	ECL86 0.85	OA2 0.55	PL95 0.70
1U5 0.80	6AQ5 0.85	6J4 1.20	*85A2 0.85	EF80 0.40	OA3 0.75	PL504 1.05
1X2B 1.20	6AR5 0.70	6J5GT 0.80	*90C1 1.20	EF85 0.48	OB2 0.60	PL508 1.30
2CW4 4.50	6AS6 1.00	6J6 0.55	*807 1.00	EF86 0.60	OB3 0.75	PL802 2.80
*20Z1 0.80	6AS7G 1.20	6J7 0.80	*81A 3.80	EF92 0.75	OC2 1.40	PY81 0.70
*3-500Z 40.00	6AT6 0.75	6K6GT 0.85	*829B 8.80	EF97 0.70	OC3 0.75	PY82 0.55
*3E29 8.50	6AU6 0.50	6L6GT 0.85	*832A 8.20	EP98 0.90	OD3 0.75	PY83 0.70
3Q4 0.75	6AV6 0.75	6N7GT 0.85	*866A 3.00	EF183 0.70	FABC80 0.45	PY88 0.75
3S4 0.50	6AW8A 0.75	6Q7 0.90	*872A 6.00	EF184 0.70	PC86 0.85	PY500A 1.30
5AQ5 0.75	6AX4GTB 1.00	6SA7 0.80	*5763 2.85	EFL200 1.20	PC88 0.85	TT21 7.80
5AT8 0.80	6AX5GT 1.30	6S67 0.80	DAP96 0.60	EH90 0.60	PC92 0.85	TT22 7.80
5T4 0.75	6BA6 0.45	6SK7 0.80	DF96 1.00	EL34 0.95	PC95 0.70	UZ5 1.00
5U4G 0.40	6BE6 0.48	6SL7GT 0.70	DK92 1.40	EL36 0.95	PC96 0.50	UZ6 1.00
5U4GB 0.95	6BF5 0.85	6SN7GT 0.70	DL96 0.60	EL81 0.45	PC97 0.95	UABC80 0.58
5U8 0.75	6BF6 0.75	6S07 0.80	ECC84 0.60	EL82 0.60	PC900 1.00	UBC81 0.60
5V4G 0.40	6BH6 0.85	6V6GT 0.45	ECC85 0.40	EL83 0.60	PC84A 0.50	UBF89 0.60
5X4G 0.80	6BJ6 1.20	6X4 0.60	ECC86 1.25	EL84 0.45	PC85 0.40	UBL21 0.85
5X8 0.90	6BN6 0.80	6XS2GT 0.40	ECC88 0.75	EL86 0.75	PC88 0.45	UCC84 0.75
5Y3GT 0.45	6BQ7A 0.65	12AC6 0.80	ECC89 0.80	EL95 0.70	PC89 0.70	UCC85 0.55
5Z4GT 0.65	6BR8A 1.20	12AD6 0.80	ECC189 0.80	EL504 0.80	PC189 1.00	UCF80 0.75
6AB4 0.55	6BU8 0.85	12AE6 0.85	ECF80 0.60	EM80 0.65	PCF80 0.65	UCF81 0.45
6AB7 0.60	6BW7 1.00	12AT6 0.40	ECF86 0.80	EM81 0.60	PCF82 0.45	UCL81 0.70
6AC7 0.80	6BZ6 0.65	12AT7 0.50	ECF200 0.90	EM84 0.60	PCF84 0.65	UCL82 0.75
6AF4A 0.80	6BZ7 0.70	12AU6 0.65	ECF201 0.90	EM87 1.00	PCF201 1.10	UCL83 0.80
6AG5 0.65	6C4 0.55	12AU7 0.45	ECF801 0.95	EY51 0.40	PCF806 1.00	UF85 0.50
6AG7 0.85	6CB6 0.55	12AV6 0.85	ECF802 0.95	EY81 0.80	PCL81 0.65	UL84 0.85
6AH6 0.95	6CS7 0.85	12AY7 1.00	ECF803 0.55	EY82 0.50	PCL82 0.80	UM80 0.60
6AJ5 0.85	6CU5 1.00	12AX7 0.55	ECH83 0.60	EY88 0.55	PCL84 0.75	UM81 0.75
6AK5 0.55	6CU6 1.00	12AY7 0.85	ECH200 0.80	EY500A 1.50	PCL86 0.85	UM84 0.45
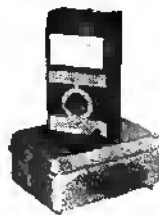
## AC/DC TAUT SUSPENSION MULTIMETERS TYPE U4315



Sensitivity D.C. 20,000 o.p.v.  
Sensitivity A.C. 2,000 o.p.v.  
D.C. Current 50µA-2.5A  
A.C. Current 0.5mA-2.5A  
D.C. Volts 75mV-1000V  
A.C. Volts 1V-1000V  
Resistance 300Ω-500kΩ  
Capacity 0.5µF  
Accuracy 2.5% D.C., 4% A.C.

Price complete with pressed steel carrying case and test leads. £15.85\*  
Packing & postage £1.50\*

VAT is not included. Please add 12½% on all items except those marked with asterisk, on which VAT is 8%. Postage and packing charges are £0.10 per £ subject to a minimum of £0.30.

OUR NEW 1977/1978 CATALOGUE IS NOW READY AND WILL BE SENT ON RECEIPT OF REMITTANCE FOR £0.30

# ELECTROVALUE

All the many types of components we supply are BRAND NEW and guaranteed and only from manufacturers direct or approved suppliers. (No surplus, no seconds)

### CMOS—buffered and protected (BE)

4050 23p	4013 51p	4023 23p	4043 1.00	4081 23p
4091 23p	4014 0.07	4024 1.04	4044 94p	4092 26p
4092 23p	4015 1.14	4025 23p	4046 1.40	4510 1.42
4096 1.14	4016 51p	4026 1.75	4049 84p	4511 1.90
4097 23p	4017 1.14	4027 60p	4050 53p	4514 3.30
4098 99p	4018 1.32	4028 99p	4060 1.40	4516 1.44
4099 62p	4019 62p	4029 1.33	4069 30p	4518 1.26
4010 62p	4020 1.33	4030 51p	4070 30p	4520 1.36
4011 23p	4021 1.14	4031 84p	4071 26p	4543 1.90
4012 23p	4022 1.13	4032 99p	4072 26p	4583 1.49

### OUR COMPUTER TAKES GOOD CARE OF YOUR ORDERS

#### SIEMENS CAPACITORS\*

World-famous for quality and dependability—exceptionally large stocks held.  
PCB TYPES—7.5mm PCM 0.001 to 0.01 5p each; 0.15 to 0.047 4p each; 0.068, 0.1 7p each.

GERMIC—2.5mm PCM 0.01, 0.022 4p; 0.033, 0.047 5p each; 0.068 6p 5mm PCM 0.1 7p; 0.22 10p.

#### ELECTROLYTICS—1/100, 10/25, 10/63, 100/25, etc., etc.

For full range see our current lists.

#### RESISTORS

½, ¼, ⅓ watts—2p each\*: metal film, metal oxide and 1 watt carbon 5p each\*: Good quantity discounts. Magnetic field dependent from £1.50. Hall effect from £1.23.

#### SIEMENS TRANSISTORS

Silicon npn and pnp from 8p each; LEDs, red 19p; yellow or green 23p (3 or 5mm); Photo transistors from 76p.

### KEEN PRICES • GOOD SERVICE • WIDE RANGES

#### DISCOUNTS

3% if list value of order over £10  
10% if list value of order over £25  
Discounts available where cash, P.O. or cheque is sent with order.

#### V.A.T.—Add 8% to value of order or 12½% with items marked\*.

(No V.A.T. on overseas orders). Goods sent post free on C.W.O. orders in U.K. over £5 list value. If under, add 27p per order.

#### MONTHLY BARGAIN LISTS S.A.E. brings monthly list of bargains.

Also current quick reference price list of all ranges.

Cash with order (P.O. or cheque payable to Electrovalue Ltd) or your Access or Barclaycard number.

#### TRADE AND INDUSTRIAL ENQUIRIES INVITED

For all round satisfaction—be safe—buy it from ELECTROVALUE

# ELECTROVALUE LTD

Dept PW7, 28 St. Judes Rd, Englefield Green, Egham, Surrey TW20 6HB.  
Phone Egham 3603; Telex 264475  
Northern Branch (Personal shoppers only) 680 Burnage Lane, Burnage, Manchester M19 1NA. Phone (061) 432 4945.

### TV GAMES

TV games mains adaptor 9V 100ma stabilized £3.75. Fully assembled attractively cased TV games (tennis, football, squash and polo)—black and white £11.95. Colour £22.95. Also 6 game colour model with pistol attachment £21.95. Modified shoot kit £4.95. Stunt motor cycle game chip + economy kit £17.95. Tent battle game chip + economy kit £17.95. AY-3-8500 £4.95. Kits for AY-3-8500—black and white standard model £8.95. Economy version £4.95. Colour model standard £17. Economy colour £12.45. Rifle kit £4.95. Colour generator kit, adds colour to most games £7.50. Send see for details.

### COMPONENTS

Plastic versions of BC108/9 5p. 2N3055B 37p. 1N4148 23p. 1N4002 3p. Resistors 5% carbon £12.10 to 10M. 3W 0.8p. 1W 2p. Preset pots sub-miniature 0.1W horiz or vert 100 to 4M 8p.

Pentodes/meters 1W 4K7 to 2M2 log or lin. Single 25p. Dual 75p. Polyester capacitors 250V DC 10 to 0.088mF 2p. 0.1mF 2p. 15mF 5p. 22mF 4p. .33, 47mF 8p. Poly-styrene capacitors £12 63V 15pF to 6800pF 21p. Ceramic capacitors 50V £12 220pF to 1000pF 2p. £5 1000pF to 6800pF 2p. Mylar capacitors 100V .001, .002, .005mF 4p. 0.1, 0.02mF 4p. .04, .05mF 5p. Electrolytic 50V .47, 1.2mF 5p. 25V 6mF 5p. 10mF 4p. 18V 22mF 5p. 33, 47, 100mF 6p. 220, 330mF 5p. 470mF 11p. 1000mF 8p. Zeners 400mV £24.2V to 35V 75p.

### MAINS TRANSFORMERS

0-0-0V 100ma 75p. 0-0-0V 75ma 84p. 12-0-12V 50ma 75p. 13V 1A 85p. 0.3 1A £1.85. 0-0-0V 1A £2.35. 0-0-0V 1A £1.85. 12-0-12V 100ma 99p. 12-0-12V 1A £2.48. 18-0-18V 1A £2.78. 30-0-30V 1A £2.39. 0-0-0V 2A £2.84.

### PRINTED CIRCUIT MATERIALS

PC etching kits—economy £1.79, standard £2.82. 50 sq in pcb 40p 1 lb FeCl £1.05. Etch resist pens—economy 45p, dial 75p. Small drill bit 20p. Etching dish 99p. Laminator cutter 75p.

### S-DECS AND T-DECS\*

S-DeC £2.23. T-DeC £3.99. 0-DeCA £3.97. 0-DeCB £6.67. 16 di0 or 10T05 adaptors—with socket £1.81. Plain 99p. New S-dec £4.99.

### SINCLAIR PRODUCTS\*

PDMS5 digital multimeter £25.95. Mains adaptor £3.24. Deluxe padded carry case £3.25. 30kV probe £18.38. Cambridge scientific programmable calculator £15.13. Prog. library £4.95. Mains adaptor £3.20. Cambridge scientific £3.43.

### JC12, JC28 AND JC48 AMPLIFIERS

A range of integrated circuit audio amplifiers supplied with free data and printed circuits. JC12 6 watts £1.99. JC20 10 watts £2.95. JC40 20 watts £4.22. Send see for free data on our range of matching power and preamp kits.

### FERRANTI 2N414

IC radio chip £1.95. Extra parts and pcb for radio £3.85 Case £1. Send see for free data.

### BATTERY ELIMINATOR BARGAINS

TV games power unit stabilized 7-7V 100ma £2.10. 3-way model with switched output and 4-way multi-jack—3/44/6V 100ma £2.92. 6/73/9V 300ma £3.30. 100ma radio model same size as a PP9 battery, with press stud connectors. 9V £2.85. 9V £2.85. 41V £2.85. 9V + 9V £2.85. 9V + 6V £4.58. 41V + 41V £4.58. Cassette recorder mains unit 71V 100ma with 5 pin di0 plus £2.85. Fully stabilized model switched output 3/6/73/9V 400 ma £6.40. Car converters 12V dc input. Output 9V 300ma £1.50. Output 71V 300ma £1.98.

### BATTERY ELIMINATOR KITS

Send see for free leaflet on range. 100ma radio types with press stud connectors. 41V £1.98. 9V £1.98. 9V + 41V £2.98. 9V + 9V £2.98. 9V + 9V £2.98. Cassette type 71V 100ma with di0 plus £1.98. Transistor stabilized 8-way types for low hum 3/41/6/73/9/12/15/18V. 100ma £3.20. 1 Amp £4.40. Heavy duty 13 way types 4/6/7/9/11/13/14/17/21/25/28/34/42V 1 Amp £4.95. 2 Amp £7.25. Car converter kit input 12V dc. Output 6/73/9V 1A stabilized. Stabilized power kits 3-18V 100ma £3.86. 3-30V 1A £3.95. 3-30V 2A £14.95.

### BULK BUY OFFERS

Minimum purchase £18 any mix from this section only. AC76923N exact equiv. of SN70023N with improved heat sink 75p. ZN414 4p. 4.3MHz PAL crystals 45p. 741 8 di0 20p. NE555 8 di0 20p. dialo pane 58p. Plastic equiv. of BC108/9 3-6p/8-4p. 2N3055 27p. 1N4148 1-9p. BD131 19p. BC107 7p. BC129 7p. BC122 8p. 4-2p. 25V polyester caps .01mF 1.1p. .068mF 1.4p. .1mF 1.5p. .33mF 2.2p. 3W resistors 5% £12 1 to 10M 0.8p. Zener diodes 400mV E24 3V3 50 33V 3p.

### SI-PAK AUDIO MODULES

New low prices. 3450 tuner £21.95. AL80 £4.84. PA100 £15.95. MK80 audio kit £26.45. Stereo 30 £16.78. SPM80 £3.67. BMT £5.95. Send see for free data.

### SWANLEY ELECTRONICS

DEPT. PW. PO Box 44, 32 Gosden Rd., Swanley, Kent BR8 8TQ  
Mail order only. Please add 30p to the total cost of order for postage. Prices include VAT. Overseas customers deduct 7% on items marked \* and 11% on others. Official credit orders welcome.

Published on approximately the 7th of each month by IPC Magazines Limited, Westover House, West Quay Road, FOLKE, Dorset BH13 1JG. Printed in England by Index Printers, Dunstable, Beds. Sole Agents for Australia and New Zealand—Gordon and Ootoh (Asia) Ltd., South Africa—Central News Agency Ltd. Subscriptions INLAND and OVERSEAS £10.00 payable to IPC Services, Oakfield House, Ferryport Road, Haywards Heath, Sussex. PRACTICAL WIRELESS is sold subject to the following conditions, namely that it shall not, without the written consent of the Publishers first having been given, be lent, resold, hired out or otherwise disposed of by way of Trade at more than the recommended selling price shown on the cover, excluding Birc where the selling price is subject to V.A.T., and that it shall not be lent, resold, hired out or otherwise disposed of in a mutilated condition or in any unauthorised cover by way of Trade or affixed to or as part of any publication or advertising, literary or pictorial matter whatsoever.

# U.K. RETURN OF POST MAIL-ORDER SERVICE ALSO WORLD WIDE EXPORT SERVICE

## R.C.S. 100 watt MIXER/AMPLIFIER ALL VALVE



Four inputs. Four way mixing, master volume, treble and bass controls. Built all speakers. This professional quality amplifier chassis is suitable for all groups, disco, P.A., where high quality power is required. 5 speaker outputs. A/C mains operated. Slave output. Produced by demand for a quality valve amplifier. Send for details.

Chassis only £94 carr. £5

## CASSETTE TAPE TRANSPORT MECHANISM

Complete with mono record/playback and erase heads. Five push buttons, record, play, forward, rewind and pause.

Less motor, brand new £3-50 Post 50p.



## 10" ELAC HI-FI SPEAKER

Large ceramic magnet. Response: 60-18,000 cps. Bass resonance 55 cps. 16 ohm impedance. 10 watts. Post 40p

£4-50

## TEAK VENEER HI-FI SPEAKER CABINETS

MODEL "A", 20 x 13 x 12in. For 12in. dia. or 10in. speaker. £14-50 Post £1-00 Illustrated.

MODEL "B" BOOKSHELF For 12 x 8in. or 8in. speaker. £8-50 Post £1

MODEL "C" BOOKSHELF For 8in. and tweeter. £5-95 post 75p

LOUDSPEAKER CABINET WADDING 18in. wide, 20p ft.

## GOODMANS CONE TWEETER

3 1/2in. diam., 18,000 C.P.S. 25 WATTS 8 Ω £3-25  
8in. EMI mid range £5  
10in. 30 watt GOODMANS woofer 4 ohm £10-95.  
ELAC TWEETER 4 ohm 20 watt £2-50

BARGAIN 4 CHANNEL TRANSISTOR MONO MIXER. Add musical highlights and sound effect to recordings. Will mix Microphone, records, tape and tuner with separate controls into single output. 9 volt battery £6-75 operated.

TWO CHANNEL STEREO VERSION OF ABOVE £8 50

BARGAIN 3 WATT AMPLIFIER. 4 Transistor Push-Pull Ready built with volume, treble and bass controls. 18 volt battery operated or Mains Supply £2 95.

THE "INSTANT" BULK TAPE ERASER & HEAD DEMAGNETISER Suitable for cassettes, and all sizes of tape reels. A.C. mains 200/240V. Lead Set S.A.E. £4-95 Post 60p

## ELECTRIC MOTORS

2 Pole, 240V. 2 Amp. Spindle 1.43 0-212in. £1.75.  
8 x 5in. £1.40; 10 x 7in. £1.55; 14 x 8in. £1.80; 18 x 8in. £1.95;  
12 x 5in. £1.20; 16 x 10in. £2.20; 12 x 8in. £1.70.  
ALUMINIUM PANELS. 18 s.w.g. 6 x 4in. 20p; 8 x 5in. 40p;  
10 x 7in. 50p; 12 x 5in. 50p; 12 x 8in. 50p; 16 x 6in. 75p;  
14 x 9in. 80p; 12 x 12in. 80p; 16 x 10in. 85p.  
ALUMINIUM ANGLE BRACKET 9 x 7 x 3/4 in. 15p.  
ALUMINIUM BOXES. MANY SIZES IN STOCK.  
4 x 2 x 2in. 85p; 3 x 2 in. 60p; 3 x 4 x 2in. £1; 8 x 2in. £1.80; 8 x 4 x 2in. £2.12; 4 x 4 x 2in. £2.40.

## DE LUXE BSR HI-FI AUTOCHANGER

Plays 12in, 10in, or 7in. records Auto or Manual. A high quality unit backed by BSR reliability with 12 months guarantee. A.C. 200/250V. Size 13 1/2 x 11 1/2in. Above motor board 3 1/2in. Below motor board 2 1/2in.



£21-50

WITH MAGNETIC STEREO CARTRIDGE Cuenk Device, Bias Compensator, Balanced Arm, All Post 75p

## NEW DECKS

BSR MP80/F123 with Goldring G850 magnetic cartridge. £24-50  
BSR Budget Autochanger with ceramic cartridge. £18-95  
Gerrard AP76. Single player less cartridge. £28-50  
BSR P163. Belt drive Turntable, less cartridge £27-50  
Gerrard 5300. Autochanger with ceramic cartridge. £14-95  
Gerrard Minichanger. Plays all size records. Ceramic cartridge. £9-95  
BSR P132. Snake arm, Bared turntable, ceramic cartridge. £19-95

## BAKER MAJOR 12" £15-00



Post £1  
80-14,500 c/s. 12in. double cone, woofer and tweeter cone together with a BAKER ceramic magnet assembly having a flux density of 14,000 gauss and a total flux of 146,000 Maxwells. Bass resonance 40 cps rated 25 watts. NOTE: 4 or 8 or 16 ohms must be stated.

## MAJOR MODULE KIT

Post £1-00  
30-17,000 c/s with tweeter, crossover, baffles 18 x 12 1/2in. Price £19-00  
Plate 4 or 8 or 16 ohms.

## BAKER SPEAKERS "BIG SOUND"

Robustly constructed to stand up to long periods of electronic power. As used by leading groups. Useful responses 30-13,000 cps. Bass resonance 55 cps.

### GROUP "25"

12in. 30 watt 4, 8 or 16 ohms.

£12-00

Post £1

### GROUP "35"

12in. 40 watt 4, 8 or 16 ohms.

£14-00

Post £1

### GROUP "50/12"

12in. 60 watt professional model. 4, 8 or 16 ohms.

£21-00

Post £1-00

Response = 30 - 16,000 cps.

With aluminium presence dome.

### GROUP "50/15"

15in. 75 watt 8 or 16 ohms.

£26-00

Post £1 80

Send for leaflets on Disco, P.A. and Group Gear.

## BAKER 150 WATT QUALITY TRANSISTOR MIXER/AMPLIFIER



Professional amplifier using advanced circuit design. Ideal for disco, groups, P.A. or musical instruments. 4 inputs 4 way mixing. Master treble, bass and volume controls. 3 speaker output sockets to suit various combinations of speakers. 4-5-16 ohm. Slave output. A/C mains. Guaranteed. Details S.A.E. £75 Carr. £1-60

## 100 WATT DISCO AMPLIFIER

MADE BY JENNINGS MUSICAL INSTRUMENTS £59 Carr. £1  
4 Speaker outputs volume, treble, bass, controls CAN BE USED AS 100 WATT SLAVE

## B.S.R. SINGLE PLAYER DECK

3 speed. Plays all size records, Stereo Cartridge, Cueing device, Ideal Disco Deck. £15-50 Post 75p



DRILL SPEED CONTROLLER/LIGHT DIMMER KIT. Easy to build kit. Will control up to 600 watts AC mains. £3-25 Post 35p

STEREO PRE-AMP KIT. All parts to build this pre-amp. 3 inputs for high medium or low gain per channel, with volume control and P.C. Board. Can be ganged to make multi-way stereo mixers. £2-95 Post 35p

## R.C.S. SOUND TO LIGHT DISPLAY MK 2

Complete kit of parts with R.C.S. printed circuit. Three channels. 600 to 1,000 watts each. Will operate from 200V. to 100 watts signal source. Suitable for home use. Cabinet extra £4. Price £17

200 Watt Rear Reflecting White Light Bulbs. Ideal for Disco Lights. Edison Screw Fitting 75p. Each.

## MAINS TRANSFORMERS

Post 50p  
6 VOLT 1 AMP. £1-00 3 AMP. £1-95 9 VOLT 3 AMP. £2-75  
12 VOLT 200 MA. £1-00 750 MA. £1-80  
30 VOLT 5 AMP. AND 34 VOLT 3 AMP. C.T. £3-46  
50 VOLT 1 AMP. £2-00 20-0-20 VOLT 1 AMP. £2-95  
50 VOLT 1.5 AMP. £2-50 40 VOLT 2 AMP. £2-95  
0-20-40-00 VOLT 1 AMP. £3-50 2 x 18 VOLT 5 AMP. 2p.

GENERAL PURPOSE LOW VOLTAGE. Voltages available at  
2A, 2.5, 5, 6, 8, 9, 10, 12, 15, 18, 24 and 30V £0-50  
1A, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 £0-50  
2A, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 £2-80  
3A, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 £21-00  
5A, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 £24-50

## R.C.S. BOOKSHELF SPEAKERS

13 x 10 x 6in. 50 to 14,000 cps. 12 watts rms. 8 ohms £19 pair Post £1-50

## BAKER DISCO SPEAKERS HIGH QUALITY-BRITISH MADE 2 x 12" CABINETS

For Disco or PA all fitted with carrying handles and corners. Black vinyl covered. Other cabinets in stock. SAE for leaflet

### 60 WATT R.M.S. £52

With one horn £60

With two horns £68 Carr. £3

### 80 WATT R.M.S. £56

With one horn £64

With two horns £72 Carr. £3

### 100 WATT R.M.S. £69

With one horn £78

With two horns £86 Carr. £6

## SINGLE 12inch CABS COMPLETE

30 WATT R.M.S. £32. WITH HORN £40.

40 WATT R.M.S. £34. WITH HORN £42.

60 WATT R.M.S. £41. WITH HORN £49. CARR £3 EA.

## "SUPERB HI-FI" 12in 25 watts

A high quality loudspeaker. Its remarkable low cone resonance ensures clear reproduction of the deepest bass. Fitted with a special copper drive and concentric tweeter cone resulting in full range reproduction with remarkable efficiency in the upper register. Bass Resonance 25cps Flux Density 15,500 gauss Useful response 20-17,000cps 8 or 16 ohms models.



## "AUDITORIUM" 12in. 35 watts

A full range reproducer for high power. Ideal for Hi-Fi and Discotheques. Electric Guitars, public address, multi-speaker systems, electric organs. Bass Resonance 35cps Flux Density 15,000 gauss Useful response 25-18,000cps 8 or 16 ohms models.



## "AUDITORIUM" 15in. 45 watts

A high wattage loudspeaker of exceptional quality with level response to above 8,000 cps. Ideal for Public Address, Discotheques, Electronic Instruments and the home Hi-Fi. Bass Resonance 35cps Flux Density 15,000 gauss Useful response 20-14,000cps 8 or 16 ohms models.



## £22-00 Post £1 80

## £21-00 Post £1 80

## £26-00 Post £1 80

## £22-00 Post £1 80

## £21-00 Post £1 80

## £26-00 Post £1 80

## £26-00 Post £1 80

## £26-00 Post £1 80

## £26-00 Post £1 80


# RADIO COMPONENT SPECIALISTS

Minimum post 30p. Components List 20p. Cash price includes VAT. Access & Barclay cards welcome. Open 9-6 Wed. 9-1 Sat. 9-5 (Closed for lunch 1.15-2.30) Phone your order Tel. 01-684 1665


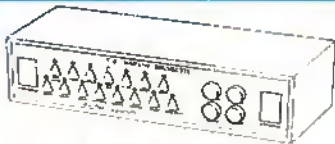
# MAPLIN

everything for the modern D.I.Y. electronics enthusiast and more.




## THE 'DRUMSETTE' RHYTHM GENERATOR

Organists, pianists, guitarists... an automatic drum set to accompany you! Nine highly realistic instruments play fifteen different rhythms. Fifteen rhythm-select touch switches and a touch plate for stop/start without rhythm change gives absolute ease of operation. Build it yourself for under £65 including smart teak-effect cabinet. See it and hear it in our shop! Send for full construction details now: MES49 price 25p. (All prices include V.A.T. and p & p).


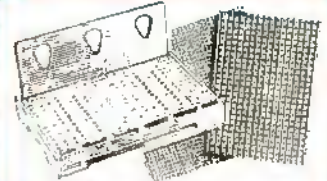
## REVERBERATION SYSTEMS

High quality spring line driver module uses 4 integrated circuits and two transistors. Built and tested circuit board with wiring instructions for spring line. XB85G, price £8.80. Power supply to suit driver module costs around £2.50 and construction details are in catalogue, or ask for leaflet MES24. Mechanical spring lines: Short line (XL06J) £4.49; Long line (XB84F) £10.39. (All prices include V.A.T. and p & p).



## BOARDS AND PCB'S


Pages 59 to 61 of our catalogue show you our range of Veroboards and S-Decs or if you prefer to make your own pcb's a range of etching systems including the novel etch-in-a-bag system, plus printed circuit transfers for the professional finish to your boards.


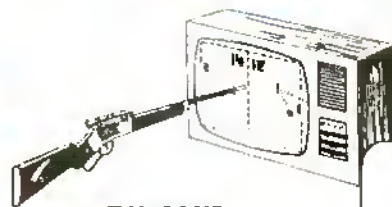
## 9-CHANNEL RADIO CONTROL SYSTEM

A comprehensive model control system, featuring nine independent fully proportional channels achieved by a design using very few components thus keeping the cost to a minimum. Full construction details in our booklet (XF03D)

price £1.20. (All prices include V.A.T. and p & p).



## T.V. GAME

A fascinating TV game kit that plays football, tennis, squash and practice for only £21.59. Reprint of construction details 25p. Add on rifle kit only £10.60. (All prices include V.A.T. and p&p).



## MASSIVE RANGE OF COMPONENTS

For instance the capacitor section in our catalogue includes non-polarised electrolytics and our resistor section includes even 1% tolerance types. Get our fascinating catalogue now—you won't regret it.




## AUDIO MIXER

A superb stereo audio mixer. It can be equipped with up to 16 input modules of your choice and its performance matches that of the very best tape-recorders and hi-fi equipment. It meets the requirements of professional recording studios, FM radio stations, concert halls and theatres. Full construction details in our catalogue. A component schedule is available on request.


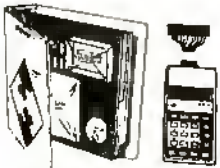
## ELECTRONIC ORGAN

The only organ you can build in stages and tailor to your requirements as you go along—and at each stage you'll have a fully working instrument. We haven't got the gimmicks yet—(they're coming soon) but we have got the most beautiful sounds—you won't find them on any organ less than twice our price. So get our MES50 series leaflets now! 65p buys the three available so far.



## MICROPROCESSOR

Build a mini-computer with our microprocessor kit. Features: 46 different instruction types; 256 bytes of read/write memory (more are easily added); microprocessor can address up to 65,536 8 bit-bytes. Complete kit for use with teletype etc. (XB91Y) £74.10. 20-key keyboard for use with above (in place of teletype) (XB92A) £71.11. Both kits with detailed instruction books. See our newsletters for details of additional RAM's, hi-size interfacing chips, number-cruncher and standard cassette tape-recorder interface to store your programmes. (All prices include V.A.T. and p&p).



Our bi-monthly newsletter keeps you up to date with latest guaranteed prices - our latest special offers - details of new projects and new lines. Send 30p for the next six issues (3p discount voucher with each copy).



POST THIS COUPON NOW FOR YOUR COPY OF OUR CATALOGUE PRICE 60p

Please rush me a copy of your 216 page catalogue I enclose 60p, but understand that if I am not completely satisfied I may return the catalogue to you within 14 days and have my 60p refunded immediately.

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

IT'S A FANTASTIC BESTSELLER!

216 big (11" x 8") pages! Over a thousand illustrations! Over 30 pages of complete projects to build! Thousands and thousands of useful components described and illustrated! No wonder it's a bestseller!

DON'T MISS OUT! SEND 60p NOW!

MAPLIN ELECTRONIC SUPPLIES

P.O. BOX 3 RAYLEIGH ESSEX SS6 8LR  
Telephone: Southend (0702) 715155  
Shop: 284, London Road, Westcliff-on-Sea, Essex

(Closed on Monday) Telephone: Southend (0702) 715157