

# RADIO



# BOOKS

**Tape and Wire Recording.** A selection of articles reprinted from the pages of *The Radio Constructor*, covering both the theory and practical applications. A really useful book on this latest development of the hobby. **2/8**

**Receivers, Presetters and Converters.** Practical articles, again reprinted from past issues of *The Radio Constructor*, which will prove of interest to many radio enthusiasts. **2/8**

**TV Fault Finding.** Profusely illustrated with photographs taken from a television screen depicting the faults under discussion, and containing a wealth of technical information, with circuits, enabling those faults to be eradicated. **5/3**

**Inexpensive Television.** Build yourself a television from surplus. Latest edition includes all the data necessary for any area. **2/8**

**World Radio Handbook (1955 edition).** The S.W. broadcast enthusiasts' handbook. You are missing something from your hobby if you have not a copy of this excellent publication. **9/9**

**Report Pads.** If you need that QSL card, send a comprehensive report. A convenient and accurate form for reporting. **3/9**

**Radio Amateur Operator's Handbook.** An indispensable aid to the amateur transmitter and listener, containing all details of information which are constantly required. Prefix Lists, Zone Boundaries, Call Areas, Codes, and Mileage Tables, together with Maps and much other useful operating data. Revised edition. **3/2**

**Inexpensive Car Radio.** In which two versions, one constructed from surplus and one from new components, are described. **1/8**

**Radio Control for Model Ships, Boats and Aircraft,** by F. C. JUDD, G2BCX. A comprehensive work on this fascinating subject. **Standard edition, 8/9**  
**Cloth bound edition, 11/9**

*All above prices include postage and packing*

All available from your local bookseller, or from

**DATA PUBLICATIONS LTD**

**57 MAIDA VALE LONDON W9**

Telegrams Databux London Telephone CUNNINGHAM 6141 (2 lines)

Printed in Great Britain for the Proprietors and Publishers Data Publications Ltd., 57 Maida Vale, London, W9, by A. Quick & Co. Ltd., Oxford House, Clacton-on-Sea, Essex. Is obtainable abroad through the following: Continental Publishers & Distributors Ltd., William Dawson & Sons Ltd., Australia and New Zealand; Gordon & Brech Ltd., South Africa; Central News Agency, U.S.A.; Gillier Associates, Holland; Radio Electronica, Scandinavia; Nurapress. Registered for transmission by Magazine Post to Canada (Including Newfoundland).

# The RADIO Constructor




FOR THE RADIO AND TELEVISION ENTHUSIAST

VOLUME 9

NUMBER 3

OCTOBER 1955
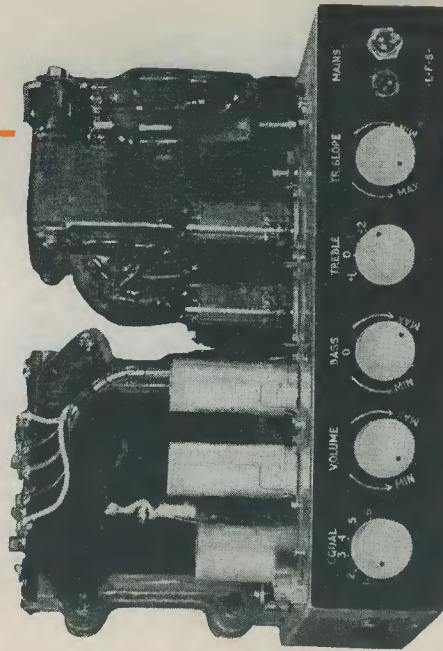
## HIGH QUALITY 10 WATT ULTRA-LINEAR AMPLIFIER



by  
L. F. SINFIELD

Also in this issue  
PRACTICAL BAND III TELEVISION, Part 4  
A SIGNAL TRACER - PLUS  
BAND III BOOSTER UNIT  
"METEOR" MINI-RECEIVER, Part 2  
"MARBLE" REFLEX LOUSPEAKER ENCLOSURE  
and all the usual features.

DATA PUBLICATIONS 16

## THE MODERN BOOK CO

Frequency Modulation Tuner Units for Fringe and Local Area Reception. Reprinted from *The Radio Constructor*. 2s. 0d. Postage 2d.

T V Fault Finding. A Data Publication. 5s. 0d. Postage 3d.

Radio Control for Model Ships, Boats and Aircraft. By F. C. Judd. 8s. 6d. Postage 4d.

Questions and Answers on Radio and Television. By E. Molloy. 6s. 0d. Postage 4d.

Practical TV Aerial Manual for Bands I and III. By R. Laidlaw. 4s. 6d. Postage 3d.

Basic Radio Course. By J. T. Frye. 18s. 0d. Postage 6d.

T V Pre-amplifiers for Bands I and III. By B. L. Morley. 5s. 0d. Postage 3d.

We have the Finest Selection of British and American Radio Books in the country

*Complete list on application*

**19-23 PRAED STREET (Dept RC) LONDON W2**

Telephone PADDINGTON 4185

The "Lodestar" Tape Recorder. By A. S. Torrance. 3s. 6d. Postage 3d.

Practical Wireless Service Manual. By F. J. Camm. 17s. 6d. Postage 6d.

Electronic Musical Instruments. By R. H. Dorf. 55s. 0d. Postage 1s.

High-Fidelity Techniques. By J. R. Langham. 8s. 0d. Postage 4d.

Simple Electronic Musical Instruments for the Constructor. By A. Douglas. 5s. 0d. Postage 3d.

An Introduction to Colour Television. By G. G. Gouriet. 8s. 6d. Postage 4d.

The A.R.R.L. Antenna Book. 18s. 0d. Postage 1s.

The A.R.R.L. Handbook 1955. 30s. 0d. Postage 1s.

Radio Valve Data. Compiled by Wireless World. 3s. 6d. Postage 3d.

## BAND III CONVERTER COIL KITS

Mk1, a two-valve converter for use with TRF or Superhet TV receivers. Complete set of coils, with wiring diagram and alignment instructions, 15/-.  
Mk2, a two-valve cascade converter (featured in this issue). Set of coils, complete with wiring diagram and alignment instructions, 17/6.

## SUPER INDUCTOR COILS - MINIATURE DUST CORE TYPES

Type HAX selective crystal diode coil, as specified for the "Paragon" Tape Recorder, 3/-; HAX L (LW), 3/6. Dual wave TRF coils type A/HF with adjustable iron dust cores, matched pairs, 7/- (as illustrated). Type WA5 for the "R.C. Simple Wobbulator", 4/- each. Complete range of superhet coils, I.F. transformers, wavetraps, etc., 3d. Stamps for complete list and circuits. All types available from leading stockists.

## TELETRON FERRITE ROD AERIALS

Wound on high permeability Ferroxcube rod. No external aerial required. Full sensitivity. Reduces static and whistles. Extremely selective. Simply fitted as replacement for Ae coil or frame aerial. Ideal for battery portable receivers.



Medium wave type FRM, 4" x  $\frac{1}{8}$ " 8/9  
Dual wave type FRD, 8" x  $\frac{1}{8}$ " 12/9

**THE TELETRON COMPANY LIMITED**  
266 Nightingale Road - London N9

HOW 2527

Trade enquiries to sole distributor S. Mozer, 95 Kendal Ave N18 Telephone EDMonton 7707

# Bigger and Better Pictures— with **BRIMAR**

★ Shortly available ★

## THE BRIMAR 21-inch TELETUBE C21HM

This Rectangular Wide Deflection Teletube with Aluminized Screen and external Conductive Coating, operates at 16kV. It is fitted with an improved tetrode gun assembly giving excellent overall focus and minimum astigmatism.

BRIMAR have developed powerful valves suitable for use with existing or future types with larger screen areas.

### 6CD6G/50CD6G (AC/DC)

Line Output Valves with a peak current of  $\frac{1}{2}$  amp. and plenty of power in hand for wide angle scanning.

### 6U4GT

Efficiency Diode—The high working peak heater to cathode potential renders a separate highly insulated heater supply unnecessary.

### RI9

E.H.T. Rectifier—A replacement for the American IX2A but with higher ratings.

### RM5

H.T. Rectifier—A worthy successor to the RM4, with a rating of 300mA. This rectifier has a reserve of power and should be used initially in equipment so that additional valves may be added if required without redesigning the power supply stages.

## VALVES for the BAND III CONVERTOR (FOR 6-VOLT OPERATION)

### \*ECC84

Consists of two separate high slope triode units designed for use as a V.H.F. cascade amplifier.

### \*ECF82

Is a triode pentode frequency changer featuring a high slope triode and a high slope pentode with a high input impedance.


### 6BW7

The 6BW7 is recommended in areas where extra sensitivity is required. It has a slope of 9.3mA/V with anode and screen voltages of 180V.

\* The PCC84 and PCF82 are 3 amp equivalents of these types and are suitable for equipments where series connected valves are used.


**STANDARD TELEPHONES AND CABLES LIMITED**  
FOOTSCRAY SIDCUP KENT  
Footscray 3333

**MAXI-Q**  
REGD.

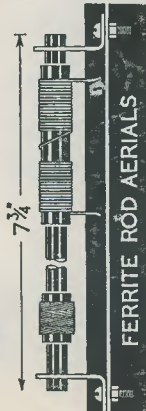

**FERRITE ROD AERIALS**

Gives high selectivity with consequent reduction in second channel and adjacent channel whistles. Ideal for portable receivers. Supplied complete with insulated mounting brackets. Send 6d. in stamps for leaflet giving suitable circuits and layout with full application data.

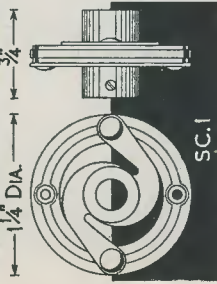

**SC.1**

**FLEXIBLE SPINDLE COUPLERS, SC.1.** Price 2/6

The lining up of coupled components is made easy with these Play-thene insulated flexible couplers. They are completely flexible but entirely free from backlash. The insulator is 1 1/4" dia. and the complete coupler is 3/4" in width. The bushes are drilled for 3/8" dia. spindles. Obtainable from all reputable stockists or, in cases of difficulty, direct from works. General catalogue covering technical information on full range of components, 1/- post paid.

**DENCO (Clacton) LTD 357/9 OLD ROAD ESSEX**

Stop Press.—Coil L3/3 for the R.C. "Band III Television for the Home Constructor" 2/9. Ogram FM Tuner—Chassis, front panel, printed dial plate and drive mechanism, 3/7/6; aerial coil O/T1, 2/9; R.F. coil O/L1, 2/6; oscillator coil O/L2, 2/-; 1st, 2nd and 3rd I.F. coils, L.F.T. 1/1/6; 6/- each; radio discriminator transformer, 1/10/6; (15) complete with crystals, 1/9/6. Multiband FM Tuner—receivers, ref. 3/10/6; 2/6; aerial coil L/J1/2, ref. 3/10/6; 4/6; choke 3, ref. 3/10/6; C, 2/-; R.F. coil L4, ref. 5/10/6; 2/6; oscillator coil L5/L6, ref. 5/10/6; 4/6; 1st I.F.T. L7/L8, ref. 5/10/6; 7/6; 2nd I.F.T. L9/L10, ref. 5/10/6; 7/6; ratio detector transformer L11/12/13, ref. 5/10/6; 12/6; aluminium chassis, completely punched, 12/-.

**TWO NEW COMPONENTS**

**FERRITE ROD AERIALS**

**FRA.1.** Dual Wave for 300pF tuning, 12/6 each. Suitable Oscillator Coils "Miniature Dual Purpose," Range 1 Red and Range 2 Red, 3/11 each.  
**FRA.2.** Dual Wave for 500pF Tuning, 12/6 each. Suitable Oscillator Coils F/LW and F/MW, 3/11 each. Litz wound M.W. coils and Wavearound L.W. coils wound on high permeability Ferrromagnetic rods 7 3/4" x 1 1/4" dia. No separate aerial coil or external aerial is required. Inductance is easily adjusted for alignment. Second channel and adjacent channel whistles. Ideal for suitable circuits and layout with full application data.

**NEW!**

**EXPERIMENTAL KITS in Radio, T.V. etc.**

**LEARN THE PRACTICAL WAY**

Specially prepared sets of radio parts from which we teach you, in your own home, the working of fundamental electronic circuits and bring you easily to the point when you can construct and service radio sets. Whether you are a student for examination; starting a new hobby; intent upon a career in industry; or running your own business — these Practical Courses are intended for YOU — and may be yours at very moderate cost.


**EASY TERMS FROM 15/- A MONTH**

With these outfits, which you receive upon enrolment, you are instructed how to build basic Electronic Circuits (Amplifiers, Oscillators, Power Units, etc.) leading to complete Radio and Television Receiver Testing and Servicing.


**BEGINNER'S RADIO OUTFIT**

For carrying out basic practical work in Radio and Electronics, from first principles and leading to the design and building of simple Receivers.

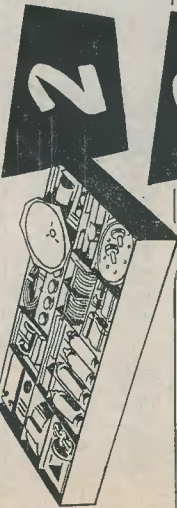**ALL EQUIPMENT SUPPLIED IMMEDIATELY AND REMAINS YOUR PROPERTY**



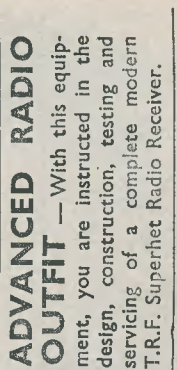**TELEVISION** — With this equipment you are instructed in the design, construction, servicing and testing of a modern high quality Television Receiver.



**ADVANCED RADIO OUTFIT** — With this equipment, you are instructed in the design, construction, testing and servicing of a complete modern T.R.F. Superhet Radio Receiver.

**F.M. TUNER POWER PACK AUDIO STAGE**

- TUNER (KIT OF PARTS)**
- Chassis 6" x 4" 4/10
  - Nuts, Bolts, Tags 3/-
  - Coils and Choke 9/-
  - (2) I.F. Transformers 12/-
  - Tuning Condenser 4/6
  - R.D. Transformer 12/6
  - Resistor Kit 9/6
  - (2) Plugs & Sockets 2/-
  - Condenser Kit 16/9
  - (5) Valveholders (with cans) 11/3
  - Tag Strips 2/4
  - 5 Valves—(2) 6AM6, (1) 6BE6, (1) EF80, (1) 6AL5, 34/10
- Complete Kit £6 2 0  
Circuit Diagram 1/- (Free with kit)

- POWER PACK KIT**
- Chassis 6" x 4" 4/10
  - 16 x 16 Condenser 6/6
  - Transformer 28/6
  - (1) Valveholder 10d.
  - Choke 8/6
  - (1) Valve 6X4 6/6
  - (2) 4-pin Plugs and Sockets (1) Switch 3/6
- Complete Kit £3 12 2  
Circuit Diagram 1/- (Free with kit)

- AUDIO STAGE KIT**
- Chassis 6" x 4" 4/10
  - Resistor Kit 3/6
  - (2) Valveholders 1/8
  - Condenser Kit 5/3
  - (1) Volume Control (1) Valve 6BW6 6/6
  - Output Transformer 7/6
  - (1) Valve 6AM6 6/-
- Complete Kit £1 18 9  
Circuit Diagram 1/- (Free with kit)  
Postage Extra

★ Also BAND III CONVERTER KIT £3 5 0 ★

**TELEKIT SUPPLY**  
104 HIGH STREET BECKENHAM KENT  
BEC 3720

**No Resistance with ERSIN MULTICORE**



**SOLDER**

One imperfectly soldered joint can ruin reception and frustrate hours spent in assembly work. Be sure you use ERSIN Multicore Solder on all connections in your equipment. Five cores of extra-active, non-corrosive ERSIN flux, prevent oxidation, clean surface oxides and eliminate 'dry' and H.R. joints. The Size One Carton gives you waste-free, trouble-free soldering without the need for extra flux. Get a carton today — and ensure good reception.

**SIZE 1 CARTONS 5/- RETAIL**

Ref. No.	Alloy	Lead	S.W.G.	Appr. Length
C 16014	60/40	14	21 feet	
C 16018	60/40	18	55 feet	
C 14013	40/60	13	19 feet	
C 14016	40/60	16	38 feet	

**MULTICORE SOLDERS LTD., MULTICORE WORKS, HEMEL HEMPSTEAD, HANTS (BOXMOOR 5656).**

**E.M.I. INSTITUTES**

The only Postal College which is part of a world-wide Industrial Organisation

**POST THIS COUPON TODAY**

Please send me your FREE book on Practical Courses.


Subject(s) of interest.....

To: E.M.I. INSTITUTES, Dept. 179x, Grove Park Road, London, W.4.

NAME.....

ADDRESS.....

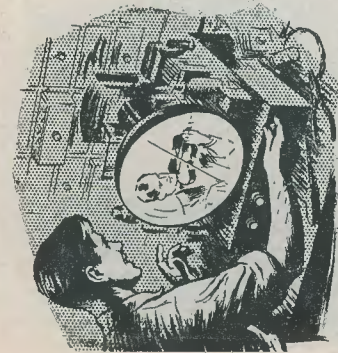- OTHER COURSES WITH EQUIPMENT INCLUDE:**
- MECHANICS · ELECTRICITY
  - CHEMISTRY · PHOTOGRAPHY
  - CARPENTRY
  - ALSO
  - DRAUGHTSMANSHIP · COMMERCIAL ART
  - AMATEUR S.W. RADIO · LANGUAGES · ETC.



# The Bennett College can make you an expert TV technician

—IN YOUR OWN HOME!

**Here's your big chance!** The Bennett College, famous the world over for its first-class postal tuition, now offers you a course in Television Servicing. Right away you can start adding to your knowledge of television repairs and maintenance, increasing your technical ability—and making a sound investment for your future.

**Studying with The Bennett College is a pleasure.** You work in your own home, as quickly—or as slowly—as you like. Your personal tutor at the College sends you your lessons—and gives you his friendly help based on years of teaching experience. The College guarantees to continue teaching you until you reach the standard you wish—and all your text-books are provided free of charge.

Send for a free prospectus to-day! Just fill in the coupon opposite and post it off—The Bennett College will send you a prospectus free of charge and without obligation.

**EXCELLENT COURSES** in the following subjects are also offered by The Bennett College. Write on your coupon the course that interests you.

**ELECTRICAL ENGINEERING RADIO ENGINEERING**  
**ELECTRICAL WIRING TELECOMMUNICATIONS**  
**POWER STATION ENGINEERING**

**To: THE BENNETT COLLEGE**  
(Dept. J162), SHEFFIELD

Please send me free of charge and without obligation, a copy of your prospectus on

SUBJECT/S \_\_\_\_\_

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

AGE (if under 21) \_\_\_\_\_ Please write in block letters

# POST TODAY FOR OUR BROCHURE ON THE LATEST METHODS OF HOME TRAINING FOR OVER 150 CAREERS & HOBBIES

**PRIVATE & INDIVIDUAL TUITION IN YOUR OWN HOME**  
City and Guilds Grouped Certificates in Telecommunications: A.M.Brit. I.R.E. Examinations, Radio Amateur's Licence, Radio and Television Servicing Certificates, General Radio and Television Courses, Radar, Sound Recording, etc. Also Courses in all other branches of Engineering and Commerce.

## The advantages of E.M.I. training

★ The teaching methods are planned to meet modern industrial requirements. ★ A tutor is personally allotted by name to ensure private and individual tuition. ★ Free advice covering all aspects of training is given to students before and after enrolling with us.


**POST THIS COUPON TODAY**

Please send without obligation your FREE book, E.M.I. INSTITUTES, Dept. 179K, Oct. Grove Park Road, London, W.4.

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

SUBJECT(S) \_\_\_\_\_ [C.38]

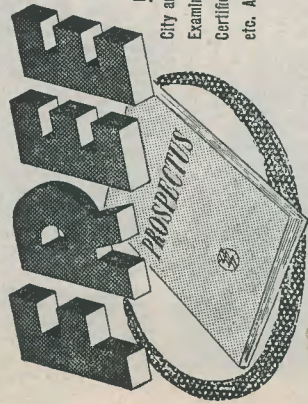


**NEW LEARN THE PRACTICAL WAY COURSES WITH EQUIPMENT**  
With many of our courses we supply actual equipment which is sent upon enrolment and remains your property. Courses include: Radio, Television, Electronics, Draughtsmanship, Carpentry, Photography, and Commercial Art, etc.

**E.M.I. INSTITUTES**  
The only Postal College which is part of a world-wide Industrial Organisation.

# W. & L. COMPONENTS LTD

8 CAMDEN HIGH STREET LONDON NW1 (nr Mornington Crescent Underground) Tel EUS 7844


## FM TUNER

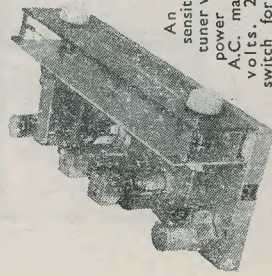

An extremely sensitive 5-valve tuner with internal power supply for A.C. mains 200/250 volts, 2-position switch for gram and FM (tuner switched off in gram position). Permeability tuned and temperature compensated against drift. Geared drive with illuminated calibrated dial. Valve line-up: ECC85 twin triode as grounded grid R.F. stage and mixer, 6B16 I.F. amplifier, 6B16 limiter, 6AL5 ratio detector, 6V4 rectifier. Your existing radio or amplifier converted to FM in a few minutes.

Price **£13.15.0** complete (including tax)  
Carriage and Packing 7s. 6d. extra

## DC to AC CONVERTER

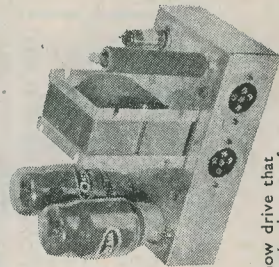

You can now drive that A.C. record changer from your D.C. mains using this effective 50 cycle electronic converter. Input 200/250 D.C.; output 200/250V A.C. 25/30 watts; variable frequency and output controls; valves: Osram 277 and two KT55s; in push-pull; frequency stable with mains; variations from 190 to 250 volts. Easily fitted. Full instructions.

Price **£7.10.0** complete  
Write for full particulars to Dept. 2B

Instrument Cases in steel, complete with light alloy front panel. Colour black (grey 1/6 extra). Back punched for ventilation.

- Type "9" 8" x 9" x 8", 18/6
- Type "9-12" 9" x 12" x 9", 21/-, takes a 10" x 8" chassis
- Type "10-12" 10 1/2" x 12" x 10 1/2", 25/-, takes a 10" x 9" chassis
- Type "13-14" 9" x 14" x 9", 26/-, takes a 12" x 8" chassis
- Type "14" 10 1/2" x 14" x 10 1/2", 30/-, takes a 12" x 10" chassis

Chassis at the following prices. These are in aluminium of 18G.

6 x 4 x 2 1/2	5/6	6 x 5 x 2 1/2	7/6
8 x 6 x 2 1/2	8/-	10 x 6 x 2 1/2	8/6
10 x 7 x 2 1/2	9/-	10 x 8 x 2 1/2	9/6
12 x 8 x 2 1/2	10/6	10 x 9 x 2 1/2	11/-
14 x 8 x 2 1/2	13/9	14 x 9 x 2 1/2	14/-
16 x 8 x 2 1/2	14/9	16 x 9 x 2 1/2	15/6

Suppliers of technical publications. A full range of components, by well-known manufacturers, are stocked: Mullard, Brimar, Cossor, T.C.C., Dubilier, Erie, R.E.P., Weatite, Eison, Morgantite, etc. High stability 1/2 and 5 per cent resistors available from stock or to order.

## KENDALL & MOUSLEY LIMITED

Electronic Engineers and Laboratory Equipment Manufacturers  
18 MELVILLE ROAD - BIRMINGHAM 16

# 20 CIRCUITS for 2/6 only

- Our 1955 Super-Handbook, "The Home Constructor", \* 76 pages now incorporates:
- SUPERHERO'S Superstics, T.R.F. Sets, super-simplified layout and point-to-point wiring diagrams for building a variety of circuits
- COIL PACK—Full constructional details for building a super-net coil pack
- BATTERY RADIO—Full constructional details for a CHEAP CHARGER—Details for building a know-how, your Code, Formulae, and a radio list.
- RADIO CONTROL—General information for building a super-net coil pack
- RADIOLOGUE—Constructors list.
- SUPACOILS—Profusely illustrated price lists of components including—covered coils 10-30, 16-50, 30-75, 75-200, 190-550 3/- each.
- SUPACOIL PACK—All-wave (L/M/S) super-net pack—single hole fixing—recom-mended for numerous receivers—ready aligned. 47/5.

Send for YOUR copy to-day  
**SUPACOILS (DEPT. RC10)**  
21 Markhouse Road London E17  
Telephone: KEY 6896



## FOR ONLY 30/- DOWN

Choose now one of the wonderfully useful B. & D. Home Workshop Outfits—to drill, sand, polish, de-rust, buff, grind, saw or turn wood. Any one of 8 different outfits based on either the 1/4" Utility Drill or more powerful high-speed Sander-Polisher-Drill (both fully suppressed against TV interference) can be yours on the new reduced easy H.P. terms!

A typical outfit—Sander-Polisher-Drill, Polish Pack, Horizontal Stand, Portable Saw Attachment and Buffing and Polishing Kit—costs 30/- down, 12 monthly payments of 27/- (cash value £15 10 6).

# Black & Decker

HANDY **UTILITY** TOOLS

WE CAN SUPPLY ALL your TV and Radio component requirements. Specialists in TELE-KING, SOUNDMASTER, VIEWMASTER, W. W. FM TUNER, TELETRON Converters, etc. ENQUIRIES WELCOME.

(Terms C.W.O. or C.O.D. plus post and packing)

**MARYLANDS ELECTRICS 6 MARYLANDS ROAD LONDON W9**

Telephone CUN 7877

### FREE GIFT OFFER

12 one-yard lengths of various coloured sleeving given FREE with all orders of 10/- or over.

100 ASSORTED RESISTORS 10/-  
100 ASSORTED CONDENSERS 12/6



# The Radio Constructor

incorporating THE RADIO AMATEUR

## CONTENTS FOR OCTOBER

- 140 Suggested Circuits: A Booster Unit for Band III, by G. A. French
- 142 Can Anyone Help?
- 143 In Your Workshop, by J.R.D.
- 148 Band III Interference from Band I—Re-Aligning the Magna View and Universal Televisors
- 149 Notes on Radio Control: An Automatic Switch, by C. Grant Dixon
- 150 The "Meteor" Mini-Receiver for the Beginner, Part 2, by F. A. Baldwin, A.M.I.P.R.E.
- 154 Trade Review—Telecraft Band III Aerials
- 155 A Signal Tracer—Plus, by A. Shaw
- 158 Band III Television for the Home Constructor—A High Gain Band III Converter, Part 4, by S. Welburn
- 164 High Quality 10 Watt Ultra-Linear Amplifier, Part 1, by L. F. Sinfield
- 170 A Constructor Visits the 1955 National Radio Show
- 172 A "Marble" Reflex Loudspeaker Enclosure, by F. Johnson
- 177 Query Corner—A Service for Readers
- 180 Radio Miscellany, by Centre Tap
- 182 Let's Get Started, 28: The Transistron, by A. P. Blackburn
- 186 Vibrator Data, Part 3, compiled by E. G. Bulley

VOL. 9 NO. 3

OCTOBER 1955

ANNUAL SUBSCRIPTION 18/-

Editorial and Advertising Offices  
57 MAIDA VALE LONDON W9

Telephone  
CUNNINGHAM 6141  
(2 lines)

Telegrams  
DATABUX, LONDON

Editor  
C. W. C. OVERLAND, G2ATV

Advertising Manager  
F. A. BALDWIN, A.M.I.P.R.E

THE CONTENTS of this magazine are strictly copyright and may not be reproduced without obtaining prior permission from the Editor.

Opinions expressed by contributors are not necessarily those of the Editor or proprietors

## NOTICES


THE EDITOR invites original contributions on construction of radio subjects. All material used will be paid for. Articles should preferably be typewritten, and photographs should be clear and sharp. Diagrams need not be large or perfectly drawn, as our draughtsmen will redraw in most cases, but all relevant information should be included.

All MSS must be accompanied by a stamped addressed envelope for reply or return. Each item must bear the sender's name and address.


TRADE NEWS. Manufacturers, publishers, etc., are invited to submit samples or information of new products for review in this section.

ALL CORRESPONDENCE should be addressed to THE RADIO CONSTRUCTOR 57 MAIDA VALE LONDON W9

WE BOUGHT OUR OWN HOME WORKSHOP OUTFIT

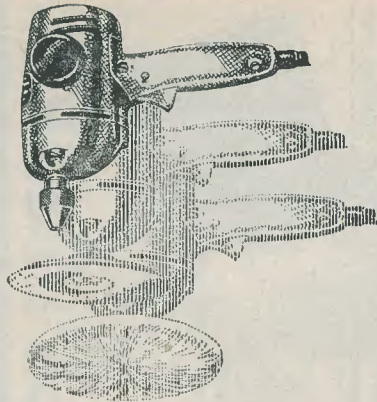
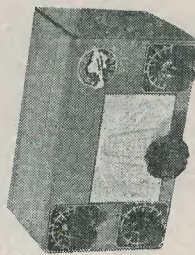
## Explore the World on Short Waves with the "METEOR"




This fine little set will bring the world to your fireside. We can supply all parts including genuine EDDYSTONE components.

Panel and chassis with major holes ready punched. 3/6  
BBA valveholders, 9d. ea. Fixed resistors, 4/-, 50K potentiometer 3/-, Fixed condensers 9/-, Eddystone 1072 3/6, Eddystone 585 11/6, Eddystone 586 12/-, Eddystone 707 2/6, Eddystone coils 706LB, 706Y, 706R 6/6 ea. Eddystone coils 706W, 706P 8/6 ea. Eddystone coil stand type 775 2/9. VALVES EF41 10/6, EL42 10/6

Send s.a.e. for detailed list.

We also stock the full range of components for TELETRON converter, JASON FM tuner, FULL-TONE amplifier, MULLARD 5/10, G.E.C. "912 PLUS," etc.

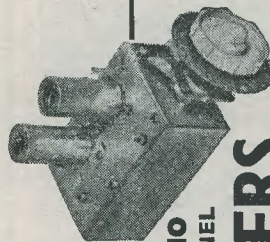**HOME RADIO of MITCHAM**  
187 LONDON ROAD MITCHAM SURREY  
Telephone MITT 3282



**VALRADIO 13 CHANNEL TUNERS**


**NOW AVAILABLE TO THE HOME TV CONSTRUCTOR**

Adapt your set to receive the Commercial TV programmes. Valradio tuners are suitable for home constructed receivers including "The Wireless World," "Magnaview," "Teleking," "Premier," etc.

Complete with fitting instructions ... **£6**  
Bracket for fixing tuner to cabinet ... 2/6



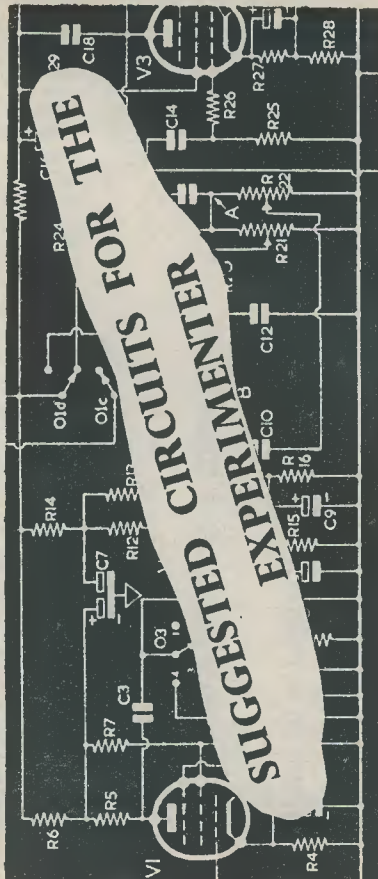Valradio Limited, New Chapel Road, High Street, Faltham, Middlesex, Phone Feltham 4242 & 4837



**SUGGESTED CIRCUITS FOR THE EXPERIMENTER**

The circuits presented in this series have been designed by G. A. FRENCH, specially for the enthusiast who needs only the circuit and essential relevant data

**No. 59. A BOOSTER UNIT FOR BAND III**

**B**Y THE TIME THIS MONTH'S SUGGESTED Circuit appears in print, I.T.A. transmitters in Band III should have commenced. These will mark the culmination of many months of work in the past on the part of the Radio Industry, together with the fulfilment of a considerable amount of preliminary publicity given by the Press and other organs.

It is possible that some viewers will be slightly disappointed with the strength of the signals received when they finally appear, and that others may have the quality of their pictures degraded by interference. In the first instance, the viewer who suffers from poor signal strength will almost certainly be one of those residing in a fringe area, or in an area which is "screened" from the transmitter by local land formations or buildings. The alternative instance of viewers suffering from interference would be given mainly by cases where this is caused by alternative services.

In both of these instances, the use of a booster unit tuned to Band III appears to be very attractive. Such a unit should, for example, be capable of providing just the extra gain which is required to bring fringe area signals to satisfactory picture strength. In cases of interference, the unit could also

increase the strength of the Band III signal such that the effect of the interference was noticeably reduced, or was made negligible in comparison.

It may finally be argued that a Band III booster, being tuned to a single frequency, would possess the additional advantage of having an input tuned circuit which could be relied upon to give optimum results with the particular aerial being employed, especially insofar as neutralisation was concerned. Such a point cannot be guaranteed in a turret tuner, which has to function as best it may with whatever set of coils is selected by the user.

**The Circuit**

The circuit of the booster unit is illustrated in the diagram accompanying this article. As may be seen, it is extremely simple in design. It consists of a single cascode acting as a straightforward v.h.f. amplifier, its output feeding into the aerial socket of the associated receiver (or Band III converter).


The aerial input socket of the booster connects directly to the coupling coil, L<sub>1</sub>, of the first tuned coil, L<sub>2</sub>. L<sub>2</sub> is tuned by the grid-cathode capacity of V<sub>1a</sub> plus other capacities existing in the circuit. V<sub>1a</sub> is the

first part of a double triode v.h.f. cascode, and its anode connects to the cathode of V<sub>1b</sub> via a small "peaking" coil. V<sub>1b</sub> then feeds into the anode tuned circuit formed by L<sub>4</sub> and stray capacities to chassis. A second coupling coil, L<sub>5</sub>, next connects to a coaxial feeder; this terminating at the input socket of the associated television.

A neutralising arrangement is employed in the first tuned circuit, this helping to increase the signal/noise ratio given at the grid of V<sub>1a</sub>. Neutralising is carried out via a small condenser C<sub>2</sub>, this feeding out-of-phase voltage to the lower end of the grid coil L<sub>2</sub>. The degree of neutralisation obtained is controlled by the trimmer C<sub>1</sub>.

available from several well-known manufacturers. The type required is that which, in effect, a variable feed-through condenser, and whose earthy connection is soldered direct to the chassis.

The series peaking coil should be self-supporting and may be wound quite simply. It should consist of approximately four turns on a diameter of three-sixteenths of an inch. Normal tinned copper (around 22 to 26 s.w.g.) could be employed here, and the coil may be soldered directly across the appropriate pins of the valveholder. The peaking coil is intended to resonate just above Band III frequencies. If its inductance is made too large, and its resonant fre-

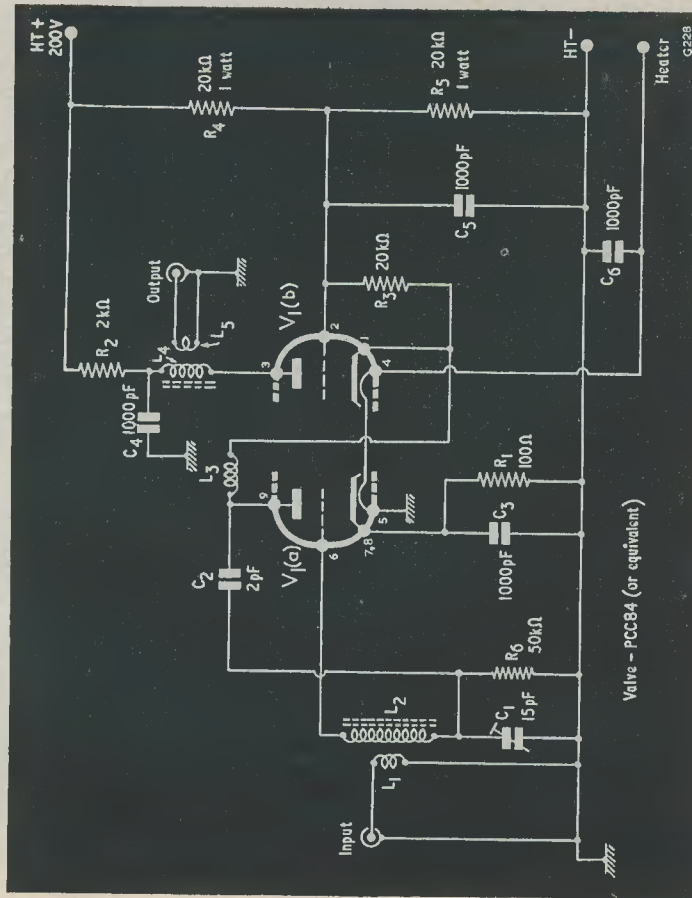

*Circuit of Band III Booster Unit*

**Components**

Apart from the coils, the components for this circuit should be readily available through the normal retail channels. All condensers should be ceramic as, also, should the valveholder for the cascode. To attain the full gain possible, all component leads should be made extremely short, and all earth returns soldered direct to the chassis. The neutralising trimmer, C<sub>1</sub>, is

quency consequently approaches the operating frequency of the booster unit, it is liable to introduce regeneration and consequent instability. There is an interesting field of experiment here for those who wish to obtain the maximum amount of gain from the cascode.

**The Tuned Coils**

The tuned coils will require a certain amount of experiment to find the final

optimum number of turns. Assuming an unscreened Aladdin former, some three turns of 18 to 22 s.w.g. enamelled wire will probably cope for L<sub>2</sub>, and some four turns for L<sub>4</sub>. The turns should be close-wound. The coupling coils, L<sub>1</sub> and L<sub>5</sub>, should consist of one to two turns of thinner enamelled wire (from 32 to 36 s.w.g.), interleaved at the earthy end of the tuned coil. (The earthy end of L<sub>2</sub> is that connecting to C<sub>1</sub>). Iron-dust or brass cores (preferably brass) will be required to finally set the inductance of L<sub>2</sub> and L<sub>5</sub>. To prevent the risk of an h.t. short-circuit between L<sub>4</sub> and L<sub>5</sub>, the wire for the latter may be covered by thin-wal sleeve before it is interwound with L<sub>4</sub>.

The two coils should be mounted as close as possible to the valveholder and should be screened from each other to prevent instability. Extensive screening is not required.

#### Setting Up

If the television with which the booster is to be employed is capable of receiving the Band III signal faintly, setting up is reasonably

simple. If not, a reliable signal generator will be initially required.

The first coil to bring into correct operation is L<sub>4</sub>. After the optimum number of turns for this coil has been decided, the coupling coil, L<sub>5</sub>, should be adjusted for optimum transfer of energy to the television.

L<sub>2</sub> is the next coil, followed by L<sub>1</sub>. The number of turns required on L<sub>1</sub> will probably be a compromise between maximum transfer of energy and minimum damping of L<sub>2</sub>. L<sub>1</sub> should be adjusted using the Band III signal and the aerial which will finally be employed.

The trimmer C<sub>1</sub> is then adjusted for maximum signal/noise ratio. The optimum setting of this condenser may be difficult to determine accurately if a strong signal is being received. In consequence, this component could be finally set when the Band III transmitter is off the air, it being adjusted for minimum "noise" on the screen. (This may necessitate also the removal of the aerial plug, and its substitution by a 75 ohm fixed carbon resistor).

## Can Anyone Help?

D. B. COLLINS, of 286 Heckmondwike Road, Lewsbury Moor, Dewsbury, Yorks, who needs the circuit, power requirements, plug connections and other data on the Transmitter 1154.

R. A. SMITH, 253 Fir Tree Road, Epsom Downs, Surrey, who needs circuit diagrams and constructional data on an electronic densitometer, capable of reading densities of 0 to 4 in 0.1 steps. A wider range would be even more acceptable.

R. S. LANGDON, 11 Boyson Road, Walworth, S.E.17, would like to know of any modifications to enable the Bendix R.A.10.F.B., R.A.F. Serial No. 1100/159, to be used on normal mains supply. The loop aerial, relay and 28V band-change motor have been removed. He would also like to know if the crystal is required. Is willing to pay reasonably for such information.

S. DINGWALL, 12 Llewelyn Road, Colwyn Bay, N. Wales, has tried in vain to obtain data for his MCR1 receiver, which is giving trouble. Can anyone supply service instructions on the receiver and power pack?

H. R. FRX, of 108 Glenfield Road, Longbenton Estate, Newcastle-on-Tyne 12, would like to obtain a copy of the May 1952 issue of *The Radio Constructor*. He is interested in obtaining a circuit for a bridge which will

measure inductance of iron-cored I.f. chokes with a heavy d.c. load.


W. J. ELLESMERE, 23 Rawlings Road, Bearwood, Smethwick, Staffs, would like to obtain information regarding the circuit and conversion of the ex-R.A.F. v.h.f. transmitter/receiver type T.R.3171, ref. no. 10DB913, serial no. G1123.

J. Moss, 4A Kent Street, Upper Gornal, near Dudley, Worcs, asks if anyone can supply the circuit diagram or preferably the service sheet of the Alba a.c./d.c. table model 3-band receiver No. 462. Expenses gladly refunded.

J. W. BARNETT, 77 The Crescent, Dunsroft, near Doncaster, needs information on the P.O. Receiver W31/3T (RL127) (PL Receiver)—all these markings on panel—and the R.A.F. Wavemeter W1310. All letters answered and costs covered.

R. K. SAXENA, 70 James Street, Rugby, Warwick, would like to buy or borrow the circuits of the BC348 and DST100. He would also like to know where to obtain a 3-gang (3 × (130 + 360)) pF.

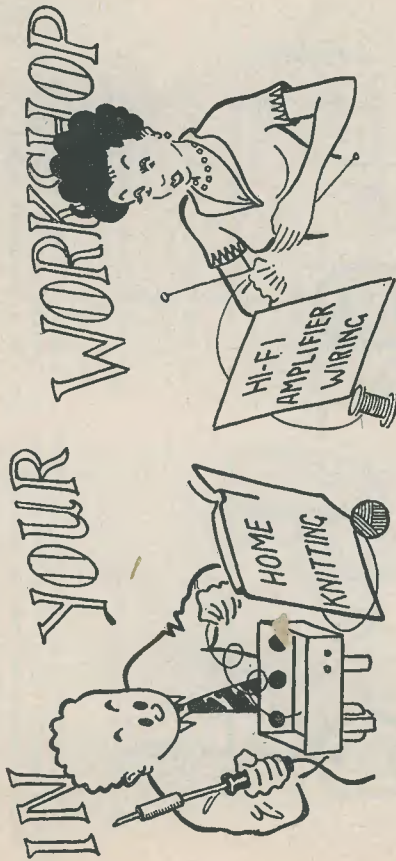H. W. BONFIELD, 73 Grove Road, Hitchin, Herts, wishes to buy or borrow the circuit or any information on the R1120 battery t.r.f. receiver, AM reference No. 10D/10472.



In which J. R. D. discusses Problems and Points of Interest based on Letters from Readers and his own experience

NOW THAT V.H.F. TRANSMISSIONS ARE with us in the London area, and will shortly be available over most of the country, it follows that a certain amount of re-orientation of mind becomes necessary to absorb the new techniques which are necessary at these higher frequencies. The v.h.f. transmissions referred to are, of course, those in Band II from Wrotham and the I.T.A. signals in Band III. The latter are not in existence at the time of writing, except as a low power test signal, but should be by the time this appears in print.

#### Frequency-Changers

Readers may remember that as long as a year ago I contributed some notes concerning the cascode and triode-pentode combination which is now accepted as "standard" for Band III manufactured television "front ends." At that time I paid special attention to the cascode, but did not devote a great deal of space to the triode-pentode; and some readers have asked me to give further details concerning the working of this second valve.

From the theoretical point of view there is, of course, nothing very complicated in the functioning of the additive mixers (such as the triode-pentode) that are nowadays so commonly used for v.h.f. work. In practice, however, things may not be quite so easy. (They seldom are!) I have been in a position to carry out some v.h.f. experimental work recently, and so I may be able to pass on some useful tips concerning those valves which will be of interest and help to constructors.

Let us start at the beginning and ask ourselves why we employ additive mixers for v.h.f. reception in the first place. (Additive mixers are those in which the signal and oscillator voltages are applied to the same grid, usually via a condenser and leak). Why not carry on with the normal well-known frequency-changers, such as the 6K8, 6SA7, 12AH8, etc., etc., in which frequency conversion takes place in the electron stream? The answer to this question is that the electrode assemblies used in the types of frequency-changer employed for broadcast band and short-wave reception do not permit of satisfactory mixing at v.h.f. The main difficulty is caused by transit time. This is the time taken by the electron stream to travel from one modulating grid to the next; and at v.h.f. it becomes an appreciable fraction of the time occupied by one cycle of the signal or oscillator frequency. The transit time could be reduced by mounting the grids very closely together, of course; but the best answer consists of applying both signal and oscillator frequencies to a single grid. This is done in the additive mixers intended for v.h.f. operation.

#### The Oscillator

Practically all v.h.f. frequency-changers employ two valves in the one envelope. Typical types are the 12AT7 double-triode, or the PCF80 triode-pentode. One of the two valves functions as an oscillator, the other as the mixer.

Since the oscillator plays a very important rôle in the functioning of the valve as a whole, it might be as well to consider next



this section of the v.h.f. frequency-changing circuit.  
 Most v.h.f. oscillators employ a form of the Colpitts circuit, a typical example of which is shown in Fig. 1(a). The frequency at which this circuit oscillates is that given by the coil  $L_1$  and the two condensers  $C_2$  and  $C_3$  in series. Thus, if each of these

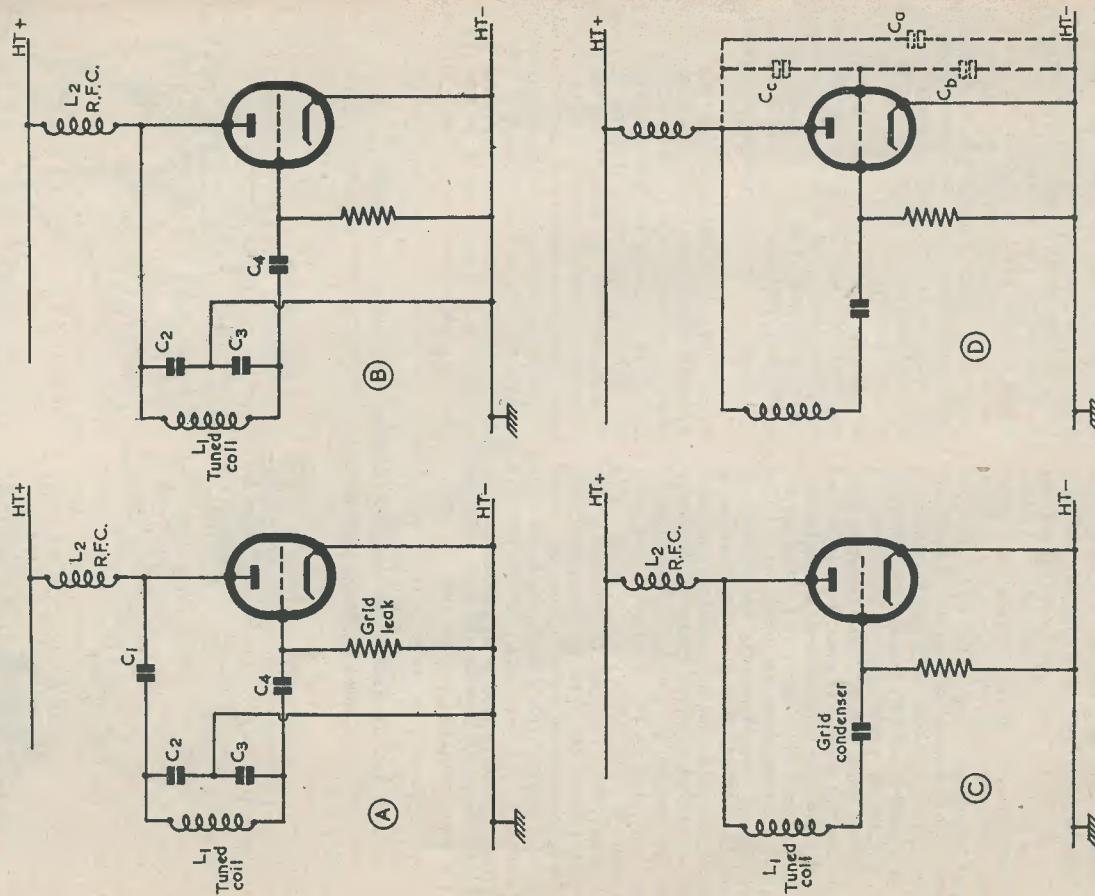


Fig. 1 (a) A typical Colpitts oscillator. (b) An economy in components may often be effected by cutting out the anode coupling condenser, as shown here. (c) A typical v.h.f. oscillator. (d) When the stray capacities are taken into account, circuit (c) is similar to circuit (b).

condensers had a value of 200pF, the resonant circuit of the oscillator would be by the coil paralleled by an effective 100pF condenser. To keep an oscillator of this type running, it is necessary to ensure that the r.f. at the grid of the valve is of opposite phase to that at the anode. To ensure this relationship, an early tap has to be made into some point in the tuned circuit. This tap could be made into the coil. Or it could be made into the capacitive half of the tuned circuit, as is done in Fig. 1(a).

It will be realised that the ratio between the capacities of  $C_2$  and  $C_3$  in Fig. 1(a) determines the ratio between the r.f. voltage appearing at the anode and the grid. This is quite an important point. In practice, if we wish to obtain optimum working conditions in the oscillator circuit we have to choose the relative values of  $C_2$  and  $C_3$  with some care.

It will be noticed that the circuit of Fig. 1(a) is shunt fed; i.e., the anode does not receive an h.t. supply through the windings of the coil.  $C_1$  is merely a coupling condenser and prevents h.t. being applied to the coil. The r.f. choke,  $L_2$ , in the anode circuit may be replaced by a resistor if desired, provided that the latter does not introduce too many losses into the tuned circuit or drop too many h.t. volts.

Two Condensers for One


If we wanted to save ourselves the price of a condenser in the circuit shown in Fig. 1(a), we could do this by re-drawing it so that it resembles Fig. 1(b). In Fig. 1(b) we have cut out  $C_1$ , and the coil is now at the same d.c. potential as the anode. No trouble will result from this, however, because there is no d.c. connection between the coil and chassis; it is still isolated by the condensers  $C_2$ ,  $C_3$  and  $C_4$ .

There is an important point about v.h.f. working with which we should next deal. Due to the high frequencies involved, the resonant circuits used for frequency-changer oscillators must employ components having very low values of inductance and capacity. Also, to keep losses low, we want to ensure that the L/C ratio of the tuned circuit is high; i.e., that the inductance is large compared to the capacity. Indeed, the tuning capacity should be of the order of a small number of picofarads only.

Because of this requirement, v.h.f. oscillators usually appear in a form similar to that shown in Fig. 1(c). This circuit looks a little "bereft" at first, but it is quite a workable proposition in practice. Fig. 1(d) may help to make it clearer. As may be seen, the coil in Fig. 1(d) is tuned by the stray capacities existing in the circuit. Of these,  $C_a$  is the capacity existing between

the anode and cathode of the oscillator, this being in parallel with the stray capacities between the anode wiring and chassis.  $C_b$  is the capacity between grid and cathode and is also in parallel with stray wiring capacities.  $C_c$  is the capacity between grid and anode, plus stray wiring capacities, plus the self-capacity of the coil. Apart from the additional tuning capacity given by  $C_c$ , Fig. 1(d) is identical to Fig. 1(b).

As was mentioned earlier, the values of the two capacities tuning the coil should have a particular ratio if optimum working is to be obtained. It is desirable, therefore, to ensure that  $C_a$  and  $C_b$  of Fig. 1(d) possess this optimum ratio or, at least, approach it. Usually, this state of affairs happens adequately enough with the normal stray capacities existing in the circuit, but it is sometimes necessary to add small-value fixed condensers between one end of the coil and chassis in order to achieve maximum efficiency.

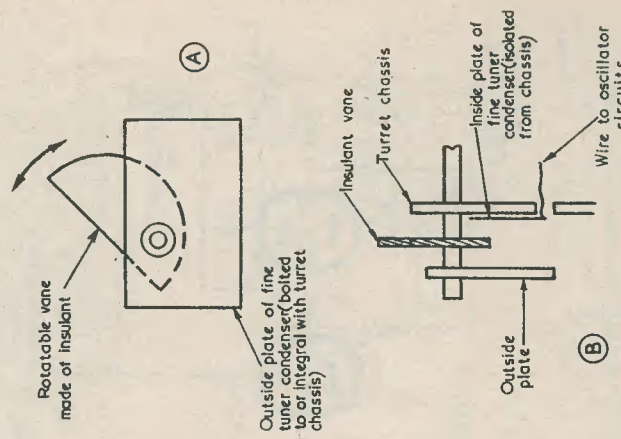

E221

Fig. 2. End view (a), and side view (b), showing the construction of the fine-tuning condensers fitted to turret tuners

It will almost certainly be necessary to tune the oscillator circuits of Figs. 1(c) and (d), even if only over a small range. The best way of doing this consists of fitting


the coil with an adjustable iron-dust or brass core. Should capacitive fine tuning also be desired this can be achieved by connecting a small-value variable condenser between one end or other of the coil and chassis. If one is going in for really superior design, the middle setting of the variable condenser should give just the capacity needed for the best ratio between the two capacities tuning the coil. In practice, things are not so critical as this unless the variable fine tuning condenser has a higher maximum value than normal design would warrant.

Incidentally, an important advantage of using the Colpitts circuit for v.h.f. operation is the fact that only two connections are needed to the coil. Because of this the design of Band III turrets can be considerably simplified, since only two contacts are needed to connect to the oscillator section of the coils for each channel.

The dielectric constant of the vane material differs from that of air, with the result that the capacity of the condenser varies as the vane is rotated. Capacity variation is of the order of a few pF only.
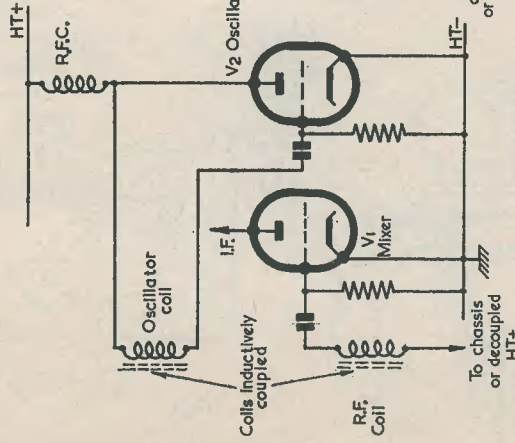
#### Application to the Mixer

Having obtained an oscillatory voltage, it is necessary to apply this to the grid of the mixer. This may be done either inductively or capacitively. Inductive coupling is given when the signal frequency coil is mounted close enough to the oscillator coil to enable r.f. currents at oscillator frequency to be induced in it. This arrangement is illustrated in Fig. 3(a). (A rejector r.f. tuned circuit is assumed here and in Fig. 3(b)). What occurs in Fig. 3(a) is that the oscillatory voltage induced into the r.f. signal coil is applied, together with the r.f. signal, to the single grid of the mixer valve.



E222

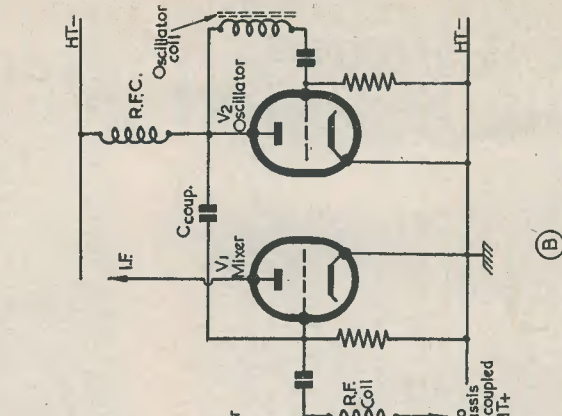


Fig. 3 (a) Illustrating inductive coupling in a v.h.f. frequency-changer stage.  
(b) Showing how capacitive coupling may be obtained at v.h.f.  $C_{coup}$  usually has a value between 1 and 4pF.

As we are dealing with practical points, the type of condenser employed for fine tuning with almost all Band III turret tuners is also worthy of mention here. This condenser consists of two fixed plates, as in Fig. 2, between which rotates a specially shaped vane made of insulating material.

Capacitive coupling is shown in Fig. 3(b). In this case the oscillator and r.f. coils are mounted some distance away from each other (being also screened, if desired), and the oscillatory voltage is applied to the mixer grid via  $C_{coup}$ .  
When using these circuits in practice,

one is sometimes liable to forget the stray capacities which are continually in existence. Thus, whilst the coupling employed in the circuit of Fig. 3(a) may appear to be wholly inductive on paper it can, in practice, be quite largely capacitive as well.

In Fig. 3(b) the nominal coupling capacity  $C_{coup}$  may, in fact, be accompanied by stray capacities as well. It should be remembered also that some of these stray capacities may tend to reduce the transfer of energy between the oscillator and mixer grids instead of assisting it. As an example, any stray capacity existing between the two control grids in Fig. 3(b) will actually oppose the coupling given by  $C_{coup}$ .

To make things more complicated, there is the question of stray inductive coupling as well. This is usually caused if the oscillator and mixer share a common inductive impedance. Since a straight piece of wire an inch long has an appreciable amount of inductance at v.h.f., care has to be taken to prevent both valves sharing a single connection, such as a common cathode lead. Normally, fortunately, the valve pin layout automatically prevents stray inductive coupling if care is taken with the layout.

This picture of stray inductances and capacities may appear to be rather gloomy to the constructor who is just about to embark on Band III experiments. However, they do not, in practice, cause any insurmountable obstacles; so long, that is, as the normal commonsense rules of wiring layout are observed. Nevertheless, the existence of strays should not be ignored. What may sometimes appear to be quite unexpected results are frequently due to the presence of these "unseen components."


#### Conversion Conductance

To obtain maximum conversion conductance from a v.h.f. mixer, the oscillatory voltage applied to the mixer grid should be kept within the bounds recommended by the valve manufacturer. The limits set are, frequently, fairly critical.

The usual, and simplest, method of measuring the voltage applied to the mixer grid consists of reading the current (d.c.) flowing through its grid leak. This method has the advantage of causing minimum circuit disturbance, and it takes into account practically all the stray couplings which are in existence. Manufacturers sometimes state the value of grid leak recommended for a particular valve, and give a figure also for optimum grid current. Usually, however, a voltage is quoted; in which case the requisite current has to be worked out. For instance, if a grid leak of 47kΩ and an oscillatory voltage of 4 volts are recommended, the resultant grid current should be 85μA.

The grid current-reading meter may be inserted into the oscillator grid circuit as shown in Fig. 4. In this diagram, the connection between the lower end of the grid leak and chassis is broken, and the meter inserted in between. As the meter will almost certainly have to be connected via fairly long leads it is worth while to decouple these by a condenser mounted very close to the grid leak and chassis. No other wiring in the mixer circuit should be altered.

The best way of getting the frequency changing stage into top condition consists of making the oscillator work at its highest efficiency. This can be done by experimentally finding the value of capacity required between either end of the coil and chassis which gives greatest oscillator output. This point was explained above. It may happen in some cases that, when additional capacity is needed at the grid end of the coil, this can with advantage be connected from chassis to the grid itself and not directly to the coil. This capacity is then applied to the coil in series with the grid condenser. Experiment is the best way of determining these points. (Optimum oscillator operation will be shown by connecting a milliammeter in the oscillator grid leak circuit in the same manner as shown in Fig. 4 for the mixer).

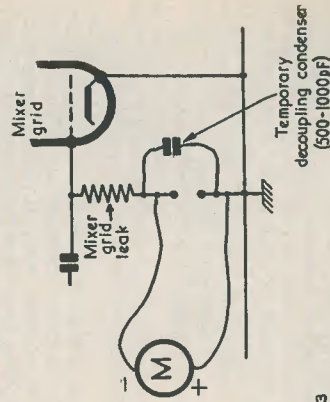

E223

Fig. 4. The oscillator volts at the mixer grid can be measured as shown here. A similar circuit may be employed for checking oscillator grid current as well.

Having got the oscillator working correctly, the coupling to the mixer grid should then be adjusted. This is done either by varying the relative position of the r.f. and oscillator coils if inductive coupling is employed; or the value of the coupling condenser when capacitive coupling is employed. The signal frequency circuits should be set to their

correct frequency during this process. If all goes well, the entire frequency-changer stage should then be working as efficiently as it possibly can be under the limitations imposed by its components and layout.

It should be mentioned, before concluding, that some additive mixers are recommended to work with a cathode bias resistor and

condenser. A useful solution to the consequent problem of measuring grid voltage consists of short-circuiting the cathode to chassis by a short piece of wire during the tests, and assuming that only slight errors will be introduced when it is later removed. This assumption appears to be well justified by practical experience.

## BAND III INTERFERENCE FROM BAND I

### RE-ALIGNING THE MAGNA-VIEW AND UNIVERSAL TELEVISORS

by A. S. TORRANCE

(By kind permission of *Ikopatens Ltd*)

IT IS REGRETTABLE THAT WHEN THESE excellent sets made their bow some three years ago, alternative television was a mere pipe-dream—and there was no indication of the likely wavelength to be used for commercial T.V. In consequence the intermediate-frequency chosen for the "Magnaview" and "Universal" Televisors, although free at that time of adjacent channel difficulties, has now revealed itself as the unfortunate victim of the chosen wavelength for the I.T.A. transmitter in the London or Channel 9 areas. It should also be noted that the presence of a converter, pre-amplifier or other subsidiary apparatus attached to these receivers in no way diminishes the nuisance, which remains constant from the harmonic generated in the oscillator circuit.

Any apparatus embodying an oscillator may have a harmonic either on or close to the new Band III signals.

The power from the oscillator is usually high and will interfere with any T.V. set adjusted to Band III in the near vicinity. It is the third harmonic which is troublesome. The conditions which must be remedied are graphically shown by the following figures taken from the T.V. receivers in question.

Vision I.F. . . . .	19.75 Mc/s
Channel I vision R.F. . . . .	45.00 Mc/s
Osc. frequency, the sum of:	64.75 Mc/s

The third harmonic. . . . . 194.25 Mc/s  
This offending radiation is only half a megacycle from the London I.T.A. transmitter and would produce a most objectionable "patterning" on the screen of any receiver nearby tuned to the London commercial station. It is therefore imperative that any apparatus operating under these conditions should be re-aligned.

Further to this, as stations make their appearance elsewhere equipment other than

## NOTES ON RADIO CONTROL

### An Automatic Switch

by C. GRANT DIXON


WHEN EXPERIMENTING RECENTLY WITH radio control circuits for the control of a model boat, the writer was faced with the problem of generating pulsed r.f. signals with variable mark/space ratio. Long experience of pulse techniques led to the consideration of the multivibrator, but it soon became evident that with battery valves and a 90V h.t. supply this was going to be quite a problem, especially as a low repetition rate was desired. As a result of a different approach to the problem, the following automatic switch was evolved; this appears to have uses in other directions as well.

Referring to the diagram, it will be seen that the condenser C charges up through the variable resistance R, and when a suitable voltage has built up, the relay is energised, thus breaking the charging circuit. The relay remains energised until the charge on the condenser has leaked away, then it ceases to hold, and the contact with the charging circuit is restored and the whole process starts all over again. The values given in the diagram refer to a repetition rate of about 2 or 3 per second, and it may be noted that the low working voltage of the condenser is possible because it only charges up to a few volts before the relay disconnects it from the supply. With a given relay, the repetition rate is governed by the value of condenser chosen. The variable resistor is used to control the mark/space ratio. With a low value of charging resistance the condenser charges quickly, but its time of discharge is already fixed by the resistance of the relay coil, hence the relay is held closed for a longer time than it is released.

The relay actually used had a set of SPICO contacts, and if a similar one is available these contacts can be used for a variety of switching purposes. In addition to its original function of switching the h.t. to an r.f. oscillator, this automatic switch can be used for the production of accurate, very low frequency, square waves by switching a battery or other d.c. supply. Such square waves can be used for testing the i.f. response of amplifiers, but care should be taken to check the Y amplifier

of the oscilloscope before investigating any other amplifiers.

Another possible use for the device is the beam-switching of an oscilloscope by using two Y amplifiers and switching them alternately to the deflector plates. D.C. shift of one trace may be added by additional relay contacts, or else incorporated in the amplifiers by d.c. coupling. For very low frequency switching of this type it is advisable to use a cathode ray tube with a long persistence screen.

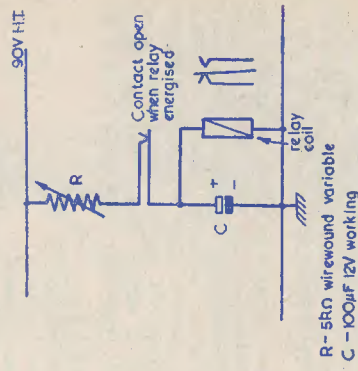

R—5Rn wirewound variable  
C—100µF 12V working  
Relay—post office type—500 ohm coil

E219


Everything has its disadvantages, and the clicking noise may be somewhat irritating to some people, but this is compensated by the saving of valves and their associated components. A more serious disadvantage is that there is a limit to the mark/space ratio in the "short on—long off" direction, as this means a large value of charging resistance, and because of the potential divider effect across the h.t. supply an insufficient voltage is built up across the condenser to pull the relay.

To sum up—the circuit appears to offer scope for further development, particularly with regard to its applications, and will certainly appeal to those who are fond of the unusual.

# The "METEOR" MINI- RECEIVER

for the  
Beginner

by F. A. BALDWIN, A.M.I.P.R.E.

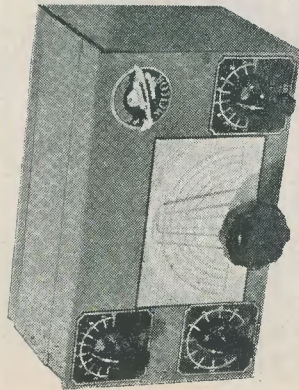

PART 2.

(A receiver using modern miniature components, specially designed for, and directed at, our beginner readers. In this issue the wiring details and power unit circuit are given.)

HAVING PREVIOUSLY DESCRIBED THE CIRCUIT and drilling details in the last issue of the magazine, we now proceed to outline the wiring of the receiver. Before going any further, however, a few words about tools for the job, and soldering itself, may not come amiss to the beginner—for the benefit of whom this article has been prepared.

Obviously, as a first consideration, the possession of a good quality soldering iron—preferably of the electric type—is of paramount importance. Although this involves some capital outlay at the outset, it will last for many years—being virtually a necessity in the workshop, and without which it is not possible to construct even the most simple modern receiver. Before operations commence, the bit, preferably one of the so-called pencil types, must be "tinned," i.e., cleaned with flux and covered with a thin layer of solder; the latter being then shaken off so that no blobs of solder are left adhering to the iron.

Apart from the iron already mentioned, the other tools required are a pair of side-cutters pliers, fairly small ones, and a "Bib" wire stripper. For materials, lengths of various coloured PVC wire (in effect, plastic covered wire), a length of systoflex (flexible insulating material for covering bare wire ends of components), and last but not least, something not often mentioned in radio

periodicals—the humble piece of rag. This latter item is very necessary for wiping the iron from time to time thus removing old solder and accumulated dirt etc. A further point worth mentioning to the beginner is the provision of a suitable iron stand on which the heated bit can be placed, both for safety and convenience. It must, of course, be of metal, and a small length of aluminium bent into the shape of a letter L (viewed sideways), bolted onto the bench and with a cut-away notch in the centre (see Fig. 10), would serve admirably.

### Wiring the Receiver—The First Stage (V<sub>1</sub>)

Although only the wiring of the first valve is dealt with in this section, the heater wiring should be completed for both valves at the outset. The two valveholder pins (No. 1), should therefore be connected together via a suitable length of PVC wire. From pin 1 of V<sub>1</sub>, a nine inch length of wire should be taken out through the grommet. This lead will constitute the h.t. + input when connected to the power unit later. Pins 8 of both valves should now be soldered to the nearest soldering tags which are fastened under the respective holding bolts of the valveholders. The same length of wire should also be soldered to the central metal spigot of the holder. This latter operation ensures that an earthed screen is between the grid and anode pins of the

valve. This completes the heater wiring. Pin 7 should now be soldered to pin 8. To pin 2, solder one end of the r.f. choke, the other end of which goes to the tag on the 3-way strip nearest the chassis (see photograph). Having done this, return to pin 2 and solder both C<sub>2</sub> and C<sub>4</sub> to it. The other end of C<sub>2</sub> is now connected to the coil (see Fig. 3). C<sub>4</sub> is then taken to pin 8 of the valveholder. No. 3 pin is left blank. No. 4 is connected to the earthing tag. Next, pin 5 is taken, via a suitable length of PVC wire, to the centre tag of the potentiometer (R<sub>4</sub>). Pin No. 6 is soldered to R<sub>1</sub>, the other end of which is taken to pin No. 8, and C<sub>3</sub> connected from pin 6 to the coil (again see Fig. 3). This completes the actual valveholder soldering operations.

instance. This being so, the wire ends of this condenser must not only be cut to length but must also be covered with a length of systoflex in order to provide some measure of insulation. For connections to the phone jack see Fig. 8, where it will be seen that C<sub>5</sub> is wired to the tag furthest from the chassis wall, while the other tag is taken to chassis (to pin 8 of V<sub>2</sub>). There are four tags on the phone jack altogether, but the two we are concerned with are those comprising the long spring-metal portions which extend through the cut-away portion of the bakelite body. The remaining two tags are not required in this circuit. The resistor R<sub>2</sub> is taken to the other outer tag of the strip (again see Fig. 9). To this same tag connect a nine-inch length of wire, taking

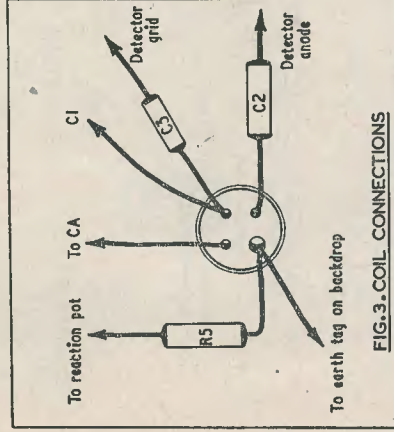


FIG. 3. COIL CONNECTIONS

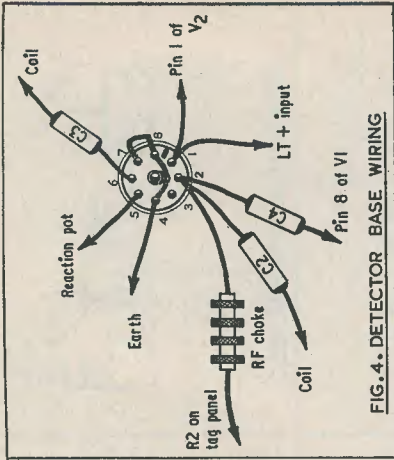


FIG. 4. DETECTOR BASE WIRING

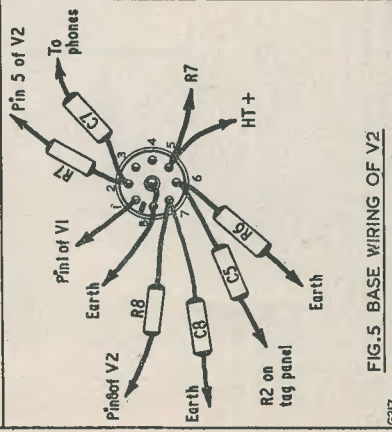


FIG. 5 BASE WIRING OF V<sub>2</sub>

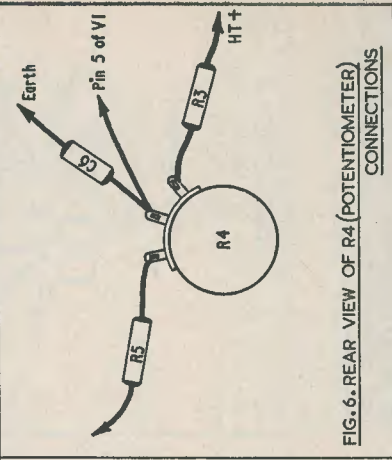


FIG. 6. REAR VIEW OF R<sub>4</sub> (POTENTIOMETER) CONNECTIONS

The next step is to wire up the tag strip (see Fig. 9). On the same tag holding r.f. choke, solder both C<sub>5</sub> and R<sub>2</sub>. Now C<sub>5</sub> has to be connected at the other end to the phone jack—assuming that the receiver is being built as a one-valver in the first

the other end of this through the rubber grommet. This will constitute the h.t. + input to the receiver. Also to this tag solder R<sub>3</sub>, the other end of which is then taken to the right-hand tag on the potentiometer (R<sub>4</sub>), for which see Fig. 6.

Still dealing with R<sub>4</sub>, to the centre tag, on which we already have a wire from pin 5 connected, also solder C<sub>6</sub>—the other end of which is connected to the earth tag contained on the aerial/earth strip bolted to the chassis rear wall. To the left-hand tag on R<sub>4</sub> (Fig. 6), solder the resistor R<sub>5</sub>, the other end of which is then taken to the coil (see Fig. 3).

Dealing with coil connections next, most of which are already done in the foregoing instructions, a study of Fig. 3 will show

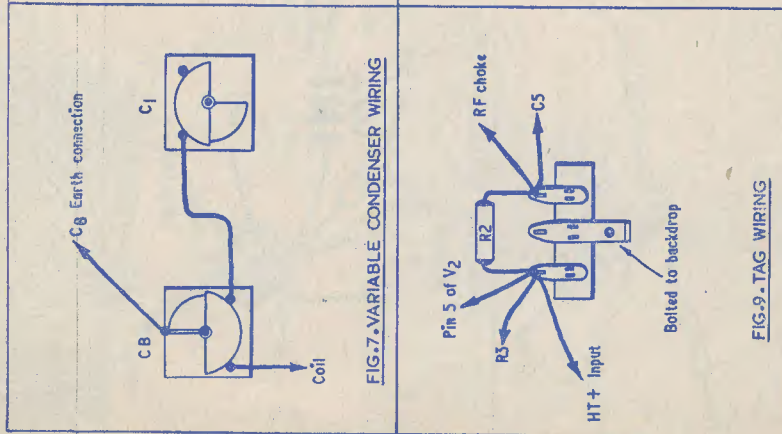


FIG. 7 - VARIABLE CONDENSER WIRING

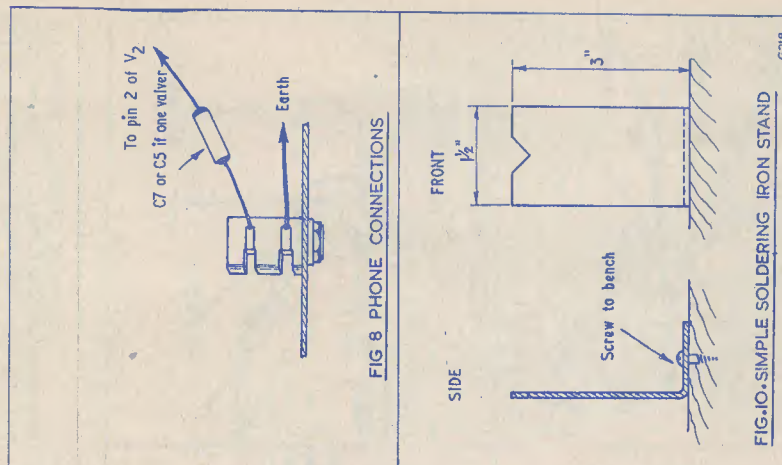


FIG. 8 - PHONE CONNECTIONS

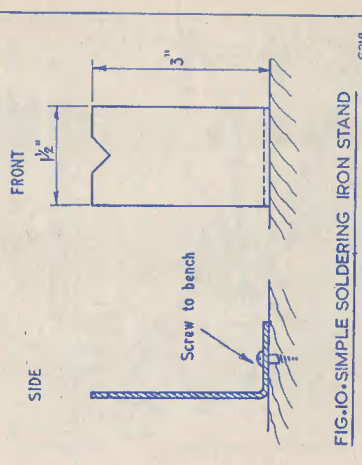


FIG. 9 - TAG WIRING

that the key to these is that pin larger than the remaining three. Base details of this are given when the coils are purchased. (See component list). To the same connection as R<sub>5</sub> (the thick pin), take a wire direct to the earth tag on the aerial/earth strip. From the same pin to which C<sub>3</sub> has been connected, solder a length of PVC wire to the variable condenser C<sub>6</sub>; this latter is the small condenser occupying the central position in

### Putting the One-Valver on the Air

First, insert the valve (EF41) into the valveholder. Next, insert the phone plug into the jack and connect the aerial and earth to the appropriate terminals on the aerial/earth strip (crocodile clips would be an advantage here). Plug in one of the coils—the medium wave one would do—although it is not important which one is finally chosen, except that the signals received on MW are of course stronger in comparison than those on the short waves. Lastly, connect the power unit to the three leads protruding through the rubber grommet. (It is assumed here that the power unit has been purchased already made up. In any event, this was fully described in the

heard. Adjust C<sub>a</sub> for the loudest signal and follow this by slowly advancing R<sub>4</sub> until the receiver oscillates, i.e., a loud breathing sound is heard and the signal becomes distorted. Slowly retard R<sub>4</sub> to a point just below oscillation level. Then, with C<sub>b</sub>, fine-tune the station. For this latter control to be used effectively, always commence operations with this set at a reading of 10. (Details of the perspex pointer and dial are given next month). By slowly turning C<sub>b</sub> from 10 to 100 on the dial, the various signals will appear as they are tuned in. To read C.W. (Morse) signals, R<sub>4</sub> should be advanced slightly into oscillation, when these transmissions will be thrown into relief, as it were, enabling them to be read

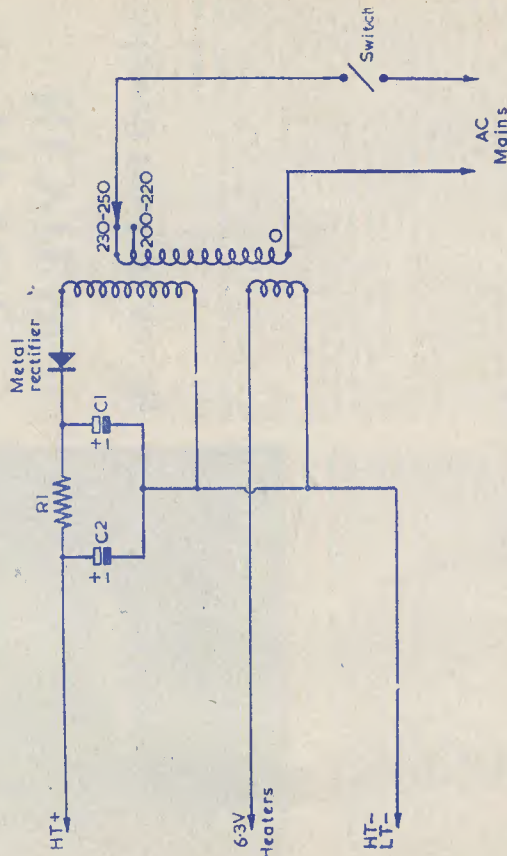


Fig. 11  
Circuit of RCS power unit type PU1

E70

October, 1954 issue of this magazine, copies of which are still available. Alternatively, the company supplying these units will forward full constructional details with the component parts). The leads coming from the power unit are:—Red (h.t.+)—join to tag strip, see Fig. 9; orange (l.t.+)—connect to the wire from pin 1 of V<sub>1</sub> valveholder; black and blue (h.t.— and l.t.—)—join to wire going to soldered earth tag of V<sub>2</sub>. Connect power unit to the mains and switch on.

### Operation of the One-Valver

With C<sub>a</sub> and R<sub>4</sub> at approximately half mesh, slowly rotate C<sub>1</sub> until a signal is

—always assuming, of course, that the constructor has a knowledge of the code. Further operating details are given in Part 3 next month.

### Power Unit Type PU1

For those who require the circuit of this unit, it is presented herewith. It is capable of delivering some 120 volts at 20mA for the h.t. supply, and 6.3 volts at 1.5 amps for the valve heaters. This rating is adequate for the Mini-Receiver and the power unit will be found to run cool at all times—a sure sign that it is not being overworked. (To be continued)

# A SIGNAL TRACER—PLUS

by A. SHAW

After the unit had been in action for some time as a signal tracer, the need arose for a baby alarm and, having a high gain amplifier ready to hand, it was the work of but a moment to insert a second co-axial socket and a microphone transformer, so that now the unit does a double duty, with equal facility in both roles, at the cost of only one amplifier.

No claim is made for originality of design; on the contrary, the circuit will be seen to be depressingly conventional. To avoid undue hum pick-up and any tendency to instability the microphone transformer should be shielded and mounted under the chassis; similarly the input leads to the transformer and to V<sub>1</sub> control grid should be shielded and as short as possible. The decoupling afforded by R<sub>3</sub> and C<sub>4</sub> further reduces the possibility of instability (which may sometimes occur when the probe unit is not connected and a high gain level is set at R<sub>7</sub>), while C<sub>5</sub> removes any r.f. which may have passed through the probe unit. The remainder of the circuit follows closely the lines of the audio stages in any receiver and ultimately drives a 3½ in speaker, through a transformer to match it to 5,000 ohms.


The valves shown in the circuit diagram were chosen in preference to more orthodox amplifier types partially because two were already available in the spares box, but mainly on account of their physical size. The 6X4 and the 6J6 both mount on B7G bases, while the other two use B9A. If extreme portability is not essential, there is no reason why the more normal 1.0-based line-up of 6J7, 6J5, 6V6 and either 6X5 or 5Z4 should not be used, without any circuit value changes at all. In the miniature valve line there are no readily available equivalents to the 6BR7 or 6BW6 that would not require circuit modifications, but the 6J6, of which only one half is used, could, with suitable reconections at the valveholder, be replaced by an EAC91, which has more modest filament current requirements, 0.3A as opposed to 0.45A.

Experienced constructors will readily realise what component values must be changed in order that they may use their pet valves, or valves they happen to have available, but in general the valves shown, or their I.O.-based equivalents, or any combination of the two types, should be used.

THE UNIT DESCRIBED IN THIS ARTICLE AND shown in the accompanying circuit diagram was originally conceived as a signal tracer during a mood of black despair caused by an obscure fault in one of those veteran receivers, the insulation on whose wiring is apt to fall off in generous flakes if it is disturbed. In these receivers and, fortunately, more rarely in some more modern types, it is usually necessary and certainly advantageous to be able to monitor valve bases and other suitable points with a thin probe so that the wiring is disturbed as little as possible. If such a probe is feeding a device capable of reproducing, at a comfortably audible level, either by earphone or loudspeaker, whatever signal is present at the monitored point, then finding those less obvious faults which often occur is much less difficult. Assuming that such a fault does not lie in the first tuned circuit, which is relatively unlikely and, in any case, becomes immediately apparent, it is only necessary to probe the frequency changer or r.f. amplifier grid, tune for maximum output from the tracer and successively to monitor suitable points through the receiver in order to localise the stage on which maximum effort must be concentrated. To achieve impartial reproduction of r.f. or audio signals with one probe unit capable of detecting r.f. and the same probe unit calls firstly for a passing audio signals and, secondly, for relatively high gain, since tuned circuits cannot conveniently be incorporated in a signal tracer. The probe unit shown in the circuit diagram does all that is required in this respect, while the gain provided by the circuit as shown is sufficient to reproduce all the stronger signals which are present on an indoor aerial in an area notorious for its bad reception, without, of course, any sort of tuning whatever.

The usefulness of a signal tracer is by no means confined to "awkward" receivers; any receiver having a fault may be investigated as desired. Being of a conveniently portable size, the writer's unit was endowed with a carrying handle and has several times proved a great labour saver, in that *in situ* investigations have sometimes prevented large and heavy receivers having to be hummed over quite considerable distances for faults which were trivial but not readily apparent.

The usefulness of a signal tracer is by no means confined to "awkward" receivers; any receiver having a fault may be investigated as desired. Being of a conveniently portable size, the writer's unit was endowed with a carrying handle and has several times proved a great labour saver, in that *in situ* investigations have sometimes prevented large and heavy receivers having to be hummed over quite considerable distances for faults which were trivial but not readily apparent.

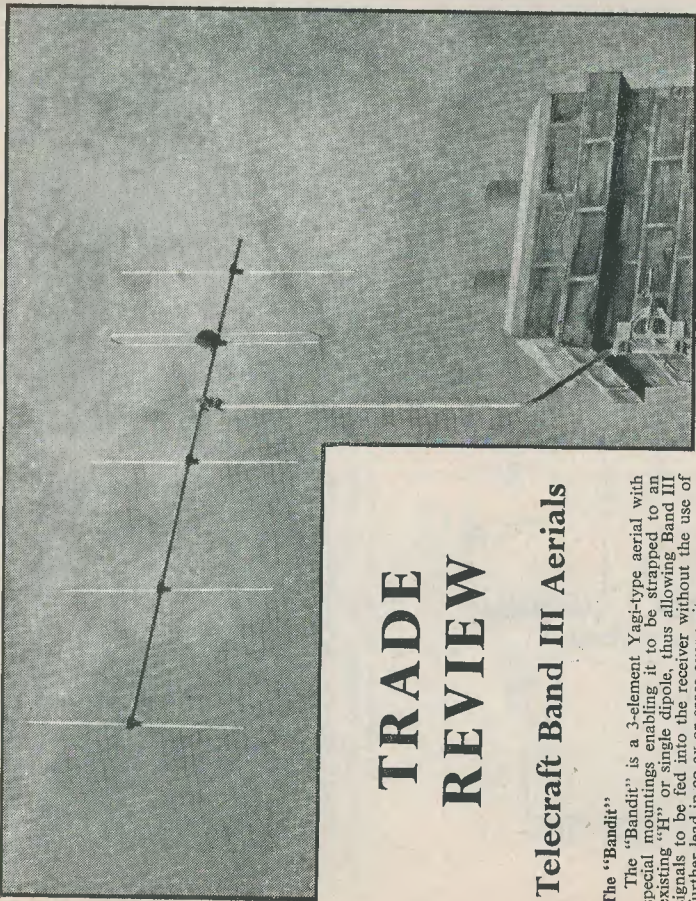

## TRADE REVIEW

### Telecraft Band III Aerials

#### The "Bandit"

The "Bandit" is a 3-element Yagi-type aerial with special mountings enabling it to be strapped to an existing "H" or single dipole, thus allowing Band III signals to be fed into the receiver without the use of further lead-in co-ax or cross-over units.

It is of unusual design in that the spacing differs from orthodox principles, the director being 4-waves spaced from the driven dipole and the reflector 1-waves spaced. The aerial is constructed of specially treated aluminium alloy giving great strength, yet the unit weighs only 12 ounces approx. All elements are insulated from the boom by polythene insulators.

A specially designed mounting enables the "Bandit" to be rotated through a full 360° irrespective of direction of the Band I aerial. This facility is of great assistance in obtaining maximum signal strength, and also the reduction of "ghosting", where this is encountered. The "Bandit" is, in fact, a complete fringe area assembly, the characteristics being approximately similar to an array of this type designed for these areas.

When attached to a standard 1/7th wave "H" type aerial, the forward gain is 6 db, front to back ratio 8 db, and the acceptance angle at half power points is better than 40°.

Some readers may require to know how it is possible to connect a Band III to a Band I aerial without loss of signal to either arrays. The answer is that it is merely a question of relative impedances—so what the value of impedance at the centre of one array looks like to the other. A half-wave driven element, at its resonant frequency, has an impedance which rises from 70 Ω at the centre to a figure of several thousand ohms at the ends. A full-wave element, assuming one was used, would therefore have a high impedance at the ends with two low impedance points a quarter wave from each end. A Band I dipole is practically four times the length of an element cut for Band III, therefore its centre impedance looks like several thousand ohms to the centre of a Band III aerial connected in parallel, hence the loss to the latter is negligible. Conversely, the short element of the "Bandit" array looks like a high impedance to the Band I aerial, hence they can both be connected to the same feeder and no cross-over unit is required. Thoroughly recommended to our readers, the "Bandit" Band III array is most interestingly priced at £1 10s., free delivery in London area. It is available to readers direct from the manufacturers: Telecraft Ltd.,


Quadrant Works, Wortley Road, Croydon, Surrey. Telephone THOrnton Heath 1191/2/3, or from retailers.

The "Bandit" Band III array has been tested and used by us at a distance of some 35 miles from the experimental transmitter with excellent results. Added to a normal "H" type aerial the results achieved fully justify the manufacturer's claims. With the added advantages and consequent saving of having no additional lead-in and cross-over unit, we feel the "Bandit" will become very popular with our readers. Complete with a Band I "H" aerial and all fittings, the whole assembly is priced at £5 2s. 6d. Complete with a single dipole Band I aerial the cost is £2 10s.
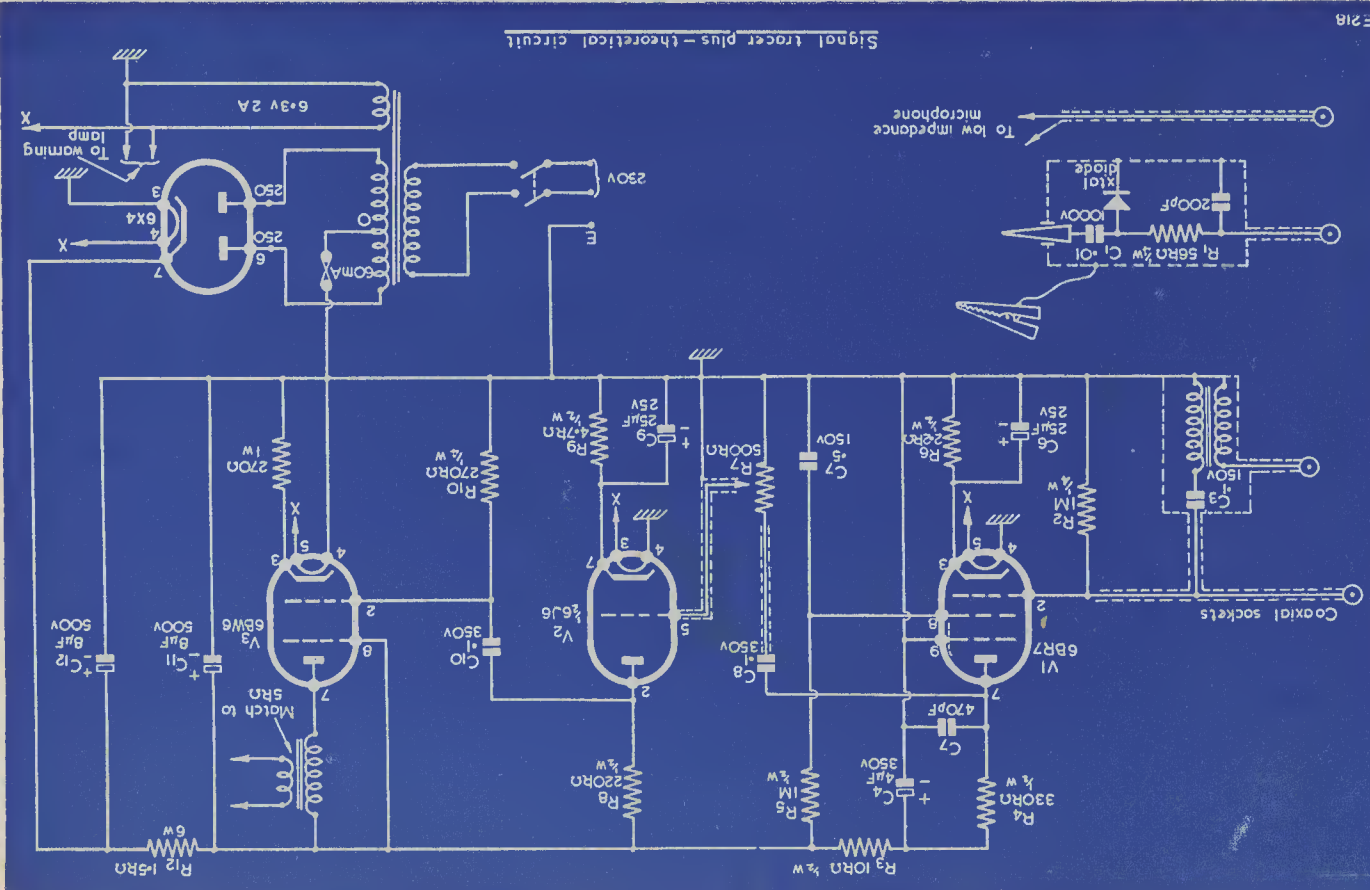
#### Type 503A—503

The 503A Band III aerial is a 5-element Yagi with folded dipole. The construction and spacing follow orthodox lines except that all elements are insulated from the boom, the whole assembly being fabricated from special heat treated aluminium alloy giving great strength with minimum weight. This is of great importance as it is assumed that the majority of Band III aerials will be required to be fitted to existing masts. The aerial is supplied with a unique fixing plate enabling the aerial to be mounted on an existing mast either in the foot or on a gutter board.

The cable connector consists of a weather-proof polythene box having insets for either standard or semi-spaced cables. Using a ¼-in outside diameter tube for the elements enables the utmost efficiency to be obtained at these frequencies, and the gain shown is 8 db with a front to back ratio of 9½ db. The forward acceptance angle at half power points is better than 25°. The type 503A aerial is priced at £2. Complete with 100 ft. of 1/8-in. diameter chimney flashing or wall brackets it is £3 10s. 6d. (type 503, as shown in heading). As with the "Bandit", it is available to readers direct from the manufacturer. This array is recommended to readers who require a separate Band III aerial. The connecting co-ax should be of the 80Ω impedance type.



E 218

The wattage rating of resistors and the voltage rating of capacitors are shown on the circuit diagram; particular note should be made of the voltage rating of  $C_1$  in the probe unit. The probe will often be applied to points which are at h.t.+; thus it is very necessary to have a capacitor of adequate voltage rating in that position. 1,000 VDCW may seem somewhat high, but in fact this component is not physically large and it is better to be safe than sorry.

The power supply is derived quite conventionally, with a 6X4 and an R-C filter. The 6X4 happened to be available, but there is no reason why a metal rectifier of adequate voltage and current rating should not be used instead. The unit takes 41 mA at 230V h.t., so a 60mA component, say two RMI's, would be quite satisfactory and would also provide a little extra space. Any mains transformer having a centre-tapped secondary giving an output of the order of 250/275V at 50mA, together with a heater winding giving 6.3V at 2A, for a normal mains input, will suffice. The primary limitation is one of physical size, but of course this is entirely up to the individual. The R-C filter was used mainly in the interests of size, but in the event there turned out to be quite enough room for a midge choke. However, the R-C filter yields a quite acceptable hum level; but if a metal rectifier is used a choke, suitably rated, would probably be a better choice.

The probe unit, which connects to the amplifier unit via a suitable length of screened cable and a co-axial plug, was originally contained within one of the screening cans that in days gone by were used to screen those massive coils, but since reading the article by W. S. Burrows in the March issue, the writer has been given to realise how pitiously primitive this arrangement is.

Potential constructors arc, therefore, recommended unreservedly to Mr. Burrows' proposed probe case.

The microphone is of the low impedance type only because it happened also to be available when the need for it arose. If, however, a high impedance type is available it can of course be used without a transformer, in which case both the microphone and probe leads can be terminated in a co-axial plug and the same socket in the tracer can be used for either. Whether a high or low impedance type is used, the lead-in cable should be screened.

The method of using the tracer has already been mentioned. It should be borne in mind, however, that it is essentially a device for locating faults which have not yielded to normal preliminary tests. The writer once knew a serviceman in America who got steamed up to such a pitch of enthusiasm over how easy fault-finding was with a signal tracer that he always used it as a matter of course, to the exclusion of more basic preliminary investigations. As a result he once spent over 30 minutes looking for a fault which in the event turned out to be a dud fuse in the wall socket. Used as a trouble shooter where normal tests fail to pinpoint the fault, it will more than repay the trouble taken to construct it. In addition, one always has a high gain amplifier to hand, which is sometimes an asset in a workshop; one also possesses a baby alarm and even a standby radio. The writer's unit was once used in conjunction with a coil and a condenser as a sick bed radio for a child. The selectivity was appalling, but the child was very happy. Most of the required components are available in any spare box, and the initial outlay is modest indeed for the service one can reasonably expect to obtain.

## NEW LABGEAR

Labgear (Cambridge) Ltd. announce a new version of their well-known LG300 Amateur Bands Transmitter, which was reviewed in our March issue. The new version is known as the LG300 Mark II, and embodies many improvements over the original model. The cabinet is even more distinctive, being finished in a dual shade of grey.

As will be remembered, the most noteworthy features of this design are the extensive harmonic filtration combined with tuned harmonic rejector circuits, making TV1 just about as much suppressed as it possibly can be at the transmitter end.

A harmonic check point is provided for test purposes, and reduced power "tune-up" facilities are also incorporated. Thorough shielding is provided, but this has not been carried out at the expense of efficient ventilation. An 813 handles the full 150 watts at A1 or

## TRANSMITTER

A3 without any signs of overheating. The 10, 15, 20, 40 and 80 metres bands are covered, and the calibrated VFO is really stable.

As our readers will know, this unit is designed to provide the Amateur with a transmitter in which all the difficult aspects of transmitter construction to cope with present-day requirements has been carried out. The construction of power supplies and the modulator is still well within the constructional ability of the average amateur. Adequate TVI-proofing, etc., is not so easy for those with limited laboratory facilities. Here is the unit to use with existing power pack and modulator.

At 55 guineas complete except for the 813, or 51 guineas less all valves, it represents a very economical way of acquiring a modern amateur transmitting station. Full details are available on receipt of an S.A.E. from Labgear (Cambridge) Ltd., Willow Place, Cambridge.

# BAND III TELEVISION for the HOME CONSTRUCTOR

## PART 4: A HIGH-GAIN BAND III CONVERTER

by S. WELBURN

*Following upon last month's double-pentode unit, we now present an up-to-the-minute Band III converter using the latest valves and techniques. The description of this converter represents yet another contribution to our Band III series by that popular writer on television topics—S. Welburn.*

**I**N LAST MONTH'S ISSUE WE DESCRIBED A Band III converter employing the Teletron two-pentode coil-set. This unit was capable of being built upon ready-drilled chassis which were available from advertisers in *The Radio Constructor*; and it was designed to give the special qualities of simplicity of alignment and construction.

Since that article was written, a considerable amount of research has been carried out with the intention of producing a cascode, triode-pentode converter which not only possessed similar qualities, but which also gave the greater gain associated with these valves. This work has now been completed; and the unit described in this article is the result.

### The New Converter

Before proceeding with a description of the circuit and layout, a few general comments on the new converter might be advisable at this point.

To begin with, the new converter employs exactly the same chassis as did the earlier model. Thus, chassis offered by advertisers for the "Teletron Band III Converter" are applicable either to the two-pentode or to the cascode, triode-pentode version.

The new converter can be run from the same heater and h.t. supplies as was the two-pentode unit. However, due to the various different types of cascode and triode-pentode now available, the heaters of the unit may, alternatively, be connected into an 0.1 or 0.3 amp series heater run.

The recommended h.t. voltage should be between 180 and 250 volts. At 200 volts, consumption should normally lie between 20 and 25mA.


### The Circuit

The circuit of the converter is illustrated in Fig. 1.

In this diagram the Band III 75 ohm aerial input connects to the coupling coil  $L_1$ . This couples into the tuned coil  $L_2$ , and is designed to provide maximum transfer of signal energy from the aerial to the grid-cathode input circuit of  $V_1(a)$ . A neutralising circuit is provided by the condensers  $C_1$  and  $C_2$ , these helping to increase the signal-noise ratio.

The anode of  $V_1(a)$  feeds into the cathode of the earthed-grid triode  $V_1(b)$  via  $L_3$  and  $R_3, C_3$ . The purpose of  $L_3$  is to provide accentuation of frequencies near its own resonant frequency (in conjunction with circuit strays). The tuning circuit of  $L_3$  is, however, slightly damped by  $R_3$  in parallel with  $C_3$ ; this arrangement causing  $L_3$  to be effective over a greater band of frequencies than would otherwise be the case.  $R_3$  is not, incidentally, intended to act as a cathode bias resistor for  $V_1(b)$ , and it is quite in order to return  $R_4$  to the upper end of this resistor.

$V_1(b)$  functions as the second half of the double-triode cascode and its anode feeds into the pi-network formed by  $L_4$ , together with the capacities to chassis existing at either end of this coil. The input impedance at the grid of  $V_2(a)$  is very low at Band III frequencies, and it is possible to obtain an accurate degree of matching for individual converter units by varying the value of  $C_6$ . For this reason it has been decided not to specify a particular value for this condenser, but to leave its final capacity to be chosen by the constructor. Out of several prototypes constructed and tested, optimum results were given by values ranging between 2,000 and 4,000pF. The final value of  $C_6$  is not,

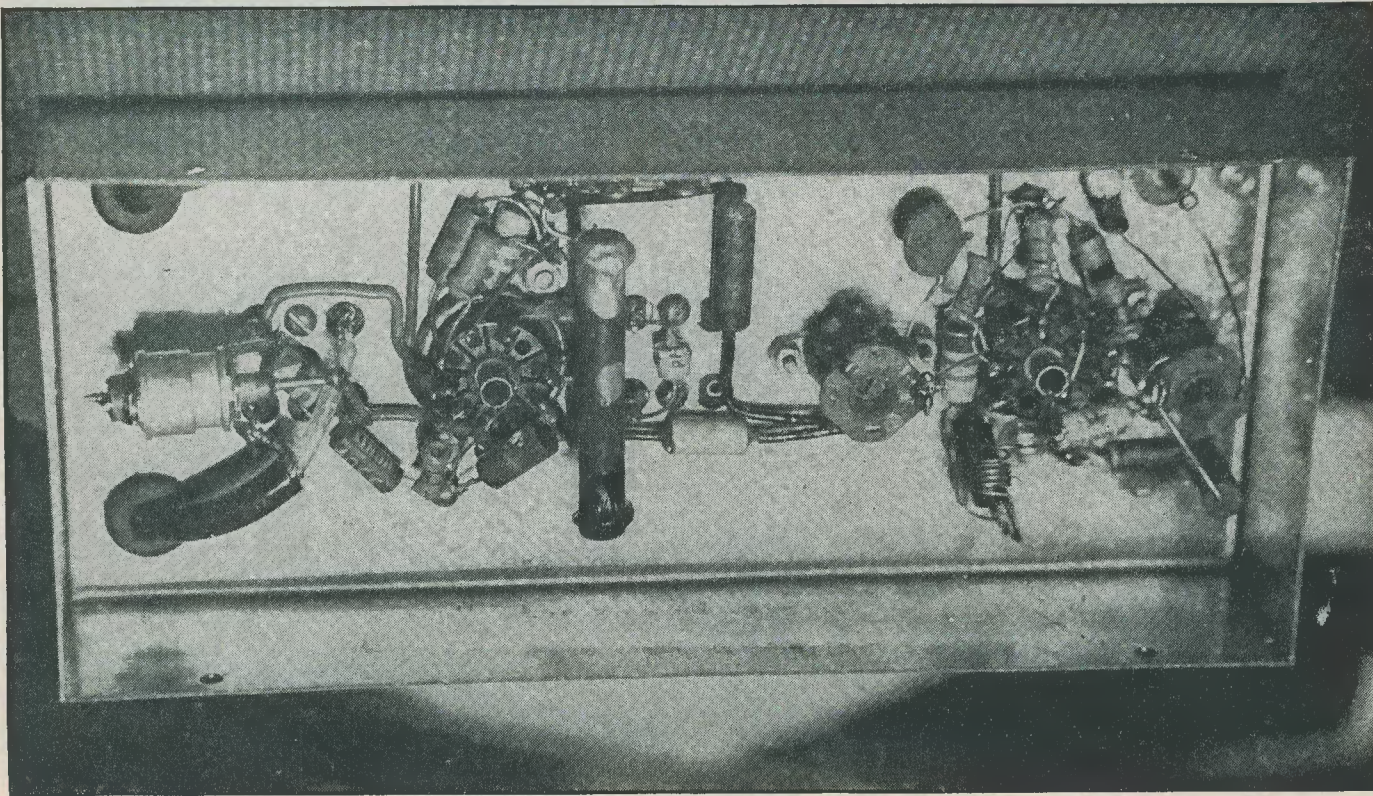

Underneath layout of the Teletron Mark 2 Band III Converter



incidentally, very critical; and the constructor is advised to commence building with a component at this position whose value is 2,000pF.

It was found that there was no necessity to couple the triode oscillator section, V<sub>2</sub>(b) of the triode-pentode to the mixer, V<sub>2</sub>(a); more than adequate oscillator transfer occurring through the stray capacities existing in the valve and valveholder. Indeed, the addition of a coupling condenser is liable to cause the appearance of too high a heterodyne voltage on the grid of the pentode, and may even cause a slight loss in conversion conductance.

The i.f. appearing at the anode of V<sub>2</sub>(a) is fed to the i.f. transformer, T<sub>1</sub>, in conventional manner. T<sub>1</sub> is tuned to Channel I, and has a response broad enough to pass the video signal without attenuation of higher frequency modulation. A coupling coil in T<sub>1</sub> transfers the i.f. built up across the primary to 75 ohm cable for connection to the aerial input socket of the Band I television receiver.

#### Heaters

The heater circuit is not shown in Fig. 1. This is due to the fact that this may vary for different types of cascode and triode-pentode. If the converter unit is to be run from a 6.3 volt heater supply, the valves required will be ECC80 and ECC84. The heaters of these valves should then be wired as shown in Fig. 2 (a). There is little which requires further description here, save that the earthy heater connection to each valve is taken direct to the chassis at an adjacent point.

If a series heater run is decided upon, the circuits of Fig. 2 (b) or (c) may be employed. The valves now required will be UCF80 and UCC84, assuming an 0.1 amp heater supply; or PCF80 and PCC84, assuming a 0.3 amp heater supply. The circuit of Fig. 2 (b) applies to the case when the converter valve heaters are at the "chassis end" of the heater chain; and that of Fig. 2 (c) to the case when the heaters of several valves in the associated television receiver are inserted between those in the converter and chassis. If the series heater arrangement is employed in conjunction with the valves in the television receiver, the chassis of the latter must be bonded by a separate wire to the chassis of the converter. Normally, this bonding will be provided automatically by the h.t. negative lead. On no account, however, should the outer conductor of the co-axial cable joining the converter and the receiver be relied upon alone for this connection; a separate lead is essential.

*It cannot be emphasised too strongly that, in the event of the converter unit having a live chassis, the normal precautions against shock must be observed. This applies especially to the aerial, and an aerial isolating arrangement*

similar to that described in last month's issue should be regarded as essential under live chassis conditions.

#### Layout

The layout of the converter is illustrated in Fig. 3. This layout applies to the 6.3 volt heater version and shows the wiring applicable to the circuit of Fig. 2 (a). Slight alterations in heater wiring will be required if the circuits shown in Figs. 2 (b) or (c) are used. In the case of Fig. 2 (c) an additional anchoring point will be required for the extra heater connection, and the 3-way tag-strip should be altered to 4-way. The layout of the altered heater wiring is not of considerable importance; and the leads concerned may follow the route of the single heater wire shown in Fig. 3.

In Fig. 3 most of the components have been illustrated as having longer leads than would be the case in practice. This has been done to provide increased clarity in the diagram. When the converter is being constructed, all component leads must be kept as short as possible (see photo). Components carrying r.f., such as C<sub>7</sub>, should be spaced away from the underside of the chassis. Decoupling condensers, such as C<sub>4</sub>, need not be so spaced.

#### Alignment

The alignment of the converter requires a little more time than does that of the two-pentode version described last month, but this is only because there are more Band III tuned circuits and, in consequence, more variables to take into account. The instructions which follow apply to the case where the constructor has no signal generator.

The television receiver and converter should be switched on and allowed to warm up. The television should then be receiving the Channel I signal.

The Band I aerial is next disconnected from the television aerial socket and connected (via 0.001 μF isolating condensers of the correct voltage rating in the case of a live chassis) between the grid of V<sub>1</sub>(a) and the converter chassis. The converter output is connected to the aerial input socket of the television.

The Channel I signal should now reappear. If necessary, the receiver contrast may be increased to allow this to occur. The core of T<sub>1</sub> and C<sub>12</sub> are next adjusted for maximum Channel I signal, turning down receiver contrast as alignment proceeds. There will be an optimum combination of settings between the core and the trimmer, and alignment should be carried out bearing this point in mind.

The Band I aerial is next removed, and the Band III aerial connected to the input of the converter. The receiver contrast control is then set to its "maximum" position. The

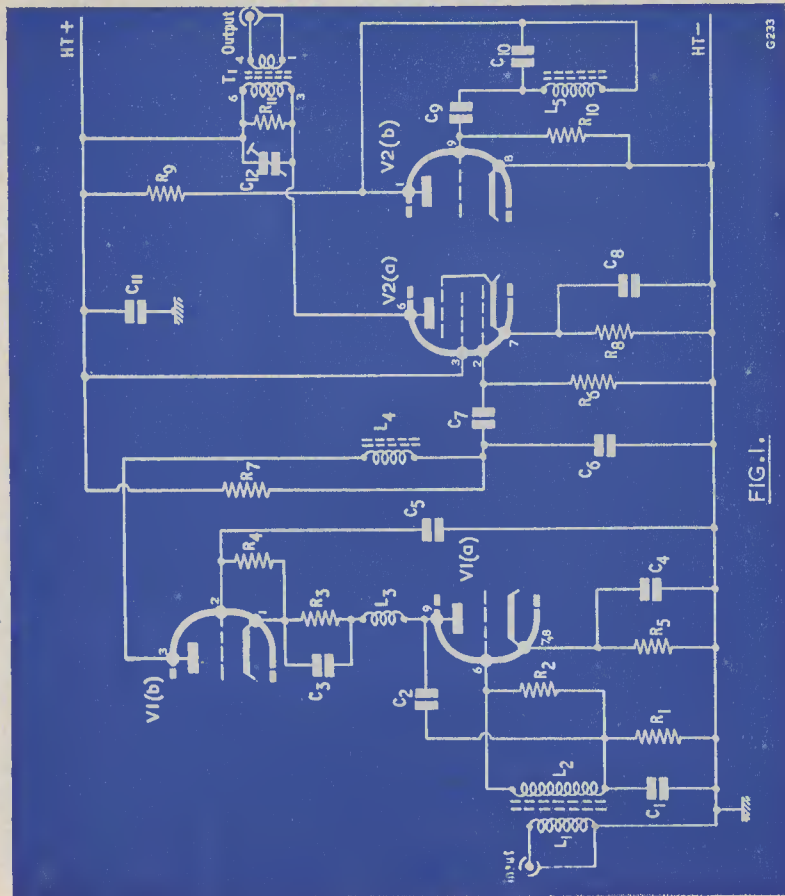


FIG. 1.

Fig. 1. Circuit diagram of the cascode, triode-pentode converter

#### COMPONENTS LIST

Resistors (all ½-watt unless otherwise stated)	C <sub>8</sub>	1000pF	
R <sub>1</sub>	47kΩ	C <sub>9</sub>	10pF
R <sub>2</sub>	10kΩ	C <sub>10</sub>	3pF
R <sub>3</sub>	100Ω	C <sub>11</sub>	1000pF
R <sub>4</sub>	22kΩ	C <sub>12</sub>	Trimmer, concentric
R <sub>5</sub>	120Ω	Valves	
R <sub>6</sub>	220kΩ	V <sub>1</sub>	ECC84 or equivalent (see text)
R <sub>7</sub>	1kΩ	V <sub>2</sub>	ECC80 or equivalent (see text)
R <sub>8</sub>	680Ω	Coils	
R <sub>9</sub>	10kΩ 1 watt	L <sub>1</sub> , L <sub>2</sub>	Aerial input coil. Green Spot
R <sub>10</sub>	22kΩ	L <sub>3</sub>	Peaking coil. Teletron
R <sub>11</sub>	5.6kΩ	L <sub>4</sub>	Coupling coil. Blue Spot Teletron
Condensers		L <sub>5</sub>	Oscillator coil. Red Spot Teletron
C <sub>1</sub>	10pF	T <sub>1</sub>	I.F. Transformer. Yellow Spot
C <sub>2</sub>	2pF		Teletron
C <sub>3</sub>	100pF		All coils available as Coilset "Mark 2"
C <sub>4</sub>	1000pF		Teletron.
C <sub>5</sub>	1000pF		
C <sub>6</sub>	see text		
C <sub>7</sub>	25pF		

cores of L<sub>4</sub> and L<sub>2</sub> should be adjusted such that their upper surface is approximately flush with the upper surface of the chassis. (The cores are clearly visible through the polystyrene formers.)

The oscillator core is now very slowly and carefully adjusted until the Band III signal

In areas of very weak signal strength it is possible that the initial settings of L<sub>2</sub> and L<sub>4</sub> may have to be fairly close to their final settings if the Band III signal is to be primarily picked up. In such a case it will be necessary to try several combinations of these cores before tuning L<sub>5</sub> through its range.


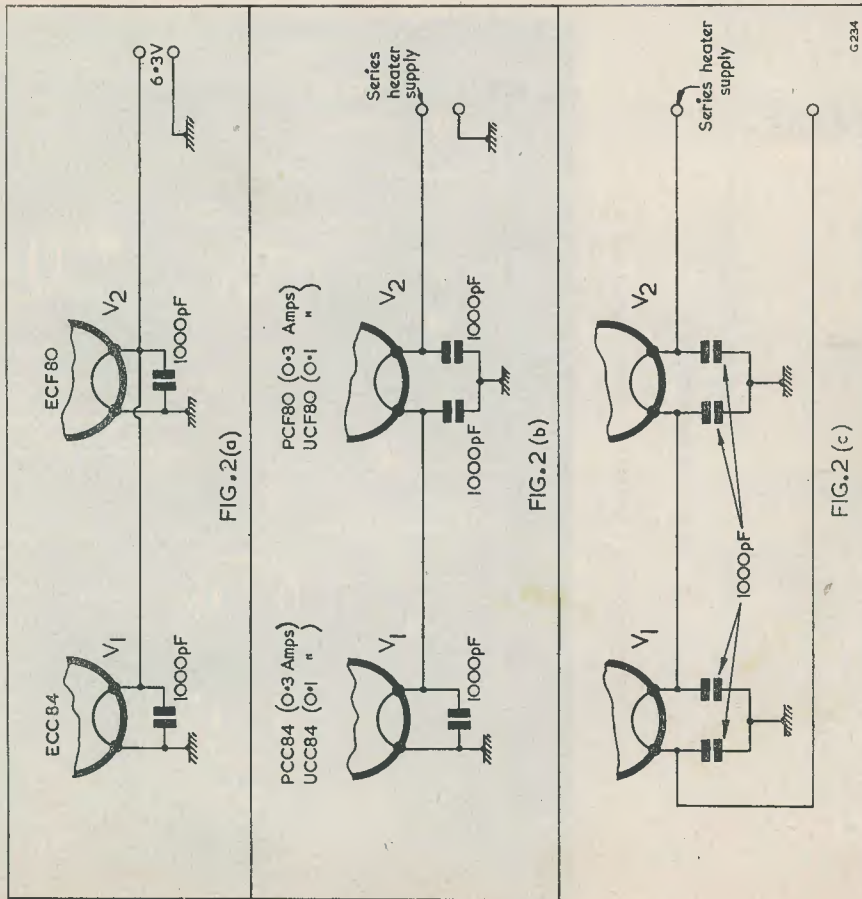


Fig. 2 (a) Heater circuit required for a 6.3 volt supply  
 Fig. 2 (b) A suitable arrangement when a series heater supply is employed  
 Fig. 2 (c) The circuit used when heaters in the television receiver are connected between those of the converter and chassis

becomes visible upon the screen, or audible from the loudspeaker. L<sub>2</sub> and L<sub>4</sub> are then adjusted for maximum signal, reducing receiver contrast as necessary. Adjusting L<sub>4</sub> may slightly off-set L<sub>5</sub>, which should be consequently re-tuned.

(To be continued)

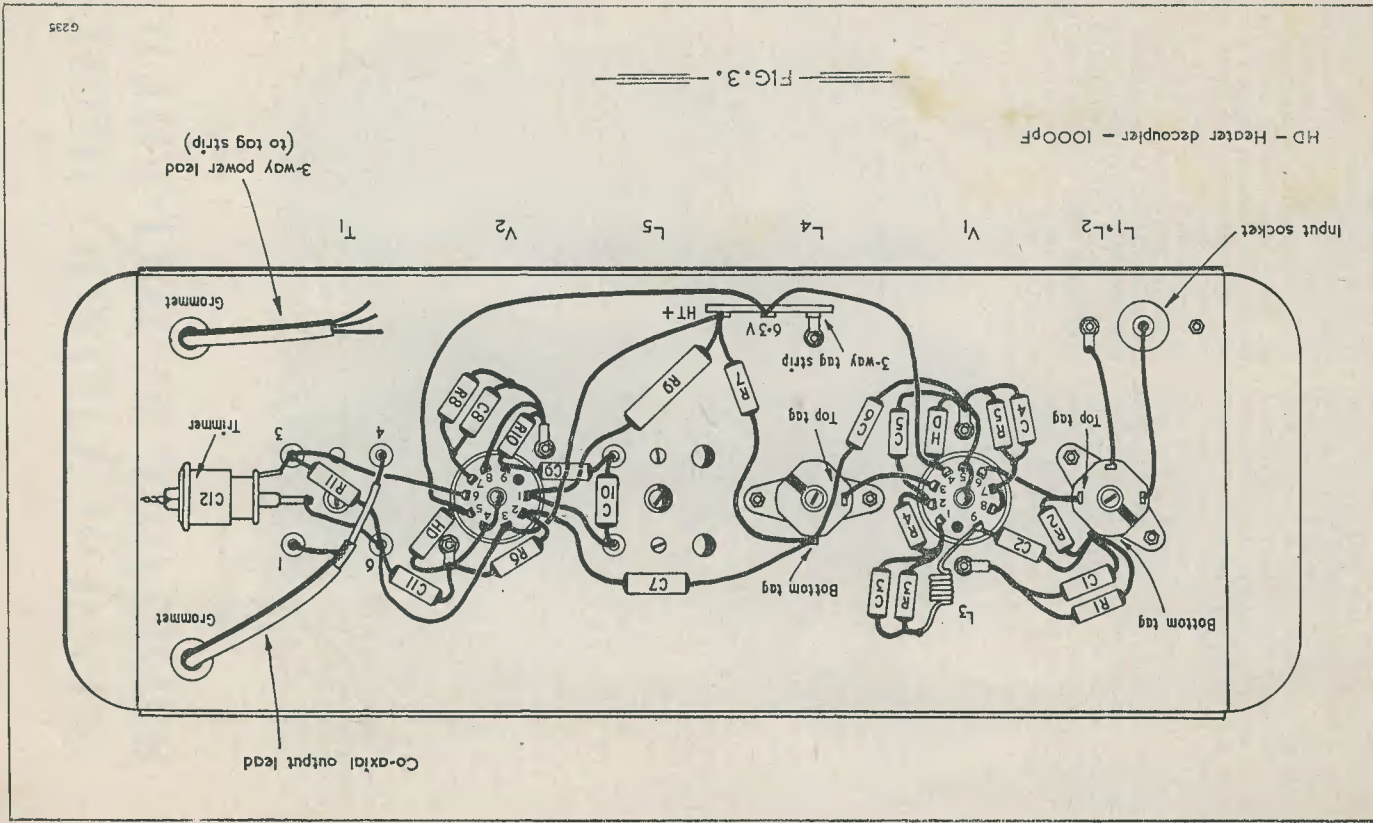

# HIGH QUALITY 10 WATT ULTRA-LINEAR AMPLIFIER

PART I.

by L. F. SINFIELD

WITH THE PRESENT AVAILABILITY OF HIGH quality recordings and increasing use of lightweight high fidelity pick-ups and wide range speakers, there is an understandable enthusiasm for suitable high fidelity amplifiers. Much of this originates from the very popular "Williamson" design, which set an extremely high standard and was very widely copied in home-construction form and also commercially.

However, this particular amplifier is extremely bulky and physically generally too large for most domestic or small hall applications. Also, the high h.t. voltage makes the use of the standard range of electrolytic condensers unsuitable and higher voltage, more expensive, types necessary. Another complaint common on this unit as applied to home construction is the low margin of stability; and even when these are run under normally stable conditions, exhaustive testing often reveals parasitic bursts under transient conditions and h.f. oscillation with capacitive loading.


It is this desirability to obtain adequate power from an amplifier of reasonably small proportions which has led to the re-introduction of the ultra-linear method of operation, and its understandable popularity. With regard to h.t. current drawn and power output, this method gives an efficiency roughly equal to pentode conditions. The maximum output is also similar to pentodes. Distortion for a given output level is lower than either pentodes or triodes. Output impedance, an important factor in ensuring good speaker damping, is very much less than for pentodes and only a little higher than triodes. Linearity is also very good. All this is not achieved without loss; as the local feedback brought about by the screen tap requires slightly extra grid voltage drive over pentodes, but this is not unduly difficult to allow for in the amplifier design. Therefore, to obtain results at least comparable with triodes it is possible to make an amplifier either give more output, when using the original valves in the new arrangement, or to make an equivalent amplifier output with smaller valves and lower h.t. supplies. For normal use the latter arrangement is by far the more satisfactory, as it then allows the use

of smaller and cheaper components (more conservatively rated) and a reduction in physical size, consumption and overall cost.

The American designers, Hafler and Keroes, who made this type circuit so popular, specify that for K166 type valves the ratio of winding for the screen tap should be 43% for optimum results, but in Britain the published data would indicate that about 20-25% would be more suitable. However, most of the high quality output transformers produced here commercially for this application adhere to the American specification; although this may, of course, be done to satisfy the export market.

For 6V6 operation these same designers specify that the optimum tap ratio is 24%.

For the amplifier design given here type 6BW6 valves are used, as these are noval based versions of the 6V6 and electrically identical. With a mains transformer of 300/0/300V secondary this gives an h.t. line of around 330 volts; a figure which allows standard type electrolytics to be used for smoothing. The reservoir fitted was a paper type, as this was handy, and allowed better reliability, but it can be replaced by an equivalent capacity plain foil electrolytic of about 450/500 volts working. Although miniature valves are used throughout, the rectifier is a standard octal type in order to give very conservative current rating and to ensure adequate continuous sine wave power output and good high power transient response. Under these conditions the amplifier gives over 10 watts continuous sine wave output (this being the actual power measured into a resistor load of 15 ohms). In the region 20-20,000 cycles the output is around 10-12 watts at low distortion. At the high frequency end distortion is just perceptible on a scope at 7.5 watts at 50kc/s. At the low end this occurs at 15 cycles at 8.8w. Beyond these points the output handling capability drops off fairly rapidly, but in any case these are beyond the limits of the recordings and their associated pick-ups. The tone controls are also determined to give a limit to the frequency response. This excellent low frequency power handling is due to the very generous core size of the output transformer.

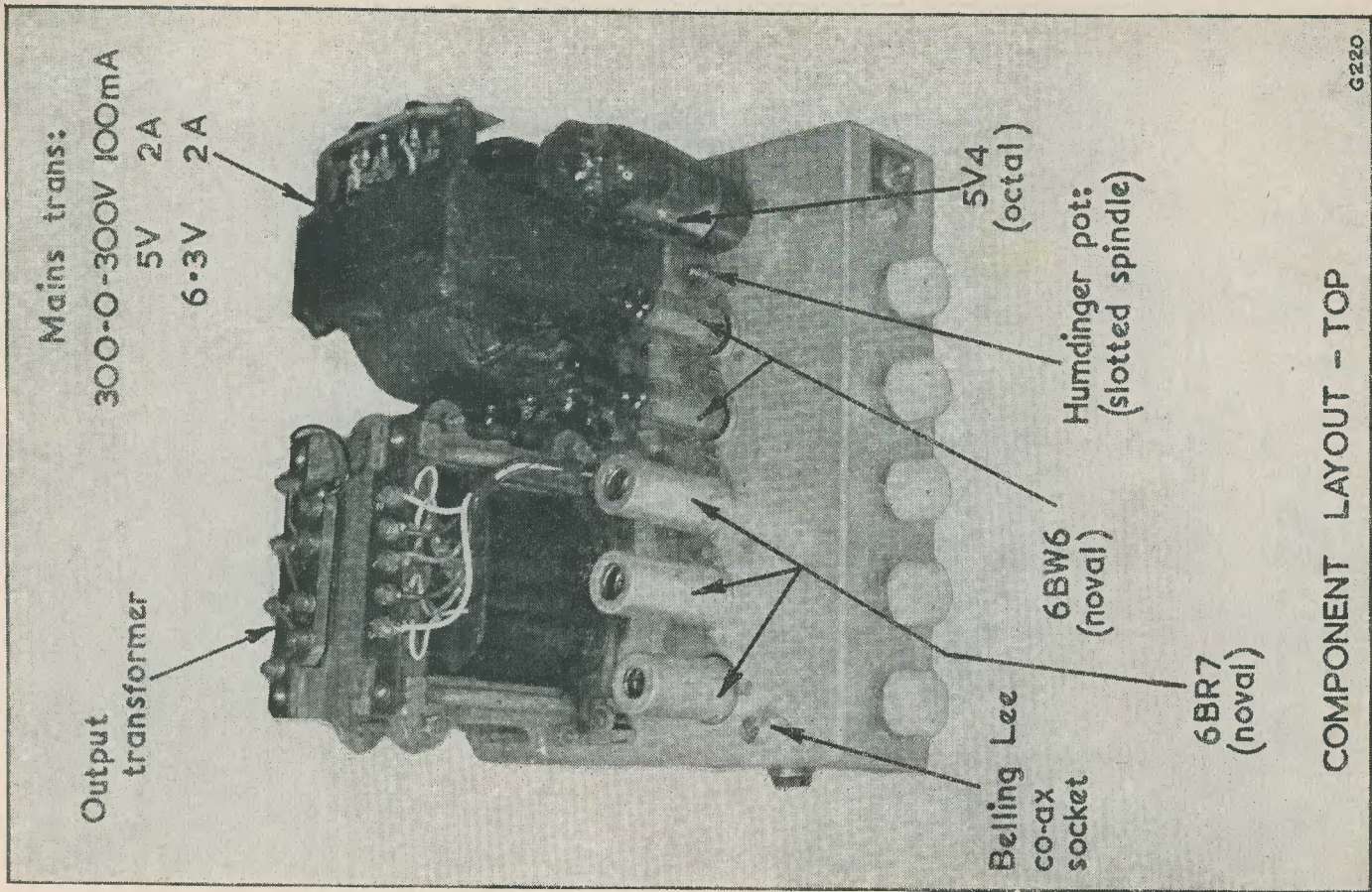


### Frequency Response

The curves are shown for this at a reference level of 5V into a 15 ohm resistor load, this being a probable average mean level of music or similar signal. The input signal source consisted of a sine wave oscillator of constant amplitude covering the range 5.5 cycles to 70kc/s. The input was injected into the main amplifier with the specified 18db of feedback.

Even without feedback the frequency response is reasonably flat over the entire audio range, so that the amount of feedback is fairly constant in this range and maintains the low output impedance, low distortion, etc., well beyond the limits of any speaker into which it will feed. It was felt very desirable to maintain a high damping factor over as wide a range as possible in order to obtain optimum speaker performance.


and rises again slightly to a minus 1db condition at 54kc/s. Beyond this the response falls again and is some 3db down at 70kc/s. It is presumed that it continues to drop further after this point, but this was the limit of the test equipment. The slight rise at low frequency and the slight kink before the fall at high frequency are general characteristics of feedback amplifiers, and similar deviations occur in the Williamson and other similar units. However, these deviations are not of any significant amplitude and are outside the frequency range set by other requirements.

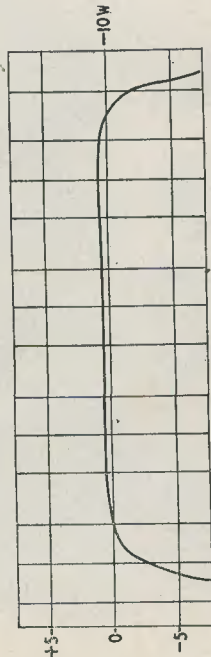At low frequencies there is a tendency to reproduce turntable rumble if the response is extended too far, so that the time constants of the tone circuits and the pre-amplifier stage are set to give some degree of attenuation at these very low frequencies, thus they



POWER RESPONSE INTO 15Ω RESISTOR

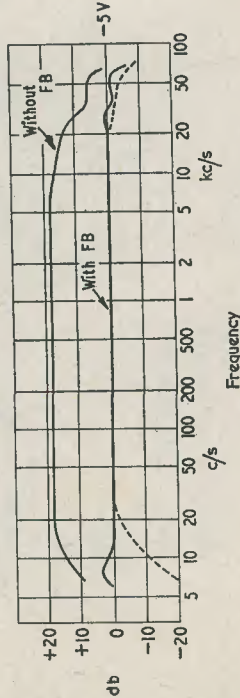
Dotted lines indicate response from PU input (tone controls set to "FLAT")



RESPONSE CHARACTERISTICS

With reference to the mid-frequency level, the output rises approximately 3db at 8 cycles and falls back to zero level at 6 cycles. At the high end, the level rises approximately 0.5db at 30kc/s, falls to minus 2db at 36kc/s,

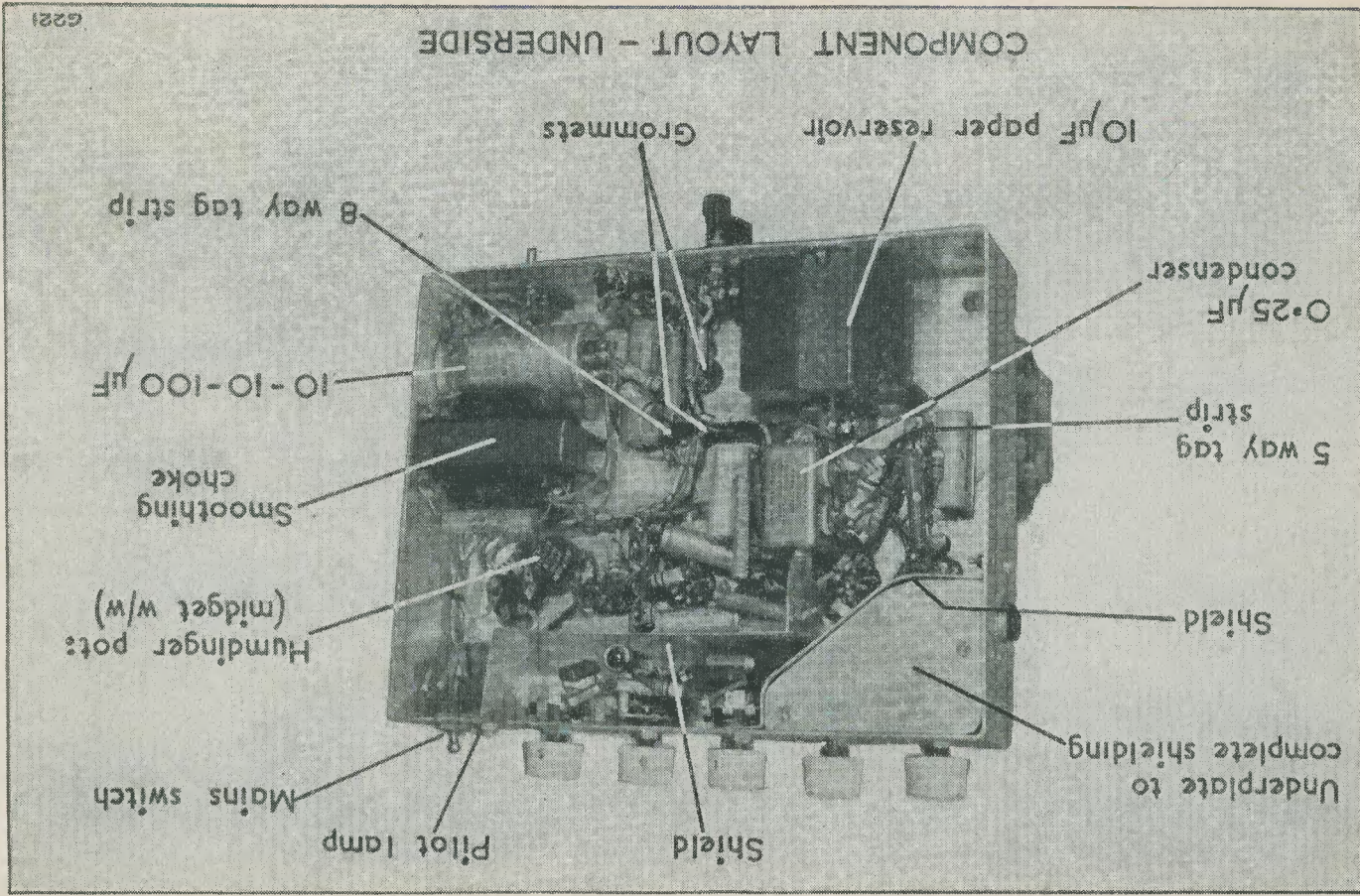do not enter the main amplifier to any extent and the slight hump at 8 cycles assumes no significance. The tone circuits and pre-amplifier constants also give a gentle fall at the high frequency end. With the input into



COMPONENT LAYOUT - UNDERSIDE

G221

the pick-up socket, tone controls set to flat, and volume control approximately half-way, the response falls 3db at 32kc/s—4db at 50kc/s—and 9db at 70kc/s. This easily satisfies the required response. These are the measurements at the "flat" setting, and a considerable plus and minus variation is possible at various settings of the tone controls, both at low and high frequency ends.

**Stability**

This is usually the bugbear of feedback amplifiers, and often the margin existing is too low to maintain absolute trouble free conditions under a wide variation of input signals (particularly transients). Also, the necessities of home construction often mean that there are very minor changes in layout and possibly component specification. Most people have the sense to adhere strictly to the output transformer specification, but there is often a great deal of variation in transformers made commercially, even though they are supposedly to the same specification. It is quite common for a specific amplifier to work satisfactorily with one make of transformer, and not with another made by a different manufacturer advertised as to the same requirements. Therefore a great deal of time was spent in very severe stability testing, and although the precautions taken and the tests themselves might possibly be regarded as over-elaborate in that they allow for conditions almost impossible to occur in practice (unless done deliberately), they do, in fact, ensure an adequate stability margin under any normal conditions.

(a) The output valves chosen are of lower slope than those often used for this type of output stage, and are less likely to suffer from parasites. As an added safeguard, grid and screen stoppers are fitted at the valve pins.

(b) Although only 18db of feedback is used, and this is ample in obtaining optimum output conditions, the correction was set to allow a much greater amount. On test it was found that the feedback resistor could be reduced to a condition of over 30db of feedback before the amplifier developed h.f. oscillation, so that an ample gain margin exists.

(c) As a loudspeaker impedance rises very considerably at some frequencies (particularly when not ideally matched to a cabinet), many experiments were tried with other load resistances and also with an open circuit load as well as speaker loading. Also, various capacities were paralleled with the various loads to determine the maximum capacity loading permissible under widely differing load conditions. Most of the effect of capacity loading is to produce h.f. oscillation at higher capacity values. As the speaker

coil looks like an h.f. choke at these frequencies, these tests can be simulated with a suitable choke. In fact, although speaker and choke were tried, the results under open circuit conditions and with pure capacitive load only, are so similar that this simple test is advised. It was found that under these conditions a resistor across the output raised the value of capacity necessary for h.f. oscillation to commence. This resistor was therefore fitted, even though the amplifier is completely stable without it, as it only absorbs some 2 or 3% of the power output and yet increases the stability against capacitive loading by a considerably greater amount. These tests were also carried out under square wave conditions.

**Circuit**

Primarily the amplifier was designed to work with crystal pick-ups of transcription quality (Collaro Studio "p," etc.) and it is possible that the use of high quality dynamic pick-ups would give insufficient output to fully drive the amplifier; particularly as these require rather more correction. However, a suitable head amplifier could be made as an extension, and an octal socket is provided at the rear of the unit in order to take off the power supply for this and similar purposes.


Following the input socket is a 6-way 2-pole switch, and this is arranged to bring in suitable equalisers for the particular type of pick-up, recording, tuner, etc., in use. Values are given for certain popular pick-ups for 78 r.p.m. and L.P. records. Other values will be dependent on the pick-up and can be obtained from the maker. Some amplifiers use a plug-in type of equaliser, but this could mean sorting out the appropriate plug and fiddling round the back of the amplifier, even to change from 78 r.p.m. to L.P. and vice versa. A switch was considered to be much more convenient.

Following the equaliser and the pre-amplifier are the tone control circuits. No originality is claimed for these, as they are similar to those used in the Osram 912. These give a range of control which covers almost every requirement, so that there is no point in spending time in making up a different circuit to achieve similar results.

The output from the tone control circuits feeds into the main amplifier. The first stage of this is a voltage amplifier. A pentode was chosen as it gives a greater undistorted output swing, and this is necessary due to the output slope and larger grid swing of the output valves. It was felt desirable, also, to reduce the phase shift within the feedback loop as much as possible, and to this end the first stage is directly coupled to the phase splitter.

*(To be continued)*

THE RADIO CONSTRUCTOR

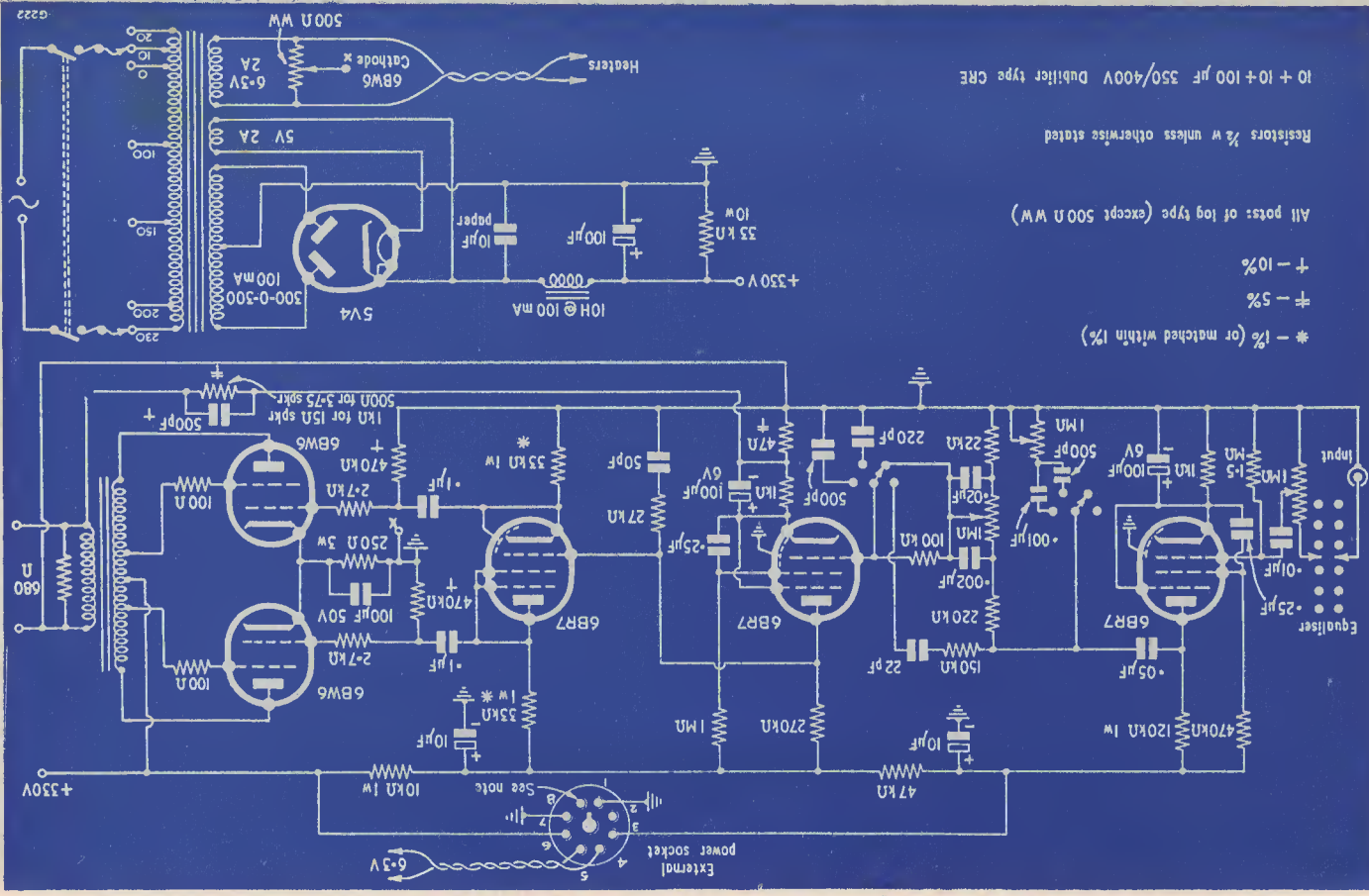

# A CONSTRUCTOR VISITS THE 1955 NATIONAL RADIO SHOW

ONCE AGAIN, THE RADIO SHOW AT EARL'S Court opened late this year. Whatever comments may have been made elsewhere, it can only be recorded here that the German Radio Show commenced on time; but the British show did not.

## Television

The Radio Exhibition this year presented the same familiar scene to your reviewer as it has done for several years past. It was a "quiet" show, but at the same time it demonstrated the solid development work which has been in hand over the last twelve months. In the previous show Band III had captured the public imagination; with the result that Band III sets and associated equipment were in the forefront of almost every manufacturer's publicity campaign. Band III is now accepted as being part and parcel of the television scene, and 13-channel receivers were shown everywhere as standard equipment.

Nevertheless, one or two manufacturers went to considerable lengths to illustrate the effectiveness of their receivers on Band III. Pye, in particular, put on an eye-catching display which was especially impressive. This consisted of thirteen separate receivers ranging along the top of their stand, each of these being tuned to a separate channel and showing a different picture. The thirteen separate signals consisted of the B.B.C. and R.I.C. signals available at Earl's Court, plus pictures picked up by Pye cameras on their own stand.

Ferguson were also very much to the fore. The popular "Halolight" fitted in some Ferguson televisions showed its effectiveness especially well under the varying conditions of ambient lighting given by the show. The "Halolight" consists of a transparent surround around the tube screen which may be diffused with white light at any degree of brilliance desired. The result is a surprisingly strong impression of greater contrast in the picture itself. Ferguson, who have been amongst the first to introduce Band III converters for their existing Band I receivers, exhibited their full range of these converters.

These differ from each other mainly in power requirements. However, their type "C" converter, which was designed for use with their earlier receivers, has an output at Channel 1, and could presumably be used with televisions of any other manufacture.

Converters by other firms were also in evidence, these including the Channel converters, the Ikopatent "Univertex," and the units manufactured by Valradio. Bush exhibited an "opened-out" sample of their "Telepic" tuning control, this being fitted to their converters and televisions in place of the more conventional turret tuner. The "Telepic" covers all 13 channels, tuning being effected by three ganged slugs moving in and out of the appropriate coils. Movement of the slugs is controlled by a cam coupled directly to the 13-position selector knob; whilst fine tuning is carried out by a mechanical device which causes a small amount of movement of the cores. A different set of coils is employed for either band, these being selected automatically by a switch mechanism operating from the selector knob.

The television which captured most attention in the lay Press was the Ekco portable receiver. This set functions either from the mains or from a car battery, drawing 7 amps at 12 volts in the latter application. A pull-out aerial is incorporated, and the screen diameter is 9 inches. A range of 25 to 30 miles is anticipated when the receiver is used with its own aerial. This set will also pick up f.m. on Band II. Its price, when released, will probably be around £60.

The writer, on making enquiries, was shown a small portable monitor developed by Ekco for use by the G.P.O. The portable "civilian" television is a development of this monitor. There were, apparently, only a few of these portable receivers in existence when the Show started, and Ekco were not taking any chances with one of the two they had on display. It was chained to their stand!

## Home-Constructors

This year our new transistor receiver was displayed by Standard Telephones and

Cables, whose transistors are employed in its construction. This little receiver attracted considerable attention from the public and it is due to be described very shortly in future issues. On the S.T.C. stand, in addition, was our A.M.-F.M. Signal Generator—also to be described shortly. The transistor receiver, incidentally, was the only one of its type to be seen.

Mullard devoted part of their demonstration room space entirely to the home-constructor. Members of the Mullard staff were present to deal with technical queries. The new Mullard 20 watt amplifier, employing EL34's in the output stage, was also being demonstrated.

G.E.C. exhibited their new amplifier, the "912-Plus." This amplifier is suitable for radio, tape and mic. inputs. Existing "912" amplifiers can readily be converted to the new version.

Printed circuits for both the G.E.C. and Mullard amplifiers are now available from T.T.C. This firm also exhibited condensers having terminations especially designed for printed circuit work.

To return to transistors again, these were exhibited both by Standard Telephones and Cables, and by Mullard. Mullard had an interesting exhibit which consisted of a small transistor transmitter and receiver. Both of these units employed Ferroxcube loop aerials, and the output of the transmitter was kept to a few milliwatts to prevent interference with other exhibits. For the same reason a low radio frequency was employed—50 kc/s. The receiver was arranged such that its a.f. output was connected to an oscilloscope. Members of the public were then invited to speak into a microphone at the transmitter, whereupon the waveform of their speech was shown by the oscilloscope.

## V.H.F.

Considerable space was given in the Show to v.h.f. sound receivers. It is, indeed, very encouraging to note that the new service is receiving such excellent support from manufacturers. The demise of the present "standard" broadcast superhet, with its attendant whistles and higher audio frequency attenuation, may prove to be earlier than was originally anticipated.

The v.h.f. sets at the Exhibition could roughly be divided into two classifications. The first of these is that in which the f.m. programme is reproduced with somewhat better quality than that given by normal broadcast receivers. In this category, no expensive attempts were made to fully utilise the superior fidelity feasible with the new medium; although reproduction would nevertheless still be better than that normally available on medium and long waves whilst

the quiet background given by v.h.f. would provide an added attraction. The second category is that in which full advantage is taken of the wider frequency range available, and the resultant a.f. circuitry and components approach or are equivalent to those associated with high fidelity reproduction systems. Receivers in the first category started from around £20 upwards, whilst those in the second category were in excess of £30.

## The 1955 Radio Show

The most frequently encountered a.m.-f.m. sets were those in which the v.h.f. band replaced the short-wave band; and such versions were quite numerous. Slightly more expensive receivers incorporated a short-wave band as well as the f.m. band.

There were few f.m. adaptors. One exhibited by K.B. could be used as a simple f.m.—only set or as an adaptor. Others (Dynatron, Ferguson, and H.M.V.) were intended for connection to a subsequent amplifier.

## Other Details

Considerable space was devoted to radio as a career, and a large area of the first floor was occupied by a special "Electronics and Careers" display. This showed specialised branches of electronics (including an effective operating theatre scene, complete with TV camera focused on the operating table) and depicted the various ways in which a young man may advance in this sphere. Be it known, incidentally, that the chief engineer of a company may be drafted just as readily from production as he may from the laboratory.

R.E.M.E., in the Services section, put on an interesting little exhibit, this consisting of a model of the globe which turned in mid-air without any obvious physical means of support. The secret was a heavy a.c. magnetic field in a box just below the rotating globe, the "levitation" being the result of the eddy currents consequently induced in the metal of the globe itself.

A word on the general appearance of the Show may not be out of place before concluding. As always, an effective layout was obtained; but it cannot be gainsaid that the stands seem to be becoming more and more box-like as the years go by. A most welcome break from this tradition was provided by the Philips exhibit. Here the motif was that of the harlequin who features in their advertisements. This firm had two adjoining stands and the manner in which these had been planned in relation to each other was so effective that one felt that one had walked into a separate exhibition altogether.

# A "MARBLE" REFLEX LOUDSPEAKER ENCLOSURE

by F. JOHNSON

THERE COMES A TIME WHEN THE "QUALITY" enthusiast, having done his best to achieve high-fidelity in his amplifier, pre-amp, pick-up, radio tuning unit, etc., realises that the weakest link in the chain is the loudspeaker.

A good L.S. chassis is, however, wasted unless the diaphragm is adequately loaded by a suitable mass of air. Even from a cheap speaker the reproduction can usually be improved by proper loading. It can be taken as axiomatic that best results are secured more easily by mounting the speaker external to the cabinet which contains the radio tuner and/or gramophone pick-up.

The simplest method of mounting the speaker is, of course, the flat baffle board. This prevents the sound wave from the back of the cone cancelling out the wave from the front; obviously these two waves are exactly opposite in phase. The longer the wavelength of the note to be reproduced, i.e. the lower the frequency, the larger the size of baffle required. For the reproduction, without undue attenuation, of the lowest musical frequencies, a baffle size of approx. 6ft. square is necessary—quite simple in a hall but difficult at home.

In order to achieve similar results in domestic surroundings we turn to the popular reflex cabinet. This, briefly, is a cabinet so designed that the front of the speaker cone faces an opening in the cabinet and is therefore loaded only by the volume of air in the room. The back of the cone, however, faces a critical volume of air in a confined space, which is compressed with each backward excursion of the cone.

This pressure is usually relieved by means of small vents or ports in the cabinet, although it can be made airtight (infinite baffle). It is very easy to see that these pressure waves will tend to make the cabinet material itself vibrate in sympathy; this would be in order if it vibrated uniformly at all frequencies but, of course, the cabinet sides have a resonant frequency of their own. Reproduction is affected adversely far more than the uninitiated would suppose, and the obvious requirement is a cabinet free from audible resonances.

It will be found in practice that wooden resonance-free structures of this kind are not easy to make. Naturally the *real* enthusiast gets busy in the front sitting-room with bricks and mortar and so achieves his heart's desire by means of a brick enclosure. As this type of activity is (to say the least of it) frowned upon by the gentler sex, a concrete reflex cabinet has been designed to fit into the corner of a room.

This is pre-cast in suitable surroundings, e.g. on the garden-path, and moved into position when completed: in order to enhance the appearance and render it suitable for inclusion in a nicely furnished room, the outside surface is polished to imitate marble. As concrete is 4 times as dense as hardwood, an enclosure of 2" concrete is as good as a wooden structure having sides 8" thick! When completed, it will be found to look very attractive, and the foregoing theoretical considerations are fully borne out in practice. The bass is crisp and clear without noticeable boom or resonances.

It will be noted from Fig. 1 that the two ports serve the dual purpose of relieving the air pressure inside the chamber and of clearing the skirting boards.

The speaker chassis is mounted on a wooden sub-cabinet constructed as follows: take a piece of  $\frac{3}{4}$ in. plywood or Weyroc 15in.  $\times$  15in. and cut out a circular hole suitable for the speaker chassis being used; plane the edges—not square but at a slight angle. (See Fig. 2). When bedded in concrete this helps to "key" the wooden insert securely. Cut 4 pieces of 1 $\frac{1}{4}$ in.  $\times$   $\frac{3}{4}$ in. timber; plane square one edge only of each. Pin and glue the front to these, making a shallow box as shown in Fig. 3. Punch in the pins slightly below the surface and fill the holes with putty; waterproof glue is best to use but ordinary glue is permissible. All round the perimeter drive nails and screws at different angles but only half-way in. Give a coat or two of cheap oil paint everywhere excepting the front face; smooth this with glass paper and give a coat of undercoating of suitable colour (see later in the text).

The next step is to make the temporary wooden mould for the enclosure wall. This is made of boarding about  $\frac{3}{4}$ in. thick and held together by wood screws (greased before insertion). Once the idea is grasped from the diagrams and cutting list, the reader will no doubt be able to improvise and to utilise existing materials. If old timber is used it should first be scrubbed clean.

The 2 pieces *E* are secured firmly to the bottom ends of the 2 in. wide boards *C* in order to form the ports (see Fig. 6); the panel *F* can be of plywood or hardboard 3ft. 6in.  $\times$  2ft.  $\times$   $\frac{3}{4}$ in. or  $\frac{5}{8}$ in., but will need the support of board *D* underneath owing to the weight of concrete to be laid

The screws fit through the ends *A* into boards *B*, *C*, and *D*, but through the sides *G* into ends *A*. Also through *B* into *C*. Before final assembly the inside surfaces should be coated with grease or crude vaseline. Final assembly should be made on a piece of level firm ground—not soft earth. A few small nails may require to be knocked through panel *F* into board *D* to prevent it slipping, and any small holes or gaps at the edges can be filled with putty.

Now regarding the materials for the concrete—a mix in the proportions by volume of 4 aggregate, 2 sand, 1 cement is recommended, but 6:3:1 or 5:2 $\frac{1}{2}$ :1 are cheaper and would be satisfactory. The aggregate can be white chips of marble


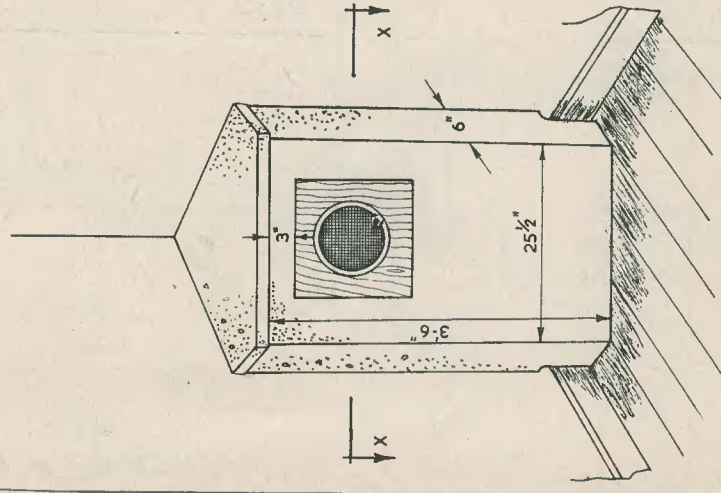


FIG. 1.

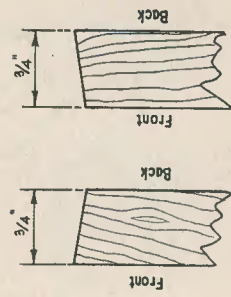

The other 2 opposite sides planed as (a) Edges of 2 opposite sides planed as (b)

FIG. 2.

—either purchased as such or made oneself by cracking up scrap pieces from a monumental mason. The sand should be a good sharp washed sand of good quality. White Portland cement is used, and in order to obtain the appearance of marble it is coloured by means of green, pink, or

on top: it should be supported at the ends by strips of wood 10in.  $\times$  1in.  $\times$   $\frac{1}{2}$ in. nailed to the insides of the ends *A*. (Fig. 7). The wooden sub-cabinet previously made should be temporarily fixed in the middle at a distance of 3in. from the top end (see section drawing).

black pigment according to the effect desired. A small quantity only of pigment is required, say 2 to 4 ozs., and a few experimental tablets can be cast to ensure getting the desired colour and effect. The white cement is rather expensive compared to ordinary grey Portland, so I will explain at this point that I (being an indigent type) made two mixes—approx. half (the inner) being made of grey cement and broken brick; and the outer half, which shows, of white Portland and marble chips. The two kinds of concrete bond together and make just as good a job, with very little more trouble, but at smaller cost.

and pat it down with a straight-edge, level with the top of the end boards A and the front face of the wooden insert. If a plasterer's "float" can be borrowed, so much the better.

The whole thing can, if desired, be reinforced with expanded metal or steel wires. If there is any danger of frost the job should be given protection. When the "initial set" is completed in a few hours (say 24-hours for convenience), the outer boards G should be unscrewed and gently removed. The whole of the outside surface is now exposed; it should be rubbed down smooth with a flat piece of carborundum stone, using plenty of

6200

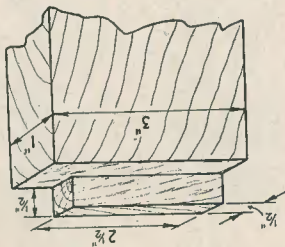


FIG. 5.

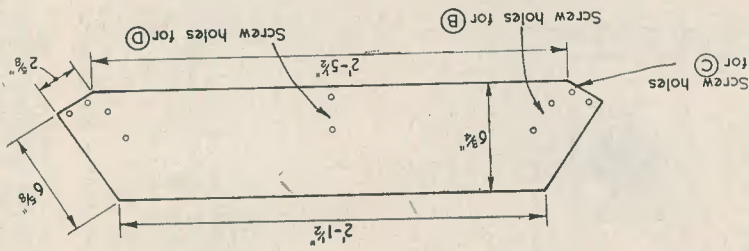


FIG. 7.

VIEW OF END (A) 2 OFF

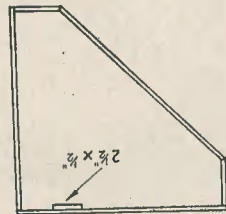


FIG. 4.

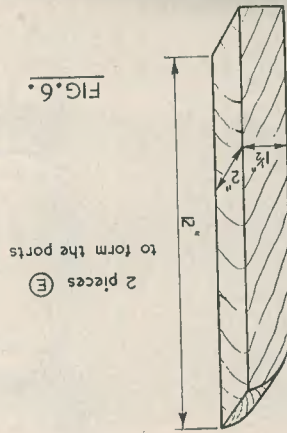


FIG. 6.

2 pieces (E) to form the ports


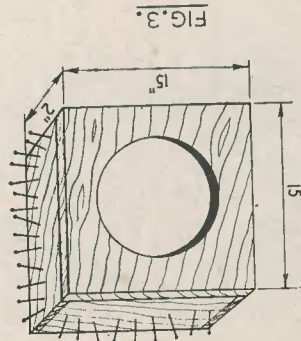


FIG. 3.

CUTTING LIST

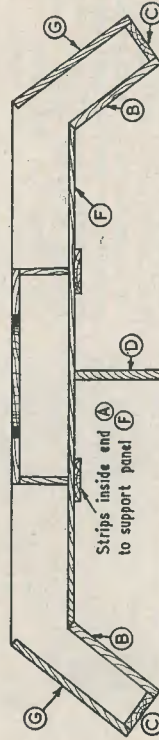- 2 ends A as FIG. 7. -----2'-10" x 6 3/4" x 5/8"
- 2 boards B-----3'-6" x 5 7/8" x 5/8"
- 2 " C-----3'-6" x 2" x 5/8"
- 2 " D-----3'-6" x 4 1/2" x 5/8"
- 2 " G-----3'-7 1/4" x 6 5/8" x 5/8"
- 1 panel F-----3'-6" x 2'-0" x 3/8" or 1/4"



END SECTION OF MOULD TAKEN ON LINE X-X OF FIG. 1.

FIG. 8.

6201

Approx. quantities can easily be worked out from the figures given in the Appendix. Thoroughly mix the dry materials with a clean shovel, and again, and again, after wetting, thus producing a nice sloppy mixture. Ram the concrete to the bottom of the side wings in the mould, and tightly around the outside of the sub-cabinet and its projecting nails, etc. which will now reinforce the concrete and firmly fix the wooden insert. Fill the mould with concrete

water to wash away the slush—the carborundum easily grinds the chips of marble down until a mottled effect is obtained. The background tint will be the shade of the coloured concrete flecked with irregular patches of the colour of the aggregate used. Any colour scheme can be adopted as desired, e.g. black on white, white on green, etc. A final polish can be given with a smooth stone. Leave the mould undisturbed for a few



days to attain strength. It is an advantage at this point—especially if the weather is hot—to keep the concrete wet; either by repeated spraying or covering with wet cloths. Should the weather be normal, however, you have nothing to worry about; rain will help to prevent it cracking. The reader should clearly understand that the concrete gets harder and stronger every day for a very long period. By now it would be too hard to carry out the polishing process without a lot of work. In, say, 4 or 5 days time it will be safe to move. Remove the end boards A; lift the structure into a vertical position; remove boards B and C and the panel F. Generally clean up the edges and wash it down; if desired a strip of thin felt can be stuck with Bostik on each of the vertical sides so that the concrete does not need to touch the walls when in position.

In case transportation to the permanent position presents a problem, I will explain that the slab can be lifted by two people; but it is more readily moved by means of rollers, first lifting the slab on to a board. For rollers the writer recommends half a dozen beer or lemonade bottles (previously emptied during rest intervals—mixing concrete is thirsty work!)

Just before placing into position, fix the speaker chassis by means of wood-screws. The wooden sub-baffle will accommodate speakers up to 12in., but 15in. bass speakers would require slight modifications to this item. The wooden part of the front will now require enamelling two coats of a suitable colour. With regard to finishing off the front aperture—some readers may prefer a high note diffuser of hardwood strips; others perhaps will be satisfied with a piece of expanded aluminium mesh, fixed by means of wooden beading. It is suggested this should be of octagonal shape with mitred joints.

The 1in. thick lid is similarly cast and polished, using a mould made of 1in. x 1/2in. wooden strips lightly nailed together. Do not assume the corners in your house are right-angles; make the mould an actual fit by trying it in the corner; also note that the lid should be large enough to overhang the front of the enclosure by about 1/2in.

Cut a small piece of wood 2 1/2in. x 3/4in. x 3/4in. and pin it to the lid mould at a distance of 2 1/2in. from the corner as shown in Fig. 4, so as to produce a slot in the lower half of the finished lid.

A piece of wood 3ft. 6 1/2in. x 3in. x 1in. has a tenon cut at one end as in Fig. 5. It should fit in the slot under the lid. This support for the rear of the lid rests on the floor and is loosely fixed by a single screw to the skirting near the corner of the room,

in a position such that the lid slot will just engage with the tenon when the lid is in position.

When casting the lid, the mould should be laid on a clean smooth surface; a couple of pieces of glass placed side by side is ideal. Polish the top and the front edges as before with the stone; a 1/2in. bevel can easily be ground on the upper edge.

The enclosure does not require any bolting or fixing; it merely stands in the corner of the room. As its centre of gravity is inside the chamber, the cabinet cannot possibly fall outwards. The lid is lowered gently, keeping the fore-arm underneath, until its rear is held by the support; the arm is then withdrawn and the front of the lid lowered gently until at rest on the front wall of the enclosure.

The completed reflex chamber will be found to give excellent results and is well worth the labour involved. It costs less than a wooden one of similar size and gives better reproduction. Furthermore, if two or more enthusiasts can get together, one mould can be used to cast several sound chambers.

If it is found that high notes are a little too pronounced, owing to internal reflections, they can be damped down by lining the chamber with felt or merely sticking some corrugated cardboard inside.

It is very doubtful if the whole of the chamber would ever need lining with any type of speaker, as this would deaden the reproduction quite a lot, but this question of "to line or not to line" is largely a matter of personal taste.

Possibly some readers may prefer a lighter model than the one described: in this case it is merely a matter of modifying the dimensions of the mould so that the front wall is 1 1/2in. thick instead of 2in.

#### Appendix

Volume of air column—approx. 8 1/2 cub. ft.

Weight of front—approx. 190 lbs.

Weight of lid—approx. 34 lbs.

Quantity of aggregate required—approx.

2 cub. ft.

Quantity of sand required—approx.

1 cub. ft.

Quantity of cement required—approx.

40 lbs.

#### THE "MICROAMP" HI-FI MINIATURE AMPLIFIER

We understand from the author of this article in the September issue, Mr. O. J. Russell, that improved performance of the treble control will result if a 470KΩ resistor is inserted between the grid of V<sub>1</sub> and the volume control. The 0.001μF and 2MΩ variable will remain on the grid side of this resistor.

## Query Corner

### A Radio Constructor Service for Readers

#### Audio Distortion

The increasing interest which is being shown by constructors in high fidelity amplifiers has been apparent for some time now. Many readers take advantage of our circuit checking service and send in circuit diagrams of apparatus which they propose to construct; about three-quarters of these now refer to high quality reproducing gear, whereas two years ago this same proportion was concerned with t.v. problems. In dealing with these audio queries it has frequently been noted that the sender has not fully appreciated the differences between the various types of distortion which may be present in his equipment, and as a result he may be overhauling the amplifier when in fact it is the speaker which requires attention. This month's article is therefore being allocated to a short survey of the various forms in which distortion can present itself. There is no doubt that the search for realism in audio reproduction is a most absorbing part of our hobby, and one which can provide keen satisfaction as each new step is taken towards perfection.

When a good reproducer is compared in performance with an ordinary radio receiver, the latter can be made to sound lifeless and artificial. A piano may assume the sound of a banjo and a cymbal like the scraping of sand on a piece of tin. Such loss of realism is often attributable to a number of different forms of distortion which have to be traced and eliminated individually. The wider the frequency coverage is made the more obvious will the various forms of distortion become.

#### Frequency Response

Without adequate coverage of the audio spectrum one cannot hope to obtain realistic reproduction. It is, however, important for the response to be balanced at both ends of the spectrum; to have good bass with little top

is as bad as having very good treble with attenuated bass. It is not advisable to spend a lot of effort in extending the top response if,

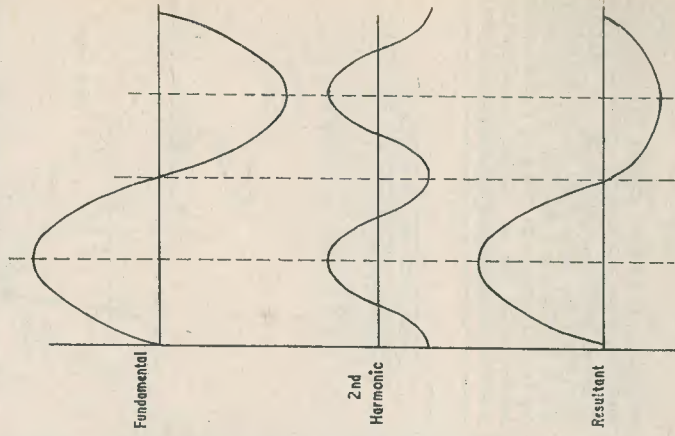


FIG. 1.

SHOWING SECOND HARMONIC DISTORTION

G229

for example, the speaker and its associated transformer are incapable of handling frequencies below about 70 c/s. It has been

claimed, correctly in the writer's opinion, that to achieve a balanced response the ends of the response curve should be limited as follows:

*Limit of H.F. End*      *Limit of L.F. End*  
 5 kc/s                      100 c/s  
 8 kc/s                      70 c/s  
 10 kc/s and over        40 c/s

The range chosen will depend largely upon such limiting features as the pick-up, the speaker and transformer and the speaker enclosure. A coverage of 40 c/s to 15 kc/s is sufficient to reproduce the complete range of orchestral music with no loss which is appreciable to the trained ear. Lack of h.f. response can remove the higher order har-

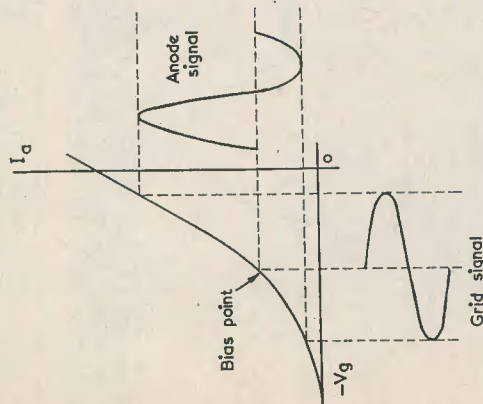


FIG. 2. SECOND HARMONIC PRODUCED BY CHOICE OF WRONG BIAS POINT

monics from basic tones which may produce a certain unnaturalness in the reproduction accompanied by a lack of brilliance. On the other hand, a very good top which is not supported by a good bass response can produce an annoying "thinness" which impairs realism. These effects are avoided by observing the correct balance as indicated above.

#### Harmonic Distortion

Any distortion of the original waveform which is fed into an amplifier will produce harmonics of the fundamental frequency. Unless this type of distortion is severe, it often goes undetected provided it is not accompanied by some other form of distortion. Harmonics are most readily produced

as a result of amplitude non-linearity which occurs during each individual cycle. This does not necessarily mean that the amplifier has amplitude distortion (which means that changes in amplitude at the input do not cause corresponding changes in level at the output). This trouble is described later. Reference to Fig. 1 shows how adding a second harmonic to the fundamental produces a distorted waveshape. Figure 2 illustrates the manner in which a similar second harmonic distortion is produced by incorrect biasing in an amplifier valve causing non-linearity. This is but one example of how harmonics are produced, but it serves to illustrate the principle.

#### Intermodulation Distortion

This is perhaps the form of distortion which is most apparent and is usually the most difficult to avoid. It results in a certain confusion occurring in the reproduction, which is usually particularly noticeable on loud passages, making it difficult to pick out any individual instrumentalist. Because of this it is possible for an amplifier which has a remarkably good frequency response to still not give the sharp clear-cut reproduction which is so much sought after. To understand the manner in which intermodulation distortion occurs, assume an amplifier into which two separate sine waves of different frequencies are fed, the lower frequency wave having the greater amplitude. Now if all is well the output waveform would appear as shown in Fig. 3A, where both halves of the low frequency wave are of equal amplitude. If, however, non-linearity is present in the amplifier it can distort the lower half of the wave as already shown (Fig. 2) and this in turn will reduce the amplitude of the higher frequency signal. The result on this signal is shown in Fig. 3C, from which it is seen to be amplitude modulated in sympathy with the larger signal. The effect caused by intermodulation between two separate tones has been demonstrated, the effect upon the very complex series of tones which make up the sound of an orchestra can be imagined. Any reader who possesses two separate sine wave sources may be interested in repeating the experiment described and listening to the results. It will be found that at low volume levels, where the non-linearity of the amplifier is negligible, the two separate tones are clear and easily distinguished. As the volume is advanced to the point at which non-linearity occurs, the output degenerates into a harsh combined note. If all is well this should not occur until the normal point of overload is reached.

Intermodulation distortion is also produced in the speaker, and, to overcome this, quite complicated double cone loading enclosures

have been devised, or conversely twin speakers with a suitable cross-over network are employed. Such arrangements are intended to segregate the greater amplitude bass response from the treble notes, thus reducing the risk of intermodulation.

#### Amplitude Distortion

As has already been stated, a graph of the output of an amplifier plotted against input should be substantially a straight line. It is claimed that a dynamic range of 70 db is required to give the maximum realism from modern recording if overloading on the peaks is to be avoided. Because of the wide dynamic range of long playing records, contrast expansion is not employed on modern amplifiers.

#### Resonance

An abrupt peak or hump in the frequency response curve of the amplifier can cause shrillness if it is in the treble region, or boominess if it is in the bass. The trouble is sometimes traced to a defective negative feedback arrangement or a poorly designed output transformer. If the amplifier is in order but the trouble is present, it may be due to acoustic feedback between speaker and pickup or a resonance in the speaker enclosure.

#### Transient Distortion

The equipment must be capable of responding to sudden impulse sounds without any tendency to overshoot. To test for this characteristic a square wave is fed into the amplifier and the output viewed on an oscilloscope. Any tendency for spikes to appear after the vertical sides of the waveform shows that overshoot is present. This can sometimes be corrected by modifications to the feedback circuit to reduce the dynamic output impedance of the amplifier, and thus improve the speaker damping. If the vertical sides of the square wave appear slightly sloping, this indicates a poor transient response—a defect which should also show up as a poor treble response.

#### Phase Distortion

Due to the use of capacitative and inductive elements in the amplifier, there will be a small but progressive phase shift across the amplifier as the signal frequency is increased. This will have the effect of shifting the phase of harmonics with respect to their fundamental, but extensive listening tests have shown that within the limits normally encountered this shift is not aurally detectable. It is, however, important to keep the phase shift of that part of the amplifier over which negative feedback is employed to a minimum. For this reason the tone control circuit is rarely included within the feedback loop.

Phasing is important when two or more speakers are used simultaneously in close proximity to each other, and care is thus required when connecting up the speakers.

#### Wow

This trouble is most readily detectable on a constant tone record, when it will show up as a wavering in pitch of the tone. It is usually traceable to minor deviations in turntable speed.

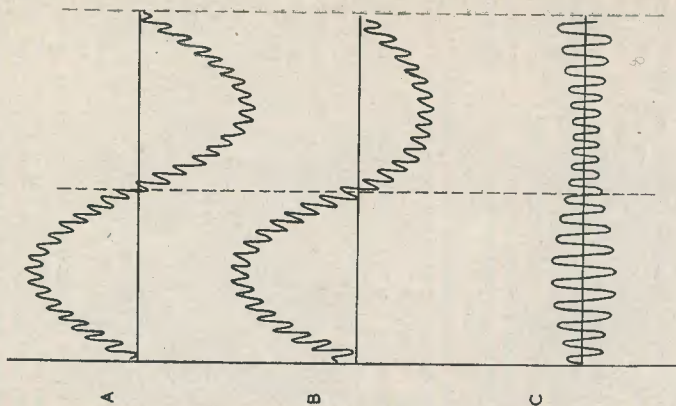


FIG. 3.

INTERMODULATION DISTORTION

The various types of audio distortion have been described separately, but in many cases they are attributable to the same fundamental cause. Unless test gear is available to definitely prove the presence of distortion, it must not be assumed to be there merely because it is heard on one recording; the record may be a bad one. Careful listening tests on good quality records are usually necessary before it can be definitely decided that some particular form of distortion has to be eliminated.

(For QUERY CORNER RULES, see page 89, September issue)

# Radio Miscellany

**B**Y THE TIME THESE WORDS APPEAR IN print, the I.T.A. will be getting into its swing. While it is impossible to get an accurate figure of the percentage of t.v. receivers in current use which have been constructed by amateurs, it is obviously higher than many people thought possible. I have myself often been surprised at the most unlikely people who have successfully built t.v. sets from kits and wiring plans. Add to these the many hundreds with some radio knowledge who have bought sets, and one ceases to be surprised that the number of home-built converters already runs into many thousands. As soon as the test transmissions from Upper Norwood began, many dealers in Greater London found the demand for coils and components outpaced delivery from the makers. The B.B.C. sat up and took even more notice, although, of course, they had long since been worried by I.T.A. "pinching" their technical staff and artists. They intensified their campaign by stepping up the programmes—a notable example of the beneficial effect of even the threat of a little competition. The artists and the B.B.C. staff, too, must feel more cheerful now they have an alternative employer to whom they can take their talents. To crown it all, the Chief of the T.V. Service (at the Radio Show) admitted that they could no longer grumble about the money allocation.

In recent weeks there has been a conspicuously strange silence among the normally verbose opponents of Independent T.V. Perhaps they are busy studying statistics so they can let us know all about it if there should happen to be an increase in juvenile delinquency next year!

## At a Discount

Not only those engaged in other forms of entertainment, and moralists who concern themselves over t.v. as time-waster No. 1, but transmitting amateurs also are growing to view the expanding hours of t.v. programmes with anxiety. Especially the amateurs now that colour and 3-D t.v. loom in the background with their consequential demand for greater bandwidths. Amateur operation during t.v. hours becomes an increasingly

difficult problem. The short waves were given to amateurs because they were thought to be of little use for much else. Now, what with f.m. and t.v., it is possible that they will get pushed off the short waves and given a few kc/s in the broadcast bands. More unlikely things have happened.

Amateur communications radio has already suffered a recession for various reasons, not only in Britain but throughout the world. Perhaps the most spectacular drop has been in Italy, where the number has slumped by nearly three-quarters. In addition to their other troubles a special licence and a fee was required—plus the introduction of a Morse test.

Maybe the fee part wasn't regarded as so important. In Italy taxes and other Government dues seem to be a matter of mutual adjustment. They simply go along to the collecting office and have either a friendly or argumentative discussion about it. The possessor of quick wits and a persuasive tongue often gets away with half-price or even less. Imagine trying that with the dame behind the counter at the local post office and getting your t.v. licence for thirty bob!

Thinking of cut prices reminds me that much is being made in the press of a new t.v. tube firm who threaten to slash prices by a third. When I recently mentioned tube prices several readers wrote to tell me that prices ought to be cut by 80%—not a mere 33%. However, I gather they will not be in production for eighteen months yet—then for a time it will be 2 lin. tubes only, and even they will be for new sets and not available for replacements until some time after that.

## More Space

My recent comments on this subject have brought several letters from readers. Undoubtedly the recent announcements of "Step 1" experiments will quicken and extend that interest.

To quote from a letter from Mr. J. D. Pearson (BR520368) of Barrow-on-Humber, "As any future development in space travel is inevitably and inextricably bound up with radio, it is only fitting that *The Radio Constructor* (along with other radio periodicals) should at last begin to evince an interest

in the problems involved in solar exploration. A regular series of articles on the lines of your notes would no doubt increase circulation tremendously, and at the same time provide interesting reading matter for the majority of your regular readers.

"Like yourself I am very interested in this subject and have studied it for some years. I soon discovered that a knowledge of electricity and magnetism is an almost indispensable aid to the study of astronomy and solar navigation.

"There are several sources in outer space from which emission of radio waves has been detected and recorded; recently from the planet Jupiter on a frequency of 22Mc/s. This would suggest that the ionosphere does not work in reverse—i.e. it will reflect waves reaching it from the earth on 22Mc/s but does not reflect back into space the transmissions of the same frequency from Jupiter.

"With reference to your "bat-men" paragraph, I fear it does not appear to have occurred to your learned self that any life which there may be on the planets will have evolved and adapted itself to the conditions. Therefore it is quite feasible that the inhabitants of Mercury (if any) should be 'red-skinned' types with crustaceous, lobster-

## The Younger Set

A 17-year-old reader, Brian C. Smith, of 9 St. Margarets Road, Westgate-on-Sea, Kent, forwards details of a proposed "Experimenters Club" to cover radio, chemistry and matters of scientific interest for the under 21's. Despite the attacks from a certain quarter on organisations of this nature, I feel it would be a mistake to condemn such efforts out of hand.

Incidentally, I understand the particular organisation criticised offered to open their accounts for inspection and audit—naturally at the expense of any responsible person wishing to investigate them. The offer does not appear to have been taken up.

Correspondence with many readers has convinced me that they are not such chumps as to send money to any organisation (or person) without finding out what it is all about first. It is therefore only fair to accede to Brian Smith's request that the proposed club and its activities should be made known. I know nothing of him other than the fact that he seems to have plenty of enthusiasm, but there is certainly no reason why such a club, sensibly managed, should not be a success. Here's wishing them luck.

## CENTRE TAP

talks about

## TV HOURS SPACEMEN PROPOSED CLUB

### Conversation Piece

Reader: "You remember a couple of months ago you wrote of plugging unwanted holes with wire wool before making an invisible repair with solder?"

Me (cautiously): "Yes."

Reader: "Do you know how tinkers repair holes in pots and pans?"

Me: "To be quite honest, I have never seen a tinker filling in holes."

Reader: "Well, they hold a piece of clay against the hole. This is called a tinker's dam. After the solder sets they throw it away, hence the expression 'Not to care a tinker's dam.'"

Me: "Oh! I thought it was a tinker's cuss."

Reader: "Perhaps in those days they were too polite to use the word dam, so they may have called it a cuss instead. The people using the expression, I mean, not the tinkers."

Me (unable to think of anything better to say): "We live and learn."

Reader: "I thought you might as well have the full story."

Me (humbly): "Thanks, OM."

Reader: "You're welcome. So long."

# Let's Get Started 28:

## THE TRANSITRON

by A. P. BLACKBURN

**L**AST MONTH, IN DEALING WITH TIMEBASES, we arrived at the Miller circuit. It was mentioned that this circuit was often used in conjunction with a "transitron." This is probably one of the most versatile circuits in electronics. In its normal form it only requires one valve, and with very little modification may be used as a generator of sine waves, sawteeth or square waves, as required.

Like so many circuits in wide use to-day, it originally made its appearance many years ago. It was first described by Herold in 1935. It finally came into prominence just before and during the war.

Before thinking about its applications, the first thing to do is examine the circuit in its basic form.

seen that an unusual feature of the circuit is the use of the suppressor grid in the valve. The first relevant feature to note is that if  $g_3$  were made negative with respect to cathode, the current flowing to the anode would be reduced.  $G_2$ , however, would take a greater current and the screen voltage would drop. If  $g_3$  were made more positive the anode would take more current and the screen less, therefore the screen voltage would rise.  $G_2$  and  $g_3$  are then in phase, and if coupling were placed between them, oscillation could occur. That is what, in fact, does happen. Imagine for a moment that the suppressor was at cathode potential. The anode and screen would both be taking current. If some disturbance now occurred which caused the suppressor to become a little more

negative than the cathode, some of the current to the anode would be diverted to the screen. The screen voltage would drop, and by virtue of the coupling capacitor  $C_1$  the suppressor  $g_3$  would be driven more negative.

This in turn would divert more current to the screen from the anode, and the screen voltage would drop further, thus driving the suppressor more negative.

This action takes place very rapidly until all current to the anode is cut off. At this point, then, the action ceases. The charge that has accumulated on  $C_1$  during this process will now begin to leak away through  $R_g$ , and the suppressor grid will slowly become more and more positive until some current is permitted to flow to the anode. When this occurs, the screen voltage will begin to rise, because some of its current is now being diverted to the anode. The rise in screen voltage is transferred to  $G_3$  via  $C_1$ , and  $G_3$  becomes yet more positive and permits more current to flow to the anode. There is, therefore, less current in the screen and its voltage rises still further, taking the suppressor with it. Once again this process continues until the valve approaches saturation, when any further increase in  $G_3$  voltage produces no increase in anode current.

At this point the action ceases, and  $C_1$  will be nearly completely discharged.  $C_1$  will now slowly charge, taking the suppressor back toward cathode potential. However, in this case, the time will be shorter than when the

the suppressor to go negative once again. Well, this is where we came in. The cycle is complete and another has started. Note that during the charging and discharging periods of  $C_1$ , the screen voltage remains constant. The screen waveform therefore is square in shape, as shown in Fig. 2. The anode waveform is also shown in Fig. 2 and can be seen to be an inverted version of the screen.

In its simplest form, then, the transitron produces a square wave of either polarity. There are very many applications where square waves are of tremendous use, but we will leave that and return to the transitron for timebase applications.

### Timebases

The simplest transitron timebase is shown in Fig. 3. The circuit is the same as before, except that the capacitor  $C_T$  has been added. The transitron action is still the same as before, except that when the anode current is cut off, the capacitor  $C_T$  will charge toward h.t. through the anode load resistor  $R_L$ .

If the time constant of  $C_T$ ,  $R_g$  is just right, the circuit will begin to change state when the capacitor  $C_T$  is on the way to being fully charged. The change of state will turn on anode current and the capacitor  $C_T$  will discharge through the valve.

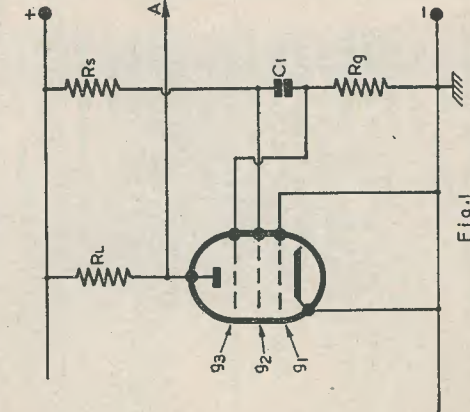


Fig. 1

E227

### Operation

The transitron is an oscillator of a type similar to a multivibrator. That is, it does not itself produce a sinusoidal waveform. The basic circuit is shown in Fig. 1. It can be


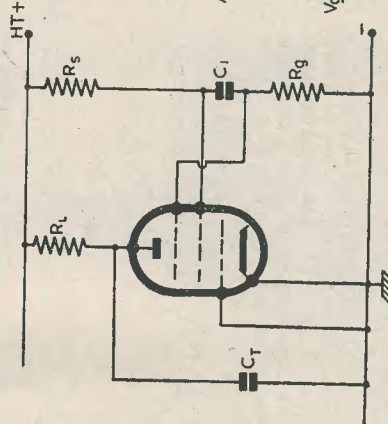


Fig. 3

E228

suppressor was cut off, because current will flow not only through  $R_g$  but also into  $G_3$ . After a while, the suppressor voltage will have dropped sufficiently to regain control of the anode current.

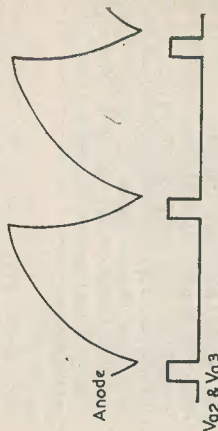When this occurs, the anode current will begin to decrease, the screen current to increase, the screen voltage to drop, causing



Waveforms in fig. 3


Fig. 4

A disadvantage of this circuit is the non-linearity of the resultant sawtooth. Waveforms are shown in Fig. 4 where it can be seen that the screen waveform is essentially the same as in Fig. 2, but the anode waveform is a sawtooth.

An almost ideal circuit is obtained by combining the Miller circuit described last

month and the transitron. The whole circuit may be combined within the same valve, but the two parts of the circuit perform quite separate functions. The Miller connection provides the linear sawtooth, and the transitron acts as the switch which initiates and terminates the sawtooth. The circuit is shown in Fig. 5 and the waveforms in Fig. 6.

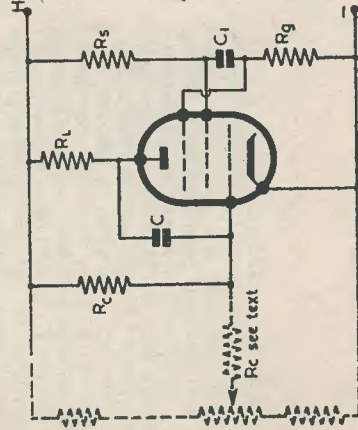In this circuit the two actions are comparatively separate from one another. Let us start from the moment when the suppressor is negative and there is therefore no anode current. Capacitor C<sub>1</sub>, the Miller capacitor, will be charged; that is, one plate will be at



E229

Fig. 5

h.t.+, and the grid plate at cathode potential. When the transitron changes state and anode current flows, the anode voltage will drop, this drop being transferred to the control grid, via C. The Miller run-down then commences, as explained last month. When the run-down is complete, and the valve has "bottomed," no fly-back will occur until C<sub>1</sub> has charged through R<sub>g</sub>, and the transitron has changed state.

When this occurs, the anode current will cease, and C will charge up to h.t.+ once more, thus completing the cycle. In order to avoid a waiting period between the end of the run-down and the fly-back, the time constant C<sub>1</sub>R<sub>g</sub> should be chosen to cause the transitron to fly back just before the pentode bottoms. This is illustrated in Fig. 6.

During the fly-back, a negative pulse appears at the screen and suppressor of the valve. This may be used to "black out" the flyback trace on the c.r.t. tube, by connecting the transitron screen to the grid of the c.r.t.

If a large range of timebase speeds are required it is normally necessary to switch the timebase capacitor C and the recycling capacitor C<sub>1</sub>. Also, if continuous variation of the timebase speed is required, R<sub>c</sub> may be returned to a point of adjustable voltage, as shown dotted in Fig. 5. This control becomes the fine frequency control and the switched capacitors the coarse control.

A suitable point for the injection of synchronising signals is either at the screen or suppressor. If either of these points is used, care must be taken to ensure that the synchronising voltage is not too great, other-

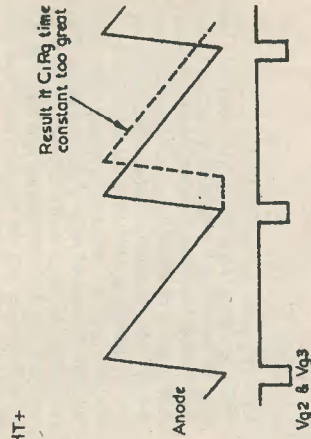


Fig. 6

wise the trace will be distorted or may even collapse altogether.

Triggered, or single stroke operation—briefly mentioned last month—although infrequently used in oscilloscopes used for radio purposes, may be achieved with the circuit of Fig. 5. All that is necessary is to return R<sub>g</sub> to a point sufficiently negative with respect to earth to ensure that the suppressor grid is cut off. The application of a brief pulse to the suppressor will cause the circuit to produce one sweep, whereupon it will fly back and wait until another pulse is applied.

#### Wide Range Oscillator

The transitron makes a very useful solid oscillator. The frequency range obtainable can be from a few cycles per second up to nearly 100Mc/s. The circuit is shown in Fig. 7. One advantage immediately becomes clear. The oscillator circuit merely requires a tuned circuit. There are no taps on the coil, and no coupling winding. For

this reason the circuit is, sometimes called a "two terminal oscillator."

The output may be taken from the junction of C<sub>2</sub> and the tuned circuit. However, in order to reduce loading on the oscillator, a coupling winding may be introduced. If the oscillator is to be used over a wide frequency range the value of C<sub>2</sub> would have to be switched. If the reactance of C<sub>2</sub> becomes too high at the operating frequency, oscillation will not be maintained. Typical component values would be:

- R<sub>L</sub> = 20kΩ;
- R<sub>s</sub> = 20kΩ;
- R<sub>g</sub> = 50kΩ;

and C<sub>1</sub> and C<sub>2</sub> may be found experimentally at the frequency in use.

#### A Frequency Divider

The original circuit shown in Fig. 1 may be used as a frequency divider. The action is very similar to that of a multivibrator. Imagine that a synchronising signal cut off the suppressor just before the normal action of the circuit drove the suppressor into cut-off. Subsequent synchronising signals would not affect the circuit, because they would only try to drive the suppressor further into cut-off.

The cut-off condition will remain until C<sub>1</sub> has discharged sufficiently to allow the circuit to change state. When this occurs the circuit will remain in the other condition until C<sub>2</sub> has charged sufficiently to cause a relapse to the original condition, thus completing the cycle. The transitron will, therefore, have produced one cycle for a number of synchronising cycles, i.e. it is frequency dividing.


#### Valves

It is worth mentioning a few suitable valves for transitron operation. Obviously, they must be pentodes and the suppressor grid must be available at a pin. Among surplus types, the EF50 (VR91) is particularly suitable. The suppressor cut-off is in the region of 50-60 volts. The SP61 (VR65) will work reasonably well, but the suppressor has a very long base and the valve is therefore less flexible than the EF50.

A surplus valve especially designed for the use of the suppressor is the VR116. In this case the suppressor cut-off voltage is about 10 volts.

Among modern miniature valves are the EF91 and the 6F33. The latter is a miniature equivalent of the VR116, but an internal diode is connected between the suppressor and cathode. The EF91 makes a fairly good transitron valve, despite the suppressor grid base, which is of the order of 90V, and very variable from specimen to specimen. Another valve is the triode pentode ECL80, which works very well in most transitron circuits, and has the extra triode free for some other purpose.

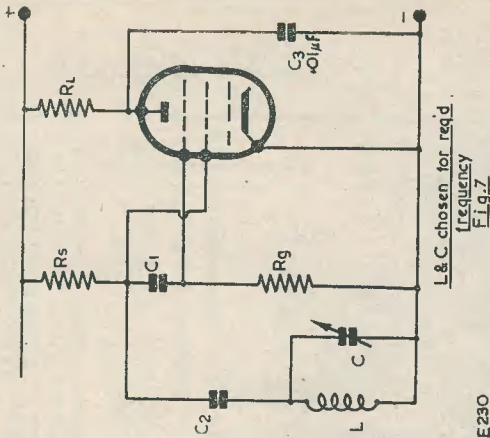It should be remembered that the suppressor characteristic is not necessarily held within close limits on most valves (except the



E230

VR116 and 6F33) and one may therefore strike an occasional valve which will not work in a transitron circuit, but which is perfectly good in every other way.

#### ERRATA

On page 160 of this issue, the third paragraph under "Alignment", the Band I aerial should be connected to the grid of V<sub>2</sub>(a), and not V<sub>1</sub>(a) as stated.

**INDEXES** for Vol. 8, Aug. 1954—July 1955 are now available, price 6d. post free.

**BOUND VOLUMES** A limited number of bound volumes (Vol. 8 only) are available, price £1. 1. 0 post free.

**DATA PUBLICATIONS LIMITED**

**57 MAIDA VALE · LONDON W9**  
Telephone: CUNningham 6141 (2 lines)

# LANES (RADIO) LTD

11 GARDNER STREET • BRIGHTON • Telephone BRIGHTON 20773

**ALL LEADING MAKES OF STANDARD COMPONENTS FROM STOCK** ★ LET US QUOTE INCLUSIVE PRICE FOR YOUR FULL REQUIREMENTS

**FREE** To introduce our service to Radio Constructor readers a free copy of Denco's FM Feeder Unit booklet will be given with all orders of £1 or over.

ALL BASIC COMPONENTS AVAILABLE—ALSO THIS FINE SELECTION OF INEXPENSIVE CONSTRUCTORS TOOLS

**RADIO SCREWDRIVERS 4" & 6" 1/- each**

**SCREWDRIVER MAINS TESTER 6/9 "**

**UNIVERSAL TOOL SETS with 3 screwdrivers, Phillips tools, etc. 12/- "**

**BOX SPANNER TOOL SETS 2, 4, 6, BA & 3 sizes Screwdrivers 25/- "**

**WIRE STRIPPING PLIERS Fully adjustable 15/9 "**

**BIB WIRE STRIPPERS 3/6 each SIDE CUTTERS 5/- "**

**TEST PRODS. Bulgin. Red & Black 2/9 "**

**Radio Point NOSE PLIERS and Wire Benders 7/6 "**

**HENLEYS SOLDERING IRONS**

25 watt . . . . . 19/8  
65 " . . . . . £1.3.8  
125 " . . . . . £2.2.8

ALL SPARES for the above from stock. £1 POST FREE.

**ERSIN SOLDER Multicore 5/- Pkt.**

TERMS.—Cash with order or C.O.D. (over £1). Please add postage and packing on orders below £1. Over £1 POST FREE.

## Scottish Insurance Corporation Ltd.

62-63 CHEAPSIDE • LONDON • EC2

Established 1877 Telephone CITY 4936-9 (4 lines)

### THE SHEDDING OF A LOAD

An ACCIDENT can cause serious financial embarrassment. Could you meet your commitments on the National Insurance Benefit?  
A "SCOTTISH" Policy will carry the load for you if you are disabled by ANY ACCIDENT and will pay compensation for as long as two years for any one accident.

For a BENEFIT of £5 PER WEEK the annual premium varies between £1 10s. and £2 2s. 6d. according to occupation, and the premium can be paid half-yearly or quarterly if desired.  
If you will complete and return this form to the Corporation's office at the above address, a quotation will be sent with a proposal for completion, or write for details quoting reference /JB.

NAME (Block Letters) .....

OCCUPATION .....

ADDRESS (Block Letters) .....

/JB 187

Compiled by E. G. BULLLEY

PART 3.

## VIBRATOR DATA


Remarks	Frequency c/s	Max. Volts	Wearite	Oak	Utah	National Union	Meissner	Mallory	James	Elec-tronics	Delco	Turner	Radiart
	115	12	QL12		4SP5		W245			835		5409-4	5409-4
	115	12	QL12		4SP5		W245			835		5409-12	5409-12
	115	12	QL12		4SP5		W245			835		5410	5410
	115	12	QL12		4SP5		W245			835		5411	5411
	115	12	QL12		4SP5		W245			835		5412	5412
	115	12	QL12		4SP5		W245			835		5413	5413
	115	12	QL12		4SP5		W245			835		5414	5414
	115	12	QL12		4SP5		W245			835		5415	5415
	115	12	QL12		4SP5		W245			835		5416	5416
	115	12	QL12		4SP5		W245			835		5417	5417
	115	12	QL12		4SP5		W245			835		5418	5418
	115	12	QL12		4SP5		W245			835		5419	5419
	115	12	QL12		4SP5		W245			835		5420	5420
	115	12	QL12		4SP5		W245			835		5421	5421
	115	12	QL12		4SP5		W245			835		5422	5422
	115	12	QL12		4SP5		W245			835		5423	5423
	115	12	QL12		4SP5		W245			835		5424	5424
	115	12	QL12		4SP5		W245			835		5425	5425
	115	12	QL12		4SP5		W245			835		5426	5426
	115	12	QL12		4SP5		W245			835		5427	5427
	115	12	QL12		4SP5		W245			835		5428	5428
	115	12	QL12		4SP5		W245			835		5429	5429
	115	12	QL12		4SP5		W245			835		5430	5430
	115	12	QL12		4SP5		W245			835		5431	5431
	115	12	QL12		4SP5		W245			835		5432	5432
	115	12	QL12		4SP5		W245			835		5433	5433
	115	12	QL12		4SP5		W245			835		5434	5434
	115	12	QL12		4SP5		W245			835		5435	5435
	115	12	QL12		4SP5		W245			835		5436	5436
	115	12	QL12		4SP5		W245			835		5437	5437
	115	12	QL12		4SP5		W245			835		5438	5438
	115	12	QL12		4SP5		W245			835		5439	5439
	115	12	QL12		4SP5		W245			835		5440	5440
	115	12	QL12		4SP5		W245			835		5441	5441
	115	12	QL12		4SP5		W245			835		5442	5442
	115	12	QL12		4SP5		W245			835		5443	5443
	115	12	QL12		4SP5		W245			835		5444	5444
	115	12	QL12		4SP5		W245			835		5445	5445
	115	12	QL12		4SP5		W245			835		5446	5446
	115	12	QL12		4SP5		W245			835		5447	5447
	115	12	QL12		4SP5		W245			835		5448	5448
	115	12	QL12		4SP5		W245			835		5449	5449
	115	12	QL12		4SP5		W245			835		5450	5450
	115	12	QL12		4SP5		W245			835		5451	5451
	115	12	QL12		4SP5		W245			835		5452	5452
	115	12	QL12		4SP5		W245			835		5453	5453
	115	12	QL12		4SP5		W245			835		5454	5454

(to be continued)

NS = Non synchronous.

\*S = Synchronous.

**COMPLETELY BUILT SIGNAL GENERATOR**

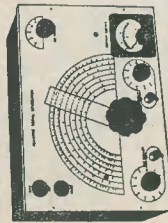

Coverage 120 Kc/s-320 Kc/s, 300 Kc/s-900 Kc/s, 900 Kc/s-2.75 Mc/s, 2.75 Mc/s-8.5 Mc/s, 8 Mc/s-28 Mc/s, 16 Mc/s-56 Mc/s, 24 Mc/s-84 Mc/s. Metal case 10" x 6 1/2" x 4 1/2". Size of scale 6 1/2" x 3 1/2". 2 valves and rectifier. AC mains 230-250V. Internal modulation of 40 per cent, modulated or unmodulated. RF output continuously variable 100 milli-volts. CW and mod. switch, variable AF output and white coil output meter. Black crackle-finished case and wiring panel. Accuracy  $\pm 2\%$ . £4 19 6 or 34/- deposit and 3 monthly payments 25/-. P. and p. 4/- extra.

**PERMEABILITY TUNED TV CONVERTER for new Commercial Stations**



Input 300 ohm balanced line or 80 ohm coax. Coverage 180-200 Mc/s. Vision IF: 10.7 Mc/s. Valve line-up: 6AK5 RF amplifier; 6AK5 mixer; 6CA separate oscillator. This is a high gain unit, ideal for fringe areas. Can also be used as FM TUNER, frequency coverage 80-100 Mc/s. IF 10.7 Mc/s. Size 9 1/2" wide, 6 1/2" deep, 4 1/2" high; scale: width including overlap, 14". Complete with 3 valves, £4 9 6, p. and p. 3/-; 10.7 Mc/s IFs to suit above, 4/6 each

**USED 9" TUBE 22/14C** with ion burn, 17/6. Post paid. Mazda CRM92A, used with heater cathode short, guaranteed for 3 months. P. and p. 7/6. £3 17 6  
Used Mullard 9" tube 22/17 and 18 ion burn, 25/-, p.p.

Three-speed automatic changer, B.S.R. Monarch, current model. Will take 7" 10" records. Turnover crystal head. Cream finish.  
Brand new, AC mains, 200/250, £7 15 0, p. & p. 3/-


**Line and EHT Transformer**, 9kV Ferrarcore core. EY51 heater winding, complete with scan coils and frame output transformer and line and width control. P. and p. 3/-, 35/-  
As above but, complete with line and frame blocking transformers, 4, Henry 250mA choke, 100 mid and 150 mid 350 wkg 50mA AC ripple. P. and p. 3/-, £2 9 6  
**Standard Wave-change Switches**, 4-pole 3-way, 5-pole 3-way, 3-pole 3-way, 1/9 each. 9-pole 3-way, 3/6  
Miniature type, long spindle 4-pole 3-way and 4-pole 2-way, 2/6 each. 2-pole 11-way twin water, 5/-; 1-pole 12-way, 5/-, P. and p. 3/-

**USED Metal Rectifier**, 250V 150mA, 6/6  
**Combined 12" Mask and Escutcheon perspex**, 12/6 aspect, edged in brown. Fits on front of cabinet, 12/6  
As above for 14" and 15" tubes, 17/6

**Polishing Attachment** for electric drills. 1/2" spindle, chromium-plated 5" brush, 3 polishing cloths and one sheepskin mop mounted on a 3" rubber cup. Post and pkg. 1/6, 12/6. Spare sheepskin mops, 2/6 each  
**Line or Frame Oscillator Blocking Transformers**, 4/6 each. Smoothing Choke, 250mA, 12V, 8/6  
250 mA, 10/6. **Wide Angle PM Focus Unit** (emitter adj., state tube, 15/-)  
Mullard tubes with vernier adjustment, 15/-  
Ion Traps for Mullard or English Electric tubes, 5/-, post paid.  
**RF EHT Oscillator Coil**, 6-9kV with EY51 rectifier winding and circuit diagram, 15/-

**R. & TV COMPONENTS (ACTON) LTD**  
23 HIGH STREET ACTON LONDON W3

**PATTERN GENERATOR**

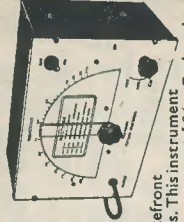

40-70 Mc/s direct calibration, checks frame and line timebase, frequency and linearity, vision channel alignment, sound channel and sound rejection circuits and vision rejection band width. Silver-plated coils, black crackle-finished case 10" x 6 1/2" x 4 1/2" and white front panel. AC mains 200/250 volts. This instrument will align any TV receiver, accuracy  $\pm 1\%$ . Cash price £3 19 6 or 29/- deposit and 3 monthly payments of £1. P. and p. 4/- extra.

Both generators guaranteed for 12 months

**COMPLETELY BUILT TV CONVERTER**  
for the new commercial stations, complete with 2 valves. Frequency can be set to any channel within the 186-196 Mc/s band. IF will work into any existing TV receiver between 42-68 Mc/s. Input arranged for 80 ohm feeder. EF80 as RF amplifier, ECC81 as local oscillator and mixer. The gain of the first stage RF amplifier 10dB. Required power supply of 200 DC at 25mA, 6.3V AC at 0.6 amp. Input filter ensuring freedom from unwanted signals. Simple adjustments only, no instruments required for trimming. Will work into any TRF or superhet. Size 4 1/2" x 2 1/2" x 7". P. and p. 2/6. £2 19 6. Double wound mains transformer. Pri. 200/250V metal rectifier, and smoothing condenser to suit above, 18/6




40 watt Fluorescent kit, AC mains, 230/240. Power-factor compensating choke, 2 tube denser, 2 starter holders, 17/6 and starter-holder. P. and p. 3/-, 17/6

20-watt AC or DC 200/250V. Fluorescent kit, comprising trough in white stove enamel, 2 tube holders, starter, starter-holder and barretter. P. and p. 1/6, 12/6  
TV Coils, moulded former, iron cored, wound for rewinding purposes only. All-can 1 1/2" x 1 1/2", 1/- each; 2 iron cores All-can, 2 3/8" x 3/8", 1/6 each. Suitable for Band III Converters.

**Dubilier**, 0.001 10kV working, 3/6  
As above but complete with 6V6, EY51 and associated resistors and condensers. Circuit diagram, 37/6  
The above unit completely built and tested in metal box, size 5" x 5" x 4 1/2". 42/6. P. and p. 3/-  
**Used AC Mains 200/250 volts**, 4 valve plus metal rectifier, medium wave superhet in polished walnut cabinet, size 14" x 9 1/2" x 7 1/2", complete with valves 6K8, 6K7, 6Q7 and 6F6, 6 1/2" PM speaker. Fully guaranteed. P. and p. 7/6. £3 15 0  
1,200ft High Impedance Recording Tape on aluminium spool, 12/6, post paid.  
Valveholders, moulded, 16mid, 500 wkg 3/3 octal Mazda and local, 7d. 8mid, 500V wkg, 2/6 each. Paxolin, octal Mazda wire ends 1/6 and local, 4d. each. 8mid, 350V wkg tag ends 1/6  
Moulded B7G, B8A and B9A, 7d. each. B7G and B9A moulded with screening can, 1/6 each.  
32mid, 350 wkg 2/-  
16 x 24, 350 wkg 4/6  
4mid, 200 wkg 1/3  
40mid, 150 wkg 1/6  
16 x 8mid, 500 wkg 4/6  
16 x 16mid, 500 wkg 5/9  
16 x 32mid, 450 wkg 3/9  
32 x 32mid, 350 wkg 4/6  
25mid, 25 wkg 1/6  
250mid, 12V wkg 1/-

Where cost and packing charge is not stated, please add 1/6 up to 10/-, 2/- up to £1 and 2/6 up to £2. All enquiries SAE. Lists 5d. each.

**TRANSFORMER SNIP**

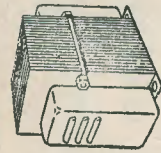

11/6  
Post 2/-  
Fully shrouded—standard 100-250V primary, 280-0-280 at 80 mA, 6.3V at 2 amp, 5V at 2 amp.


**INFRA LAMP WARMER**

Means real comfort in bed as it emits Infra-red Rays which warm and keep you healthy. Economical. Costs only 1d. per hour (electricity at 1d. per unit). Absolutely safe, no health or fire risk. Ideal for many other uses—over pet's basket, rearing pup, chicks, over desk, work-bench, etc. All complete and ready to work. MAJOR 4-lamp model £6 10 0

Price 36/-  
Post and Packing 2/-

**CAR STARTER/CHARGER KIT**  
All parts to build 6 and 12-volt charger battery can be connected to a "flat" battery and will enable the car to be started instantly. Kit comprising the following:  
Mains transformer... 19/6  
6 amp rectifier... 32/6  
Regulator stud switch... 3/6  
Resistance wire... 2/6  
Mains on/off switch... 1/6  
0.5 amp moving coil meter... 9/6  
Constructional data... 1/6  
or if bought all together price is 69/6 plus 2/- post and packing.


**RECORD PLAYER** £4 10 0

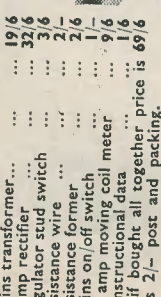

3-speed Induction Motor rubber mat. Latest rim drive with speed selection by knob at the side. No auto. stop, but there is a stop position on the selector. Small mod. makes speed variable for special effects and dance work.

**Hi-Fi Pick-up**  
Using famous Cosmocond Hi-Gi turn-over crystal. Separate apphires for each speed. Neat bakelite case with simple adjuster for weight compensation.  
Special Snip Offer this Month  
The two units for £4 10 0, or 30/- deposit and four payments of 18/-, post and insurance 5/-

**ENTIRELY NEW CIRCUIT**  
Redesigned and developed and built by the Cleveland Co.—very good reports received.  
THE "WINDSOR 5"  
This is a 5-valve AC superhet covering the usual long, medium and short wavebands. It has a particularly fine clear dial with an extra long pointer travel. The latest type local valves are used and the chassis is complete and ready to operate. Chassis size 15" x 6" x 6". Price £9 19 6 complete with 8" speaker, carriage and insurance 10/-, H.P. terms if required.

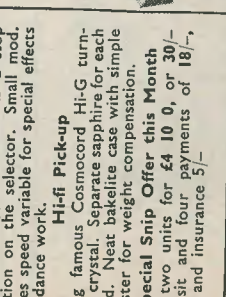

**ELECTRONIC PRECISION EQUIPMENT LTD**  
Post orders should be addressed to Dept. 34, 123 Terminus Road, Eastbourne  
Personal shoppers, however, can call at  
42-46 Windmill Hill, Ruislip, Middlex. Telephone: RUISLIP 5780. Half-day Wednesday  
29 Stroud Green Road, Finsbury Park, N.4. Telephone FLEET 2833 Half-day Sat.  
1049, Half-day Thurs.


**ADDITA BAND III CONVERTER**

Our Addita is giving very satisfactory results and we have had many pleasing reports regarding its performance. It is a very neat-looking unit and fits to the side or the back of the television. It is designed to convert any TV superhet or TRF and no internal modifications of any kind are required. You have Band I or Band III at the flick of a switch.


**Build it Yourself**  
Priced at all components, including stove enamelled case and even transfers for the front, is £4 5 0, plus 2/6 post, or £5 5 0 if mains components also required.

**BAND III LOFT AERIAL KIT**  
Known as the Folded 'Y' this is directional, signal strengthening and noise reducing. Complete kit including alloy elements, plastic centre piece, and fixing bracket. Mounts anywhere. Price 8/6 plus 1/6 post.

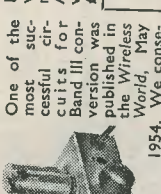
**WIRELESS WORLD BAND III KIT**  
One of the most successful units for Band III conversion. Published in the Wireless World, May 1954. We consequently offer a complete kit of parts, including the specified EF80 valves, wound coils, dialled chassis, in fact, everything included a copy of the circuit diagram. Price only 42/6, post 2/6 extra. Mains components if required, 25/-



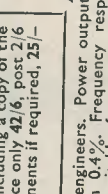**MULLARD '510' AMPLIFIER**  
A high quality Amplifier delivers 10 watts, harmonic distortion less than 0.4%. Frequency response almost flat from 10 to 20,000 c.p.s.—very suitable for use with the Acos 'Hi-G' and other good pick-ups. Completely made up and ready to work is £12 10 0 or 85/- deposit, plus 10/- carr. and insurance.



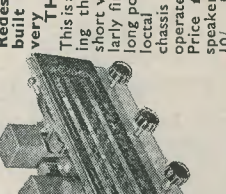**THE TWIN 20**  
This is a complete fluorescent lighting fitting. It has built-in ballast and starters—stove enamelled white and ready to work. It uses two 20-watt lamps. Price, with two tubes, 39/6. Post and insurance 5/-. Extra 20-watt tubes, 7/6 each.



**ELECTRONIC PRECISION EQUIPMENT LTD**  
Post orders should be addressed to Dept. 34, 123 Terminus Road, Eastbourne  
Personal shoppers, however, can call at  
42-46 Windmill Hill, Ruislip, Middlex. Telephone: RUISLIP 5780. Half-day Wednesday  
29 Stroud Green Road, Finsbury Park, N.4. Telephone FLEET 2833 Half-day Sat.  
1049, Half-day Thurs.



you are a keen constructor with an interest in television, this advertisement is aimed at you. We are specialising in Band III converter kits which give good results, repeat results, when they are built.

We have the complete coil kit for the Teletron Converter described in last month's *Radio Constructor*, at 15/-. Also, we have the complete coil kit for the Teletron Mark 2 Converter, described this month, at 17/6. Chassis for either of these converters are obtainable at 3/9. Output: Channels 1 to 4.

A very superior design is the "Univerter" (Patent Pending). This four-valve converter, for which we supply a kit complete with instructions, has its own power pack and an output at any Channel in Band 1. Every component supplied, except valves. The kit is £6 15s. and a wooden polished cabinet is available at a further £1 5s.

Please add p.p. when ordering these kits

## HOME CONSTRUCTOR'S HANDBOOK

Published by RODING LABORATORIES

This famous handbook is now available in the NEW 1955 Edition. It contains 22 tested circuits, complete with descriptions, constructional details, full parts lists, etc., etc. Also contains hints, formulae, data. Circuits include superhets, communications receiver, oscilloscope, signal tracer, tape recorder, amplifiers, beginner's receiver, and many more items of gear. And the book is backed by Roding Laboratories, who are so well known for their quality home constructor products. This 70-page book represents unbeatable value at 2s. 6d. (plus 3d. postage and packing). Order now and take immediate advantage of the wealth of information it affords.

**R. DAVIES 54 Newton Road Mumbles Swansea**

MAIL ORDER ONLY—NO C.O.D.

## "FM TUNER UNITS for FRINGE & LOCAL AREA RECEPTION"

This booklet, now in its Second Edition, includes a description of a Suitable Tuning Indicator and of The Osram 912 High Fidelity Amplifier. 32 pages with art board cover, price 2s. 2d., *post paid*.

**DATA PUBLICATIONS LTD**  
57 MAIDA VALE · LONDON W9 Telephone CUNningham 6141 (2 lines)


**GLYNE RADIO LTD.**  
24-26 HAMPSTEAD ROAD  
LONDON NW1  
EUSon 5533 (4/5)

**18 TOTTENHAM COURT RD LONDON W1**

MUSEum 5929/0095

(50 yards only from Tottenham Court Road Tube)

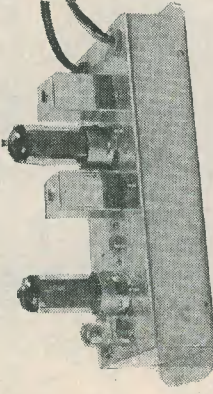A working TV receiver with this converter attached may be seen at our shop premises at 18 Tottenham Court Road.



**AERIALS, etc.** We carry what is probably London's largest selection of Band III TV Aerials. Price range from 7/6 upwards. Also filter boxes, and the latest Aerialite Axial (air-spaced-co-ax) especially manufactured for Band III, price 9d. per yard only plus p. and p. If unable to call we are sure you will receive our usual prompt attention. We can now supply a very efficient Band III Indoor aerial at 6/6 only.

**POWER SUPPLY.** Should the receiver itself be unable to provide the necessary power we shall be pleased to supply a complete kit for a power pack at the special inclusive price of 22/6 only! plus 1/6 p. and p. This includes our own wiring diagram, or alternatively, separate items as under:

Drilled chassis .....	3	0
Transformer: input 230V, output 200V at 30mA, 6.3V at 0.6A .....	8	6
Miniature contact cooled rectifier, 250V at 50mA .....	7	6
Electrolytic 32+32mfd 275V .....	3	6
5 watt cement-coated Resistor .....	1	3
Tag strip .....	3	0
Wiring wire .....	2	0
Nuts and screws .....	2	9
	<b>£1</b>	<b>4 11</b>

We can supply this power unit ready assembled and tested at 30/- plus 1/6 p. and p.

### HIGH GAIN MODEL Teletron Mk2 (This issue)

Teletron Mk. 2 coil set .....	17	6
Additional resistors .....	ea	3
Additional condensers .....	ea	9
Valves, type PCF80 (tax paid) .....	12	6
Valves, type PCC84 (tax paid) .....	12	6

Or the complete Mk. 2 Kit at 59/6  
It should be understood that this Mk. 2 version is essentially a fringe area model, and excellent results are already being obtained with the Mk. 1 version as above. At the time of going to press we cannot offer valves type ECC84 and ECF80. We hope, however, that they may become available at our usual competitive prices in the very near future.

London's most comprehensive component stocks, all under the same roof! Our fully competent technical staff is at your service. Why not pay us a visit!

All Post orders please to—  
**24-26 HAMPSTEAD ROAD  
LONDON NW1**  
EUSon 5533 (4/5)  
Monday-Friday  
9-6 p.m.  
Saturday  
9-1 p.m.

The Mk I chassis illustrated and described in the Sept. issue was that constructed by our Technical Staff. All items supplied and listed below are exactly to specification described therein.

### INDIVIDUAL COMPONENT LIST

Drilled chassis size 7" x 3" x 1 1/2"	3	9
complete with bottom plate		
Coil set and wiring diagram	15	0
complete (Teletron) .....		
2. Valves, type EF80, brand new, tax paid, at 10/6 each .....	1	0
7 1/2 watt resistors at 3d. each .....	1	9
1 1/2 watt resistor .....	1	5
8 Ceramic capacitors at 9d. each .....	6	0
2. 2-8pF Phillips trimmers at 9d. each .....		
3 Power leads (each 2ft) .....	1	6
1 yd Wiring flex .....	2	2
Hardware bag (nuts, bolts, tags) .....	1	6
Solder .....	1	4
Coaxial socket .....	1	4
2. Amphenol B9A v holders at 9d. each .....	1	6
2 ft Coaxial cable .....	1	6
	<b>£2</b>	<b>15 2</b>

We shall, however, be pleased to supply the complete kit as itemised above at the special inclusive price of **48/6** plus 2/- p. and p.

If required we can supply this unit ready assembled and tested at **67/6** plus 2/- p. and p.

### VALVES

We have perhaps the most up-to-date valve stocks in the trade. A stamp will bring complete list but the following is a selection only of brand new imported valve types, fully guaranteed. Purchase tax paid.

DAF96	10/6	EF41	10/6	PL83	11/6
DF96	10/6	EF80	10/6	PY80	10/6
DK92	10/6	EF85	10/6	PY81	10/6
DL96	10/6	EF89	10/6	PY82	9/6
EABC80	10/6	EL41	10/6	PY83	11/6
		EL84	11/6	UCB41	10/6
		EM80	9/6	UCH42	10/6
		EY11	7/6	UL41	10/6
		EY51	(large)	UY41	9/6
		EBC41	10/6	(small)	12/6
		ECC81	9/6	6AQ5	8/6
		ECC82	9/6	EZ40	8/6
		ECC83	9/6	EZ80	8/6
		ECC85	10/6	PCF80	12/6
		ECH42	11/6	PCF82	12/6
		ECH81	11/6	PCC84	12/6
		ECL80	11/6	PL81	13/6
				PL82	10/6



# BAND III CONVERTER UNIT

Complete Kit of Parts for 'Teletron' Converter. Including 2-EF80 and Chassis and Wiring Diagram. Voltage required 200V @ 30M/A 6.3V

0.6 amps... 48/6 plus 2/- p.p.

Or assembled and tested ... 67/6 plus 2/- p.p.

Power Supply Components ... 22/-

The Unit complete with Power Supply. Tested and ready to plug in ... 97/6

★ AS DESCRIBED IN AUGUST ISSUE ★

## BC966A I.F.F.

Containing 13 valves, three 7193, seven 6SH7, three 6H6 metal, 18W dynamotor and fan output 450V 60m/a with three-speed geared motor plus 4 relays, condensers and resistors, in good condition 35/-, carr. 5/-

## "426" CONTROL UNIT

Containing four red EF50, two SP61, two EA50, one EB34, two single-gang 0.0005 condensers, W/W volume controls and switches, etc. Size 12" x 9" x 5" 35/-, carr. 3/-

Post Free unless otherwise stated

SEND STAMPS FOR 28-PAGE CATALOGUE

# HENRY'S

(RADIO LTD)

SHOP HOURS

Mon-Sat. 9 a.m.-6 p.m. Thursday 1 p.m.

Telephone Paddington 1008/9 & 0401

5 HARROW RD. LONDON W2

## High Gain Model Teletron Mk2 (This Issue)

Teletron Mk. 2 coil set ... 17/6  
Additional resistors ... 3d.  
Additional condensers ... ea 9d.  
Valves, type PCF80 (tax paid) ... 12/6  
Valves, type PCC84 (tax paid) ... 12/6  
Or the complete Mk. 2 Kit at 59/6

It should be understood that this Mk. 2 version is essentially a fringe area model, and excellent results are already being obtained with the Mk. 1 version as above.

At the time of going to press we cannot offer valves type ECC84 and ECF80. We hope, however, that they may become available at our usual competitive prices in the very near future.

## SMALL ADVERTISEMENTS

Readers' small advertisements will be accepted at 3d. per word, including address, minimum charge 2/- per word. Trade advertisements will be accepted at 9d. per word, minimum charge 6/-. If a box number is required, an additional charge of 1/- must be made. Terms: Cash with order. All copy must be in hand by the 8th of the month for insertion in the following month's issue.

### PRIVATE

**AMATEUR EMIGRATING.** Send SAE for list of TV, radio and electronic equipment, cheap. Iovey, 59 Fourth Avenue, London, E.12.

**FOR SALE.** Taylor 66A signal generator, £12. Taylor 20B circuit analyser, £6. Both as new with instruction books. Also Invicta battery/mains portable, needs slight attention, £4. Madde, 8 Acacia Avenue, Hornchurch, Essex.

**FOR SALE.** Homelab type 10 signal generator, working, £5. Premier 12in magnetic television chassis with valves, £9. *Practical Wireless* Minifour all-dry portable, £4. Stems 4-valve battery suitcase portable, £5. 52 copies *Radio Constructor* August, 1950-July, 1955. 67 copies *Practical Wireless* Ap.1, 1949-December, 1954. 57 copies *Practical Television* May 1950-May 1955. Offers: G. Goodwin, 6 Upper Tollington Park, London, N.4.

**UNWANTED GIFT.** New unused American service valve tester by Hickcock, with instruction book. First £7 10s. received secures this bargain. Carriage paid. Smith, 35 Aldersley Road, Tettenhall, Wolverhampton, Staffs.

**REAL BARGAIN.** Portable O.v.1 SW battery receiver, will cover all bands; fitted bandset, bandspread; calibrated, very economical, excellent condition, very cheap. SAE for particulars. Box No. D161.

**EDDYSTONE 750** speaker and S meter, good condition, £45. Qualtape tape deck, 2 motors, needs attention, £5. Box No. D169.

**FOR SALE.** AVO model "D" and Pullin series 100, both guaranteed in perfect condition after manufacturer's overhaul. Best offer over £6 each. Box No. D170.

**TAPE DECK** parts or complete outfit wanted. Reasonable price. Box No. D171.

**FIRST CALLER** with £15 gets two incomplete Pye television with two 9-inch tubes; one Premier television with 5-inch tube, less power pack; one Pye 45Mc/s strip; 30 B7A valves (including 9 EF91); over 50 used old type valves; two mains radios and a lot of good junk. Harrow area. Phone first, WOR 7512.

**FOR SALE.** 17in TV chassis, complete valves, less tube and speaker, £37 10s. Sound and picture demonstrated to caller. S.E. London, SAE full details. Box No. D172.

**FOR SALE.** Studio "O" pick-up £1 10s. Denco FM tuner, 5-valve model, perfect, very sensitive, bargain, £7 10s. W.B. S10 tweeter, 150ohm, £2. Stentor 6cc petrol engine, suitable for model boat or aircraft, £2. BC 342 receiver, 6 waveband, Xtal filter, BFO, very good condition, unmodified with original input 110v. a.c., supplied with auto trans. for 200/280v. a.c. £15 or near offer. Wright and Weaire tape deck, model 2, with manual, perfect, £22 10s. or near offer. Denco 5-valve FM tuner, perfect, £6. Box No. D173.

(continued on page 193)

## The Walk-around Shop

offers you a selection of

**INDICATORS Type 62a.** Ideal for conversion to Oscilloscopes. TV Units etc. Containing V.C.R. 97 12, VR91 (EF50), 2 VR54 (EB34), 3 VR92 (EA50), 4 CV118. Slow-motion dial, 13 posts, and scores of useful components. Size 8 1/2" x 1 1/2" x 18". New. In wooden packing case, price £3, carriage 7/6

**ABSORPTION WAVEMETER.** Easily converted to 2 metres or 70cm. In copper-plated metal case 3 1/2" x 4 1/2" x 5 1/2" with dial calibrated 0.100 and 80V neon tube. Coverage approx. 190-210 Mc/s. New. 6/6 each, post paid.

**CATHODE RAY TUBES.** Type 3 BP 1, 3" short persistence, complete with mu-metal screen and base. New. Post paid, only 22/6

**MAKE A MINIATURE POCKET RADIO.** Incorporating high Q technique using the new Ferrite rod. Made possible by simple conversion of an ex-Govt. hearing aid. £2 6s. 0d., post paid, with circuit diagram and full instructions. Batteries extra: 1.5V LT (type D18) 8d.; 30V HT (type B119), 4/3

**FL8a FILTERS.** Splendid value. 10/-, pkg. & pstg. 1/6

**NEON TUBES.** Miniature bayonet type, 80V striking (1 megohm in series for mains), 1/6 post paid

NOTE.—Orders and Enquiries to Dept. "R"

**PROOPS**  
BROS. LTD. 52 Tottenham Court Road W1  
Hours 9-6 p.m. Thursday to 1 p.m. Llantham 0141  
Open all day Saturday

**TV 12" Chassis, 97/6.** Drawing 2/6 or free with order. Complete chassis by famous manufacturer (London or Birmingham) RF EHT unit included. Owing to this chassis being in separate units (power, sound and video) it is easily fitted to table or console model. This chassis is less valves and tube, but see our catalogue for cheap valves to request. Carr. 5/-, London, 10/-, Provinces. 5-valve Radiogram Chassis, 29/9, Incl. speaker. 5-valve 8/11s 3 w band AC mains, complete but less valves. All used, tested and guaranteed. Postage and packing 4/6

**Radiogram Chassis, 7/9.** AC or universal, 5 sheet, less valves, dial and electrolytics. Otherwise believed to be in working order. Post: 3/6

**Mains Transformers, 5/9.** 6V and 5V heaters, 200-250 primary, 350-0-350, post 2/-

**Mains Transformers, 5/9.** 12V and 4V heaters, 100-250 primary (ideal auto-trans.), post 2/-

**Mains Transformers, 3/9.** 4V and 4V heaters, 200-250 primary, 350-0-350, post 2/-

**O.P. Transformers, 1/9.** Std. size, surplus guaranteed. 2-5 ohms, post 9d.

**2-Gang Condensers, 1/9.** Std. size. 0.0005 used, tested, post 9d.

**3-Gang Condensers, 1/9.** Std. size. 0.0005 used, tested, post 9d.

**Chokes, 60mA, salvage, guaranteed, 6/9.** post 9d  
**Chokes, 250mA, salvage, guaranteed, 5/9.** post 9d  
**Chokes, 60mA, salvage, guaranteed, 4/9.** post 9d.

## DUKE & CO

621 ROMFORD ROAD · LONDON · E12

Telephone GRA 6677

# Solder with



**LIGHTWEIGHT**  
CELEBRATION

With the "PERMABIT"

- NO TRANSFORMER NECESSARY
- FOR MAINS OR LOW VOLTAGES

Sole Manufacturers and Distributors  
**LIGHT SOLDERING DEVELOPMENTS LTD**  
106 GEORGE ST. CROYDON SURREY  
Telephone CROYDON 8589

Rapid Heating  
— Extreme  
— Lightness  
— 20 different  
models — Bit  
sizes, 1/8",  
3/16", 1/4",  
5/16", 3/8"  
Prices from 19/6  
Details of full  
range in folder  
No. 58, sent on  
request

## REPANCO HIGH GAIN \*\*\* COILS \*\*\*

Dual range miniature 2/6  
Crystal Set Coil with  
circuit, type DRX1

Dual range Coil with  
reaction with 2 mains  
and 2 battery circuits, 4/0  
type DRK2

Matched pair Dual Range T.R.F. Coils  
with reaction; with battery and mains  
circuits, type DRM3

Standard I.F. Transformers, type SE, 1 1/2" x 2 1/2", pre-aligned 465 k/c

Miniature I.F. Transformers, type MSE, 1 1/2" x 1 1/2", pre-aligned 465 k/c

Ferrite Rod Aerial, type FRI, long and  
medium wave, complete with fixing  
brackets.


★ All Coils wound on low loss formers  
★ Individually tested and guaranteed

★ Post 3d. on all orders ★ Trade supplied

Distributed by  
**RADIO EXPERIMENTAL PRODUCTS LTD**  
33 MUCH PARK STREET COVENTRY

Telephone Coventry 62572

## BAND 3 CONVERTERS

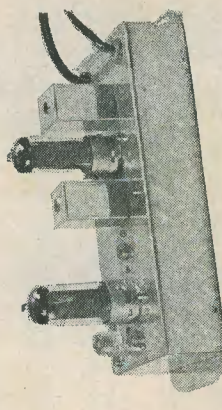

Teleton Mark 1 Converter Kit. Complete kit of  
parts, including coils and valves, etc., £2 7s. 0d.,  
post 6d.

Teleton Mark 2 Converter Kit. As featured in this  
issue. Complete kit of parts as illustrated above,  
including valves (PCC84 & PCC80) and coils, etc.,  
£1 15s., post 6d. Mk. 2 Kit, less valves, £1 15s., post 6d.

Both these Kits include all resistors, condensers,  
valves, valve bases, coil sets, pre-punched chassis with  
bottom screen, nuts, bolts, etc., wiring instructions,  
circuit diagram and alignment instructions.

Mark 1 Coil Set, complete with wiring diagram,  
circuit and alignment instructions, 15/-, post 3d.

Mark 2 Coil Kit, complete with wiring diagram,  
circuit and alignment instructions, 17/6, post 3d.

Chassis, pre-punched with bottom screen, 3/9, post 3d.

## Wireless Marketing Co

29 PRAED STREET  
LONDON W2  
Telephone PAD 1903  
Established 1926

## SMALL ADVERTISEMENTS

continued from page 193

### TRADE

**FM DIPOLE**, comprising two rod elements complete  
with junction box, suitable indoor or outdoor  
erection, 8s. 3d. plus 6d. carriage. **BAND III TV**  
aerial, suitable loft or outdoor erection, 2 elements.  
Yagi complete with junction box, 7s. 6d. carriage 6d.  
Cheapest aerials on the market. Complete range  
Teleton coils at list prices. All radio components  
stocked. Goods sent per return. Wireless Marketing  
Co. (Supplies), 29 Praed Street, London, W.2. Tel.  
PAD 1903.

**BLUEPRINTS**. High Gain 10 metre converter, with  
a de-luxe circuit comprising EF91 RF stage, ECC91  
double triode mixer and oscillator, EF92 IF amplifier,  
with stabilised voltage supply via a 7475, 1s. 8d. post  
free with full instructions. Data Publications, 57  
Maida Vale, London, W.9.

**KENDALL AND MOUSLEY LTD.** Manufacturers of  
laboratory equipment, chassis and instrument cases.  
1s. Also suppliers of B.V.A. valves, Radio and TV  
components. 18 Melville Road, Birmingham 16.

**COILS, COILS, COILS**. We can supply coils for all  
frequencies, RF chokes, filters, etc. Coils wound to  
specifications—send details for estimate. Send SAE  
for circuits and data. The Teleton Co., 266 Nightin-  
gale Road, London, N.9.

**I.P.R.E. PUBLICATIONS**, 5,500 alignment peaks for  
superhets, 5s. 9d. Sample copy *The Practical Radio*  
*Engineer*, 2s. Membership examination particulars,  
1s. Syllabus of TV and Radio Courses free and post  
free. Secretary, I.P.R.E., 20 Fairfield Road, London,  
N.8.

**GOVERNMENT SURPLUS ILLUSTRATED CATA-  
LOGUE No. 12**, containing over 400 items of  
electrical, mechanical and radio equipment for  
experiments, etc., price 1/6, post free. Arthur Sallis,  
93 North Road, Brighton, Sussex.

**OSMOR**—for efficient coils, coilpacks, etc. Send 5d.  
stamp for FREE circuits and lists. Dept. RCC,  
Osamor Radio Products, Ltd., 418 Brighton Road,  
South Croydon, Surrey. Telephone Croydon 5148/9.

**JOIN THE ISWL**. Free services to members including  
QSL Bureau, Translation, Technical and Identifica-  
tion depts. DX certificates, contests and activities  
for the SWL. Monthly magazine "MONITOR"  
duplicated, containing articles of general interest to  
the SWL and League members, 12s. 6d. per annum,  
post free. ISWL HQ., 86 Barringer Road, London,  
N.10.

**BUILD YOUR OWN TV** and learn about its operation,  
maintenance and servicing. Qualified engineer-  
tutor available whilst you're learning and building.  
Free brochure from E.M.I. Institutes, Department  
R.C. 58, London, W.4. (Associated with H.M.V.)

**LEARN AS YOU DO IT**—we provide practical  
equipment combined with instruction in radio,  
television, electricity, mechanics, chemistry, photo-  
graphy, etc. Write for full details to E.M.I. Institutes,  
Department R.C. 47, London, W.4.

NEW SURPLUS	5/-	808	30/-	EF86	12/6
OZ4A	6/	1813	60/	EP9	5/-
IR5	4/	807 (U.S.A.)	7/6	EP2	5/-
IS5	5/		30/	EL32	5/-
IT4	6/	832	12/6	EL31	10/6
IA3	4/6	866A	5/	EL91	11/6
IL4	4/6	874	5/	EX1	12/6
ILN5	5/6	875	5/	EZ40	8/6
2A3	3/6	900	5/	EZ60	8/6
2X2	3/6	903	5/	PC604	12/6
3A4	6/6	906	5/	PC680	12/6
3D8	5/6	906	10/	PL81	13/6
354	8/6	CV286	6/6	PL82	7/6
3V4	8/6	CV287	6/6	N16	12/6
5U4G	8/6	DL33	6/6	N12	12/6
5Z4G	8/6	DAF96	6/6	Y240	30/-
6AB7M	7/6	DK96	6/6	SF8	3/-
6AC7M	6/6	DK96	6/6	U41	10/6
6AK5	6/6	EA30	2/	U41	10/6
6AL5	6/6	EA42	6/6	U110A	4/6
6AP6	6/6	EB3	10/	U120A	3/6
6AT6	8/6	EB91	6/6	VR105/30	7/6
6AU6	8/6	ECC81	10/6	VR150/30	7/6
688M	8/6	ECC82	10/6	VT62	10/-
68A6	8/6	ECH35	10/	W77	5/-
6BE6	7/6	ECH42	10/	X66	7/6
6B57	7/6	EF37	7/6	Z77	8/6
6BR7	11/6	EF50	(3s)	EM80	9/-
6C4	5/	EF5	10/		
6CH6	6/6	EF6	10/		
6F6G	7/6	EF54	5/		
6F7	8/6	EF80	10/		

### DENCO FM RECEIVER

Drilled chassis, FM manual, all components, nuts  
and bolts, etc., and 5 valves (for 2 P stages),  
EB91, 68A6 (2), 12AH8 and EF91. £6 7s. 6d.  
or with Denco dial and drive 9/- extra

**P.O. Type 3000 Relays**. 20,000 ohms, heavy make  
and break (light contacts). Both types 10/6 ea.  
"Panl" Crackle Paint. Black, brown and green,  
3/— tin.

**B7G and B7A** moulded V/hdrs. with screens, 2/— set  
22/6 doz.

**BI Type Tubular, screw fixing Condensers**. 0.05  
mid, 3.5kV wkg. 2/—, Ditto 0.5 mid 800V wkg. 1/6.

Mica 0.001 mfd. 0.01 mid, 350V wkg. 3/— doz., 24/— gross

T.C.C. 100 mid 450V wkg. can elects. 4/6 ea.

B.E.C. 60+100 mid 275V wkg. 350V pk. 4/6 ea.

**American oil-filled Block Condensers** with clips.  
10 mid 600V wkg. 7/6

**M.C. Meters**, 2" round flush, 0-500 micro-amps (scaled  
0-10V) 17/6. 2" sq. fl. 0-50M/A 8/6

**For the Radio Controller**. 5-way solenoid operated  
selector mechanisms. A.M. ref. 5D 609. Will operate  
5 sequential controls. See picture in "Radio Control  
of Models", 10/- ea.

### SPECIAL

**Triplet Multirange Foundation Meters**  
scaled for volts, M/A and ohms. 2 1/2" rectangular  
dial. FSD 400 micro-amps. Complete with  
engraved top plate. Brand new—only 27/6 ea.  
Carriage paid.

All surplus material advertised last month still available  
Post/packing—Under 10/- (6d.), 20/- (1/-), 40/- (1/6),  
free over 40/-

## JOHN ANGLIN

160 CLEETHORPE ROAD GRIMSBY LINGS  
Telephone 56315

## ADCOLA

(Regd. Trade Mark)

### SOLDERING INSTRUMENTS



Reg. Design No. 860302 (British, U.S. and Foreign Patents)

Designed for wireless assembly and maintenance

Supplied for all volt ranges from 6/7V to 230/250V 3/16" dia. Bit Standard Model, 25/6

Sole Manufacturers **ADCOLA PRODUCTS LTD.**

Sales Office and Works

Gauden Road London SW4 (MAC 4272)

**H.A.C. SHORT-WAVE EQUIPMENT**  
Suppliers for over 18 years of Radio S.W. Receivers of Quality One-Valve Kit price 25/- Two-Valve Kit price 50/- Improved designs with Denco coils. All kits complete with all components, accessories and full instructions. Before ordering call and inspect a demonstration receiver or send stamped addressed envelope for descriptive catalogue.

**H.A.C. SHORT-WAVE PRODUCTS (DEPT. R)**  
11 OLD BOND STREET LONDON W1

#### OUR NEW

### GOVERNMENT SURPLUS CATALOGUE No. 12

containing over 400 items, price 1/6 post free 2/6 overseas seaml

**ARTHUR T. SALLIS (R.C.)**  
93 NORTH ROAD BRIGHTON SUSSEX  
Telephone Brighton 25806

### BRASS, COPPER, DURAL ALUMINIUM, BRONZE

ROD, BAR, SHEET, TUBE, STRIP, WIRE

3,000 STANDARD STOCK SIZES

No Quantity too Small List on application

**H. ROLLET & CO. LTD**

6 Chesham Place SW1 Telephone SLOane 3463 also at Liverpool Birmingham Manchester Leeds

## PANEL-SIGNS TRANSFERS

**Set No. 1: Receivers and Amplifiers**  
Five sheets 8 1/2" x 5 1/2" containing one Large scale, twelve control panels and wording. 3s. 6d.

**Set No. 2: Test Instruments**  
Five Sheets 8 1/2" x 5 1/2" containing two Medium scales, twelve control panels and wording. 3s. 6d.

Published by

## DATA PUBLICATIONS LTD

57 MAIDA VALE · LONDON W9

Telephone CUNningham 6141 (2 lines)

Trade Enquiries Invited

Telegrams Databux London

### HIGH FIDELITY

COMPONENTS IN STOCK FOR THE  
MULLARD 5-10 AMPLIFIER circuits 2/6  
OSRAM 912 AMPLIFIER circuits 3/6  
DENCO FM TUNER circuits 1/6  
RADIO CONSTRUCTOR FM TUNER circuits 2/-  
Price lists available on request

**J. T. FILMER** ESTATE  
MAYPOLE KENT  
BEXLEY  
Telephone BEXLEYHEATH 7267


### GUARANTEED VALVES — Over 3,000 in Stock

6AM6, 6C4, EF92, 6AL5, EAC91, 6J6  
12AT7, 12AX7, 6AK5, 6F33, EC91, EL91, 6SN7, 6SL7, 6SK7, 6SJ7, R10, 6BA6, 6F17, 6CH6, 6BW6 ... 5/-  
12AU7, 2D21 ... 7/6

**A. A. W. SKILLMAN**  
74 FRANCHISE STREET : WEYMOUTH
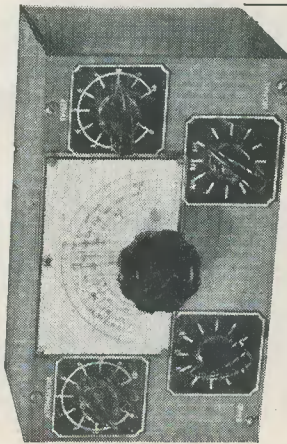
# PANL

Most of the nationally known mail order houses now stock this popular air-drying crackle finish as a regular line at 3/- per 1/2 pc. can, in black, green and brown. If you have any difficulty in obtaining your supply, send 3/6 to **G. A. MILLER 8 Kenton Park Crescent Kenton Middx.**




**Set No. 3: Wording**  
Wording for Receivers, Amplifiers, Transmitters, Test Equipment and other Radio Apparatus.

(4 Sheets, Approx. 400 Words 2s. 6d.)  
Panel-Signs Transfer Fixing Varnish 1s. per bottle

## CONSTRUCTORS build these at low cost!
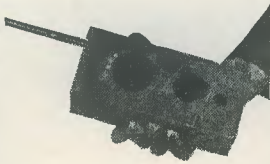
### PERSONAL PORTABLE RADIO

This little set was designed to give you a real personal portable radio that you can enjoy anywhere without disturbing others. Ideal for the holiday, hiking, fishing, camping, cycling, etc. Use it at home, at the office, in bed, or just anywhere.




Send 2/- for layout, Wiring diagram and Components Price List.

### “METEOR” MINI-RECEIVER
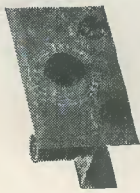
#### COMPONENTS

All Resistors ... 4/3  
All Fixed Condensers ... 9/-  
25pF Variable Condenser ... 2/6  
100pF Variable Condenser ... 2/6  
Panel & Chassis ... 3/6  
Cabinet ... 7/-  
50K Potentiometer ... 3/-  
Phone Plug & Jack ... 5/-  
Knob & Pointer ... 1/6  
PVC Wire, nuts and Bolts, Solder Tags, Solder, Rubber Grommet, Aerial/Earth and 3 way Tag Strip ... 2/6

Ideal for the beginner or those requiring a simple standby receiver.



This 1 valve S.W. receiver can be built for 30/-, from our list of components, which can be purchased separately. It includes valve and 1 coil covering 20-40 metres. Provision is made to increase to 2 or 3 valves if required, and all components are colour-coded so that the beginner can build this set quite easily. Send 2/- for specification, wiring diagram, layout and price list.

Send 2/- for layout, Wiring diagram and Components Price List.

**R.C.S. PRODUCTS (RADIO) LTD**  
11 OLIVER ROAD (Mail order only) LONDON E17

## YOU CAN RELY ON US

We specialise ONLY in radio and electronic components, a comprehensive stock of which are held by us, to supply Government, educational and commercial laboratories. Can we be of some help to you, the experimenter and constructor?

Here are a few of our many stock lines—

**Tapped Volume Controls**, 1/2mg, 1mg, 10mg, 100mg, 1000mg, 10mg, 100mg, 1mg, 10mg, 100mg, 1000mg; **Surplus Stock Potentiometers**, less switch, 2/3; with, 4/3; D/P, 5/-; midget, wirewound, preset, etc., in stock.

**All J.B. Scales and Gangs**. Full vision, 13/9; SL8, 27/6; SL5, 26/-; 3-gangs in .0003 and .0005, 18/3; Single gang .0005, 9/-; Twin midget gang, covered, 11/-.

**Bulgin Plugs, Sockets, Panel Lights, etc.** Belling-Lee Co-ax. Plugs, 1/3, Sockets, 1/2. Plugs, Sockets, etc. Resistors, 10 ohms to 15 mgs in 1/2W, 1/4W, 4d.; 1W, 8d.; 2W, 1/4; midget 1/2W T-type, 6d.; High stability 2% 100-2 megs, 1/6 each; wirewound (green vitreous), 33 ohms to 10K, 10 watts Max., 2/- each.

**Over 200 T.C.C. types of Condenser**. 189 types of Hunts. Electrolytics new and surplus. 10,000 surplus Valves plus large stock BVA Valves.

**1% Silver Micas**, 1.5pF to 100pF, 1/-; 100pF to 280pF, 1/2; 300pF to 500pF, 1/4; 515pF to 815pF, 1/6; 1,000pF to 5,000pF, 2/6.

**COILS—COMPLETE RANGE OF DENCO, WEYMOUTH, WEARITE, OSMOR, R.E.P., TELETRON, DENCO F.M. UNIT PARTS, '912' PARTS, MULLARD '510' PARTS—ALL TAYLOR, AVO INSTRUMENTS IN STOCK, CELESTION, ROLA, ELAC, W.B., WHARFEDALE, GOODMAN'S SPEAKERS.**

Send now for our Supplementary Winter List with H.P. Terms—Quotes S.A.E. Please. Postage extra Next to South Ealing Tube Station 65 Bus.

82 SOUTH EALING ROAD  
LONDON W5 Telephone EAL 5737

**RADIO SERVICING 00**