

# RADIO



# BOOKS

### DATA BOOK SERIES

- DB5 **TV Fault Finding.** Profusely illustrated with photographs taken from a television screen depicting the faults under discussion, and containing a wealth of technical information, with circuits, enabling those faults to be eradicated. B.B.C. and I.T.A. 5/-, Postage 5d.
- DB6 **Radio Amateur Operator's Handbook.** Contains Prefix Lists, Zone Boundaries, Call Areas, Code and Mileage Tables and much other useful operating data. 1958/9 Edition. 3/6, Postage 4d.
- DB8 **Tape and Wire Recording.** A selection of articles covering both the theory and practical applications. 4th Edition. 3/-, Postage 4d.
- DB9 **Radio Control for Model Ships, Boats and Aircraft.** By F. C. Judd, G2BCX. Now considered a standard work on this subject.  
Standard edition 8/6, Postage 7d.  
Clothbound edition 11/6, Postage 8d.
- DB10 **Radio Control Mechanisms.** By Raymond F. Stock. The only book devoted to this subject, and complementary to DB9. 4/6, Postage 4d.
- DB11 **Quality Amplifiers.** Contains a selection of popular quality amplifiers, including latest versions of the Mullard "3-3" and "5-10" 4/6, Postage 4d.

### RADIO REPRINT SERIES

- RR3 **The Argonaut AM/FM/MW/VHF Tuner Receiver.** A Jason design. 2/-, Postage 4d.
- RR4 **The "Eavesdropper."** 3-Transistor local station pocket receiver. 1/6, Postage 2d.
- RR5 **Mercury Switched-Tuned FM Tuner.** A Jason design. 2/-, Postage 2d.
- RR6 **The Cooper-Smith B.P.I. High Fidelity 10-12 watt Amplifier and Control Unit.** 2/6, Postage 4d.
- RR7 **A Versatile 2-valve Audio Pre-Amplifier.** A Mullard design. 1/-, Postage 2d.
- RR8 **High-Gain Band 3 Pre-Amplifier.** 1/-, Postage 2d.
- RR9 **The Jupiter Stereophonic Amplifier and Pre-Amplifier.** 2/6, Postage 4d.

All available from your local bookseller, or from

## DATA PUBLICATIONS LTD

57 MAIDA VALE LONDON W9

Telegrams Databux London

Telephone CUNningham 6141 (2 lines)

Published in Great Britain by the Proprietors and Publishers  
Data Publications Ltd 57 Maida Vale London W9

Printed by A. Quick & Co. (Printers) Ltd 125 High Holborn London WC1 England also at Clacton-on-Sea  
Obtainable abroad through the following Collets Subscription Service Continental Publishers & Distributors Ltd  
William Dawson & Sons Ltd Australia and New Zealand Gordon & Gotch Ltd South Africa Central News Agency  
Holland "Radio Electronica"

Registered for transmission by Magazine Post to Canada (including Newfoundland)

MULLARD TAPE AMPLIFIER TYPE "C", Part 2

VOLUME 12  
NUMBER 5  
DECEMBER  
1958

# The RADIO Constructor



RADIO · TELEVISION · AUDIO · ELECTRONICS

## THE PREMIER *Petite* BATTERY PORTABLE RADIOGRAM

Described by  
*James S. Kent*



Included in this issue  
A SHORT WAVE CONVERTER  
SIMPLE POCKET TRANSISTOR TESTER  
WIDE RANGE AUDIO OSCILLATOR  
TWO-VALVE SHORT WAVE RECEIVER  
UNDERSTANDING TELEVISION, contd.  
WIDE RANGE GRID DIP METER, Further Notes

## DATA Publications 1/9



## THE MODERN BOOK CO

**A Beginner's Guide to Television.**  
By F. J. Camm. 7s. 6d. Postage 6d.

**TV Fault Finding.** A Data Publication.  
5s. Postage 6d.

**Oscilloscope Equipment.** By D. W. Easterling. 5s. Postage 4d.

**Elements of Tape Recorder Circuits.**  
By H. Burstein and H. C. Pollak. 23s.  
Postage 9d.

**The Radio Amateur's Handbook.**  
By A.R.R.L. 32s. 6d. Postage 1s. 9d.

**World Radio Handbook for Listeners.** 1958 ed. 13s. 6d. Postage 1s.

**Radio Valve Data.** 6th Ed. Compiled  
by "WW". 5s. Postage 9d.

**Quality Amplifiers for A.C. Mains.**  
Data Publications. 4s. 6d. Postage 4d.

**Electronic Puzzles and Games.** By  
M. Mandl. 15s. Postage 8d.

**An Electronic Organ for the Home  
Constructor.** By A. Douglas. 15s.  
Postage 9d.

**Electronic Hobbyists' Handbook.**  
By R. P. Turner. 20s. Postage 9d.

**High Fidelity Sound Reproduction.**  
By E. Molloy. 20s. Postage 1s.

**Basic Mathematics for Radio and  
Electronics.** By F. M. Colebrook and  
J. W. Head. 17s. 6d. Postage 1s.


**Transistor Circuits.** By R. P. Turner.  
22s. Postage 9d.

We have the Finest Selection of British and American Radio Books in the Country  
Complete catalogue 6d.

**19-23 PRAED STREET (Dept RC) LONDON W2**

Telephone PADdington 4185

## YOU CAN RELY ON US

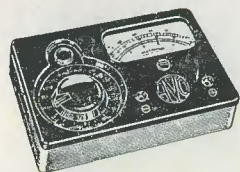

### The New AVO MULTIMINOR

A first quality pocket instrument

Sensitivity 10,000Ω/V 0 to 1A in five ranges, 0 to 1,000V in 7 ranges. A.C. volts 0-1,000 in 5 ranges. Resistance 0-2 Meg in two ranges.

**PRICE £9.10.0** Leather Case 32/6

or 63/4 Deposit and 6 Payments of 22/2 or 9 monthly payments of 23/3

ALL AVO INSTRUMENTS IN STOCK

### COSSOR HI-FI AMPLIFIER KIT

3 valve 3W, Printed Circuit, twin speaker. Beautifully kitted by  
Cossor Radio and Television Ltd to the last nut and bolt.

**COMPLETE KIT** or 65/- Deposit and 6 monthly Payments of 23/4  
**£9.15.0** or 23/10 Deposit and 8 monthly Payments of 23/10

82 SOUTH EALING ROAD  
LONDON W5 Tel EAL 5737


## RADIO SERVICING CO

## THERE'S NO KIT LIKE
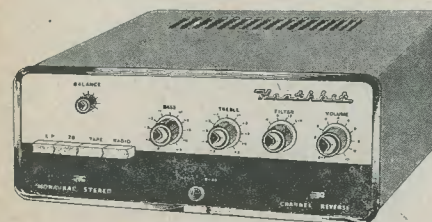
# Heathkit

'BUILD-IT-YOURSELF' ELECTRONIC EQUIPMENT

Other new Heathkits to be released during  
DECEMBER 1958



**THE NEW MODEL S-88  
HI-FI STEREO SOUND  
PRE-AMPS & POWER AMPS  
COMBINED IN ONE UNIT**

16 WATTS OUTPUT  
0.1% DISTORTION

**CASH PRICE £25.5.6**  
Delivered free U.K.

**OTHER RELEASES**

\* **TRANSISTOR  
PORTABLE  
SPEAKER  
SYSTEMS**

Shall we  
send you  
details?

COMING  
SHORTLY  
**OSCILLOSCOPE  
TRANSISTOR RECEIVER  
TRANSISTOR PORTABLE  
TRANSMITTER**

ABRIDGED SPECIFICATION

7 voltage ranges (A.C. & D.C.) 1.5 to 1,500V  
Electronic Ohmmeter (7 ranges) .1Ω to 1,000MΩ  
Input Resistance 11MΩ  
Multipliers 1% Precision Type  
Circuit Board Printed Circuit, Gold Plated  
Frequency Response ±1dB, 42 c/s to 7.2 Mc/s  
Meter 4½" scale, 200μA movement, reading directly  
D.C. & A.C. volts (RMS) & Pk to Pk, Ohms & Decibels  
Comprehensive construction manual  
for simplified assembly, operation & servicing

**£15.14.0**

Delivery free U.K. complete with test leads and battery. Deferred terms available.


**DAYSTROM LIMITED** GLEVUM HALL  
GLOUCESTER · ENGLAND

A MEMBER OF THE DAYSTROM GROUP, MANUFACTURERS OF

**THE LARGEST-SELLING ELECTRONIC KITS IN THE WORLD**


DELIVERY  
EX STOCK

## VALVE VOLTMETER

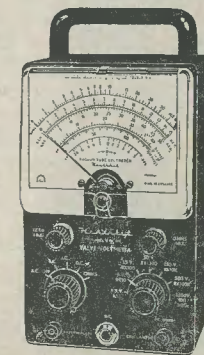

MODEL  
V-7A



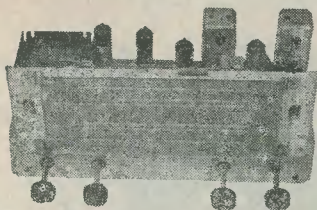

### 1959 RADIOGRAM CHASSIS

THREE WAVEBANDS FIVE VALVES  
S.W. 16 m.-50 m. LATEST MULLARD  
M.W. 200 m.-550 m. ECH42, EF41, EBC41,  
L.W. 800 m.-2,000 m. EL41, EZ40  
12 month Guarantee. A.C. 200/250V, 4-way switch.  
Short-Medium-Long-Gram. A.V.C. and negative feed-  
back. 4.2 watts. Chassis 13 1/2" x 5 1/2" x 2 1/2". Glass dial  
12 1/2" x 5 1/2" horizontal or vertical 10" x 4 1/2". 2 pilot lamps.  
Four knobs, walnut or ivory, aligned and calibrated.  
Chassis isolated from mains. Immediate delivery.

**BRAND NEW £9.10.0 Carr. 4/6**

TERMS: Deposit £5.5.0 and 5 monthly payments of £1  
MATCHED SPEAKERS: 8" 17/6, 10" 25/-, 12" 30/-

★ **GARRARD 4-SPEED SINGLE RECORD PLAYER 4SP** ★  
**£8 AUDIO PERFECTION POST FREE**

De luxe Cabinet with amplifier and 6 1/2" speaker £6.15.0  
or complete kit £14.10.0

### BUILD THIS REPRODUCER BARGAIN SPECIAL SINGLE PLAYER KIT

COLLARO 4-speed Gram-Pick-up Unit £4.12.6  
Handsome portable case 17 1/2" x 13 1/2" x 7" with  
room to play 12" records £2.5.0  
Ready-built 3 watt amplifier with two valves  
and 7" elip. speaker, printed circuit £3.12.6

or **£9.15.0** complete kit post free  
£3.5.0 extra with Garrard 4SP

### I.F. TRANSFORMERS 7/6 pair

465 kc/s slug tuning miniature can 2 1/2" x 1" x 1".  
High Q and good band width. By Pye Radio. Data  
sheet supplied.  
Wearite M800 Midget I.F.S. 465 kc/s 12/6 pair  
Wearite 550 Standard I.F.S. 465 kc/s 12/6 pair

### New boxed VALVES 90-day Guarantee

1R5	8/6	6K8	8/6	EA50	1/6	EZ80	9/6
1S5	8/6	6L6	10/6	EABC8010/6	1/6	E1148	1/6
1T4	8/6	6Q7	10/6	EB91	6/6	HABC80	12/6
2X2	2/6	6SA7	10/6	EBC33	8/6	HVR2A	7/6
3S4	8/6	6SJ7M	10/6	EBC41	10/6	MU14	10/6
3V4	8/6	6SN7	8/6	EBF80	6/6	P61	6/6
3Y4	8/6	6V6G	7/6	ECC84	12/6	PCB84	12/6
5Y3	8/6	6X4	7/6	ECF80	11/6	PCF80	11/6
5Z4	10/6	6X5	7/6	EFC82	11/6	PCF82	11/6
6AM6	8/6	757	10/6	ECH42	10/6	PCL82	11/6
6B8	5/6	12AH8	10/6	ECL82	12/6	PEN25	6/6
6BE6	7/6	12AT7	10/6	EF39	7/9	PL82	10/6
6BH6	10/6	12AU7	9/6	EF41	10/6	PY80	10/6
6BW6	10/6	12AX7	9/6	EF50	5/6	PY81	10/6
6D6	7/6	12BE6	9/6	EF50	8/6	PY82	10/6
6F6	7/6	12K7	8/6	Sylv.	5/6	SP61	5/6
6H6	3/6	12Q7	8/6	EF80	10/6	UBC41	10/6
6J5	6/6	35L6	9/6	EF92	5/6	UCH42	10/6
6I6	7/6	35Z4	9/6	EL32	5/6	UF41	10/6
6J7	8/6	80	10/6	EL84	10/6	UL41	10/6
6K6	6/6	807	6/6	EY51	12/6	UY41	10/6
6K7	5/6	954	1/6	EZ40	10/6	U22	10/6

A Merry Christmas to all readers of "The Radio Constructor"

### C.R.T. ISOLATION TRANSFORMERS

For Cathode Ray Tubes having heater-cathode short circuit and for C.R. Tubes with falling emission.  
**Type A.** Low leakage windings. **Optional 25%** and **50%** boost on secondary: 2V, or 4V, or 6.3V, or 10.3V, or 13.3V, with mains primaries, 12/6  
**Type B.** Mains input. Low capacity. Multi-output 2, 4, 6.3, 7.3, 10 and 13V. Boost 25% and 50%. This transformer is suitable for all TV tubes. 21/- each.  
**Type C.** Low capacity transformer for 2V tubes with falling emission. Mains input. Output 2, 2 1/2, 2 3/4, 3V at 2A, 17/6 each

**RESISTORS.** Preferred values. 20% 10 ohms to 10 meg. 1/4W 4d., 1/2W 4d., 1W 6d., 1 1/2W 8d.

**HIGH STABILITY.** 1/4W 1%, 2/- All preferred values 100Ω-10MΩ. Ditto 5% 100Ω-5MΩ 9d. each

5 watt } **WIRE-WOUND RESISTORS** { 1/3  
10 watt } 25 ohms-10,000 ohms { 1/6  
15 watt } { 2/-

15,000 ohms-50,000 ohms, 5W, 1/9; 10 W, 2/3

**WIRE-WOUND POTS** 3W Lab. Colvern, etc. Pre-set min. TV type. Standard size Pots, 2 1/2". Knurled slotted knob. Spindle, high grade. All values 25 ohms to 30k. Spindle, 100 ohms to 50k, 3/- each, 50k, 4/-  
5W/100k, 6/6  
Ditto Carbon Track 50k W/W EXT. SPEAKER CONTROL 10Ω, 3/-

### MAINS TRANSFORMERS

**STANDARD.** 250-0-250, 80mA, 6.3V tapped 4V 4A. Rectifier 6.3V 1A tapped 5V 2A and 4V 2A 22/6  
Ditto 250-0-350 22/6

**MINIATURE.** 200V 20mA, 6.3V 1A 10/6  
**MIDGET.** 220V 45mA, 6.3V 2A 15/6

**SMALL.** 220-0-220, 50mA, 6.3V 3A 17/6  
**STANDARD.** 250-0-250, 65mA, 6.3V 3.5A 17/6

**HEATER TRANS.** 6.3V 1 1/2A 7/6  
Ditto, tapped sec. 2, 4, 6.3V 1 1/2A 8/6  
Ditto, sec. 6.3V 3A 10/6

Mullard "510" Mains Transformers 38/6

**O/P TRANSFORMERS.** Heavy duty 50mA, 4/6. Multi-ratio push-pull, 7/6. Miniature 3V4, etc., 4/6. Small pentode, 4/6. Hygrade push-pull 7 watts, 15/6. Mullard "510" 6k or 8kΩ, 30/-

**L.F. CHOKES** 15/10H 60/65mA, 5/-; 10H, 85mA, 10/6; 20/15H, 120/150mA, 12/6; 5H, 250mA, 15/-

**CRYSTAL MIKE INSERT** by Acos, 6/6  
Precision engineered. Size only 3/4" x 3/4"  
**ACOS CRYSTAL DESK MIKE** 33/2, 35/-

**ALADDIN FORMERS** and cores. 1/8" 8d., 3/8" 10d. 0.3" FORMERS 5937/8 and cans TV1/2. 3/8" sq. x 2 1/2" and 3/8" sq. x 1 1/2", 2/- complete with cores

**SLOW MOTION DRIVES.** Epicyclic ratio 6-1, 2/3 TYANA. Midget Soldering Iron. 200/250V or 230/250V, 16/9. **SOLON MIDGET IRON**, 25W, 24/-

**MAINS DROPPERS.** 3" x 1 1/2". Three adj. sliders, 0.3A 750 ohms, 4/3; 0.2A 1,000 ohms, 4/3

**LINE CORD.** 0.3A 60 ohms per foot, 0.2A 100 ohms per foot, 2-way, 6d. per foot; 3-way, 7d. per foot

**MIKE TRANSF.** 50:1, 3/9; 100:1, potted, 10/6

**LOUDSPEAKERS.** P.M. 3 ohm. 2 1/2" and 5", 17/6; 6" x 4" Rola, 18/-; 4" Hi-Fi Tweeter, 25/-; 8" Plessey, 19/6; 6" Goodman, 18/6; 10" R.A., 30/-; 12" Plessey, 30/-; 10" x 6" R.A., 27/6; 12" Baker 15W 3 ohm or 15 ohm models, 105/-; Stentorian HF1012 10" 3 to 15 ohms 10W, 99/6

**CRYSTAL DIODES.** G.E.C., 2/-; GEX34, 4/-

**40 CIRCUITS FOR GERMANIUM DIODES,** 3/-

**TUNING AND REACTION CONDENSERS** 100pF, 300pF, 500pF, 3/6 each, solid dielectric

**H.R. HEADPHONES** 4,000 ohms, brand new, 16/6 pr.

**SWITCH CLEANER FLUID,** squirt spout, 4/3 tin

**TWIN GANG CONDENSERS.** 365pF, miniature, 1 1/2" x 1 1/2", 10/-; 0.0005 standard with trimmers, 9/-; less trimmers, 8/-; Midget 7/6; 50pF single, 2/6

**Aluminium Chassis.** 18 s.w.g. Plain, undrilled, with 4 sides, riveted corners and lattice fixing holes, with 2 1/2" sides. 7" x 4", 4/6; 9" x 7", 5/9; 11" x 7", 6/9; 13" x 9", 8/6; 14" x 11", 10/6; 15" x 14", 12/6; 18" x 16" x 3", 16/6

### Volume Controls

Midget size Long spindles. Guaranteed 1 year. All values 5,000 ohms to 2 Meg.

No Switch D.P. Switch 3/- 4/9

Linear or Log Tracks

### 80Ω Coaxial Cable

Semi-air spaced Polythene insulated 1/8" dia. stranded core. Ideal Band III 9d. yd. Losses cut 50%

FRINGE QUALITY Air-spaced Coaxial 1/6 yd

Coaxial Plugs 1/- Double Socket 1/3

Sockets 1/- Outlet Boxes 4/6

Balanced Twin Feeder, per yd 6d., 80Ω or 300Ω

Twin Screened Balanced Feeder, 1/6 yd, 80 ohms

Trimmers. Ceramic, 30, 50, 70pF, 9d. 100pF, 150pF, 1/3; 250pF, 1/6; 600pF, 750pF, 1/9. Philips, 1/- each

**BLACK CRACKLE PAINT.** Air drying, 3/- tin

**P.V.C. CONN. WIRE,** 8 colours, single or stranded, 2d. yd. Sleeving 1, 2mm, 2d., 2, 3mm, 3d., 6mm, 5d. yd

**5" RADIO SCREWDRIVERS,** 6d. each

**NEON MAINS TESTER SCREWDRIVERS,** 5/3

**SOLDER RADIOGRADE,** 3 yds 9d., 1/6 2/6

**Sentercel Rectifiers.** E.H.T. Type Flyback. Voltages: K3/25 2kV, 5/-; K3/40 3.2kV, 7/-; K3/45 3.6kV, 7/6; K3/50 4kV, 8/-; K3/100 8kV, 14/6

50 cps voltage 30% of above ratings

**Mains Type RM1,** 125V 60mA, 5/-; RM2 100mA, 6/-; RM3 120mA, 8/-; RM4 250V 275mA, 16/-; RM5, 20/-

**Miniature Contact Cooled Rectifiers.** 250V 60mA, 7/6; 250V 85mA, 9/6. Selenium Rect. 300V 85mA, 7/6

Coils. Wearite "P" type, 3/- each. Osrom Midget "Q" type, adj. dust core, from 4/- each. All ranges

**Teletron A.H.F. L. & Med. T.R.F.** with reaction, 3/6

**Ferrite Rod Aerials.** M.W., 8/9; M. & L., 12/6

**T.R.F. Coils A/HF, 7/- pair. H.F. Chokes, 2/6**

**Speaker Fret.** Gold cloth, 17" x 25", 5/-; 25" x 35", 10/-

Expanded metal, silver, 15 1/2" x 9 1/2", 2/- each; Tygan. 4" 6" wide, 10/- ft; 2" 3" wide, 5/- ft. Samples

**SUPERHET COIL PACK 27/6**

Miniature size high Q coils. Short, Med., Long, Gram, switching, with connection diagram. 465 kc/s i.f.

**Condensers.** New stock, 0.001μF 7kV T.C.C., 5/6 ditto 20kV, 9/6; 100pF to 500pF Micas, 6d.; Tubular 500V 0.001 to 0.001μF, 9d.; 0.05, 0.1, 1/-; 0.25, 1/6; 0.5, 1/9; 0.1/350V, 9d.; 0.01/2,000V, 1/9; 0.1/2,000V, 3/6

**Ceramic Condensers.** 500V 0.3pF to 0.01μF, 10d.

**Silver Mica.** 10% 5pF to 500pF, 1/-; 600pF to 3,000pF, 1/3; close tolerance (plus or minus 1pF), 1.5pF to 47pF, 1/6; ditto 1% 50pF to 815pF, 1/9; 1,000pF to 5,000pF, 2/-

**NEW ELECTROLYTICS FAMOUS MAKES**

**TUBULAR TUBULAR CAN TYPES**

1/350 2/2- 64/350 5/6 8/500 3/-

2/450 2/3- 100/25 2/- 16/500 4/-

4/450 2/3- 250/25 2/6 32/350 4/-

8/450 2/3- 500/12 3/- 400/270 5/6

8/500 2/9- 8+8/450 4/6 2,500/3 4/-

16/450 3/6- 8+8/500 5/- 6,000/6 5/-

16/500 4/6- 8+16/450 5/- 32+32/350 4/6

32/450 5/8- 8+16/500 5/6 50+50/350 7/-

25/25 11/9- 16+16/450 5/6 64+120/275 7/6

50/25 2/- 32+32/350 4/6 64+120/350 11/6

50/50 2/- 32+32/500 7/6 100+200/350 12/6

**Full Wave Bridge Selenium Rectifiers.** 2, 6 or 12V 1 1/2A, 8/9; 2A, 11/3; 4A, 17/6. Free charger circuit

**Charger Transformers.** Tapped input 200/250V for charging at 2, 6 or 12V 1 1/2A, 15/6; 2A, 17/6; 4A, 22/6

**12/6 PURETONE RECORDING TAPE** 1,200ft on standard fitting, 7" metal reels. Spare reels 7" metal, 2/3; 5 1/2" plastic, 3/-; 7" plastic, 4/-

**SUPERIOR 1,200ft plastic tape, 21/-; 7" plastic reel**

**EMITAPE 7" Long Play 1,800ft, 45/-**

**INSTANT bulk tape eraser, 200/250V a.c., 27/6**

### TELETRON MINIATURE

## "TRANSIDYNE" Superhet Portable

6 Transistors, T.C.C. Printed Circuit

Ferrite aerial, cabinet and all parts. For medium and long wave Designer's Specified Kit

Our price

**£12.19.6**

post free

Size 6" x 4" x 1 1/2"

Plans and parts list

9d.

**6 GENUINE PYE GOLTOP TRANSISTORS ARE INCLUDED WITH THIS KIT, FOR MAXIMUM RESULTS**

**TRANSISTORS.** Pye Goltop Audio V10/15A, 15/-; R.F. 3 Mc/s, V6/R2, 24/-; Sub-miniature Electrolytics 5μF 12V, 8μF 6V, 16μF 12V, 25μF 6V, 3/- each

**THE HIGH GAIN BAND III ITV PRE-AMP Tunable Channels 8, 9 and 10, Gain 17dB, Cascode Circuit.** Complete kit with ECC84 valve, plans and instructions, 29/6 less power, or 49/6 with power pack. Plans only, 6d. Band I B.B.C. version available for channels 1 to 5, same prices

**Wavechange Switches.** 2 p 2-way, 3 p 2-way, short spindle, 2/6; 5 p 4-way 2 wafer, long spindle, 6/6; 2 p 6-way, 4 p 2-way, 4 p 3-way, long spindle, 3/6; 3 p 4-way, 1 p 12-way, long spindle, 3/6; wave change "MAKITS", 1 wafer, 8/6; 2 wafer, 12/6; 3 wafer, 16/-; 4 wafer, 19/6; 5 wafer, 23/-; 6 wafer, 26/6

**Toggle Switches,** s.p. 2/-, d.p. 3/6, d.p.d.t. 4/-

**JASON FM TUNER COIL SET, 26/-.** H.F. coil, aerial coil, oscillator coil, two i.f. transformers 10.7 Mc/s, detector transformer and heater choke. Circuit and component book using four 6AM6, 2/-

**Complete Jason FM Kit,** with valves and Jason superior calibrated dial, £6.15.0, post free

**Mullard 3-3.** Quality amplifier ready built, with power socket for tuner, £7.17.6

**Valveholders.** Pax. int. oct., 4d. EF50, EA50, 6d. B12A, CRT 1/3. Eng. and Amer. 4, 5, 6 and 7 pin, 1/-

**MOULDED Mazda and int. oct., 6d., 6/6, B8A, B8G, B9A, 9d. B7G with can, 1/6. B9A with can, 2/6.**

**Ceramic, EF50, B7G, B9A int. oct., 1/-.** B7G with can, 1/9; B9A with can, 2/9

**HANDY VOLTMETERS.** 2" Twin Range 0-25V, 0-250V d.c. with leads and leather case, 9/6 each

**TV Fault Finding.** Data Publications 5/- each









**Radio Valve Guide.** Books 1, 2 or 3 5/- each

**TELETRON 'COMPANION' PRINTED CIRCUIT TRANSISTOR THREE**

**£5.15.0**

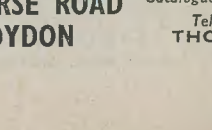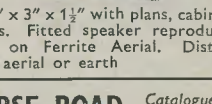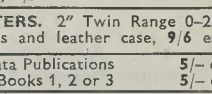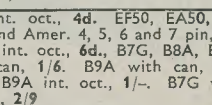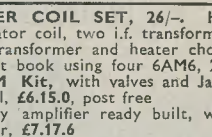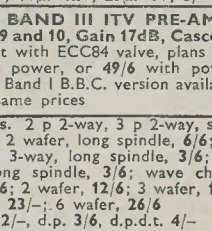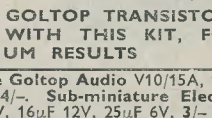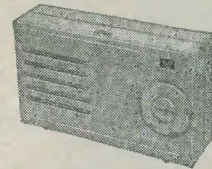**WITH 3 PYE GOLTOP TRANSISTORS**

Pocket receiver kit, 4 1/2" x 3" x 1 1/2" with plans, cabinet, all parts and batteries. Fitted speaker reproduces strong local stations on Ferrite Aerial. Distant reception with simple aerial or earth



### 48-HOUR POSTAL SERVICE



# PREMIER RADIO COMPANY

B. H. MORRIS & CO (RADIO) LTD

(Dept. R.C.7) 207 EDGWARE ROAD LONDON W2  
Also 23 Tottenham Court Road London W1

Telephone  
AMB 4033  
PAD 3271

Open till 6 p.m.  
Saturday



## THE "PETITE" PORTABLE

MAY BE BUILT FOR **7 GNS.**  
plus 3/- post & pkg.

Batteries extra  
H.T. 10/- (Type B126) or equivalent.  
L.T. 1/6 (Type AD 35) or equivalent.

- ★ Size only 8" x 8" x 4 1/2"
- ★ Weight including batteries 5 1/2 lb
- ★ 4 valves of the economy type
- ★ Medium and long wave superhet circuit
- ★ High Q frame aerial
- ★ High sensitivity on both wavebands
- ★ Pre-aligned i.f. transformers
- ★ 5" speaker of the latest type
- ★ Automatic on/off switch operated by lid
- ★ Designed in our own laboratory
- ★ Backed by an up-to-date Technical Information Dept.
- ★ Components available separately if desired
- ★ Simple to construct, using normal soldering methods
- ★ Instruction book 1/6

## THE "PETITE" PORTABLE & REPRODUCER

(As featured in this issue)


MAY BE BUILT FOR **13 GNS.**  
plus 5/- post. & pkg.

Batteries extra: H.T. 10/- (Type B126 or equiv.) L.T. 996, 3/6

45 r.p.m. Single Record Player  
£5.5.0 including P.T.  
"Petite" Components  
£5.13.0

Portable Case £2.10.0

- ★ Size 10 1/2" x 9 3/4" x 6"
- ★ Weight including batteries 7 lb
- ★ 45 r.p.m. single record player complete with pick-up
- ★ 6V battery operated
- ★ Incorporates pick-up head protection dome and automatic stylus cleaning brush, overall size 7 1/2" x 6" only
- ★ Automatic stop-start
- ★ Completely battery operated
- ★ Attractive two-tone rexine covered case
- ★ Construction simplicity itself
- ★ Components available separately if required
- ★ Instruction Book 1/6

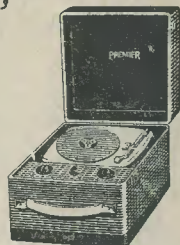


## A COMPLETE RANGE OF PREMIER STEREO EQUIPMENT

Including:


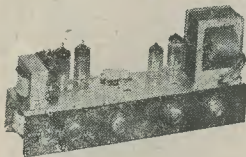
### THE PREMIER DE-LUXE STEREO RECORD PLAYER AMPLIFIER

This is a 4-valve Stereo Amplifier with tone balance, speaker switch and volume control, size 12" long, 5 1/2" high, 3" wide, output of each section is 3 1/2 watts. £8 plus pkg. and post 4/6



De Luxe Portable Cabinet suitable for housing the above Stereo Amplifier with detachable lid which will accommodate an 8" x 5" elliptical speaker, overall size of cabinet 18 1/2" x 13 1/2" x 9" deep. Price 75/- plus 5/- packing and postage

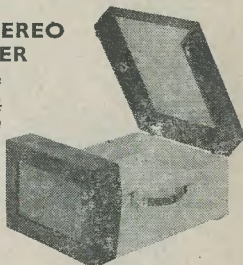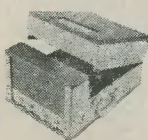Collaro 4-speed Changer £8.19.6, plus 5/- pkg. & post  
B.S.R. 5-speed Changer £6.19.6, plus 5/- pkg. & post



Amplifier Cabinet £2.19.6, plus pkg. and post 5/-

### THE "TRANSIDYNE"

Printed Circuit Transistor Pocket Superhet  
A printed circuit pocket size Transistor Receiver, professional in appearance and of outstanding performance. Incorporates T.C.C. printed circuit, six transistors (push-pull) to cover medium and long waves, utilises 2 Ever-Ready, or equivalent, No. 8 batteries. Attractive cream and red plastic cabinet with engraved dial. Overall dimensions 7 1/2" x 3 3/4" x 1 1/2". Total weight when assembled, including batteries, only 20 oz. Our price for all required components, including batteries, £11.19.6, plus 2/6 p. and p. Complete cabinet and dial assembly, printed circuit, battery holder, nuts and bolts and full assembly instructions, 25/-, plus 1/6 p. and p.

PLEASE ADDRESS ALL ENQUIRIES TO — 207 EDGWARE ROAD . LONDON . W2

### THE NORA AM/FM RADIOGRAM CHASSIS

Designed for the American market by a famous continental manufacturer

CASH PRICE **£16.19.6** Plus 7/6 packing and carriage

OR Deferred Terms:


H.P. Deposit £8.9.6 and 10 monthly payments of 19/-  
Credit Deposit £2.2.6 and 8 monthly payments of £2.1.3.

This chassis is of the very latest design and has a much wider coverage on f.m. than standard receivers. It has 5 valves plus a full-wave metal rectifier, piano type push buttons for long, medium, f.m. and gram., separate tuning on f.m. and a.m. and incorporating a ferrite rod aerial for medium and long wavebands, also gram. pick-up switching. Output 5 watts, dial size 12 1/2" x 2 1/2". Overall size 12 1/2" x 5 3/4" x 7 1/2"

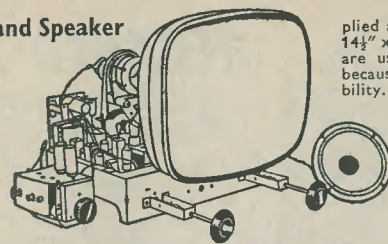
## 17" TV Chassis, Tube and Speaker

£19.19.6

17" Rectangular Tube on modified chassis. Supplied as single channel chassis covering B.B.C. channels 1-5, or incorporating Turret Tuner, which can be added as an extra, at our special price to chassis purchasers of 50/-, giving choice of any two channels (B.B.C. and I.T.A.). Extra channels can be supplied at 7/6 each.



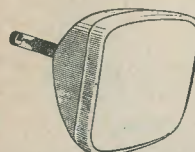Chassis size 12" x 14 1/2" x 11" less valves. Similar chassis are used by well-known companies because of their stability and reliability. With tube and speaker, £19.19.6. With all valves £25.19.6. Complete and working with Turret Tuner, £28.9.6. 12 months guarantee on the tubes. 3 months guarantee on the valves and chassis. Ins. carr. (including tube) 25/-



REGETTERED IMPROVED VACUUM TV TUBES—12 Months Guarantee

17" Rect. £7.10.0 14" Rect. £5.10.0

Our 12 months guarantee (6 months full replacement, 6 months progressive) illustrates our wholehearted confidence in the tubes we offer. We sell many hundreds a week throughout the country and have done so for the past seven years. Many of them go to the trade, i.e. to Insurance Companies, Renters and Retailers, who are thoroughly satisfied with our supplies. Remember, they also hold a 10 days money-back guarantee.

9", 10", 14", 15" and 16" Round Tubes. Our special offer of these sizes, £5. 12" TV tubes, £6. Three months guarantee on round tubes. Ins. carr. 15/6

EXPRESS DESPATCH SERVICE.—Please phone to confirm tube in stock. Send Telegraph Money Order. Tube despatched passenger train same day.

SOUND/VISION & I.F. STRIP, 25/6. Plessey. Tested. I.F.s 10.5 Mc/s sound, 14 Mc/s vision. 8 valveholders. Less valves. Size 8 1/2" x 5" x 4 1/2". Circuit incl. P. & P. 2/6. The tuner unit plugs directly into this chassis.

SOUND/VISION & I.F. STRIP, 10/6. Salvaged. Complete sound and vision strip. 8 valveholders. Less valves. I.F.s 16-19.5 Mc/s. Size 8 1/2" x 4 1/2" x 4 1/2". Drawings free with order. P. & P. 2/6


SOUND/VISION & I.F. STRIP, 10/6. Salvaged. Superhet. 8 valveholders. Less valves. I.F.s 7.25 Mc/s sound, 10.75 Mc/s vision. Vision complete from input up to video output. Sound complete from input to a.f. amplifier. P. & P. 2/6

POWER PACK & AMPLIFIER, 29/6. R.F. E.H.T. tested. Amplifier stage 6V6 with o.p. transformer. 3 ohms matching. Smoothed h.t. 350V at 250mA, 6.3V at 5A, 22V at 3A, 6.3V at 4A and 4V centre tapped. Size 14 1/2" x 8" x 7" (less valves). Drawings free with order. Ins. carr. 5/6

POWER PACK & AMPLIFIER, 19/6. Tested. Output stage 6V6 with o.p. trans. (3 ohms) choke. Smoothed h.t. 350V at 250mA, 6.3V at 5A, 22V at 3A, 6.3V at 4A and 4V centre tapped. Less valves. Ins. carr. 5/6

POWER PACK & AMPLIFIER, 19/6. Output stage PEN45 o.p. trans. choke. Smoothed h.t. 325V at 250mA, 4V at 5A, 6.3V at 5A, 4V at 5A centre tapped. Valve base for rectifier, octal or 4-pin. Output is taken from standard plugs. Less valves. Ins. carr. 5/6

## RECORD PLAYER CABINET 39/6

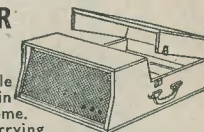

Latest contemporary style rexine covered cabinet in two-tone colour scheme. Hinged clipped lid, carrying handle. Space available for all modern amplifiers and auto-changers, etc. Size 19 1/2" x 15 1/2" x 9". Many other modern designed cabinets at prices from 39/6-79/6. Carr. and ins. 4/6

COLLARO 4-SPEED AUTO-CHANGERS, £7.19.6. Incorporating auto and manual control complete with studio crystal p.u. and sapphire stylus. Also other makes at similar prices. P. & ins. 5/6. A few only, Stereophonic 4-speed Auto-changers

PORTABLE AMPLIFIER MARK D.1, 59/6. 12 months guarantee. Brand new. Latest design with printed circuit. Dimensions 7" x 2 1/2" x 5". A.C. only. Mains isolated. 2-3 watts output. Incorporating EL84 as high gain output valve. Volume and tone controls. Knobs 2/6 extra. P. & P. 3/6



### EXTENSION SPEAKERS 29/9

Polished wood cabinet of attractive appearance. Fitted with 8" P.M. speaker, W.B. or Goodmans, of the highest quality. Standard matching to any receiver (2-5 ohms). Switch and flex included. Ins. carr. 3/6

STEREOPHONIC SOUND. You will find our speakers ideal for this purpose. 8" p.m. speakers, 8/9. With o.p. transformer fitted, 10/- 6 1/2" p.m. speakers, 12/6. Postage 2/9

### MAINS TRANSFORMERS

Drop Through Type, 12/9. 350-0-350V at 250mA, 6.3V at 4A, 6.3V at 4A, 4V at 3A, 22V at 0.3A, 4V centre tapped at 1.5A. Primary 200-250V, 50 c/s. P. & P. 3/9

Half Shrouded Type, 5/9. 280-0-280V at 80mA, 6.3V at 3A, 4V at 2A, 4V at 2A. Primary 200-240V. P. & P. 2/9

Upright Type, 3/9. 350-0-350V at 80mA, 12V at 1.5A, 4V at 2A. Primary 100-120-200-250V. Fully shrouded. Ideal for mains auto transformers. P.P. 2/9

Mains Auto, 12/6. 0-205-225-245V at 300mA. Isolated windings of 6.3V at 2-6A, 6.3V at 3-6A, 2V at 1-4A. P. & P. 3/9

O.P. Trans., 1/3. Standard size 2-5 ohms. Post 1/- 20 for £1. P. & P. 5/6

Send for FREE Catalogue


Liverpool St. to Manor Park Stn. 10 mins.

OPEN ALL DAY SATURDAY  
THURS. CLOSED 1 p.m.

TERMS AVAILABLE

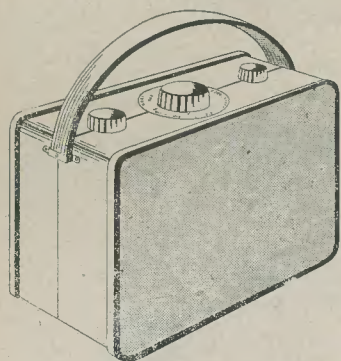**DUKE & CO** (Dept. K.12) 621/3 ROMFORD ROAD MANOR PARK EI2 Telephone 1LF 6001/3





## REPANCO MAJOR-7

ALL-TRANSISTOR PORTABLE

A design embodying 7 brand new transistors

- ★ New Transistors throughout—no surplus.
- ★ Output: 200 milliwatts.
- ★ Fully Tunable over Long and Medium Wave.
- ★ Super sensitive Ferrite Slab Aerial.
- ★ Elliptical Speaker 7" x 4".
- ★ Eyeletted chassis for easy wiring.
- ★ Automatic Volume Control.
- ★ Negative Feed Back.
- ★ 465 kc/s Intermediate Frequency.
- ★ Contemporary Cabinet in Cream and Black.
- ★ Cabinet Dimensions: 9" x 6½" x 4".
- ★ Easy to Build—point to point plans.
- ★ May be used as a combined Car Radio/Portable.

The MAJOR-7 may be built for

(Post Free) **£13 · 19 · 6**

Comprehensive wiring plans and instructions with detailed price list 1/9 (post free)

**RADIO EXPERIMENTAL PRODUCTS LTD**

33 MUCH PARK STREET COVENTRY

POST

21 SELF  
CONTAINED

RANGES

COUPON NOW



You, too, can be SELF-CONTAINED, or completely equipped to tackle any testing job, by owning one of the well-known M.I.P. Series 100 Multi-Range Test Sets. You can have one sent you almost immediately, simply by sending a deposit of 47/6. Balance is payable in 6 monthly instalments of £1.16. Cash price is £12.7.6. Post coupon for full details.

### MULTI-RANGE TEST SET - SERIES 100

To MEASURING INSTRUMENTS (Pullin) Ltd.  
Electrin Works, Winchester Street, Acton, W.3  
Please send illustrated leaflet of the Series  
100 with details of easy payment scheme  
Ditto Series 90  
\*Please indicate instrument required

NAME   
ADDRESS   
F1258

★  
10-1,000 d.c. volts  
10-1,000 a.c. volts  
100 Microamps to  
500 Milliamps d.c.  
100 Microamps a.c.  
0-1 Megohm  
0-10,000 ohms

★  
There is also the SERIES 90 MULTI-RANGE  
TEST SET having 19 SELF-CONTAINED ranges:

ac/dc volts up to 1,000V  
dc current up to 500mA  
ac current up to 200µA  
Resistance 0-200,000Ω  
Deposit 35/- and six  
monthly payments of  
28/10 (cash price £9.15.0)



GD21

326

# There's MORE SCOPE

for the Technical man

## IN A R.A.F. SHORT SERVICE COMMISSION\*

In this age of missiles, electronics and nuclear weapons, the Royal Air Force offers almost unlimited scope for technical ability. As a R.A.F. Technical Officer you would be a key man in a key branch of the Service, doing work that is absorbing, responsible and, above all, varied.

In fact, if you have recently qualified, a R.A.F. Short Service Commission for 3, 4, 5 or 6 years in the Technical Branch gives greater opportunities for gaining all-round experience than almost any civilian appointment.

## Good prospects in the Service—and after


The main need is for electronic engineers and, to a lesser extent, for mechanical engineers. Promotion comes fast in this vital Branch. If you join at, say, 24½ you could be earning £1,250 a year by 30 if married. There are also opportunities of applying for a Permanent Commission; but, if you return to industry, special facilities are available to help you obtain a post in line with your age and added experience. On leaving the R.A.F., you receive a gratuity of £135, free of income tax, for each year served.


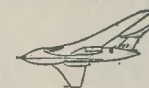
### THESE ARE THE QUALIFICATIONS

You do not necessarily have to be a university graduate; a sound scientific or engineering training is the essential. You must be medically fit and hold, at least, the Higher National Diploma or Certificate in electrical or mechanical engineering, plus G.C.E. at ordinary level in English Language—or equivalent qualifications. You can join as soon as you are

qualified, and up to the age of 37 (or 45 if you have previously held a Service Commission). This is a priority job in a foremost technical service. It offers you valuable experience for your career, excellent pay—and all the wider interest of life as a R.A.F. officer. Write now for full details to Air Ministry (E.C.A.211), Adastral House, London, W.C.1.



## THE ROYAL AIR FORCE

\*IF YOU ARE A GRADUATE with a Science or Engineering degree, and under 30, you can apply for a R.A.F. Permanent Commission straight away. Write for details of the fine career prospects and pay offered.



327



# There's nothing so good as building it yourself

AND IT'S BEST IF IT'S A

**Jason**kit

When good circuitry and design are presented with straightforward, easily followed instructions, it becomes relatively simple to build technically advanced items of radio, audio and electronic equipment. There are already years of specialised experience in kit design and production behind the new Jasonkit programme. From it, the constructor can choose stereo amplifier and pre-amp designs, first-class f.m. tuners, and soon, a number of items of valuable electronic test equipment. Such is the quality of Jason designs that even to-day, the popularity of the original f.m. tuner, which was the first Jasonkit to be produced, is as great as ever and large numbers continue to be built with complete success.

No special tools or experience are required to build Jasonkits. To the satisfaction of building your own apparatus is added the knowledge that its performance will be the finest possible in its class. Kits are complete, too, down to the last detail, and include chassis and panels punched and drilled to size. Only valves are extra except where otherwise stated.

### BRITISH THROUGHOUT

Details of kits in which you are interested gladly sent on request

DEMONSTRATIONS AT OUR SHOWROOMS EVERY SATURDAY MORNING

**THE JASON MOTOR & ELECTRONIC SALES CO**

- FM tuners
- am/fm tuners
- fm/tv tuners
- stereo amplifiers
- stereo pre-amplifiers
- electronic instruments



### AUDIO

- STANDARD FM TUNER** in chassis form (less valves) **£5.5.0**  
Power Pack Kit **£2.1.9**
- ARGONAUT AM/FM TUNER.** As tuning unit only (less valves) ... .. **£10.10.0**  
As complete receiver (less valves) ... .. **£11.10.0**
- MERCURY SWITCHED FM TUNER** including front end with 2 valves **£9.0.0**
- STEREO AMPLIFIER** (10+10 watts) Power Amplifier with 7 valves ... .. **£17.8.0**
- STEREO PRE-AMP J.4-4** with case, but less valves ... .. **£16.10.0**
- STEREO PRE-AMP J.3-3** with valves and case ... .. **£16.15.0**
- STEREO PRE-AMP J.3-3** with valves, less case ... .. **£16.0.0**
- SIMPLIFIED STEREO AMP** with tone, balance and channel controls (3+3 watts) with valves and case ... .. **£13.19.0**
- FRINGE FM TUNER**, self-powered, less valves ... .. **£8.5.0**
- SWITCHED FM/TV SOUND TUNER**, self-powered, less valves ... .. **£12.19.0**

### INSTRUMENTS

**VALVE VOLTMETER : WOBBULATOR : STABILISED POWER PACK : OSCILLOSCOPE.**—For all who wish to build and experiment to a high degree of accuracy. These kits have attractive uniformly styled front panels and may be built with or without the standardised cases. **FOR RELEASE SHORTLY.**

**3-4(E) GT. CHAPEL STREET OXFORD STREET LONDON W1**

(between Tottenham Court Road and Oxford Circus Station Underground)

Telephone GERard 0273/4



# CLYNE RADIO LTD.



**"The Component Specialists"**

ALL POST ORDERS AND CORRESPONDENCE TO  
162 HOLLOWAY ROAD · LONDON N7  
NOR 6295/6/7

18 TOTTENHAM COURT RD. LONDON W1  
MUS 5929/0095

Callers welcome at both branches

## MULLARD TYPE "C" TAPE PRE-AMPLIFIER

(as described in this issue)

All necessary components, including valves, for this truly "Hi-Fi" pre-amplifier can be supplied at a special inclusive price of

All components available separately if required; send stamp for price list.

**POWER PACK.** All necessary components for power pack for above amplifier.

ONLY  
**£12-9-6**

plus 3/6 P. & P.

**50/-**  
inclusive  
plus 1/6 P. & P.

This combination will be the envy of anyone interested in quality recording and reproduction!!!

## MULLARD 510 ULTRA-LINEAR PRINTED CIRCUIT HI-FI AMPLIFIER

This very famous amplifier is ideal and recommended for use in conjunction with the Type "C" Pre-Amp., enabling unequalled Hi-Fidelity recording and playback from any tape deck! All required components available at only **£9-9-0** (including Ultra-Linear output stage) plus 3/6 P. & P. or assembled and tested **£12.12.0**

Itemised price list and comprehensive instruction book 3/6, post free

## CONSTRUCTORS BARGAINS!

**6V Vibrator Pack.** Ex-W.D. Output 140V 30mA. Fully smoothed. Size only 6½" x 5" x 2½". New condition. 12/6 plus 1/6 p. and p.

**12V Vibrator Pack.** Mallory, brand new. Output 150V 40mA Complete with synchronous vibrator. 12/6 plus 1/6 p. and p.

**12" Plessey P.M. Loudspeaker.** 3 ohm speech coil. Brand new. Only 32/6 plus 2/6 p. and p.

**12" Bakers Selhurst Loudspeakers.** 15 ohm, 15 watt, 30/14,000 c/s. Few only. Brand new. £4 10s. plus 3/6 p. and p.

**Morse Keys. Superior Quality.** Brand new 2/6 plus 1/- p. and p.

**9 WB Hi-Fi Speaker.** Ex-Equip., as new, 3 ohm speech coil, with O.P. Trans., 22/6 plus 2/- p. and p.  
**3-Section Whip Aerials.** Ideal for fishing rods, etc. Each section 4ft. Only 7/6 set, plus 2/6 p. & p.  
**CLR Low Impedance Headphones** 7/6 pair plus 1/- p. and p.

A straightforward guide to the principles of television

## A FIRST COURSE IN TELEVISION

By "Decibel." This new book not only deals in a simple manner with the reception of television pictures but also explains how the signals originate and the techniques involved in the transmission of pictures by television—including colour transmission. Written by the author of that best-seller—A First Course in Wireless, this handy book can be followed easily by the interested amateur as well as those engaged in, or studying for employment in, broadcasting and the servicing of receivers.

From booksellers, 15/- net.

**PITMAN TECHNICAL BOOKS**  
Parker St. Kingsway London WC2

## Transistor Supplies

Red Spots, 7/6; White Spots, 15/-; Yell./Gr., 10/-; Yell./Red, 21/-; OC70, 21/-; OC71, 24/-; OC72, 30/-; OC45, 35/-; OC44, 40/-; XA102, 40/-; XA101, 35/-.

Sub-min. Electrolytics: 5, 8, 10, 16, 25 and 32µF, all 3/6 each.

**Teletron Companion**—all parts with printed circuit, £5.11.6.

**Repanco Mini-7**, all parts, £11.2.6.

**5" P.M. Speaker**, 18/6; 2½", 29/-.

**Ardent Transformers**, D239 and D240, 10/- each; T1079, 12/-; D131 and D132, 12/9 each; D167, 12/-.

**Mullard Circuit Trans.** Driver P.P., 13/6 and 18/6; output to 3 ohms, 13/6 and 18/6.


**BARGAINS.**—These prices include post. Phones (h.r. ex-Govt.), 10/6; **Power Hand Mikes**, 6/6; **Crystal Inserts**, 4/9; **Super 75 ohm Coax.**, 8d. yd; **Condensers**, variable air, .0003, 4/-; .0005, 6/6; .0005 T-gang, 7/6; **Morse Keys**, 3/3.

**TERMS.**—Cash with Order. Post extra; excess refunded. Don't miss our notes on transistors—send 8d. stamp for same.

## MORCO EXPERIMENTAL SUPPLIES

8 & 10 GRANVILLE STREET SHEFFIELD 2  
Telephone 27461

# data for AUDIOPHILES\*

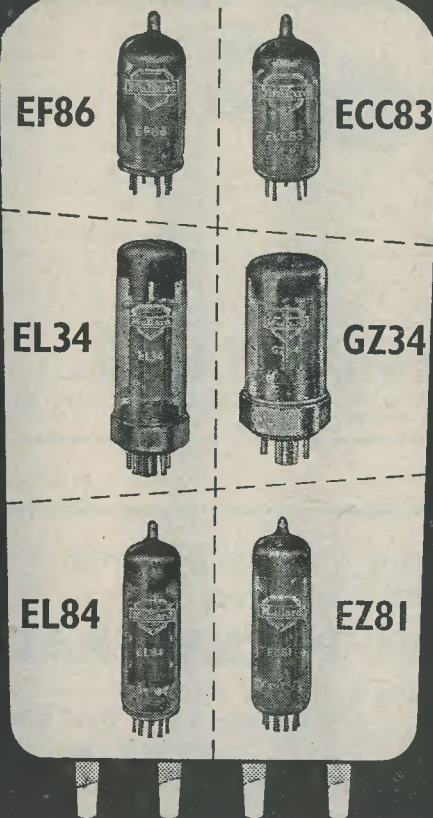

## COUPON

TO: MULLARD LTD., PUBLICITY DIVN.

Please send me, free of charge, leaflets on the Mullard World Series of Audio Valves, and details of "High Quality Sound Reproduction".

NAME .....

ADDRESS .....

Audiophiles all over the world are demanding Mullard audio valves for their high quality sound equipment. And who can blame them when they know that the Mullard World Series of Audio Valves is the finest in the world.

Fill in the coupon below for free data on Mullard World Series Audio Valves.

\* Audiophile—Enthusiast for high quality sound reproduction who is satisfied with nothing but the best.



This popular book is available now from most dealers, price 3/6d. It contains designs and full constructional details of the new Mullard EL34 High Quality 20 Watt Amplifier, a Mullard Band II F.M. Tuner, pre-amplifiers for the Mullard EL34 Amplifier and for the popular Mullard 5 Valve 10 Watt Amplifier, together with other useful technical information.

# Mullard



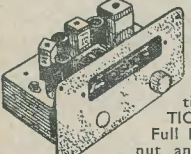

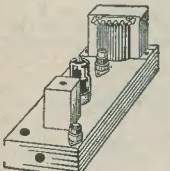
WORLD SERIES  
AUDIO VALVES



Mullard Ltd · Publicity Division  
Mullard House Torrington Place  
London WC1

MVM 349A



<p><b>MULLARD TAPE AMPLIFIERS</b></p>  <p>All parts in stock for the Mullard Type A and Type C tape amplifiers including ready wound ferroxcubes. Send 3d. stamp for full detailed price list.</p>	<p><b>JASON STEREO</b></p>  <p>Start this new exciting super Hi-Fi today and amaze your friends. All component parts in stock for the Jason "Jupiter" Stereo pre-amplifier and amplifier. Send 3d. stamp for detailed price list. Full constructional data reprint 2/9 post paid.</p> <p>WE STOCK THE FULL RANGE OF "BERON" CHASSIS AS ADVERTISED IN THIS ISSUE.</p>						
<p><b>JASON FM TUNER</b></p>  <p>The most popular and successful f.m. tuner kit ever. Build one today and enjoy high quality interference-free reception. FULL CONSTRUCTIONAL DATA 2/4 post paid. Full kit of parts down to last nut and bolt £7.7.6, post 1/-</p>	<p><b>EMPRESS SA9 STEREOPHONIC AMPLIFIER</b></p>  <p>Complete twin channel stereo amplifier. 3½ watts output each channel. Tone, volume and balance controls. Ready to use. Amazing value. Call for demonstration. PRICE £8, post 2/6</p>						
<p><b>I.T.V. PRE-AMPLIFIER</b></p>  <p>Gives amazing improvement to your commercial t.v. picture and sound. No need to touch inside of t.v. Full data in The Radio Constructor March issue. Back numbers or reprint available 1/6 post paid. COMPLETE KIT OF PARTS £2.14.0. Ready built and tested £3.14.0. All post paid.</p>	<p><b>STEREO PICK-UP CARTRIDGES</b></p> <table border="0"> <tr> <td>Ronette L.P. and Stereo with sapphire stylus</td> <td>£3.9.6</td> </tr> <tr> <td>Ronette 78, L.P. and Stereo turn-over</td> <td>£4.3.5</td> </tr> <tr> <td>ACOS GP71 L.P. and Stereo with sapphire stylus</td> <td>£2.15.5</td> </tr> </table> <p><b>"TRANSIDYNE" and "MINI-SEVEN"</b></p> <p>All parts in stock for these transistor pocket portables. Send 3d. stamp for detailed price lists.</p> <p><b>HOME RADIO</b> (MITCHAM) LTD Dept. C 187 LONDON ROAD MITCHAM SURREY Shop Hours 9-6.30 p.m. Weds. 1 p.m. MIT 3282</p>	Ronette L.P. and Stereo with sapphire stylus	£3.9.6	Ronette 78, L.P. and Stereo turn-over	£4.3.5	ACOS GP71 L.P. and Stereo with sapphire stylus	£2.15.5
Ronette L.P. and Stereo with sapphire stylus	£3.9.6						
Ronette 78, L.P. and Stereo turn-over	£4.3.5						
ACOS GP71 L.P. and Stereo with sapphire stylus	£2.15.5						

**A SMALL DEPOSIT** will bring you enough parts to make a complete **TRANSISTOR POCKET RADIO** (Size 5¾ x 3¼ x 1¼) using a printed circuit

★ Send for FREE PRICE LIST (all parts sold separately) and/or 3/- for new simplified instruction booklet with suggested circuits and assembly details.

**FULL MEDIUM & LONG WAVE COVERAGE**  
for as little as **£9.19.6**

- OUR CIRCUITS OFFER  
**HIGH SENSITIVITY**  
**HIGH SELECTIVITY**  
using
- |                  |                  |
|------------------|------------------|
| R.F. Transistors | <b>1GN.</b> each |
| L.F. Transistors | <b>10/-</b> each |
- all specially selected to give **HIGH OVERALL GAIN** with A.V.C.
- Miniature loudspeakers, only 1⅜" deep x 2⅜" diam. **27/6**
  - Miniature oscillator and i.f. coils, 1½" high, ⅝" diam. **8/-**
  - Jackson 00 twin gang tuning condenser with intersection screen **10/6**
  - Attractive high impact polystyrene cabinet with fittings for tuner, trimmers, speaker and circuit board **12/6**

MANY OTHER SUB-MINIATURE COMPONENTS AVAILABLE

**SPECIALISED ELECTRONIC COMPONENTS LTD** 8 Eccleston Square London SW1  
MAIL ORDERS ONLY

The **Radio Constructor**  
incorporating THE RADIO AMATEUR

Vol. 12 No. 5      DECEMBER 1958      ANNUAL SUBSCRIPTION 25/- (including postage)

**CONTENTS**

- |                                     |  |
|-------------------------------------|--|
| <i>Editor</i>                       | <b>334</b> Suggested Circuits: A Short Wave Converter<br><i>by G. A. French</i>                        |
| <b>C. W. C. OVERLAND, G2ATV</b>     | <b>339</b> In Your Workshop  |
| <i>Associate Editor</i>             | <b>344</b> Understanding Television, Part 12<br><i>by W. G. Morley</i>                                 |
| <b>A. C. GEE, G2UK</b>              | <b>348</b> Can Anyone Help?  |
| <i>Business Manager</i>             | <b>349</b> A Simple Pocket Transistor Tester<br><i>by W. E. Griffiths</i>                              |
| <b>J. H. BURROWS, A C A</b>         | <b>350</b> Radio Miscellany, <i>by Centre Tap</i>  |
| <i>Advertising Manager</i>          | <b>352</b> Further Notes on the Wide Range Battery Operated Grid Dip Meter, <i>by D. W. Easterling</i> |
| <b>F. A. BALDWIN, A MIPRE</b>       | <b>355</b> Experimental Chassis Construction,<br><i>by B. T. Denvir</i>                                |
| <i>Offices</i>                      | <b>356</b> A Two-Valve Short Wave Receiver<br><i>by R. E. S. Coulson</i>                               |
| <b>57 MAIDA VALE LONDON W9</b>      | <b>359</b> The Premier "Petite" Battery Portable Radiogram<br><i>described by James S. Kent</i>        |
| <i>Telephone</i>                    | <b>362</b> Book Review   |
| <b>CUNNINGHAM 6141</b><br>(2 lines) | <b>363</b> Technical Forum   |
| <i>Telegrams</i>                    | <b>366</b> The Mullard Tape Amplifier Type "C," Part 2<br><i>described by R. Webb</i>                  |
| <b>DATABUX, LONDON</b>              | <b>374</b> Models for Radio Control—The "Wavemaster",<br>Conclusion, <i>by Raymond F. Stock</i>        |
|                                     | <b>376</b> Trade Review  |
|                                     | <b>377</b> A Wide Range Audio Oscillator<br><i>by W. E. Woodhead</i>                                   |
|                                     | <b>382</b> Inexpensive Loudspeaker Cabinets, <i>by E. G. Wilson</i>                                    |

**NOTICES**

THE CONTENTS of this magazine are strictly copyright and may not be reproduced without obtaining prior permission from the Editor.

ARTICLES appearing in this magazine which describe kits are inserted only on condition that such kits, or special components thereof, are freely available at a trade discount to all retail advertisers.

OPINIONS expressed by contributors are not necessarily those of the Editor or proprietors.

THE EDITOR invites original contributions on construction of radio subjects. All material used will be paid for. Articles should preferably be typewritten, and photographs should be clear and sharp. Diagrams need not be large or perfectly drawn, as our draughtsmen will redraw in most cases, but all relevant information should be included.

ALL MSS must be accompanied by a stamped addressed envelope for reply or return. Each item must bear the sender's name and address.

TRADE NEWS. Manufacturers, publishers, etc., are invited to submit samples or information of new products for review in this section.

TECHNICAL QUERIES should be submitted in writing. We regret that we are unable to answer queries, other than those arising from articles appearing in this magazine; nor can we advise on modifications to the equipment described in these articles.

ALL CORRESPONDENCE should be addressed to THE RADIO CONSTRUCTOR 57 Maida Vale London W9  
REMITTANCES should be made payable to "DATA PUBLICATIONS LTD."



## No. 97 A Short Wave Converter

**SUGGESTED****C  
I  
R  
C  
U  
I  
T  
S**

The circuits presented in this series have been designed by G. A. FRENCH, specially for the enthusiast who needs only the circuit and essential relevant data

FASHIONS CHANGE IN THE FIELD OF commercial sound radio manufacture just as much as they do in other spheres wherein mass-produced articles are dealt with. Up to some four years or so ago the conventional domestic radio receiver nearly always boasted three wave ranges, these consisting of the long, medium and short wave bands. So far as reception conditions in the U.K. were concerned, the provision of a short wave band to a domestic receiver was normally more of a "sales point" than an actual aid to greater programme enjoyment. This was because few listeners ever bothered to leave the long and medium wave bands, being quite content to rely on the material transmitted on the Light Programme and Home Service. Over the last four years the growing popularity and availability of i.m. reception has considerably altered this state of affairs, and the "third wave band" of the average receiver is now almost always devoted to the v.h.f. band. Today, one rarely sees a domestic sound receiver in the normal price ranges which carries a short wave band.

Ironically enough, this situation is beginning to create a certain demand for short wave broadcast reception. The reason for such a demand is obvious enough. There is much of interest in the short wave bands and even the idlest of listeners can derive some casual satisfaction from occasionally swinging the dial of a reasonably sensitive short wave receiver. There seems to be, in particular, a marked interest amongst home-constructors for short wave converters, such converters being capable of installation before the aerial terminals of a conventional sound receiver and of taking advantage of the amplification and selectivity which that receiver offers.

**Design Problems**

The circuit which is described this month is that of a short wave converter which may be connected to the aerial input terminals of most broadcast sound receivers. It offers reception on the single range of, approximately, 5 to 18 Mc/s (60 to 16.5 metres), and thereby includes most of the more important short wave broadcast stations. Such a range can be adequately covered by a conventional

500pF twin-gang tuning condenser, provided that trimming and stray capacities are kept reasonably low.

A notable difficulty encountered in the design of a short wave converter of the type we are considering here is that of obtaining an efficient r.f. coupling to the subsequent receiver. What is almost certainly the best coupling method consists of injecting the output of the converter into the receiver frequency changer at the a.m. intermediate frequency of the receiver. Unfortunately, however, this involves the provision of switching circuits around the receiver frequency changer stage and, whilst they might be fairly simple to install in an a.m.-only receiver, such switching circuits would be extremely difficult to add to an a.m./f.m. receiver wherein frequency changer wiring is complicated.

Because of the difficulties of coupling up at the a.m. intermediate frequency the short wave converter described here works on a different principle. Its output is fed into the associated receiver's aerial circuit at a frequency lying between 500 and 600 metres (600 to 500 kc/s); that is, at the lower end of the medium wave band. As a result the converter and the sound receiver function together as a double superhet, the short wave converter changing the frequency of the desired signal to one which appears between 500 and 600 kc/s (described in this article as the "first i.f."), and the frequency changer in the receiver converting this to the a.m. i.f., which is normally of the order of 465 kc/s. The main difficulty which follows from this method of operation is that it is possible for existing medium wave transmitters between 500 and 600 kc/s to break through into the "first i.f." circuits and cause heterodyning with any short wave signals which may be received. Fortunately, the lower end of the medium wave band usually appears to be less crowded than the remainder and it should be possible in most instances to find a frequency for the "first i.f." which is free from interference by existing transmitters. Heterodynes caused by short wave stations close in frequency to that required beating with medium wave stations close to the "first i.f." are reduced in the converter by reason of the fact that a relatively highly selective band pass circuit is included between the converter frequency changer anode and its output terminal. In an effort to further reduce heterodynes caused by existing transmitters, the aerial input is switched in the converter itself, coupling between this unit and the receiver being made via screened coaxial cable. In addition, a wave-trap tuned to the "first i.f." is inserted in series with the converter aerial coil. These measures should offer a useful protection against the formation

of heterodynes at the "first i.f." Despite such precautions, nevertheless, some difficulty may still be experienced if the associated receiver employs a ferrite frame aerial for a.m. reception, because an aerial of this type is liable to pick up interfering signals on its own. In consequence, it is advisable to ensure that it is possible to obtain a completely "dead spot" in the 500 to 600 kc/s section of the medium band of a receiver employing a ferrite frame before attempting to use a converter of the type described in this article.

It should be pointed out that, due to the particular design employed, a signal generator is essential for alignment of the completed converter.

**Functioning**

In a simple circuit of this nature it is possible to discuss most of the salient points of layout and practical construction whilst describing the functioning of the individual components.

In Fig. 1, which shows the complete converter, the incoming aerial signal is applied, after switching by  $S_{1(a)}$ , to the wave-trap provided by  $L_1$  and  $C_1$ . This wave-trap is tuned to the frequency in the 500 to 600 kc/s range which has been decided upon for the "first i.f." After  $L_1$ ,  $C_1$  the aerial signal is fed, via the optional condenser  $C_2$ , to the primary of the short wave signal frequency coil  $L_2$ ,  $L_3$ . This coil is tuned by the tuning condenser  $C_5$ , and trimmer  $C_6$ , in normal fashion.

Coil  $L_5$  provides the oscillator tuned circuit in company with the tuning condenser  $C_{12}$  and trimmer  $C_{13}$ , feedback being applied by the coupling winding  $L_6$ . Oscillator padding is provided by  $C_{14}$ . Both  $L_2$ ,  $L_3$  and  $L_5$ ,  $L_6$  may be conventional short wave signal frequency and oscillator coils intended for operation with a subsequent 465 kc/s i.f. amplifier, the only proviso being that  $L_5$ ,  $L_6$  must be a dust-cored component. Such a proviso is necessary because, although the "first i.f."—lying within the range 500 to 600 kc/s—is relatively close to 465 kc/s, some slight adjustment of the oscillator coil inductance may be required for accurate tracking. Preferably,  $L_2$ ,  $L_3$  and  $L_5$ ,  $L_6$  would be matched components from the same manufacturer, in which event a cored oscillator coil would automatically ensure that  $L_2$ ,  $L_3$  was cored as well.

The frequency changer functions in conventional manner, the intermediate frequency appearing at its anode. The conversion conductance of the frequency changer, and hence the overall gain of the converter, is varied by potentiometer  $R_2$ , this adjusting the amount of negative bias applied to  $g_1$  of the valve via  $L_3$ . The slider of  $R_2$  adjusts







10M $\Omega$  resistor. When L<sub>1</sub>, L<sub>4</sub> and L<sub>7</sub> have been adjusted the circuit can then be returned to its correct state.

The alignment of the short wave coils proper then follows. This may be carried out in normal fashion, trimming C<sub>6</sub> and C<sub>13</sub> at the high frequency end of the band, and padding with the aid of the dust cores at the lower end of the band. Final alignment is liable to vary somewhat according to the value chosen for C<sub>2</sub>, should this condenser be fitted. The purpose of C<sub>2</sub> is that of reducing damping of L<sub>3</sub> when a large aerial is used. With most commercially available short wave coils, good results should be given if C<sub>2</sub> has a value around 20pF.

#### Operation

Few difficulties should result in operation of the converter. As with all short-wave

input to the receiver, or to the converter, should be reversed.

#### A.G.C. Operation

If the sound receiver with which the converter is to be used has a mains transformer and a chassis which is isolated from the mains supply it becomes possible to bond the receiver and converter chassis together. An a.g.c. voltage from the receiver may then be applied to the converter frequency changer, and the gain control circuit deleted.

The a.g.c. circuit is illustrated in Fig. 2. As will be noted, R<sub>2</sub>, R<sub>6</sub>, C<sub>8</sub> and W<sub>1</sub> of Fig. 1 are not now needed, a.g.c. from the receiver being applied via R<sub>9</sub> and R<sub>8</sub>. R<sub>9</sub> must be fitted close to the a.g.c. diode load in the receiver.

When the sound receiver has an isolated chassis it may also be possible to derive h.t. and heater supplies for the converter from its power unit, thereby obviating the necessity

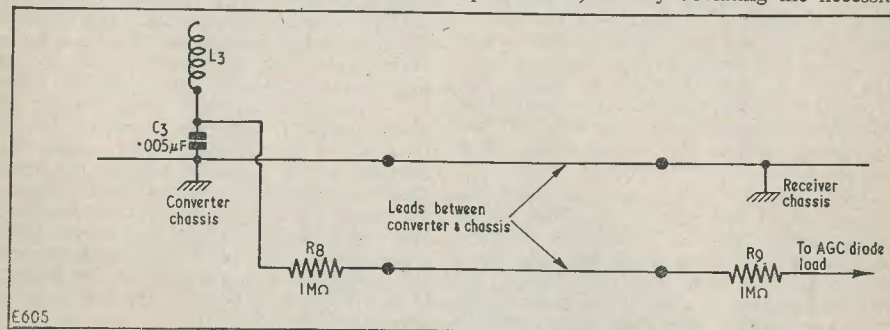


Fig. 2. Applying a.g.c. to the converter

equipment, careful tuning is necessary, and it is essential that the tuning condenser be fitted with a good slow motion drive which is free from backlash.

Some slight difficulty may be given by mains modulation. If this occurs, the mains

of the mains transformer and h.t. rectifier circuits shown in Fig. 1.

The circuit of Fig. 2, and any common power supply arrangements, must not be used if the associated sound receiver has a "live" chassis.

## The "PRODIGY" and STEREO


Many readers of the last two issues will be wondering if it is worth while proceeding with construction of the "Prodigy" in view of the fact that in the near future they may wish to go in for stereo reproduction. The answer is definitely, yes!

Indeed, at this time work is proceeding on the development of a stereo version. It is anticipated that this version will be made available early in 1959. At this time, also, a conversion kit will have been produced to enable readers who have already built the single-channel "Prodigy" to adapt it for stereo. This conversion will, briefly, consist of a separate control unit and an add-on unit

which will provide the second channel output stage. Part of the existing chassis and practically all the components, including the control panel, will be utilised in the conversion, and in appearance the converted "Prodigy" will be only slightly less pleasing than the actual stereo version, while the performance will be identical.

It is hoped that this advance notice will enable readers who, because of financial or other considerations, cannot yet undertake to construct a stereo amplifier, to enjoy meanwhile the undoubted quality of performance given by the single-channel "Prodigy."

# In your Workshop

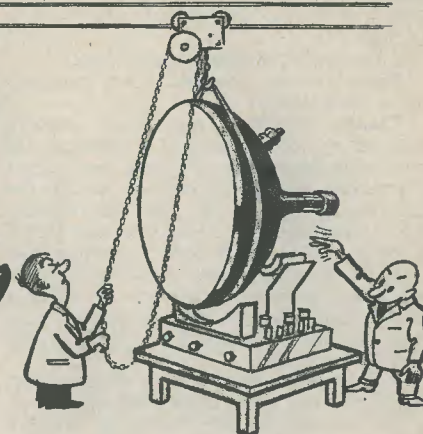

Aided by his able assistant, Dick, Smithy the Serviceman continues to run the Workshop

THERE WAS A LOUD, SUDDEN EXPLOSION, and the startled Dick jumped backwards from the smoking receiver on the bench in front of him. Involuntarily he held on to his soldering iron, whereupon its consequently tightened lead swept across the bench and caused all the components in its way to be pushed on to the floor. There was a heavy crash as several chokes and transformers bit the linoleum, this being accompanied by the rattle and tinkle of sundry resistors and condensers. There were also three distinct and separate implosions, these marking the demise of as many perfectly good valves. Dick's instinctive move backwards caused the soldering iron lead to become strained even further beyond its normal tension; with the result that, firstly, its hot barrel was pulled between his thumb and forefinger and, secondly, the leads at the plug began to pull away from their anchorage. As soon as Dick felt the heat of the soldering iron barrel he threw it away from him with a violent yell, whereupon it crashed to the floor and commenced to burn a hole in the linoleum. At the same time the bare ends of the wires pulling from the soldering iron plug had untwisted sufficiently from their terminals to touch together. There was a bright flash, and all the lights in the Workshop became extinguished. Shocked by the events which had so suddenly overtaken him, Dick stumbled clumsily across the darkened Workshop towards the cold water tap at the

sink, knocking over on the way his stool, the Workshop teapot and a cup and saucer. He finally reached the sink, whereupon he turned on the cold tap and held his injured thumb and forefinger beneath it.

In the gloom of the December afternoon, the long-suffering Smithy turned round and stared quietly at the wreckage which was strewn around him. He heaved a long drawn-out sigh. For once he had no comment to make.

After some moments the Serviceman came to grips with the situation. His eyes becoming accustomed to the wintry light filtering through the windows, he looked at his assistant at the sink and saw that he looked somewhat pale. Smithy forgot the damage and assumed the role of ministering angel.

"Here," he said to Dick. "I can't see that cold water serving any particularly useful purpose apart, perhaps, from cleaning dirt away from your burns. You'd better sit down for a moment and I'll have a look at them."

Dick sat down obediently and Smithy quickly examined the burnt thumb and finger. Then he walked over to the first aid box.

"They're not so bad," he remarked. "In fact they're quite mild—just a reddening of the skin, that's all. What we want to do, therefore, is to put a spot of something nice and soothing on to them. First of all, I'll gently dab off the water you ran over your hand with this bit of cotton wool. Then I'll



smear some Acriflavine cream over the red-dened parts of the skin. After that I apply two pieces of lint, one to the forefinger and one to the thumb, and hold them in place with a bandage."

Smithy busied himself with his task.

"There you are," he said a few moments later. "Job done!"

"Thanks, Smithy," said Dick, making ready to rise from the seat. "Perhaps I'd better start clearing up the mess I've made."

"I should stay just where you are for the time being," chuckled the Serviceman. "After all is said and done, you *have* had a bit of a shock. And there's nothing like taking it easy for a minute or two after shock even when, as in your case, it's of rather a minor nature. Besides, the way you are now you'd probably start knocking everything all over the place again!"

Following the Serviceman's instructions, Dick sat silently in his chair watching Smithy as the Serviceman first took the still-hot soldering iron off the floor and, secondly, set about repairing the fuses. After a minute the Workshop was cheerfully lit up again.

"How're the burns?" asked Smithy, sitting down and lighting a cigarette.

"Not too bad," replied Dick, "although they're still hurting quite a bit."

"Not to worry," commented Smithy, soothingly, "they'll probably burn and irritate for an hour or two, but the pain should pass off after that. Do you feel ready to start clearing up the debris?"

"Sure," said Dick, "let's get at it."

#### The Cause

"Well, Dick," said Smithy, after he had helped his assistant to return the components on the floor back to the bench, and had tut-tutted over the three broken valves, "we'll examine these bits and pieces later on. For the time being let's have a look-see at what started all this off."

A somewhat chastened Dick indicated the television chassis which had caused all the trouble.

"Ah," commented Smithy, peering closely at the receiver, "I see we have an open-and-shut case of blown-up electrolytic. Exploding electrolytics are by no means so common nowadays as they used to be when they were housed in cardboard containers. In fact, this is the first I've encountered for quite a few years. At any rate, the electrolytic we have here hasn't caused much damage in the receiver, despite the fact that it gave such an almighty pop. As an amateur student of ballistics I can see that it was aimed away from the chassis and the other components.

"Now the first thing to note," continued Smithy, "is that it is the 100+200 $\mu$ F h.t. electrolytic which has gone up. The question

we must now ask ourselves is, why?"

The Serviceman turned an enquiring glance on his assistant.

"Well," volunteered Dick, "the history of this set is that it came in with low e.h.t. and low line scan. Before doing anything else I checked the h.t. potential, whereupon I found that this was down to about 150 volts or so. I decided to suspect the h.t. metal rectifier."

"A good diagnosis," said Smithy approvingly.

"The next thing I did," Dick carried on, "was to hunt around for a replacement rectifier. We seem to be running low on these, however, and all I could find was a rectifier at the back of the spares cupboard which looked as though it had already been used once or twice for checking circuits or something of that order. At any rate the varnish on it looked nice and new but there was evidence that leads had at some time been soldered to its tags."

"That doesn't sound too good," said Smithy. "I like to give my customers brand-new spares, if possible. Still, I *do* vaguely remember using a metal rectifier many moons ago for an hour or so for some test or another, so I'll let this pass."

"The only trouble," continued Dick, warming up to his story, "was that the red mark had got rubbed off the positive tag of the rectifier I found. So, before I connected it into the receiver, I checked its polarity."

Smithy looked interested.

"How did you do that?" he asked quickly.

"By using the testmeter on an ohms range," replied Dick with evident surprise at the sharpness of Smithy's question. "What I did was to pop the positive lead of the meter on to one end of the rectifier and the negative lead on to the other end. The meter indicated a very high resistance and so I presumed that the end to which the positive meter lead was connected was the negative end of the rectifier."

"After which you connected it into circuit?"

"That's right."

"How often have you used this particular check for h.t. rectifier polarity in the past?"

"Only twice before, and it worked O.K. then."

Smithy raised his eyes to the ceiling. "One can only thank the fates," he remarked devoutly, "for having previously spared us from today's catastrophes, which have undoubtedly been caused by your connecting up the rectifier wrong way round. However, Dick, I must confess I really blame myself for not having previously told you how to check h.t. rectifier polarity. Let me just say for the present that the test you've described is of no use at all.

"To begin with, I think you're making an

untrustworthy assumption when you suppose that the polarity markings on a testmeter's terminals bear any fixed relationship to the voltage which appears at those terminals when the meter is switched to an ohms range. One couldn't be certain about such a point until one had checked the meter's circuit or had connected another meter, switched to volts, across its terminals. There may, perhaps, be a convention amongst meter manufacturers on the question of ohmmeter terminal polarity, but I haven't heard of it myself.

"So I feel that you first made an error with your assumption of meter polarity. Your second error was much more naughty. You didn't reverse the meter leads to see whether the rectifier conducted when connected the other way round."

"Why?"

"Apart from the fact that a double check is always worth carrying out if it can be done quickly," said Smithy, "it would have demonstrated that the rectifier had just as high a resistance when connected the other way round as it had in the first case!"

"Hey?"

"That's right! Germanium diodes and other low voltage rectifiers would have shown different resistances, but such things as h.t. metal rectifiers would give you almost the same reading either way."

"Why is that, Smithy?"

"Because the forward resistance of h.t. metal rectifiers is very high at low voltages. The rectifier is able to work at high voltages because its forward resistance decreases as the voltage increases. As a matter of interest it is because of the non-linear resistance characteristic of metal rectifiers that you can use them for such jobs as expanding meter scales and so on. Thus, if you slap a rectifier of the right type across a meter (Fig. 1) that rectifier can cause the range of available readings to be considerably increased. When low voltages appear across the meter the rectifier offers a relatively high resistance and the meter sensitivity is high. When the voltage across the meter rises the rectifier resistance drops and the meter gets progressively less sensitive. The rectifier enables the meter to read quite high voltages whilst still being capable of measuring low voltages accurately. The result is that you get a meter scale something like this (Fig. 2).

"However, we're getting away from the point, which is concerned with detection of polarity of h.t. metal rectifiers when their markings are rubbed off. So far as I'm concerned there is only one simple foolproof method of doing this, and that consists of connecting up the rectifier in series with an a.c. supply whose voltage is the same as that it will eventually handle. Connect a moving-

coil testmeter switched to a suitable voltage range to the other side of the a.c. supply and the remaining lug of the rectifier, and you

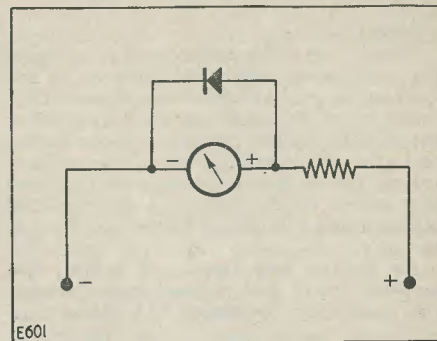


Fig. 1. The effective scale of a voltmeter may be expanded by connecting a suitable metal rectifier to it in the manner shown here. The forward resistance of the rectifier decreases as the voltage across it rises

will get a definite indication of polarity. (Fig. 3.) This method is so fool-proof that I feel it should be used even if an appreciable amount of time has to be spent in carrying it out. In actual fact the test takes only a few seconds. Most of the metal rectifiers we work with are intended to operate from mains voltages, whereupon it is usually necessary to make only two quick connections, and these can be done with crocodile-clip leads.

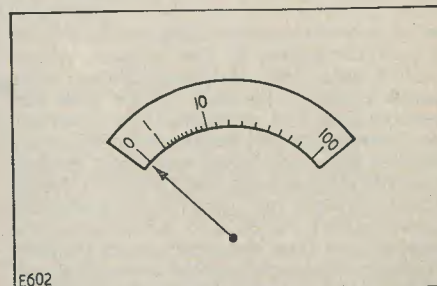


Fig. 2. A typical instance of an expanded scale, as would be given by the circuit of Fig. 1

"And, my boy, it is only *after* a check of that type," concluded Smithy, surveying the battered components now lying on Dick's bench, "that you should start wiring in your smoothing and reservoir electrolytics."



Dick looked at his bandaged hand. "O.K. Smithy," he said. "I've been taught something today. And I've certainly learned it the hard way!"

#### Clearing Up

Smithy and Dick commenced to examine the components which had fallen on to the floor earlier on. As very often happens, what appeared at first sight to be damage of a considerable nature turned out to be not so bad after all. Apart from the three defunct valves, few of the components had suffered any injury which could not be corrected mechanically with the judicious use of a pair of pliers.

As Smithy had mentioned earlier, the receiver chassis had suffered little damage: the electrolytic condenser had blown out-

"There you are, Smithy," he exclaimed triumphantly. "Things aren't so bad after all."

"I suppose not," said Smithy guardedly, "but I have to remind you of the matter of the heavy costs you have incurred this morning. To wit: a needlessly burnt-out double electrolytic and rectifier, three good valves, and at least six inches of fuse wire. To say nothing of wear and tear on my ageing nerves."

"Honestly, Smithy, I'm sorry about the damage," said Dick contritely. "You'll have to dock it from my lolly next Friday!"

"No, I shan't do that," replied Smithy. "I don't think the overheads will totter too much under the strain."

Dick grinned, having expected this answer. He next pulled the aerial plug out of the

socket and the tuner is capable of picking up the locally generated corona. I have a more sensitive 'local' aerial when I put the test prod in the aerial socket, and that is why the flashing on the screen increases in intensity when I do this. I think I'll have a sniff around."

Smithy carefully examined the e.h.t. components and wiring in the receiver.

"I can't see any very obvious corona," he remarked eventually, "which leads me to suspect the line output transformer or deflection yoke. Sometimes, one gets poor internal connections in line output transformers or deflection yokes, these sparking, especially during current pulses, and giving flashes on the screen which are rather similar to those given by corona. Ah, wait a moment, though!"

Smithy's eye had fallen on the final anode connector of the cathode ray tube.

"I think I can see a thin bluish haze here," said Smithy. "So before we start suspecting major components I am going to do a little elementary cleaning up."

Smithy switched off the receiver, discharged the e.h.t. terminal to chassis and pulled out the connector. The soldering of the polythene e.h.t. lead to this connector seemed satisfactory, with no stray strands of wire which could cause "spikes" and consequent corona. The Serviceman next picked a rag off the bench, applied it to the tube bulb around the connector and, with a wry expression, showed Dick the black greasy deposit he had cleaned from the glass. Smithy proceeded to clean the glass carefully with carbon tetrachloride, after which he applied some grease from a small tube. He

then replaced the connector and switched on the receiver.

The flashes on the screen had cleared. "There you are," said Smithy. "Just an instance where common-or-garden muck and nothing else causes trouble."

"You've certainly cleared the corona," remarked Dick. "What's in that little tube?"

"Oh, that's MS4," replied Smithy. "It's a silicone grease made by Midland Silicones Ltd. especially for electrical purposes. It's excellent for keeping moisture off things and for stopping tracking. In fact, any surface coated with MS4 becomes actually water-repellent. It's also a lubricant and contact grease; and one well-known firm of turret tuner manufacturers specifies it for their turret contacts. Further, like all silicone compounds it is a very stable material; it doesn't change its consistency due to long-term oxidation, nor does it melt. I certainly wouldn't be without a tube in this Workshop."

"That's all very well," said Dick, examining the small yellow-labelled tube. "But, very often, products of this nature are available to people in the trade only. Can amateurs buy this?"

"Certainly," said Smithy. "Any amateur can buy it. Perhaps the easiest way is by post from distributors."\*

"Fair enough," said Dick. "I'm always doing a few odd jobs at home. I'll get some in for my own private use."

"As you like," said Smithy. "But I think I should back it up with plenty of Acriflavine cream!"

\*MS4 is available to amateurs from Holiday and Hemminger Ltd., 71 Ardwick Green North, Manchester 12.

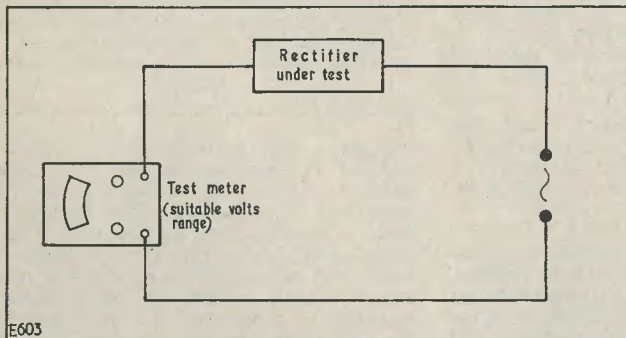


Fig. 3. A fool-proof method of determining the polarity of an h.t. metal rectifier. The a.c. voltage used for the test is of the same order as that which would be applied to the rectifier under working conditions

wards into clear space. Dick hopefully fitted a new component in this position, whilst Smithy unearthed a new rectifier from some secret cache of his own. Dick took this rectifier from him, examined it very carefully and, despite the fact that its positive lug was marked with very bright red paint, checked it in the manner suggested by Smithy before finally wiring it into the chassis. Somewhat apprehensively, Dick next switched on the receiver, but there were no signs of incipient eruption. Instead, to Dick's surprise and pleasure, the sound came up after the usual initial warming up period. A little later, the line output transformer commenced to sing its familiar 10,125 c/s song, and a nice bright picture appeared very shortly after. The set checked satisfactorily on both the local channels, and the h.t. line read a healthy 210 volts (this being some 10 volts or so in excess of what would be given when the new rectifier had "settled in"). Dick beamed. Even his burnt finger and thumb had stopped aching.

socket on the chassis he had been handling, preparatory to switching it off and returning it to its cabinet. His cheerful expression changed to one of exasperation when he saw that what had previously been a perfect picture suddenly changed to a mass of small bright flashes.

"Oh, no," he groaned loudly. "Don't say that something else has gone wrong with this blamed set."

Smithy wandered over and looked at the receiver. Experimentally, he picked up one of the test prods of the bench testmeter and applied it to the centre conductor of the aerial socket. The white flashes became much more prominent.

"We have corona," pronounced the Serviceman. "And I would say with certainty that it's coming from an e.h.t. component inside the set. When the aerial is disconnected the a.g.c. circuit causes the receiver to work at full sensitivity, whereupon the wire inside the cabinet between the aerial

## Catalogues Received

AVO Ltd., Avocet House, 92-96 Vauxhall Bridge Road, London, S.W.1, have forwarded their latest Instrument Catalogue which is available to readers post free on request. Attractively produced on heavy art paper, it comprises some 38 printed pages, plus cover. All the current range of test instruments is fully described, each item being featured on two facing pages and each including an illustration of the instrument complete with descriptive text and the full technical specification.

The completely new A.M. Signal Generator, type 378, is one example, this instrument covering from 2 to 225 Mc/s on fundamentals in 7 ranges with adequate overlap and from 160 to 450 Mc/s on the harmonic range. The range details are: Range A from 2 to 4.5 Mc/s; B from 4 to 9 Mc/s; C from 7.5 to 16 Mc/s; D from 11 to 24 Mc/s; E from 22 to 50 Mc/s; F from 45 to 100 Mc/s and G from 80 to 225 Mc/s. The harmonic range 2G is thus the second harmonic of range G.

Another new product, featured for the first time, is the AVO "Proclips." These patented spring-loaded test prods are invaluable for reaching those test points difficult of access, with which we all have to contend at some time or another.

Home Radio (Mitcham) Ltd., 187 London Road, Mitcham, Surrey, have just produced one of the finest retail catalogues that we have recently seen. Of 100 pages, literally packed with over 4,000 items, it is available to readers at 2s. (1s. 6d. plus 6d. postage). Completely indexed and cross referenced, there is also a handy section finder card which greatly assists in the location of any item required.

In all the vast range of items listed, we can think of nothing that has been omitted—everything from nuts and screws to complete hi-fi equipments are featured. Well illustrated both with line drawings and photogravure, we recommend this complete catalogue to all our readers.



# UNDERSTANDING TELEVISION

PART 12

By W. G. MORLEY

The twelfth in a series of articles, which, starting from first principles, describes the basic theory and practice of television

HAVING COMPLETED OUR EXAMINATION OF the aerial input and signal frequency amplifier stages of the television tuner unit, we may now carry on to the oscillator and mixer.

The mixer carries out the function of converting the signal frequency to the intermediate frequency, so that amplification by the i.f. stages of the receiver may take place. Following normal superhet practice, this conversion occurs due to the injection into the mixer of an oscillator voltage, the oscillator frequency being spaced away from the signal frequency by the intermediate frequency. We shall now devote our attention to the oscillator circuit.

## The Oscillator

It is conventional practice in modern tuners to employ a combined triode pentode as oscillator-mixer valve, the triode section functioning as the oscillator. The oscillator circuit universally employed for television tuners has the basic form illustrated in Fig. 68 (a). In Fig. 68 (b) the inter-electrode capacities of the triode are added to the circuit, whereupon it may be seen that the oscillator is, in reality, of the Colpitts type. The inductance in the tuned circuit is provided by the oscillator coil itself, whilst the capacity tuning this inductance is given by  $C_{ag}$  connected directly across the coil, and by  $C_{ak}$  and  $C_{gk}$  in series. (It is assumed that

the series grid condenser has a value which is sufficiently high for it to be ignored when compared with the low values of the inter-electrode capacities.) The earth tap into the tuned circuit is made at the junction of  $C_{ak}$  and  $C_{gk}$ , with the result that, at the resonant frequency, the voltages at anode and grid are  $180^\circ$  out of phase, and oscillation occurs. A grid leak is included in Figs. 68 (a) and 68 (b) and this, together with the series grid condenser, ensures that the valve is biased in conventional leaky-grid manner. The anode feed resistor allows positive h.t. potential to be available for the anode of the valve. At the frequencies involved in television tuner oscillators the impedance of the anode feed resistor is sufficiently high to prevent excessive damping of the oscillator tuned circuit. This point is, however, dealt with in greater detail later.

Whilst the circuit of Fig. 68 (a) is perfectly capable of oscillating as it stands, it requires a number of modifications if it is to work at optimum efficiency in a practical tuner. One of the first points which requires consideration is the position of the earth tap into the tuned circuit. For best results the amount of voltage fed back to the grid of an oscillator should be less than that appearing at the anode. In most practical instances the grid voltage should be one-third to one-quarter that given at the anode. The ratio between anode and grid voltages may be altered in

Figs. 68 (a) and 68 (b) by varying the effective position of the earth tap into the tuned circuit, the simplest method of doing this consisting of adding an additional condenser between the grid end of the coil and chassis. The parallel combination of this additional condenser and  $C_{gk}$  provides a lower reactance than is given by  $C_{ak}$  on its own, with the result that the earth tap into the tuned circuit is brought closer to the grid end of the coil and the grid voltage becomes lower in relation to the anode voltage. By choosing the correct value for the additional condenser the ratio of grid voltage to anode voltage may be made equal to that which provides optimum efficiency. Fig. 68 (c) shows the oscillator circuit with the added condenser.

In Figs. 68 (a), (b) and (c), the series anode feed resistor is shown as being connected to the anode end of the coil. In practical tuner units, however, it is almost always connected to the grid end. There are two reasons for this. The first of these is that, as we have already seen, there is less oscillatory voltage at the grid than at the anode. In consequence, any damping resulting from the presence of the resistor will have less effect on the overall tuned circuit if the resistor is connected to the grid end instead of to the anode end of the coil. Secondly, if the oscillator circuit is used in a turret tuner, connecting the resistor to the grid end of the coil will ensure that the h.t. supply to the oscillator anode is broken if no coil happens to be presented to the turret contacts. Such a condition would occur when switching from one channel to the next, or if the tuner is inadvertently left in a position for which no coil segment has been fitted. Should an h.t. feed be maintained to the valve with no oscillator coil in circuit its grid bias would fall to zero volts and excessive anode current could flow. Fig. 68 (d) shows the anode feed resistor in its new position.

Finally, it becomes necessary to fit a fine tuner and, possibly, a trimmer to the oscillator circuit. The necessity for having a fine tuner is that it is difficult to ensure that the oscillator circuit will remain exactly on tune over long periods of time. A panel control, capable of offering small adjustments in oscillator frequency, overcomes this difficulty. At the same time, trimmers are employed, on most turret tuners, to ensure that production chassis may all present the same tuning capacity to the oscillator coils. Both fine tuners and trimmers consist usually of variable condensers, whereupon they may be connected between chassis and either end of the oscillator coil. Fig. 68 (e) illustrates a fine tuner and trimmer connected in parallel between the anode of the oscillator and chassis. This diagram also gives component values typical of those encountered in current

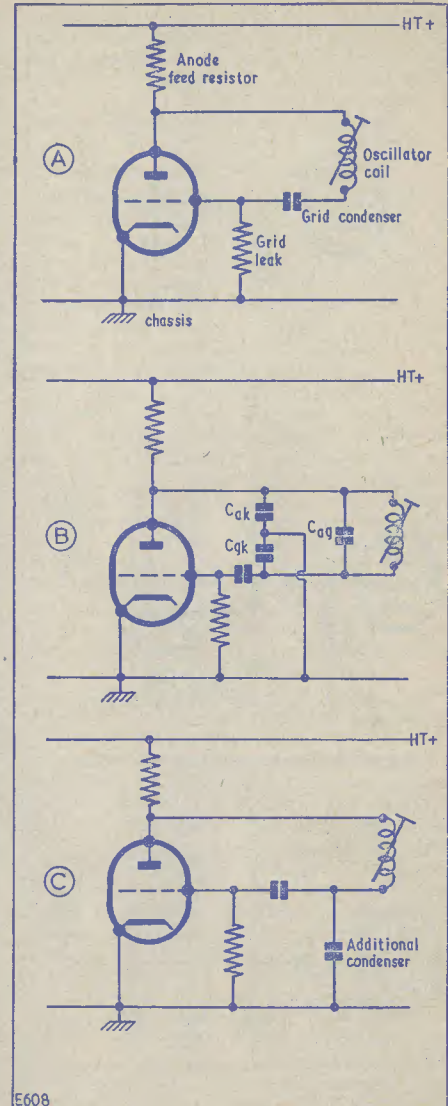


Fig. 68. Successive steps in the development of a practical tuner oscillator circuit. (a) The fundamental oscillator circuit. (b) When inter-electrode capacities are shown it may be seen that the oscillator circuit is a Colpitts. (c) In order to provide an earthy tap into the tuned circuit which provides optimum oscillator efficiency, an additional condenser is connected across  $C_{gk}$ .



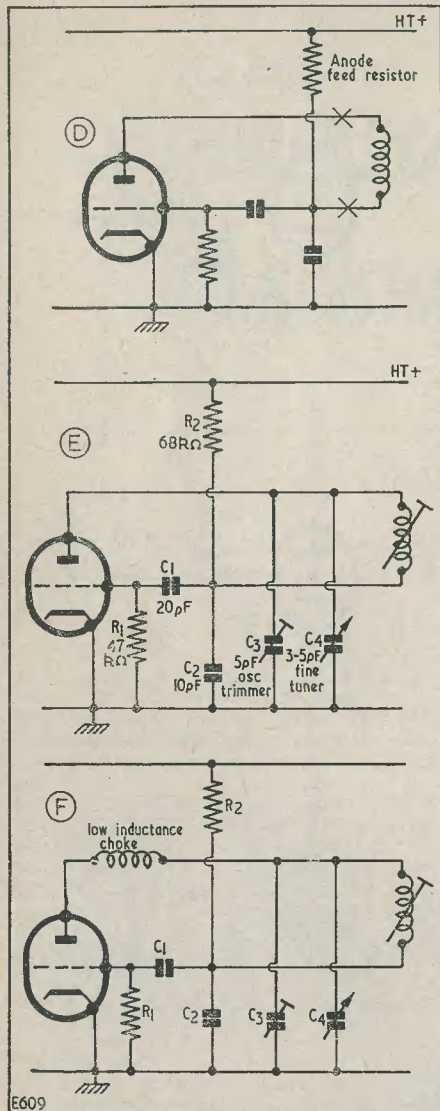


Fig. 68 (d) Connecting the anode feed resistor to the grid end of the coil reduces damping. In turret tuners it also ensures that the h.t. supply to the oscillator is broken when no coil is in circuit. The crosses indicate the points at which turret contacts would appear in the circuit. (e) Adding a fine tuner and a trimmer brings the basic circuit of (a) into line with typical manufacturing practice. This

tuners. It should be mentioned that the addition of a fine tuner and trimmer causes a shift in the position of the earth tap into the tuned circuit. In practical tuners, the value of  $C_2$  is chosen to give optimum oscillator efficiency when the fine tuner and trimmer are set to their mid-capacity positions.

Whilst the circuit of Fig. 68 (e) is typical of most modern tuners, some units may incorporate a small choke inserted into circuit in the manner shown in Fig. 68 (f). The choke has a low inductance and consists of a few turns of wire only. The reason for the addition of this component is as follows. In Fig. 68 (e) the fine tuner is liable to give increasing shifts in oscillator frequency as the latter increases (due to the selection of higher channels). This is because the capacitive range of the tuner remains unaltered despite the fact that the oscillator inductance decreases. In consequence, whilst the fine tuner may be capable of offering only a small shift in oscillator frequency at low Band 1 channels it may be capable of offering a disproportionately large shift at Band 3 channels. The circuit of Fig. 68 (f) causes this effect to be partly compensated. At Band 1 frequencies the inductance of the choke is very small when compared with that of the oscillator coil, and the range of the fine tuner is very nearly the same as would be given if the choke were omitted. At higher Band 3 frequencies the inductance of the choke becomes comparable with that of the oscillator coil and it contributes a significant amount of the inductance in the oscillator tuned circuit. As a result, the fine tuner is now connected across a smaller portion of the oscillator tuned circuit and its frequency range is reduced, becoming comparable with that provided at the lower Band 1 channels.

When the circuit of Fig. 68 (e) is used the fine tuner range provided in most British tuners is normally of the order of 1 to 3 Mc/s at Band 1, and of 2 to 6 Mc/s at Band 3. When the circuit of Fig. 68 (f) is used the fine tuner frequency range is of the order of  $1\frac{1}{2}$  to 3 Mc/s on all channels.

#### Oscillator Drift

Since it is the oscillator frequency which, by beating with the signal frequency, causes the latter to be selected and applied to the i.f. amplifier of the receiver, it is of the utmost

importance to ensure that the oscillator frequency does not drift due to temperature rises in the tuner unit after the associated receiver has been switched on. Such rises in temperature are largely the result of heat dissipation by turret valves and components, the former usually providing by far the greater amount of heat. So far as components are concerned, that which dissipates most heat is the oscillator feed resistor. A further cause of tuner unit temperature rise is heat dissipation from other components inside the receiver cabinet, these affecting the tuner either by convection currents or by direct radiation. In a well-designed receiver this latter effect is kept to a minimum by mounting the tuner at a relatively cool part of the chassis.

Oscillator frequency drift results from temperature rises because these cause dimensional changes in coils and condensers, and in the inter-electrode capacities of the oscillator valve itself. Also, the dielectric constants of condensers may be altered. In practice, the effect of temperature rise on tuner oscillator circuits is somewhat complex, firstly because alterations in oscillator frequency given by changes in individual components may be in opposite directions and, secondly, because there is a time factor which causes some components to be affected more rapidly than others. At the instant of switching on the receiver in which the tuner is fitted, it may be assumed that all components in the tuner are at room temperature. The oscillator valve then begins to warm up, and after cathode emission commences, to dissipate h.t. power in the form of heat. There is, in consequence, a rapid increase in valve temperature over the first 15 to 30 minutes, after which it begins to stabilise at a relatively fixed temperature. The rapid increase in valve temperature causes changes not only in its own inter-electrode capacities, but also in the valveholder insulating material and in the components soldered directly to the valveholder tags. The remaining parts of the circuit rise in temperature more slowly (although there may be a quicker rise of temperature in components soldered directly to the anode h.t. feed resistor) and they do not reach a stable temperature until a longer time (normally one or two hours) has elapsed. Because of this, the effects of temperature rise in the oscillator stage of a television tuner can be described as being two-fold. There is firstly the "short-term" rise caused by the relatively abrupt temperature rise of the valve, and there is the "long-term" rise wherein all the components on the chassis gradually rise to a stable temperature.

Whilst good tuner design is always aimed at keeping oscillator components reasonably cool, the only practicable method of prevent-

ing oscillator drift due to temperature rise in commercially priced units consists of fitting components which compensate for the rise. The drift-compensating components which are employed in practice are condensers having special *temperature coefficients*.

#### Temperature Coefficient Condensers

All condensers exhibit a change in capacity when their temperatures are increased, this being caused, as we have already noted, by dimensional changes and, in some cases, by changes of dielectric constants. Changes in capacity become of considerable importance when condensers are employed in tuned circuits, as such changes will obviously cause changes in resonant frequencies.

In order to obtain a measure of the changes in value of fixed condensers of the types which are employed in tuned circuits, the term "temperature coefficient" is employed. The temperature coefficient of a condenser defines the change in its capacity for a given rise in temperature, and is expressed in parts per million change for a rise in temperature of  $1^\circ\text{C}$ . (A worked example is given later.) If, with a rise in temperature, the capacity increases, the condenser is stated to have a *positive temperature coefficient* and the coefficient figure is preceded by the letter P. If the capacity decreases with rise in temperature the condenser is stated to have a *negative temperature coefficient* and the coefficient figure is preceded by the letter N.

In turret tuners the type of fixed condenser universally employed for tuned circuits employs a ceramic dielectric. It has been found that different types of ceramic cause the condensers in which they are used to have different temperature coefficients; whereupon a condenser can be given a previously determined temperature coefficient by the simple process of employing the requisite ceramic during its manufacture. The normally-available range of temperature coefficients currently used by tuner manufacturers is as follows: P100, NP0, N030, N080, N150, N220, N330, N470, N750, N1500.<sup>1</sup> For economic reasons the cheapest of these condensers are N750 and P100, and condensers to intermediate coefficients are usually found only in positions (such as tuner oscillator stages) where temperature coefficients are most critical.

Before proceeding further, it might prove helpful to give a numerical example of the manner in which the temperature coefficient defines capacity change with relation to rise in temperature. As has just been stated, temperature coefficient defines the change in

<sup>1</sup> An NPO condenser is one whose capacity remains (within tolerances) unaltered by temperature rise. N1500 condensers are used for drift compensation very infrequently.



capacity expressed in parts per million per degree rise Centigrade. Let us assume that we have a condenser which, at a room temperature of 20°C, has a capacity of 100pF. The condenser has a temperature coefficient of P100, and, in service, its temperature increases to 70°C, this representing a rise of 50°C. What is its capacity at the elevated temperature?

Since the temperature coefficient is P100 the increase in capacity will be 100 divided by 1,000,000 and multiplied by 100 (the value, in pF, of the condenser) and by 50 (the number of degrees Centigrade rise). That is:—

$$\frac{100}{1,000,000} \times 100 \times 50 \text{pF,}$$

which is equal to 0.5pF.

The new value of the condenser at 70°C will, therefore, be 100.5pF.

Such an increase in capacity may appear small but, in practice, it could completely

upset the working of a turret tuner oscillator.<sup>2</sup>

In practical tuner units the condensers employed in the oscillator tuned circuits have selected temperature coefficients which enable them to compensate for frequency drifts caused by other components. In order to compensate for "short-term" and "long-term" drifts temperature compensating condensers may be soldered direct to valveholder tags or wired-in some distance away. Most manufacturers aim at a frequency drift which is less than some 50 kc/s at Band 3 frequencies.

#### Next Month

It is hoped, next month, to conclude our discussion of the tuner unit by a consideration of the mixer and its test points, together with alignment by the aid of a wobulator.

<sup>2</sup> All else remaining constant, a change of 0.5 of 1% in the tuning capacity of a tuner oscillator would result in a frequency shift of 300 kc/s in 200 Mc/s, a quite unacceptable figure.

## Can Anyone Help?

Requests for information are inserted in this section free of charge, subject to space being available

**ZA.11324 U.H.F. Receiver Special Mk. 3.**—J. Edghill, 3 Albacore Crescent, Lewisham, London, S.E.13, needs information on this receiver, and will be willing to pay for any expenses involved.

**R.1155 and T.1154.**—S. McCrorie, 23 Newcastle Gardens, Whitleigh, Plymouth, Devon, wishes to obtain a circuit diagram for a power pack for the above.

**Philips Type 186A-IS 6-Valve Receiver.**—C. Davies, 102 Buckingham Road, Bicester, Oxon, would like to borrow or preferably buy the circuit diagram with component values, and also if possible modification data for reception of 50–200m. Valve line-up ECH35, two EF39, EBL31, AZ31, EM34

**German Communications Receiver R3.**—H. G. Odd, Verona, Harrow Lane, Knockholt, Sevenoaks, Kent, asks if anyone can supply information on this receiver. Three wavebands cover 2.5 to 6.8 Mc/s, 6.7 to 14.7 Mc/s, 14.7 to 25.7 Mc/s; valve line-up: EF13, ECH11, EF12, EBC11, EDD11, EBC11 BFO, EZ11. Any expenses gladly refunded.

**Pye P.C.R. 2 Receiver.**—R. J. Derk, Bankers Farm, Bucks Cross, Bideford, Devon, would like any details, circuit diagram, power supplies, etc.; also information on the Admiralty Amplifier Type N.24. Willing to pay, or would exchange real Devonshire Cream.

**Admiralty Receiver Type B.46.**—H. Knowles, 12 Fairview Road, Denton, near Manchester, offers to pay any fair price for either circuit details or handbook; would also like to correspond with anyone who has used or modified this receiver.

**P.C.R.2 and R.208 Receivers.**—J. Brookes, 1 Dean Street, Blackpool S.S., Lancs., wishes to obtain information on fitting "S" meters to these receivers. Any expenses refunded.

**Series 920 Valve and Set Tester.**—C. T. King, 13 Monks Brook Close, Eastleigh, Hants, wishes to borrow, buy or be advised where to obtain an instruction book or manual for this instrument, manufactured by the American firm Precision Apparatus Co., Elmhurst, Long Island, New York.

**Sobell TV Receiver T.89.**—A. E. Franklin, 12 Queensland Crescent, Chelmsford, Essex, wishes to obtain, and will gladly purchase, the circuit of this television.

**Ekco C.R.6.1. Car Radio.**—P. Broom, Burn Rew Farm, Willand, Cullompton, Devon, wishes to purchase a service sheet.

**British Blue Spot Model AC/5.**—G. H. Hamilton, 30 Wishmoor Road, Camberley, Surrey, is willing to buy or borrow service sheets (circuitry and alignment data) on this pre-war receiver, the line-up of which is FC4, VP4A, TDD4, PEN.A4 and IW3.

**High-Gain Band 3 Pre-Amp (Radio Constructor).**—V. Jeremy, 21 Incline Top, Penyard, Merthyr Tydfil, Glam., would like suggestions for modification of this unit where diplexer is on masthead and only one downlead is available—this attenuates B.B.C. almost to zero at present. Successful and inexpensive mods gladly paid for.

**RF24 Unit and LU.51.**—P. Burbidge, Park View Hostel, Abbey Road, Gt. Malvern, Worcs., would like to borrow or buy manuals for these and would like to know if anyone has successfully modified the R.F.24.

## POCKET TRANSISTOR TESTER

### A Simple


By W. E. GRIFFITHS

DU TO THE LARGE SPREAD OF CURRENT gain in transistors, the writer has found a need for a very simple pocketable transistor current gain tester. The simple unit described here enables transistors to be tested for current gain in the earthed emitter connection (i.e.  $\beta$  or  $\alpha'$ ), and also indicates when  $I_{co}$  (i.e. leakage current) is excessive. The advantage of being able to make these tests at the time of purchase of the transistor is obvious.

This tester is only intended to be used as an approximate estimate of the "goodness" of a transistor where  $I_{co}$  is not considered too important unless excessive. With this in mind, the bias was arranged to operate the transistor at a collector current of 1mA for a current gain of 30, so that in most cases

outside for connection to the transistor.

The scale is calibrated 0–150 and marked  $\beta$  or  $\alpha'$ . To test for current gain, the transistor connections need not be screwed into the terminal block but may simply be held on by holding the leads in position, taking care not to hold the body of the transistor as this will cause the reading to rise due to temperature increase. To read  $I_{co}$ , the collector and emitter leads only are connected and the reading noted. This should not be more than around 5 on the 0–150 scale (i.e. less than 200 $\mu$ A) and very often can be neglected. If the reading is *not* negligible, then after the base connection has been made and  $\beta$  read, the reading obtained for  $I_{co}$  must be subtracted from it. If it is desired to read  $I_{co}$  where this is excessive, the scale should be also calibrated 0–5mA and marked  $I_{co}$ .

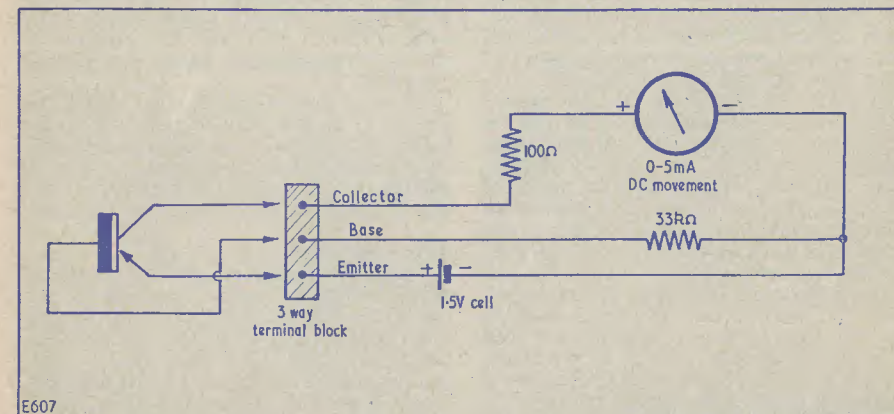

$I_{co}$  will be small enough to be neglected.

The only components needed are a 2in 0–5mA moving coil instrument, a 33k $\Omega$  and a 100 $\Omega$  resistor, a 1.5V penlight cell and a 3-way terminal block. These are wired as shown in Fig. 1 and are housed in a box which need be only a little larger than the meter instrument itself. By the use of the extremely small 1.5V hearing aid cells now available, it should be possible to build the components into the meter instrument case. The 3-way terminal block is mounted on the

The drain on the battery is so small that it can be soldered into the circuit. As the reading will be affected by falling battery voltage, a periodic check can be made on this by measuring the voltage at the terminal block between collector and emitter terminals.

Every care should be taken to correctly connect transistors into the circuit, but should a mistake be made, the current flow will be limited by the 100 $\Omega$  resistor to 15mA maximum.



# Radio Miscellany

ALREADY A NUMBER OF LETTERS HAVE BEEN received from readers advocating even further the widening of the range of interests covered in *R.C. Radio* and electronics are now used so much in the development of other branches of science that they have become almost inseparable from them. With the advent of the Space Age the relaying back of information by automatic communication and radio control are only parts of the role they play. Who, can foretell what developments may take place in the transmitting of power to space ships?

The recent moon rocket, although it failed to achieve its objective and burned up on re-entry in atmosphere, penetrated nearly 80,000 miles into space and much valuable new knowledge of the universe was gained. It can be confidently expected that within the next few years reasonably certain control of space ships in orbit will be achieved. Unhappily they are likely to be used for military reconnaissance, but peaceful uses such as the relaying of t.v. programmes and long range weather forecasting will quickly follow. From that stage we may discover means of controlling the weather to some degree—an alluring promise to us poor inhabitants of the British Isles when we ruefully look back over our last two summers!

The implications, however, go far deeper. With the world's fast-growing population vast new areas for food production will need to be made available. It is a frightening thought when one considers it, that nearly a quarter of the land surface of the world is already desert. This area, too, increases annually at an alarming rate—in some places advancing as much as 30 miles a year on a frontage hundreds of miles long. The erosion of these fringe areas is accelerated by nomadic herdsmen overgrazing the sparse plant life and using the few remaining trees and scrub as fuel.

It was only when, during the war, I saw a little of the deserts that I became aware of the acuteness of this problem; although, of course, I had heard about it in a general sort of way. It came as rather a surprise to me

to learn that deserts are not all sandy, flat wastes. Much of it is gravelly and strewn with broken rock, and it is far from flat. In an area where by repute there had been no rainfall for over four years I saw a sudden tropical downpour, following which plant life appeared as if by magic. The plants, too, grew at a seemingly fantastic rate only to later disappear for lack of moisture.

Since then the problem of deserts, of which Europe is the only continent to remain free, have held a fascination for me. Much of these areas could be made fertile if we had some measure of control over rainfall, and it is by no means impossible that we may yet learn to precipitate, from space, our passing clouds to make these barren areas food producing—or even to release some of our own unwanted rain into the Atlantic to ensure ourselves of a warm, dry summer every year.

At this point an odd thought strikes me. Should we discover how to guide rain clouds before precipitating them to the desired area, we in Britain will need to invent new opening gambits for our casual conversations, and also to find something else to grumble about.

## Rays—No Laugh

The recent announcement that “sterilised zones” are to be formed extending up to a mile in the path of N.A.T.O. forward-scatter radio links located in the U.K. will have been noted with interest by many readers. For security reasons the sites are secret although, with the gradual clearance of their frontal areas, the secret may be hard to keep. The public, for their own safety, will not be allowed to remain permanently in these zones. Occupied farms and homesteads will have to be evacuated, nor will cattle be allowed to remain on the pastures. At present, even when concentrated into a narrow beam, the effects are unlikely to be very damaging; but with the early development of even more powerful equipment the local danger zone might well extend up to several miles. Modern tropospheric forward-scatter radio links operating with only 40kW

into highly directional aeriels can produce a continuous beam of energy of around 40 megawatts, and even greater efficiencies are likely in the near future.

Such efficiencies are, of course, a very long way from becoming a “death ray” and such a ray is still a highly improbable development, but prolonged exposure to radiation may easily cause deep-seated heating inside the human body. Nor is one conscious that one is in the path of the beam. Some of the effects on the human body have long been known to the medical profession, and for years short spells of such radiation have been used for various forms of treatment. Indeed, I had two courses of such treatment earlier this year (and may yet have to have a third). Perhaps I am partially immune, but the only ill effect upon me was a mild feeling of sickness on a couple of occasions. A few other patients, however, did not get off so lightly—possibly due to other physical weaknesses.

An interesting sidelight was that the nurses and ward staff, who themselves never went near the carefully screened treatment chambers, often complained of ill-effects and frequently went sick because of it. They were firmly convinced that the effects they suffered

of angering the non-gramo readers. Still, I suppose nearly everybody is interested to know if a line considerably cheaper than the standard article is as good in service, and if that's true it undoubtedly applies to gramophone records as much as anything else.

Firstly, E.F.G. of Malvern makes some criticism of “Classics Club” records (which were praised by earlier correspondents). He has tried a dozen titles and is obviously a lover of serious music, so his opinion is well worth quoting. While agreeing that many of their records are excellent in every way, he has found two or three of their discs lacking. E.F.G. adds that he has a friendly feeling for these records even after the occasional lapses, if only because their choice of titles has introduced him to a number of new musical pleasures. The only comment I would add to this clearly thoughtful opinion is that quite a few standard recordings suffer pre-emphasis, bass or top cut, imperfect balance or other pitfalls which make the lives of recording engineers difficult.

Now for a further opinion re the “World Record Club” discs (whose records came in for some criticism). G.A.N., who is a radio technician at London Airport, writes to say

## Centre Tap talks about items of general interest

from were due to re-radiation from us patients. At the time it seemed to me highly improbable that patients who themselves suffered little more than a feeling of general debilitation could re-radiate enough to affect normal and perfectly healthy people. I half-dismissed it as being largely psychological, but there may well have been more to it than I then thought. Recently special protective undies, even down to bras and girdles, have been designed. These are claimed to give up to 95% protection from radiation effects. Whether such clothing is to be available for nursing staffs whose only need for protection is from re-radiation from those who have been treated, doesn't seem to have been yet decided.

## A Different Tune

Last month, in quoting a few of the later letters on the subject of the reproduction quality of the various “club” gramophone records, I wound up by saying that correspondents had been unanimous in their opinions. So they were, but alas I spoke too soon. The day following my copy going off to the printers, letters expressing exactly the opposite view began to arrive. Thus, in fairness to the latecomers I have to re-open the subject briefly this month, even at the risk

he has submitted them to most searching tests from which they emerged with flying colours. He has had experience in a manufacturer's test department and his judgment on the satisfactory reproduction of World Records is based on playings made under exacting conditions with top grade equipment. These and other belated letters in similar vein set me wondering whether people write more readily when they see something with which they disagree. If so, perhaps some of the original correspondents will return to the fray.

Also rather belated is a fresh title entered for our recent quest for the ideal “Test-cum-pleasurable-listening” record. It comes from J.N. (No. 1 Wing, R.A.F. Locking) who recommends “A Grand, Grand Overture” backed by “Sound Barrier” (Columbia SED5542). He says the music of both is excellent and exciting, but thrown in for good measure are vacuum cleaners, floor polishers, rifles, cannon, plus an organ and other weird and wonderful effects. Weird and wonderful at least to the world of music! On top of all this there are some rapid changes from double pianissimo to extra fortissimo, high density percussion groups and woodwind top notes

*continued on page 373*



Further  
Notes on the  
WIDE RANGE  
BATTERY OPERATED

# GRID DIP METER

By D. W. EASTERLING

CONSTRUCTORS OFTEN FIND THAT OVER A period of time operational experience makes desirable some modification or added refinement to apparatus which initially appeared to be completely satisfactory. A typical example was the grid dip meter designed by the writer and described in the October '58 issue of *The Radio Constructor*.

The changes made to the original design were aimed at increasing the usefulness of the instrument when used as an ordinary signal generator for test and alignment purposes. It was also considered necessary to make better provision for tests involving screened coils. The incorporation of these additional facilities necessitated the use of only a few extra components and no extra valves. Because the original unit was so compact, however, it was found necessary to rebuild into a slightly larger case. This led to further advantages such as room for a bigger and directly calibrated tuning dial, also slightly larger batteries could be used permitting more economical operation. The net result is an instrument simple in design, yet comparable with a signal generator for many purposes, plus additional facilities which the average signal generator does not possess.

It will be recalled that the principle of the grid dip meter is as follows: a valve oscillator generates grid current proportionate to the oscillator power. If some of the power is absorbed by an external circuit, the grid current will fall. Maximum absorption will occur when the resonant frequency of the external circuit is the same as the oscillator frequency. By tuning the oscillator frequency across the resonant frequency of the external circuit, therefore, the oscillator grid current will dip at the precise point where both frequencies are identical. If the oscillator is calibrated, and the grid current indicated, the unit may be used to determine the resonant



frequency of an external tuned circuit. From this information, it is often possible to derive other information also.

The original design consisted of a Shunt Colpitts Oscillator tuned by a two-ganged variable capacitor, with plug-in coils for each frequency band. The coils were arranged to protrude from the end of the unit, enabling direct inductive coupling to be obtained with the external circuit under test. A DM70 magic eye was arranged to indicate variations in oscillator grid current.

The revised circuit, which is basically the same as the original, is shown in Fig. 1.
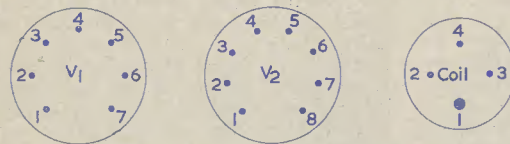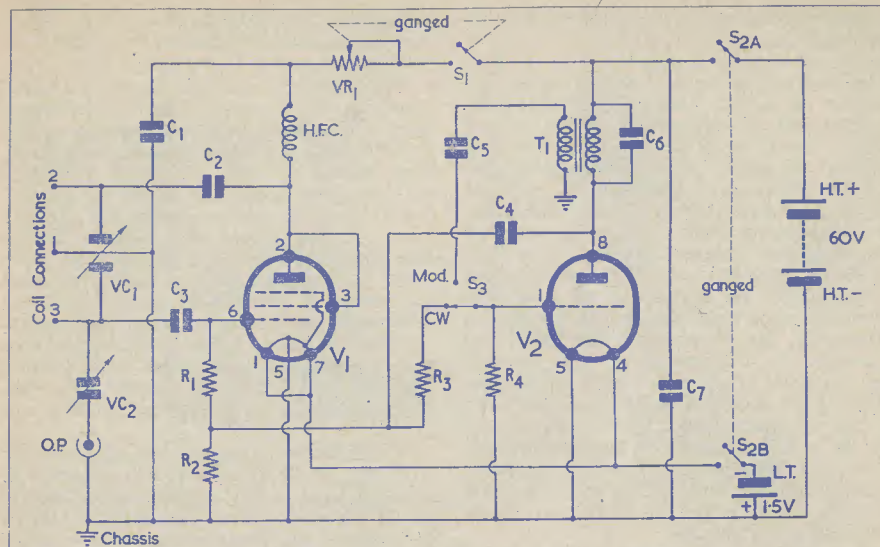
### Components List

- R<sub>1</sub> 10kΩ ¼ watt resistor
  - R<sub>2</sub> 1MΩ ¼ watt resistor
  - R<sub>3</sub> 47kΩ ¼ watt resistor
  - R<sub>4</sub> 1MΩ ¼ watt resistor
  - C<sub>1</sub> 0.001μF tubular capacitor
  - C<sub>2</sub>, C<sub>3</sub> 47pF silver mica capacitors
  - C<sub>4</sub> 0.001μF tubular capacitor
  - C<sub>5</sub> 0.005μF tubular capacitor
  - C<sub>6</sub> 0.005μF tubular capacitor (see text)
  - C<sub>7</sub> 0.1μF tubular capacitor
  - VR<sub>1</sub>, S<sub>1</sub> 1MΩ potentiometer with s.p. switch
  - VC<sub>1</sub> 75+75pF two-gang capacitor
  - VC<sub>2</sub> 30pF (max) variable capacitor
  - H.F.C. H.F. Choke, Eddystone type 1066
  - S<sub>2a</sub>, S<sub>2b</sub> D.P. On-Off switch } see text
  - S<sub>3</sub> S.P. changeover switch
  - O.P. Socket Belling and Lee L604/s
  - L.F. Coils, wound on Eddystone formers, type 763
  - H.F. coils, wound on Eddystone formers, type 765
  - Coil Holder, Eddystone type 707
  - V<sub>1</sub> DL94 Mullard valve
  - V<sub>2</sub> DM70 Mullard tuning indicator
- Batteries, case, knobs, valve holder, tag-strip, nuts, screws, wire, sleeving, etc.



Base Connections viewed from underside.

FIG.1.

Revised Circuit of the Wide Range Battery Operated Grid Dip Meter.

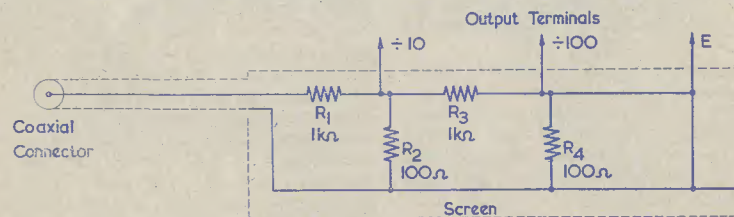


FIG.2.

A Simple Attenuator Network.

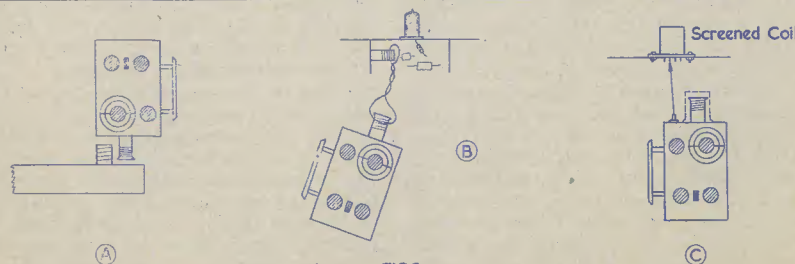


FIG.3

Different Methods of Coupling the Grid Dip Meter.

M559



Consider first the main changes in the r.f. oscillator circuit associated with  $V_1$ . An additional variable capacitor ( $VC_2$ ) has been fitted connecting the grid end of the tuning coil to an output socket. The sensitivity control  $VR_1$  has been moved from the grid circuit, where it is replaced by  $R_2$ , and inserted in series with the oscillator h.t. supply. Previously, variations in oscillator power due to different coils, etc., were compensated in the display circuit by adjusting the negative voltage derived from the oscillator grid current. This arrangement also enabled the display to be controlled when the unit was used as an absorption wavemeter, but in practice was found unnecessary. In the new circuit  $VR_1$  controls the oscillator h.t., and hence its power, enabling the oscillator to be always operated at the optimum level.  $S_1$ , which may be ganged to  $VR_1$ , enables the oscillator supply to be cut completely, when the oscillator ceases to operate, and  $V_1$  functions as a diode detector enabling the unit to be used as an absorption wavemeter.

Now take a look at the display circuit associated with  $V_2$ . It will be seen that with switch  $S_3$  in the CW position, the grid of  $V_2$  is d.c. coupled via  $R_3$  to the grid leak network of  $V_1$ , permitting variations in oscillator grid current to be indicated by the display of  $V_2$  in the usual way. When  $S_3$  is switched to MOD, however, the grid of  $V_2$  is coupled via  $C_5$  to the transformer  $T_1$ . The magic eye then behaves as a normal triode in a tuned anode oscillator circuit operating at audio frequency. This audio signal is fed via  $C_4$  to the grid circuit of  $V_1$ , thus modulating the r.f. signal.

The transformer  $T_1$  is an ordinary intervalve transformer with a winding ratio in the region of 3:1. None of the component values associated with  $V_2$  are critical, but  $C_6$  may be selected to give the required frequency and waveform. Clean panel layout will be maintained if  $S_3$  is incorporated with  $S_2$  as a 3-pole, 3-way switch.

The anode current of  $V_2$  should not exceed  $100\mu A$ , and if the oscillation is too fierce it may be necessary to dampen the primary of  $T_1$  with a parallel-connected resistor. An indication that  $V_2$  is oscillating is given by the display, which appears fuzzy.

To obtain a nominal 20–30% modulation, the oscillator control ( $VR_1$ ) should first be set to half illuminate the display of  $V_2$  with  $S_3$  in the CW position. If an audio signal only is required, the r.f. oscillator should be switched off by  $S_1$ , and  $VC_2$  increased to maximum, when the output can be taken from the output socket. Due to low capacitive values associated with this circuit, the waveform at this point, although suitable for signal tracing purposes, is far from good. A

better waveform may be obtained by fitting a special audio output socket connected via a  $0.01\mu F$  capacitor to the anode of  $V_2$ .

When the grid dip meter is used as a signal generator, it is necessary to control the output level while limiting random radiation. The first step is to fit a screening can over the coil. This should be easily removable to permit coil changing, and direct inductive coupling when required. Unfortunately the can will tend to effect the tuned circuit, causing changes in calibration. This can be minimised to some extent by using a fairly large can made of non-ferrous metal. Even so, differences are bound to occur, and consequently it is best to calibrate initially with the can in position, as it is under this condition that the unit is used as a signal generator, when accuracy of calibration is most important.

A suitable screening can may be obtained from an old EF50 valve ( $VR91$  available in quantity from ex-Government surplus equipment). This is of a convenient size, made of aluminium, and easily secured into position (yet just as easily removed) by using the special retaining clip made for this type of valve. To remove the can from the valve assembly, the flange at the base is carefully prised open, permitting the baseplate and valve to be withdrawn. The flange should afterwards be bent over with pliers to form a rigid edge.

With the coil screened, the output is taken from the special socket which should be a co-axial type such as the Belling and Lee L604/s (which takes the plug L734/P/AL). To reduce the effect external circuits may have on the oscillator, and also to provide further control of output level, the simple attenuator network illustrated in Fig. 2 may be used. This consists of two L networks, each attenuating by 10 (20dB), making a total attenuation of 100 (40dB). If desired, the network may be extended. The unit is constructed in a small screened container (a small tobacco tin, for instance), and is fitted with suitable sockets to take the output leads. A short length of co-axial lead suitably terminated is used to connect the attenuator network to the main unit. It is important that this should be less than 6in to prevent serious shunting of the oscillator.

When the instrument is used as a grid dip meter or wavemeter, coupling to external circuits may be made direct, as in Fig. 3 (a); via a low impedance coupling loop, as in Fig. 3 (b); or capacitively, with a single lead connecting the inner contact of the output socket with the "hot" side of the circuit under test, as in Fig. 3 (c). At all times, the variable coupling capacitor  $VC_2$  should be set to minimum capacitance, consistent with reasonable results.

## MISCELLANEOUS

# Experimental Chassis Construction

By B. T. DENVIR

IT IS OFTEN FOUND DESIRABLE TO MODIFY A receiver or improve it in some way; to add an a.f. stage, to put in an a.f. filter, i.f. crystal stage, a.f.c., a.v.c. amplification, etc., etc. When the set is already built on a chassis, this nearly always proves very difficult, or impossible, without entirely dismantling and rebuilding, possibly on another chassis. Many, quite reasonably, will abandon their idea, deciding that it is not worth the labour involved.

The following method of chassis construction was therefore devised, with the end in view of allowing modification and improvements, and general experimenting to take place with minimum dismantling and reconstruction, etc.

The basis of the construction consists of three  $12\frac{1}{2}$ in Meccano girders. These girders have holes at  $\frac{1}{2}$ in intervals, and are bolted to smaller  $2\frac{1}{2}$ in girders as shown in Fig. 1. Then small "L" section chassis are made, measuring  $2\frac{1}{2}$ in x  $2\frac{1}{2}$ in, one for each "unit" of the set. (For instance, one for r.f. and f.c., one for i.f. amp., one for det. and a.v.c. and b.f.o., etc., as is convenient.) Incidentally, in the interests of stability, it is not wise to divide h.f. circuitry into several chassis; thus, for example, it is safest to put the r.f. and f.c. stages on to one chassis. These chassis are then bolted to the girder framework, as shown in Fig. 2, and components may be put in place and wired up. If it is more convenient, the order of these events could be reversed.

The only leads which need go from one chassis to the next are h.t.+, heaters, earth,

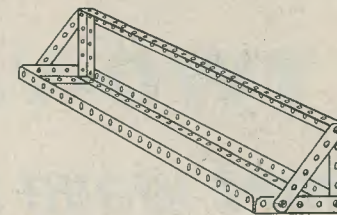


FIG. 1

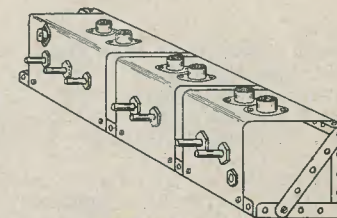


FIG. 2

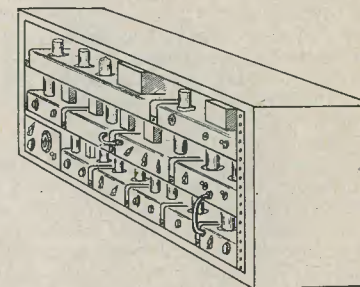


FIG. 3

M557

and the signal lead; also possibly a.v.c., bias or some other such lead, depending on the application. A short stout wire for an earth lead must be used, as the painted surface of the girders is not a reliable conductor. Also, twisted pairs of wires must be used for the heaters, and these must not be earthed except at the power-pack, otherwise 50 c/s voltages will be set up across the earth leads, causing disturbing hum.

Thus, when a new unit is added, an i.f. stage, say, only five or six wires need be cut and resoldered, maybe less, and the chassis

continued on page 373



# a TWO-VALVE short wave receiver

By  
R. E. S. COULSON

### Description

THIS SET IS ESSENTIALLY VERY SIMPLE. THE first stage, round  $V_{1A}$ , is just a normal detector with reaction (or regeneration); the second, round  $V_{1B}$ , is a normal voltage amplifier. The third  $V_3$ , is the power output stage.

Signals are brought into the set through  $L_1$  and the 300pF variable condenser  $C_1$ . This condenser is for avoiding aerial resonances, and thus eliminates "dead spots."  $L_2, C_2, C_3$  form the tuning circuit. I used the two condensers  $C_2$  (variable, 500pF) and  $C_3$  (1,000 pF) because I had no 300pF tuner. The two in series behave approximately as a 300pF tuner and are cheaper, but there is no reason why a 300pF condenser should not be used. It should in any case be ceramic-insulated.

The signal, or at least some part of the signal, is rectified in  $V_{1A}$ , but some r.f. does get through. This cannot pass through the r.f. choke (which should be a S.W. one), and so has to pass through  $L_3$  to earth.  $L_3$  is tightly coupled to  $L_2$  and thus some positive feedback is introduced; this is increased by the  $C_4, C_5$  combination until just before the oscillation point. Here the set is most sensitive. It is often very difficult, even under the best of conditions, to keep the set uniformly sensitive over, say, 300 kc/s by adjusting  $C_4$ ;  $C_5$  has therefore been introduced to make the job easier. If it is still difficult and oscillation begins suddenly, it might be as well to adjust experimentally the values of  $C_6$  and  $R_1$ . Audio signals are passed through the r.f.c. and  $C_7$  to  $S_1$ .

$S_1$  is the radio/gramophone switch and  $R_3$  is the main volume control, operating in both positions of  $S_1$ .  $R_4$  is to drop the h.t. voltage on  $V_{1A}$  down to about 200 volts.  $C_8$  is to remove any trace of hum (at 50 c/s) from the detector, and of voice frequencies from the h.t. line and thus the rest of the set. The cathode resistance of  $V_{1B}$  is unbypassed because this introduces slight negative feedback and also because it is cheaper. The

### Components List

#### Condensers

- $C_1$  300pF, mica, variable
- $C_2, C_3$  See text
- $C_4$  300pF mica, variable
- $C_5$  15pF, air, variable
- $C_6$  200pF mica
- $C_7$  0.05 $\mu$ F, paper—350 VDC
- $C_8$  2  $\mu$ F, paper—350 VDC
- $C_9$  0.5 $\mu$ F, paper—350 VDC
- $C_{10}$  25 $\mu$ F, electrolytic—25 VDC

#### Resistors

- $R_1$  2.2M $\Omega$
- $R_2$  47k $\Omega$
- $R_3$  1M $\Omega$  potentiometer, log
- $R_4$  220k $\Omega$
- $R_5$  1k $\Omega$
- $R_6$  270k $\Omega$
- $R_7$  330 $\Omega$
- $R_8$  220k $\Omega$

#### Valves


- $V_1$  6SL7GT or 6SL7M
- $V_2$  6V6GT or 6V6M
- $V_3$  5Y3GT

#### Switches

- $S_1, S_2, S_3, S_5$  All single-pole change-over switches
- $S_4$  4-pole 3-way rotary switch
- $S_6$  2-pole on/off switch
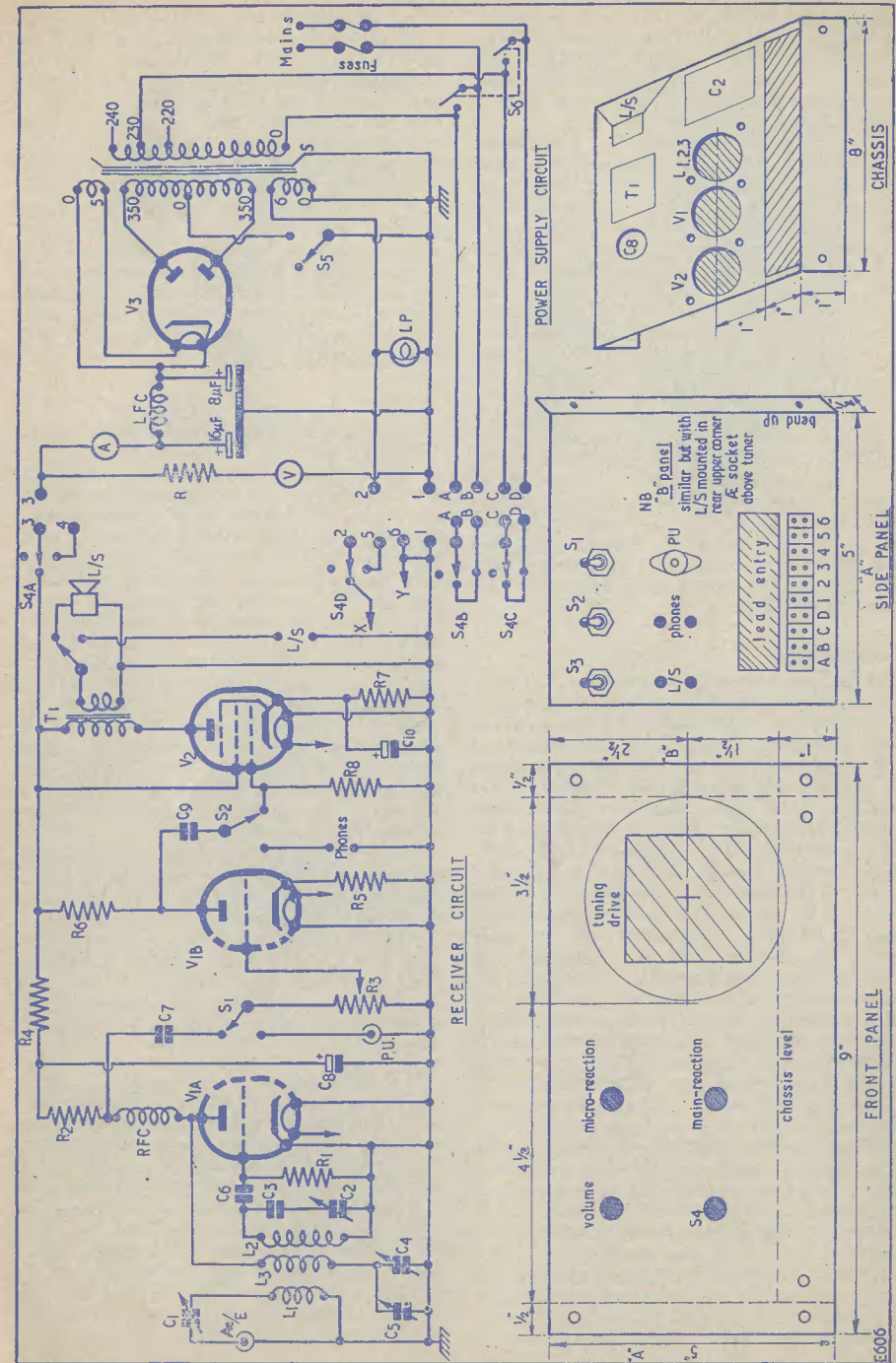
#### Miscellaneous

- R.F. choke—short wave type
- L.F. choke—20H—80 mA
- Smoothing condensers—8+16 $\mu$ F 450V d.c. working, 550V surge
- Mains transformer:
  - 200–230V primary
  - 350–0–350V h.t. secondary
  - 0–6.3V heater secondary
  - 0–5V rectifier heater secondary
- Output transformer ( $T_1$ )—Multi-ratio or 6V6 to 3 $\Omega$  type
- Loudspeaker (internal) 3in Rola
- Metal plugs, sockets, terminals, tags, etc.
- Tuning drive—Admiralty type No. 8419 was used in prototype





anode load resistor,  $R_6$ , is high enough in value to provide a nice large a.f. voltage when using low-voltage output pick-ups, and plenty of audio gain is available when receiving weak signals.  $C_9$  is made large to avoid attenuating the bass.

$S_2$  is the phones/l.s. switch. The phones socket is useful when listening for weak signals and also when listening in a noisy room (or one in which one is supposed to be quiet!). The rest of the output stage is quite conventional. A switch which changes between internal and external loudspeakers was fitted because L.P.s don't sound very good on a 3in speaker. For most S.W. listening the small speaker is quite adequate.

The switch  $S_4$  is for control of the power circuits of the set. It is shown in the "receiver" position.  $S_{4D}$  is responsible for controlling the l.t. (6.3V) circuit. Terminals are fitted for, say, a QRP transmitter (up to 10W) or a v.h.f. receiver, or a M.W./L.W. set.  $S_{4A}$  switches the h.t.+ lead. When using a transmitter (and  $S_4$  as send-receive switch), "5" and "x" on  $S_{4D}$  may be shorted, so that there is no delay. Switches  $S_{4B}$ ,  $S_{4C}$  are for remote control of the power pack. (In my case the power pack was about 10ft away from the set.)

#### Construction

First, assemble all parts roughly on a piece of paper the size of the chassis to determine how they are to be fixed. A good layout is that shown in Figs. 2, 3, 6, 7, but much, of course, will depend on what parts you have. I, for example, used a 500pF tuner, a 3in speaker, octal valves, and that tuning drive merely because they were in my spares box. It would be possible to use a 300pF tuner, a 5in or 8in speaker (but not on the same chassis), B9A valves, or a non-surplus tuning drive. Use the best output transformer that can be afforded; cheap ones can give really shocking quality, almost unnoticed on average jazz, but showing up on classical music and always noticeable on piano. In the prototype, Denco octal plug-in coils, Green ranges 3, 4, 5, were used to cover all the short waves from 1.6 to 32 Mc/s. (Ranges 1 and 2 cover L.W. and M.W. respectively.) This firm also makes similar coils with B9A bases.

Mark out the positions of holes, etc., on the metal, not forgetting the 7in x 1in slot in the front of the chassis; this helps a lot with wiring up the front panel. A glance at the left end of the set will show that the wiring is pretty tight. The best method is to make sure that the chassis fits together all right and then wire up  $S_4$ , with terminal block and a tag strip (not shown) on left of set. Next put all the rest of the mountable components on the chassis, with a solder tag under at least

every valveholder nut, and the coil holder.

Now wire up the detector stage,  $V_{1A}$ .  $C_1$  does not appear in the diagrams showing layout, as I had an aerial tuner at the lead-in and thus did not need it. Keep all leads in this part of the set as short as possible. There is a great temptation to leave them long "just in case the set won't work," but it is more likely not to work if the leads are left long.

$V_{1B}$  circuits are comparatively straightforward, and so are  $V_2$ . It may be necessary to use a separate box for l.s. and transformer circuits. If it is possible to use screened leads for a.f. wiring, do so; I did not and I found the hum level (which may have been due to bad smoothing in the power pack) a little high, though bearable.

#### Testing

Although the circuit of the set is simple, working it properly is not quite so easy. Plug in the valves and aerial and connect up the power supplies. Put in coil range 4 and with the reaction condenser at minimum capacity tune over the band. About the middle, some stations ought to be heard; when they are, turn up the reaction control and retune the set, as any considerable alteration in the reaction control alters the tuning slightly. If the reaction is turned up too far, the set will oscillate and whistle. Severe distortion is usually audible first. Many people who have tried to get stations on this set for the first time have failed through not adjusting it properly; with careful adjustment an apparently empty band can be made to yield signals—all that is needed is practice and patience. The main trouble is that the tuning alters with the reaction.

When tuning over a limited (e.g. amateur) band, the micro-reaction control is set at half capacity and the tuning set to the middle of the band. Bring up the main reaction until the set just oscillates. Then reduce capacity with the micro control. There is now no need to touch the main control. Any searching can be done by adjustments to the vernier tuner and micro-reaction controls.

#### Power Pack

This uses a 350-0-350V transformer ( $T_2$ ) with 5V and 6.3V heater windings and a standard mains primary. Two fuses are fitted in case of shorts in the remote control circuit. My power pack was fitted on a 6in x 4in x 2in chassis; the 6in x 6in front panel was fitted with h.t. switch ( $S_5$ , in lead from middle of h.t. winding, to earth), local mains switch ( $S_6$ ), "l.t. on" lamp, and two meters, one for voltage, one for current, to read d.c. h.t. output. A is an 0 to 80mA meter, V an 0 to 1mA meter with a 450k $\Omega$  resistor, R, in

*continued on page 365*

## THE PREMIER *Petite* BATTERY PORTABLE RADIOGRAM



Described by JAMES S. KENT

THE "PETITE" BATTERY PORTABLE SUPERHET was fully described in this magazine some time ago (December 1957 issue—Ed.), and since that time many hundreds of these excellent little receivers have been successfully constructed by hobbyists. A recent innovation, however, has been the addition to the basic circuit—the receiver—of a battery operated gramophone reproducer. By this means, one is able not only to enjoy the radio programmes when out of doors but also to select and listen to one's own favourite recordings. To the best of the writer's knowledge, this is the very first time that such a kit has become available to the home constructor; although, of course, battery-operated turntable motors have been available to manufacturers for some time past.

The complete receiver and reproducer is relatively inexpensive and simple to construct and here may well lie one of the answers to the Christmas gift problem. The turntable, motor and pick-up are supplied ready assembled and tested—all that is required of the intending constructor is to build the receiver, or modify an existing one, connect the pick-up, fit into the case and all is complete. For those who already have the "Petite" portable radio, a new case will be required in place of the old one, additional room being required in order to accommodate the motor.

From the front cover illustration it will be noted that the whole assembly is housed in an extremely attractive two-toned carrying case; there are two choices of colour arrangements. The turntable is of cream plastic, as is the motor board, and the pick-up arm is white. The latter fits snugly into position whilst the case is being carried. The pick-up head has a clear plastic protection dome and an automatic stylus cleaning brush. The motor incorporates its own stop-start mechanisms.

#### Circuit

The circuit of the portable radio and reproducer is shown in Fig. 1. From this, it will be seen that some modifications to the original design have been made in order to incorporate the gram position, etc. For those to whom the circuit is new, a short description follows.

The frame aerial assembly, fitted inside the cabinet lid, is tuned by  $C_{3A}$  on the Medium wave position and by the combination  $C_{3A}$ ,  $C_1$  and  $C_2$  on the Long wave position of the wavechange switch. The frequency changer is the Mullard DK96, a heptode type that performs extremely well in such an application. The numbers around the valve refer, of course, to the actual base connections.  $R_1$ ,  $R_5$  decoupled by  $C_{11}$  apply the a.v.c. voltage to both the frequency changer and the first i.f. stage. This effectively prevents over-




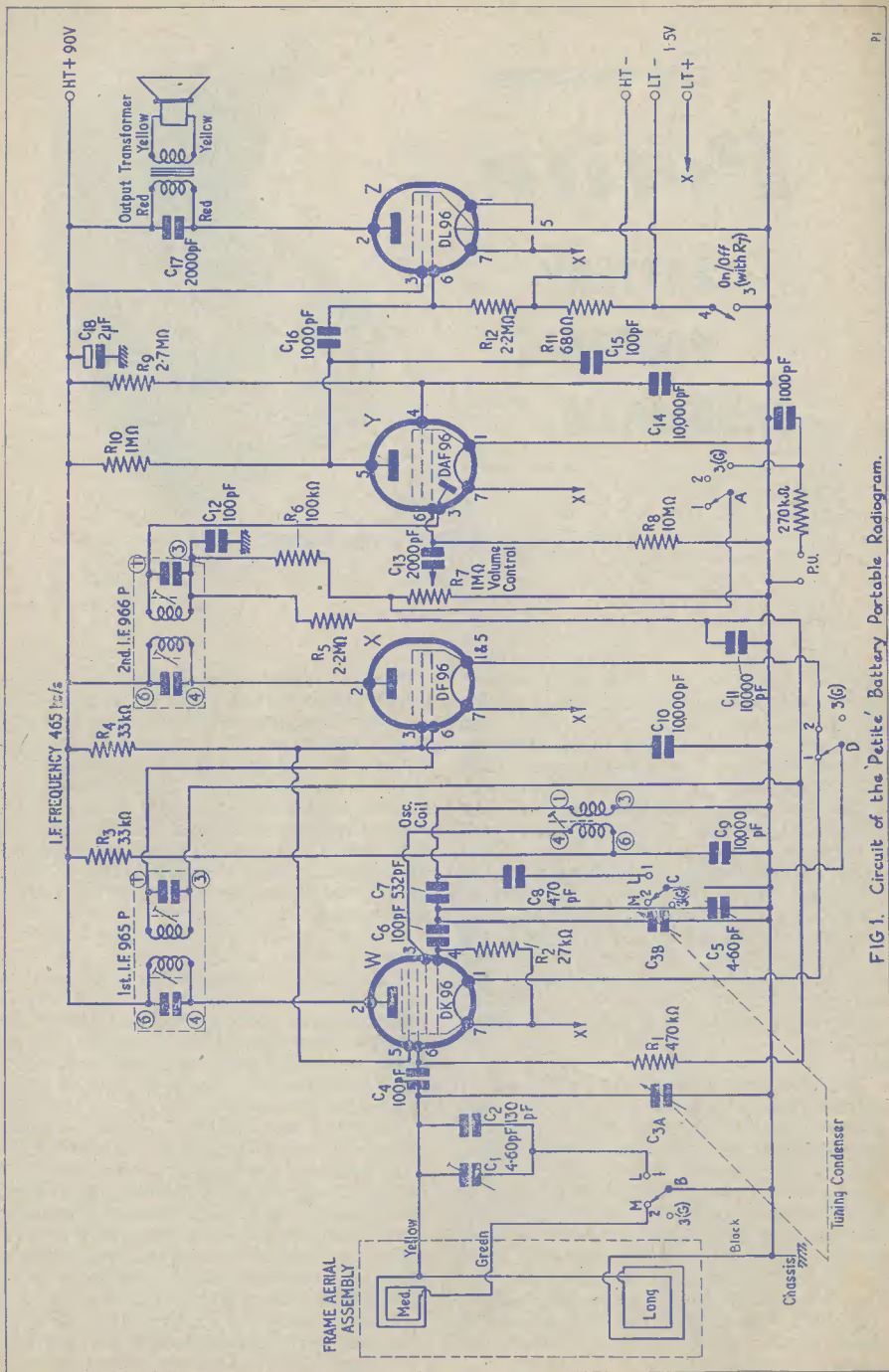


FIG. 1. Circuit of the 'Petite' Battery Portable Radiogram.

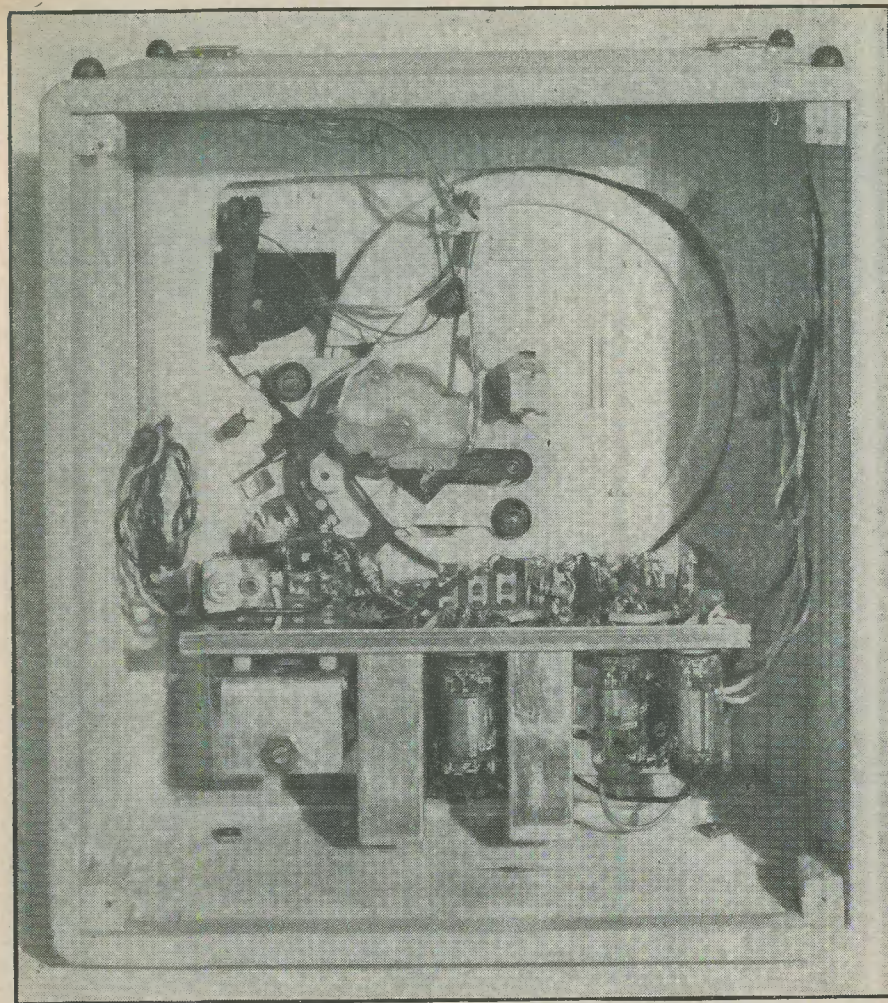

Underneath view of the motor and chassis layout

loading when tuned to the local transmitter. The oscillator section is tuned by C<sub>3B</sub> with C<sub>5</sub> in parallel on the Medium wave and the additional C<sub>8</sub> on the Long wave position. C<sub>7</sub> is the oscillator padding condenser, and is in series with C<sub>6</sub>; the latter, together with R<sub>2</sub>, forms the oscillator grid components; the oscillator "anode", grid 3, is fed directly from the oscillator coil winding. The output from this stage is applied across the first i.f. transformer, type 965P (465 kc/s) and from thence into the i.f. stage. This is a perfectly standard circuit designed

around the Mullard DF96 r.f./i.f. pentode. The resultant output from this stage is rectified by the diode section of V<sub>3</sub>, and the audio is fed via the slider of R<sub>7</sub> and C<sub>13</sub>, into the pentode section of the DAF96. The potentiometer R<sub>7</sub> acts as the volume control. R<sub>10</sub> is the V<sub>3</sub> anode load component, while R<sub>9</sub> is the screen series resistor decoupled by C<sub>14</sub>. The amplified a.f. is fed into the output stage via C<sub>16</sub>, the condenser C<sub>15</sub> filtering any residual r.f. to chassis. The grid leak and bias components respectively are R<sub>12</sub> and







When lifting 12in or larger tubes from the carton they should be handled around the edge of the screen and preferably not extracted by lifting from the neck. If handling by the neck is essential, great care is required to keep the axis of the tube vertical, avoiding any sideways leverage and supporting the bulb where-ever possible. It is usually necessary to take the tube from the packing and place it face downward on the bench prior to installation; remember to have a pad of soft cloth handy to receive it and make very sure that the cloth is free from dirt. Small particles of coal or metal splinters can produce a very severe scratch on a tube face plate. Another possible source of glass scratches is the presence of rings on the fingers of the person handling the tubes. The tube manufacturers have experienced the trouble which such rings can cause, particularly when they are fitted with ready-made

possible to remove a tube from a set which has recently been in operation with a charge still remaining on the capacitor formed by the internal and external coatings on the cone. By placing a hand over the e.h.t. terminal of the tube whilst contact is made with the external aquadag coating, it is possible to obtain quite a nasty shock. Whilst it is very unlikely that this could be serious to the handler, it can easily cause an involuntary action resulting in the tube being dropped.

#### Metal Cone Tubes

The handling of metal tubes requires the same degree of care as outlined for the glass counterpart, and two additional items are applicable to them. These tubes are vulnerable to knocks on the metal rim as damage may result to the glass-to-metal seal. Some readers will no doubt have had experience of the cracks which occur radially towards the outside of the face plate of these tubes when they are subjected to a blow on the rim. This is an expensive fault and can often be avoided by a little care.

The cones of these tubes are made from a ferrous metal which can be readily magnetised. The cone should, therefore, be kept well away from magnetic components such as speakers and focusing units. Should the cone become accidentally magnetised it will produce a non-uniform steady deflection field within the tube and will appear as very asymmetrical raster distortion. This form of distortion can be distinguished from that due to deflection coils and the other tube accessories because it will rotate as the tube is rotated.

#### Tube Mounting

The mounting of television tubes has been very carefully investigated of recent years as it is recognised that some of the implosions which have occurred have been due to the tube being under mechanical stress in the receiver. Because of the vast number of different tubes and chassis layouts which are possible it is difficult to give specific mounting

details, so perhaps we may commence this section by describing a system which has given quite a lot of trouble in an attempt to show what should be avoided. The receiver in mind had a 17in tube mounted on the chassis. The tube was supported in two places, the main weight being taken under the face plate where a metal strap clamped it to the chassis. The other support was by means of a rubber grommet in the back of the focus magnet which was in turn mounted towards the centre rear of the chassis. Now, as described, this set-up would appear to be satisfactory, but unfortunately the whole chassis assembly was of rather too light construction to take the weight of a relatively large tube. In fact, if the chassis was lifted at two opposite corners the back would move relative to the front where the tube was supported, and this caused the focus magnet to apply appreciable pressure to the tube neck. Steps were taken to reinforce the chassis when one day as it was being lifted from the cabinet there was a loud report which investigation subsequently revealed as due to the tube neck being removed from the cone. This proved to be a somewhat expensive way of finding out the importance of preventing relative movement between the cone and neck supports.

In general, the weight of the tube should be taken near the centre of gravity which is two or three inches behind the face plate. Also, the relatively flat surface of the glass in this area makes it suitable for taking a clamping band designed to hold the tube rigidly to the chassis. The tube should rest on two blocks whose combined length is greater than one-third of the length of the horizontal edge of the tube, and the metal clamp should be held off the glass by means of a plastic or rubber strip. This arrangement is depicted in Fig. 1.

An alternative assembly is shown in Fig. 2, which is used in receivers where the tube is fixed permanently in the cabinet and the deflection and focusing components are

supported from the sides of the cabinet. Here again it is most essential to make the cabinet sufficiently rigid to prevent the focus unit being forced against the tube neck upon lifting. With this form of mounting the tube face is usually supported by the mask and is held in position by spring-loaded cords encircling the cone and attached to the front of the cabinet. A harness of this type is easily made up and can be fastened to the cabinet by means of four hooks screwed into the wood.

#### Electrostatic Tubes

In the mounting of magnetically focused tubes it is impossible to allow the weight of both the deflection coils and the focus magnet to rest on the tube neck so some additional support is necessary and is usually obtained via the focusing unit. However, with the electrostatically focused tube the position is different as the neck carries only the deflection unit and a small ion trap magnet. As the deflection coils are pushed up against the cone section their weight is distributed over a reasonably large area of the glass and it is permissible to rely on the face plate clamp only with no additional support given to the neck end of the tube.

One final point is worthy of mention and is applicable to all types of picture tubes. The socket should not be rigidly mounted, but should be equipped with flying leads which are sufficiently flexible not to apply any pressure to the neck. Also when removing the chassis from the cabinet of a receiver in which the tube is clamped, don't forget to first remove the tube socket. A sudden tug on the leads can produce sufficient strain to crack the neck.

Whilst some of the precautions described may be obvious, it is quite surprising how many tubes have been lost because they have not been observed. So perhaps we may conclude with the familiar saying, "To be forewarned is to be forearmed."

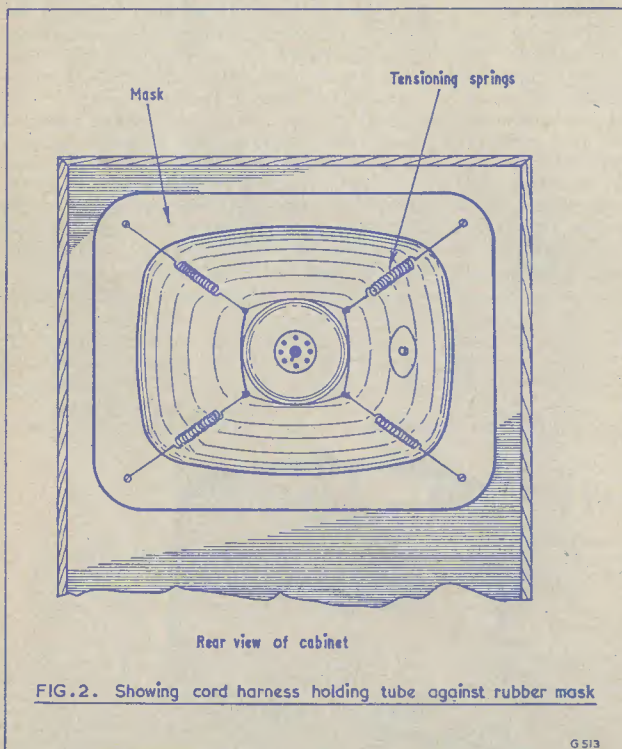


FIG. 2. Showing cord harness holding tube against rubber mask

glass cutters in the form of diamonds. There is another possible way in which a tube may be damaged and it is one which is by no means obvious, but it has caused the loss of several tubes to the writer's knowledge. Most tubes are made from glass which had a high electrical resistivity so that it is

## Two-Valve Short Wave Receiver continued from 358

series. F.S.D. is thus 450 volts. (This is the absolute maximum voltage that may be allowed to appear across the smoothing condenser, but it is not likely to be exceeded; the maximum will not ordinarily be more than 425V.)

The history of this set may present some points of interest. Two years ago, in April, 1956, it was planned as a two-stage T.R.F., battery-driven. In May, two articles appeared in *The Radio Constructor*, under the titles "Simple Kitchen Radio" (page 634) and


"Simple All-Wave Receiver" (page 636), describing very similar sets. The original circuit borrowed many values from the former and some from the latter, and these two will be seen to bear some resemblance to the circuit I eventually used. The frills (all the switching, the micro-reaction, etc.) were added about six months later. The final product seems to me as good as many, and better than some, commercial T.R.F.s and a few superhets, especially in the tuning, which is very sharp indeed.



# The MULLARD

## TAPE AMPLIFIER

### "Type C"\*

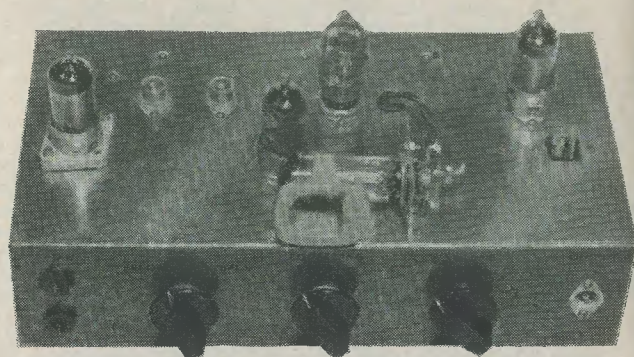

PART 2


Described by R. WEBB

**Component List.**— $C_{18}$ , it should be noted, variable.  $C_{28}$ , shown in Fig. 13 (a) is a 2,200pF silvered mica capacitor and was omitted from the circuit diagram Fig. 2 (Part I, November issue) and also from the component list given.  $C_{29}$ , also omitted, but shown in Fig. 16, is rated at 0.5 $\mu$ F, 350V.

purposes of this article it is assumed that a ready punched chassis will be purchased, and those which can be obtained from advertisers in this publication can be recommended as providing a professional finish to your amplifier. It does certainly help to start off with a nice piece of well shaped metal work.

Somehow this seems to impress the constructor with the need for a careful and neat job with the result that an all-round high class finish is achieved. A little time spent polishing up this item before commencing assembly is well worth the trouble. Any minor blemishes incurred during assembly can usually be removed quite easily afterwards, provided a good preliminary polish

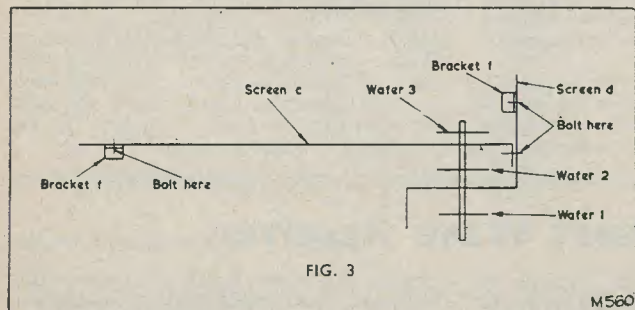
is imparted to the chassis. With regard to the lettered control panel which can be obtained from the same advertisers, and which is recommended to give the finishing touches to the amplifier, there are two kinds available, one with the lettering horizontal as in the photograph of the complete amplifier, and another with the lettering vertical in case you should wish to house the unit in a console


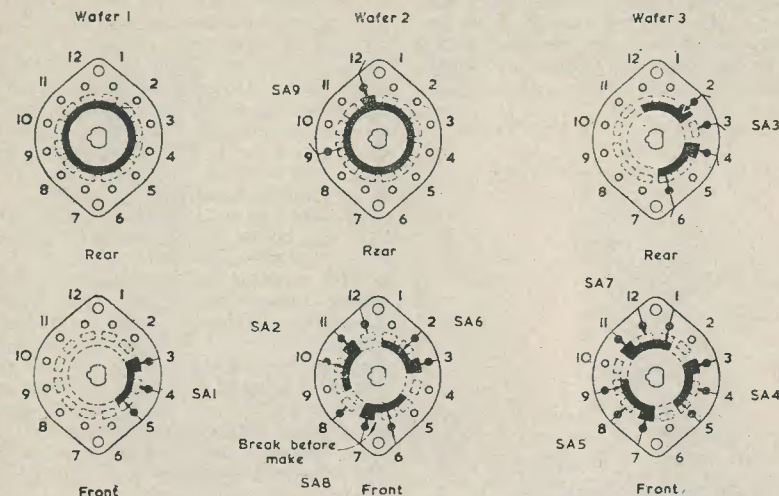
#### Chassis Construction

DETAILS HAVE BEEN PUBLISHED BY, AND are still obtainable from Mullard Ltd. of the layout and disposition of the various holes for components. For the

\* The prototypes of this amplifier were designed and built in the Mullard Applications Research Laboratory by D. H. W. Busby, C. Hardcastle and J. C. Latham.



Number of waters: 3

Number of positions (ways): 2

#### SWITCH LEGEND (also applies to Fig. 5)



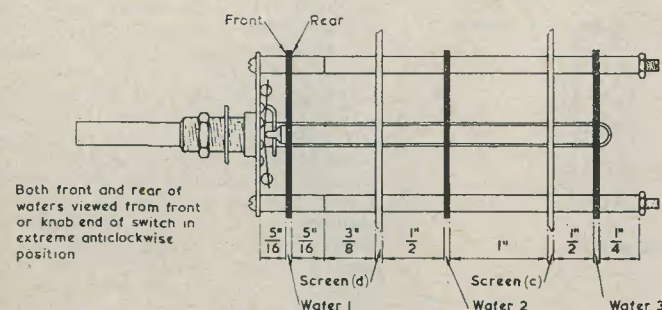


Fig. 4—RECORD/PLAYBACK SWITCH DETAILS

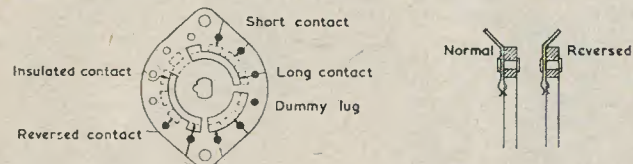

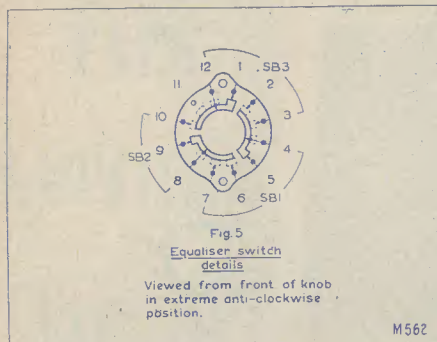
cabinet, for example, which might require the lettering to be read vertically. This is mentioned because the question of filing "flats" on the control spindles may arise and it is as well to do this before wiring them in permanently, seeing that the pointers of the knobs register accurately according to whichever way the lettering runs.


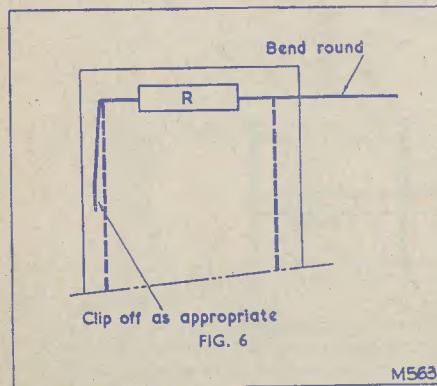
#### Assembly and Wiring Details

For the rest of this article, extensive use is made of the Mullard Publication TP322 which describes the first "Type C", subsequent modifications being kindly supplied by Technical Service Dept. of Mullard Ltd., to whom due acknowledgment for assistance and information supplied is given.

In this section, all positional references to the amplifier should be interpreted as follows: The chassis is upside down for wiring. The top of the chassis is the surface nearer to the viewer; the bottom is the farthest surface. The front of the chassis is the panel with the control knobs on it.




#### Initial Assembly

Before assembling the record/playback switch SA around the screens, it will be found

convenient to fix some of the components to the chassis. These components are:

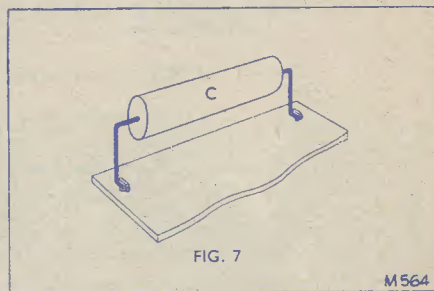- (1) The erase and record/playback coaxial sockets which have to be fitted to the chassis beneath wafer 3 of the change-over switch SA.
- (2) All the valveholders. Only the three EF86 valves should be skirted, and the holders for these valves should be nylon-loaded. The holder for the input valve  $V_1$  (EF86) should be of an antimicrophonic type—that is, having a flexible mounting.
- (3) The two small brackets f, which should be bolted to the internal screens c and d as shown in Fig. 3

The construction is continued after the above components have been fitted by assembling wafers 1 and 2 around the internal screen d. The wafers should be arranged so that positions 6 and 7 are at the bottom and the face of each wafer described as "rear" in the switch diagram (Fig. 4) is farthest from the switch plate. The internal screen c should be added to the assembly, both screens should be bolted



together, and wafer 3 should be fitted in position, again with its "rear" face (Fig. 4) farthest from the switch plate. The general arrangements of the switch wafers and internal screens, is shown in Fig. 3. Details of the spacers required for the assembly are shown in Fig. 4.

On the switch used for the prototype the wafers have a slotted edge to captivate the contacts and soldering tags. This meant that in the Mullard Technical Publication T.P.322, although the soldering tags are in position as shown on that drawing the corresponding contacts are on the other face of the wafers. This has been rearranged in Fig. 4 by reversing the "Front" and "Rear" positioning.

The switch and screens should be fitted to the main chassis, a shakeproof washer being used between the switch plate and the front panel of the chassis. It will be necessary to drill a hole in the chassis so that one of the small fixing brackets, attached to the internal

screen c, can be bolted down. The other small bracket should be fixed by one of the screws holding the record/playback coaxial socket.

The assembling of the unit is best continued by referring to the diagram giving the component layout (Fig. 16). The components that should be fitted at this stage are listed below, and some remarks are made when the exact positioning of the components is perhaps doubtful.

- (1) EM81 mounting bracket—The valveholder should be fastened to the bracket so that the solder tags are on the same side as the flange on the bracket. The gap between pins 1 and 9 on the holder should face the flange to ensure that the tuning eye of the EM81 faces forwards. The level indicator should appear in the centre of the front panel of the equipment, and the bracket should be bolted to the chassis in the correct position for this to be so.
- (2) Input jacks—The soldering tags should be on the inside, and the radio jack, which has two contacts only, should be beneath the microphone jack.
- (3) Recessed coaxial socket for the output.
- (4) Supply input plug—Pins 1 and 3 should be on the outside.
- (5) Equaliser switch—Positions 9 and 10 (Fig. 5) should be adjacent to screen "d."
- (6) Ferroxcube pot core.

#### Wiring Instructions

With this set of instructions, it should be possible to complete the wiring without reference to the circuit diagram. It will be of help, however, to make reference to the diagram, especially if it is intended to use different coloured wires for various sections of the circuit.


It will obviously be more convenient to solder most of the smaller components to the tagboards before they are mounted in the amplifier. Several general remarks may be of use in assembling these small components. Needless to say, all connecting wires are executed in good quality P.V.C. insulated wire.

The small carbon resistors should be laid across two tags on the board, and the lead wires bent around the tags in the manner shown in Fig. 6. If the tagboard wiring diagrams show that the neighbouring tags are to be connected together, the lead wires of the appropriate components should be cut to lengths to allow this.

Waxed capacitors, silvered-mica capacitors and high-stability resistors will require longer

leads so that they will not be overheated when they are soldered into position. The leads should be bent as shown in Fig. 7, care being taken in doing so to avoid sharp bends very close to the ends of the components.

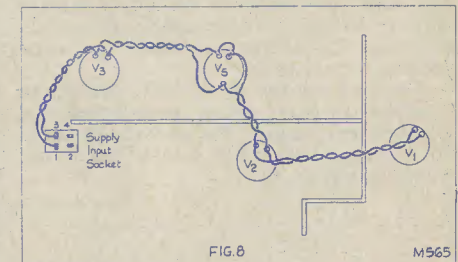Where dotted lines indicate links between tags, the connections should be made with insulated wire.




#### Heater Supply

This is the first stage in the wiring of the amplifier. From pins 1 and 3 of the supply input socket (Fig. 8) a pair of twisted wires should be taken to pins 4 and 5 on the valveholder for valve  $V_3$ . From these pins the wires should be taken to pins 4 and 9 on the valveholder for  $V_5$  (the ECC82) and link 4 and 5. Two sets of heater leads should be taken from  $V_5$ . One set should pass through the rubber grommet to pins 4 and 5 on the holder for the EM81, and the other set should be connected to pins 4 and 5 on the holder for  $V_2$ .

From  $V_2$ , the heater leads should be taken to pins 4 and 5 on the holder for  $V_1$  to complete the heater wiring of the amplifier.
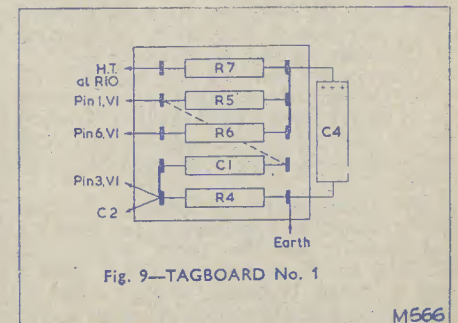
#### The Input Stage (Valve $V_1$ , Type EF86)

The construction of this stage should be started by wiring Tagboard No. 1. The




components:  $R_7$  (33k $\Omega$ ),  $R_5$  (1M $\Omega$ ),  $R_6$  (220k $\Omega$ ),  $C_1$  (0.5 $\mu$ F),  $R_4$  (2.2k $\Omega$ ) and  $C_4$  (8 $\mu$ F) should be soldered to the small tagboard as shown in Fig. 9. It is important







The resistor  $R_{30}$  ( $390k\Omega$ ) should be connected between position 8 on switch  $SB_2$  and position 10 on  $SA_2$ , and the connection should be continued from position 10 on  $SA_2$  to pin 9 on  $V_2$ . The resistors  $R_{31}$  ( $2.7M\Omega$ ),  $R_{32}$  ( $1.2M\Omega$ ) and  $R_{33}$  ( $680k\Omega$ ) should all be joined to position 12 on  $SA_2$ , and the free ends of these resistors should be connected to positions 5, 6 and 7 respectively on switch  $SB_1$ .

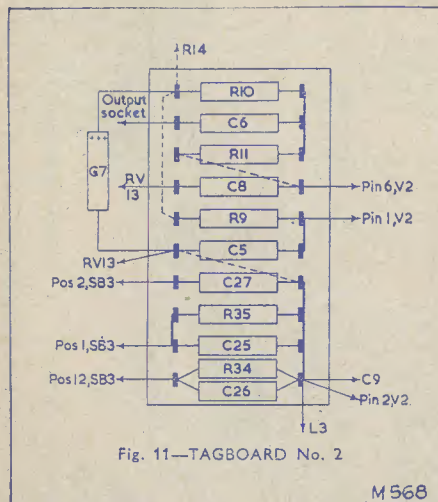

A connection should be made between position 12 on  $SA_2$  and position 12 on  $SA_9$ . Position 9 on  $SA_9$  should be connected to pin 7 on the valveholder for  $V_1$ .

The gain control  $RV_{13}$  ( $500k\Omega$  logarithmic) should be mounted on the chassis at this stage with the tags pointing upwards. The right-hand tag should be joined to the junction of  $C_5$  ( $0.1\mu F$ ) and  $C_7$  ( $8\mu F$ ) on Tagboard No. 2. The left-hand tag of the gain control should be connected to the near end of  $C_8$  ( $0.1\mu F$ ) on Tagboard No. 2, and the capacitor  $C_{22}$  ( $82pF$ ) should be joined between this tag and position 4 on switch  $SB_1$ . The free end of the capacitor  $C_6$  ( $0.1\mu F$ ) on Tagboard No. 2 should be connected directly to the output socket.

#### Recording Output Stage ( $V_3$ , Type EF86)


The following components should be fitted and wired to Tagboard No. 3 as shown in Fig. 12:  $R_{17}$  ( $1k\Omega$ ),  $R_{19}$  ( $10k\Omega$ ),  $R_{14}$  ( $27k\Omega$ ),  $R_{15}$  ( $220k\Omega$ ),  $R_{16}$  ( $68k\Omega$ ),  $C_{11}$  ( $0.1\mu F$ ),  $R_{18}$  ( $470k\Omega$ ),  $C_{13}$  ( $18pF$ ), OA81,  $C_{14}$  ( $0.05\mu F$ ) and  $R_{20}$  ( $1.0M\Omega$ ). In fitting the germanium diode type OA81, plenty of wire should be left at its ends to prevent overheating when it is soldered in position. Preferably, the wires should be held with pliers, which act

as a heat shunt. The end with the band on it should be connected to  $R_{18}$  ( $470k\Omega$ ). When assembled, the tagboard should be bolted to the chassis in the position indicated in Fig. 16.

Pins 2 and 7 on the valveholder for  $V_3$  should be connected to the centre spigot. From pin 2, leads should be taken to pin 2 on the supply input socket and to  $R_{17}$  ( $1k\Omega$ ) on Tagboard No. 3. From pin 7 a lead should be connected to the nearer end of  $C_{13}$  ( $18pF$ ) and continued from this point through the grommet to pin 2 on the valveholder for  $V_4$  (EM81).

A wire for the h.t. supply to the equaliser stage of the amplifier should be connected to the junction of resistors  $R_9$  ( $390k\Omega$ ) and  $R_{10}$  ( $18k\Omega$ ) on Tagboard No. 2, and should be taken to the near end of the resistor  $R_{14}$  ( $27k\Omega$ ) on Tagboard No. 3 and continued from  $R_{14}$  to the free end of  $R_7$  ( $33k\Omega$ ) on Tagboard No. 1. Pin 4 on the supply input plug should be joined to position 6 on switch  $SA_8$ . From this point, the connection should be taken to position 2 on section  $SA_6$ .

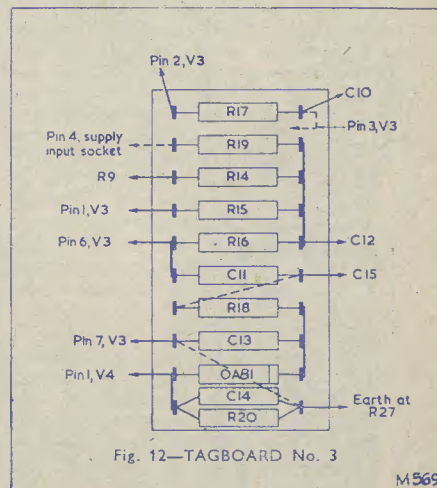The end of  $R_{17}$  ( $1k\Omega$ ) farthest from the  $V_3$  holder should be connected to pin 3 on the holder, and the connection should be continued to pin 8. The nearer end of  $R_{15}$  ( $220k\Omega$ ) should be connected to pin 1 and  $C_{10}$  ( $0.5\mu F$ ) should be connected between pin 1 and the remote end of  $R_{17}$ .



The junction of  $R_{16}$  ( $68k\Omega$ ) and  $C_{11}$  ( $0.1\mu F$ ) should be joined to pin 6 of the  $V_3$  holder. The end of the OA81 with the lettering on it should be connected through the rubber grommet to pin 1 of the EM81 valveholder.

The capacitor  $C_{12}$  ( $16\mu F$ ) should be connected between the junction of  $R_{19}$  ( $10k\Omega$ )

and  $R_{16}$  ( $68k\Omega$ ) on Tagboard No. 3 and pin 7 on the holder for  $V_3$ . The positive end of  $C_{12}$  should be joined to the junction of the resistors. The other end of  $R_{19}$  should be connected to pin 4 on the supply input socket.

To complete the assembly of this stage, pin 9 on the valveholder should be connected to the centre tag of the volume control  $RV_{13}$ , the wire passing under the internal screen c.

*To be concluded*

## RADIO MISCELLANY *continued from page 351*

superimposed on a very heavy background.

Unfortunately I have had no opportunity of hearing this record yet, but surely after such treatment any imperfection in the reproducing equipment should quickly be revealed.

### Junk, First-class

On several recent occasions this column has made references to the rebuilding and modernising of old or discarded receivers. We agreed there was a lot of fun in it. So does a correspondent, but he cynically adds "and by the time you have hunted down and bought all the components of suitable dimensions to fit in the existing gaps on the old chassis, it doesn't cost you much more than about twice the amount needed to build a new set."

The question of cost, I suppose, depends on the depth of one's junk box, and talking

of junk boxes reminds me of a friend who keeps two! One is marked "Junk" and the other is labelled "Bits." The bits box holds all the odds and ends likely to be needed in the early future, but the stuff in the junk box is a collection of items for which there is no foreseeable use—speaker magnets, screening cans, broken down soldering irons and burnt-out transformers. Hence, if he has a pair of i.f. transformers they are carefully taped together and gently stored in the bits box, but an odd single i.f.t. would be simply slung in the junk container.

I thought I had been systematic since my last spring-clean, but I haven't yet got round to classifying my junk into first and second class. However, in future when referring to junk I will try to remember to specify the grade just in case this sort of thing is general. (Personally, I scrap "junk," and keep "soares."—ED.)

## EXPERIMENTAL CHASSIS CONSTRUCTION *continued from page 355*

beyond the stage concerned are simply unbolted from the girders and moved an appropriate distance along the framework and bolted back again, leaving a space for the new stage to be inserted. If it is foreseen at the outset of construction what modifications will be made, gaps may be left between the chassis for the new stage to be inserted, provided instability is not likely to arise from the length of wires bridging the gap.

Clearly, these ideas may be very much modified, particularly as regards dimensions, to the readers' own applications and opinions, and this article is only intended as a pointer. The chassis may be put into several decks if desired, as shown in Fig. 3. Aluminium girders, of course, would be more suitable, but the writer has not been able to find any

standard types which are reasonably available. In fact, it should be pointed out that there may well be several other firms which manufacture girders, etc., just as suitable, or more so, than the Meccano ones described here. The latter, however, may easily be obtained separately from many shops.

It might be said that this form of construction lacks aesthetic value; but since it was designed for experimental work, it seems reasonable to consider this aspect of secondary importance. The requirements of rigidity and reasonable safety are fulfilled, provided the chassis are isolated from the mains, and that no bare h.t. wires, etc., are exposed. To ensure the latter, it may be necessary to make a box of five sides into which the whole may slide.



The Editor and Staff of  
**The RADIO CONSTRUCTOR**  
 wish all their many friends and readers  
**A HAPPY CHRISTMAS**



# MODELS FOR RADIO CONTROL

## THE "WAVEMASTER" KIT

Part 5


by Raymond F. Stock

### Construction

HAVING CONSIDERED THE VARIOUS POINTS relating to the model as a whole, and after making any necessary modifications to components, construction may be started.

a plank of wood at least 12in by 36in by approx.  $\frac{3}{4}$ in as a building board. No doubt many constructors would use the top of the bench directly for this purpose, but the surface must be truly flat.

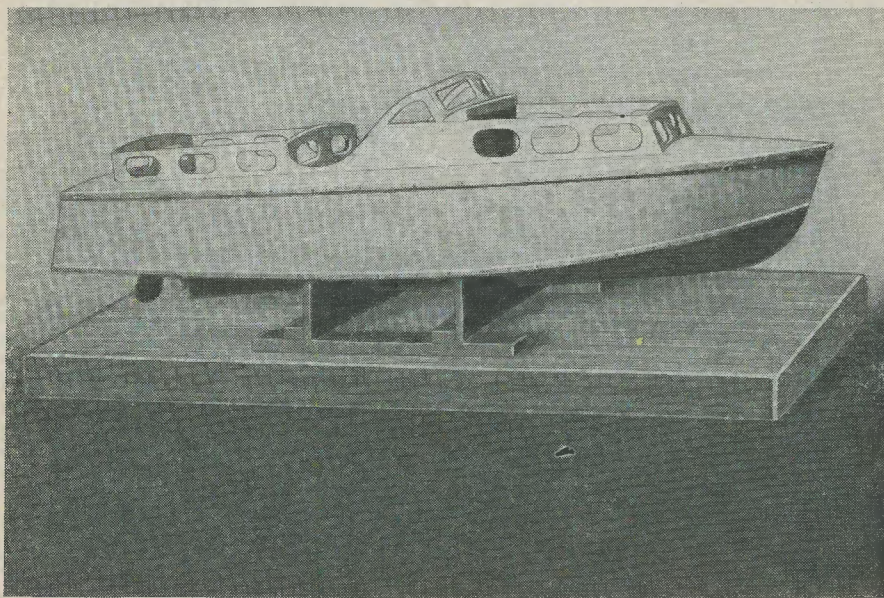Before starting, it is desirable to clean up



The hull nearly complete

In addition to the materials provided, it is necessary to have some pieces of scrap wood (about four yards of  $\frac{1}{2}$ in square is ideal) for supporting the bulkheads while building, and

some of the components where the cutting process has left ragged edges. This will facilitate assembly, but care must be taken not to enlarge slots and so spoil the fit.

The "Wavemaster" is a simple design and the instructions are clear enough to enable even a beginner to produce an excellent model. The following notes, however, may be useful to intending constructors who are less familiar with glue than with solder.

For the sake of authenticity, a complete model was made up by a constructor having no previous experience of modelling. The kit was supplied by the manufacturers in standard form, and no additional information or supervision was applied. Total construction time proved to be thirty hours.

The constructor made up a building board by pinning a sheet of 5-ply wood to a rectangular frame (36in x 15in x 2in) having two transverse supports across it, spaced 12in apart.


The following tools were to hand, and found useful, though were not all essential: half-round smooth file; 8in smooth flat file;  $\frac{1}{2}$ in chisel; sharp penknife;  $\frac{1}{4}$ in round file; small hammer; small frame saw; hand vice;  $\frac{1}{8}$ in and  $\frac{1}{4}$ in drills; one sheet each of numbers 0 and 2 sandpaper; and an old compass used as a scriber.

The sequence of operations described with the kit was followed closely, and in general no difficulty was experienced in making good joints.

Fitting the keel and keel blocks to the bulkheads was a simple matter of careful fitting, but the next stage, fitting the stringers, was thought to be potentially tricky. Consequently, the constructor felt it wise to preset the sharper curves by soaking the strips and teasing to shape over a low gas flame. The curve was maintained and fixed by allowing the strips to dry out in a curved jig made by hammering small nails into a board, thus trapping the strip in the required curve. The instructions note that the use of two pieces  $\frac{1}{2}$ in x  $\frac{1}{4}$ in obviates this process, but the additional trouble expended was thought to be worth while. It is essential to allow any dampness to dry thoroughly before glueing, particularly when a cement is used.

The stringers were shaped to the hull, by cautious use of a sharp knife and of sandpaper wrapped around a curved block, before the framework was sanded overall.

When the framework was tacked down

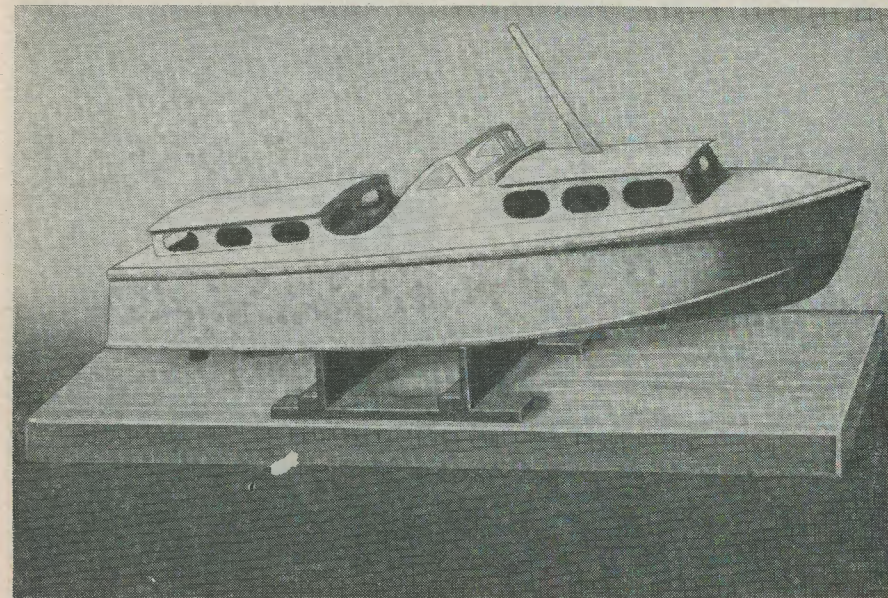

The completed model ready for painting

It was decided to use Durofix as an adhesive (though several other types of glue would have sufficed); about 7 or 8 ozs of this cement were used in all.

again to the building board, it was thought to be a good policy to pack up the deck surfaces with thin card; the side skins, when fitted, could then be butted hard against the



building board and finally sanded off flush with the deck structure. The thin card ensured that the skins would not lie below the top of the deck stringers, and would, if anything, be slightly proud of them.

After the side skins were firmly attached and the cement dry, great care was taken to trim off the excess (at the forward end particularly), level with the face of the chine stringer and at the correct angle to ensure a good surface for attachment of the bottom skins.

Fitting the bottom skin panels was the only difficult part. In general, the method described in the instructions was adopted, but the initial approximate curve was formed by soaking, heating and drying to shape rather than simply heating as described.

Forward, the bottom panels were overlapped (as shown on the plans) on top of the side skins, but the overlap was cut away at an angle in the vicinity of B.2 as soon as the greater angle through which the ply needed to be bent began to cause it to wrinkle and to crack.

After the cement was thoroughly dry the hull was well sandpapered, and replaced on the building board while the chine rubbing strakes were applied. These were pre-bent by soaking and heating, as for the stringers.

The stern tube was fitted as described in the instructions, a large amount of cement being used around all junctions between the tube and the surrounding structure.

The cabin produced no problems and was made up entirely according to the instructions. After the deck structure was added the deck rubbing strakes were bent by soaking, as before, then glued into position. After the deck and wash strakes were fixed, the deck surface inside the latter was scribed with indented lines to represent planking.

Two coats of clear dope were given inside and outside to waterproof the hull. Several coats of paint were then applied, using a  $\frac{1}{2}$  in flat and a  $\frac{1}{4}$  in round camel hair brush.

After completion of the painting, the celluloid was cut and cemented inside the window areas. The handrails were sanded, varnished and fixed last of all.

The main lessons learned from construction were the need for care when cutting parts to fit accurately together, and the desirability of doing this by filing and sanding rather than by indiscriminate cutting. Surfaces to be glued should be carefully prepared to lie close together—the cement should not be used to fill large cracks between components. Nevertheless, plenty of cement should be applied to both parts of a joint, and the excess squeezed out as the parts come together.


The finished hull has a good appearance, considerable strength, and plenty of room for equipment. It is, in fact, a thoroughly practical model and one which we have no doubt could be made up successfully by any radio amateur.

cap is of phenolic insulation, the inner plated contacts being mounted on paxolin. The jack is likewise mounted on paxolin, this having two sturdy eyeletted holes for fixing purposes. The Bulgin type numbers for these are: plug P523 and jack J33. They are available to readers at 1s. 3d. and 9d. respectively.

Kendall & Mousley Ltd., 18 Melville Road, Edgbaston, Birmingham 16, have now commenced a new ceramic switch service. A wide variety of both paxolin and ceramic Yaxley type switches are now being produced to readers' requirements. The maximum length of switch which is at present being produced is  $8\frac{1}{2}$  in from clicker plate to the end of the flatter shaft.

Constructors often find that the stock pattern of switch has either too many or too few contacts, poles, or contacts that cannot be earthed when not required in circuit. Kendall & Mousley Ltd. now issue a leaflet setting out specimen charges and details of the service. The samples submitted to us were of first-class workmanship, sturdy and robust. All contacts were of the double type with heavy plated tag connections.

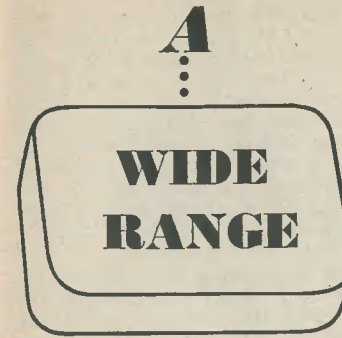Readers requiring that special Yaxley-type switch are advised to get in touch with the above firm.



## Audio Oscillator

By W. E. WOODHEAD

IN THE COURSE OF DESIGN AND EXPERIMENTAL work, the need for a signal generator covering the audio frequencies must be considered sooner or later. Several designs have been produced in the past, and described in a number of technical and practical publications.

The instrument to be described in this article is a compact piece of apparatus and will not take up too much space on the average experimenter's work bench. It will be noticed that the generator does not carry its own mains supply, but is fed from an outside source. It has been found in the writer's experience that one power pack can supply a number of pieces of equipment; and where this can be done, represents an overall economy in the setting up of a small laboratory.

Many people stress the necessity of instruments incorporating their own power supply, and in some cases stabilisation of that supply is essential for the maintenance of accuracy in calibration.

In the majority of cases, however, small variations in supply are not important and one power pack will serve a number of pieces of test gear. The essential features of the present design are as follows:—

1. Purity of sine wave.
2. Stability and constant output amplitude.
3. Wide range.
4. Facilities for square waves.
5. Reasonable cost.

The first consideration was the type of oscillator to use. The B.F.O., or Beat Frequency Oscillator, was rejected as a great deal of careful design is necessary to get the apparatus to work well. The two oscillator circuits are working at radio frequency, and any stray coupling between the two would lead to "pulling" in, particularly as they have

similar characteristics. Greater freedom from this pulling in or locking together can be achieved by a push-pull detector system, but this adds to the complexity and cost of the equipment.

The phase shift oscillator works well on certain conditions but operation is confined, in the writer's experience, to the use of particular valves of high slope and certain other characteristics.

The final choice was a Wien Bridge controlled R.C. Oscillator which fulfilled most of the conditions required. Another point which had to be settled was whether the variable frequency control should be capacitive or resistive. Variable capacity has the required smoothness of control, but to keep the resistive part of the bridge arms within reasonable limits the condenser has to be large in value. The usual method is to use a four-gang 500pF unit, and to parallel the sections to make two capacitors of 1,000pF each. This makes a bulky item, and even this value requires a resistive component of 10 megohms on the lowest frequency range.

In addition to using excessive space, the whole R.C. combination requires careful screening to avoid hum pickup.

Finally, variable resistance was adopted, a two-gang component being compact and having the advantage of giving a dial rotation of 300° against the 180° of the capacitor.

Large wirewound two-gang potentiometers with log characteristics can be obtained at a price, but the writer has used a carbon element component supplied by the Reliance Manufacturing Co., which after a long period of use continues to give complete satisfaction.

Although most textbooks explain the Wien Bridge in principle, it would not be out of place to analyse, for the benefit of beginners, the theory of the circuit as applied to this instrument.

### TRADE REVIEW

A. F. Bulgin & Co. Ltd., Bye-Pass Road, Barking, Essex, have sent us samples of their type J.30 Miniature Jack and the P.519 Miniature Jack-Plug. This is a new 2-pole concentric jack and jack plug, for miniature uses. The plug has axial cable exit, screw-on phenolic cover, plated members and internal solder tags for the connections. The jack also has phenolic insulation, nickel-silver contacts and tags. One pole is live to the fixing bush and a third contact mates with the tip-contact when the plug is removed. Technical specification—for 1A max, 50V max, 10W max, loaded and connected. Maximum test voltage 250V.


These small precision made and highly finished components would find many ready uses, e.g. for 2-pole audio, in or out; for telephones; portable bells; or test points, etc. They would be absolutely ideal for modern miniature equipment.

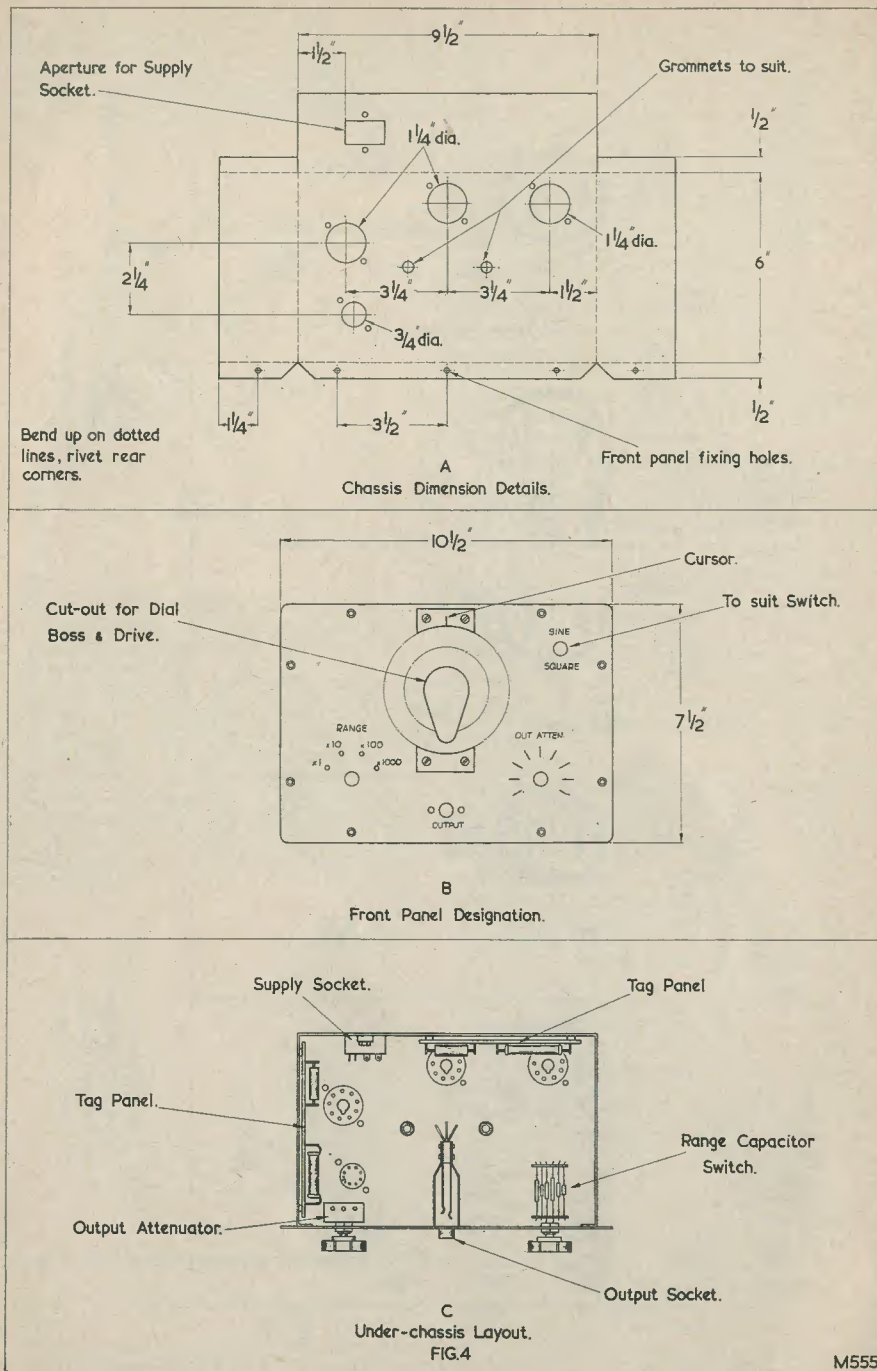R. Fagelston, 46 Hardwicke Road, London, N.13, are currently offering, among their many other ranges, a Bulgin "little brother" version of the above jack-plug and jack. Somewhat less robust than the above, the plug has no provision for axial outlet but is designed for two-wire exit only. The plug










M555

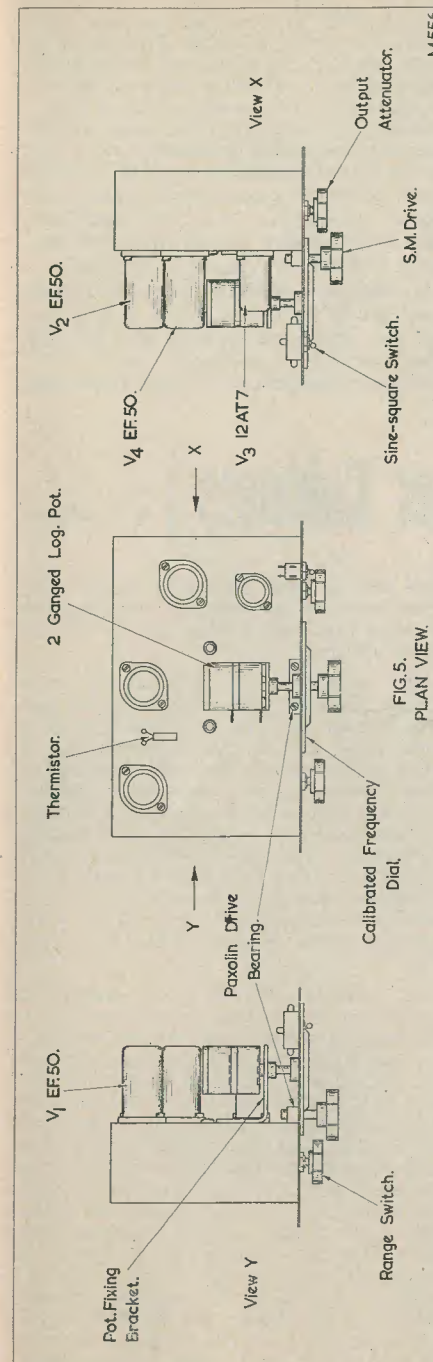

M556

14-2,000 c/s. Any higher frequency than this is undesirable, and is unnecessary in any case for audio work. Reference to Fig. 2 will show waveforms for various frequencies.

Sine wave coverage is 14 c/s to 200 kc/s, this being obtained by four overlapping ranges. The coarse range switch is marked in multiples of 10 and is used in conjunction with a single frequency scale.

To provide an output of low impedance a cathode follower buffer stage was inserted between the oscillator and output terminal. In addition, to block d.c. from the output a large capacitor was fitted between  $R_k$  of  $V_4$  and a load resistance of  $22k\Omega$ . This load resistor can be replaced by a calibrated attenuator if so desired. It should be mentioned that valves 1, 2 and 4 used in the generator are the familiar and easily obtained EF50. These give good results in the present circuit and it would be difficult to find a more suitable component. The other valve concerned is that which provides the square waves, and satisfactory results were obtained by the use of a miniature 12AT7.

Reference to Figs. 3, 4 and 5 will give the necessary information regarding the construction of mechanical details. As most constructors have their own particular preference as to the final finish and site of an item of test gear, only the main points of interest will be considered.

The chassis is the conventional box type which is screwed to the front panel. This forms an integral unit which may be fitted into almost any type of casing.

The case and slow motion dial used in the writer's instrument was salvaged from surplus war material. These items fitted nicely into the constructional plan, although it meant that the dial would have to be re-calibrated.

It is well worth while paying a visit to the local war surplus dealer to see what he has to offer in hardware before being committed to unnecessary work and expense. The wiring and general layout follows no particular plan, and anyone who wishes to make alterations may do so providing component values are not altered.

The oscillator circuit wiring should be rigid and as short as possible. Failure to observe this point will possibly result in stray capacitances altering calibration, especially on the higher frequency ranges.

It must be admitted that frequency calibration was carried out with the aid of an accurate decade oscillator. While being most convenient it is by no means essential, and was in any case double checked by the oscilloscope method.

The 50 cycle mains are a very good standard of accuracy and if the timebase of the



oscilloscope is locked to this frequency it is possible, with care, to obtain a number of calibration points on scale 2 (140–2,000 c/s).

If the timebase speed is increased by a known multiple of 50 cycles, while keeping the scan locked to the mains, it will be found that if the switched capacitors are exact multiples of 10 the same marks on the scale for Range 2 should coincide with 10 times the frequency of Range 3. If this does not occur, then the capacitors for Range 3 should be trimmed until the variable scale suits both Ranges 2 and 3.

Plots on log paper can be made of these two ranges and with the aid of these and the oscilloscope, Range 1 capacitors can be adjusted to fit the frequency scale. Range 4

(14 kc/s–200 kc/s) capacitors will need setting for every individual instrument, as strays will alter the calibration considerably. They can be set to suit a point on the low frequency end of the scale and left at that.

Frequency accuracy on this range was not considered absolutely necessary, and if one point was fairly accurate the rest of the range would be within a reasonable tolerance. It should be pointed out that amplitude stability falls away slightly after 100 kc/s, and is 2dB down at the end of the scale.

In conclusion, it is felt that this instrument is well worth the time spent on its construction and is an asset to those who take full interest in their experimental work.

## MISCELLANEOUS

# Inexpensive Loudspeaker Cabinets

By  
E. G. WILSON

IT IS OFTEN POSSIBLE TO OBTAIN OLD WIRELESS cabinets at very small cost, and many experimenters will have collected some over the years. For a small outlay these can be modified to house an extension speaker or one of the speakers of a multi-speaker system (Fig. 2 is especially suited to this purpose and looks well standing on the top of the main cabinet).

Before commencing any work, select a cabinet which is strongly made, with the veneer in good condition and not peeling. It is advantageous if the speaker aperture is at the top. Cut the cabinet as suggested in the diagrams, using a sharp tenon saw for the external cuts and a keyhole saw for the speaker aperture. The actual size of the aperture will, of course, depend on the size of the cabinet and the personal taste of the constructor but, as a general guide, dimension "B" should be about 2in or 1/5th of the aperture width, dimension "C" about 1 1/2in and "D" about 2 1/2in. Dimension "A" will depend on the depth of the speaker to be housed, but 4in is normally adequate. These dimensions retain sufficient strength in the cabinet and also give a result that is pleasing to the eye.


Construct a base and fit this to the new cabinet using wood blocks glued inside (the old base can usually be modified for use quite simply). A couple of strips of foamed plastic can be glued to the base to avoid scratching any polished surface on which the cabinet may stand.

Finish off by rubbing the whole cabinet down with fine sandpaper and varnishing with "Valspar" stain. This latter should be

done with a good quality brush in a dry atmosphere, and extreme care must be taken to avoid any dust getting on the varnish before it is dry.

The speaker should be mounted on a suitable sized baffle, covered with silk and fitted behind the aperture. Alternatively, a metal grille can be used although this is rather more expensive than silk. If a sloping front cabinet has been constructed, the use of a metal grille is not recommended as many of these consist of a series of holes sloping downwards. The slope at the front of the cabinet means that these holes are seen in the wrong perspective and the brilliant metallic colour expected appears drab. In the worst cases the speaker is often visible through the grille.

An effective alternative to cutting an aperture for the speaker is shown in Fig. 3. This consists of a piece of 1/4in thick wood cut to a size equivalent to the aperture required and covered with silk. Before fitting the silk, four 2BA countersunk screws and nuts are fitted at the corners and several 1in holes cut in the wood. The whole assembly is fitted to the cabinet by the four 2BA screws. Clearance holes for the 2BA nuts are required in the cabinet and oversize washers are necessary to clamp the assembly to the cabinet. Full details are shown in Fig. 3. When this method is used it will not normally be necessary to alter the original speaker aperture in the cabinet, and in many cases it will be possible to fit the speaker directly to the cabinet without the need for providing a separate baffle.

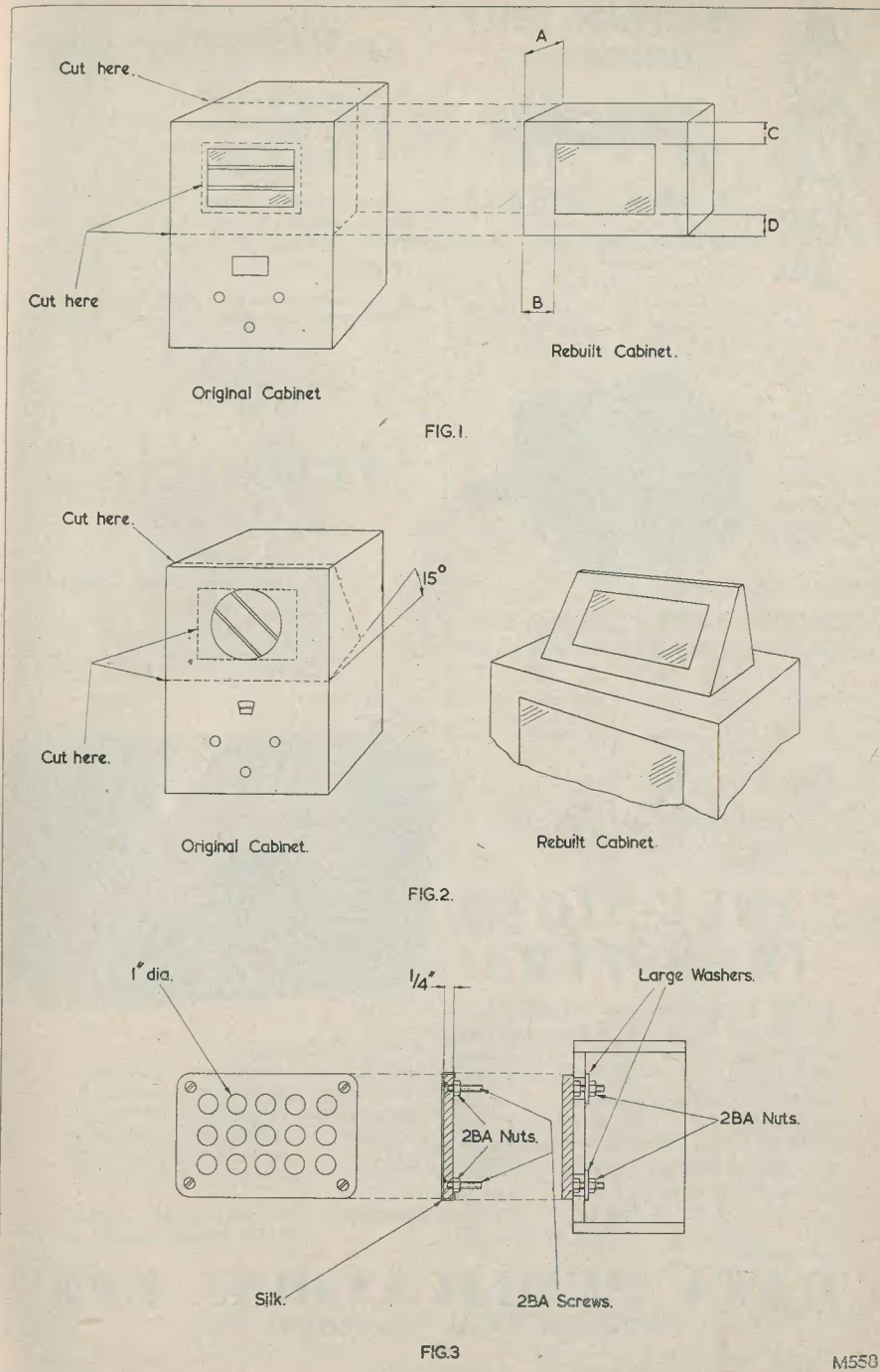





## PRECISION - BUILT COMPONENTS


# JACKSON

### 'O' GANG CONDENSER

Miniature model in 1 or 2 gang, capacities up to 365pF swing, front area  $1\frac{1}{8}'' \times 1\frac{1}{2}''$  including sweep of vanes, length: 1 gang  $1''$ , 2 gang  $1\frac{3}{4}''$ , spindle  $\frac{1}{8}''$  dia. x  $\frac{3}{8}''$  long. Aluminium vanes, cadmium plated steel chassis

1 gang 7/6  
2 gang 11/6

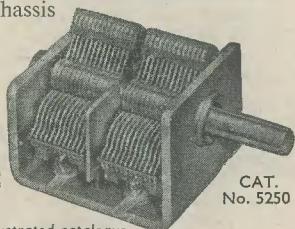It's Reliable  
If It's Made  
By JACKSONS



CAT.  
No. 5250

Please write for illustrated catalogue

**JACKSON BROS. (London) Ltd**  
Kingsway · Waddon · Surrey Phone CR0ydon 2754/5

## Ask "ARTHURS" First

NOTE NEW ADDRESS AT  
125 Tottenham Court Road  
London WCI  
Close to Warren Street Station

You will have the same service and obtain all your requirements in Radio Components, Electrical Goods, Accessories and Television as previously.

Test Instruments in stock include Avo, Advance, Cossor and Taylor. List on request

VALVE MANUALS AVAILABLE  
Mullard 10/6 Brimar No. 7 6/-  
Osram Part 1, 2nd Edition 7/6  
Post and packing 9d. each extra.

# Arthurs first

Est.  
1919

Proprietors ARTHUR GRAY LTD

Gray House  
125 Tottenham Court Road  
London WCI

Telephone EUSton 5802/3/4

For a really  
professional finish  
use . . .

## PANEL-SIGNS TRANSFERS

### Set No. 1: Receivers and Amplifiers

Five sheets  $8\frac{1}{2}'' \times 5\frac{1}{2}''$  containing one large scale, twelve control panels and white wording. 3s. 6d. postage 2d.

### Set No. 2: Test Equipment

Five sheets  $8\frac{1}{2}'' \times 5\frac{1}{2}''$  containing two medium scales, twelve control panels and white wording. 3s. 6d. postage 2d.

### Set No. 4: Wording

As set No. 3, but in black. 3s. 6d. postage 2d.

### Set No. 3: Wording

Wording for Receivers, Amplifiers, Transmitters, Test Equipment and other Radio Apparatus, and Station Names. Five sheets, over 750 words and symbols. White. 3s. 6d. postage 2d.

Panel-Signs Transfers Fixing Varnish 1s. per bottle . postage 6d.


Published by

# DATA PUBLICATIONS LTD

57 MAIDA VALE · LONDON W9

Telephone CUNningham 6141 (2 lines)


Telegrams Databux London

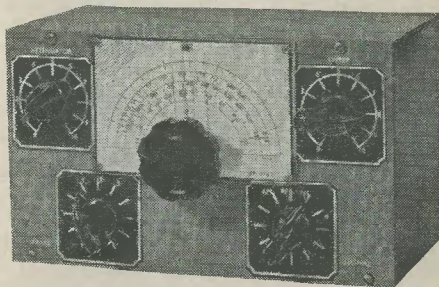

# BRIMAR 6T8
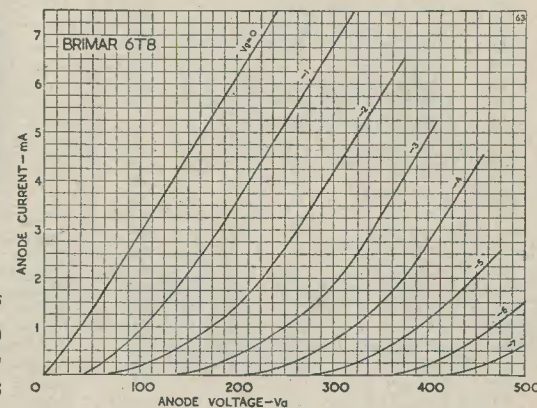
## TRIPLE DIODE TRIODE

The Brimar 6T8 is a triple-diode-triode in which one diode has a separate cathode. The triode section has a high amplification factor making the valve suitable for use in AM/FM receivers in the demodulation and first stage audio circuits. The diodes may be used in series shunt limiter circuits, for example in the audio sections of television and communications receivers, followed again by the triode section for AF amplification.



Near Equivalents

EABC80  
DH719  
6AK8

Typical Triode Operating Characteristics as an R.C. coupled amplifier

Heater Voltage	6.3 volts	Heater Current	0.45 amp
Anode Supply Voltage	250	250 volts	
Anode Load Resistor	0.25	0.25 megohms	
Grid Resistor	1.0	10 megohms	
Cathode Bias Resistor	3	0 kilohms	
Peak Output Voltage	43	40 volts	
Stage Gain (for 24V peak to peak output)	42	42	
Distortion (for 24V peak to peak output)	1	5%	

Cut this out for further reference or write to the Publicity Department at Footscray for a data sheet




Standard Telephones and Cables Limited  
(Reg. Office 63 Aldwych London WC2)

FOOTSCRAY SIDCUP KENT

Telephone 3333



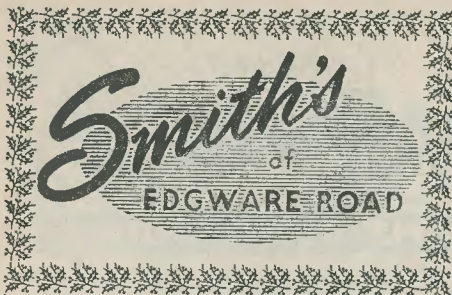

The  
**Cooper-Smith**  
**"Prodigy"**  
High Fidelity Amplifier

(As described in October and November issues)

**COMPONENT PRICE LIST**

Buy direct from the Designers to ensure 100% results

All enquiries promptly dealt with

R1	10MΩ high stability 1/2W	...	6d	C6, 12, 18 & 19	0.1μF 350V paper	each	9d.
R2	390kΩ high stability 1/2W	...	6d.	C7, 8, 15 & 17	50μF 12V electrolytic	each	1/7
R3	680kΩ high stability 1/2W	...	6d.	C9	560pF silver mica 20%	...	7d.
R4	12MΩ 1/2W	...	3d.	C10	8,000pF (2 x 4,000pF) silver mica 20%	...	2/2
R5	390kΩ high stability 1/2W	...	6d.	C11 & 22	50-50μF 350V electrolytic	...	8/6
R6	180kΩ high stability 1/2W	...	6d.	C13	2,000pF silver mica 20%	...	9d.
R7	47kΩ 1/2W	...	3d.	C14	0.02μF moldseal	...	1/-
R8	2.2MΩ 1/2W	...	3d.	C16	50μF 25V electrolytic	...	1/10
R9	1.8kΩ high stability 1/2W	...	6d.	C20	8μF 350V electrolytic	...	2/6
R10	100kΩ high stability 1/2W	...	6d.	C21	3,000pF silver mica 20%	...	1/-
R11	47kΩ high stability 1/2W	...	6d.	V1	12AX7 (inc. P.T.)	...	18/11
R12	100kΩ 1/2W	...	4d.	V2 & 3	ECL82 (inc. P.T.)	...	each 22/4
R13	1.2kΩ high stability 1/2W	...	6d.	V4	EZ81 (inc. P.T.)	...	11/6
R14	47kΩ 1/2W	...	3d.	(No Purchase Tax is payable on the valves when included in a kit)			
R15	39kΩ 1/2W	...	3d.	Mains Transformer (T1), A.E.E.	...	...	51/8
R16	68kΩ 1/2W	...	4d.	Output Transformer (T2), A.E.E.	...	...	49/6
R17	6.8kΩ 1/2W	...	4d.	Switch, 2-pole 4-way (S1, S2)	...	...	10/6
R18 & 23	*100kΩ 1/2W	pair	1/4	Voltage selector	...	...	1/6
R19	270kΩ 1/2W	...	3d.	Mains plug and socket	...	...	3/9
R20	1.2kΩ 1/2W	...	3d.	Output plug and socket 5-pin	...	...	9d.
R21	100kΩ 1/2W	...	3d.	Power plug and socket 4-pin	...	...	9d.
R22	1.2kΩ 1/2W	...	3d.	Motor plug and socket 2-pin	...	...	7 1/2d.
R24	390Ω wire wound 5W	...	2/-	Coaxial sockets (3)	...	each	1/3
R25	2.2kΩ 1W	...	6d.	Coaxial plug	...	...	1/3
R26	10kΩ 1/2W	...	3d.	Fuse, 2A, and holder	...	...	4/-
R27, 28 & 32	*1MΩ 1/2W	set	1/9	Valveholder, with skirt	...	...	3/10
R29	10kΩ 1/2W	...	3d.	Valveholder, paxolin (3)	...	each	6d.
R30 & 31	47Ω 1/2W	pair	6d.	Group board, 26-way, 1 blank	...	...	4/6
R33	680Ω 1/2W	...	3d.	Panel light holder and bulb	...	...	1/3
R34	(See note on power output)	...	1/6	Knobs, pointer (4)	...	set	5/-
*Matched to within 5%				Nuts, screws, solder tags	...	...	4/-
VR1 & VR2	250kΩ	...	each 3/6	Wire, flex, sleeving	...	pkt.	2/-
VR3	250kΩ with switch	...	4/6	Chassis, punched, bronze finish	...	...	17/6
C1	16μF 275V electrolytic	...	2/6	Base plate, with screws	...	...	2/6
C2	470pF silver mica 5%	...	7d.	Grommets (8)	...	...	6d.
C3	270pF silver mica 5%	...	6d.	Control Panel	...	...	12/6
C4 & 5	68pF silver mica 5%	...	pair 1/-	TOTAL	...	...	£15.18.0

INCLUSIVE PRICE FOR COMPLETE KIT ... £13. 7. 6

LABORATORY-BUILT AND TESTED ... £16. 16. 0

Carriage free in U.K.

Send 2/8 for Radio Reprint No. 10 which gives full instructions, additional material and price list of parts

**H. L. SMITH & CO LTD**

287/9 EDGWARE ROAD . LONDON W2 . Telephone Paddington 5891 & 7595


Officially  
recommended  
by Collaro

TAPE  
RECORDER  
COILS



Type Price  
Bias Osc. QT9 7/6  
Bias Filter QT6 7/6  
Treble Boost QT7 27/6  
Bias osc. for push-pull circuit 7/6

Also recommended types for other makes

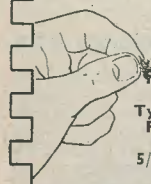

New

SUB-MINIATURE  
HIGH Q COIL  
RANGE

Type S.M.  
Ferrite  
Core  
5/- retail

For  
SUPERHET-TRF  
TRANSISTOR  
CIRCUITS


**OSMOR**

(Dept.29) 418 Brighton Rd.  
South Croydon · Surrey  
Telephone Croydon 5148/9

COILS  
for the  
**NEW MULLARD**

**TAPE  
AMPLIFIER**  
EXACTLY TO  
SPECIFICATION

**RADIOSETTE**

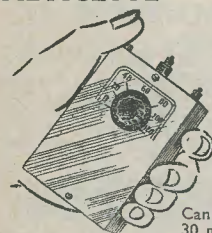


The ideal low cost transistor pocket radio for the beginner. The circuit utilises the new R.C.S VARILoop-STICK transistor coil. A specially designed miniature .0004 tuning condenser permits the set to be in a case which fits the palm of your hand.

Can be built in 30 minutes **30/-**

All components are sold separately, full construction data including plan of parts, 2/-

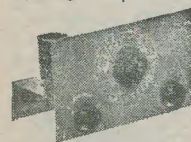**ALL-WAVE RADIO 35/-**

Ideal for the beginner or for those requiring a simple stand-by receiver



This 1 valve S.W. receiver can be built for 35/- from our list of components, which can be purchased separately. It includes valve and 1 coil covering 20-40 metres. Provision is made to increase to 2 or 3 valves if required, and all components are colour-coded so that the beginner can build this set quite easily. Send 2/- for specification, wiring diagram, layout and price list.

Postage: Under 10/-, 9d. Under 40/-, 1/6  
Over 40/-, post free

**R.C.S. PRODUCTS (RADIO) LTD**

11 Oliver Road London E17 Mail Order only

**The Teletron  
TRANSIDYNE**

Portable 6-Transistor Superhet  
Receiver with printed circuit

Circuit diagram with instructions available from most advertisers in this magazine, 1/- post free

**SAM MOZER LTD**

288 Hedge Lane London N13

Telephone PALmers Green 1748

Sole Distributors to the Trade



## QUICK EFFICIENT UP-TO-DATE COMPONENT SERVICE!

### Pocket Valve Radio

Anyone can build this beautiful precision Pocket Radio in 1 hour. No knowledge whatever needed, our simple, pictorial plans take you step by step!

You can't go wrong. Remarkably sensitive—covers all medium waves incl. Luxembourg, Home, Light. Size only 2" x 3" x 5/8".


Not a toy! but a real valve radio! Uses self-contained battery and is a really personal-phone, pocket radio with detachable rod aerial. Ideal for bedroom, garden, etc. We can supply all the parts necessary, including case, screws, easy step-by-step plans for the Special Price of 37/6 (plus 2/6 post, etc.). **BUILD YOURS NOW!** (All parts sold separately.) Priced parts list, etc., 1/9. Big demand certain—send today! C.O.D. 2/- extra.

Can be Built for 37/6



Can be Built for

47/6

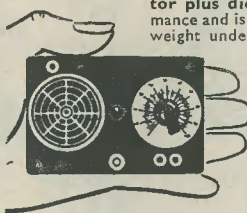

### TWO TRANSISTOR POCKET SET

Build the "Sky Pixie" Vest-pocket two-transistor plus diode radio which gives a superb performance and is highly sensitive. Size only 4 1/2" x 3 1/4" x 7/8" weight under 7oz!—yet it is a three-stage receiver covering all medium waves, working entirely off a tiny "pen-light" battery. Every part tested before despatch! **Special step-by-step plans for absolute beginners. Total building cost including case, transistors, etc.—everything down to the last nut and bolt—ONLY 47/6 with plans.** Postage, etc., 2/-, C.O.D. 2/- extra. (Parts sold separately. Priced parts list and plans 1/6.) **RUSH YOUR ORDER TODAY!**

### PRINTED CIRCUIT POCKET SET

Build this 3-transistor pocket radio... Printed Circuit Version! The "Companion" is comparable in sensitivity to a three-valve battery set; it is exceptionally small in size (4 1/2" x 3" x 1 1/2") and is a self-contained pocket radio that does not need aerial or earth. It has built-in speaker and covers medium and long waves. This unique little set can be built for only 97/6, everything included! (plus post and packing 2/6). All parts sold separately. Price list, etc., 6d.

## CONCORD ELECTRONICS

(DEPT. RC2)

69 PRESTON STREET  
BRIGHTON 1



### CONSTRUCTOR CHASSIS SERVICE

With our products the amateur can obtain that professional look

MULLARD "510" ready punched (except transformer holes) including base plate and alternative rectifier plate	18/9
Postage and packing	1/6
MULLARD "TYPE C" TAPE AMPLIFIER ready punched to designer's specification with all screws and brackets	29/6
Postage and packing	1/6
Power Pack Chassis	11/-
Postage and packing	1/3
Control panel, drilled, sprayed gold hammer and clearly lettered—stove-enamelled mild steel	7/-
Postage and packing	1/-
MULLARD 2-VALVE PRE-AMP, ready punched, with all screws and brackets, in aluminium	14/-
Postage and packing	1/3
Control panel, drilled, sprayed gold hammer and clearly lettered—stove-enamelled mild steel...	7/-
Postage and packing	1/-

Other well-known designs available, details on request. All above may be obtained from your usual supplier or, if any difficulty, please write to address below

Trade enquiries invited

BERON LTD 34 NAPIER ROAD BROMLEY KENT



### IN SAFETY

with AVO "PRODClips"

Patent No. 748811

Safety first every time with these patented spring-loaded AVO "Prodclips."

Cleverly designed for use as insulated prods, they are invaluable for reaching and holding test points which are difficult of access.

Post Free

15/-  
per pair

AVO LTD

Avocet House, 92-96 Vauxhall Bridge Road  
London, SW1 Victoria 3404 (9 lines)



### TELETRON MINIATURE TRANSISTOR 42/-

Superhet coil kit (as illustrated) 470 kc/s I.F. Transformers and Oscillator coil in screening cans 3/4" x 1/2" dia. Dual wave Ferrite rod aerial 5 1/2" x 1/8" dia. Designed for the TRANSIDYNE miniature superhet receiver.

Price 9d.

Descriptive folder with circuit and assembly instruction

### TELETRON TYPE FX.25 15/- each

Self-tuned, dual wave Ferrite rod aerial.



### TRANSISTOR I.F. TRANSFORMERS

High Q "potted" construction with Ferrite screw cores. Mounted in screening cans 1" x 3/8" dia., 6/6 each. Oscillator coil, 6/6. Transistor type Ferrite rod aerial for MW band, 10/-.

Selective crystal diode coil type HAX, 3/- each. Type HAX.L (for LW band), 3/6. Dual wave TRF coils, type A/HF, matched pair, 7/-, with adjustable iron dust cores.

FERRITE ROD AERIALS Wound on high permeability Ferroxcube rod. Medium wave, FRM 4" x 5/16", 8/9. Dual wave FRD, 8" x 5/16", 12/9.



Send 5d. in stamps for complete data and circuits. All types available from advertisers in this Magazine and local component stockists

THE TELETRON COMPANY LIMITED

112b Station Road . Chingford . London E4 Telephone SIL 0836

### RADIO AMATEURS . . .

get your Licence in

### Half The Usual Time!

You must be a good Morse operator! A "slap-dash" 12 w.p.m. neither satisfies the authorities, yourself, nor your operator friends. Morse operating is an exacting art unless your training is made simple and is based on sound fundamentals. For this reason, the Candler System was invented to take the "grind" out of Code tuition, turning a tricky subject into a pleasurable pursuit.

\*Send 3d. stamp for the "Book of Facts"

### CANDLER SYSTEM CO

(Dept. 55 RC) 52b Abingdon Rd London W8  
Candler System Company Denver Colorado U.S.A.

COME TO . . .

Open all day Sat.

# Burleigh's

for your "WAVEMASTER" BASIC KIT  
72/6 plus 3/6 p. & p.


We also keep in stock suitable Diesel and Electric Motors, Receivers & Kits, Actuators & Servos, Steering Mechanisms and all requirements for a first class job

BURLEIGH of Edgware Road Ltd.

303 Edgware Rd W2 Telephone PAD 8827-8-9

## PULLIN

SERIES 100 TEST SET

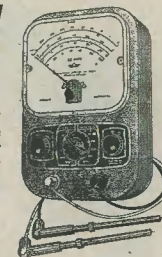

Completely restyled with new Diakon meter cover giving wide angle of vision and very clear scales. Carrying handle and very ingenious three-position stand incorporated. Printed circuit gives a rugged accurate instrument with 21 ranges and sensitivity 10,000 ohms per volt. Fully illustrated leaflet on request

CASH PRICE £12.7.6

Deposit £2.10.0 (delivery by return) and balance by nine monthly payments of £1.4.6.

### HEADPHONES

Brand new lightweight high resistance headphones. Resistance 4,000 ohms. Made to highest standard by B.T.H. and individually boxed. These are NOT ex-Govt. Made to sell at



OUR PRICE 15/- plus 1/- post


### HOME RADIO (MITCHAM) LTD

Dept. C 187 London Road Mitcham Surrey

Shop Hours 9-6.30 p.m. Weds. 9-1 p.m. MIT 3282



### FLUORESCENT LIGHTS

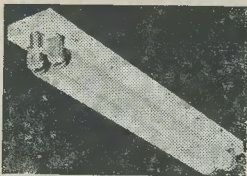

These are complete fluorescent lighting fittings. Built-in ballast and starters—stove enamelled white and ready to work. Ideal for the kitchen, over the work-bench and in similar locations.

**Single 40.** 4' 3" long, uses a 40 watt tube. **Twin 20.** Uses two 20 watt standard tubes.

Price for either type 39/6, with tubes.


**Inductor 80.** Uses one 5ft. 80W tube, 59/6 complete. Carr. and ins. up to 150 miles 5/6, up to 250 miles 7/6.

### BAND III CONVERTER

Suitable Wales, London, Midlands, North, Scotland, etc. All the parts including 2 EF80 valves, coils, fine tuner, contrast control, condensers and resistors. (Metal case available as an extra.) Price only 19/6, plus 2/6 post and ins. Data free with parts or available separately 1/6



**SPEAKER BARGAIN**

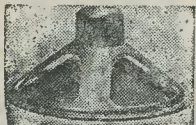

12" hi-fidelity Loudspeaker. High flux. Permanent magnet type with standard 3 ohm speech coil. Will handle up to 12 watts. Brand new by famous maker. Price 32/6, plus 3/6 post and insurance.

**TUBE TESTER & RE-ACTIVATOR**

We can supply all the main components for making this unit which will not only test Cathode Ray Tubes but also will re-activate them, supplied complete with full instructions. Price £3, plus 2/6 post and ins.


**TV SERVICE SHEETS**  
150 sheets covering the most popular post-war televisions, by leading makers—Cossor, Ekco, Ferguson, Pye, etc. £1.10.0 post free

### Build this 17" TV for 22 guineas

This is a very modern circuit and when you have completed it, it will be equal to any factory-made model. Note these special features:

- ★ Miniature valves and metal rectifier
- ★ 12 Channel turret tuner
- ★ Ferrox E.H.T. and scan coils
- ★ A.G.C. and A.V.C.

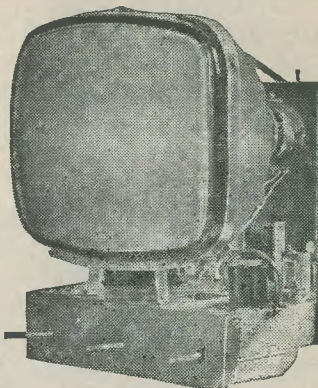Supplied in component form with all metal work prepared and supplied with pictorial layout and theoretical wiring diagram (these are available separately price 3/6). Total cost is only £23.2.0



### THIS MONTH'S SNIP

17" TV Tubes as illustrated in our copy above. Not rebuilt or regunned but brand new with 12 months guarantee. £16.10.0 or £1 deposit and 33 weekly payments of 10/-. Non-callers add 10/- carr. and insurance.


### LATEST AVO TESTMETER



Can be yours for only 10/- deposit and 19 payments of 10/- fortnightly. Like all AVO meters it is a very fine instrument: it has a sensitivity of 10,000 ohms per volt and 19 most useful ranges as follows—D.C. volts 0-1,000 (seven ranges), A.C. volts 0-1,000 (five ranges), D.C. current 0-1 amp (5 ranges), resistance 0-2 megs (2 ranges); (complete with test leads). Immediate delivery. Cash Price £9.10.0.

**FREE GIFT.**—All purchasers will receive Range Extender Scale and data which add: capacity 0-1µF in two ranges. Inductance 0-100 henrys, etc.
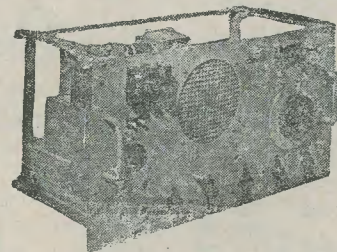
### SHORT WAVE COMMUNICATIONS RECEIVER R208 10/- DOWN



This is a super short wave receiver covering 5-30 metres (10-60 Mc/s). Uses 6 valves. Has r.f. stage, 2 i.f. stages, b.f.o., etc. Muirhead instrument drive, two internal power packs, mains and battery vibrator pack. Complete with own p.m. speaker. Provision for phones and speaker muting. Complete in metal transit case; size approx. 24" x 18" x 12"; weight 70lb. Suitable a.c. mains, 100-250 and 6 volt battery. In perfect condition, practically unused. Tested before despatch and guaranteed. Handbook free with each. Price £6.19.6, carriage and insurance 15/-. Or 10/- deposit plus 15/- carriage, and 15 fortnightly payments of 10/-.

### ELECTRONIC PRECISION EQUIPMENT LTD

For prompt attention post orders should be sent to our Eastbourne address marked Dept. 34

42/46 Windmill Hill Ruislip Middlesex Telephone RU1slip 5780 Half-day Wednesday	66 Grove Road Eastbourne, Sussex Telephone Eastbourne 6565 Half-day Saturday	29 Stroud Green Road Finsbury Park N4 Telephone ARChway 1049 Half-day Thursday	266 London Road Croydon Telephone CR0ydon 6558 Half-day Wednesday
--	---	---	--

### REPANCO HIGH GAIN COILS

<b>DUAL RANGE CRYSTAL SET COIL</b> , Type DRX1				...	...	...	...	...	...	2/6
<b>DUAL RANGE COIL</b> with Reaction, Type DRR2				...	...	...	...	...	...	4/-
<b>MATCHED PAIR DUAL RANGE T.R.F. COILS</b> , Type DRM3				...	...	...	...	...	...	8/-
<b>PAIR DUAL RANGE SUPERHET COILS</b> , Type SH4				...	...	...	...	...	...	8/-
<b>MINIATURE IRON DUST CORED COILS</b> , Type "R":										
Range	Aerial	H.F.	Osc.		Range	Aerial	H.F.	Osc.		
800-2,000m.	RA1	RHF1	RO1	} each 3/3	70-230m.	RA3	RHF3	RO3	} each 3/3	
190-550m.	RA2	RHF2	RO2		15-50m.	RA4	RHF4	RO4		
<b>FERRITE ROD AERIAL</b> , Dual Range Type FR1...				...	...	...	...	...	...	12/6
<b>FERRITE I.F. TRANSFORMERS</b> , Type MSE (465 kc/s)...				...	...	...	...	...	...	12/6
<b>STANDARD I.F. TRANSFORMERS</b> , Type TCG (465 kc/s)...				...	...	...	...	...	...	13/6

### REPANCO EASY-TO-BUILD RECEIVERS

Constructors' Envelopes of easy wiring plans, instructions and detailed price lists of components		
<b>THE HIWAYMAN</b>	Four-valve superhet Dual-range Portable using Ferrite Rod Aerial	Envelope 1/6 (post 3d.)
<b>REPANCO ONE-VALVE</b>	Beginner's Dual-range Radio Set for use with headphones	Envelope 9d. (post 3d.)
<b>REPANCO FM TUNER UNIT</b>	Using 4 EF91, 1 EB91, 1 EM80 Valves, Ratio Detector	Envelope 1/6 (post 3d.)
<b>REPANCO "THREE DEE"</b>	Dual-range Transistor Radio using 3 Transistors and Crystal Diode. Amazing loudspeaker reception from 7½ volt battery supply	Envelope 9d. (post 3d.)
<b>REPANCO "TRANSEVEN"</b>	A new 7 Transistor superhet Portable with preset station tuning using Repanco transistor components	Envelope 1/6 (post 3d.)
<b>REPANCO "MINI-7"</b>	The amazing new transistor pocket portable radio with all the technical features of a standard receiver. Seven transistors, superhet circuit, fully tunable over medium wave. Size 5½" x 3½" x 1½"	Envelope 1/6 (post 3d.)

MAIL ORDER and TRADE

**RADIO EXPERIMENTAL PRODUCTS LIMITED**  
33 MUCH PARK STREET COVENTRY  
Telephone 62572

WHOLESALE and EXPORT

**REPANCO LTD**  
O'BRIEN'S BUILDINGS  
203-269 FOLESHILL ROAD COVENTRY  
Telephone 40594

### GRAMDECK TAPE RECORDERS

Why not convert your radiogram into a Tape Recorder for Christmas? In a matter of seconds—yes, seconds—and you have a first-class tape recorder.

It runs off any make of radiogram. Just attach to the turntable at 78 speed. Any standard of tape can be used.

**DON'T HESITATE!**

BE THE ENVY OF YOUR FRIENDS

**TRANSISTORISED PRE-AMP AND UNIT CONTROL YOUR GRAMDECK**

PRICE £13.2.6

Normal Trade Discount

Full information from

**The High Fidelity Co**  
18 MELVILLE ROAD EDGBASTON BIRMINGHAM 16

### REBUILT TUBES

12" Type MW31-74	...	£6. 0.0
14" Type MW36-24/44	...	£8.10.0
17" Type MW43-64/69	...	£8. 0.0
21" Type MW53-20/80	...	£10.10.0

Customers must supply own tubes for rebuilding

### COMPLETE NEW ASSEMBLY

Purchase Tax Paid

### IMMEDIATE DELIVERY

12" Type MW31-74	...	£8. 0.0
14" Type MW36-24/44	...	£8.10.0
17" Type MW43-64/69	...	£9.10.0

We deeply regret our new schedule of prices which have been forced upon us by the new demand of purchase tax.

Carriage and insurance 10/-

Free delivery Greater London


### VIDIO REPLACEMENT COMPANY

Hales St. Deptford High St. London SE8  
Telephone TIDeway 4506

Midland Distributors

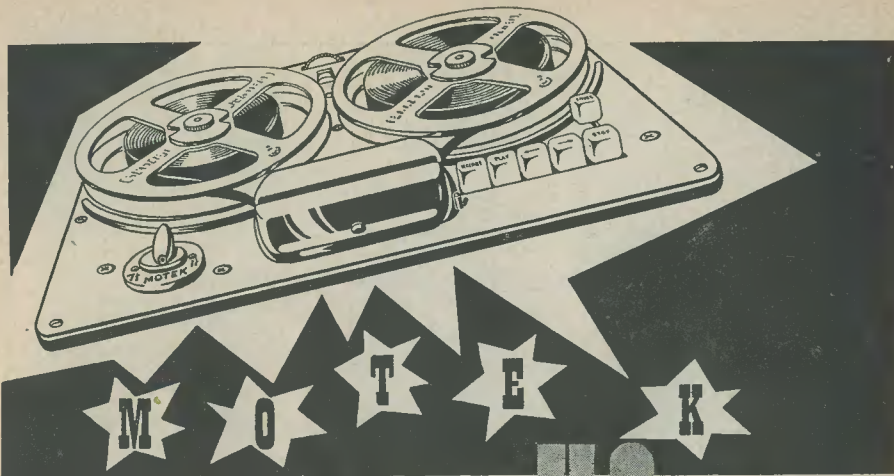**INRAXIA LIMITED**  
65 COLESHILL BIRMINGHAM 4  
Telephone Aston Cross 1829





The safety record button is only one of the features which keeps the famous MOTEK tape-deck way out ahead. It is designed especially to combine all that is best with the minimum of maintenance. Illustrated literature on request. Patents Pending.

## The Five Star Tape Deck

List 21 gns.

## MODERN TECHNIQUES

WEDMORE STREET LONDON N.19  
DHB/5894

Telephone: ARCHway 3114

★ VALVES		NEW TESTED AND GUARANTEED	
1R5	7/6	6X4	7/6
1S5	7/6	6X5G	6/-
1T4	6/-	12AH8	9/6
3S4	7/6	12AT7	7/6
3V4	8/-	12AU7	7/6
5U4G	6/-	12AX7	9/-
5Z4G	9/-	12K8GT13/6	EB91
6AM6	6/9	12K7GT	8/6
6AL5	5/6	12Q7GT	7/-
6AT6	7/6	25A6G	10/6
6BA6	8/6	25L6GT	7/6
6BE6	7/6	35Z4GT	8/6
6BR7	10/6	35L6GT	9/6
6BW6	8/6	53KU	11/6
6J5G	5/6	807	6/9
6J7GT	8/6	5763	10/6
6K7G	2/6	DAF91	7/6
6K8G	7/6	DAF96	9/-
6Q7GT	8/6	DF91	7/6
6SL7GT	8/-	DF96	9/-
6SN7GT	8/6	DH76	8/6
6V6G	7/6	DH77	7/6
		EF91	6/9
		EW76	8/6

Matched Pairs. EL84, 23/1; 6V6G, 17/-; 6BW6, 18/-; KT33C, 19/6; KT66, 27/6; 807 14/6 pair

1R5, 1S5, 1T4, 3S4, 3V4, DAF91, DF91, DK91, DK92, DL92, DL94, any four, 27/6 per set

P.P. Op. Transformers. MR 3-15 ohms for EL84, 6V6, 6BW6, etc., 18/6; Op. Pen. 50mA, 5/6; 30mA, 4/6

Volume Controls. All values, long spindle. L/S 3/-, s.p. 4/-, d.p. 4/9, ext. spkr. control 3/-

W. W. Pots. Pre-set 3/-; 3W long spindle 5/6, s.p. 6/6

P.M. Speakers. 3 ohm. 5" 16/6, 6 1/2" 17/6, 8" 21/-, 10" 25/-, 12" 30/-, Bakers 12" 15 ohm 15W, 90/-

Coaxial Cable. 75 ohm 1/2" stranded, 8d. yd; semi-air spaced, 9d. yd; screen cable single and twin, 9d. yd

Coaxial Plugs 1/- each; Sockets 1/- each

P. and p. 9d. to £1; 1/6 to £2; over £2 post free. C.O.D. 2/6

**R. COOPER G8BX** 32 SOUTH END CROYDON SURREY CROYDON 9186

C.R.T. Isolation Transformers with nil, 25% and 50% boost, low capacity a.c. mains 200/250V for 2V 4V, 6.3V and 13V tubes. All 10/6 each

Valveholders. 4, 5, 7 pin English and U.S.A. B7G, B9A, 1.0 Mc. B8G, 9d. each; B7G, B9A with screening can, 1/6; B12A, 1/3. Aladdin formers 1/2" with core, 8d. each

Scotch Boy Recording Tape, 1,200ft reels, 27/-

Jack Plugs, miniature standard, 3/-; Sockets 3/-

2-Gang Condensers, 0.0005 small size, 7/6

I.F. Transformers, 465 kc/s, small size, 7/6 pair

Capacitors, small mica, 5% 1pF to 100pF, 8d.; 120pF to 1,000pF, 9d.; 1,000V wkg. .01, .0015, .0025, .004, .005, 1/- each

Crystal Diodes, G.E.C., 1/6 each

Headphones, lightweight, 4,000 ohm, 16/6 pair

Ceramic Capacitors, close tol. 500V for V.H.F., 9d.

Paper Capacitors, tubular, .01, 1,000V, 1/-; 0.1 to 0.5 500V, 10d.

Paper Blocks, 4µF, 1,000V wkg., 3/6

Rectifiers, contact cooled, 250V 50mA, 7/6; 85mA, 9/6

Reaction Condensers, .0001, .0003, .0005, 4/6 each

Heater Trans. 200/240V, 6.3V, 1.5A, 7/6

Resistors, 1/2 and 1/2W, insulated, 4d. and 6d.; 1W, 8d. 6W W.W., 1/-; 10W, 2/-

Electrolytics. Wire ends. 25/25V, 1/6; 50/50V, 2/-; 12/50V, 9d.; 8/450V, 2/-; 16/450V, 2/9; 16/500V, 3/6; 32/450V, 4/-; 8+8/450V, 4/6; 8+16/450V, 4/6; can types: 16/450V, 3/6; 16+16/500V, 6/-; 32/500V, 6/6; 32/450V, 6/6; 20+20/450V, 4/6; 64+120/275V, 7/6

Wavechange Switches, midget: 1p 12W, 2p 6W, 3p 4W, 4p 3W, 4p 2W, long spindles, 4/6

Toggle Switches. QMB, s.p.s.t., 2/-; s.p.d.t., 3/3; d.p.s.t., 3/6; d.p.d.t., 4/-

Chokes, 80mA, 15H, 8/6; 100mA 10H, 10/6; 150mA 10H, 14/6

Solder, Multicore, 4d. yd; Slewing 2mm, 3d. yd



Radio Component Specialists since 1946. Staffed by Engineers and Radio Amateur Constructors who enthusiastically try to give you a square deal and

## FULL VALUE FOR MONEY—

Try Us!

SPEEDY MAIL ORDER SERVICE

### BAND III TV CONVERTER

180 Mc/s-205 Mc/s

Suitable London, Birmingham, Northern, Scottish, Welsh and I.O.W. ITA transmissions  
Mk. 2 Model. Latest cascade circuit using ECC84 and E80 valves giving improved sensitivity (12 dB) over standard circuits, built-in power supply a.c. 200-250V. Dimensions only 6 1/2" x 3", ht. 4". Simple and easy to fit—only external plug-in connections. Wired aligned and tested ready for use. State channel required. Guaranteed. Bargain offer—good results or full refund. **ONLY £13.19.6** Carr. and pkg. 2/6  
Band I/Band III changeover switch and B.B.C. aerial socket can now be fitted and wired to the above converter for 8/- extra

CONDENSERS. Mica or s. mica. All pref. values. 2pF to 680pF, 6d. each. Ceramic types, 2.2pF to 5,000pF, 9d. each. Tubulars, 450V, Hunts and T.C.C. 0.001, 0.005, 0.01 and 0.1, 350V, 9d.; 0.02, 0.05, 0.1, 500V Hunts, T.C.C., 1/-; 0.25 Hunts, 1/6; 0.5 Hunts, 1/9; 0.001 6kV T.C.C., 5/6; 0.001 20kV T.C.C., 9/6 etc.

RESISTORS. Pref. values 10 ohms 10 megohms, 20% tol., 1/2W, 3d.; 1/2W, 5d.; 1W, 6d.; 2W, 9d.; 10% h-stab., 1/2W, 5d.; 3/4W, 7d.; 5% tol., 1/2W, 9d.; 1% h-stab., 1/2W, 1/6  
PRE-SET W/W POTS. TV knurled slotted knob type. 25 ohms to 30,000 ohms, 3/-; 50,000 ohms, 4/-; 50,000 ohms to 2 Megohms (carbon), 3/-

### VOLUME CONTROLS

Log. or Lin. ratios, 10,000 ohms-2 Megohms. Long spindles. 1 year guarantee. Midget Ediswan type, 1 1/2" dia. No sw. 3/-, d.p sw. 4/9

S.T.C. RECTIFIERS. E.H.T. types, K3/25 2kV, 5/-; K3/40 3.2kV, 6/9; K3/45 3.6kV, 7/3; K3/50 4kV, 7/9; K3/100 8kV, 13/6, etc. Mains types: RM1 125V 60mA, 4/9; RM2 125V 100mA, 5/6; RM3 125V 120mA, 7/6; RM4 250V 250mA, 16/-; RM4B type 250V 275mA, 17/6, etc.

LOUDSPEAKERS. P.M. 3 ohm, 2 1/2" Rola, 17/6; 3 1/2" Goodmans, 18/6; 5" R. & A., 17/6; 6" Celes., 18/6; 7" x 4" Goodmans, 18/6; 8" Rola, 20/-; 10" R. & A., 25/-, etc.

SPEAKER FRET. Expanded bronze anodised metal: 8" x 8", 2/3; 12" x 8", 3/-; 12" x 12", 4/6; 12" x 16", 6/-; 24" x 12", 9/-, etc. TYGAN FRET (Murphy pattern): 12" x 12", 2/-; 12" x 18", 3/-; 12" x 24", 4/-, etc.

### ANOTHER T.R.S. RECORD PLAYER WINNER

- LATEST 4-SPEED BSR Player unit and pick-up, £4.12.6, carriage 3/6
- 2-VALVE AMPLIFIER wired complete with speaker, etc., on mounting board, £3.5.0, carr. 2/6
- CONTEMPORARY STYLED LIGHT-WEIGHT CASE in maroon and grey, size 14 1/2" x 11 1/2" x 6", £1.7.6, carriage 2/6

**SPECIAL OFFER**  
**ALL 3 UNITS ONLY £9, Carriage 4/6**

We can only show a small selection from our vast stocks in this advert. Write now for full Bargain Lists, 3d.



## RADIO COMPONENT SPECIALISTS

70 Brigstock Road Thornton Heath Surrey Telephone THO 2188  
Terms: C.W.O. or C.O.D. Post and packing up to 1/2 7d., 1lb 1/1, 3lb 1/6, 5lb 2/-, 10lb 2/9

### RECORDED PLAYER BARGAINS

New Reduced Prices!

SINGLE PLAYERS. 4-speed BSR (TU9) 92/6; 4-speed GARRARD (4 S.P.), £7.15.0, carr. and ins. 3/6  
AUTO-CHANGERS. 4-sp. BSR (UA8), £6.19.6  
4-speed COLLARO, £7.19.6; 4-speed GARRARD (RC120/4H/2), £9.15.0, carr. and ins. 4/6. All above units are latest 4-speed models, fitted lightweight crystal p.u. and twin sapphire styli. Complete and ready to use.  
4-sp. COLLARO JUNIOR, £4.10.0  
4-sp. GARRARD RC121/4D/Mk.II, 10 gns.  
**FINEST SELECTION AVAILABLE—ALL BRAND NEW AND GUARANTEED**

### 80 OHM COAX CABLE

NOW ONLY 8d. YARD!

Highest Quality Cable, low-loss Polythene Aerial, semi-air spaced, feeder losses cut 50%. Standard 1/4" dia. Stranded core. Famous make.  
20 yds 12/6, carr. 1/6  
40 yds 20/-, carr. 2/6  
Coax Plugs 1/-, Coax Sockets 1/-, Couplers 1/3, Outlet Boxes 4/6, B1-B3 Xover Unit 7/6

### C.R.T. HEATER ISOLATION TRANS.

New improved types—mains prim. 200/250V tapped. All isolation transformers now supplied with alternative no boost, plus 25%, and plus 50% boost taps at no extra cost, all in one transformer. 2V 2A type, 12/6; 6.3V 0.6A type, 12/6; 10.5V 0.3A type, 12/6; 13V 0.3A type, 12/6. P. and p. 1/6. Other voltages in course of production. Small size and tag terminated for easy fitting. P. and p. 1/6

### EMITAPE RECORDING TAPE

ALL NEW AND BOXED

Type 88 (Stand.)	Type 99 (Long Play)
3" ... 175ft ... 7/-	250ft ... 9/-
5" ... 600ft ... 19/-	850ft ... 24/-
5 1/2" ... 850ft ... 24/6	1,200ft ... 31/6
7" ... 1,200ft ... 30/-	1,800ft ... 45/6

Spare Reels (unboxed). 7" metal 1/6, 7" plastic (EMI) 3/6

### RE-GUNNED TV TUBES—GENUINE OFFER

New heater, cathode and gun assembly can now be fitted to your old tube, revacuumed and reconditioned virtually as new. Fully guaranteed to highest standards—as used by our own Service Department. 12" £8; 14" £8.10.0; 17" £10. We regret only Mullard and Mazda types at present. Delivery approximately 7 days. Carriage and insurance 12/6

MIDGET TRANSISTOR TYPE ELECTROLYTICS. T.C.C. 2µF, 4µF, 8µF 6V, 3/6; 6µF, 10µF, 16µF 3V, 3/6; 32µF 1 1/2V, 3/6, etc.

### VALVES—NEW BOXED—ALL GUARANTEED


1R5, 1T4, 7/6; 1S5, 154, 7/6; 3S4, 3V4, 8/-; 5Z4, 9/6; 6AT6, 8/6; 6K7, 6/6; 6K8, 8/6; 6Q7, 8/6; 6SN7, 8/6; 6V6, 7/6; 6X4, 7/6; 6X5, 7/6; 7C5, 9/-; 7Y4, 8/6; DAF96, 9/-; DF96, 9/-; DK96, 9/-; DL96, 9/-; 35L6, 10/6; EAB80, 9/6; EB91, 6/6; EBC-11, 10/6; EBC33, 8/6; ECC84, 12/6; ECH42, 10/6; ECH81, 10/6; ECL80, 12/6; EF41, 10/6; EF80, 10/6; EF86, 14/6; EF91, 8/6; EY51, 12/6; EZ40, 8/6; EZ80, 8/6; MU14, 9/6; PCC84, 10/6; PCF80, 10/6; PCF82, 10/6; PCLB3, 12/6; PL81, 14/6; PL82, 10/-; PL83, 11/6; PY80, 9/6; PY81, 9/6; PY82, 8/6; U25, 14/6; UY41, 8/6

SPECIAL—1R5, 1T4, 155, 154 or 3S4 or 3V4 per set 27/6

Hours 9 a.m.—6 p.m., 1 p.m. Wed.


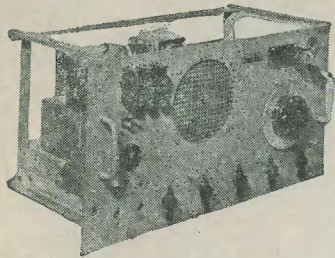
# SPUTNIK-SPECIAL — THE WORLD IN YOUR HOME



## SHORT-WAVE RECEIVER 10-60 MC/S (5-30 Metres) RECEPTION SET TYPE 208

Complete with 6 valves, 2 6K8G, 2 EF39, 6Q7G and 6V6G. Internal mains power pack and 6V vibrator pack. Built-in 6½" speaker. Muirhead slow-motion drive. B.F.O. and R.F. stage. I.F. freq. 2 Mc/s. Provision for phones and muting and 600 ohms input 110/250V a.c. 6V vibrator pack included for battery operation. All sets in new condition and air tested. £6.19.6 carr. 15/6

6½" Extension Speaker 27/6 in cabinet

**NO WORK REQUIRED : JUST PLUG IN AND SWITCH ON!**

## AC/DC PORTABLE RADIO

- ★ 5 valve superhet
- ★ Built-in frame aerial
- ★ Size 10" x 10" x 4" deep
- ★ All Marconi valves
- ★ Med., long and short waveband
- ★ OR Med. and two short wavebands
- ★ Gram. sockets (for crystal or magnetic pick-ups)
- ★ 7" x 4" elliptical speaker
- ★ Slow motion tuning
- ★ Ideal for a radio-gram

ONLY £7.12.6 post 7/6

Portable polished cabinet ... 27/6  
Super portable rexine cabinet ... 37/6

ABSOLUTELY GUARANTEED BRAND NEW AND IN PERFECT WORKING ORDER

## CRYSTAL CALIBRATOR For No. 19 Set

10 kc/s; 100 kc/s; 1 Mc/s; spot frequencies; crystal controlled oscillators; includes 5 12SC7 valves, neon modulator handbook, etc.

BRAND NEW £4.19.6 Post free

## TRANSMITTER/RECEIVER Army Type 17 Mk. II

Complete with valves, high resistance headphones, handmkie and instruction book and circuit. Frequency range 44.0 to 61 Mc/s. Range approximately 3 to 8 miles. Power requirements: Standard 120V h.t. and 2V l.t. Ideal for Civil Defence and communications. BRAND NEW 45/-  
44-61 Mc/s calibrated Wavemeter for same, 10/- extra

## RADAR UNIT TYPE 1683

Complete with the following valves: 2 6C4, 832A, 829B, 2 5R4G, 3 6AC7, 6V6GT, 931A photo multiplier with associated network. Also 2-blower motors. Input 30-115V 400 to 2,600 c/s cd 26V d.c. £6.10.0 Post free  
BRAND NEW AND boxed

**VIBRATOR PACKS.** Input 6V d.c. Output approx. 100V d.c. at 30mA, fully smoothed and r.f. filtered. Size 6½" x 5" x 2". Fitted with Mallory 629C vibrator. BRAND NEW. Boxed. 12/6

## TRANSISTOR SQUARE GENERATOR

Complete kit with 2 Transistors, Components, Circuit and plastic case 20/-

## TRANSISTOR SIGNAL TRACER

Complete kit with 2 Transistors, Components, Phones and Circuit and plastic case 37/6

## 373 MINIATURE I.F. STRIPS 9.72 MC/S



12/6 (less valves) 42/6 (with valves)

Postage and packing 2/6 (either type)

FM AT ITS CHEAPEST!

The ideal f.m. conversion unit as described in P.W., April/May 1957. Complete with 6 valves, three EF91's, two EF92's and one EB91. I.F.T.'s etc., in absolutely new condition. With circuit and conversion data.

## RCA 6½" P.M. SPEAKER IN CABINET

With vol. control and 600V line trans. 27/6, P.P. 2/6

## MIXER UNIT TYPE 79

Frequency range 172 to 190 Mc/s. Comprising: VCR139A cath. ray tube; 7 EF50's; EF55; 4 EA50's; 2 EB91's; 5U4; VU120 and EC52. Standard main input 200-250 volts 50 c/s. Ideal Scope basis.

£5.10.0 carriage 5/-

## A.C./D.C. 200/250V Portable-Gram AMPLIFIER

Completely assembled on baffle board size 12½" x 4½", depth 3". Containing two Mullard valves type UL84 and UY85, Elac 7" x 4" elliptical speaker, volume control, tone control. Nothing else to buy, just plug in to mains and connect your pick-up to amplifier.

Absolute bargain 67/6 Carr. 2/6

## DYNAMOTORS

12 volt d.c. input, 220 volt 165mA output, 32/6. Post free

## BATTERY CHARGER


Input 200/250V a.c. Output for 12V batteries at 2½A trickle charge. BRAND NEW in metal case 27/6 P.P. 2/6

## RF UNITS

TYPE 25 Switched. Tuning 30 to 40 Mc/s. Includes 3 SP61's Carriage 2/6 10/-  
TYPE 26. Variable tuning, 50 to 65 Mc/s, Including 2 EF54's and 1 EC52. Carr. 2/6 25/-  
(Circuits in stock for both types 9d.)


Send 3d. stamp for new transistor components list: new quartz crystal list; valve list; transistor receiver circuits, etc. Complete Catalogues 6d.

## MINOR (Ideal Xmas Presents) MAJOR

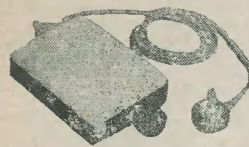

- ★ Variable tuning over medium waves
- ★ 3-stage reflex circuit
- ★ Highly sensitive
- ★ Internal ferrite aerial
- ★ Drilled chassis
- ★ Long-life battery

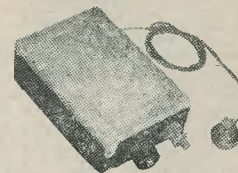- ★ Complete constructional details
- ★ Weight less than 2 oz.
- ★ Size only 3" x 2" x ¾"



- ★ 4-stage reflex circuit
- ★ Variable tuning over medium waves
- ★ Highly sensitive
- ★ No aerial or earth
- ★ Home, Light and Third
- ★ Economical
- ★ Drilled and mounted chassis
- ★ Size 4½" x 3" x 1½"
- ★ Internal ferrite aerial

- ★ Weight less than 4 oz
  - ★ Complete layout diagram
  - ★ May be built in 1 hr.
- All items can be supplied, including EDISWAN transistors, battery, case and personal phone, etc., for 72/6, post free. All components sold separately. Circuit and shopping list FREE. Call and Hear Demonstration Model.

Total cost, including transistor, personal miniature phone, case, battery and complete circuit and layout diagrams, 52/6 post free. All components sold separately. Circuit and shopping list FREE. Call and Hear Demonstration Model.

As described in October issue of *The Radio Constructor*


## "THE TRANSISTOR - 8" Push-Pull Portable Superhet

This Portable 8-Transistor Superhet is tunable for both Medium and Long Waves and is comparable in performance to any equivalent Commercial Transistor Set. Call and Hear Demonstration Model.

- ★ 8 EDISWAN Transistors
- ★ 250 Milliwatts output Push-pull
- ★ Medium and long waves
- ★ Internal ferrite rod aerial
- ★ Elliptical speaker
- ★ Drilled chassis 8½" x 2½"
- ★ Point-to-point wiring and practical layout
- ★ Economical. Powered by 7½V battery
- ★ Highly sensitive
- ★ Attractive lightweight contemporary case. In various colours

**COMBINED PORTABLE/CAR RADIO**  
Two sets for the price of one

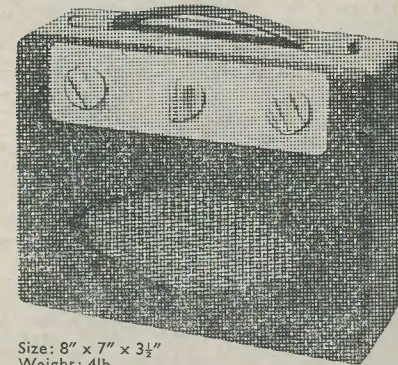We can supply all these items including cabinet for £11.10.0 P.P. 2/6. All parts sold separately. Circuit diagrams and shopping list free



Size: 8" x 7" x 3½"  
Weight: 4lb.

Car Radio Conversion Components, 8/- A.V.C. 5/9  
325mW version, 40/- extra

## TELETRON "TRANSIDYNE" RECEIVER

Six-Transistor Pocket Superhet

- ★ TCC printed circuit
- ★ Medium and long waves
- ★ Powered by two No. 8 batteries
- ★ Push-pull output 150mW
- ★ Moulded plastic case
- ★ Rola 2½" p.m. speaker
- ★ Internal ferrite aerial
- ★ Weight 20 oz
- ★ Complete layout instructions
- ★ Easy to assemble (All components identified)

Size: 6½" x 3½" x 1½"

★ THE BEST YET!  
All components, including NEW EDISWAN TRANSISTORS, cabinet, batteries, etc., can be supplied for £11.19.6, P.P. 2/6  
All parts sold separately. Circuit and shopping list 9d.

## CRYSTAL MIC. INSERTS

¾" square ... 3/6 1½" round (Acos) ... 7/6  
¾" round (Acos) ... 5/- 2½" round (Acos) ... 12/6  
Moulded plastic hand mic. case suitable for any of above, only 2/6


## NEW TYPE TRANSISTORS — PRICE REDUCTIONS

**JUNCTION TYPE P.N.P. — ALL EDISWAN**  
XA104 6 Mc/s osc./mixer or r.f. amplifier ... 18/-  
XA103 4 Mc/s r.f. and i.f. amplifier ... 15/-  
XB104 audio output ... 10/-  
(A pair in push-pull will give up to 250mW audio output)  
RED SPOT 800 kc/s audio amplifier ... 7/6  
WHITE SPOT 2 to 5 Mc/s r.f. and i.f. amplifier 12/6

## CONSTRUCTORS PARCEL FOR
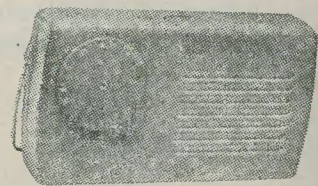
## TRANSISTOR POCKET RADIO

Perdio attractive moulded cabinet, 12/6  
J.B. screened twin gang 208+176pF, 10/-, Perdio 2½" min. 3 ohm speaker, 21/-



Single ended output transformer to match, 10/- ALL FOR ONLY 49/6 P.P. 2/6

## HENRY'S RADIO LTD · 5 HARROW ROAD · LONDON W2

Opposite Edgware Road Tube Station

(DEPT. RCD)

Telephone PADDington 1008/9

## HENRY'S RADIO LTD · 5 HARROW ROAD · LONDON W2

At junction of Edgware Road and Harrow Road

(DEPT. RCD)

Telephone PADDington 1008/9



### The TRANSIDYNE RECEIVER

(Page 119 Sept. issue)

We guarantee all components to be exactly as specified by designer & approved by Messrs. Teletron

Drilled case, printed circuit, battery holder, dial, nuts, screws £1.5.0  
Complete coil and aerial kit £2.2.0  
Resistor kit (with circuit refs.) 6/-  
Cond. kit (with circuit refs.) £1.5.0  
Rola speaker (tax paid) £1.8.2  
J.B. tuning condenser with centre screen 10/6  
Ardente D131 & D132 per pr. £1.5.6  
Ardente volume control (R15) 12/6  
Slider wavechange switch 3/6  
GEX34 diode 4/-

### COMPLETE KIT AS ABOVE AT THE SPECIAL PRICE OF

Transistors— £8.15.6  
Red/Yellow (r.f.) 15/- each  
Green/Yellow (audio) 9/6 each

### COMPLETE KIT WITH TRANSISTORS AT THE SPECIAL REDUCED PRICE OF £11.19.6

FREE—Special 'printed circuit' solder with each kit

Full constructional details, 9d. S.A.E. Price List

TRANSISTOR KITS. Companion £5.9.0. Leaflet 6d. 'Mini-7', £12. Envelope 1/6. Radiosette £2.3.0 (with phones)  
Price Lists—S.A.E.

We recommend the 'LITESOLD' soldering iron for all work and especially printed circuits, mains or battery. 21/6 complete (state mains voltage)

CONNECTING WIRE. p.v.c. 50ft coil, 5 colours, 1/9. Sleeving, 15ft, asstd. colours and thicknesses, 8d. Tinned Copper Wire 24 s.w.g., 15ft 8d. Combined pack (3 above items) 2/9

QUOTATIONS gladly given (S.A.E. please)

## R. FAGELSTON (MAIL ORDER)

Please add Postage to above prices

• ~~~~~ 46 HARDWICKE ROAD · LONDON N13 ~~~~~ •

## Res/Cap Bridge

FOR

# 35/- ONLY

P. & P. 2/-

For checking all types of resistors and condensers

**BUILT IN 1 HOUR! DIRECT READING!!**

**READY CALIBRATED!!!**

Stamp for details of this and other instruments

**RADIO MAIL** Dept CD Raleigh Mews  
Raleigh Street Nottingham

## HIGH FIDELITY

Quality components of all types always in stock for the

**MULLARD 2-VALVE PRE-AMPLIFIER**  
**MULLARD 3-VALVE 3-WATT AMPLIFIER**  
**MULLARD TAPE AMPLIFIER TYPE C**

Circuits free on request

510 AMPLIFIER FM TUNER	circuits 3/6
912 PLUS AMPLIFIER	" 4/-
JUPITER STEREO UNIT	" 2/6
RADIO CONSTRUCTOR FM	" 2/-
MERCURY SWITCHED FM	" 2/-
DENCO FM TUNER	" 1/6

Price list available on request

**J. T. FILMER** 82 DARTFORD ROAD  
DARTFORD KENT  
Telephone Dartford 4057

TRANSISTOR ITEMS. Electrolytics 8µF 6V, 16µF 12.5V, 32µF 3V, 5µF 12.5V, 5µF 40V, 2.5µF 40V, 1.6µF 6V, 25µF 6V. All 3/3 each; 100µF 6V 3/-; Paper 0.01, 0.001, 0.002, 0.005µF, all 8d. each. Transistor Holders 1/- each, 6 for 5/9, 11/- doz. Ardente T.1065 transformers (page 911—July), 12/-, Subminiature Speakers 1½" round, 27/-; 2" x 3" elliptical, 33/-, Sub-miniature Output Transformers, single-ended or p/p, 12/6. Volume Controls, button type (totally enclosed), 47k and 1MΩ, 2/6; preset skeleton type 5k, 2/6; spindle type, ½M, 1M, 2M, 4/3 (page 705—'R.C.' May). Ardente Deaf Aid Earpieces E.R.100, with cord and plug. Limited number at 13/9. Ardente Catalogue 6d.

### TRANSISTORS—CHEAPER STILL

Yellow/Red R.F.	15/-
White Spot R.F.	14/-
Yellow/Green A.F.	9/6
Red Spot A.F.	9/-

GENERAL ITEMS. Miniature neons (as used in mains testers), 1/10. Resistors, carbon from 3d., wire wound from 1/3, hi stabs from 6d. Mixed Carbon 50 for 7/-. Capacitors, paper from 10d., s/mica from 18d. 'Ajax' Crystal Kit complete, 14/6 (L.V. 15/-). Phones 14/- and 16/-, 'Ajax' Case with chassis, 5/9. Multicore Solder 4d. yd, 19 ft reel 2/6, 1lb reel 14/9. Fine gauge for printed circuits, 40 ft reel 2/6. Switches, s/p from 2/3, d/p from 3/6. Ferrite Rods 8" x ¼" diam., 2/-, Mains neon indicators with built-in resistor. Domed top, chrome bezel, 1" long ½" diam. Opal, red, amber, 3/10; green 4/7. Assorted nuts, bolts, washers, 25, 1/-; 72, 2/9; 144, 5/-

### JACK PLUGS AND SOCKETS

(by Bulgin) See p. 376

Miniature type ¾" diameter panel space. ¾" behind panel. With optional closed circuit leaf. Plug 3/- Socket 2/6 See p. 376  
Sub-miniature type ¾" x ½" panel space. ½" behind panel, ¾" projection.  
Plug 1/3 Socket 9d.

### GIFT IDEAS

AJAX CRYSTAL RECEIVER. Complete kit to make this well-known receiver. Easy to assemble—superb reception. M.W. set 14/6. L.V. 15/-

Headphones 14/-, Superior Type 16/6, Crystal Headphones 21/-

REP. 1 VALVE RECEIVER. For excellent headphone reception. With battery but less phones, £2/10/0

File Set. 6 wood handled files in smart wallet... 12/6

Screwdriver Set. 6 blades (including 2 Phillips type) with amber handle. In compact wallet 7/6

Pliers Set. 1 pair large pliers, 1 pair slender nosed, 1 pair side cutters. In wallet... 12/6

Drill Set. 7 sizes 1/8" to 1/2". In wallet... 6/10

Side Cutter Pliers. 5" insulated handles... 5/8

Long Slender Side Cutters. For compact work. Lap jointed 4½" long... 8/9

Box Jointed Side Cutters. Superior make, polished steel, 4½" ... 12/9

Screwdriver Mains Testers 3/9

### HI GAIN BAND 3

PRE-AMPLIFIER

(See page 568 March)

Resistor Set, 1/6; Capacitor Set (with clip), 8/9; Valve ECC84, 17/-; Rectifier (50mA), 7/6;

Transformer, 13/-; Coil Set (L1-L5) 9/-; Chassis (punched for coils, space for Power Pack), 3/9; Coax Sockets, V/holder, Tag Strip, Nuts, Bolts, 5/6.

COMPLETE KIT AS ABOVE £3.3.0

### SMALL ADVERTISEMENTS

Readers' small advertisements will be accepted at 3d. per word, including address, minimum charge 2/-, Trade advertisements will be accepted at 9d. per word, minimum charge 6/-, If a Box Number is required, an additional charge of 2/- will be made. Terms: Cash with order. All copy must be in hand by the 12th of the month for insertion in the following month's issue. The Publishers cannot be held liable in any way for printing errors or omissions, nor can they accept responsibility for the bona fides of advertisers.

### PRIVATE

FOR SALE. PCR2 receiver, mint condition, fitted internal power pack, £7.—W. Oakley, "Pearl Dene," Craig Walk, Bowness-on-Windermere, Westmorland.

SALE. The Radio Constructor, 5 years back issues, perfect, 55s. Hallicrafters S27, needs attention, 55s. 25 valves, new and boxed, B7G and B9A, 50s.—Booker, 77 Goldsmith Avenue, London, E.12.

SALE. Metal rectifiers 14A86 and 14A100 (200mA 250V). Used but good, 5s. each or 5 for 20s. Please add postage.—Box No. E.192.

COLLARO TAPE DECK Mk. II, perfect, £13. AR88 Manual, £1 Valves 35T, unused, boxed, 15s.—Anderson, 16 Warrander Way, Ruislip, Middx.

FOR SALE. Wearite tape deck, unused, 7 x 1,200 feet reels Emitape, m/c microphone, £25 o.n.o.—Yallop, Standard Road, Downe, Kent.

SALE. TV engineer's entire private stock, valves, components, etc. Value £150, accept £35 but no reasonable offer refused.—HATCH End 5162 after 7 p.m.

BAIRD "SOUNDMASTER" tape recorder in working order, 110/230V a.c. Less microphone. Compact carrying case, snip, £23 15s. 0d., carriage paid. C.W.O.—L. Starling, 11 Benson Road, Croydon, Surrey.

WHAT OFFERS? 23 Bound Volumes Wireless World plus many single issues. Sheffield or Hertford. Box E.191.

FOR SALE. Newnes Radio and TV Servicing, 6 volumes, new, £8.—Martin, 4 Beech Road, Princes Risborough, Bucks.

FOR SALE.—Cossor 399 Double Beam Oscilloscope, £15, also Taylor Multimeter type 71, 1000 ohms per volt, overhauled recently by manufacturer, guaranteed with circuit diagrams.—Phone for appointment to view, CL1 6335 or, after 6 p.m., 20 Brooke Road, London, N.16.

FOR SALE. Taylor model 55A Wobbulator, Taylor model 30A Oscillograph, Taylor model 65C Signal Generator. All complete with Instruction Manuals, £25 for the three instruments.—Snell, Central Garage, Stairfoot, Barnsley.

FOR SALE. TSL Concert Soundcorner, Hi-Fi corner hanging speaker system, as new, £8 10s. 0d., Wednesday/Thursday evenings.—Thomas, 8 Lysia Street, London, S.W.6.

WANTED. Partridge Williamson output transformer, first class condition only, reasonable—Cooke, 35 Victoria Grove, Bridport, Dorset.

WANTED. Quad II main amplifier, also Ferrograph, Vortexion, or similar tape recorder.—Terry, 39 Ronaldstone Road, Sidcup, Kent.

### NEW SURPLUS...

1A3	2/6	6L6M	10/6	803	20/-	EY51	12/6
1L4	5/-	6Q7G	7/6	830B	15/-	EY86	13/6
1R5	7/6	6Q7GT	9/6	866A	15/-	EZ40	8/6
1S5	7/6	6SA7M	7/6	959	5/-	EZ80	8/6
1T4	6/-	6SG7M	7/6	1616	5/-	EZ81	9/6
2A3	8/6	6SH7M	5/-	1629	4/-	GT1C	10/-
2X2	3/6	6SJ7M	7/6	EA50	1/6	GZ32	12/6
3A4	4/6	6SK7M	6/6	EAB8C10	1/6	HK24G	25/-
3C4	7/6	6SL7GT	7/6	EAC91	4/6	KT33C	9/6
354	8/6	6SN7GT	6/6	EAF42	10/6	PCC84	10/6
5763	12/6	6SQ7M	7/6	EB34	2/6	PCF80	13/6
5R4GY	15/-	6V6G	7/6	EB91	5/6	PCF82	10/-
5Y3G	8/6	6V6GT	8/6	EBC33	7/6	PCL82	13/6
5Y4G	6/6	6X4	6/6	EBC41	10/6	PL81	15/6
6AC7M	5/-	6X5GT	7/6	EBF80	10/-	PL82	9/6
6AG5	3/6	7B7	8/6	EBF89	10/-	PL83	10/6
6AK5	5/-	7C5	8/6	ECC82	9/6	PY80	9/6
6AL5	5/6	7C6	8/6	ECC83	10/-	PY81	9/6
6AM6	6/6	7S7	10/-	ECC84	11/-	PY82	9/6
6AQ5	8/6	7Y4	8/6	ECC85	10/6	PY83	11/6
6AT6	8/-	12A6M	7/6	ECC86	12/6	R19	12/6
6AU6	8/6	12AT6	8/-	ECC82	11/6	TT11	4/-
6B8G	4/6	12AT7	9/-	ECH42	10/6	UAF42	10/6
6BA6	8/6	12AU6	9/-	ECH81	10/6	UBC41	10/6
6BE6	7/6	12AU7	8/6	ECL80	12/6	UBF89	10/6
6BH6	7/6	12BE6	8/6	ECL82	12/6	UCC85	10/6
6BJ6	7/6	12CBM	7/6	EF36	4/-	UCH42	10/6
6BR7	11/6	12Q7GT	7/6	EF39	5/-	UCH81	10/6
6BW6	9/-	12K7GT	7/6	EF41	10/6	UF41	10/6
6C4	5/-	12SC7M	2/6	EF50	3/6	UF89	10/6
6CSM	5/6	12SJ7M	5/-	EF50(S)	4/6	UL41	10/6
6F6M	5/6	12SK7M	5/6	EF55	7/6	UY41	8/6
6J5GT	5/-	12SQ7M	8/6	EF80	9/-	UY85	8/6
6J5M	6/-	35L6GT	9/6	EF85	10/-	UABC80	
6J6	4/-	35Z4GT	7/6	EF86	15/6	VU39	10/6
6J7G	7/6	35Z5GT	8/6	EF89	10/-	VU39	9/6
6K7G	5/6	42	7/6	EF91	6/6	VR150/30	
6K8G	7/6	50L6GT	9/6	EL32	4/6		7/6
6K8M	10/6	80	8/6	EL41	10/-	VS70	3/-
6H6M	3/6	446A	10/6	EL84	9/6	XP1.5	3/-
6L6G	9/-	801A	7/6	EM80	10/-	Z77	6/6

M.C. Meters. 2½" rd. fl. (2" dial), 0-1mA, 21/-, Ditto but scaled 0-30V, 16/6. 0-500µA, 17/6. 2½" rd. plug in electrostatic 0-1,500V, 16/6.

R107 Front End. For r.f. mix, osc. 3 bands 1.2-18 Mc/s (465 kc/s i.f.) with half-moon calibrated dial and slow motion drive, 40/- carr. paid, less valves.

Special Value Offer! All prices per dozen. 1A3, XP1.5, 12SC7M, 18/-; 6H6M, 6AG5, 6K7G, EL32, 6B8G, TT11, 1626, VS70, 25/-; 6AC7M, 6J6, 6C4, EAC91, 1629, 801A, 2X2, 37/6; 6SN7, 12A6M, 1T4, 1625, 6F6M, 60/-; 6X5, 6K8G, 3Q4, EE91, 70/-

Latest Model Acos Crystal Stick Microphones MIC39-1. Frequency response flat to 6 kc/s, and within 5dB to 12 kc/s. List price £5.5.0. Our price 67/6 or 55/- less stand. New, boxed. Post paid.

Transistors. Yellow/green, aud, 250mV, 7/6; OC70, 12/6; OC71, 15/-; yellow/red, r.f. to 8 Mc/s, 15/-

Midget Mains Transformers (same size as std. spoke o/p). Input 230/250V, o/p 220V 20mA, 6.3V 0.6A. Ditto but 175V 25mA, both types 11/9 each, post paid.

Transmitter/Receivers. Army Type 17 Mk. 2. Complete with h.r. phones, hand mike and valves. 44-61 c/s. In good used condition, 29/6 each. Carr. paid. Few only. New ones 45/- each

### SPECIAL OFFER

Performance Meters No. 2. Comprising 230V 50 c/s mains trans. 250-0-250V 30mA, 6.3V 1½A, 5V 2A (60mA h.t. may safely be drawn), 20H choke, 5Z4, Y65 magic eye, 2 EF50, 1 EC52, 1 EA50, dozens of components, all in smart grey louvered case 10" x 9" x 9". Made by Parmeko. Brand new and boxed. Unrepeatable component value at only 32/6 each carr. paid (U.K. only)

Post 9d. Free over £2

S.A.E. Enquiries

## JOHN ANGLIN

385 CLEETHORPE ROAD GRIMSBY Lincs

Telephone 56315

continued on page 399



# EDDY'S (NOTTINGHAM) LTD

(DEPT. RC) 172 ALFRETON ROAD NOTTINGHAM

**MIDGET BATTERY ELIMINATORS.** To convert all types portable radio to mains operation, 57/6 each, 2/6 post. Size 3.7" x 2.5" x 1.8". Smaller than h.t. battery alone. (Please state make and model No.) Brand new and boxed.

**THROAT MIKES, 1/-** each, post 6d. Can be used for electrifying musical instruments.

**NEON MAINS TESTER/SCREWDRIVERS, 4/6** each, post 6d.

**B.S.R. MONARCH 4-SPEED AUTOMATIC CHANGER.** Complete with high fidelity turnover head. Plays 10 records—12", 10", 7"—intermixed in any order. 78, 45, 33 and 16 r.p.m. For a.c. mains 100-250 volts. Exclusive Magi-Disk selector gives quickest and quietest change ever. Brand new. £6.19.6. Post, etc., 5/-

**25μF x 25V d.c. MIDGET CONDENSERS.** Size 1", 1/3 each; 14/- doz. Post 4d.

**RECTIFIER/STABILISER.** Input voltage 150V at 10mA. For low consumption battery valves. 6/6, post 6d.

**JACK PLUGS.** Standard type, 1/11, post 4d.

**GERMANIUM DIODES, 1/-** each, 10/- doz. Post 4d.

**MORSE TAPPERS.** Plated contacts, adjustable gaps, heavy duty, good quality. Special price 3/6 each, post 9d.

**TRANSISTORS.** Yellow/Green Spot 6/11, post 4d.

**TRANSISTORS.** R.F. Yellow/Red Spot 13/11, post 4d.

**SUB-MINIATURE TRANSISTOR CONDENSERS.** 1.6μF, 5μF, 10μF, 16μF, 32μF, 2/6 each Post 4d. New and guaranteed.

**ACOS MIKE INSERTS, 4/11** each. High quality. Can be used for tape recorders, baby alarms, musical instruments, etc. Post and packing 8d. New and guaranteed.

## SURPLUS, NEW AND GUARANTEED VALVES

1D5	10/-	6B8G	2/11	6SN7GT	5/9	12Q7	7/6	807(U.S.A.)	AZ31	12/6	EB91	5/11	EY51	12/6	
1R5	7/6	6C4	4/9	6V6G	5/11	25A6G	12/11		5/6	CY31	12/11	EBF80	9/11	EY86	14/6
1S5	7/-	6F1	13/11	6V6GT	6/6	35A5	10/6	954	1/6	DAF96	9/6	ECL80	13/11	L63	5/11
1T4	5/6	6F13	12/6	6X5GT	6/6	35Z3	13/6	955	3/11	DF96	9/6	EF41	9/6	MU14	8/6
3D6	4/9	6K7G	2/11	12AH7	7/6	35Z4	7/6	956	2/11	DL96	9/6	EF50	3/6	PY81	8/6
5U4G	6/6	6K8G	7/6	12K7	7/6	807(B)	3/9	AZ1	12/6	DM70	7/11	EF50(R)	4/11	UF41	9/-

All tested before despatch

Cash on delivery or cash with order only

Postage and Packing 6d. per valve extra. Over £3 post free. S.A.E. with all enquiries

All parcels insured against damage in transit for only 6d. extra per order. All uninsured parcels at customer's risk.

SEND 1/- FOR 56-PAGE ILLUSTRATED CATALOGUE

## SMALL ADVERTISEMENTS

continued from page 397

PRIVATE—continued

**FOR SALE TO CLEAR.** Valves, German RV12P. 2000, 3s. 6d. each; 807, 5s.; VT136, 3s. 6d.; VR91, 2s. 6d.; EC52, 2s. 955 with base, 5s. Xtals, 7/17, 7/154, 7097 kc/s., Q.C.C. in holders, 7s. 6d. each. Coils, Labgear DSL 14 and DSL 21, 7s. 6d. each. Speakers, 6 inch PM at 7s. 6d. each, extension speakers in stained wooden cabinets, approx. 12 x 12 x 4 inches, 15s. Morse keys on metal base, 7s. 6d. Meters, 0-3A r.f. 2 1/2 inches square, 7s. 6d.; 30-0-30 charging amps, 5s.—"East Keal," Romany Road, Oulton Broad, Lowestoft, Suffolk.

**FOR SALE—PORTABLE TOP BAND RIG.** Tx and Rx in black crackle cabinet, 12 x 7 x 8 inches, handle on top, xtal Tx, T.R.F. Rx, cw/phone, 12V input, with rotary, microphone, key and whip aerial. Smart rig, £15.—Box No. E.193.

**WANTED.** Circuit of powerful transistor hearing aid using readily obtainable components.—Croxson, 37 Canterbury Avenue, Ilford.

**WANTED.** G2UK would like to hear from anyone who has information about the Morse Re-perforator and the Morse Tape Printer illustrated on pages 46 and 47 of the advertisement section of the 32nd Edition of the "ARRL Radio Amateur's Handbook" 1955. News of any such equipment for sale would be particularly welcome.—"East Keal," Romany Road, Oulton Broad, Lowestoft, Suffolk.

**WANTED.** Prop Pitch Motor, good price paid.—Bartlett, White Ladies, Cheyney Gate, Pinhoe, Nr. Exeter.

## TRADE

**AMERICAN MAGAZINES.** Popular Electronics, Radio and TV News, annual subscriptions 35s. 6d. each. Specimens 5s. each.—Hobson, 344 Topsham Road, Exeter, Devon.

**THOUSANDS** of interesting items. List. Stamp please.—Rogers, 31/33 Nelson Street, Southport, Lancs.

**DISAPPOINTED WITH TRANSISTOR CIRCUITS? TRY MORCO REFLEX CIRCUIT** (2 transistors)—the best of its kind—loudspeaker results from indoor aerial (some districts no aerial). All parts available for Teletron "Companion" and Repanco "Mini-7" receivers. Send 8d. stamps for Notes on Transistors.—Morco Experimental Supplies, 8/10 Granville Street, Sheffield 2.

**MORSE CODE TRAINING.** Special course for Beginners. Full details from (Dept. R.C.), Candler System Company, 52 Abingdon Road, London, W.8.

**ILLUSTRATED CATALOGUE No. 13** containing over 450 items of Government Surplus and Model Radio Control Equipment, 2s. 2d. Refunded on purchase of goods, 2s. 6d. overseas seamount.—Arthur Sallis Radio Control Ltd., Department R.C., 93 North Road, Brighton. Telephone 25806.

**PRIVATE TUITION** given in Radio Theory for the R.T.E.B. examination in radio servicing. Terms reasonable.—Box No. E.190.

**NEW SWITCH-TUNED FM UNITS** with AFC. Gold hammer front panel engraved Home, Light, Third, £10 15s. 0d. With internal power supply, £13 10s. 0d. Write for details.—Box No. E.189.

continued on page 400

## REVACUUMED TV TUBES

All Guaranteed 6 months, carr. and ins. 12/6  
9-10", 3/16, CRM91, MW22/7-14, etc., £3. 12", CRM 121A-B, MW31/7-14-17-18, etc., £5. 14", 141K MW 36/24, CRM141/2, etc., £4 10s. 15-16", 6901A, CRM153, etc., £5. 17", MW43/64, C17BM, CRM171, etc., £5 15s. **TRANSISTORS.** Red Spot, 7/-; White Spot, 12/6


## GUARANTEED VALVES—24-HOUR SERVICE

6AM6	6/9	B36	11/-	EF89	9/6	PY31	10/-
6BA6	6/6	FAF42	9/-	EP91	6/6	PY80	8/-
6BE6	6/6	EB41	7/6	EL33	11/-	PY81	8/6
6C4	4/9	EB91	5/6	EL41	9/6	PY82	8/9
6C9	9/6	EBC33	7/-	EL84	9/6	PY83	8/6
6D2	5/6	EBC41	9/-	EY51	10/3	PZ30	12/-
6F12	6/6	EC91	4/6	EY86	15/-	SP61	3/-
6F13	9/6	ECC81	7/6	EZ40	8/-	U22	7/6
6F14	11/-	ECC82	6/6	EZ40	10/-	U24	12/6
6F15	11/-	ECC83	8/6	EZ80	7/6	U801	11/6
6J6	4/6	ECC84	9/9	GZ32	10/-	UAF42	9/-
6L1	9/-	ECC85	9/-	KT33C	9/6	UB41	9/-
6L8	9/6	ECH42	9/3	KT36	11/-	UBC41	8/6
6LD20	9/6	ECL80	12/6	KT61	9/6	UCH42	9/6
6P28	11/-	EF36	4/-	P61	2/6	UF42	9/-
6X4	6/-	EF39	5/-	PCC84	9/-	UF41	9/-
10F1	9/6	EF41	9/6	PCF80	9/6	UL41	8/6
10P13	11/-	EF42	12/-	PL33	11/-	UL44	9/6
10P14	12/-	EF50(A)	3/6	PL38	11/-	UL46	9/6
20D1	9/6	EF50(B)	4/9	PL81	14/6	UU8	11/-
20F2	9/6	EF80	7/6	PL82	9/-	UY41	8/-
20P1	11/-	EF85	7/-	PL83	11/-	Z66	15/-

For all details send 6d. for  
**12-PAGE LIST OF 800 SNIPS**  
Post 1/3 in £1. Min. 9d. No C.O.D.  
10,000 SNIPS FOR CALLERS

**TECHNICAL TRADING CO**  
350/352 FRATTON ROAD PORTSMOUTH

## ★ XMAS BARGAINS ★

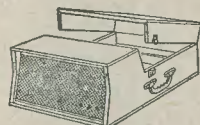

### RECORD PLAYER CABINETS from 39/9.

Latest contemporary style, rexine covered cabinets, in two-tone colour scheme. Hinged clipped lid. Carrying handle. Space available for all modern amplifiers and auto-changers, etc. Slightly store soiled. P. & P. 4/6.

**8" P.M. SPEAKERS 5/9.** A bargain offer, but limited quantity of these modern type speakers. All tested and "money back guarantee." They have a slight cone fault which is repaired, not affecting the quality. P. & P. on 1, 2/6; on 2, 3/6. Also an **8" P.M. SPEAKER 8/9.** An ideal gift if fitted in small cabinet. Complete with o.p. transformer fitted, 10/- P. & P. 2/9.

**EXTENSION SPEAKERS, 19/9.** Attractive cabinet. Complete with 8" p.m. speaker, flex and switch. Standard matching to any receiver 2-5 ohms. Size 11" x 13 1/2". A nice present and a real bargain. P. & P. 3/6.

**RECORD CASES.** In leatherette, various colours. Keep your records as new. Easy to transport when going to record sessions or parties. Hinged top, plated clip fasteners. Numbered index. Ideal Christmas gift or birthday.



12" holding 25 records 32/6  
12" holding 40 records 46/-  
7" holding 25 records 31/-  
7" holding 40 records 32/6 P. & P. 2/6 extra

## P. P. COMPONENTS LTD

**SOUND AND VISION STRIPS, 10/6.** 5/het. Takes 6 EF91, 1 6D2, 16 F14. Valves extra. Not tested. P. & P. 2/6.

**PLESSEY SOUND AND VISION STRIPS, 25/6.** S/het. Takes 6 6F1, 2 6D2. Valves extra. Tested. P. & P. 2/6.

**TIME BASE, 7/9.** With scanning coil, focus unit, line trans. Aluminium chassis. Less valves. Free drawing. P. & P. 3/6.

**POWER PACK AND AMPLIFIER, 12/6.** A must in every workshop. Smoothed h.t. 325V 250mA. L.T.s 4V, 6.3V and 4V centre tapped. P. & P. 3/9.

**MODULATOR 165, 8/9.** Will give 10 watts audio. Contains mod. trans., class B driver trans., mic. trans. and a host of conds., resist., etc. Ideal for a low power TX modulator. Less valves. Carr. 3/6. Valves (5) 28/9 extra.

**MAINS TRANSFORMER, 12/9.** 350-0-350V 250mA. 6.3V at 5A, 4V at 4A, 4V at 7A, 4V centre tapped at 1A. Prim. 200-250V 50 c/s. P. & P. 1/-

**HEATER TRANS., 1/9.** 4V to 6V at 3A. P. & P. 1/-

**O.P. TRANS., 1/3.** Std. matching 2-5 ohms. P. & P. 1/-, 20 for £1, P. & P. 5/6

**MAINS POWER TRANS., 12/6.** 350-0-350V 250mA. 22V at 0.3A, 6.3V at 4A, 6.3V at 0.08A, 4V centre tapped. P. & P. 3/9

**MAINS TRANSFORMER, 3/9.** 350-0-350V 80mA, 12V, 4V. 200-250V prim. P. & P. 2/3

**VISCONAL CONDENSERS, 5/9.** 0.001μF 12.5kV working. P. & P. 6d.

**VISCONAL CONDENSERS, 5/9.** 0.1-7kV working. P. & P. 6d.

**CAR AERIALS, 6/9.** Whip antennae. Plated, 50" long, collapsing to 11". One-hole fixing. P. & P. 1/-

(DEPT. C12) 219 ILFORD LANE ILFORD ESSEX  
Stamp for FREE Catalogue. Regret U.K. ONLY ILF 0295



**Forrest**

Transistor Transformers  
for Quality Equipment

H. W. FORREST (TRANSFORMERS) LTD.  
349 Haslucks Green Road Shirley Solihull  
Warwickshire Telephone SHrley 2483

**NYLON • P.T.F.E**

ROD BAR SHEET TUBE STRIP WIRE  
No quantity too small List on application  
BRASS COPPER BRONZE  
ALUMINIUM LIGHT ALLOYS  
H. ROLLET & CO LTD  
6 Chesham Place SW1 SLOane 3463  
Also at Liverpool Birmingham  
Manchester Leeds

LARGE STOCKS MANUFACTURERS' AND  
GOVERNMENT SURPLUS EQUIPMENT  
VALVES METERS CONDENSERS  
RESISTORS TRANSFORMERS CHOKES  
SWITCHES, ETC. Callers only. Usual shop hours

**N. R. BARDWELL & CO**

81/83/83A SELLERS STREET SHEFFIELD 8  
Telephone 52886

**BUILD YOUR OWN TAPE RECORDER**

Two-speed, twin track tape deck, kit of parts £8.5.0  
Amplifier kit £5.18.0; Power Pack kit £2.18.0. Both  
less valves. Send for full details of these excellent kits.  
Also available made up

WISEMAN'S

21A ANCASTER ROAD BECKENHAM KENT

**H.A.C. THE ORIGINAL SUPPLIERS  
OF SHORT-WAVE KITS**

One-valve Super Sensitive All-dry Short-wave Receiver  
Model "K." Complete kit including valve and chassis,  
77/-. (Other S.W. kits from 25/-.) Before ordering  
call and inspect a demonstration receiver, or send  
stamped envelope for full specification, catalogue and  
order form.

H.A.C. SHORT-WAVE PRODUCTS (DEPT. R)  
11 OLD BOND STREET LONDON W1

**CHASSIS** 18 s.w.g. aluminium. Strengthened  
corners. All 2 1/4" deep.

6" x 4" 4/- 10" x 7 1/2" 6/6 12" x 8" 8/-  
7 1/2" x 5 1/2" 5/6 11 1/2" x 7 1/2" 7/6 14" x 9" 11/-  
Prompt service. Add 1/- post and packing. Orders over  
£1 post free. Any published chassis available. Enquiries  
invited. Latest addition—Cooper-Smith Prodigy, 16/-.

**SWEETNAM & BRADLEY**

BRISTOL ROAD · MALMESBURY · WILTS

**BOUND VOLUMES**

Vol. 11, August '57 to July '58  
inclusive, attractively bound in  
blue cloth, with gold blocked  
spine, price £1.5.0. post 1/9

**DATA PUBLICATIONS LTD**

57 MAIDA VALE · LONDON W9

**SMALL ADVERTISEMENTS**

continued from page 399

**TRADE—continued**

**JOIN THE INTERNATIONAL S.W. LEAGUE.**

Free Services to members including Q.S.L. Bureau  
Translation. Technical and Identification Dept.—  
both Broadcast and Fixed Stations, DX Certificates,  
contests and activities for the SWL and transmitting  
members. Monthly magazine, "MONITOR" con-  
taining articles of general interest to Broadcast and  
Amateur SWL's, Transmitter page and League  
affairs, etc. League supplies such as badges, headed  
notepaper and envelopes. QSL cards, etc., are  
available at reasonable cost. Send for League  
particulars. Membership, including monthly maga-  
zine, etc., 15s. per annum.—Secretary, ISWL, 86  
Barrenger Road, London, N.10.

PANL, recognised for many years as the unique one-  
coat black crackle finish. Brush applied, no baking.  
Available by post in 4th pint cans at 3s. 9d. from  
G. A. Miller, 255 Nether Street, London, N.3.

LEARN as you do it—we provide practical equipment  
combined with instructions in Radio, Television,  
Electricity, Mechanics, Chemistry, Photography, etc.  
—Write for full details to E.M.I. Institutes, Dept.  
RC47, London, W.4.

THE INTERNATIONAL HAM HOP CLUB is a  
non-profit-making organisation open to RADIO  
AMATEURS AND SHORT WAVE LISTENERS. OBJECT:  
To improve international relationships through an  
organised system of hospitality. MEMBERS offer over-  
night hospitality to visiting members, entrance fee  
2s. 6d. ASSOCIATE MEMBERS invite radio amateurs  
to visit their stations, S.A.E. for FREE Associate  
membership. FAMILY EXCHANGE holidays arranged,  
also FRIENDSHIP LINKS between radio clubs. H.H.C.'s  
official journal, *Ham Hop News*, 5s. per annum.  
Hon. Gen. Secretary: G. A. Partridge, G3CED,  
17 Ethel Road, Broadstairs, Kent.

INCORPORATED Practical Radio Engineers home  
study courses of radio and TV engineering are  
recognised by the trade as outstanding and authorita-  
tive. Moderate fees to a limited number of students  
only. Syllabus of Instructional Text is free. *The  
Practical Radio Engineer*, journal, sample copy 2s.  
6,000 Alignment Peaks for Superhets, 5s. 9d.  
Membership and Entry Conditions booklet, 1s., all  
post free from the Secretary, I.P.R.E., 20 Fairfield  
Road, London, N.8.

FREE. Brochure giving details in Home Study Training  
in Radio, Television and all branches of Electronics.  
Courses for the hobby enthusiast or for those  
aiming at the A.M.Brit.I.R.E., City and Guilds,  
R.T.E.B., with other Professional examinations.  
Train with the college operated by Britain's largest  
Electronics organisation. Moderate fees.—Write  
to E.M.I. Institutes, Dept. RC28, London, W.4.

SERVICE SHEETS for sale and hire. Radio/Te-  
levision. S.A.E. enquiries.—J. Palmer, 32 Neasden  
Lane, London, N.W.10.

"MEDIUM WAVE NEWS," monthly during DX  
season.—Details from B. J. C. Brown, 196 Abbey  
Street, Derby.

**SMALL ADVERTISEMENTS**

Readers' small advertisements will be accepted  
at 3d. per word, including address, minimum  
charge 2/-. Trade advertisements will be  
accepted at 9d. per word, minimum charge 6/-.  
If a Box Number is required, an additional  
charge of 2/- will be made. Terms: Cash with  
order. All copy must be in hand by the 12th  
of the month for insertion in the following  
month's issue. The Publishers cannot be held  
liable in any way for printing errors or  
omissions, nor can they accept responsibility  
for the bona fides of advertisers.



**SCOTTISH INSURANCE  
CORPORATION LIMITED**

**TELEVISION SETS  
RECEIVERS and TRANSMITTERS**

Television Sets, Receivers and Short Wave Transmitters are  
expensive to acquire and you no doubt highly prize your instal-  
lation. Apart from the value of your Set, you might be held  
responsible should injury be caused by a fault in the Set, or  
injury or damage by your Aerial collapsing.

A "Scottish" special policy for Television Sets, Receivers and  
Short Wave Transmitters provides the following cover:

- (a) Loss or damage to installation (including in the case of  
Television Sets the Cathode Ray Tube) by Fire, Explosion,  
Lightning, Theft or Accidental External Means at any  
private dwelling-house.
- (b) (i) Legal Liability for bodily injury to Third Parties or  
damage to their property arising out of the breakage  
or collapse of the Aerial Fittings or Mast, or through  
any defect in the Set. Indemnity of £10,000 any one  
accident.
- (ii) Damage to your property or that of your landlord  
arising out of the breakage or collapse of the Aerial  
Fittings or Mast, but not exceeding £500.

The cost of Cover (a) is 5/- a year for Sets worth £50 or less,  
and for Sets valued at more than £50 the cost is in proportion.  
Cover (b) and (ii) costs only 2/6 a year if taken with Cover (a),  
or 5/- if taken alone.

Why not BE PRUDENT AND INSURE your installation  
—it is well worth while AT THE VERY LOW COST  
INVOLVED. If you will complete and return this form to  
the Corporation's Office at the address below, a proposal will  
be submitted for completion.

NAME (Block Letters) .....

(IF LADY, STATE MRS. OR MISS)

ADDRESS (Block Letters) .....

/JB

**62-63 Cheapside London EC2**