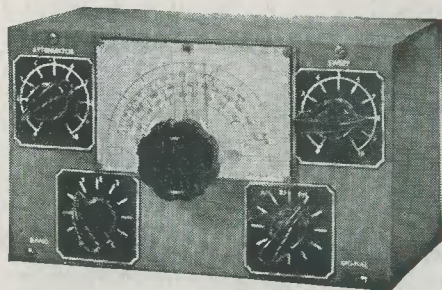


PUBLISHED IN CONJUNCTION WITH  
THE  
**RADIO CONSTRUCTOR**

**Panel-Signs  
Transfers**



**Set No. 1—RECEIVERS AND AMPLIFIERS**

Five sheets  $8\frac{1}{2}$ in x  $5\frac{1}{2}$ in, including one large scale 6in x 4in (0-100 graduations in 4 bands), twelve control panels  $1\frac{1}{8}$ in x  $1\frac{1}{8}$ in, and two sheets of white wording, figures and symbols.

**Set No. 2—TEST EQUIPMENT**

Five sheets  $8\frac{1}{2}$ in x  $5\frac{1}{2}$ in, containing two medium scales 4in x  $2\frac{3}{4}$ in approx. (may be "married" for R-C Bridges), twelve control panels  $1\frac{1}{8}$ in x  $1\frac{1}{8}$ in, and two sheets of white wording, figures and symbols.

**Set No. 3—WORDING**

Five sheets, including four of appropriate wording, for Receivers, Amplifiers, Transmitters, Test Equipment, and other Radio Apparatus. Also included are Transistor symbols, six alphabetic sets A-Z, and six sets of figures 0-9. One sheet of Station Names. Over 750 words and symbols in all. White, no background.

**Set No. 4—WORDING**

As Set No. 3, but wording in black.

(Each Set is contained in a strong envelope giving full instructions for fixing)  
All Panel-Signs Transfers 3/6 per Set. Postage 2d.

**DATA PUBLICATIONS LTD**

57 MAIDA VALE LONDON W9

Telegrams Databux London

Telephone CUNningham 6141/2

Published in Great Britain by the Proprietors and Publishers  
Data Publications Ltd 57 Maida Vale London W9

Printed by A. Quick & Co. (Printers) Ltd 125 High Holborn London WC1 England also at Clacton-on-Sea  
Obtainable abroad through the following Collets Subscription Service Continental Publishers & Distributors Ltd  
William Dawson & Sons Ltd Australia and New Zealand Gordon & Gotch Ltd South Africa Central News Agency  
Holland "Radio Electronica"  
Registered for transmission by Magazine Post to Canada (including Newfoundland)

GETTING STARTED ON RTTY


VOLUME 13  
NUMBER 4  
NOVEMBER  
1959

The  
**RADIO  
Constructor**



RADIO · TELEVISION · AUDIO · ELECTRONICS

**CRYSTAL CALIBRATOR CC10**

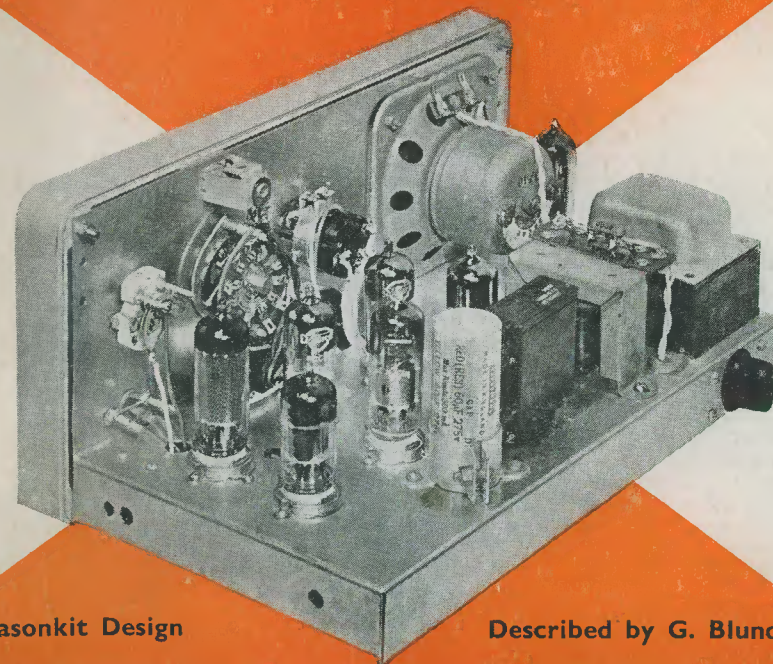

A Jasonkit Design

Described by G. Blundell

Included in this issue  
DO-IT-YOURSELF PRINTED CIRCUITS  
TRANSISTORS IN HYBRID CIRCUITS  
THE "DIFFERENT" HI-FI UNIT  
A REED RADIO-CONTROL RECEIVER  
"VIBRATO" UNIT FOR ELECTRONIC GUITARS  
V.H.F. AERIALS, etc., etc.

**DATA  
Publications 1/9**



## THE MODERN BOOK CO

**Servicing Transistor Radios.** By L. D'Airo. 23s. Postage 1s.

**TV Fault Finding.** A Data Publication. 5s. Postage 6d.

**How to Get the Best out of Your Tape Recorder.** By P. J. Guy. 8s. 6d. Postage 6d.

**Electronic Hobbyists' Handbook.** By R. P. Turner. 20s. Postage 8d.

**Quality Amplifiers for A.C. Mains.** A Data Publication. 4s. 6d. Postage 6d.

**Brimar Valve and Teletube Manual, No. 8.** 6s. Postage 9d.

**Radio Valve Data.** Compiled by "WW". 6th Ed. 5s. Postage 9d.

**Mullard Circuits for Audio Amplifiers.** 8s. 6d. Postage 1s.

**Television Servicing Handbook.** By G. J. King. 30s. Postage 1s. 3d.

**The All-in-One Tape Recorder Book.** By J. M. Lloyd. 12s. 6d. Postage 8d.

**Radio Engineering Formulae and Calculations.** By W. E. Pannett. 17s. 6d. Postage 8d.

**A Beginner's Guide to Radio.** By F. J. Camm. 7s. 6d. Postage 6d.

**Guide to Mobile Radio.** By L. G. Sands. 22s. Postage 9d.

**Elementary Telecommunications Examination Guide.** By W. T. Perkins. 17s. 6d. Postage 9d.

We have the Finest Selection of British and American Radio Books in the country  
Complete catalogue 6d.

19-23 PRAED STREET (Dept RC) LONDON W2

Telephone PADdington 4185

## MINIATURISE & PROFESSIONALISE with your own Printed Circuitry . . .

ETCH-Your-OWN Kits give every constructor the opportunity of turning out a dozen and one novel pocket-sized units or building more elaborate apparatus from two or three highly efficient sub-assemblies with losses and stray capacities cut to a minimum.

Each kit contains more than sixty square inches of laminated board and sufficient chemicals to make dozens of printed circuits: additional laminated board can be supplied to order. All materials are of high quality completely safe to handle, and are carefully prepared to ensure fine definition and consistently satisfactory results without laboratory technique or precision control.

Supplied complete with specially comprehensive instruction book giving advice and examples on translating theoretical circuits into printed circuit layouts ready for etching.



SEE SPECIAL ARTICLE IN THIS ISSUE  
KIT REVIEWED IN OCTOBER ISSUE

**ETCH-YOUR-OWN**  
**21/-** Printed Circuits  
POST FREE

**PROOPS BROS. LTD.** Open all day Saturday  
Dept R, 52 Tottenham Ct. Rd. W1

Hours 9-6 p.m. Thursdays 9-1 p.m. Telephone LANGham 0141


# CQ . . . CQ . . . CQ . . . HAMS



## QTR?

time you  
bought a

# MULTIMINOR

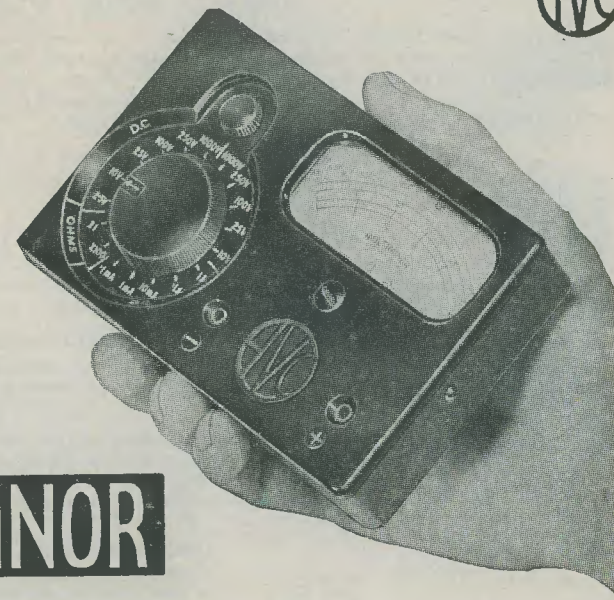

## OM!

This splendid AVO Instrument has been developed to meet a definite demand for a sturdy pocket-size multi-range test meter at a modest price, suitable for use on modern electronic apparatus as well as for radio and television receivers, motor vehicles, and all kinds of domestic appliances and workshop equipment.

Readings are obtainable quickly and easily on a very open scale, and range selection is by means of a robust clearly marked rotary switch of the characteristic AvoMeter type. Measurements of A.C. and D.C. Voltage, D.C. Current and Resistance are made by means of only two connection sockets.

List Price: **£9. 10s.**

complete with Test Leads and Clips  
Leather Case if required 32/6

Size:  $\frac{3}{4}$  x  $3\frac{1}{2}$  x  $1\frac{1}{2}$  inches  
Weight: 1lb approx.

Write for fully illustrated pamphlet

### 19 RANGES

D.C. Voltage	A.C. Voltage
0-100mV	0-10V
0-2.5V	0-25V
0-10V	0-100V
0-25V	0-250V
0-100V	0-1000V
0-250V	
0-1000V	

D.C. Current
0-100µA
0-1mA
0-10mA
0-100mA
0-1A

Resistance
0-20,000Ω
0-2MΩ

**Sensitivity**  
10,000 Ω/V on D.C. voltage ranges  
1,000 Ω/V on A.C. voltage ranges

**Accuracy**  
3% of full scale value on D.C.  
4% of full scale value on A.C.


To meet special requirements, instruments can be supplied to a higher degree of accuracy for a small additional charge

**AVO LTD** AVOCET HOUSE · 92-96 VAUXHALL BRIDGE ROAD · LONDON · SW1  
Telephone VICtoria 3404 (12 lines)





Here are our **NEW** models

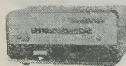

FM TUNER

**FM TUNER.** This model is available as two units which, for your convenience, are sold separately. They comprise a Tuner Unit, Model FMT-4U (£32.0 including Purchase Tax) and an Amplifier Unit complete with attractively styled cabinet, power supply and valves, Model FMA-4U (£10.10.6) making a total cost for the equipment of £13.12.6.



DX-100U

**DX-100U AMATEUR TRANSMITTER.** The DX-100 is the most popular Amateur transmitter in the world and requires no introduction to 'Hams' the world over. £78.10.0



CM-1U

**ELECTRONIC SWITCH (TRACE DOUBLER) MODEL S-3U.** This extremely useful low-priced device will extend the application of your single-beam oscilloscope by enabling it to give simultaneous traces of two separate and independent signals. £9.18.6




RP-1U

**DIRECT READING CAPACITANCE METER MODEL CM-1U.** Full-scale ranges of 100 micro-microfarad, 1,000 micro-microfarad, 0.01 microfarad and 0.1 microfarad. Easily built in a few hours. £14.10.0

**TRANSCRIPTION RECORD PLAYER, RP-1U.** This new RP594 Collaro Transcription Unit has a Ronette Stereo Pick-up, giving excellent results on stereo or mono (33, 45 or 78 r.p.m.) discs. Complete with furniture-grade wooden plinth. £12.10.0


**THE "GLOUCESTER".** It will house Tape Deck and/or Record Player—as well as FM Tuner and Stereo Amplifier, and storage space is provided for records, tapes and power amplifiers. Furthermore, to meet the needs of those with whom room-space is an overriding consideration, provision is made in the cabinet ends for matched Hi-Fi Stereo Speaker Systems.

**THE "COTSWOLD".** This is an acoustically designed enclosure 26" x 23" x 14½" housing a 12" bass speaker with 2" speech coil and foam surround, together with a pressure unit to cover the full frequency range of 32–20,000 c/s. Capable of doing justice to the finest programme source, its polar distribution makes it ideal for really Hi-Fi Stereo. Delivered complete with speakers, cross-over unit, level control, Tygan grille cloth, etc. All parts pre-cut and drilled for ease of assembly and left "in the white" for finish to personal taste. £19.18.6

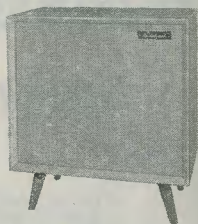

THE "COTSWOLD"

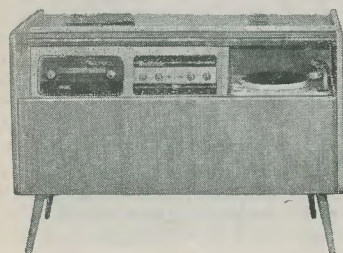
- Mk. I Tape Deck or Record Player ..... £15.18.6
- Mk. II Tape Deck and Record Player ..... £17.8.6



THE "GLOUCESTER"

← open

closed →

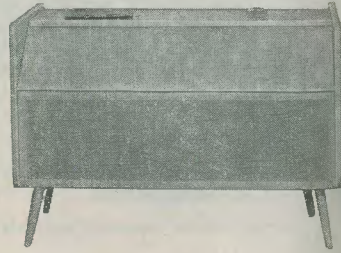

Easy to build, first-class components and excellent performance

PRODUCED BY

**DAYSTROM LTD**

GLOUCESTER

# You can build **HEATHKIT** models easily and save

## £££s

### EXAMPLES

**CAPACITANCE/RESISTANCE BRIDGE C-3U.** Measures capacity, 10pF to 1,000µF; Resistance, 100Ω to 5MΩ; Pwr. F.ctr. £7.19.6 (Not illustrated)

**AUDIO GENERATOR: AG-9U.** 10 volts, 10 c/s to 100 kc/s pure sine-wave. Switch-selected frequencies/attenuation. £19.3.0

**HI-FI SPEAKER SYSTEM: SSU-1.** Ideal twin speaker/ducted-reflex cabinet for stereo/mono. in average room (left "in the white") Legs £1.7.0 extra. £10.5.6

**HI-FI STEREO 6 WATT AMPLIFIER: S-33.** Low priced but high quality; less than 0.3% distn at 2½ watts per channel. £11.8.0

**TRANSISTOR PORTABLE: UXR-1.** In elegant solid hide case, with golden relief. Six transistors, dual-wave, fine reproduction, very easy to build. £15.18.6

**HI-FI STEREO BOOSTER: USP-1.** Input of 2 to 20mV gives output adjustable from 20mV to 2V. Negligible distn. £5.19.6

**HI-FI STEREO 16 WATT AMPLIFIER: S-88.** Superb reproduction for the man who wants the best in Hi-Fi. Only 0.1% distortion at 6 W/chnl. Many special features. £25.5.6

**5" OSCILLOSCOPE: O-12U.** "Y" sensitivity 10mV/cm., 3 c/s to over 5 Mc/s Rise time, 0.08 µsecs. or less. Sweep, 10 c/s to 500 kc/s. Electronically stabilised. £34.15.0

**VALVE VOLTMETER: V-7A.** The World's largest-selling VVM. Measures Volts to 1500 (DC & RMS) and 4000 pk. to pk.; Resistance 0.1Ω to 1000MΩ. Sensitivity: 7,333,333 Ohms per volt. £13.0.0

(Following models not illustrated)

**"HAM" TRANSMITTER: DX-40U.** 75 W. CW; 60 W. pk. c/c phone; 40 W. into Aerial. £29.10.0

**VARIABLE FREQUENCY OSCILLATOR: VF-1U.** 10V. output; covers 10 to 160 metres. £10.12.0


**AUDIO WATTMETER: AW-1U.** Up to 25 W. continuous, 50 W intermittent. £13.18.6

**AUDIO VALVE-MILLIVOLTMETER: AV-3U.** 1mV to 300V AC. 10 c/s to 400 kc/s. £13.18.6


**AT LAST! COMPLETE MATCHED STEREO OUTFIT** comprising record player, amplifier and twin speaker systems. **£42.10.0**




VALVE VOLTMETER Model V-7A

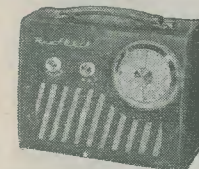

TRANSISTOR PORTABLE Model UXR-1

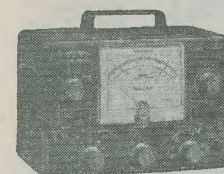


AUDIO GENERATOR Model AG-9U

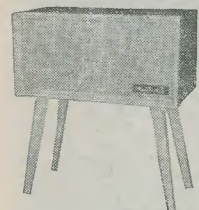


HI-FI SPEAKER SYSTEM Model SSU-1




HI-FI STEREO AMPLIFIER S-33

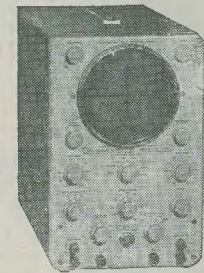

5" OSCILLOSCOPE Model O-12U

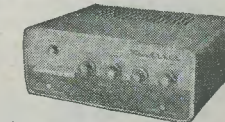

HI-FI STEREO AMPLIFIER S-88

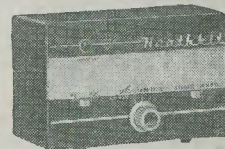

HI-FI STEREO BOOSTER Model USP-1



The range is growing fast! SEND THIS COUPON NOW FOR FREE CATALOGUE

(Please write in BLOCK CAPITALS)

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

ALL PRICES INCLUDE FREE DELIVERY IN U.K. AND ANY P.T. (Deferred terms are available)

Without obligation please send (Tick here)


BRITISH HEATHKIT CATALOGUE

FULL DETAILS OF MODEL(S)

**DAYSTROM LTD.** DEPT. RC11 GLOUCESTER, ENGLAND

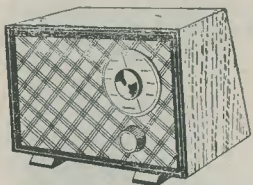A member of the Daystrom Group, manufacturers of the WORLD'S LARGEST-SELLING ELECTRONIC KITS





**THE SKYSEARCHER**  
1960 Version uses Mains Transformers

This is a three valve receiver kit using modern circuitry. Ideal as a second set for the bedroom, workshop, etc. All parts including mains transformer, valves, resistors, coils, etc., but not cabinet, chassis or speaker, 29/6, plus post and ins., 3/6. Data free with parts or available separately 1/6.

1960 ALL MAINS AMPLIFIER



Undoubtedly finest value obtainable in amplifiers—powerful three valve circuit ideal for dances, parties, etc. Complete with valves, mains transformers, volume and tone controls, but less chassis, speaker and cabinet. Price only 29/6 plus 2/6 post and ins. Data free with parts or available separately 1/6.

**BEGINNER'S SUPERHET**

As supplied to many schools and colleges. A simple basic superhet—easy to understand and which can be progressively extended—ideal for students; components include valves, metal rectifier tuning condenser, I.F. transformers, etc. In fact complete superhet except speaker. Price £3 plus 3/- post and insurance. Data included free or sep. 1/6.



**RECTIFIER BARGAINS**

Selenium rectifier type 12, 500 volts. 1/2 amp. half-wave, easily rebuilt into full wave or multiple type, contains 30 35mm discs. Price 8/6, plus 1/6 post. Type 13, 36 volt 9 amp. easily rebuilt into six full wave charger rectifiers suitable for 6 or 12 volt batteries at 3 amps., contains 24 84mm discs. Real bargain at 19/6, plus 1/6 post. Type 14 240 volts 1/2 amp. 7/6.

**Unique Opportunity to build Fine Transistor Set**

Constructor's parcel to build Pocket 6 Transistor Set as currently being sold at £17.17.0. Parcel comprises modified two-tone cabinet as illustrated, tuning dial, two gang tuning condenser, combined bakelite chassis/printed circuit and easy-to-follow circuit. Costing value 57/6—offered while supplies last at only 29/6, plus 2/6 post. Suitable for your own circuit or to build original circuit. All parts available at highly competitive prices. Do not miss this tremendous bargain.



**COMPONENTS WOULD COST MORE**

Car Battery Charger—ready-made high output battery charger in stove-enamelled sheet steel louvered case. New, complete and ready to work, rated at 12V 4 amps. and variable rate selector for trickle charging, also a meter to show charging rate. Suitable for 230/250 A.C. mains. Special snip price of 55/-, plus 3/6 post and ins.



**SIX USEFUL ARTICLES**

Our 1960 catalogue now ready gives constructional hints and circuits for the following items: Moisture-operated switch; Simple but clever signal tracer; Versatile power pack costing only 10/-; Instantaneous heater for workshop or den; Six transistor pocket superhet; Simple bed warmer; Photo-flood controller. Send for this catalogue today—price 2/6 refundable from purchases.

**A.C./D.C. MULTIMETER KIT**

Ranges: D.C. volts 0-5, 0-50, 0-100, 0-500 0-1,000. A.C. volts 0-5, 0-50, 0-100, 0-500 0-1,000. D.C. milli-amps 0-5, 0-100, 0-500. Ohms 0-50,000, with internal batteries. 0-500,000 with external batteries. Measures A.C./D.C. volts. D.C. current and ohms. All the essential parts including metal case 2" moving coil meter, selected resistors, wire for shunts, range selector, switches, calibrated scale and full instructions, price 19/6, plus 2/6 post and insurance.



**BAND III CONVERTERS**


Suitable Wales, London, Midlands, North, Scotland, etc. All the parts including 2 EF80 valves, coils, fine tuner, contrast control, condensers and resistors. (Metal case available as an extra). Price only 19/6, plus 2/6 post and insurance. Data free with parts or available separately, 1/6. Please send two more kits, the one you sent last week is performing magnificently. We receive this sort of letter every day of the week, so if you have hesitated because you thought our kits too cheap you need hesitate no longer.



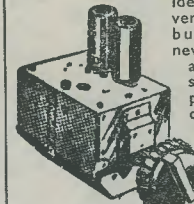**12-CHANNEL TURRET TUNER**


Ideal for converting an old or building into new TV. These are brand new stock, not surplus, supplied complete with valves and coils for local Band I and Band III stations. Model 1.

I.F. Output 33/38 Mc/s series heaters (parallel heaters, 5/- extra). Model 2. I.F. Output 16/19 Mc/s parallel heaters (series heaters, 5/- extra). With instructions and circuit diagram 79/6, knobs 3/6 extra, postage and insurance 2/6.



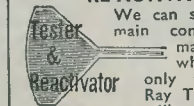**TUBE TESTER AND RE-ACTIVATOR**

We can supply all the main components for making this unit which will not only test Cathode Ray Tubes but also will re-activate them. Supplied complete with full instructions. Price £3, plus 2/6 post and ins.



**TV SERVICE SHEETS**

200 sheets covering most popular post-war televisions by leading makers—Cossor, Ekco, Ferguson, Pye, etc., £2 post free. PREVIOUS PURCHASERS OF THESE SHEETS PLEASE NOTE: WE CAN SUPPLY SHEETS Nos. 100-200, £1, or 150-200 10/-.

**MINIATURE MICROPHONE**


American make Dynamic type, real bargain at 2/6, plus 6d. postage.



**T.S.L. LORENZ SUB-MINIATURE SPEAKERS FOR TRANSISTOR SETS**

The application of transistors to small radio receiver design brings with it the need for miniature loudspeakers of good performance with "transistor characteristics" in order to take full advantage of transistor outputs. The two presented here will be found to conform ideally with the requirements involved.


**MODEL LP. 70**

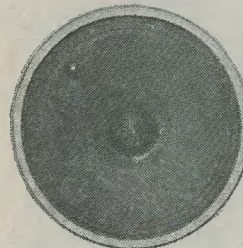

2 1/2" diam. x 1 1/4" deep. Will convert as little as 4 milliwatts loading into a loud, clearly audible signal. Special cone suspension ensures wide range response from 120 to 14,000 c.p.s. Impedance 3 ohms. Very small receivers with 1/2 watt class B output become a practical proposition with this unit.

inc. P/tax **25/-**

**MODEL LP. 31**

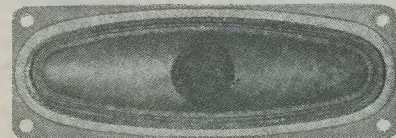

High quality elliptical speaker 4" x 1 1/2" x 1" overall. Response 120-14,000 c.p.s. Impedance 3 ohms. Loading 4 to 500 milliwatts. Enables a battery radiogram to be built only 2" in depth. The cone is specially suspended within a chassis of specially robust construction, and as such the LP.31 may also be used to advantage in larger instruments.


Price, inc. P/tax **24/-**

From your usual equipment stockist. Leaflet together with latest catalogue of constructors' handbooks free on request.

**TECHNICAL SUPPLIERS LTD**

Hudson House 63 Goldhawk Rd. London W12

Telephone SHEpherds Bush 2581 and 4794

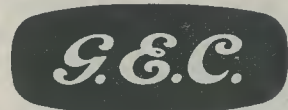

**TRANSISTOR AUDIO AMPLIFIERS**

**250 mW** Class B push-pull using GET114 transistors, operating from a 6V supply. Class B single-ended push-pull (Transformerless) using GET114 transistors, operating from a 9V supply.

**500 mW** Class B push-pull using GET114 transistors, operating from a 6V supply. Class B single-ended push-pull (transformerless) using GET114 transistors, operating from a 9V supply.

**1 W** Class B push-pull using GET114 transistors, operating from a 6V supply. Class B single-ended push-pull (transformerless) using GET114 transistors, operating from a 12V supply.

**2 W** Class B push-pull using GET116 transistors, operating from a 12V supply.


**3 W** Class B single-ended push-pull (transformerless) using GET115 transistors (mounted on 3" x 3" fins) operating from a 12V supply.

These are a selection from the range of audio amplifier circuits using G.E.C. transistors. For details of any of these circuits or information on the wide range of G.E.C. transistors, please write to:

G.E.C. SEMICONDUCTOR DIVISION,  
School Street, Hazel Grove,  
STOCKPORT, CHESHIRE.



## D.C. OSCILLOSCOPE

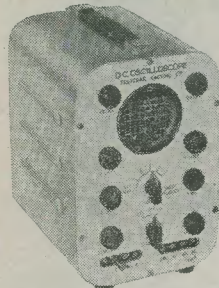


A.C. MAINS 200-250V.  
Simplified Servicing  
Problems When using

The  
**'TESTGEAR' SCOPE**  
3" D.C. Oscilloscope  
Engineered to precision  
standards, this high-grade  
instrument is made  
available at the lowest  
possible price, incor-  
porating the essential  
features usually associ-  
ated with luxury instru-  
ments.

This "Scope" will appeal  
particularly to Service Engineers and Amateurs. A  
high gain, extremely stable differential Y-  
amplifier (30 mV/C.M.). Provides ample sensitivity  
with A.C. or D.C. inputs. Especially suitable for  
measurement of transistor operating conditions  
where maintenance of D.C. levels is of paramount  
importance. Push-pull X amplifier; Fly-back suppres-  
sion; Internal Time-base Scan Waveform available for  
external use; pulse output available for checking TV  
Line O/P Transformers, etc.; Provision for external  
X I/P and CRT. Brightness Modulation. Size 10"  
high, 6 1/2" wide, 9" deep. Wgt. 11 1/2 lb. £15.15.0 plus  
P. & P. 7/6, or 30/- deposit, plus P. & P. 7/6 and 12  
monthly payments of 26/6. Full 12 months'  
Guarantee including Valves and Tube
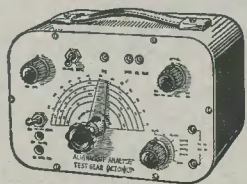
## ALIGNMENT ANALYSER TYPE MC12

A.C. mains 200/250V.  
Provides: "Wobblu-  
lator" (Swept  
Frequency) opera-  
tion, for FM/TV  
alignment linear fre-  
quency sweep up to  
12 Mc/s. From 400  
kc/s-80 Mc/s. Capac-  
itance Measure-  
ment. Two ranges  
provided 0-60pF and  
0-120pF. Special Facility enables true resonant  
frequency of any tuned cct. I.F. transformer, etc., to  
be rapidly determined. Cash price £6.19.6 plus 5/-  
P. & P. H.P. terms 25/- deposit plus 5/- P. & P. and  
six monthly payments of 21/6.



## 8 WATT PUSH-PULL AMPLIFIER

Complete with Crystal  
Mike and 8" Loud-  
speaker

A.C. mains 200/250V.  
Size 10 1/2" x 6 1/2" x 2 1/2".  
Incorporating 6 valves,  
H.F. pen., 2 triodes, 2  
output pens., and recti-  
fier. For use with all  
makes and types of pick-  
up and mike. Negative  
feed back. Two inputs,  
mike and gram., and  
controls for same.  
Separate controls for


Bass and Treble lift. Response flat from 40 cycles to  
15 kc/s, ±2dB; 4dB down at 20 kc/s. Output 8 watts  
at 5% total distortion. Noise level 40dB down, all  
hum. Output transformer tapped for 3 and 15 ohm  
speech coils. For use with Std. or L.P. records,  
musical instruments such as Guitars, etc. £4.19.6  
Plus P. & P. 7/6. Or £1 deposit, plus P. & P. 7/6 and 4  
monthly payments of 23/-.

## RADIO AND TV COMPONENTS (ACTON) LTD

23 ACTON HIGH STREET LONDON W3

GOODS NOT DESPATCHED OUTSIDE U.K. ALL ENQUIRIES S.A.E. TERMS OF BUSINESS C.W.O.

## SIGNAL GENERATOR

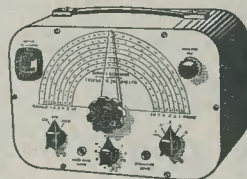


£6.19.6 or 25/- de-  
posit and 6 monthly  
payments of 21/6.  
P. & P. 5/- extra.  
Coverage 100 kc/s-  
100 Mc/s on funda-  
mentals and 100  
Mc/s to 200 Mc/s  
on harmonics.  
Metal case 10" x 6 1/2"  
x 5 1/2", grey hammer  
finish. Incorporating  
three miniature valves and Metal Rectifier. A.C.  
Mains 200/250V. Internal Modulation of 400 c.p.s. to  
a depth of 30%; modulated or unmodulated R.F.,  
output continuously variable. 100 milli-volts, C.W.  
and mod switch, variable A.F. output. Incorporating  
magic-eye as output indicator. Accuracy ±2%.


three miniature valves and Metal Rectifier. A.C.  
Mains 200/250V. Internal Modulation of 400 c.p.s. to  
a depth of 30%; modulated or unmodulated R.F.,  
output continuously variable. 100 milli-volts, C.W.  
and mod switch, variable A.F. output. Incorporating  
magic-eye as output indicator. Accuracy ±2%.
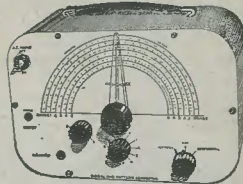
## Signal and Pattern Generator

25/- deposit plus  
P. & P. 5/- and 6  
monthly payments of  
21/6. Cash £6.19.6  
plus P. & P. 5/-.  
Coverage 7.6 Mc/s-  
210 Mc/s in five  
bands, all on funda-  
mentals, slow-  
motion tuning, audio  
output, 8 vertical  
and horizontal bars,  
logging scale. In grey hammer finished case with  
carrying handle. Accuracy ±1% A.C. mains 200-250V.




## B.S.R. MONARCH UA8 with STEREO HEAD

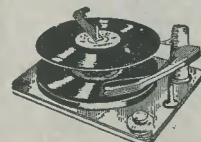

4-speed plays 10 records  
12", 10", or 7" at 33, 45  
or 78 r.p.m. Intermixes 7"  
10" and 12" records of  
the same speed. Has  
manual play position;  
colour brown. Dimen-  
sions: 12 1/2" x 10 1/2". Space  
required above baseboard  
4 1/2", below baseboard 2 1/2". Fitted with Full-Fi turnover  
crystal head. £7.19.6 Plus 5/- P. & P. (with standard  
head. £6.19.6 Plus 5/- P. & P.)
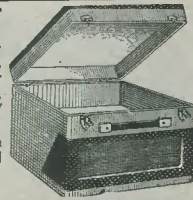
## PLAYER CABINET

Finished in 2-tone leather-  
ette, will take B.S.R. UA8,  
with room for amplifier  
and 7" x 4" speaker.  
Overall size 15 1/2" x 13 1/2"  
x 9 1/2".  
Similar to the above in  
POLISHED WALNUT, will  
take Collaro  
39/6 Plus 5/- P. & P.



## 2-TRANSISTOR POCKET RADIO

Plus Germanium diode, fully tuneable over medium  
and long waves. Size 3 1/2" x 4 1/2" x 1 1/2". Complete set of  
components including case, 2 transistors and earpiece  
(less batteries). 19/6 Plus P. & P. 1/6. Point to Point  
wiring diagram 1/6. (Free with kit).

## PUSH-PULL OUTPUT STAGE

Inclusive of transistors with input and output trans-  
formers to match 3 ohm speech coil, suitable for use  
with the above kit. Complete kit of parts including  
transistors. 19/6 Plus P. & P. 1/6. Point to Point  
wiring diagram 1/6 (Free with kit).

Get these  
**FREE**  
CIRCUITS  
&  
WIRING DIAGRAMS

T.R.F. Circuits Mains Circuits Send  
Battery Circuits Filter Circuits 1/-  
Portable Circuits TV Converter Circuits (stamps)  
S'het Circuits etc., etc.

OSMOR COILS are regularly used and recommended  
by designers writing in "Practical Wireless," "Wireless  
World" and "Radio Constructor." Why not follow  
the experts?

"Q COILS" • POTTED COILS • FM COILS  
All ranges • SPEAKER CROSS-OVER COILS

TAPE COILS • ROD AERIALS  
SUB MINIATURE COILS

COILS and I.F.s for Transistor Circuits • MIDGET I.F. TRANS With ferrite cores

**OSMOR**

418 Brighton Road  
South Croydon  
Telephone CRO 5148/9

## Ask "ARTHURS" First

NOTE NEW ADDRESS AT  
125 Tottenham Court Road  
London WC1  
Close to Warren Street Station

You will have the same service and obtain  
all your requirements in Radio Components,  
Electrical Goods, Accessories and Television  
as previously.

Test Instruments in stock include Avo,  
Advance, Cossor and Taylor. List on request

VALVE MANUALS AVAILABLE  
Mullard 10/6 Brimar No. 7 6/-  
Osram Part 1, 2nd Edition 7/6  
Post and packing 9d. each extra

**Arthurs** first  
Est. 1919

Proprietors ARTHUR GRAY LTD

Gray House  
125 Tottenham Court Road  
London WC1  
Telephone EUSton 5802/3/4

The COMPLETE introduction to the theory  
and applications of f.m.

# PRINCIPLES OF FREQUENCY MODULATION

by B. S. Camies

This new book gives in concise form and logical sequence a comprehensive account  
of the fundamentals of frequency modulation and its applications. It covers f.m.  
receivers, f.m. in transmitters, and the use of f.m. in microwave links, in radar,  
in telegraphy and in facsimile transmission. Many numerical examples show how  
simple design calculations may be performed.

21s net by post 21s 10d from leading booksellers

Published for "Wireless World" by


Iliffe & Sons Ltd Dorset House Stamford Street London SE1



# LASKY'S RADIO

THE LARGEST AND MOST COMPREHENSIVE  
STOCKS FOR ALL CONSTRUCTORS AND  
HIGH FIDELITY ENTHUSIASTS

## TAPE DECK OFFERS

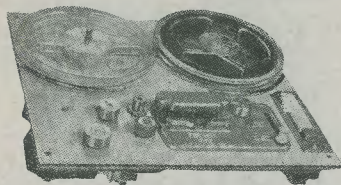

**TRUVOX** Mk. III. New in maker's cartons. 2-spd., 3 $\frac{3}{8}$  and 7 $\frac{1}{2}$ , 3 shaded pole B.T.H. motors, twin track, high impedance heads, push-button controls. Takes standard 7" spools. List 22 gns. Lasky's Price **£14.19.6**

Latest **B.S.R. "MONODECK."** Single speed, 3 $\frac{3}{8}$  i.p.s. Takes 5 $\frac{3}{8}$ " spools. Simple controls, **£9.19.6**.

Latest **COLLARO** Studio Tape Transcriber, 3-spd., 1 $\frac{7}{8}$ , 3 $\frac{3}{8}$  and 7 $\frac{1}{2}$ , fitted with digital counter. Takes 7" spools. Push-button controls, **£15.19.6**.

**COLLARO** Mk. IV Tape Transcriber, 3-spd., fitted digital counter, **£17.19.6**.

Carr. and Insur., all Tape Decks, 12/6, Tape extra.


## 4-Spd. AUTO-CHANGERS

Brand new in maker's cartons.

Latest **B.S.R. UA12**, wired for STEREO and complete with stereo cartridge.

**£8.19.6**

Ditto, monaural cartridge, **£7.19.6**.

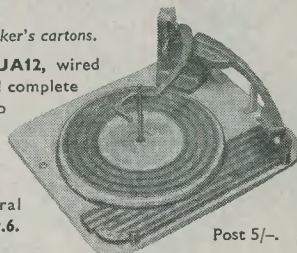

Post 5/-.

**B.S.R.** type **UA8**, complete with latest "ful-fi" pick-up. **£6.19.6**. Post 5/-.

Ditto, wired for STEREO, and complete with stereo cartridge, **£7.19.6**.

**COLLARO**, complete with Studio crystal p.u. and sapphire stylus, **£7.19.6**. Post 3/6.

**GARRARD RC121 Mk. II**, with plug-in head. **£10.19.6**

Ditto, wired for STEREO and with stereo cartridge. **£11.19.6**. Post 5/-.

## TRANSISTORS

**AUDIO** P.N.P. Junction type (yellow/green) 7/6; 3 for 20/-; 6 for 37/6. Post free.

**R.F.** P.N.P. Junction type (yellow/red) 15/-; 3 for 40/-; 6 for 75/-; Post free.

Special prices for larger quantities.

**TS/1.** Audio P.N.P. Transistor, well known make 5/-.

**SPECIAL OFFER.** Set of 7 latest types **EDISWAN** Transistors: XA/101, XA/102, two XB/102, XB/103, two matched XC/101. Price **79/6**.

All other makes and types. List post free or see our new Components Catalogue.

## The FINEST Components Catalogue



ever produced for the "ham" and hi-fi fan. 100 pages, 8 $\frac{1}{2}$ " x 5 $\frac{1}{2}$ ", copiously illustrated. Send for your copy now. Our prices will save you pounds

PRICE **2/-**  
Post 6d.

**207 EDGWARE ROAD, LONDON, W.2.**

Few yards from Praed Street. PADDington 3271/2

**42 TOTTENHAM COURT ROAD, W.1.**

Nearest station Goodge Street MUSEum 2605

Both addresses open all day Saturday, close 1 p.m. Thurs.

Please address Mail Orders and enquiries to Lasky's (Harrow Rd) Ltd, Dept. RC, 207 Edgware Road, London W2




# BUILD THE CRYSTAL CONTROLLED CALIBRATOR

with an  
authentic

# Jason kit

Designed by G. G. Blundell and described in this issue (page 274), the Crystal-Controlled Calibrator **C.C.10** enables signal generators from 100 kc/s to 200 Mc/s to be accurately checked by a system of audio marker "pips" with a basic accuracy of 0.01%. Self-powered unit. Complete kit with valves, case and loud-speaker.

**£16.19.0**

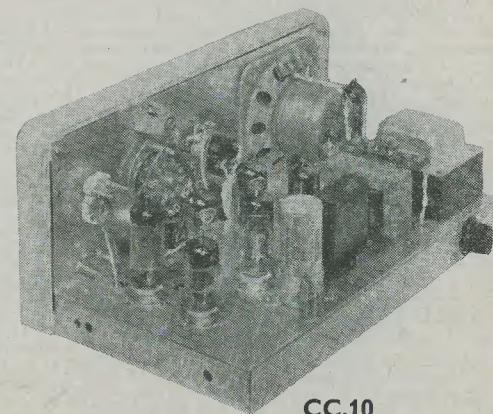

CC.10

## OTHER KITS IN THE JASON PROGRAMME

### AUDIO GENERATOR AG.10

Excellent stability with output held constant over entire band. Tunes from 10 c/s to 100 kc/s over four switched stages and two scales. Switch for square or sine wave. Square wave rise time less than 2 microsecs. at all frequencies. Min. calibrated output 100mV. With case, valves and meter. **£14.5.0**

### WOBBULATOR W.11

Enables FM signals, IF signals for AM sets and TV sound and vision channels to be correctly aligned. RF circuits may also be aligned from the 40-70 Mc/s output, the second and third harmonics of which serve for Bands II and III respectively. Return trace is blanked when using a 50 c/s sine wave sweep frequency to provide a reference base line not found on most commercial instruments. **£14.15.0**. (Built **£19.10.0**.)

### OSCILLOSCOPE OG.10

Push-pull scan on X and Y plates with an X bandwidth from 10 c.p.s. to 1.5 Mc/s,  $\pm 1$ dB. Sensitivity—10mV/cm. As described in The Radio Constructor exact to spec. with valves and Mullard C.R.T. kit. **£22.10.0**.

### STABILISED POWER PACK PP.10M

175mA at 300V Mains variation of  $\pm 10\%$  produces output charge of less than 0.15% Ripple less than one millivolt. Available with or without meter. Polarity change switch. With valves, meter and case, **£22.10.0**.


Radio Hobbies Exhibition, Stand 14, Royal Horticultural Old Hall, Nov. 25-28th.

Details of the above instruments and others in the Jason range, including audio and radio units gladly sent on request. Please quote this journal when writing.
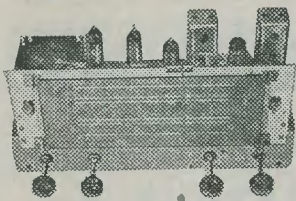
## THE JASON MOTOR & ELECTRONIC COMPANY

3-4(E) GREAT CHAPEL ST. OXFORD ST. LONDON W1 Telephone GERrard 0273/4





1959 RADIOGRAM CHASSIS

THREE WAVEBANDS S.W. 16 m.-550 m. M.W. 200 m.-550 m. L.W. 800 m.-2,000 m. 12 month Guarantee. A.C. 200/250V, 4-way switch. Short-Medium-Long-Gram. A.V.C. and negative feedback. 4.2 watts. Chassis 13 1/2" x 5 1/2" x 2 1/2". Glass dial, horizontal or vertical, size 10" x 4 1/2". 2 pilot lamps. Four knobs, walnut or ivory, aligned and calibrated. Chassis isolated from mains. Leaflet S.A.E.

BRAND NEW £9.10.0 Carr. 4/6 TERMS: Deposit £5.5.0 and 5 monthly payments of £1 MATCHED SPEAKERS: 8" 17/6. 10" 25/-. 12" 30/- New 6V AM/FM model. £18.19.6.

LATEST "E.M.I." 4 SPEED SINGLE RECORD PLAYER

Acos 73 Hi-Fi Stereo and Normal Xtal Pick-up for 7" and 12" records Silent Motor, Heavy Turntable Special offer £6.19.6 post 3/6

BUILD THIS REPRODUCER BARGAIN SPECIAL SINGLE PLAYER KIT

COLLARO 4-speed Gram-Pick-up Unit £4.10.0 Handsome portable case 17 1/2" x 13 1/2" x 7" with room to play 12" records £2.5.0 Ready built 3-watt amplifier with two valves and 7" ellip speaker, printed circuit £3.12.6 or £9.15.0 complete kit post free

I.F. TRANSFORMERS 7/6 pair 465 kc slug tuning miniature can 2 1/2" x 1" x 1". High Q and good band width. By Pye Radio. Data sheet supplied. Wearite M800 Midget I.F.S. 465 kc/s 12/6 pair Wearite 550 Standard I.F.S. 465 kc/s 12/6 pair

Table with columns for component types and values. Includes items like 1R5, 1S5, 1T4, 2X2, 3S4, 3V4, 5U4, 5Y3, 6AM6, 6B8, 6BE6, 6BH6, 6BW6, 6D6, 6F6, 6H6, 6J5, 6L6, 6J7G, 6K6GT, 6K7G.

B.B.C. Pocket Transistor. M.W. & L.W. Radio Kit 32/6. 'Phones 7/6. Ardent deaf aid earpiece with special lead and plug 15/-. Our written guarantee with every purchase

C.R.T. ISOLATION TRANSFORMERS For Cathode Ray Tubes having heater cathode short circuit and for C.R. Tubes with falling emission, full instructions supplied. Type A. Low leakage windings. Optional 25% and 50% boost on secondary: 2V, or 4V, or 6.3V, or 10.3V, or 13.3V, with mains primaries, 12/6. Our Latest Superior Product. Mains Input Type A2. High quality low capacity 10-15pF. Optional boost 25%, 50%, 75%, 16/6 each. Type B. Mains input. Low capacity. Multi output 2, 4, 6.3, 7.3, 10 and 13V. Boost 25% and 50%. This transformer is suitable for all TV tubes. 21/- each.

RESISTORS. Preferred values. 20% 10 ohms to 10 meg, 1/4W 4d., 1/2W 4d., 1W 6d., 1 1/2W 8d., 2W 1/- HIGH STABILITY. 1/4W 1%, 2/-. All preferred values 100Ω-10MΩ. Ditto 5% 100Ω-5MΩ 9d. each. WIRE-WOUND RESISTORS. 5 watt } 1/3 10 watt } 2/6 15 watt } 2/- 25 ohms-10,000 ohms 15,000 ohms-50,000 ohms, 5W, 1/9; 10W, 2/3. WIRE-WOUND POTS. 3W Lab. Colvern, etc. Pre-set min. TV type. Standard size Pots, 2 1/2". Knurled slotted knob. Spindle, high grade. All values, 100 ohms to 50k, 3/- each, 30k, 50k, 4/-, 6/6; 100k, 7/6. Ditto 1/4W Carbon Track W/W EXT. SPEAKER CONTROL 10Ω, 3/-

MAINS TRANSFORMERS-200/250 AC STANDARD 250-0-250, 80mA, 6.3V tapped 4V 4A, Rectifier 6.3V 1A tapped 5V 2A and 4V 2A 22/6 Ditto 350-0-350 22/6 MINIATURE. 200V 20mA, 6.3V 1A 10/6 MIDGET. 250V 45mA, 6.3V 2A 15/6 SMALL. 250-0-250V 100mA, 6.3V 3.5A 19/6 STANDARD. 250-0-250, 65mA, 6.3V 3.5A 17/6 HEATER TRANS. 6.3V 1 1/2A 7/6 Ditto tapped sec. 2, 4, 6.3V 1 1/4A 8/6 Ditto, sec. 6.3V 3A 10/6 Mullard "510" Osram "912" 300-0-300, 120mA, 6.3V 4A c.t., 6.3V 2A tapped 5V 38/6

O/P TRANSFORMERS. Heavy duty 50mA, 4/6. Multi-ratio push-pull, 7/6. Miniature 3V4, etc., 4/6. Small pentode, 4/6. Hygrade push-pull 7 watts, 15/6. Heavy duty 10/20W 6k or 8k c.t., 30/- L.F. CHOKES 15/10H 60/65mA, 5/-; 10H, 85mA, 10/6; 10H 150mA, 14/-

CRYSTAL MIKE INSERT by Acos 6/6 Precision engineered. Size only 3/8" x 1 1/8" ACOS CRYSTAL HAND or DESK MIKE, 35/-

ALADDIN FORMERS and cores. 1 1/2" 8d., 3/8" 10d. 0.3" FORMERS 5937 or 8 and cans TV1 or 2. 3/8" sq. x 2 1/2" or 3/8" sq. x 1 1/2" with cores. SLOW MOTION DRIVES. Epicyclic ratio 6-1, 2/3. TYANA. Midget Soldering Iron. 230V 40W, 16/9. REMPLOY INSTRUMENT IRON, 230V 25W, 17/6. MAINS DROPPERS. 3" x 1 1/2". Three adj. sliders, 0.3A, 750 ohms, 4/3; 0.2A, 1,000 ohms, 4/3. LINE CORD. 0.3A 60 ohms per foot, 0.2A 100 ohms per foot, 2-way, 6d. per foot; 3-way, 7d. per foot. MIKE TRANS. 50:1, 3/9; 100:1, potted, 10/6. LOUDSPEAKERS. P.M. 3 ohm. 5". Rola 17/6; 6" x 4" Rola, 18/-; 4" Hi-Fi Tweeter, 25/-; 8" Plessey, 19/6; 6 1/2" Goodmans, 18/6; 10" R.A., 30/-; 12" Plessey, 30/-; 10" x 6" R.A., 27/6; 12" Baker 15W 3 ohm or 15 ohm models, 105/-; Stentorian HF1012 10", 95/- CRYSTAL DIODES. G.E.C. 2/-; GEX34, 4/- 40 CIRCUITS FOR GERMANIUM DIODES, 3/- H.R. HEADPHONES FLUID, squirt spout, 4/3 tin. SWITCH CLEARER FLUID, 365pF, miniature. TWIN GANG CONDENSERS. 365pF, miniature, 1 1/2" x 1 1/2" x 1 1/2", 10/-; 0.0005 standard with trimmers, 9/-; less trimmers, 8/-; Midget, 7/6; 50pF single, 2/6. SHORT WAVE Single 75pF, 100pF, 160pF, 7/- each. TUNING AND REACTION CONDENSERS. 100pF, 300pF, 500pF, 3/6 each, solid dielectric.

HIGH GAIN TV PRE-AMPLIFIERS BAND I B.B.C.—See page 852 June issue Tunable channels 1 to 5 Gain 18dB. ECC84 valve. Kit price 29/6 or 49/6 with power pack. Details 6d. BAND III I.T.A.—Same prices Tunable channels 8 to 13. Gain 17 dB ECC84 valve.

Volume Controls 80Ω Coaxial Cable Midget size. Long spindles. Guaranteed 1 year. All values 5,000 ohms to 2 Meg. No Switch 3/- Linear or Log Tracks 4/9 Post 1d. per yard Semi-air spaced Polythene Ideal Band III 6d. yd. Losses cut 50% FRINGE QUALITY Air spaced Coaxial 1/- yd.

Coaxial Plugs 1/- Panel Sockets 1/- Lead Socket 2/- Outlet Boxes 4/6 Balanced Twin Feeder, per yd 6d., 80Ω or 300Ω. Twin Screened Balanced Feeder, 1/6 yd, 80 ohms. Trimmers. Ceramic 30, 50, 70pF, 9d.; 100pF, 150pF, 1/3; 250pF, 1/6; 600pF 750pF, 1/9; Philips, 1/- each. BLACK CRACKLE PAINT. Air drying, 3/- tin. P.V.C. CONN. WIRE, 8 colours, single or stranded, 2d. yd. Sleeving 1, 2mm, 2d., 2, 3 mm, 3d., 6 mm, 5d. yd. NEON MAINS TESTER SCREWDRIVERS, 5/- SOLDER RADIOGRADE, 4d. yard 1 1/2 2/6.

Aluminium Chassis. 18 s.w.g. Plain, undrilled, 4 sides, riveted corners, lattice fixing holes, 2 1/2" sides. 7" x 4", 4/6; 9" x 7", 5/9; 11" x 7", 6/9; 13" x 9", 8/6; 14" x 11", 10/6; 15" x 14", 12/6; 18" x 16" x 3", 16/6.

Miniature Contact Cooled Rectifiers. 250V 50mA 7/6; 250V 85mA, 9/6, Selenium Rect. 300V 85mA, 7/6. Coils. Wearite "P" type, 3/- each. Osrom Midget "Q" type, adj. dust core, from 4/- each. All ranges. Teletron D.W.R. L & Med. T.R.F. with reaction, 3/6. Ferrite Rod Aerials. M.W., 8/9; M. & L., 12/6. T.R.F. Coils A/HF, 7/- pair. H.F. Chokes, 2/6. Speaker Fret. Gold cloth, 17" x 25", 5/-; 25" x 35", 10/-; Tygan, 4" 6" wide, 10/- ft; 2" 3" wide, 5/- ft. Samples, S.A.E.

Condensers. 0.001µF 7kV T.C.C., 5/6; ditto 20kV, 9/6; 0.1µF 7kV, 9/6; 100pF to 500pF Micas, 6d.; Tubular 500V 0.001 to 0.05, 9d.; 0.1, 1/-; 0.25, 1/6; 0.1/350V, 9d.; 0.5, 1/9; 0.01/2,000V, 1/9; 0.1/2,000V, 3/6. Ceramic Condensers. 500V 0.3pF to 0.01µF, 9d. Silver Mica. 10% 5pF to 500pF, 1/-; 600pF to 3,000pF, 1/3; close tolerance (plus or minus 1pF), 1.5pF to 47pF, 1/6; ditto 1% 50pF to 815pF, 1/9; 1,000pF to 5,000pF, 2/-

Table with columns: NEW ELECTROLYTICS, TUBULAR, CAN TYPES, FAMAUS MAKES. Rows include values like 1/350V, 2/450V, 4/450V, 8/450V, 8/500V, 16/450V, 16/500V, 32/450V, 25/25V, 50/25V, 50/50V.

Full Wave Bridge Selenium Rectifiers. 2, 6 or 12V 1 1/2A, 8/9; 2A, 11/3; 4A, 17/6. Free charger circuit. Charger Transformers. Tapped input 200/250V for charging at 2, 6 or 12V 1 1/2A, 15/6; 2A, 17/6; 4A, 22/6. LONG PLAY "GEVAERT GEVASONOR" Plastic tape 50% extra 1,700ft 7" reel, 35/-; 850ft 5" reel, 21/-; MSS 225f, 3" reel, 7/6. Spare reels, 3/- SUPERIOR 1,200ft plastic tape, 24/-, 7" plastic reel, 600ft plastic tape on 5" plastic reel, 15/- LONG PLAY 1,200ft, 5 1/2" reel, 28/- INSTANT bulk tape eraser, and Head Defluxer, 200/250V a.c., 27/6.

BRAND NEW AND BOXED Model UA8 OUR PRICE £6.19.6 STEREO MODELS UA8 £7.19.6 UA12 £10.10.0

★ COLLARO ★ HI-FI ATUOCHANGER £7.19.6 4 SPEEDS-10 RECORDS or with Cabinet, Amplifier and Speaker OUR PRICE £11.19.6 Carr. 5/6

★ GARRARD 4-SPEED RECORD CHANGERS RC12/D MK II MODELS ★ With Plug-in Normal Head £10.10.0 Stereo Head £2 extra

★ AUTOCHANGER ACCESSORIES Suitable player cabinets (uncut boards) 49/6 Amplifier player cabinets with cut boards 63/- 2-valve amplifier and 6 1/2" speaker for above 79/6 3-valve amplifier and 6 1/2" speaker for above 95/- Wired and tested ready for use

★ GARRARD 4-SPEED SINGLE RECORD PLAYER 4SP ★ £7.10s. AUDIO PERFECTION POST FREE MODEL TA MK 11 £8.10.0 Stereo Heads MODEL 4 HF £18 £2 extra.

Wavechange Switches. 2 p. 2-way, 3p. 2-way, short spindle, 2/6; 5p. 4-way 2 wafer, long spindle, 6/6; 2 p. 6-way, 4 p. 2-way, 4 p. 3-way, long spindle, 3/6; 3 p. 4-way, 1 p. 2-way, long spindle, 3/6; wavechange "MAKITS," 1 wafer, 8/6; 2 wafer, 12/6; 3 wafer, 16/-; 4 wafer, 19/6; 5 wafer, 23/-; 6 wafer, 26/6.

Toggle Switches, s.p., 2/-; d.p., 3/6; d.p.d.t., 4/- JASON FM TUNER COIL SET, 26/- H.F. coil, aerial coil, oscillator coil, two i.f. transformers 10.7 Mc/s, detector transformer and heater choke. Circuit and component book using four 6AM6, 2/6. Complete Jason FM Kit, with valves and Jason Chassis with calibrated dial, £6.15.0, post free.

Valveholders. Pax. int. oct., 4d. EA50, EF50, 6d. B12A, CRT 1/3. Eng. and Amer. 4, 5, 6 and 7 pin, 1/- MOULDED Mazda and int. oct., 6d., B7G, B8A, B8G, B9A, 9d. B7G with can, 1/6. B9A with can, 1/9A. Ceramic, EF50, B7G, B9A, int. oct., 1/- B7G, B9A Cans, 1/- each.

TV Fault Finding, 5/- Quality Amplifiers, 4/6. Radio Valve Guide. Books 1, 2 or 3 5/- each TRANSISTORS. Ediswan Audio XB102, 10/- R.F. XA103, 15/- XA104, 18/- OC71, 7/6. Sub-miniature Electrolytics (15V), 1µF, 2µF, 4µF, 5µF, 8µF, 25µF, 50µF 3/-

TELETRON POCKET RADIO Transidyne Superhet Six 6" x 4" x 1 1/2" T.C.C. Printed Circuit, internal Ferrite aerial, Rola loudspeaker push-pull output. All parts, cabinet, 6 Ediswan or Mullard transistors. £11.19.6 Details 9d.

RADIO COMPONENT SPECIALISTS

337 WHITEHORSE ROAD WEST CROYDON Telephone THO 1665



# NEW! DO-IT-YOURSELF TRAINING TECHNIQUE in RADIO & ELECTRONICS

You LEARN while you BUILD...

SIMPLE...PRACTICAL...FASCINATING...

**ANNOUNCING**—after many years of highly successful operation in the U.S.A. and in Europe—the latest system in home training in electronics is now introduced by an entirely new British training organisation.

**AT LAST**—a comprehensive and simple way of learning—by practical means—the basic principles of radio and electronics, with a minimum of theory.

**YOU LEARN BY BUILDING** actual equipment with the components and parts which we send you. You advance by simple steps using high quality equipment and performing a whole series of interesting and instructive experiments. No mathematics!

**INSTRUCTION MANUALS** and our teaching staff employ the latest techniques for showing clearly how radio works in a practical and interesting manner. You really have fun whilst learning! And you end by possessing a first rate piece of home equipment with the full knowledge of how it operates and—very important—how to service and maintain it afterwards. A full library of magnificent illustrated textbooks is included with the courses.

**IN FACT** for the "Do-it-Yourself" enthusiast, the hobbyist or those wanting help with their radio career training, or to set up their own full or part-time servicing business—then this new and exciting instructional system is exactly what is needed and it can all be provided at very moderate cost. Easy payments available. Post the coupon now, for full details. There is no obligation of any kind.

BUILD YOUR OWN: • RADIO EQUIPMENT • HI-FI INSTALLATION • TEST GEAR—AND LEARN AS YOU DO IT.

**FREE-POST TODAY**

# RADIOSTRUCTOR

BRITAIN'S LEADING RADIO TRAINING ORGANISATION.

LOTS OF INSTRUCTIVE EXPERIMENTS AT HOME!

Power supply circuits

Test equipment supplied

Amplifier, oscillator and detector circuits

Basic 1st stage receiver

Servicing of commercial receivers

**No Mathematics!**

To: RADIOSTRUCTOR (Dept. G31)  
46 Market Place, Reading, Berks.


Please send full details of your Radio Equipment Courses without any obligation to:

Name.....

Address.....

BLOCK CAPS PLEASE

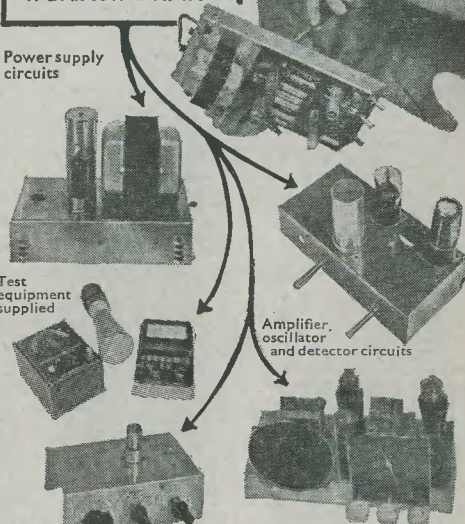(802) We do not employ representatives 11.59



The Biggest Money-Maker in the Business!

NEWNES  
**RADIO & TELEVISION SERVICING**

SERVICING DATA FOR

**300 Popular Models**  
(1958-1959)

IN ONE VOLUME

In response to the heavy demand more copies of Newnes latest volume have now been printed. It contains all the circuits, components and chassis layout diagrams you need for 300 popular 1958 to 1959 Models. Examine it Free for 7 days

See next page for details and post-paid form

672 PAGES OF WANTED DATA

TELEVISION, RADIO, RECORD AND TAPE SERVICING DATA

Alba, Argosy, Berec, Beethoven, Bush, Champion, Collaro, Cossor, Cyldon, Decca, Defiant, E.A.R., Eddystone, Ekco, Ever Ready, Ferguson, Ferranti, G.E.C., Grundig, H.M.V., Invicta, K.B., McMichael, Marconiphone, Masteradio, Murphy, Pageant, Pam, Perdio, Peto Scott, Philco, Philips, Pilot, Portadyne, Pye, Pye Telecommunications, Raymond, Regentone, R.G.D., Roberts' Radio, Sobell, Spencer-West, Stella, Ultra, Vidor, Walter.

RECENT DEVELOPMENTS SECTION Includes: Picture Tube Repair, Car Radio Interference Suppression, Valve and Picture Tube Data.

HEATER RATINGS, BASE CONNECTIONS, EQUIVALENTS

SERVICING DATA PRE-1953 UP TO 1959

Over **2,300 Models**

COMPLETE LIBRARY IN SEVEN VOLUMES

Includes the 300 models and data in the volume on left

Here you have Newnes Complete Servicing Library—early popular models to 1959—almost every set you will ever be called upon to service. This data is, as you know, absolutely invaluable. It is worth its weight in gold for years on end—increasing your income by quicker servicing. Study the complete set for 7 days—without obligation.

TELEVISION, RADIO, RECORD AND TAPE SERVICING DATA

Ace, Alba, Ambassador, Argosy, Armstrong, Baird, Banner, Beethoven, Berec, Brayhead, Bush, Champion, Collaro, Cossor, Cyldon, Decca, Defiant, E.A.R., Eddystone, Ekco, E.M.I., English Electric, Ever Ready, Ferguson, Ferranti, G.E.C., Grundig, H.M.V., Invicta, K.B., McCarthy, McMichael, Marconiphone, Masteradio, Motorola, Murphy, Pageant, Pam, Perdio, Peto Scott, Philco, Philips, Pilot, Portadyne, Pye, Pye Telecommunications, Radiomobile, Rainbow, Raymond, Regentone, R.G.D., Roberts' Radio, Sobell, Spencer-West, Stella, Strad, Ultra, Valradio, Vidor, Walter, Webcor, White-Ibbotson.

Also — Large Fold-out Charts—TV Trouble Tracing; Servicing VHF/FM and AM/FM receivers; Servicing Printed Circuit Equipment; Servicing Transistorised Equipment. Data on—Colour Codes, Valves and Picture Tubes, Medium and Long Wave Broadcasting Station Wavelengths, TV and VHF/FM Stations and Channels.

2 Years' Free Postal Advisory Service

EXAMINE EITHER—**FREE** FOR 7 DAYS

without obligation to buy

See overleaf for more details and REPLY-PAID FORM FOR POSTING



4,250 CIRCUITS AND DIAGRAMS  
4,150 PAGES



# Newnes Radio & Television Servicing

**PAYS FOR ITSELF OVER AND OVER AGAIN!**

"More than repaid the cost in a short period," says E.J.S. (Wolvercote).  
 "One glance only was enough to convince me of its worth," writes J.F.B. (Leicester).  
 "Of immense help and in constant use."—T.A. (Uxbridge).  
 "A boon and a must."—J.S. (Manchester).

**SEND FOR FREE EXAMINATION TO-DAY—See below**

(B) Fold along here

Postage  
will be  
paid by  
George Newnes  
Ltd.

No Postage  
Stamp  
necessary if  
posted in  
Gt. Britain or  
Northern Ireland

**BUSINESS REPLY FOLDER**  
Licence No. W.C. 1129

**GEORGE NEWNES LIMITED,**  
15-17 LONG ACRE,  
LONDON, W.C.99

(C) Fold along here

## POST TO-DAY-NO STAMP REQUIRED

Place tick against your choice below

Radio and Television Servicing  
(Pre-1953 to 1959 Models)  
**SEVEN VOLUMES**  
10/- Dep. 15 monthly payments of 15/-, Pay-  
ing £11.15s. in all. Cash price in 8 days £11.5s.

Radio and Television Servicing  
(1958-1959 Models)  
**SINGLE VOLUME**  
12/6 Deposit. 4 monthly payments of 10/-.  
Paying 52/6 in all. Cash price in 8 days 50/-

Send me the book or books I have selected, without obligation to purchase. I will either return the book or books in 8 days or send the deposit 8 days after delivery, then the monthly subscriptions as set out above, until the total subscription price of the book or books I have selected has been paid.

Mr., Mrs., Miss .....

Address .....

Occupation .....

Your Signature ..... **R42/RV63**  
(Or Parent signs if you are under 21)

Tick (✓) where applicable

HouseOWNER	<input type="checkbox"/>
Householder	<input type="checkbox"/>
Living with Parents	<input type="checkbox"/>
Lodging Address	<input type="checkbox"/>

### HOW TO FOLD THIS PAGE FOR POSTING

← (B)

1. Detach complete page and fold at (A), turning this strip downwards out of sight.

2. Then fold at (B) and (C)

3. Tuck (C) into (B) so that Reply-paid portion with NEWNES address is shown.

**FINALLY POST QUICKLY**

(A) Fold along here

DETACH PAGE HERE

← (C)



# Mullard

## CIRCUITS FOR AUDIO AMPLIFIERS

**- a book every enthusiast will want!**

This new Mullard publication is a practical manual for every audio enthusiast. In addition to describing twelve of the most popular Mullard circuits, it has introductory chapters

on many of the theoretical and practical aspects of high quality sound reproduction.

Whether you are interested in disc or tape, monaural or stereo, you will find that "Circuits for Audio Amplifiers" gives just the sort of information you need.

This informative book costs only 8/6d. The demand for it is high, so get your copy now from your local radio dealer.



**MULLARD LTD • MULLARD HOUSE • TORRINGTON PLACE • LONDON • W.C.1**

MVM 422A



# HOME RADIO OF MITCHAM

Dept. AC 187 LONDON ROAD MITCHAM SURREY  
Shop hours: 9-6.30 (Weds. 1.0 p.m.) MIT 3282

Meet us at  
Stands 15 and 16  
RADIO HOBBIES EXHIBITION  
Royal Horticultural Hall  
November 25th to 28th

## THE BEST COMPONENTS CATALOGUE EVER


Exclusive to Home Radio the largest and most comprehensive component catalogue ever produced. Size 9 1/2" x 7 1/2", beautifully printed on high grade paper and comprising 128 pages and listing well over 4,000 items of interest to the constructor. Over 400 illustrations and plenty of technical information. Included are full ranges of Eddystone short wave components and receivers also WB Stentorian speakers and cabinets. All items in this catalogue are normally available from stock as it has been carefully compiled from actual components in our stores. We anticipate large demand for this catalogue and we are giving readers of the "Radio Constructor" first opportunity to obtain their copies.

Please mark your envelope "Catalogue" in top left corner  
**AVAILABLE NOW**

**PRICE 2/-** plus 9d. post U.K. (Overseas post 2/-)




### JASON "MERCURY" Switched FM Tuner

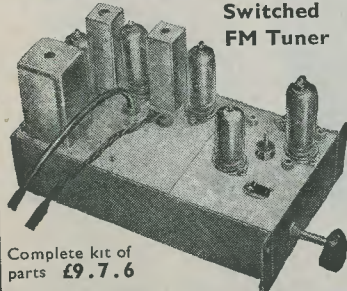

Complete kit of parts **£9.7.6**


VHF/FM at its best. The programme you want at the turn of a switch, always "spot-on" tune with automatic frequency control. Ideal for family use. Crystal clear and perfect quality. Easy to build and all parts standard and available separately. Full Data 2/4 post paid.

### JASON FMT2 TUNER

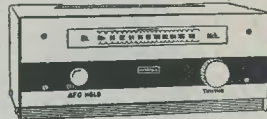

Crystal clear Hi-Fi reception at all times. Modern slide rule scale and smart case for shelf or cabinet mounting. The best home constructor circuit ever produced now even better with higher gain. Easy to build and with pre-aligned coils works first time, every time. Self-powered to avoid complications. Full constructional data 2/9 post paid. Complete kit with Power unit **£9.8.0**.

### "GLOBE KING" SHORT WAVE RADIO KITS

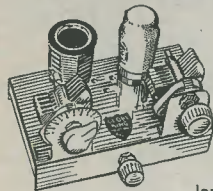

The best hobby of them all. Travel the world from the comfort of your fireside. News from America, music from Hawaii, sport from Australia, and listen in to amateurs from every part of the world. The Globe King gives you real long distance reception at minimum cost. Built up to a standard—not down to a price. Complete kit for 1-valver with three matched coils covering 10 to 20 metres, price **79/6**. Leaflet on request.

### "CIRCUITS FOR AUDIO AMPLIFIERS"


Latest book by Mullards with constructional data for over 12 different designs including amplifiers, pre-amplifiers, mixers, tape amplifiers, stereo amplifiers, etc. Price **8/6** plus 1/- post.

All parts in stock for these designs including ready-punched chassis, ferrox pot cores, ganged controls, printed front panels, special switches, etc.

### HI-FI EQUIPMENT

We stock comprehensive range of Hi-Fi equipment including Pye Mozart tuner and amplifier, Leak, Armstrong, Dulci, etc. Demonstration room now open and a range of SENSIBLE high quality systems fitted up to hear, both ready-built units and various kit units. Leaflet on request.


### WB STENTORIAN

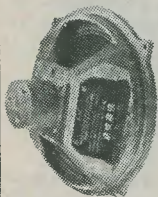

The best and most popular range of Hi-Fi speakers, tweeters, cross-overs and cabinets, etc. Full range always in stock and leaflets on request. Illustrated the famous HF.1012.10" speaker unit Die-cast chassis. Response 30 to 14,000 cycles Universal speech coil. Price **£4.15.0** plus 2/- post
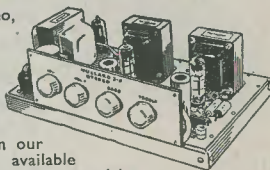
### MULLARD 3 WATT STEREO AMPLIFIER

The 3 watt, the 3 watt stereo, and Five-Ten amplifiers now available on printed circuit. Easy to build and perfect results every time. Full constructional drawings and price lists. Price **1/9** each post paid. Demonstration models in our showrooms. All parts available separately. Trade and overseas enquiries invited for the printed circuits.



# The Radio Constructor

Incorporating THE RADIO AMATEUR



Vol. 13 No. 4

NOVEMBER 1959

ANNUAL SUBSCRIPTION 25/- (including postage)

## CONTENTS

- 250 Suggested Circuits: A Remote Volume Control for Television Receivers, by G. A. French
- 253 Trade Review
- 254 In Your Workshop
- 259 Understanding Television, Part 22 by W. G. Morley
- 263 Do-It-Yourself Printed Radio Circuits by Squadr.-Ldr. S. W. Sarri, A.M.BRIT.I.R.E.
- 268 Can Anyone Help?
- 269 On Buying an HRO Receiver by L. H. Rouse and J. B. Dance, M.S.C.
- 271 Radio Hobbies Exhibition, 1959—List of Exhibitors
- 272 The "Different" Hi-Fi Unit by R. S. Squires
- 274 The Jason Crystal Calibrator CC.10 by G. Blundell
- 283 Transistors in Hybrid Circuits by F. L. Ash
- 288 Radio Topics, by Commentator
- 290 Getting Started on RTTY by Arthur C. Gee, G2UK, Hon. Sec. British Amateur Radio Teletype Group
- 292 "Vibrato" Unit for Use with Electronic Guitars by E. W. Bones
- 294 V.H.F. Aerials, by A. W. Collis
- 296 A Reed Radio-Control Receiver, by Michael A. Cole
- 298 Tuning Coil Calculations—conclusion by W. E. Thompson, A.M.I.P.R.E.
- 300 Memo to Wives and Mothers

### Editor

C. W. C. OVERLAND, G2ATV

### Associate Editor

A. C. GEE, G2UK

### Business Manager

J. H. BURROWS, A C A

### Advertising Manager

A. BALDWIN, A M I P R E

### Offices

57 MAIDA VALE LONDON W9

### Telephone

CUNNINGHAM 6141  
(2 lines)

### Telegrams

DATABUX, LONDON

## NOTICES

THE CONTENTS of this magazine are strictly copyright and may not be reproduced without obtaining prior permission from the Editor.

ARTICLES appearing in this magazine which describe kits are inserted only on condition that such kits, or special components thereof, are freely available at a trade discount to all retail advertisers.

OPINIONS expressed by contributors are not necessarily those of the Editor or proprietors.

THE EDITOR invites original contributions on construction of radio subjects. All material used will be paid for. Articles should preferably be typewritten, and photographs should be clear and sharp. Diagrams need not be large or perfectly drawn, as our draughtsmen will redraw in most cases, but all relevant information should be included.

ALL MSS must be accompanied by a stamped addressed envelope for reply or return. Each item must bear the sender's name and address.

TRADE NEWS. Manufacturers, publishers, etc., are invited to submit samples or information of new products for review in this section.

TECHNICAL QUERIES should be submitted in writing. We regret that we are unable to answer queries, other than those arising from articles appearing in this magazine; nor can we advise on modifications to the equipment described in these articles.

ALL CORRESPONDENCE should be addressed to THE RADIO CONSTRUCTOR 57 Maida Vale London W9. REMITTANCES should be made payable to "DATA PUBLICATIONS LTD."



# suggested

# circuits

The circuits presented in this series have been designed by G. A. FRENCH, specially for the enthusiast who needs only the circuit and essential data

No. 108

## A Remote Volume Control for Television Receivers

WHAT WOULD VERY PROBABLY BE THE ideal television receiver would be one which, amongst other things, allowed all the more important controls to be situated immediately under the hand of the viewer. The set-owner would then be able to change channels, adjust contrast and brightness, and control volume level without moving from his chair. In point of fact, the design and production of television receivers having remote control facilities raise few technical problems: such receivers have, indeed, been available in the domestic market for quite some time, notably in the States. Unfortunately, the provision of remote control facilities results in a relatively large increase in overall receiver cost, with the consequence that these facilities tend to fall into a "deluxe" category.

The writer feels that the usefulness of a television receiver may be very considerably increased if only *one* aspect of its performance is made capable of remote adjustment by the viewer. This single aspect is the audio volume level of the receiver. The arguments in favour of a remote volume control are, to the writer's mind, rather compelling. It could cope very readily, for instance, with those instances where there are large differences in apparent volume level of the type which occur in programmes where speech and

music are interspersed. If, when receiving such programmes, the local volume control is adjusted for comfortable level on speech, subsequent musical items frequently tend to be almost distressingly loud. Apart from the vexation caused by this effect to the more discriminating viewer, there is the fact that annoyance to others may result. The latter point is especially important if domestic conditions necessitate receivers being operated in crowded blocks of flats, or where children close by have to get to sleep. A remote volume control overcomes these drawbacks, enabling the receiver to be operated at comfortable listening level, both for speech and for music, with no risk of annoyance to others. A second point is that the television receiver is by no means always the focus of a family's attention. When visitors call, for example, it is quite often desirable to be able to turn down the volume on the receiver easily and unobtrusively whilst introductory conversation is in progress.

This month's contribution deals with a simple modification which may be made to any conventional television receiver in order that remote volume control may be achieved.

### Connecting Into The Receiver

Practically all modern television receivers employ an a.f. section which consists of a


triode voltage amplifier followed by a pentode output valve. The input for the voltage amplifier is obtained from the sound detector, and it is customary to place the receiver volume control between this detector and the voltage amplifier grid. At first sight it would appear desirable to connect the remote volume control also into the grid circuit of the voltage amplifier. Unfortunately, coupling into this part of the circuit raises several problems. To begin with, since the full gain of the a.f. section is provided after the voltage amplifier grid, special care would be needed to prevent hum pick-up in the leads to the remote volume control. Due to this question of hum pick-up, it would also almost certainly be necessary for the outer conductor of whatever screened cable was employed in the leads to the remote volume control to be bonded direct to chassis. The screened cable outer conductor, in consequence, would become connected directly to one side of the mains, and the resultant shock hazard becomes unnecessarily high.

avoided. A simple resistive potentiometer control would not cope adequately here.

In the circuit proposed here, the remote volume control is coupled into the grid circuit of the output valve. Coupling into this part of the receiver provides the advantage that subsequent a.f. gain is not of such an order as to cause much difficulty with hum pick-up. Also, the only stage which has to continually operate at a level at least as high as the highest normally required is the voltage amplifier. The risk of distortion incurred here should be negligible. Finally, it is possible to take circuit precautions which, whilst not eradicating shock hazard altogether, do at least provide a significant reduction in this risk.

A separate feature of the circuit is that a single screened lead is all that is needed between the remote volume control and the receiver, thereby considerably simplifying wiring requirements. It is recommended that this lead be normal coaxial cable, since the relatively low capacity between conductors

Fig. 1. Receiver circuit before modification

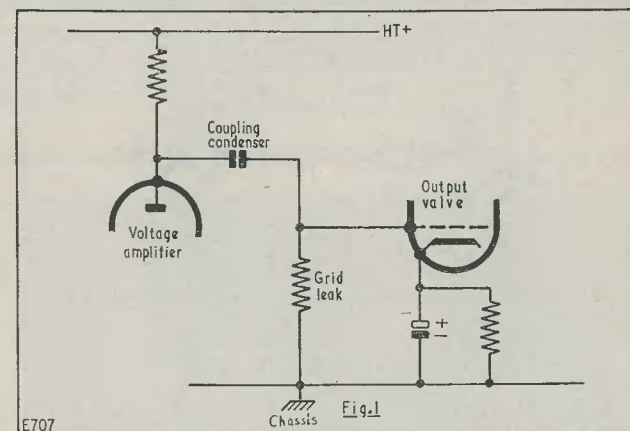

An alternative section of the receiver into which the remote volume control could connect is the sound output transformer secondary circuit. Ignoring the safety question (which would be dependent upon individual receiver design so far as isolation from chassis was concerned) there is, in this case, the disadvantage that the output valve would always have to operate at a level at least as high as the highest normally required; with the result that overall distortion would tend to increase. A further disadvantage is that the remote volume control would have to be of a special type which maintained correct matching between output valve and speaker if further distortion were to be

in such cable will cause minimum attenuation of the higher audio frequencies.

### The Modification

Fig. 1 illustrates the basic circuit likely to be encountered between the voltage amplifier and output valve of the receiver it is intended to modify. As may be seen, circuit arrangements are quite straightforward. The voltage amplifier connects to the h.t. positive line via its anode load resistor, and couples to the following grid via a condenser. The output grid is kept at chassis potential by means of its grid leak. In some receivers it may be found that the output valve cathode shares the same cathode resistor as is used by the



voltage amplifier, but this point does not affect the modification. Again, it may occasionally be found that a low value tone-correction condenser couples between the output anode and its grid, or that a grid stopper resistor is inserted between the coupling condenser and the output grid. Where encountered, such components are retained during the modification, the feed-back condenser remaining connected between output anode and grid, and the grid stopper remaining connected to the grid. In the latter case, all connections to the grid, after the modification circuit has been installed, are made via the stopper.

Fig. 2 shows the circuit after modification. The first thing that should be noted is that the grid leak has been removed. Also, the coupling condenser now connects to the grid via the additional 100kΩ resistor, R<sub>1</sub>. Further connected to the grid is the centre conductor of the coaxial cable which travels to the remote volume control, R<sub>2</sub>. The outer conductor of the cable couples to chassis via R<sub>3</sub> and C<sub>1</sub>.

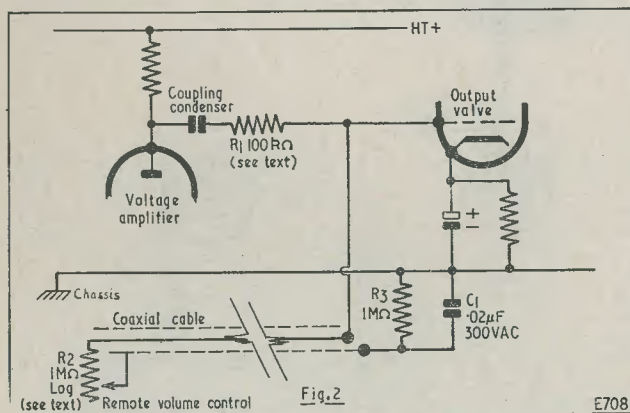


Fig. 2. How the remote volume control is connected into circuit

The functioning of the remote volume control is very simple. When the remote control is set to insert maximum resistance into circuit, the a.f. available at the voltage amplifier anode feeds into the potentiometer given by R<sub>1</sub> and R<sub>2</sub>, the end of R<sub>2</sub> remote from anode being virtually at chassis potential due to the low reactance to a.f. offered by C<sub>1</sub>. The output grid taps into the junction of R<sub>1</sub> and R<sub>2</sub>, with the result that it receives  $\frac{1}{10}$  of the a.f. voltage available at the anode.<sup>1</sup> When R<sub>2</sub> is adjusted to insert minimum resistance into circuit, the a.f. amplifier anode

<sup>1</sup> Resulting in a loss of approximately 0.8dB.

couples into a circuit which consists effectively of R<sub>1</sub> on its own. The output grid is then virtually at chassis potential, and no a.f. is passed to it. Thus, maximum volume is obtained when R<sub>2</sub> inserts maximum resistance into circuit, and minimum volume is obtained when R<sub>2</sub> inserts minimum resistance into circuit. Settings of R<sub>2</sub> between maximum and minimum resistance will then result in corresponding volume levels between these extremes, and the function of a volume control is achieved.

#### Circuit Features

One or two points need to be discussed more fully so far as Fig. 2 is concerned.

As has probably already been realised, the reason for inserting R<sub>3</sub> and C<sub>1</sub> into circuit is that a direct connection to the receiver chassis is thereby avoided. C<sub>1</sub> has a low reactance at the audio frequencies likely to be handled by the television receiver, with the consequence that the outer conductor of the coaxial cable may be considered as being at chassis potential so far as a.f. is concerned.

At the same time C<sub>2</sub> provides a reasonable measure of isolation from the chassis so far as shock hazard is concerned, this isolation being of the same order as has been used in the past for pick-up and aerial connections in a.c./d.c. sound receivers. It must be pointed out, nevertheless, that C<sub>1</sub> does not provide isolation to the level currently accepted for metal conductors capable of being touched outside the receiver cabinet. In consequence, the coaxial cable between the receiver and the remote volume control must be well and reliably insulated, the insulation extending inside the television cabinet and inside the box containing the

remote volume control. The latter should be made of an insulating material, such as wood or plastic, the remote end of the cable being securely clamped inside. It will be noted that C<sub>1</sub> is a 300 volts a.c. wkg. component, this being an obvious rating for an isolation condenser. It would be desirable for the coupling condenser to be changed for a component having this voltage rating as well. The function of resistor R<sub>3</sub> is merely that of ensuring the existence of a d.c. path between the output grid and chassis. With television receivers having better-than-average a.f. reproduction it may be found that the presence of C<sub>1</sub> gives slight bass boost at very low volume settings. This effect should be quite unnoticeable under normal listening conditions.

As was mentioned above, coaxial cable is employed because of its low capacity. This capacity is of the order of 20pF per foot,<sup>2</sup> and it should be possible in consequence to use lengths of up to 15 feet (=300pF), or even more, without incurring any excessive attenuation of the higher audio frequencies.

A log-law control is specified for R<sub>2</sub>. Such

<sup>2</sup> A sample of conventional solid-polythene spaced 75Ω cable, as employed for aerial lead-ins, had a capacity of 19.6pF per foot when checked by the writer.

a component should offer almost as "smooth" a control of volume as would be given if it were used as a true potentiometer in a conventional circuit.

A final point is that the values specified for R<sub>1</sub> and R<sub>2</sub> are those applicable to the case where the previous grid leak had a value around 470kΩ. In some receivers it may be found that the grid leak has a value around 200kΩ only. In such an instance the values of R<sub>1</sub> and R<sub>2</sub> should be halved.


#### Setting Up

After the remote volume control has been connected up it should be checked for operation. R<sub>2</sub> should be set to the maximum resistance position and the receiver adjusted to reproduce a programme. The receiver volume control should then be adjusted to a level slightly higher than that which would normally be required. It should then be found that R<sub>2</sub> will afford a range of control below this level.

It may occasionally be found that the modification causes hum to be introduced into the a.f. output of the receiver. This will occur if the chassis is at live mains potential, and the capacity between the coaxial cable and earth is sufficiently high to enable a hum voltage to be built up across C<sub>1</sub>. The cure is to reverse the mains supply to the receiver.

## Trade Review

### STEADFAST SUPER HARD POINT PHILLIPS TYPE SCREWDRIVER

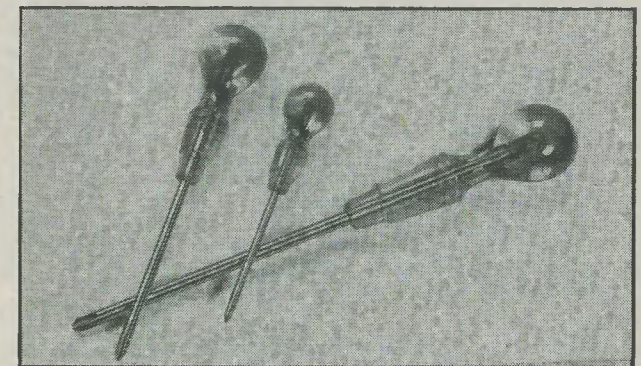

CP.1—Overall length 5 $\frac{1}{2}$ in, suitable for Phillips recess head 4 SG wood screws,  $\frac{1}{8}$ in, 5 and 6 BA metal screws.

CP.2—Overall length 8in, suitable for Phillips recess head 5-10 SG wood screws,  $\frac{3}{16}$ in,  $\frac{1}{8}$ in, 2 and 4 BA metal screws.

CP.3—Overall length 11 $\frac{1}{2}$ in, suitable for Phillips recess head 12-16 SG wood screws,  $\frac{1}{4}$ in and 0 BA, and  $\frac{1}{8}$ in round head metal screws.

To give a much greater turning power cabinet type handles are fitted. These handles are made in unbreakable plastic and can be subjected to impact without fear of damage. The super hard point blades are particularly suitable for self-tapping screws.

Prices: CP.1 5s. 4d. each; CP.2 7s. 6d. each; CP.3 9s. 3d. each.



# IN YOUR WORKSHOP



This month Smithy the Serviceman discusses, with his able assistant, Dick, the question of fuses

"WELL, NOW," SAID DICK, "BUT THAT'S a funny thing."  
 "What's a funny thing?" grunted Smithy, over his shoulder.

"This hi-fi amplifier I'm modifying for you," said Dick. "You know, the one you asked me to fit with an h.t. fuse."

"Oh, yes, I remember," remarked Smithy. "However, a simple job like fitting a fuse shouldn't cause you much trouble."

"That's what I thought. I've got the fuse in circuit, but it has a tendency to blow every now and again when I switch the amplifier on."

"Any h.t. shorts?"

"Nothing," declared Dick, "that I can detect with an ohmmeter. Also, the amplifier worked quite happily before I put the fuse in."

"What is the fuse rating?" asked Smithy. "200mA," replied Dick. "The amplifier takes about 100 to 120mA when it's running."

"Hmm," grunted Smithy. "Sounds a bit light, but it should be reasonable enough in practice."

## Charging Currents

The Serviceman walked over to the amplifier chassis which Dick had placed, inverted, on the bench. He noted that his assistant had drilled out a hole at the back of the chassis to take a panel-mounting cartridge fuse holder, and that he had wired it into circuit neatly.

Smithy looked closer at the wiring. "Ah," he remarked. "I see where you've gone wrong. You've put the fuse between the rectifier and the reservoir condenser; with the result that initial charging currents to the reservoir condenser are liable to blow it if you switch on again shortly after switching off, and while the rectifier's still warm. (Fig. 1 (a)). You should have put it between the choke and the smoothing condenser. (Fig. 1 (b))."

"But surely," protested Dick, "you wouldn't get as much protection if you put the fuse after the choke. For instance, it wouldn't guard against the case where the reservoir condenser itself broke down. You get complete protection the way I've fitted it here."

"That's true enough," admitted Smithy, contemplatively, "and I think I had better qualify my statement by saying that you could keep your fuse in the position you've chosen if you use a type with a delaying action, such as the Bulgin cartridge 'Pak' fuse. A Bulgin 'Pak' fuse is intended for applications where surges are liable to occur and it will withstand an overload of 75% for approximately 120 seconds. If the overload is of the order of 100 to 175% it blows within 5 to 30 seconds, and if it is over 200% (that is, three times the fuse rating) the fuse blows instantaneously. In your case I think a 250mA 'Pak' fuse would cope quite happily before the reservoir condenser."

"I'm getting a little baffled," complained Dick. "Why is it necessary to overload the fuse to make it blow? I always thought that if a fuse is marked with a certain current it always blows at that current."

"Not necessarily," replied Smithy. "The small glass 1½in cartridge fuses we meet in radio work are usually marked with the maximum carrying current. You then have to look up the manufacturer's literature to find out the current at which they blow. Normally, you can be pretty certain that they'll blow at 100 to 200% overload, although this may not always be instantaneous. Your assumption that a fuse is marked with its blowing current does, however, apply to the types you find in cars—you know, the glass types with pointed brass end-caps. I thought you'd like to know that not all fuses are rated in the same manner."

This last sentence was accompanied by a

blowing currents. Why can't these things be standardised?"

Smithy chuckled.


"Well, it *would* be nice to have it standardised," he admitted, "but with a thing whose performance is as complex as is that of a fuse standardisation tends to be a little difficult."

Dick interrupted him.

"Please, Smithy," he said, "don't let's get any more involved for the time being. Five minutes ago I was a happy lad who thought of a fuse as a bit of thin wire which burnt out if you screwed too many amps through it. Now I find I've stumbled on to a minor science all on its own. Isn't this one of the things that should be made the subject of a British Standard?"

"Perhaps so," said Smithy, cautiously. "In actual fact there are several separate British Standards for fuses of different types; but these tend to tackle their subjects from slightly different angles. The British Standard

Fig. 1 (a) A fuse inserted between the cathode of a rectifier and the reservoir condenser is subject to heavy switching-on surges (if the rectifier is warm or is a metal component) and has to carry the additional reservoir condenser charging current. A delay type fuse would be preferred in a circuit of this type. (b) When the h.t. fuse is inserted after the smoothing choke it is protected from switching-on surges and does not have to carry reservoir charging currents. However, the fuse does not offer protection if the reservoir condenser breaks down.

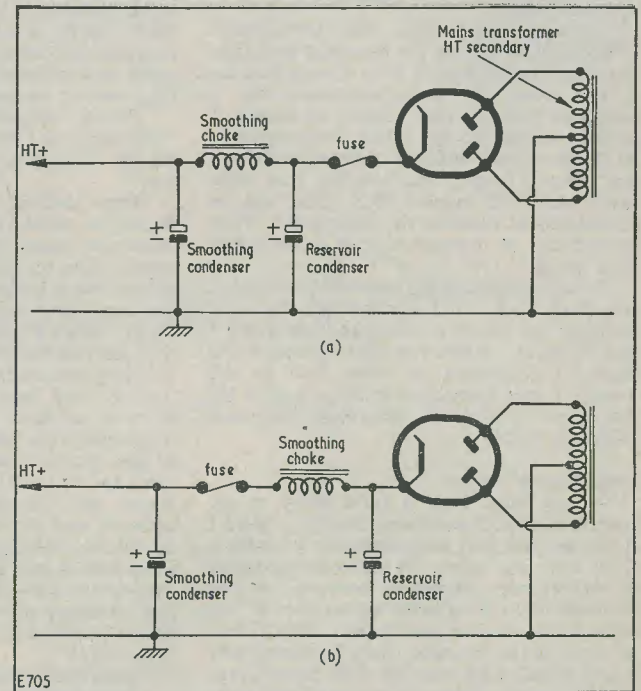

grin on the Serviceman's face. He knew that his assistant was always irritated by discrepancies of this nature.

"Isn't it always the same?" grumbled Dick, rising to the Serviceman's bait. "You get one half of an industry making fuses which are rated for carrying current, and you get the other half rating fuses with

for the 1½ cartridge fuses which we use in radio is B.S. 2950<sup>1</sup> and, amongst other things, this lays down several test require-

<sup>1</sup>The full title of the Standard is B.S. 2950: 1958, Cartridge Fuse-Links For Telecommunication And Light Electrical Apparatus, and it supersedes the type B fuse-link requirements in B.S. 646: 1935. (The term "cartridge fuse-link" defines a cartridge containing a fuse-element.)



ments so far as current is concerned. I don't want to go into too much detail on the current tests, but I can say that these state basically that the fuse should carry its rated current for 1,000 hours without blowing. It should, also, blow within 10 seconds if its rated current is doubled, in the case of trade A fuses, or if it is trebled, in the case of grade B fuses."

"What's this grade A and B business?"

"Well," replied Smithy, "the two grades only apply to fuses between 50 and 250mA, which are, I suppose, rather more difficult to manufacture. Above 250mA the grade A requirement, that of blowing on double current rating, is the only one that holds."

"Does B.S. 2950 cover surge currents, like we've met today?"

"I'm afraid not," said Smithy. "It gives details of what is described as a suitable test, wherein the fuse is subjected to continuous surges, but this is for guidance only."

"Well, that's not very helpful," commented Dick.

"Perhaps not," said the Serviceman. "Nevertheless, I think the Standard does help to quite a useful extent, even if only because it ties down rating requirements for a particular type of fuse. Also, of course, I haven't mentioned the other things covered by the Standard—such as dimensions and so on. Don't forget, incidentally, that only fuses which are marked 'B.S. 2950' can be considered as meeting the Standard.<sup>2</sup> They should also be marked A or B according to their grade."

"Well, I suppose that's reasonable enough," remarked Dick, "but our learned discourse on fuses has rather clouded another query I had in mind. When you first looked at the way I'd connected up that fuse in the amplifier your immediate reaction was to tell me to put it after the reservoir condenser. Why was that?"

#### Switching-on Surges

"I may have been a little hasty in my judgment there," confessed Smithy. "And I do rather feel that the alternative of using a delay type fuse before the reservoir condenser is rather more attractive because, as you yourself say, it affords protection if the reservoir condenser goes kaput. What I had in mind at the moment when I saw the way you'd wired it up was the very heavy surge current which flows through the reservoir condenser and rectifier whenever you switch off and switch on again shortly after. Immediately after you switch off a piece of equipment having a valve rectifier, the charge on the reservoir condenser disappears due to

the current drawn by the still-warm valves in the equipment, plus that drawn by any resistor networks which may be connected across the h.t. line. If you then switch on again, the rectifier, whose cathode may still be at emission temperature, has to pass a very heavy initial current during the first few half-cycles of a.c. until the reservoir condenser charges up to its normal voltage again. In your case the initial charging current was enough to blow your fuse, which was not, of course, of the delay type. Incidentally, you don't get the heavy initial charging current if you switch on equipment having a valve rectifier from cold. In this instance the rectifier cathode reaches emission temperature at a relatively slow rate and you get a gradual rise in charging current."

"What happens if you have a metal h.t. rectifier?"

"In that case," said Smithy, "there is no gradual warm-up and you get heavy initial surge every time you switch on. If I wanted to be pedantic, I could say that the greatest initial surge would occur if your switch contacts happened to close at the instant when peak positive voltage was being applied to a rectifier anode."

"That's interesting," remarked Dick. "Rectifiers and reservoir condensers take a bit of a bashing during their lives, don't they?"

"They certainly do," agreed Smithy. "I remember some years ago examining a little miniature radio which had come in for repair. This set, which was of rather doubtful origin, had a half-wave rectifier circuit which was absolutely cut down to the bone. (Fig. 2 (a)). When I checked around a bit I found that the rectifier valve had packed in. I was a little surprised by this at first, because it lit up O.K. and there were no shorts or flashes or any evidence of such things having happened in the past. In the end I had a look at the rectifier electrodes through its glass envelope and, so far as I could make out, I found that the internal wire between the cathode and the cathode pin lead-out had completely disappeared! There weren't any loose bits of wire in the envelope, so the only assumption I could make was that the owner had switched off and on again, whereupon the resultant surge current had just melted the wire away!"

"Well, that's a turn-up for the book."

"As you say," commented Smithy, gravely, "a turn-up, indeed. Anyway, I took the hint and, before inserting a new rectifier, I fitted a limiter resistor. (Fig. 2 (b)). The set went like a bomb with the new rectifier and, so far as I know, has not given any trouble since."

"Is, then, the purpose of the limiter resistor that of preventing initial surges?"


"Not entirely," said Smithy. "The current

in the reservoir section of a rectifier circuit is always higher than that drawn after the smoothing choke because of the charging current, which appears at each positive half-cycle. The limiter resistor helps to keep this charging current to a reasonable value. If you look up manufacturers' data for valve rectifiers you usually find that they specify a minimum value of limiting resistor as well as a maximum value of reservoir capacity. You very often find something of the same nature with condensers, too. Double h.t. electrolytics frequently state on the can which section should be used as the reservoir, this section being that which is designed to handle the consequent charging currents."

"Would that accommodate the extra current in the reservoir circuit?"

"I think so," said Smithy. "The extra reservoir current is not all that great in a full-wave circuit because the reservoir condenser doesn't have a chance to discharge very much before the next positive half-cycle comes along. If it had been a half-wave circuit, in which the reservoir condenser is charged by every other cycle only, the extra current in the reservoir circuit tends to increase quite considerably. In such an instance you might find that a 250mA fuse in the position you chose would have rather a short life, and you would have had to go up to 500mA."

Fig. 2 (a) An example of bad circuit practice, insofar that no limiting resistance appears in the reservoir circuit, either in the form of a physical resistor or in the form of "hidden" resistance in a mains transformer. If the on-off switch is closed whilst the rectifier is warm the resultant surge may easily damage the valve or the reservoir condenser. Also, reservoir charging currents may be excessive. (b) Inserting a limiter resistor prevents excessive initial surge currents and keeps reservoir charging currents within safe limits. The resistor would be just as effective if fitted between the rectifier cathode and the reservoir condenser. Its value would normally be that recommended by the manufacturer of the rectifier—a typical figure being of the order of 200Ω.

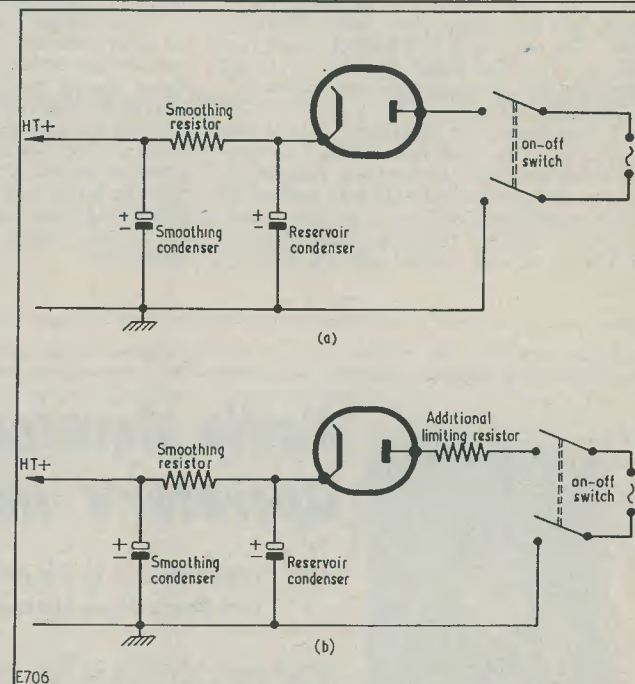

"There weren't any limiting resistors in my amplifier power pack," Dick reminded Smithy.

"Nor were there," agreed Smithy. "But in this instance you had 'hidden' resistances in the mains transformer. These 'hidden' resistances are given by the actual resistance of the wire in the secondary, plus the effective resistance reflected from the primary wire and that resulting from the losses in the transformer."

"You recommended a delay fuse of 250mA in my case," Dick pointed out.

"But," protested Dick, "that would mean you'd need something like an amp to blow the fuse!"

"True," said Smithy. "Nevertheless, it would still provide useful protection for a metal rectifier, even if it wasn't of much use for the smaller type of valve rectifier. The alternative, of course, is to fit the fuse after the choke."

#### Fuse Resistance

"Another point has just struck me," said Dick. "If a fuse blows, it means that suffi-

<sup>2</sup> Old fuse-links may be marked with the superseded Standard: B.S. 646 B; or be advertised as meeting B.S. 646 B.



cient heat has been dissipated in its wire to cause it to melt. That argues a certain amount of resistance in the fuse. Could this resistance cause any trouble?"

"Not in the ordinary course of events," said Smithy, "although you should avoid using fuses in circuits which pass heavy currents and which require very low resistances. A typical instance of the wrong way of inserting a fuse came my way some time ago when a friend of mine decided to insert a 250mA cartridge fuse in a television line output stage in order to prevent the line output valve from doing a lighthouse act if the grid drive failed. Instead of inserting his fuse in the h.t. positive feed to the line output valve, my friend inserted it in the cathode, which had previously been taken direct to deck. The result was that he lost about 1 to 2kV in e.h.t. and about an inch or so of picture width! But the fuse didn't blow."

Dick frowned.

"That's queer," he remarked. "All I can guess is that the resistance of the fuse provided degeneration in the same manner as does an unbypassed cathode bias resistor in an a.f. amplifier stage."

"That's exactly right," smiled Smithy. "When my friend shorted out the fuse by

means of the time-honoured application of a screwdriver, his e.h.t. popped up to normal and the picture expanded to full width."

"Isn't there something else wrong here?" said Dick. "I would have thought that putting a fuse in the cathode circuit of a valve is rather a naughty thing to do, anyway."


"Well, it is a little unusual," said the Serviceman, "but only because there are other circuit positions which are more obvious."

But Dick was still not satisfied.

"If a fuse in the cathode circuit blows," he continued, "what's to stop that cathode from shooting up to full h.t. potential, whereupon you run the risk of breakdown between heater and cathode?"

"Don't forget," replied Smithy, "that, if the grid remains at chassis potential, an open-circuit cathode cannot rise any higher above chassis potential than by the cut-off voltage for the valve."

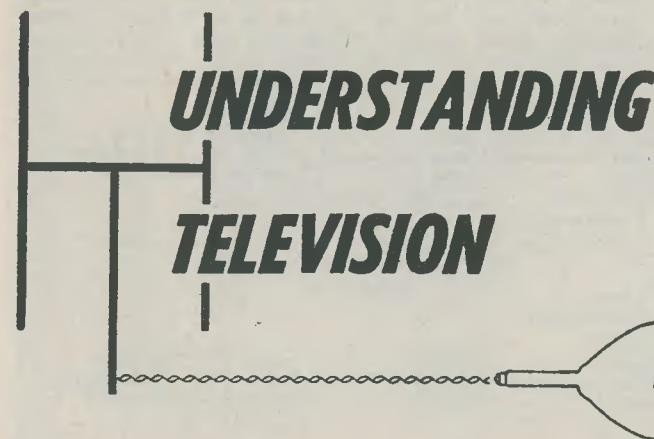
There was silence for some moments whilst Dick worked out Smithy's statement. And when he turned to the Serviceman he found that the latter had, craftily, returned to his bench, and was so engrossed in his work that he would answer no further questions whatsoever.



*The twenty-second in a series of articles which, starting from first principles, describes the basic theory and practice of television*
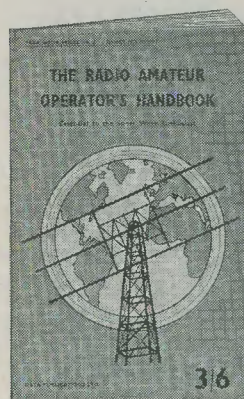
## Radio Amateur Operator's Handbook

Indispensable to the Amateur Transmitter and Short Wave Listener



More than ever, now that the Dx season is in full swing, will the latest edition of this essential aid to operators be in constant demand and use. This extremely handy and informative book should be readily to hand at every operating position—containing as it does, complete details of all information which is constantly required. The contents include complete Amateur Band Prefix lists, both Alphabetically and by Country, the 40 Radio Zone Areas, Call Areas, Mileage Tables of over 200 cities and towns throughout the world, the latest amended list of QSL Bureau addresses, the "Q" and other radio codes, WWV and MSL schedules, Record Charts for scoring and QSL purposes of (a) World Prefixes on 5 Bands, (b) American States, (c) the 40 Zones and (d) British Isles Counties Heard/Worked on 4 Bands, Maps of Dx Areas, Morse Code, Amateur Transmitting Licence details, Amateur Abbreviations, Local Time Conversion List, Amateur Bands Frequency Allocations, Directional Bearings, Frequency/Wavelength Conversion Chart, as well as articles on working the VHF Bands and Amateur Bands Dx Operating Techniques.

PRICE 3/6 Postage 4d.

DATA PUBLICATIONS LTD 57 Maida Vale London W9

THE FIRST TWO ARTICLES IN THIS SERIES<sup>1</sup> introduced the principles of deflection and synchronising, in order to explain the manner in which a television signal may be transmitted and reproduced. It was pointed out in these earlier articles that the beam in the receiver cathode ray tube was deflected quickly from left to right and slowly downwards, thereby causing a number of parallel horizontal lines to be traced out on the screen. Whenever the beam had completed its motion to the right it was quickly returned to the left again in order that another line might be traced out. Similarly, when the beam had been deflected sufficiently far downwards it was quickly returned upwards again so that a further cycle of vertical deflection could commence. The earlier articles stated that deflection of the beam from left to right was known as line or horizontal deflection, and that downward deflection was known as frame or vertical deflection. In both line and frame deflection cycles the quick return of the beam was described as the flyback, or retrace.

It was further pointed out, in the first two articles, that, when direct synchronisation is employed at the receiver, the synchronising pulses in the transmitted signal initiate the

flyback and enable the receiver deflection circuits to keep in step with those employed at the transmitter.

We shall now commence to examine in detail the deflection circuits in the receiver. In doing so we shall refer to synchronising pulses which may be either positive-going or negative-going. Such synchronising pulses are derived from the transmitted signal with the aid of the *sync separator* stage, the functioning of which will be described in a later article.

### Deflection Circuits

In order that a cathode ray tube may reproduce as a picture the signal passed to its modulating electrode by the receiver, its beam must be deflected both horizontally and vertically. In the case of an electrostatic cathode ray tube this deflection is achieved by applying sawtooth voltages of correct waveform and frequency to its deflection plates, and in the case of an electro-magnetic cathode ray tube by applying sawtooth currents of correct waveform and frequency to its deflector coils. In conventional modern television receivers electromagnetic deflection is invariably used, and the deflection circuits normally take up the appearance illustrated in Fig. 122.

This diagram shows, in block form, the stages which constitute the deflection section

<sup>1</sup> *Understanding Television* 1 and 2. *The Radio Constructor*, Jan. and Feb., 1958.



of the receiver. The line deflection section consists of the line sawtooth generator, the line output valve, and the line output transformer, the latter coupling directly into the line deflector coils. The frame deflection circuits follow the same pattern, the frame

### Sawtooth Generators

Sawtooth generators intended for the line and frame circuits of television receivers may normally be subdivided into two basic parts. One part consists of a "sawtooth-forming circuit," whilst the other consists of an

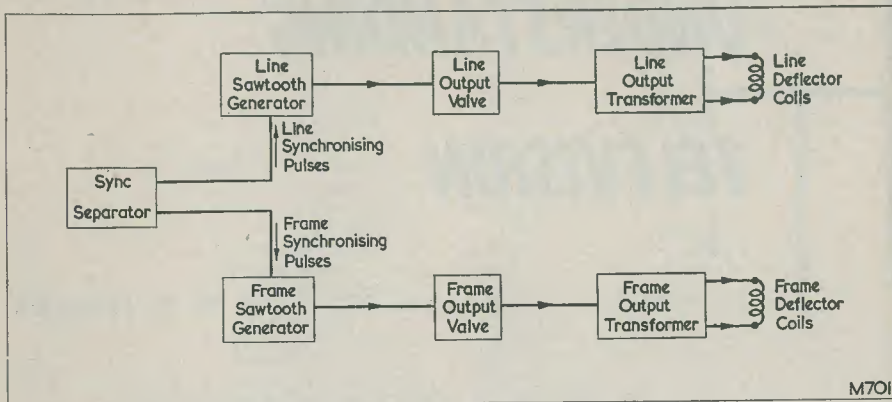


Fig. 122. A block diagram illustrating the various sections in the deflection circuits of a conventional receiver

sawtooth generator being followed by the frame output valve which, in its turn, is succeeded by the frame output transformer and the frame deflector coils. Both line and frame sawtooth generators are fed with synchronising pulses from the sync separator stage to keep them in step with the transmitted signal.

Before carrying on further, some points of terminology need to be cleared up. It is usual, in practice, to refer to the sawtooth generators as oscillators, whereupon these become known as *line oscillators* and *frame oscillators*, as applicable. Alternatively, the sawtooth generators may be referred to as *timebases* (qualified by *frame* or *line* as applicable). However, the term timebase may also be used to refer to the composite section provided by an oscillator and its output stage.

Synonymous with timebase, and less frequently encountered, are the terms deflection generator and scanning generator.

The block diagram illustrated in Fig. 122 is typical of what is most frequently employed in modern television receivers. Occasionally, by the use of suitable feedback circuits, the line output stage may be made self-oscillatory, whereupon there is no necessity for a separate line oscillator. The frame output stage may similarly be made self-oscillatory, with the result that a separate frame oscillator may also be dispensed with.

oscillator coupled to that circuit and controlling the time occupied by each part of the sawtooth.

A simple arrangement which demonstrates theoretically the operation of a sawtooth-forming circuit is illustrated in Fig. 123 (a). In this diagram we have a condenser connected to a source of h.t. voltage via a resistor. Across the condenser

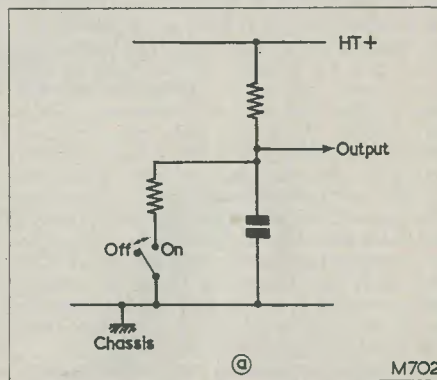


Fig. 123 (a) A "sawtooth-forming circuit". The resistor in series with the switch has a much lower resistance than that which couples the upper plate of the condenser to the h.t. positive rail

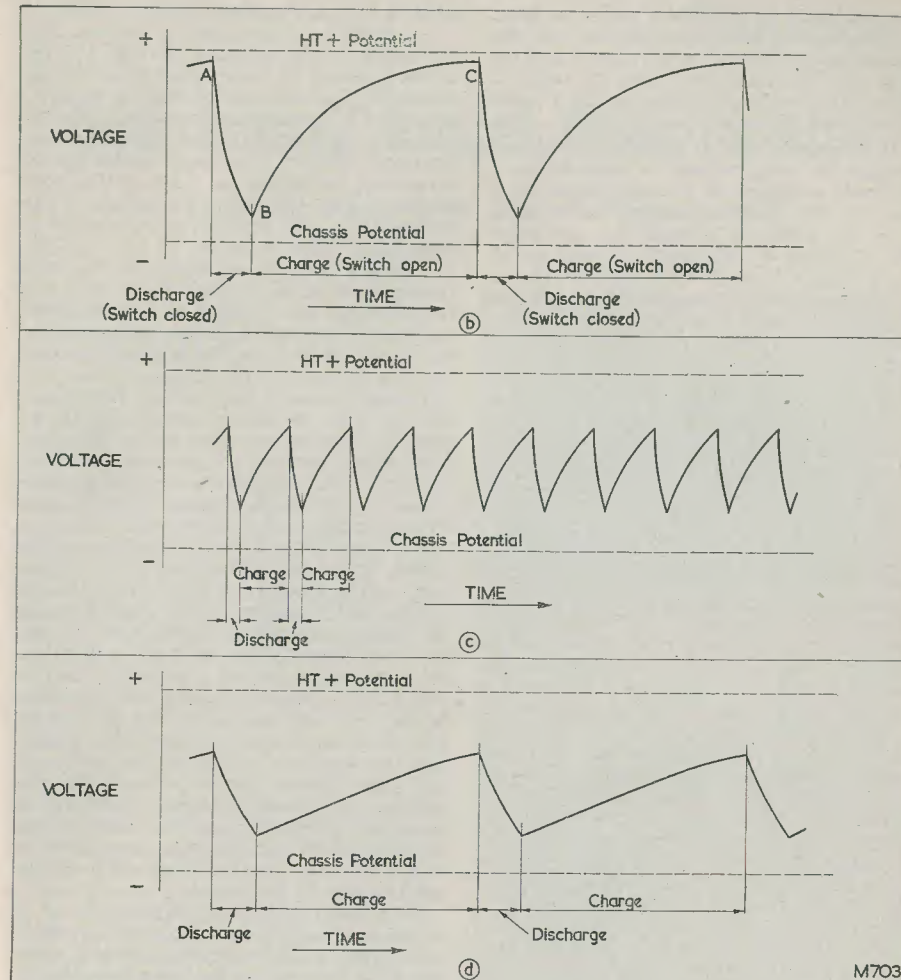


Fig. 123 (b) If the switch of the "sawtooth-forming circuit" is repeatedly held closed for a short period of time and open for a long period of time we may obtain the sawtooth waveform shown here. Each section of the sawtooth follows the normal exponential curve given when a condenser charges, or discharges, through a resistor and, because we are allowing the condenser to discharge nearly to chassis potential and to charge nearly to h.t. positive potential, we obtain a sawtooth whose sections are markedly non-linear. (c) It is possible to obtain a more linear sawtooth by allowing the condenser to charge and discharge over only a part of the exponential curve. In this diagram we have improved linearity by speeding up the switch operation, thereby restricting the range over which the condenser charges and discharges. Apart from the obvious increase in frequency which results, there is also an unavoidable reduction in amplitude. (d) Another method of improving linearity consists of increasing the value of the condenser, or of increasing the values of the two resistors. By carrying out this change in component values we may retain the original switching frequency whilst still allowing the charge on the condenser to vary over only a part of the exponential curve. Once again, the improvement in linearity is accompanied by a reduction in amplitude



# Do-it-Yourself Printed Radio Circuits

by Squadron Leader S. W. Sarll, A.M.(Brit.), I.R.E.

## Introduction

1. A printed circuit differs from a conventional wired radio or electronic circuit in that all the electrical interconnections and the component terminations fixing is done by copper sheet conductors bonded to an insulating baseboard (see Fig. 1). Such circuits can be mass-produced to a consistent standard more cheaply than conventional wiring, and the accuracy and long life stability result in a better product. For the aeromodeller, experimenter or amateur who makes printed circuit equipment there are the advantages of reduction in size, ruggedness and simplicity of construction, besides the long life stability. It is now possible to construct a "one-off" circuit at home with no special tools or equipment. Besides radio chassis, printed circuits may be used for rotary or slide switches for actuators, mechanical pulsers and other similar devices.

2. It is not proposed to discuss here the complex equipment used commercially, but to describe a simple though crude way of achieving useful results. Basically the system built around copper-clad laminate board consists of:

- (a) Painting the required pattern on the copper surface;
- (b) Etching away the uncovered copper;
- (c) Removing the protective paint and cleaning the copper;
- (d) Drilling the connection holes;
- (e) Soldering the components to the copper conductors.

Anyone capable of handling a paint brush, drill and soldering iron can produce results.

## Drawing

3. Assuming that the required pattern is a radio circuit and that a theoretical diagram is available, the first job is to make an exact full-size drawing on paper of the components and interconnections in their correct place. All components will be anchored by passing their connecting wires through small holes drilled in the baseboard. All interconnections will be by the copper laminate remaining after the surplus is etched away. If absolute miniaturisation is desired, it is a

is a switch in series with a second resistor. It is assumed that the resistance of this second resistor is much lower than that of the first, with the result that, when the switch is closed, the condenser discharges much more rapidly than it charges when the switch is open.

If the switch is closed for short periods and opened for long periods we may obtain a sawtooth waveform of the type illustrated in Fig. 123 (b). Commencing just before point A in this waveform we have the case where the condenser is very nearly charged to full h.t. voltage. At point A the switch is closed, with the result that the condenser discharges rapidly until point B is reached. At point B the switch is opened again, and we obtain the case where the charge on the condenser rises slowly. This slow rise continues until we close the switch again at point C, whereupon the condenser commences to discharge once more and another cycle is started.

If we examine more closely the production of our sawtooth waveform of Fig. 123 (b), several important factors come to light. Firstly, in order to achieve a steady frequency for the sawtooth waveform it is necessary for each successive switching cycle (on and off again) to occupy the same period of time. Secondly, it is necessary for the relationship between the time that the switch is on and the time that the switch is off, *within* the switching cycle, to remain steady if successive sawtooth cycles are to have the same shape.

The sawtooth shown in Fig. 123 (b) is not very linear, in so far that the sections representing charge and discharge are markedly curved. When a condenser discharges into a resistor, or is charged via a resistor, the graph representing voltage against time follows what is described as an exponential curve. In Fig. 123 (b) the section from A to B, and that from B to C, both trace out part of an exponential curve. Non-linearity in the sawtooth is frequently undesirable, and steps have to be taken to obtain a more linear shape, if only over the period when the condenser is charging. A simple method of doing this consists of restricting the charge and discharge range so that only part of the exponential curve is followed. A typical example is illustrated in Fig. 123 (c). In Fig. 123 (c) the condenser is not allowed to charge to as high a potential, or to discharge to as low a potential, as it did in Fig. 123 (b), with the consequence that we obtain a more linear response, this being especially noticeable for the period when the switch is open. It will be noted that the frequency of the sawtooth waveform of Fig. 123 (c) is higher than that of Fig. 123 (b), this being due to the fact that the switching cycle must obviously be made shorter if the condenser is to be prevented from charging to too high or too low a potential. Also, the amplitude of the saw-

tooth is reduced, another inevitable result.

It would be impossible to increase the amplitude of the response of Fig. 123 (c) whilst retaining the same linearity (or without increasing the potential of the h.t. supply). We could, nevertheless, revert to our original switching frequency whilst retaining our improved linearity, if we carry out the simple process of increasing the value of the condenser of Fig. 123 (a), or the values of the two resistors. The result of such a change in component value is shown in Fig. 123 (d). In this last diagram we switch at the same frequency as we did in Fig. 123 (b), and, due to the longer time required by the condenser to charge and to discharge, we obtain a waveform which is similar in amplitude and linearity to that of Fig. 123 (c).

The sawtooths of Fig. 123 are representative of the waveforms which would be applied to the output valve, line or frame, of a television receiver. The short discharge section of the waveform would then correspond to the flyback period, whilst the long charge section would correspond to the scan period. In a practical arrangement the switch and series resistor of Fig. 123 (a) would be replaced by a valve, the anode of which would connect to the upper plate of the condenser, and the cathode to chassis. This valve would then be made conductive (by applying to its grid a potential close to that of its cathode) during the discharge period, and non-conductive (by biasing its grid beyond cut-off) during the charge period. Also, the values of the condenser and the resistor coupling it to the h.t. positive rail would be made such that a sawtooth waveform having the desired linearity, amplitude, frequency, and relationship in time between the charge and discharge sections, would be formed.

In normal television receivers it is a customary requirement that the sawtooth waveform passed to the frame output valve has good linearity in the slow-changing, or scan, section. Present-day line output stages do not normally require a sawtooth input having a linear scan section: indeed, heavy non-linearity is frequently aimed for. Linearity in the fast-changing section of the sawtooth is usually of little importance, as this corresponds to the flyback period.

It is possible for a circuit containing resistance and inductance to produce sawtooth waveforms similar to those provided by the resistance and capacity arrangement of Fig. 123 (a). In television practice such circuits are employed only in the line output stage; and they will be discussed when we come to deal with this particular part of the receiver.

Next Month—In next month's issue we shall examine the functioning of oscillators capable of controlling the "sawtooth-forming circuit."



Fig. 1. 3-transistor receiver on printed panel



help to cut out some card patterns of the profiles of all components and move them around on the board to fit as closely as possible. Positioning of components is critical with some r.f. circuits and must be catered for in the layout drawing. Leave room between fixing holes for a length of lead sufficient to prevent the heat, when soldering the ends, from reaching the components. (See Fig. 2 (a).)

#### Base Material

6. Many firms are producing good laminate board, but successful results have been achieved using "Formica" Copper Clad Material Engraved DCC.20-0.0028in copper. This material is marketed by Radio and Electronic Products Ltd., 8 Station Parade, Sheen Lane, Mortlake, S.W.14, and pieces can be supplied on order as economical sub-multiples of 12in by 12in. Material with

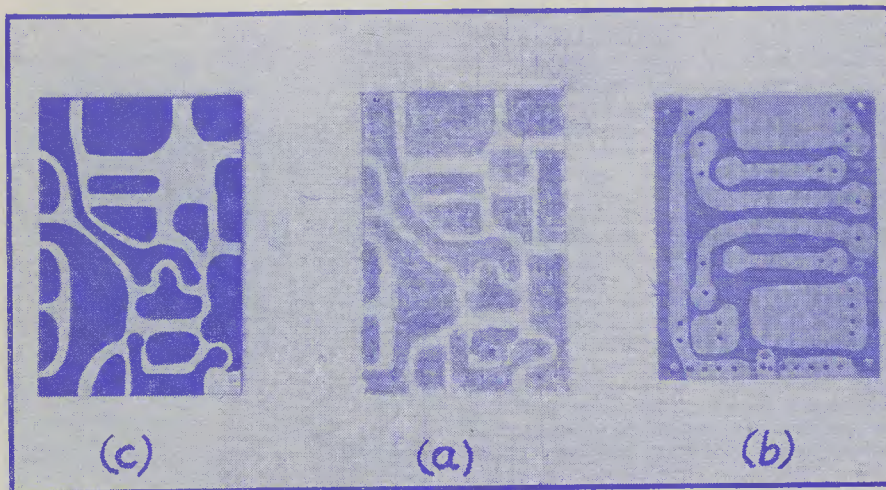


Fig. 2 (a) Receiver panel pencil sketched; (b) Transistor multi-vibrator panel ready for assembly; (c) Painted ready for etching

4. Once a satisfactory layout has been drawn, shade in with pencil the areas where the final copper connection is required. One method is to shade as much as possible leaving narrow spaces between the areas to break the continuity where necessary. This method reduces the amount of copper to be removed (less etching solution needed) and leaves a surplus of copper that may be valuable if a circuit change is subsequently necessary. Large unconnected areas can often be made "earthy" by suitable bridges or linking wires. Be satisfied that areas shaded are adequately separated and can be easily copied on the copper by painting.

5. Another method is to draw circular areas around each fixing hole and connect up circles as required by narrow shaded strips. Only the very minimum of copper is left on the board with this method, so it is recommended when the copper is to be subsequently plated (as for switches). For all other applications the first method is recommended.

copper deposit on both sides of the insulating board can be obtained for special purposes or very complicated cross circuitry, but is more expensive. Unless considerable heat is applied the 2.8 thou. copper will resist all normal attempts to peel off, but it may be removed quite easily by etching or even by cutting away with a razor blade or modelling knife. A complete kit containing 60 sq. in. of laminated board, chemicals, plastic etching bath, instructions, etc., is obtainable from Proops Bros. Ltd., Dept R, 52 Tottenham Court Road, London, W.1, for 21s.

7. The first job is to cut and sand the board to size, cleaning the cut edge of the copper with a file or sandpaper. Lay the paper pattern exactly over the board and with a sharp point mark the positions of fixing holes and any other significant reference points in the copper surface. Emphasise these points in the copper with a centre punch—do not drill yet.

#### Protecting Material

8. Anything can be used to protect the

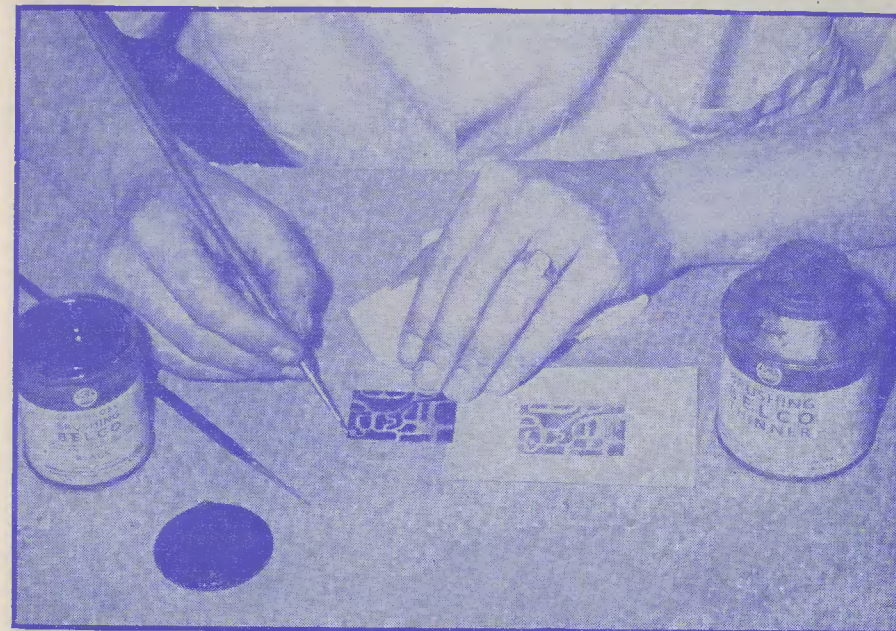


Fig. 3. Hand painting the copper-clad panel



Fig. 4. Etching in a saucer with ferric chloride



wanted copper that will resist the etching agent. Success has been achieved with:

- (a) Cellulose enamel;
- (b) Humbrol enamel;
- (c) Sellotape;
- (d) Self-adhesive plastic insulating tape.

Of those tried, cellulose enamel as sold for touching-up cars dries quickest, but even when wet the Humbrol paint resisted the etch (except where handled!). The top layer of Sellotape came loose but the sticky film still gave protection where firmly adhered in the first application.

#### Etching Material

10. Satisfactory results have been achieved using ordinary or strong solution of ferric-chloride obtained from any chemists at 1s. to 2s. 6d. per bottle, according to quantity. The solution at the strength supplied, or slightly diluted with water (up to 20%), is poured into a shallow glazed earthenware or china dish, such as a saucer or plate, large enough to accommodate the size of board to be etched. Place the panel in the liquid and allow time for the unprotected copper to be removed (Fig. 4). Keep the liquid in

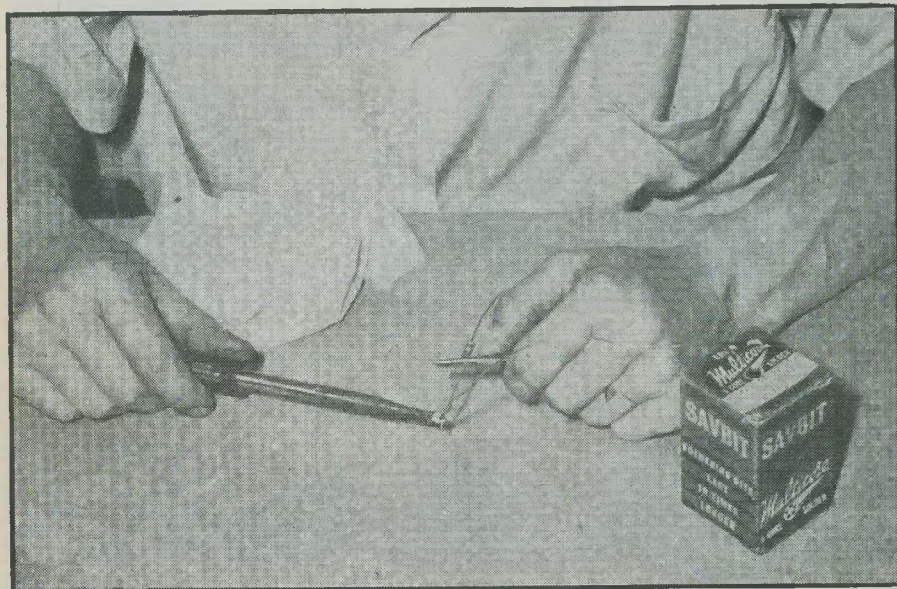


Fig. 5. Tinning a resistor

9. Assuming that enamel will be used, it can be applied to the copper by hand, using a fine paint brush. The shaded areas of the paper pattern are copied free-hand on the copper using the hole positions as a guide (see Fig. 3). Ensure that all such positions are well surrounded by paint to allow room on the copper for a good soldered joint. It is not necessary to make a good paint finish, merely cover the areas with sufficient thickness of paint. Straight edges make a better looking job, but provided adequate space is left between areas, it is unnecessary to be too particular. A mistake can be quickly removed and the area repainted. Allow time to dry, or at least to prevent the enamel "running," and the work is ready for etching.

motion with a piece of wood to prevent localised saturation by copper, but take care not to splash the liquid as it is corrosive. About half an hour will be required to remove the spare copper from a small panel, and the liquid may need replacing if it becomes saturated, but don't be impatient. After the first slight change of tone of the copper, success will only be observed by the disappearance of the copper from the edges first. Confirmation that all the spare copper has been removed is obtained by lifting the panel and looking through it at a strong light, when the full translucence of the baseboard will be apparent. Don't leave in the etch beyond this point. Pour the waste liquid away carefully, on waste ground, avoiding other metalwork.

#### Cleaning the Work

11. Both the dish and the board are washed under running water. Paint can now be removed with thinners, dope, or nail varnish remover; it comes off easier if it has not had time to dry really hard. The board is now thoroughly scrubbed under running water, using a mild household abrasive, such as Vim, to produce a bright clean surface (see Fig. 2 (b)). Unless it is intended to proceed at once with drilling and assembling, the areas to be soldered should be protected from oxidation by painting with flux as described below.

should again be cleaned and scrubbed and then the areas immediately around the holes lightly painted with a very thin film of paste flux. Too much flux will cause a run of solder when connecting and will produce an untidy job. Paste flux is useful here as a liquid flux tends to spread too far.

15. Before use all component wires should be well tinned; dirty or dry wires will not solder easily and excess heat damages the copper bond. Successful wire tinning can be achieved by:

- (a) dipping in a good liquid flux such as Enthoven Superspeed Liquid Flux;

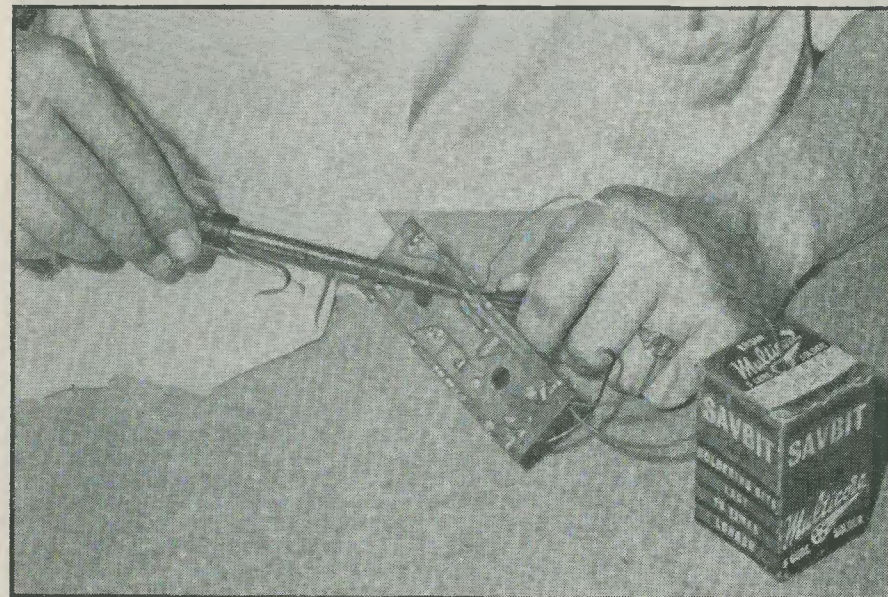


Fig. 6 Soldering-in a resistor

#### Drilling

12. All the holes can now be drilled, using a size for component wires that just gives a clearance—too large a hole produces a poor soldered joint. Larger holes for valve bases and parts, etc., can be drilled and cleaned out. Absolute accuracy is unnecessary; "surplus holes" don't matter unless the circuit is completely broken by the hole.

13. The panel should now be thoroughly inspected for good connections where required and absence of unwanted short circuits from faulty etching. A continuity tester is required here.

#### Preparing Board and Components

14. To remove any oxidation the copper

(b) holding the wire at the component end with flat nose pliers to conduct away the excess heat from the component and act as a heat shunt;

(c) drawing a clean hot iron downwards from the component end of the wire and off the other end applying the resin-cored solder to the wire at the same time (see Fig. 5).

The blob that forms at the wire end can be cut off before passing the wire through the fixing hole if the wire is left long enough.

16. Remember that a heat shunt is *always* required at the component end of wires when heating. If pliers are not used, ordinary small crocodile clips or sprung Dinkie pin curlers (available from Woolworths), with



## On Buying an HRO Receiver

By L. H. Rouse and J. B. Dance, M.Sc.

THE HRO RECEIVER HAS BEEN ON SALE ON the surplus market for many years; whilst its performance is undoubtedly surpassed by modern equipment, it is nevertheless a very good general coverage receiver and is deservedly popular with transmitting amateurs and short wave listeners. At the present time the HRO may be obtained in London for amounts varying between about £15 and £23, depending on the condition of the receiver and the number of coil units supplied. The cost of packing and postage on the receiver is well over £1 and it is therefore worthwhile contemplating a journey of reasonable length to fetch it, especially as one then has the chance to pick and choose from a large number of receivers.

The receiver has plug-in coils and this is often considered to be its greatest drawback. It must be remembered, however, that the coils are totally enclosed in metal and all of the coils for any one desired frequency range are plugged into the front of the receiver as one unit. Nine coil units were supplied with the receiver obtained by one of the authors (an HRO Senior with a crystal filter unit), but it is possible to obtain extra bandspread coil units. As each coil unit has measurements of about 10in x 4in x 2½in, it can be seen that the coils consume much space and it is highly desirable that they should be housed in a suitable cabinet. The receiver covers from 50 kc/s to 30 Mc/s in the nine ranges—an exceptionally wide coverage.

The i.f. is that which is commonly used in American receivers, that is 456 kc/s. This gives reasonable selectivity, but the selectivity could be very much improved by the addition of a second intermediate frequency unit operating at about 50 to 100 kc/s (see July 1959 article in *Practical Wireless* by one of the authors). The HRO does suffer slightly from second channel interference in the 10-metre amateur band because of the

comparatively low intermediate frequency and even the use of the two r.f. stages does not completely prevent this type of interference. Considerable modifications would have to be carried out to eliminate it, such as adding a preselector or tapping down some of the r.f. coils.

The mutual conductance of the 6D6 valves used in the r.f. stages is comparatively small and therefore the signal-to-noise ratio of the HRO between about 15 and 30 Mc/s is not as good as that of a good modern receiver. Methods have been described (for example in the February 1949 edition of *QST*) whereby the signal-to-noise ratio of the HRO may be increased by the use of modern miniature valves in the early stages of the receiver, but such methods involve considerable redesign and rebuilding. It is very doubtful if many people who have recently paid £20 or so for an HRO will wish to strip down a large part of it. The modifications described in this article are of an extremely simple type, require practically no thought whatsoever, and may therefore be easily carried out by the novice.

The "S" meter in the receiver purchased did not give suitable readings and the reason for this was found to be that the final 6D6 i.f. valve which helps control the "S" meter was not performing within its published characteristics. The 6D6 valves were changed about to provide a temporary solution to the problem until a new valve could be obtained.

The gain of the receiver can be considerably increased by reducing the value of the biasing resistor in the cathode circuit of the final intermediate frequency amplifier. The value of this resistor supplied in most receivers is between 1,000 and 5,000 ohms, but it can be conveniently reduced to about 300 ohms. Besides improving the performance of the receiver, the increased gain makes the "S" meter readings much more satisfactory.

heavy copper wire soldered to the ends, may be clipped to the wires. Locking surgical forceps have been found to be ideal for this purpose.

### Fixing and Soldering

17. Bend the component wires carefully with pliers to allow them to fit easily into the respective fixing holes. If vibration is expected, unequal lengths of wires will reduce resonance effects. Components may be mounted either side of the board, but it is preferable for accessibility to have components on the plain side and solder on the copper side. More rigid construction is achieved by fixing components close up to the board, but better heat insulation when soldering is achieved by having the components well "stood-off" if space and vibration are not critical. A small loop may be formed in the wire close to the component before it passes through the panel, so increasing the heat path to the component yet allowing the wire to be firmly held against the board. All components can be fitted to the panel, the wire ends turned to lie along the copper, and the layout "proved" before soldering.

18. To solder, use a low wattage iron with a small clean hot bit. The Adcola 25 watt or Henley instrument types are suitable. Large electrician's or gas heated irons are

useless for printed circuits (except in expert mass production hands) and so also are dirty, corroded or "lukewarm" bits. The thin (22 s.w.g.) Ersin Savbit Multicore solder is better than the larger size for printed circuit soldering as the quantity per joint can be more carefully controlled. 18 s.w.g. Ersin or Enthoven solder is satisfactory but thicker gauge solder is difficult to control.

19. Apply a heat shunt to each wire before soldering—this is particularly important for transistor wires—and apply the soldering iron tinned surface to the copper adjacent to the wire and apply the resin-cored solder at the same time to both copper and wire (Fig. 6). If maximum heat is applied to the copper and less to the wire, the solder will quickly run to form a small bright blob around the wire. Both iron and solder should be removed as soon as the wire has been completely encircled since excess heat or solder does no good at all.

20. Inspect all joints for faulty or inadequate bonds, then snip off the excess wires and the job is done. No additional protection for the joints or copper is really needed.

21. If sufficient copper has been left on the board, a circuit change can be subsequently effected by isolating a piece of copper with a razor blade, drilling new holes and linking the two areas concerned with a piece of tinned wire as if it were a component.

## Can Anyone Help?

Requests for data are inserted free of charge. Enquirers undertake to answer all correspondence and defray all expenses

**R3121 Receiver.**—M. Higginson, 8 Buckingham Road, Bicester, Oxon, would like to borrow or purchase a service sheet on this receiver.

**R1475 Receiver.**—H. S. Griffiths, 10 Parkview, Legsby, Market Rasen, Lincs, requires a service sheet or manual of this equipment, especially in relation to the "guard" channel and type of crystal used.

**Champion "Planet" Receiver.**—F. H. Holdsworth, 29A Alexandra Drive, Gypsy Hill,

London, S.E.19, wishes to borrow or purchase a service sheet for this five-valve a.c./d.c. receiver.

**"The Radio Constructor."**—A. G. Nicholl, Byard House, Stamford, Lincs, would like to purchase the November 1956, January and February 1957 issues of the magazine.

**CR100 Receiver.**—G. Coombe, 45 Saxon Road, Exeter, Devon, wishes to buy or borrow the circuit, manual, etc.

## R.A.E. and Morse classes

Grafton Radio Society (G3AFT) announce that 72 attended the first three evenings of their well-known R.A.E. and Morse classes. As 41 attended on the Monday evening, they regret that no more applicants can be considered for that evening, but there are a few vacancies for the Tuesday and Wednesday

repeat lectures which are held at Montem School (Room 35), Hornsey Road, Holloway, London, N.7 (R.A.E. 7-9 p.m.; Morse 9-10 p.m.). In addition to the above, the usual club meetings are held every Friday evening, 8-10 p.m., to which new members and visitors are indeed welcome.

### ERRATA

In the article entitled "A Guitar Amplifier" in the last issue an error occurred in the Inverse Feedback diagram on page 201. The 500kΩ grid leak should have been returned to the 10kΩ resistor side of the 0.5μF condenser and not to the top side as shown.



The automatic gain control (a.g.c.) of the receiver is connected to both the first and the second r.f. stages and also to both of the i.f. stages of the HRO. Although the a.g.c. action is improved by applying a.g.c. to the first r.f. stage, the signal-to-noise ratio on high frequencies is reduced. This is because the a.g.c. bias reduces the mutual conductance and therefore the gain of the first r.f. stage. This allows the noise generated in the input circuit of the receiver to become more important on high frequencies where the noise from the aerial is small. The receiver signal-to-noise ratio on high frequencies can therefore be improved by removing the 500k $\Omega$  resistor ( $R_1$  in Fig. 1 (a)) connecting the a.g.c. line to the first r.f. valve of the receiver. The bottom of the tuned circuit must then be earthed as shown in Fig. 1 (b). The 0.01 $\mu$ F condenser ( $C_1$ ) may be completely removed.

switching in the additional resistor,  $R_3$  in Fig. 1 (b) between the cathode resistor of the r.f. valve and earth for use only when powerful signals are being received. The value of this resistor may be between 500 $\Omega$  and 30k $\Omega$  and should preferably be chosen to obtain the desired results when powerful stations are being received. A potentiometer could be used instead of this switched resistor, but if the potentiometer is not returned to zero for reception of all but the most powerful signals, then the "S" meter readings and signal-to-noise ratio would be affected. It is generally easier to remember to return the switch than it is to return a potentiometer to zero. The additional resistor should be shorted out by the switch  $S_1$  when any signals other than very powerful ones are being received.

Further improvement of the signal-to-noise ratio may be obtained by replacing the

instead of the 6D6 has been suggested (see *QST*, February 1949). Care should be taken to choose a valve which does not load the tuned circuits too much or greater second channel interference will be experienced. The addition of a preselector would probably be a better solution to the problem of obtaining better signal-to-noise ratio and good second channel rejection.


It is necessary to adjust the control of the HRO marked "r.f. gain" before using the "S" meter readings. This control is easily knocked accidentally by the hand after the adjustment has been made and the "S" meter readings are then meaningless. The panel of the HRO was therefore drilled so that a small metal clamping device could be used on the metal circle attached to the r.f. gain control and the setting could then be maintained. This makes the "S" meter much more convenient to use.

No noise limiter is present in the HRO and this is a great disadvantage when the receiver is used at high frequencies. It is preferable not to have to punch holes in the chassis in order to add a noise limiter valve and i.f. noise silencing circuits were not therefore used, although they can give better

results than an audio limiter. A germanium diode was tried at first in an audio limiter shunt circuit, but its forward resistance was high enough to prevent it from being really effective. In order to avoid chassis drilling an EA76 sub-miniature diode was used, as this has connecting wires coming directly out of the glass; it should be clipped to the chassis. A possible alternative (if there is enough space available) is the VR92 which is easily obtainable on the surplus market. The audio noise limiter "chops off the tops" of the noise peaks and considerably improves performance in noisy localities. The limiter circuit is conveniently placed between the detector and the input to the 42 output valve. The potentiometer to set the threshold at which the limiter begins to operate was fitted to a hole drilled in the front panel on the same level and to the right of the "S" meter on/off switch.

The HRO is certainly an excellent bargain and it is very doubtful whether its performance can be surpassed by any receiver within the same price range; it is probably the cheapest receiver approaching real communications standards available.

Next Month . . . HRO ALIGNMENT DATA

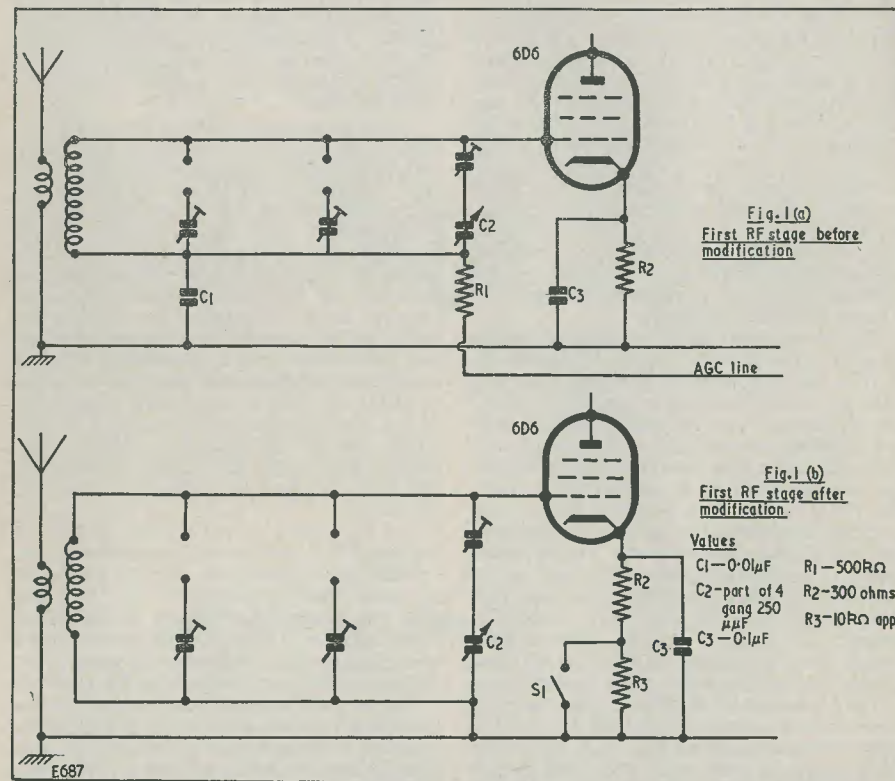

If the a.g.c. line is disconnected from the first r.f. stage as suggested, however, overloading and distortion may occur when powerful stations are being received. This trouble may be completely avoided by

first r.f. valve by one which has a higher mutual conductance; this will almost certainly require altering the valve base connections and receiver alignment, however, and may cause oscillation. The use of an 1851

## RADIO HOBBIES EXHIBITION

Royal Horticultural Old Hall, Vincent Square, London, S.W.1.  
25th to 28th NOVEMBER, 1959

### List of Exhibitors

Stand Nos.	Exhibitor	Stand Nos.
8	A.P.T. Electronics Ltd.	8
22	Avo Ltd.	22
1A	British Amateur Television Club	1A
17	Collins Radio Co. (of England) Ltd.	17
24	Data Publications Ltd.	24
(The Radio Constructor)		
18	Daystrom Ltd. (Heathkits)	18
10	Enthoven Solders Ltd.	10
26	Hi-Fi News	26
15/16	Home Radio (Mitcham) Ltd.	15/16
9	Iliffe Press Ltd.	9
(Wireless World, Electronic and Radio Engineer)		
14	Jason Motor and Electronic Co.	14
13	K.W. Electronics Ltd.	13
7	Labgear Ltd.	7
21	Minimitter Co.	21
20	Mullard Ltd.	20
32/33	Mayra Electronics Ltd.	32/33
8	Norman Price (Publishers) Ltd.	8
31	Richard Maurice Equipment Co.	31
6	Relda Radio Ltd.	6
19	Short Wave Magazine Ltd.	19
11	Siemens Edison Swan Ltd.	11
12	Taylor Electrical Instruments Ltd.	12
28	Territorial Army	28
23	Royal Navy	23
2	Royal Air Force	2
29	Radio Society of Great Britain	29
4	James Scott & Co. (Electrical Engineers) Ltd.	4
29A	U.H.F. Group	29A
1	"Communication Receivers of the World"	1

Featuring the latest designs by:  
Airmec, Collins, Eddystone, Geloso, Hall-crafter, Heathkit, Marconi, Minimitter, National, Racal, Siemens-Ediswan, and other leading manufacturers.



# The "Different" Hi-Fi Unit

By R. S. SQUIRES

THE "DIFFERENT" HI-FI UNIT WAS DESIGNED and constructed to fulfil these specific requirements. They were:

- (1) To provide a reasonable output stage for an old radiogram which had been modified to take a four-speed auto-changer.
- (2) To save the expense involved by the addition of a push-pull output stage.
- (3) As an experimental project.

The extra components required are:

- One double-pole switch (rotary type);
- Two type 6BW6 valves (and valve-holders);
- One loudspeaker with matching transformer;
- Two, perhaps three, potentiometers;
- One 8 $\mu$ F condenser; and
- Sundry resistors and condensers.

The whole fits quite comfortably into a chassis measuring approx. 5in x 4in with a depth of 2in.

## The Circuit

A glance at the circuit diagram will show that the unit consists basically of two single-ended output stages, driven from a common stage: the original a.f. output valve of the receiver to which the Hi-Fi unit is to be added.

Volume control is provided by VR<sub>1</sub> and input is selected by SW<sub>1</sub>. The other half of the switch can be used to break the h.t. supply to the receiver-unit when the auto-changer is in use.

The actual configuration of "V<sub>4</sub>" will depend on the constructor's requirements, "V<sub>4</sub>" being the last stage in a conventional superhet circuit with single-ended output. It should be a fairly simple matter, though, to arrange the output stage of any receiver to conform approximately to the circuit given.

The output transformer in the original circuit has been replaced by R<sub>1</sub>. If a pentode valve is used then a value of about 250k $\Omega$  should suffice for this resistor, as what was previously a current amplifier now has to be converted to a voltage amplifier—without causing distortion of the input signal! Experiment, no doubt, will yield the best value.

From V<sub>4</sub> anode the amplified signal is passed to C<sub>1</sub> and C<sub>2</sub> (these should be good quality components of the values indicated) and thence to the control grids of V<sub>1</sub> and V<sub>2</sub>, via gain controls VR<sub>2</sub> and VR<sub>3</sub>.

The high frequency component only of the signal is fed to the grid of V<sub>2</sub>, due to the greater reactance to lower frequencies of C<sub>2</sub>. Hence a considerable control is possible over the "high" end of the audio spectrum reaching V<sub>2</sub>.

All signal frequencies are passed to the grid of V<sub>1</sub>, via C<sub>1</sub> and VR<sub>2</sub>, but the high frequency component is eliminated, after amplification, by the low reactance to them provided by C<sub>3</sub>. VR<sub>2</sub> controls the gain of V<sub>1</sub> and hence the low-frequency response of the unit. Therefore, the whole of the response characteristic can be adjusted to the listener's choice. The unit can, of course, be constructed simply as a Hi-Fi unit for use with crystal pick-ups, and be fitted into a portable record reproducer or similar system. "V<sub>4</sub>" could then be a 6J7 and component values for this particular arrangement have been given.

Note: It should, of course, be ascertained that the receiver can supply the additional currents required by the output valves, both h.t. and l.t. Should it prove incapable of doing so, then a separate power supply, and a larger chassis, will be required. In this connection, it should be remembered that replacing the existing output valve by a type such as the 6J7 will result in a reduction of the h.t. current needed by the receiver itself.


## Construction

The original unit was made, as has been mentioned, on an aluminium chassis measuring 4in x 5in x 2in. A 12-way tag-strip was mounted down the centre of the chassis, with the valves on either side: VR<sub>2</sub> and VR<sub>3</sub> were also mounted in the chassis both on the same side, and the whole unit was screwed into the cabinet by means of woodscrews passing through the chassis flanges into the front panel. VR<sub>1</sub> was left in its original position, though its value may need to be changed to suit the crystal input. Layout is not critical; but grid leads should be kept short and

screened if they exceed an inch or so.

The switch marked SW<sub>1</sub> was a rotary switch supplied by Bulgin Ltd., and was used, in the original unit, to break the h.t. supply to the radio tuner unit when the gram was in use. It also switched the input to the

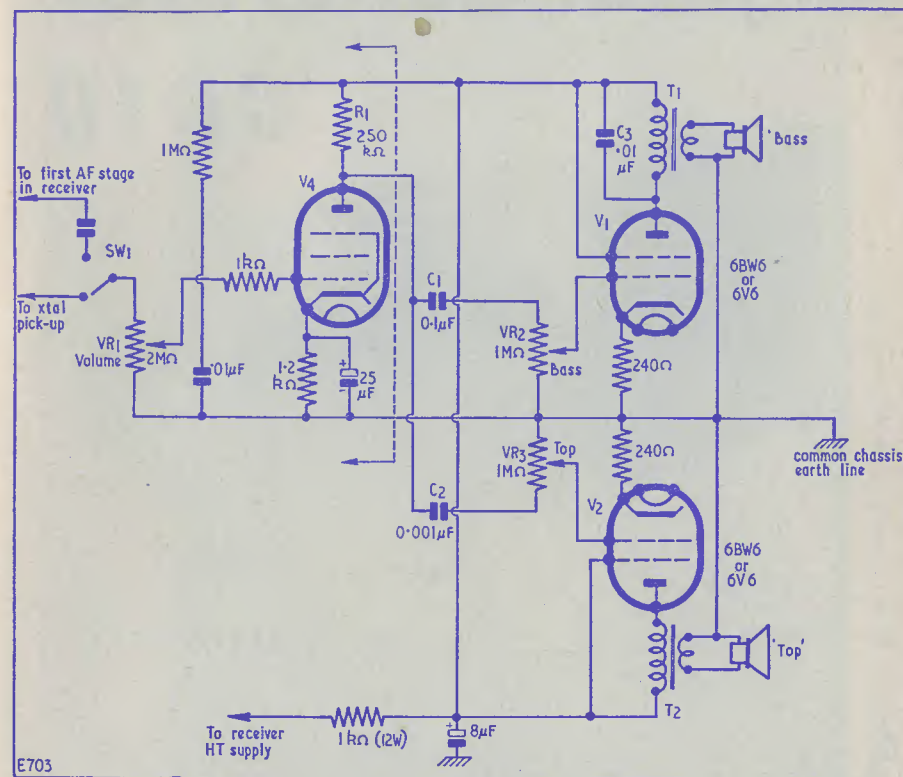transformer, the speakers must be correctly "phased." This is best done with a torch battery connected in turn to the primary of the output transformers. With the unit disconnected from the supply, of course, connect the +ve side of the battery to the



Circuit of the "Different" Hi-Fi Unit. Apart from SW<sub>1</sub> and VR<sub>1</sub>, all components to the left of the dotted line would have the original circuit values. R<sub>1</sub> replaces the original output transformer, and the values given here are those required when a 6J7 is substituted for the original output valve. This arrangement would also be used if the unit is constructed purely as a Hi-Fi amplifier

volume control from "radio" to "gram." The former function, however, is not really necessary, though a large signal appearing on the output of the receiver detector may well be coupled by "stray" effects into the input of the voltage amplifier stage.

The switch can be mounted in any convenient place. Grid leads should be kept short though, and it should not be adjacent to any wiring carrying mains or h.t.

## Speaker Phasing

When the whole has been completed, and a place found for the extra speaker and its


h.t. end of the transformer primary and the other terminal to the valve end of the primary. Note which way the loudspeaker cone "jumps" when contact is made and alter one transformer, if required, to make the cones move in the same direction when the process is repeated on the other output transformer.

## Results Obtained

The results obtained from the above system are quite satisfactory and compare favourably with the inexpensive class of Hi-Fi equipment.



# Crystal Calibrator CC10

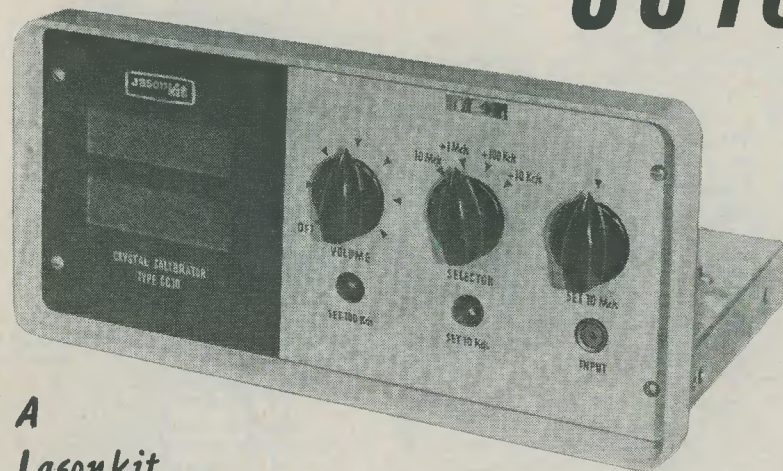

A  
Jasonkit  
Design


by G. BLUNDELL

A CRYSTAL CONTROLLED CALIBRATOR OF the type about to be described provides one of the most accurate methods of r.f. generator calibration available. The maximum accuracy which can be attained is ultimately governed by the frequency stability of the B.B.C. standard transmissions. Generators covering a frequency band of from 10 kc/s to some hundreds of megacycles can conveniently be checked.

Essentially, the CC.10 consists of a master crystal-controlled 1 Mc/s oscillator with 10 kc/s and 100 kc/s multivibrators synchronised to it. The output of these three oscillators is passed through a squarer providing a large number of harmonics into a mixer stage. This signal is combined with a further local 10 Mc/s oscillator and the signal from the generator under test. The resulting mixture is fed to an audio stage feeding an internal speaker. There is, therefore, a zero beat whenever the generator signal is such that it is an exact multiple of one of the internally generated harmonics.

Referring now to the circuit diagram, it will be seen that the crystal oscillator stage  $V_3$  consists of an EF80 valve connected as a modified Colpitts oscillator. This circuit scores over the more common type of crystal oscillator in the extremely good frequency stability with h.t. supply variation, and in that no critical component values are necessary. In fact, changes of up to 20% in the h.t. rail have little effect on the frequency. Normally the oscillator frequency will be within 0.01% of the nominal value, but greater accuracy may be achieved if it is varied slightly by means of the trimmer,  $TC_1$ . The procedure to be followed is described in the paragraph on testing procedure.

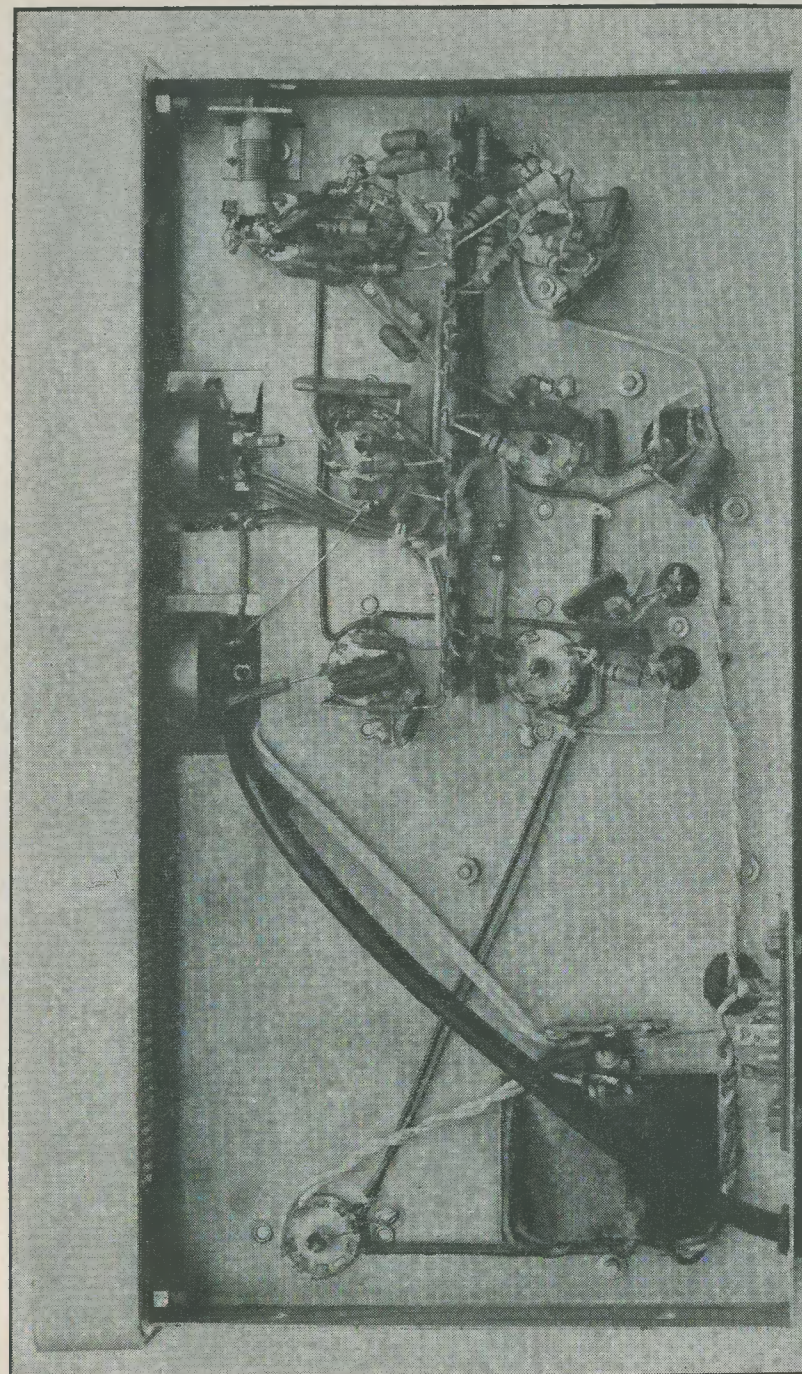$V_2$  (ECC81) is a symmetrical multivibrator which is free-running at a frequency of approximately 100 kc/s. This frequency is determined by the time constants of the cross-coupling condensers ( $C_5$  and  $C_6$ ) and the grid leaks ( $R_9$ ,  $R_6$  and  $VR_2$ ).  $VR_2$  is included in the frequency determining



Showing clean layout underneath—compare with Fig. 2



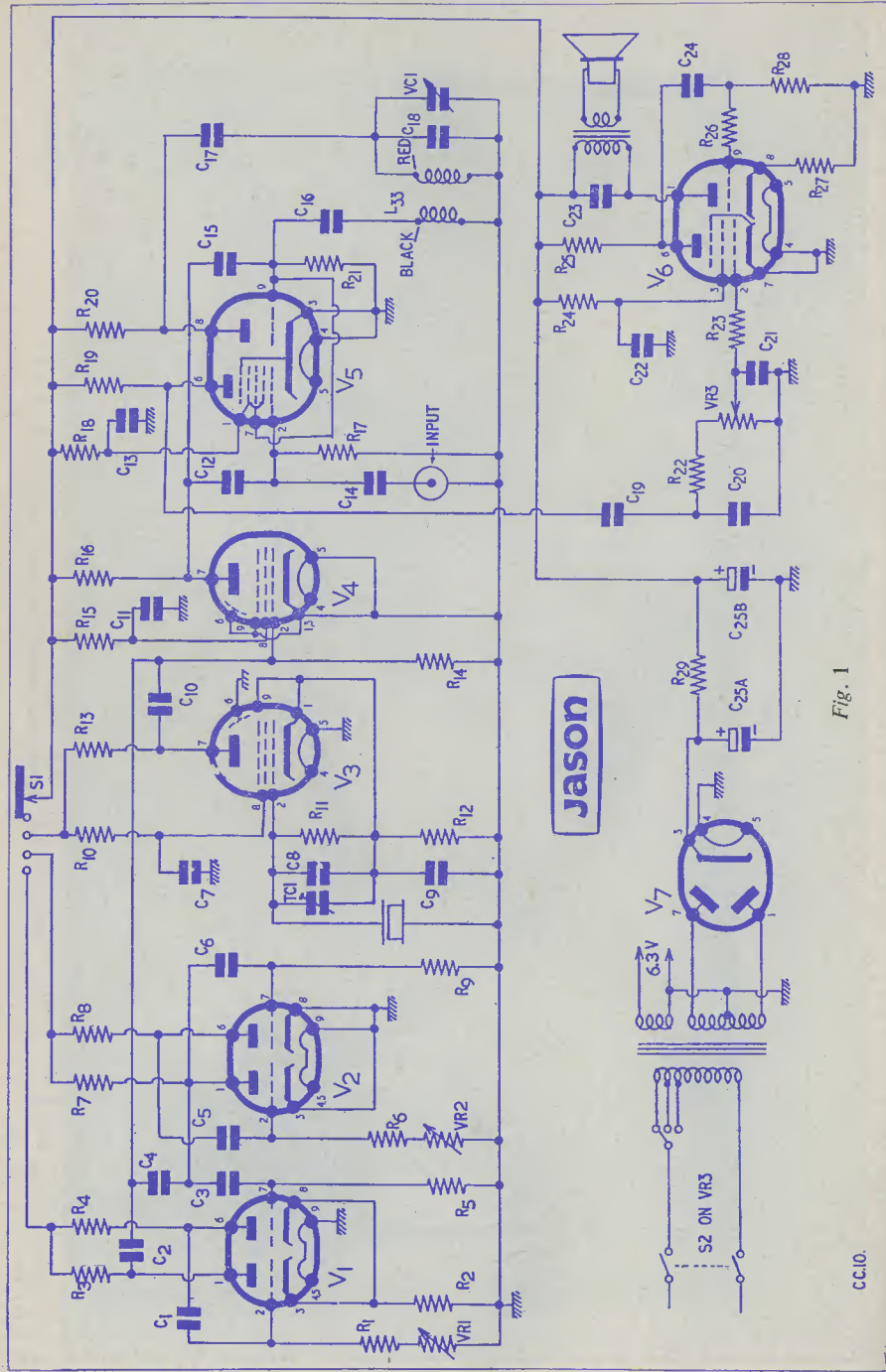


Fig. 1

## COMPONENTS LIST FOR THE JASON CRYSTAL CONTROLLED CALIBRATOR CC.10

Set out for easy reference to theoretical diagram above

### Resistors

R1	33kΩ ½W 20% carbon
R2	2.2kΩ ½W 5% high stability
R3	22kΩ ½W 20% carbon
R4	22kΩ ½W 20% carbon
R5	1kΩ ½W 20% carbon
R6	15kΩ ½W 20% carbon
R7	22kΩ ½W 20% carbon
R8	22kΩ ½W 20% carbon
R9	15kΩ ½W 20% carbon
R10	100kΩ ½W 20% carbon
R11	470kΩ ½W 20% carbon
R12	10kΩ ½W 20% carbon
R13	22kΩ ½W 20% carbon
R14	470kΩ ½W 20% carbon
R15	10kΩ ½W 20% carbon
R16	10kΩ ½W 20% carbon
R17	1MΩ ½W 20% carbon
R18	100kΩ ½W 20% carbon
R19	220kΩ ½W 5% high stability
R20	33kΩ ½W 20% carbon
R21	47kΩ ½W 20% carbon
R22	47kΩ ½W 20% carbon
R23	10kΩ ½W 20% carbon
R24	1MΩ ½W 20% carbon
R25	220kΩ ½W 20% carbon
R26	10kΩ ½W 20% carbon
R27	470kΩ ½W 20% carbon
R28	470kΩ ½W 20% carbon
R29	2kΩ 3W 10% w.w.

### Condensers

C1	500pF 2% silver mica
C2	3.3pF ceramic
C3	5pF ceramic
C4	3.3pF ceramic
C5	100pF 10% silver mica
C6	100pF 10% silver mica
C7	5,000pF ceramic
C8	33pF 10% silver mica
C9	150pF 10% silver mica
C10	500pF ceramic
C11	5,000pF ceramic
C12	5pF ceramic
C13	5,000pF ceramic
C14	5pF ceramic
C15	3.3pF ceramic
C16	100pF 10% silver mica
C17	5,000pF ceramic
C18	100pF 10% silver mica
C19	5,000pF ceramic
C20	500pF ceramic
C21	500pF ceramic
C22	5,000pF ceramic
C23	5,000pF ceramic
C24	5,000pF ceramic
C25	50+50µF 275V wkg.

### Valves

V1	ECC81
V2	ECC81
V3	EF80
V4	EF80
V5	ECH81
V6	ECF80
V7	EZ80

### Potentiometers

VR1	100kΩ linear preset pot.
VR2	10kΩ linear preset pot.
VR3	250kΩ log. pot. with switch

### Miscellaneous

TC1	3-15pF variable air spaced trimmer, Jason type CT2
TC2	1-15pF variable air spaced trimmer, Jason type CV8
S1	Jason switch type No. S112
Mains transformer,	Jason type No. MT51
Output transformer,	Jason type No. OT4
Oscillator coil,	Jason type No. L33
Loudspeaker,	Jason type No. Z155
1 Mc/s crystal,	Jason type No. Z130

circuits to enable small frequency changes to be made. A synchronising signal is taken from the output of V<sub>3</sub> (the crystal oscillator) and fed through C<sub>4</sub> to one of the double triode anodes. This condenser serves a double purpose in that the multivibrator output signal also passes through it and combines with the output of V<sub>2</sub> at the grid of V<sub>4</sub> (EF80).

The 10 kc/s multivibrator V<sub>1</sub> (ECC81) is

of the asymmetrical cathode-coupled type. The main frequency determining components in this case are the coupling condenser C<sub>1</sub> together with R<sub>1</sub>, VR<sub>1</sub>; the provision of VR<sub>1</sub> again enables small frequency shifts to be made. Synchronising signals are taken from the output of the 100 kc/s multivibrator through C<sub>3</sub> to the remaining free grid. The output is taken from an anode through C<sub>2</sub> to the grid of V<sub>4</sub>. This stage is



operated with zero bias and acts as a limiter, with the result that the sine wave input is amplified and converted to an approximation of a square wave with its large number of harmonics of the original fundamental frequency. This composite signal is fed through C<sub>12</sub> to the grid of V<sub>5</sub> (ECH81), which in some respects operates in a similar fashion to the frequency changer in a superhet receiver.

In place, however, of the usual variable frequency local oscillator there is a fixed frequency oscillator running at 10 Mc/s. This is a conventional tuned anode circuit utilising the triode of the ECH81 as the oscillator valve. An unusual part of the circuit is the provision of C<sub>15</sub>, which makes it possible to lock the 10 Mc/s oscillator to the 1 Mc/s standard.

However, instead of the usual intermediate frequency which is obtained from the mixer in a superhet receiver, the output in this case consists of audio frequency signals derived from the frequency difference between the "aerial signal" from a signal generator under test fed into the ECH81 grid and a harmonic of one of the internally generated frequencies.

This audio signal is fed to an audio amplifier V<sub>6</sub>, consisting of an ECF80 valve. The only requirement of this stage is high sensitivity together with stability, and this is achieved at the cost of a limited frequency response and a fairly high level of distortion. The pentode portion of the ECF80 acts as a high gain voltage amplifier feeding the triode acting as a power amplifier giving a power output of about ½ watt. The high note response is purposely limited to prevent instability and the low note response to reduce microphony.

At this stage, the operation of S<sub>1</sub> requires some explanation. It will be seen that the h.t. supplies of V<sub>1</sub>, V<sub>2</sub> and V<sub>3</sub> are taken through this switch with the result that the 10 Mc/s oscillator is the only one which is always operating. On turning the switch from the position shown on the circuit diagram to the next position, h.t. will become available to V<sub>3</sub> the 1 Mc/s oscillator. The 10 Mc/s oscillator which so far has been free running will lock and run in synchronisation. On turning the switch to the next position, the 100 kc/s multivibrator will be brought into operation and finally the 10 kc/s multivibrator will be switched on. This allows easy identification of the various harmonics, but this will become more apparent on reading the paragraph on operating instructions.

#### Assembly Notes

The assembly follows normal practice for fixing valveholders, tagstrips, etc., the details being given on Figs. 2 to 4, and only a few points require explanation.

(a)  $\frac{3}{16}$  in long 6BA screws are used for fixing the two preset type potentiometers. These screws must not be longer because they would lock the potentiometer centres.

(b) The co-axial output socket is spaced away from the front panel with two 4BA nuts which fit loosely over the 6BA fixing screws.

(c) The two valve retainer clips are used for holding the crystal firmly in place. They should be pushed through the small holes at the sides of the crystal holder and clipped over the body of the crystal.

(d) The fixing of the frame surround casting is best left until wiring is complete, when it can be screwed to the chassis with 4BA screws through the recessed holes at each corner of the casting. 4BA spring nuts can then be slipped over the appropriate drilled thin flanges to correspond with the fixing holes on the scale.

(e) The cover is fitted into the slot running round the rear of the casting and screwed to the 4BA hank bushes on the sides of the chassis. The base and back are screwed into place with self-tapping screws after the cover has been fixed in position.

#### Wiring Notes

(a) The components shown on the wiring diagrams Figs. 2, 3 and 4 are not necessarily drawn to scale, but indicate the connection and appropriate position taken up by each component.

(b) The wiring diagrams should be followed during assembly but to gain familiarity with the instrument it should, at every stage of the assembly, be compared with the circuit diagram.

(c) Wires and component leads should be pushed through and wrapped around tags and valveholder pins to ensure a firm mechanical connection. No tag or valveholder pin should be soldered until all the leads and components on that particular tag are in place and have been checked.

(d) Connecting wires should be straight with sharp distinct bends and be run flat touching the chassis.

#### Wiring Procedure

(a) Earth the centre spigot and appropriate pins on each valveholder to a soldering tag, as shown on Fig. 2.

(b) The wire connections are best made before the actual components are wired in place. Leads running from the underside to the top of the chassis are lettered on the diagrams to facilitate tracing.

(c) The remaining resistors and condensers can now be wired in place.

#### Testing Procedure

(a) Check all wiring thoroughly. Time

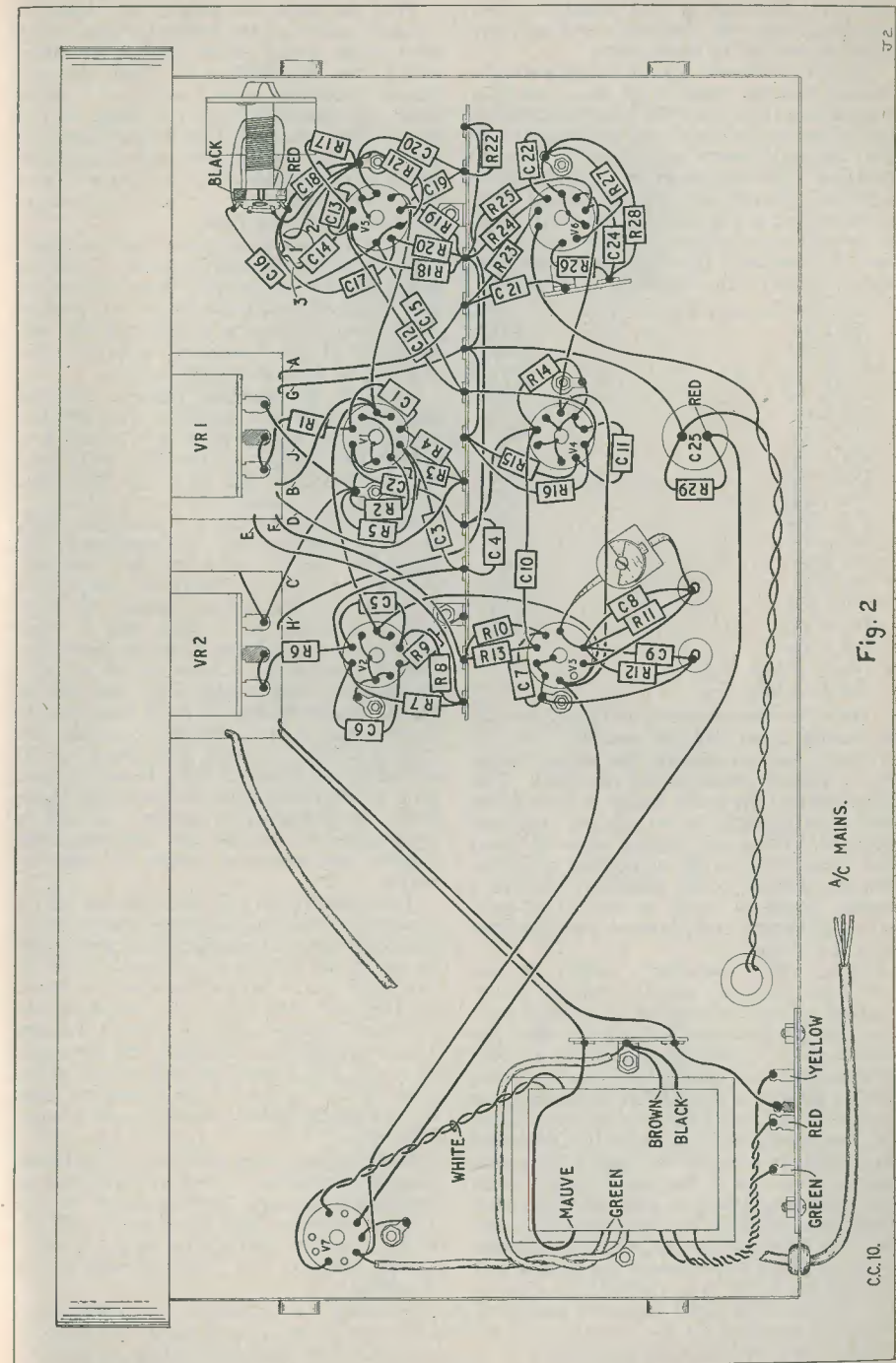


Fig. 2



spent in checking is well spent, as any mistakes may be rectified without any possible damage to components.

(b) An ohmmeter connected between the chassis and the junction of  $R_{29}$  and  $C_{25b}$  should read about  $20k-50k\Omega$ . On switching on the following voltages should be obtained with the "Selector" switch set to the "+ 10 kc/s" position. The voltages in the table should be regarded as giving the order of voltage to be expected and not necessarily the exact value, as tolerances in component values will cause some differences. The readings in the table were obtained with a 10,000 ohm/V meter.

Junction $R_{29}$ ; pins 3 and 8 $V_{1..}$	4V
Pin 1 $V_1$	95V
Pin 6 $V_1$	120V
Pin 1 $V_2$	70V
Pin 6 $V_2$	120V
Pin 7 $V_3$	105V
Pin 8 $V_3$	90V
Pin 1 $V_3$	15V
Pin 7 $V_4$	105V
Pin 8 $V_4$	125V
Pin 1 $V_5$	13V
Pin 6 $V_5$	75V
Pin 8 $V_5$	40V
Pin 8 $V_6$	$4\frac{1}{2}V$
Pin 1 $V_6$	130V
Pin 6 $V_6$	20V
Pin 3 $V_6$	15V
Junction $R_{29}$ , $C_{25b}$	135V
Junction $R_{29}$ , $C_{25a}$	200V

With the volume control set fully clockwise, a hissing noise will be audible from the speaker; and on tapping the output valve,  $V_6$ , a ringing noise should be heard. This indicates that the audio section is functioning and it is possible to set up the oscillator sections. There are several ways of doing this, depending on the equipment available, but the method to be described requires a signal generator with a minimum band coverage of from some hundreds of kilocycles to a few megacycles.

Switch the "Selector" switch to the +1 Mc/s position, and the "set 10 Mc/s" control so that the trimmer  $VC_1$  is half open and the pointer on the knob on the scale datum mark. Screw the core of  $L_{33}$  out with a non-metallic trimming tool (e.g. a knitting needle filed to a screwdriver shape) until an audible note is heard from the speaker. Carry on unscrewing until the note has decreased in frequency, passed through a zero and started to go up in frequency again. Screw the core in to the zero position. The same beat note will now be obtained on turning the "set 10 Mc/s" control, and the zero beat position of the knob should correspond with the datum mark. The oscillator is now set to 10 Mc/s. The signal generator mentioned earlier is required for the setting up of the 100 kc/s and 10 kc/s multivibrators.

Plug the generator output lead into the "Input" socket of the calibrator and switch to a range giving about 2 Mc/s frequency swing over the whole scale. With the calibrator "Selector" switch set to +1 Mc/s, tune the generator over the range of the scale. Beat notes will be heard when the generator is swung through frequencies which are a multiple of 1 Mc/s. At this point it is possible to check the scale accuracy of the generator being used.

Select two of these beats and note their position on the generator scale. Tune the generator slowly between these two points and listen if any weak beats are present. With most generators, a spurious beat will be heard at the "half-way" position. The position of these should be noted.

To give an example, suppose that the generator is set to a range covering 250 kc/s to 2.5 Mc/s; strong beats will be heard at 1 Mc/s and 2 Mc/s and probably weak beats will be heard at 500 kc/s, 1.5 Mc/s and 2.5 Mc/s.

Now set the generator to 1 Mc/s (according to the calibrator and not necessarily the generator scale!) and turn the "Selector" switch to +100 kc/s. Swing the generator to 2 Mc/s and count the number of beats including those at 1 Mc/s and 2 Mc/s (neglecting any of the spurious beats previously noted which in any case will be found to be very much weaker than the genuine ones). Anything from 8 to 12 beats will be heard, and it is necessary to adjust the "Set 100 kc/s" control until there are 11 including the 1 and 2 Mc/s beats. A faint plop will be heard as the multivibrator jumps from one frequency to another. It will be appreciated that due to the synchronisation applied, the frequency cannot be smoothly varied.

To adjust the 10 kc/s multivibrator set the generator to a range covering some hundreds of kilocycles (our imaginary generator would be set to the 25-250 kc/s range). With the calibrator set as before, beats will be heard at 100 and 200 kc/s. On switching the "Selector" switch to the "+ 10 kc/s" position, a faint whistle will be heard, the frequency of which will depend on the setting of the "Set 10 kc/s" control. The procedure given for setting the 100 kc/s multivibrator is again followed.

With the unit wired according to the layout diagram and with  $TC_1$  set to about half its maximum capacity, the frequency of the 1 Mc/s oscillator will be within  $\pm 100$  c/s. It is, however, possible to obtain a much closer tolerance by the method to be described.

Provided the calibrator has been built according to the layout diagram, no difficulty should be experienced in setting up the unit.

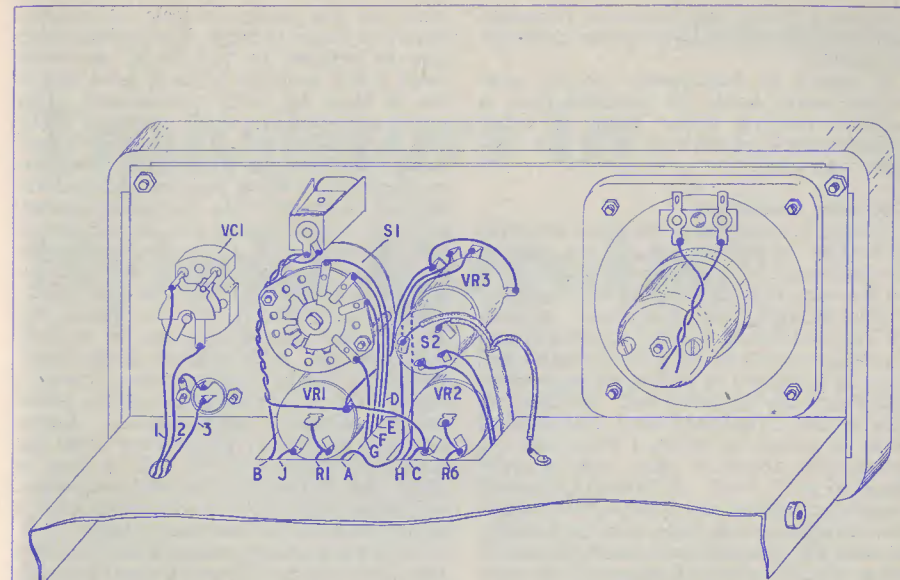


Fig. 3

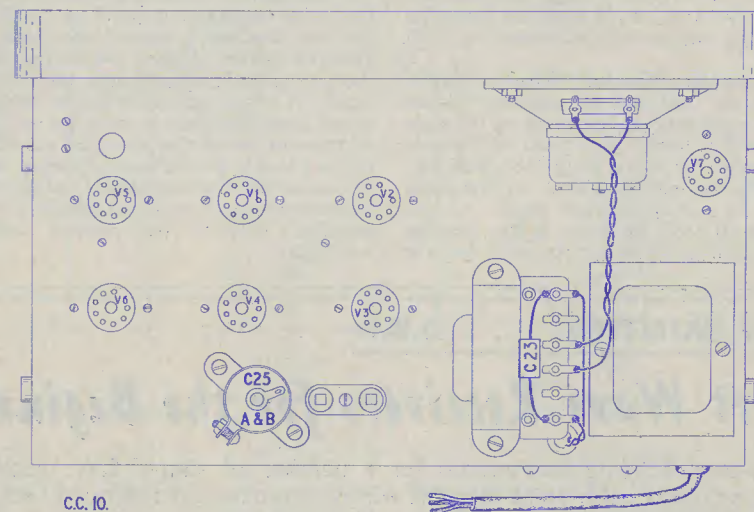


Fig. 4



The Jason Motor and Electronic Company will, however, undertake to test the calibrator if required.

It should be emphasised that the component parts should be obtained from a supplier retailing either Jason or other manufacturers' equivalents which are "designer approved."

**Operating Instructions**

On any range setting of the signal generator under test, the frequency at any one point of the scale must be approximately known with an accuracy which depends on the frequency.

For example, for frequencies between 10 kc/s and 900 kc/s, the frequency at one particular setting of the tuning control will have to be known to within 100 kc/s before calibration can be carried out. For frequencies between 1 Mc/s and 9 Mc/s, the frequency must be known to within 1 Mc/s, and for frequencies above 9 Mc/s, the accuracy required is 10 Mc/s. A little thought will show that these are not very stringent requirements, particularly as in the majority of cases the generator under test will already have a scale giving frequencies—however inaccurately. If not, the tuning scale of a domestic receiver into which the generator signal is fed can always be relied upon to give the frequency to the very wide limits laid down.

The actual calibration procedure is best explained by means of an example. Let us imagine that, at one range setting of the generator, the frequency range to be covered is reputedly 800 kc/s to 15 Mc/s; an unusually wide range, but one which serves as a good example.

If we set the calibrator "Selector" switch to "10 Mc/s" and turn the generator tuning knob over the scale at one point on the scale a "pip" will be heard. This point on the scale must clearly correspond to 10 Mc/s, and may tentatively be marked either on the scale itself or on a sheet of graph paper. At this stage the 10 Mc/s oscillator is free running and the calibration is not accurate, but the

mark on the generator scale is certainly known to within 10 Mc/s. The calibrator can now be switched to "+1 Mc/s," at which point it will probably begin to howl due to the 10 Mc/s not being synchronised. This can be remedied by a small movement of the "set 10 Mc/s" control. The generator is then tuned again over the band and the positions on the scale at which pips are obtained are marked as before. The frequencies corresponding to these pips can be established with reference to the 10 Mc/s position which has already been established. The procedure is then repeated with the 100 kc/s multivibrator switched in; and, if required, the 10 kc/s multivibrator can also be brought into operation. If the position of the "pips" have been marked on graph paper, a smooth curve can now be drawn through the points and a calibration curve obtained. Before making a calibration the generator under test should be switched on for half an hour to allow the frequency to stabilise, otherwise confusion may exist if the various markings on the calibrator are not repeatable.

To achieve greater accuracy the following procedure may be followed to set the 1 Mc/s master oscillator closer to the nominal frequency.

It is well known that the carrier frequencies of B.B.C. transmitters are maintained to very close limits; in fact, the 200 kc/s Droitwich Long Wave Transmitter frequency is maintained within the outside limits of  $\pm 0.004$  c/s.

If the output of a signal generator is fed into any receiver covering the long waveband, the signal generator may be set to 200 kc/s by zero beating it against the Light Programme carrier. If now the output lead of the generator is plugged into the calibrator input, TC<sub>1</sub> may be set for a zero beat. The signal generator must be switched on at least 15 minutes before this is carried out for it to attain a steady temperature, ensuring that the frequency will stay reasonably stable between the short period when the output lead is being switched between the receiver and the calibrator.

# Transistors in Hybrid Circuits

by F. L. ASH

ALTHOUGH NUMEROUS ARTICLES HAVE appeared, both in this magazine and others, on transistor circuits, very little has been written about using transistors in conjunction with valves in hybrid circuits. In the following paragraphs, some of the problems involved in using transistors and valves together are discussed.

One possible application of the transistor is as the voltage amplifying stage in a portable receiver. There are several possible arrangements in this application, and these will now

considered first.

The first problem is the transistor supply, which for p-n-p types must be negative with respect to earth. In hybrid circuits such as this it is always desirable to avoid the use of a separate battery for the transistor. The l.t. supply of 1.4V is too low if the transistor is to be used with a resistive load. Fortunately a convenient supply already exists—the back bias developed for the output valve. In the case of the DL96 output valve this is approximately 5.2V. The circuit,

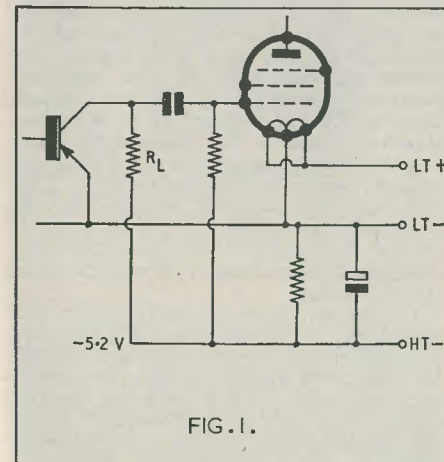


FIG. 1.

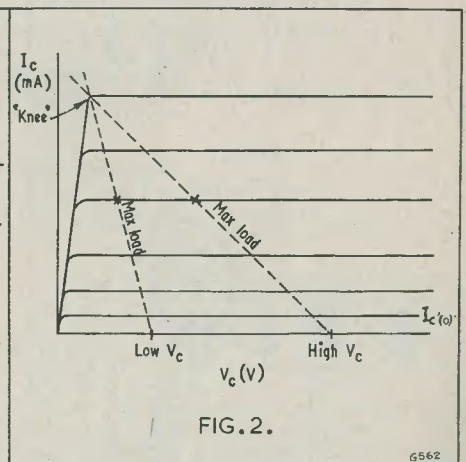


FIG. 2.

be considered. Since the transistor output will be fed into a high impedance circuit (i.e. the grid of the output valve), either a grounded base or grounded emitter circuit can be used. The latter has a higher input impedance, which is preferable when feeding from the detector circuit, and this arrangement will be

arrangement is shown in Fig. 1.

The biasing arrangement for the transistor is not shown in this circuit. Should a higher transistor supply be required, an extra 1.4V can be obtained by returning the emitter to l.t.+ instead of l.t.—.

As in the case of valves used as voltage

NOW PRINTING . . . D.B.14

## Short Wave Receivers for the Beginner

Step-by-step Building Instructions for a number of simple S.W. receivers, battery or mains, with point-to-point wiring diagrams, photographs, etc. and including an introductory chapter on S.W. techniques.

6s. 0d. postage 5d.

72 pages, plus cover

DATA PUBLICATIONS LTD



57 Maida Vale London W9



amplifiers, in general the higher the load the higher the voltage gain, although there is a maximum value for the load. Beyond this value, the gain stays constant, but distortion increases.

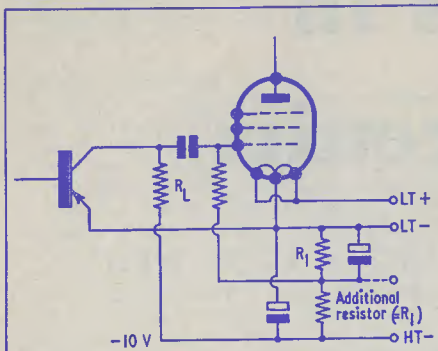


FIG. 3.

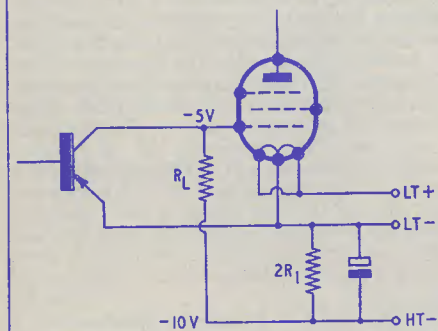


FIG. 4.

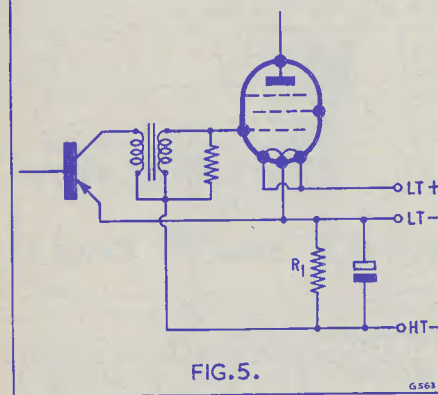


FIG. 5.

The value of transistor load which can be used is limited by three main considerations.

The first of these is the collector supply voltage. The higher the collector supply voltage the larger the load can be made, since for a given collector current more voltage can be dropped across the load, whilst still maintaining a workable voltage at the collector itself. The second factor is the "knee" of the characteristic. Operation below the knee (i.e. with high values of load resistance) will result in severe distortion. The third factor is collector leakage current ( $I_{c(o)}$ ) which is temperature sensitive. An increase in temperature will raise the leakage current and drive the operating point further up the load line towards the knee. These factors are illustrated in Fig. 2.

For these reasons a fairly low value of load must be used, 4.7kΩ being a typical value, with a maximum of about 12kΩ.

To return now to the circuit of Fig. 1. This will give quite good results but it is not possible to fully load the output valve. From the valve data for the DL96, it will be seen that an input voltage of 3.4 volts r.m.s. is required to fully load the valve. This corresponds to a peak input voltage of 4.8V (almost equal to the bias voltage). Thus the grid is driven from the normal bias point up to -0.4V, and back to -10V for full output, a peak-to-peak voltage of 9.6V.

Since a supply of only 5.2V (or 6.6V) is available, the peak-to-peak drive from the transistor cannot exceed this value, and the output valve will be underdriven. This will be found to hold true for any battery-operated output valve. The difficulty can be overcome by quite a simple modification. If an additional resistor, equal to the existing bias resistor, is connected in series with the negative h.t. terminal, an additional voltage equal to the bias voltage will be developed across this resistor. The bias voltage is taken from the same point as before, and this extra voltage used to supply the transistor. (See Fig. 3.) The additional resistor must be adequately decoupled.

Care must be taken that the voltage does not exceed the maximum value for the transistor, of course.

If suitable values of load resistor and operating current are chosen for the transistor, it can be arranged that the voltage at the collector is equal to the bias required for the output valve. If this is the case, the grid capacitor and resistor can be omitted and the two stages directly coupled, as shown in Fig. 4.

#### Transformer Coupling (Fig. 5)

If the maximum gain is required from the transistor, transformer coupling should be used. The maximum value of the grid resistor should be used for the output valve (3MΩ in the case of the DL96) and the

transistor matched to this. The optimum load for a transistor is given by:-

$$R_L = \sqrt{r_{22} r_{out}}$$

where  $r_{22}$  is the output impedance with the input open circuited, and  $r_{out}$  is the output impedance with the input short-circuited.

For the OC71, the value is about 12kΩ. Thus the ratio of the transformer required is:

$$\frac{3,000,000}{12,000} = 16:1$$

With transformer coupling, it is not necessary to use a high collector supply voltage, and the bias voltage may be used direct.

resistance used will depend on the degree of stabilisation required but it is usually about 1kΩ (20 to 25% of  $R_L$ ). The voltage drop across the emitter resistor can be determined from the current flowing, and the base-to-emitter voltage required to give the correct base current can be found from the transistor input curves.

The current through the base potentiometer is made an order of magnitude larger than the base current, and the voltage at the base is made equal to the emitter voltage plus the required base-to-emitter voltage. All these three methods of biasing are shown in Fig. 6.

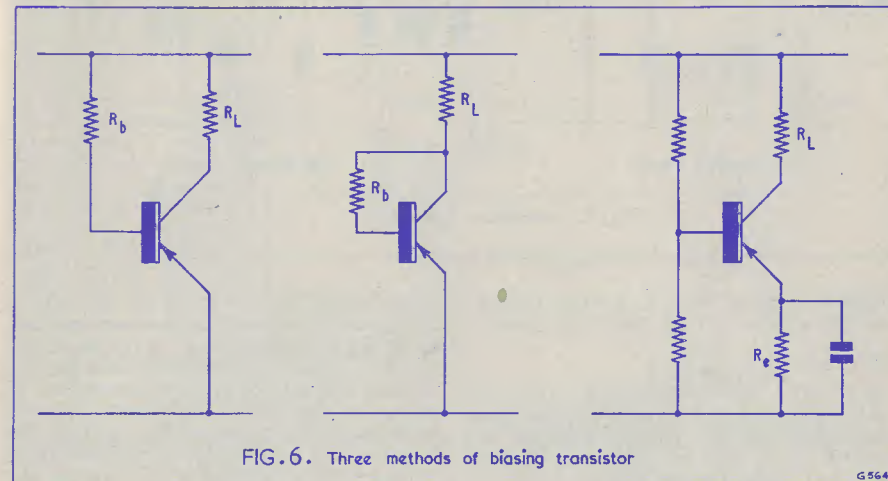


FIG. 6. Three methods of biasing transistor

G564

#### Biasing and D.C. Stabilisation

The simplest method of biasing the transistor is by means of a base resistor from the negative line. The required value is given by:

$$R_b = \frac{V}{I_b} \quad (\text{where } V \text{ is the supply voltage and } I_b \text{ the base current}).$$

This method of biasing does not safeguard against the possibility of the operating point shifting with rise in temperature, and a simple method of providing some compensation is to take the bias resistor from the collector instead of the negative line. Some gain is lost by this method, as negative feedback is applied to the transistor. The voltage at the collector (instead of the supply voltage) must be used when calculating  $R_b$  in this case.

A more successful, although more elaborate, method of stabilising the working point is to use potentiometer biasing, together with an emitter resistance. The value of emitter

#### Input Impedance

The grounded emitter circuit has a low input impedance (compared with valve circuits), normally of the order of 1 to 2kΩ. If maximum gain is to be obtained, some matching will be required; this can be done either by using a step-down transformer after the detector, or arranging that the secondary of the i.f. transformer is tapped, and is suitable for feeding a low impedance diode detector circuit.

If no base bias current is provided for the transistor, it will function as a detector, but its operation is then dependent on  $I_{c(o)}$ , and there is no straightforward method of applying d.c. stabilisation to this circuit. It is therefore preferable to use a separate diode preceding the transistor.

#### Grounded Base Circuit

Although transformer coupling is necessary when using grounded base transistors



in cascade, a single stage used as a voltage amplifier with a resistive load will give a higher voltage gain than a grounded emitter stage. The input impedance is much lower (100Ω to 200Ω) and the output impedance higher than with a grounded emitter circuit. It is less temperature dependent, and does not require d.c. stabilisation. It can be used in any of the arrangements described. There are two possible methods of biasing the emitter. Providing the base is returned to l.t.—, the l.t.+ supply can be used as a

### Microphone Pre-amplifier

The low input and high output impedances of a grounded base stage are useful when it is required to feed from a low impedance—such as a moving coil microphone—to a high impedance—such as the grid circuit of a valve. Here again the transistor supply can usually be obtained from the amplifier itself, the cathode bias voltage of the first valve providing a suitable source.

Since this is a positive source the cathode end of the bias resistor must be considered

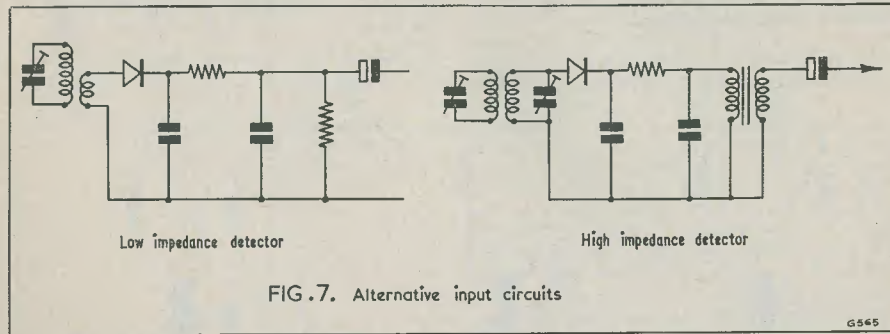


FIG. 7. Alternative input circuits

convenient source for the positive emitter bias. The value of the emitter resistor is given by  $R = \frac{V}{I_c}$ .

If  $V = 1.5V$ , and  $I_c = 0.5mA$ ,  $R = 3k\Omega$ .

The alternative method is to bias the base negatively as before, and return the emitter to earth via a resistor. The input is then applied to the emitter.

as the "earth" point as far as the transistor is concerned, the true earth line being regarded as the negative supply line. A typical circuit is shown in Fig. 9. It should be noted that the cathode bias resistor must be decoupled. If this is not possible for any reason—negative feedback being applied to the cathode, for instance—the bias voltage of another valve in the amplifier may be used as a supply. As

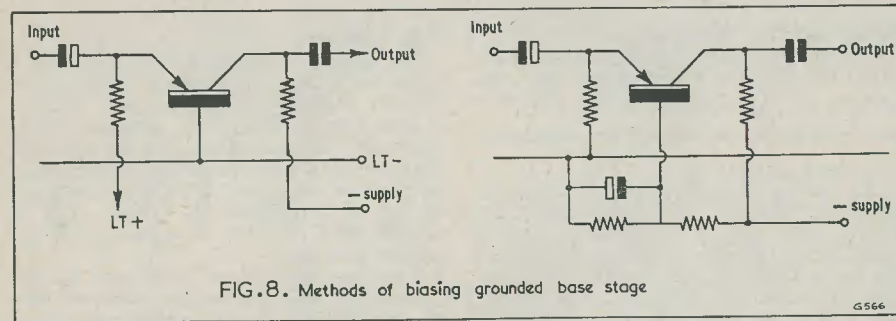


FIG. 8. Methods of biasing grounded base stage

Since the impedance looking into the transistor is much lower in this connection, it is important to match the high impedance of the detector circuit by means of a transformer. Assuming the diode circuit has an impedance of 500kΩ, a transformer ratio of at least 50:1 would be required.

before, care must be taken to ensure that the maximum voltage for the collector is not exceeded. If the bias voltage is too high, the bias resistor can be replaced by two resistors in series, and the transistor supply taken from the junction of the two. The values of the resistor must be suitably chosen to give

the correct bias for the valve, and the correct voltage for the transistor, and the junction must be decoupled.

### Coupling Capacitors

To readers familiar with valve circuits the values of coupling capacitors used with transistors may seem uncommonly high. This is due to the much lower input impedance of the transistor. The coupling capacitor and the input impedance together form a bass cut circuit. In the case of a valve with a grid resistor of 500kΩ, a capacitor of about 0.005 µF will be suitable for operation down to about 60 c/s.

To work satisfactorily down to the same frequency with a grounded emitter circuit which has an input impedance of only 1kΩ we should need a coupling capacitor of 2.5µF. With a grounded bass circuit the input impedance is even lower

(about 100Ω) and a capacitor of 25µF would be required to obtain similar low frequency response.

Since small electrolytics are normally used for these purposes, the correct polarity must be observed. In general, the positive end is connected to the "earthy" side of the circuit.

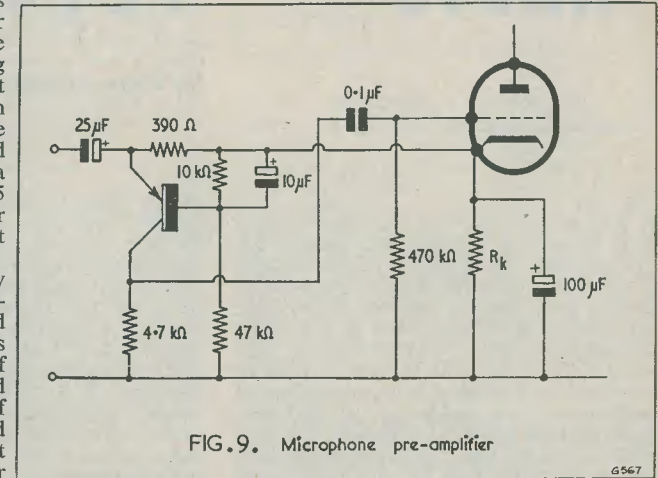


FIG. 9. Microphone pre-amplifier

## American Award for Member of English Electric Valve Co. Staff

Mr. F. Langford-Smith, B.Sc., B.E. (1st Class Honours), Senior Member I.R.E. (U.S.A.), has been named an Honorary Member of the Audio Engineering Society of the U.S.A. by the Society's Board of Governors.

Under the bye-laws of the Society, honorary membership may be presented to persons of outstanding repute and eminence in the science of audio engineering or any of its allied arts. The 1959 Awards Committee of the Society announced that Mr. Langford-Smith has been elected in recognition of the importance of his book, entitled *Radio Designer's Handbook* (Radiotron Designer's Handbook in the U.S.A. and Australia), to the education of a generation of audio engineers.

Mr. Langford-Smith, who is head of the Technical Publications Department at the English Electric Valve Company, will be visiting America during the New York Convention of the Society in October to attend the annual Awards Banquet, where A.E.S. awards are usually made.

## 1960 ELECTRICAL ENGINEERS' EXHIBITION

Yet again, a bigger-than-ever Electrical Engineers Exhibition at Earls Court is forecast for next spring (5th to 9th April).

Formal confirmations of earlier provisional space bookings indicate that around 450 manufacturers will show their products.

The large number of new exhibitors has made it necessary to increase the number of first floor stand sites and the forthcoming show will have nearly five miles of stand frontages.

The ballot for stand positions was held at Caxton Hall, London, on Wednesday, 14th October.

The "Marine Electrics" feature will occupy 5,000 square feet on the first floor. This will prove to be an extremely topical feature as the exhibition period will be near to the launching date of the largest passenger vessel to be built in the United Kingdom since the Queens. This ship, the P. & O. *Canberra*, will be the largest British passenger ship to be powered entirely by a.c. and will include much specially designed electrical equipment.

It will be propelled by 85,000 s.h.p. twin-screw turbo-electric machinery, having four turbo alternators giving an output of six megawatts.

In addition to new developments displayed within the exhibition feature, many of the exhibitors will include marine electrical equipment on their stands.



# RADIO Topics

By Commentator

## Kits

HAVING JUST COMPLETED CONSTRUCTING his second Heathkit and being about to start the third, your commentator somewhat naturally fell to reflecting what an advance the Heathkit method of assembly was over that of the days when he first began building radio gear. "Chassis bashing" was—and still is—the most tedious of occupations; and the drilling of holes, sorting out of components, and soldering in awkward places, all took a toll of the pleasure the final article eventually gave. Many attempts have been made in the past to relieve the home constructor of these monotonous tasks, but few have stood the test of time. We recall, for instance, attempts some years ago to introduce a series of chassis parts in which strips with valvholder holes were bolted to flats, ends and sides to make up the required chassis assembly. But this did not last long. Far more popular were the metalwork firms who would make up chassis to one's specific requirements. One firm, at least, has built up a permanent, successful business from this line. For the constructor who wants "one-off" a job to his own requirements, this is the answer. But for the builder of popular lines of equipment, the Heathkit system would be very difficult to improve upon. Everything from cut and drilled chassis, to all bolts, washers and nuts, components, connecting wires, solder and insulating tape—all is provided, and the constructor can go straight ahead, step by step, knowing that everything will work out correctly, that all the snags have been ironed out, and the design is such that very satisfactory performance is guaranteed when the job is completed.

## Amateur Bands

The International Telecommunications Union Conference at Geneva will, no doubt, produce some changes in the amateur transmitting band allocations. Most of the major amateur radio organisations are taking steps to see that their facilities are well represented

in the right quarters. Some of the most drastic suggestions for cutting these which we have read to date have come from the Australian Government. We were interested to note that the defence against these suggestions put up on behalf of the Australian amateur organisations made great play of the part Amateur Radio has taken in providing emergency radio communications in natural disasters. It is only recently that British amateur radio has organised its own "community service" of this nature. We hazard a guess, however, that this aspect of amateur radio will carry more weight than any other in the eyes of the "powers-that-be," when the final decisions regarding the future of amateur radio allocations are drafted.

## National Radio Show

Another National Radio Show has come and gone. Your commentator is one of those who finds the exhibits on the first floor of considerably more interest than those on the ground floor. The guided missiles and their associated equipment, and the delightful model of one of the new County Class guided missile naval vessels, provided exhibits of great interest. One hopes for still more of this type of display in future shows.

## Noise

The Noise Abatement Society is unfortunately a most necessary addition to the organisations endeavouring to make our civilisation tolerable for human beings to live in. This summer's weather has made the nuisance of the over-loud outdoor portable radio a matter which this new Society might well pay some attention to—after it has dealt with motor-bikes as a priority job. Like so many evils of civilisation, noise is primarily a matter of thoughtlessness on the part of its creator. Publicity about the evils of noise and communal education against it should help very materially in bringing about a great reduction in its general level.

## QSL's

It was surprising to read in a recent RSGB *Bulletin* that over a million QSL cards are handled by the Society QSL Bureau each year. An old-timer like your commentator has long ceased to get much of a thrill from the packet of QSL's on the doormat, but his memory is sufficiently good to vividly recall the days when he did handle QSL's with a reverence more fitting to some token of religious significance. Still, even now, those cards which strike a new style or have a photo of their originator or his QTH or gear on them do give pleasure and add interest to his hobby. It is a pity more folk do not use QSL cards with photographs on. The Americans, perhaps, give a lead to this with many of their cards, as the practice seems more widely spread there than elsewhere. In so doing, the recipient of the card is better able to get to know the chap he has been in contact with than is the case when he gets nothing more than a plain printed card. The Iron Curtain countries have been quick to realise the value of the pictorial QSL card. Almost without exception, their QSL cards show some features of their QTH's. So the next time you get some new cards done, see if you cannot run to a pictorial one.

## World Radio

From a review of a UNESCO publication—*Broadcasting Without Barriers*—one learns that more than 9,000 radio broadcasting transmitters and 335 million receivers bring information and entertainment to the world's peoples. However, the distribution of all this

We regret that, owing to continued ill-health, Centre Tap has had to give up, temporarily, the writing of his popular feature "Radio Miscellany." Centre Tap has been a regular contributor to our columns from our first issue, and we are sure readers will join with us in wishing him a speedy recovery to full health.

"mass communication" is apparently very uneven. Nearly sixty per cent of the world's population are without adequate radio broadcast services. Sixty per cent of the world's radio transmitters and eighty per cent of its receivers are concentrated in North America and Europe. Asia and Africa are the most under-developed continents in this respect. It is estimated that an additional 350 million receivers would be needed to assure a set for each family. So it looks as though there should be a good market for "steam" radio for many a long day yet!

## Your Show

By the time this is being read, the RSGB International Radio Hobbies Exhibition will be in the offing. It is to be held at the Royal Horticultural Society's Old Hall, Vincent Square, London, S.W.1, from 25th–28th November. This is the radio constructors' show, and a visit to it by all who can get to it is very well worth while. So we'll hope to see you there, on Stand 24.

## A New Series of Mullard Filmstrips

For the student electronics engineer

The Mullard Educational Service has announced the introduction of a new series of filmstrips designed to assist the teaching of electronic engineering in technical colleges, services training establishments, industrial apprenticeship courses, and so on.

The first of the series—"Thermionic Oscillators"—is available now from the distributors, Unicorn Head Visual Aids Ltd., 42 Westminster Palace Gardens, London, S.W.1, price 25s. a copy, including comprehensive teaching notes. The second, which deals with non-sinusoidal oscillators, is in preparation, and will be followed by others covering the subjects of modulation and transmission.

"Thermionic Oscillators" comprises 27

colour frames, arranged in two parts, with the break occurring at a convenient point in the development of the subject.

Part One starts with an explanation of the basic principles of electronic oscillation, using the mechanical analogy of the loaded spring. Some revision of a.c. theory and resonance is then given, and finally the operation of various forms of simple electronic oscillators—the Meissner, Hartley and Colpitts circuits—is examined in detail.

The subject is resumed in Part Two with explanations of Miller-effect, electron-coupled and crystal-controlled oscillators, and the strip concludes with an examination of a typical practical circuit comprising oscillator, buffer amplifier and output amplifier.



# Getting Started on RTTY

by Arthur C. Gee, G2UK

Hon. Sec., British Amateur Radio Teletype Group

REGULAR READERS OF THIS PERIODICAL will know that in February, March and April last there was published a series of three articles on amateur radio teletype from the well-known exponent of this subject, James T. Hepburn, VE7KX, of Richmond, B.C.

These articles produced sufficient interest to warrant the inauguration of a Group specifically devoted to furthering the cause of RTTY in the British Isles. Within a matter of weeks the Group had a membership of fifty, had acquired a number of teleprinters, built receiving FSK converters and at the time of writing is just about ready to start the first "G" RTTY QSO's.

Some twenty-five or so teleprinters have been issued to BARTG members and it is hoped that further supplies will become available, but the author was surprised to learn from correspondence with members in the early days of the Group that quite a number of people had already acquired printers from one source or another. Some had even been "RTTY listeners" for a number of years. Quite obviously, there was a nucleus of interest in this subject which needed drawing together. Also, technical data was badly wanted. Various scraps of information had been gleaned by various members as a result of personal experience, service training and so on, but no detailed account of "amateur radio RTTY" was available. So a series of News Sheets was issued giving the essential data. These of necessity had to be brief. Thanks to the kindness of our editor, who has made space in this journal available, we hope in this series of articles to enlarge on this subject and make the information the Group has acquired available to a wider readership.

First of all, just what is "RTTY"? Telegraphic equipment which would "write" down the message being sent can be traced right back to the beginnings of electrical

telegraphy. Samuel Morse's original invention used a pen, moved by the electrical impulses, to record his code on a moving paper tape. Many subsequent efforts were made to develop an electrical instrument which would record the messages in letter form, but they were unsuccessful until a Frenchman named Baudot realised that the main difficulty was that codes such as Morse's gave such differing lengths of signal for the various letters. "J" for instance is thirteen times as long as "E" when sent by morse code. Baudot introduced a code in which all the characters are of the same length, but are made up of differing groupings of impulses. It then became possible to develop electromechanical means for recording the messages in actual printed form.

The signalling code used in teleprinters met with in this part of the world—known as "International Telegraph Alphabet No. 2"—consists of a group of five impulses. Each set of five impulses occupies the same time interval; the various letters, figures and other intelligence being conveyed by various permutations of these five impulses.

Each five-impulse signal permutation is preceded by a "start" impulse, which releases the receiving printer mechanism. After each five-impulse sequence, a further "stop" impulse is sent which stops the printing mechanism.

This type of teleprinter operation is known as the "start-stop" system, i.e. the receiving mechanism is at rest until a signal is received. After the signal has actuated the receiving printing mechanism, the latter stops until another signal is received. There are other types of teleprinter systems in which the receiving mechanism rotates continuously, printing on the reception of impulses from a transmitting mechanism rotating in step with it. These systems are called synchronous systems. The advantage of the "start-stop" system is that the receiving mechanism and

the transmitting mechanism do not get out of step with each other, as is liable to happen in the synchronous systems. The latter need very accurate speed control and suffer from the disadvantage that any slight inaccuracy in this respect is cumulative.

m/secs. The code impulses are also of 20.41 m/secs. duration. These times are those used in the English standard, which is used over much of Europe and a very large number of world-wide circuits. The American system uses different timing for the impulses, viz.,

		Start	Code Elements	Stop			Start	Code Elements	Stop
		0	1 2 3 4 5	●			0	1 2 3 4 5	●
A		●	● ● ● ●	●	P	0	○	● ● ● ●	●
B	?	●	○ ● ● ●	●	Q	1	○	● ● ● ●	●
C	:	○	● ● ● ●	●	R	4	○	○ ● ● ●	●
D	who are	●	○ ● ● ●	●	S	9	○	○ ● ● ●	●
E	you	●	○ ● ● ●	●	T	5	○	○ ● ● ●	●
F	3	○	○ ● ● ●	●	U	7	○	○ ● ● ●	●
G	Optional	○	○ ● ● ●	●	V	=	○	○ ● ● ●	●
H	characters	○	○ ● ● ●	●	W	2	○	○ ● ● ●	●
I		○	○ ● ● ●	●	X	/	○	○ ● ● ●	●
J	Bell	○	○ ● ● ●	●	Y	6	○	○ ● ● ●	●
K	(	○	○ ● ● ●	●	Z	+	○	○ ● ● ●	●
L	)	○	○ ● ● ●	●	Carriage return		○	○ ● ● ●	●
M	.	○	○ ● ● ●	●	Figures		○	○ ● ● ●	●
N	9	○	○ ● ● ●	●	Letters		○	○ ● ● ●	●
O	9	○	○ ● ● ●	●	Line feed		○	○ ● ● ●	●
					Space		○	○ ● ● ●	●

Fig.1

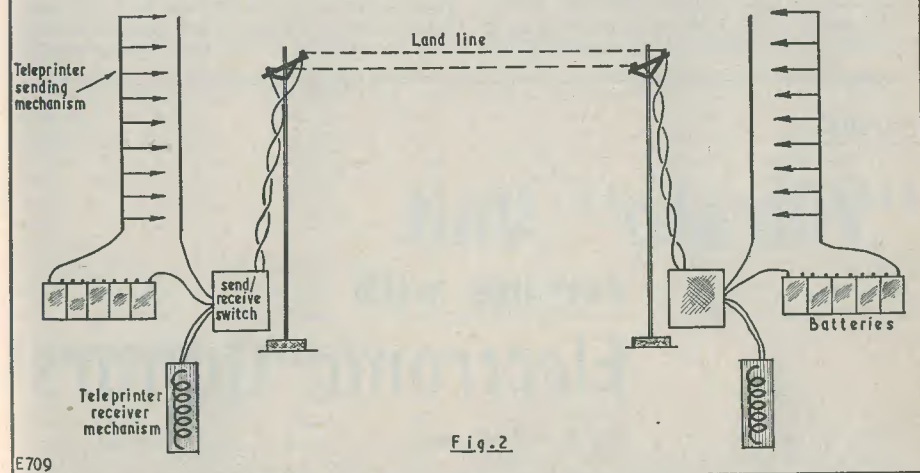


Fig.2

The teleprinter impulse code is shown in Fig. 1. Each impulse lasts for a definite, but very short space of time. For instance, the start impulse lasts for only 20.41 milliseconds. The stop impulse lasts for 30.61

22 m/sec. for start and code elements and 31 m/sec. for the stop impulse. We shall discuss this difference later on in this series of articles.

So much for general principles. How are



the machines connected up in practice? In the simplest circuit, the machines can be connected as shown in Fig. 2. Here we have the transmitting mechanism which is worked by the teleprinter keyboard contacts, in series with the receiving mechanism of a second teleprinter at a distant point. Normal telegraph land lines convey the impulses from one to the other. Now we could easily use a radio circuit in place of the land lines and this is, of course, what is done in a radio teletype circuit. The system would work if we used a simple make and break radio circuit, similar to c.w. morse code transmission, but using the teleprinter code instead of morse code. This was actually done in the early days of amateur radio teletype, but a number of snags very soon showed up in this mode of operation. It was soon superseded by the "FSK" or frequency shift keying system of radio communication. With this system, a continuous carrier is radiated by the transmitter but it is shifted in frequency slightly by the impulses from the teleprinter transmitting mechanism. Thus the radio signal varies in frequency in keeping with the impulses of each code sequence. At the receiving end, the received radio signal is made to beat with the beat frequency oscillator on the receiver, in the same way as is done for a c.w. signal, but instead of a make-and-break audio tone being produced, a two-tone audio signal is produced, the two tones being the amount of the frequency shift used at the transmitter. The two tones reproduce the impulses sent by the teleprinter. These two tones are fed into a tuned audio circuit which discriminates each tone and feeds it into an electromagnet which

in turn keys the receiving mechanism on the receiving teleprinter. The amount of shift used in amateur transmissions—and in many commercial ones as well—is 850 cycles per second. At the receiving end the two tones produced are adjusted so that one is of 2975 c/s and the other 2,125 c/s.

It would, of course, be possible to send the two audio tones over a radio carrier as an ordinary modulated signal, as one does with normal phone transmission. This system is used and is known as AFSK—audio frequency shift keying. It is not so reliable as f.s.k., being more susceptible to fading, atmospherics, and so on, but it is used on v.h.f. circuits, particularly in amateur practice. It can be used with a.m., n.b.f.m. or f.m., and will be dealt with later on in this series of articles. For the moment we will confine our attention to f.s.k., as this is the mode used on the normal short wave circuits.


It will be apparent, by now, that two additional units are needed to enable the normal amateur transmitting station to be used for RTTY. First of all a unit is required which will shift the frequency of the transmitter 850 c/s. Then we need a unit for attachment to the receiver to convert the two tones produced by the shift back again into electrical impulses sufficiently powerful to operate the receiving mechanism on the teleprinter. The first unit is applied to the oscillator section of the transmitter. We shall describe units for doing this in the course of these articles. The construction of the receiver converter will be dealt with in a near future article. Next month we shall deal with the heart of RTTY, the teleprinter itself.

volume control. To the suppressor grid of the same valve is fed the output from the EF91 "vibrato" oscillator (via the pre-set control RV<sub>1</sub>). These two signals are mixed and as a result the signal from the pick-up is modulated in amplitude at a frequency of about 3 c/s, giving the well-known "vibrato" effect.

to the main amplifier there should be heard the low frequency note of the oscillator. This will be heard as a low "thumping" sound in the speaker.

If the guitar strings are plucked then the note will be heard, suitably modulated by the oscillator.

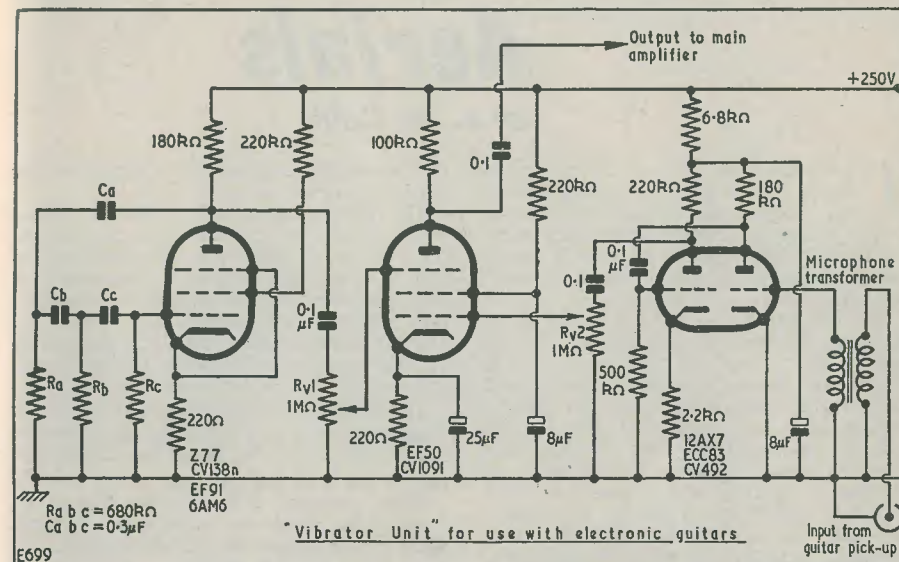By adjusting the two controls RV<sub>1</sub> and



The output from the EF50 is then fed to the main amplifier in the usual manner, but the level is such that a high gain input is not needed.

The circuit is quite usual and no comment is needed except perhaps regarding the oscillator, which is a quite conventional phase-shift oscillator. The main components are C<sub>a</sub> C<sub>b</sub> C<sub>c</sub> and R<sub>a</sub> R<sub>b</sub> R<sub>c</sub>, and these components decide the frequency of the oscillator. It will be noted that the three resistors are the same value, also the three capacitors.

When setting up, the oscillator should be tested first. With the input from the mixer

RV<sub>2</sub> it will be found that there is an optimum position for best results, but always start with the controls at maximum to ensure that the system is working correctly.

After setting up the unit it will be found that it will be desirable to be able to switch the oscillator on and off. This is best done by inserting a normal jack in series with the cathode resistor (220) and feeding this to a foot-operated switch, so that when the switch is not operated, it is open circuit; a normal bell-push might be suitable.

In the actual construction there is nothing special to observe that one would not normally note in audio practice.

## Literature Received

We have received from Daystrom Ltd., manufacturers of the excellent and well known Heathkits in this country, a copy of their two-colour, 12-page brochure. This publication, which is free on request, fully lists the current range of home constructor kits available to the public at the present time. The address is Daystrom Ltd., Gloucester, Glos.

From the Principal of the Weston-super-Mare Technical College we have received a 20-page booklet giving full and complete details of both full- and part-time courses for the session 1959-60. Among the long list of courses we note the following: Electrical Installations, Radio and Telecommunications, Radio Servicing, Television Servicing and the Radio Amateur's City and Guilds Course.

## AUDIO

# "Vibrato" Unit for use with Electronic Guitars

By E. W. Bones

ORIGINALLY DESIGNED TO BE ADDED TO AN electronic guitar amplifier, this unit has proved very simple to adjust and operate, and has fully justified the small amount of time and money needed to build the instrument.

Basically the unit consists of a vibrato oscillator and a mixer valve, and a pre-amplifier.

The output from the pick-up is amplified by the 12AX7 stage and then fed to the control grid of the EF50 via RV<sub>2</sub>, the pre-set



# V.H.F.

## Aerials

By A. W. Collis

THE FUNDAMENTAL PRINCIPLES OF AERIAL design are the same for all frequencies; but certain aspects of v.h.f. work require changes in these designs when working above 50 Mc/s. The importance of a good aerial cannot be over-emphasised in v.h.f. technique.

The simplest form of v.h.f. aerial is the familiar adornment of roof tops and chimney stacks, the centre-fed half-wave dipole (Fig. 1 (a)). From the diagram it can be seen that at the ends of the rods the induced voltage is a maximum and the induced current a minimum. In theory it would seem that the centre impedance (resistivity to an alternating current and voltage) is zero, whilst the ends represent infinity. In practice, however, the centre impedance is around 75 ohms, increasing to several thousands at its ends.

As the centre represents the lowest impedance load it is common practice to connect the transmission line there, as shown, the transmission line having the same impedance as the point of connection.

By splitting the common form of half-wave dipole into two or more parallel elements (in the same plane) with the connecting line attached to the centre of one of them, it is possible to match various line impedances. The pick-up of this dipole is equivalent to that of an ordinary single dipole, but as the current is now spread over several elements, each element will take only part of the current previously carried, which results in increased input impedance. This increase in impedance depends not only on the number of conductors in the folded dipole but also their diameters, as the latter affects the current distribution and therefore the input impedance. The most common form of folded dipole is the 2-element variety with conductors of the same diameter. When used just as a simple dipole and not part of a directive array its input impedance is near enough 300 ohms to make a good match to a 300 ohm twin lead.

The length and diameter of the dipole elements are also very important as it is the

ratio of length/diameter that determines the bandwidth of the aerial.

The polar diagram of a vertical dipole, Fig. 1 (b), shows that the signal response is the same in all directions. To increase the gain of such a dipole aerial it is necessary to add "parasitic elements" known as reflectors and directors. Although these have no electrical connection to the dipole they serve to step up the effectiveness of the aerial system over that of the dipole alone.

The step up in power or gain is measured in decibels (dB) e.g. if  $P_b$  and  $P_a$  are the power inputs before and after aerial conversion, the gain in dB is  $10 \log_{10} P_a/P_b$ .


These parasitic elements when placed in front of the dipole are called directors, and when placed behind are called reflectors.

From the graph in Fig. 2 (a) it can be seen that on adding a director and reflector the greatest gain takes place when they are spaced at about  $0.125\lambda$  and  $0.15\lambda$  respectively.


The simplest form of directional aerial is the well known "H" type whose polar diagram is shown in Fig. 2 (b). This system gives a useful gain over the dipole and also gives the aerial a "blind spot," thus minimising interference from that direction. The length of the reflector should be just long enough to ensure that the reflected signal is in phase with that of the dipole, so as to add to the signal and not to oppose it.

The length for a reflector in feet is approx.  $498/f$  (Mc/s) and that of the director approx.  $450/f$  (Mc/s).

On adding these parasitic elements, it can be seen from the graph Fig. 3 (a) that the impedance of the system will alter. It is then necessary to match the new impedance of the aerial to that of the line, to ensure maximum transference of signal voltage. This may be done by using a transformer, as the square of the turns ratio is the impedance ratio. Also, the line will have to be matched to the input impedance of the receiver. Two simple ways of doing this are Fig. 3 (b) and (c); Fig. 3 (b) being the coil coupling method and Fig. 3 (c) the tapped coil method.

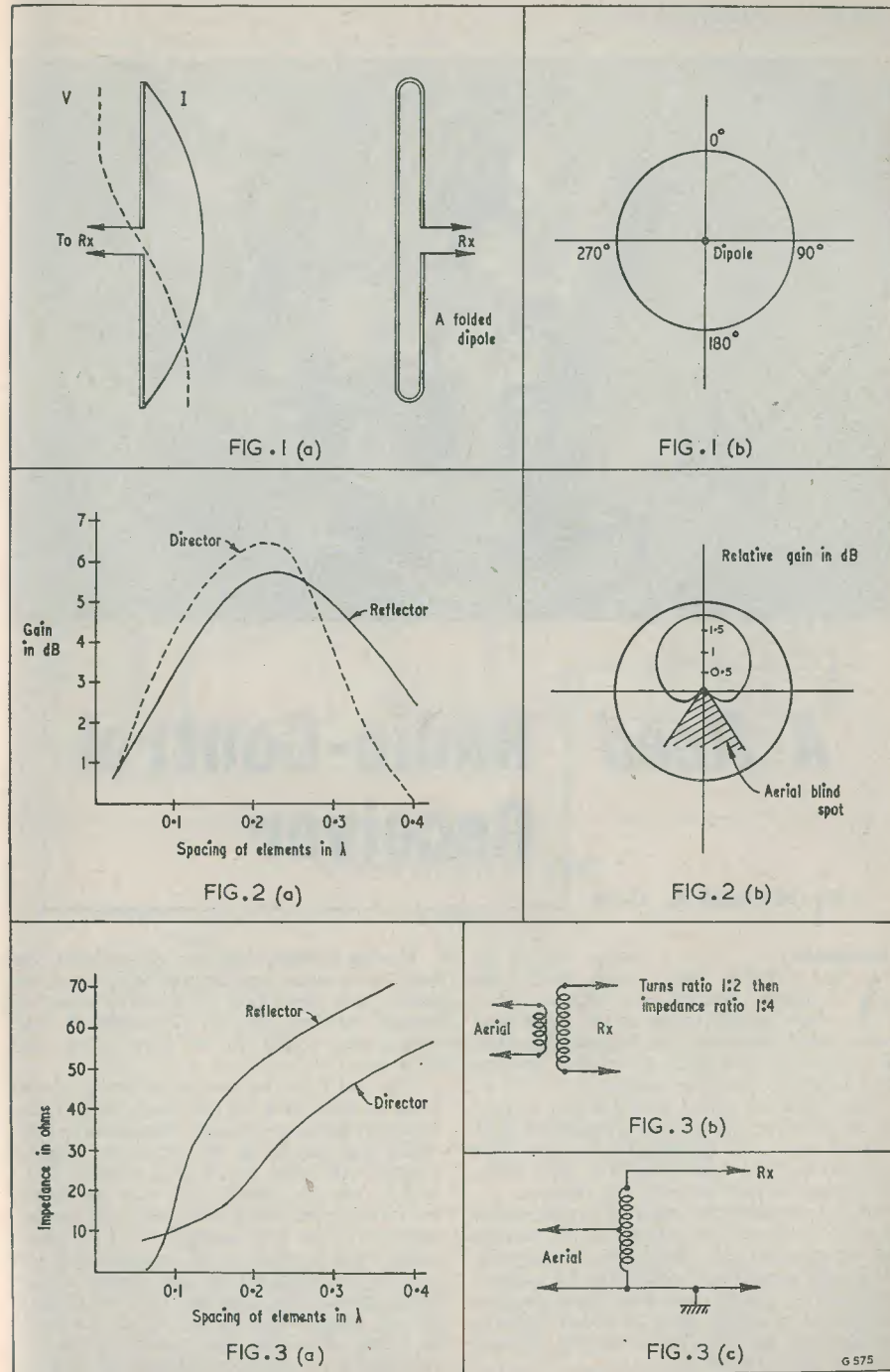



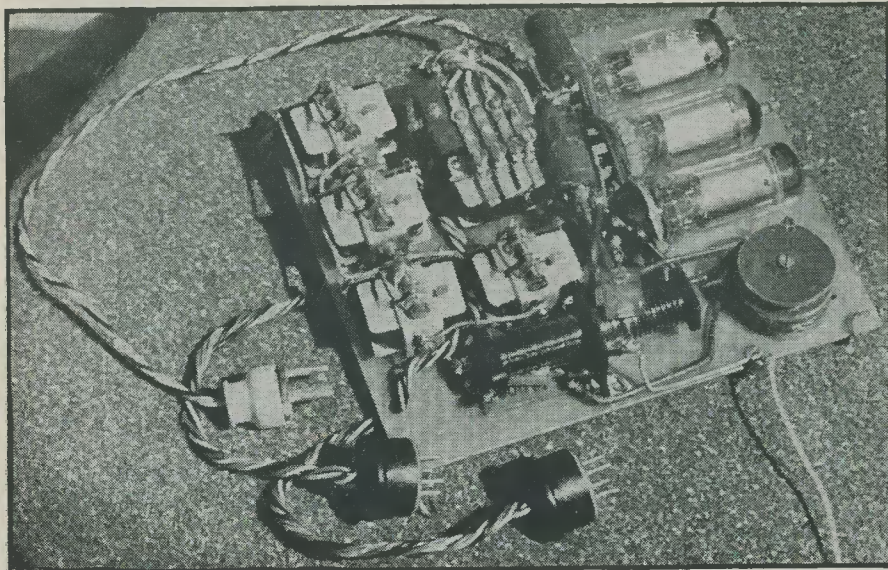

# A Reed Radio-Control Receiver

By Michael A. Cole

## Description

AFTER HAVING SPENT SOME TIME CONSTRUCTING Mark/Space Ratio gear, which tended to be rather bulky and considerably intricate, the receiver described in this article was built to combat the size and weight of the other system.

The receiver was constructed around three 3S4 type valves and a standard E.D. 3-reed unit. A home-built carrier wave transmitter was converted to give audio modulated output to work the receiver.

It was desirable that the receiver should be reasonably small and easy to get at, because of the number of adjustable components. With the intention of installing the receiver in a boat, a fourth reed was added to give: Starboard Rudder, Port Rudder, moving 10-position selector, and bringing selected control into operation.

Having thought this over, the receiver was based on a super regenerative detector circuit which was described in *Radio Control of Model Aircraft*, by G. Sommerhoff, and which was found to be very stable and reliable.


The coil  $L_2$  is the tuning coil and is placed back to back with the sensitivity coil  $L_1$ , the windings being in opposite directions to each other and placed on  $\frac{3}{8}$ in diameter Aladdin formers cut down to  $\frac{1}{2}$ in long. The coils  $L_3$  and  $L_4$  are the quench coils and are wound on formers  $\frac{1}{2}$ in inside diameter,  $1\frac{1}{2}$ in outside diameter, and  $\frac{1}{4}$ in between the two inside faces, with a total of  $\frac{1}{2}$ in between the two sets of windings which are wound in the same sense. The relay position is taken up by the resistor  $R_1$ , across which the audio is taken off. The three valveholders are mounted on aluminium brackets, all in a line

and the contact wires from the relays are taken to two B7G valveholder plugs so that the set is easily removable from the model.

The audio signal is then passed through a two-valve resistance-capacity coupled audio amplifier to the reed unit, which is placed in the anode of the last valve. Audio variations

so much smoothing is needed. The circuit can be used for any of the reed units on the market at the time of writing.

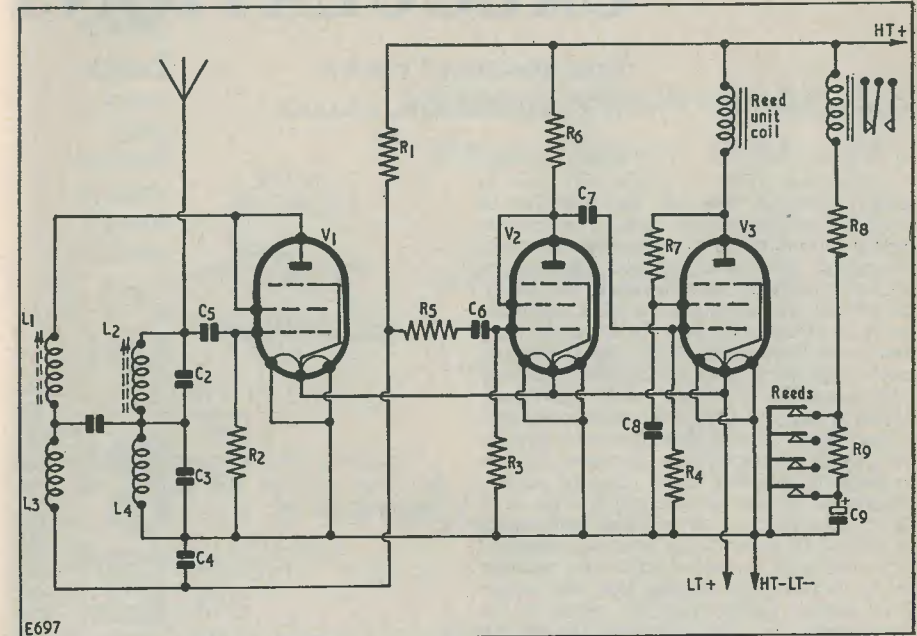In operation, on receiving the unmodulated carrier wave signal the 0-6mA meter in the h.t. line should drop from about 3.5mA to 1mA approximately, but rise to about



## COMPONENTS LIST

### Capacitors

- C<sub>1</sub> 500pF
- C<sub>2</sub>, C<sub>5</sub> 100pF
- C<sub>3</sub> 1,000pF
- C<sub>4</sub> 5,000pF
- C<sub>6</sub>, C<sub>7</sub>, C<sub>8</sub> 0.01μF
- C<sub>9</sub> 3μF Picopack elect

### Resistors

- R<sub>1</sub> 4.7kΩ
  - R<sub>2</sub>, R<sub>3</sub>, R<sub>4</sub>, R<sub>7</sub> 1MΩ
  - R<sub>5</sub>, R<sub>6</sub> 470kΩ
  - R<sub>8</sub> 5.6kΩ
  - R<sub>9</sub> 100Ω
- Note.—Repeat R<sub>8</sub>, R<sub>9</sub>, C<sub>9</sub> and relay for each reed.

### Coils

- L<sub>1</sub> 12 turns 24 s.w.g.
- L<sub>2</sub> 5 turns 24 s.w.g.
- L<sub>3</sub> 350 turns 38 s.w.g.
- L<sub>4</sub> 650 turns 38 s.w.g.

set up in the coil vibrate the particular chosen reed, which makes an interrupted contact to the relay. The interruptions are smoothed out by R<sub>9</sub>, C<sub>9</sub> and finally by R<sub>8</sub> so that the relay pulls in when the chosen reed is set in motion. If less sensitive relays are used, not

4.5-5mA on applying the audio signal.

If on a range check the receiver appears to be getting out of range, i.e. the current drop getting less when applying a c.w. signal, the sensitivity coil  $L_1$  should be adjusted for greater current drop.



# TUNING COIL CALCULATIONS

*Some one-armed combat*

**Conclusion**

W. E. THOMPSON, A.M.I.P.R.E.

Multi-layer coils are dealt with just as easily, although they are less likely to be needed than single-layer coils. The formula which follows refers to a winding with turns touching. The usual method adopted by manufacturers is wave-winding for multi-layer coils, which reduces the self-capacitance to some extent and raises the Q value. Very few home constructors will be able to produce such coils, so it is to be expected that any coil produced at home with pile-wound layers is likely to have a fair amount of self-capacitance. It will therefore tend to tune to a lower frequency than calculated, but the remedy of removing some turns to achieve resonance at the required frequency is a fairly obvious step. Nevertheless the formula is sufficiently accurate for practical purposes, but obviously it cannot take into account slight variations in winding that may occur. The referee having said his piece to the contestants, we will commence the second bout and tackle the bigger chap.

**Big Brother, or 1984 μH and Beyond**

As we shall see, things have not altered a great deal. We use the same technique, but a little more of it. Referring again to the original formula

$$L = \frac{0.2N^2D^2}{3.5D+8S} \times \left(\frac{D-2.25d}{D}\right)$$

it will be remembered that the term in brackets is the correcting factor for a multi-layer coil. Looking at what lies ahead, it will save some mental gymnastics if we represent this term by the symbol "k"; it will permit easier working in rearranging the formula, and we can revert to the full term when it is convenient for us to do so.

Assume that battle has commenced, and that we have by now reached the stage of initial struggling in Hold No. 2. Going through the motions once more, we apply

**Hold No. 3—Hari-kiri**

$$L = \frac{0.2N^2D^2k}{3.5D+8S}$$

$$\begin{aligned} &= \frac{N^2D^2k}{17.5D+40S} \\ &= \frac{N^2D^2k}{17.5(D+2.28S)} \\ N^2 &= \frac{17.5L(D+2.28S)}{D^2k} \\ N &= \frac{\sqrt{17.5} \sqrt{L} \sqrt{(D+2.28S)}}{D\sqrt{k}} \dots (4) \end{aligned}$$

Comparing this with equation (3), it is seen that here also we can replace  $\sqrt{L}$  with expression (1), so

$$\begin{aligned} N &= \frac{4.18 \left(\frac{159}{f\sqrt{C}}\right) \sqrt{(D+2.28S)}}{D\sqrt{k}} \\ &= \frac{665\sqrt{(D+2.28S)}}{fD\sqrt{C}\sqrt{k}} \\ &= \sqrt{\frac{665^2 \left(1+2.28\frac{S}{D}\right)}{f^2CDk}} \dots \dots (5) \end{aligned}$$

Taking a final look round, we see there is  $D \times k$  in the denominator, so we can expand this to:

$$\begin{aligned} Dk &= D \left(\frac{D-2.25d}{D}\right) \\ &= (D-2.25d) \dots \dots (6) \end{aligned}$$

Inserting this expression in (5), we secure the submission hold:

$$N = \sqrt{\frac{665^2 \left(1+2.28\frac{S}{D}\right)}{f^2C(D-2.25d)}} \dots \dots (7)$$

It is interesting to review our handiwork. The equation (7) can be compared with (3), when it will be noticed that  $(D-2.25d)$  in the denominator of (7) takes the place of  $D$  in



Radio Society of Great Britain

**Royal Horticultural Old Hall  
Vincent Square London SW1**

Wednesday to Saturday  
**NOVEMBER 25th to 28th**

11 a.m. to 9 p.m. Admission 2/-

INTERNATIONAL

radio hobbies exhibition

CQ CQ CQ

**HOME CONSTRUCTION  
DO-IT-YOURSELF FEATURES**  
Kits of Parts to BUILD...  
*Receivers, Transmitters, Televisors,  
Hi-Fi Amplifiers, Test Gear, Tape Recorders,  
and Transistor Equipment*

**FEATURE OF WORLDS  
COMMUNICATIONS RECEIVERS**

Six Technical Book Stands  
Live Radio Station. Home Television Station  
Army, Navy and Royal Air Force Displays

**WIN A WORLD FAMOUS £110  
EDDYSTONE 888A  
COMMUNICATIONS RECEIVER**  
*See this month's enclosed entry card*

Further details from P. A. Thorogood G4KD  
35 Gibbs Green Edgware Middlesex



(3) and that but for this difference, the two equations are similar. The virtue of reducing  $\left(\frac{D-2.25d}{D}\right)$  to "k" for manipulation purposes is clearly seen. Not at all unlike a form of ju-jutsu, which is essentially knowing what holds to apply and when to use them.

The use of formula (7) can be demonstrated with a simple example.

#### Example 2

It is required to wind a coil  $\frac{1}{2}$  in long on a  $\frac{1}{2}$  in diameter former, the height of the winding to be 1/10 in. The coil is to tune to 200 kc/s with 250pF. (Note here that 200 kc/s is 0.2 Mc/s). First of all convert the fractions to decimals: length of coil  $S=0.5$  in; depth of coil  $d=0.1$  in; outer diameter (i.e. inner diam. + twice  $d$ ) is  $D=0.7$  in. Insert the known values in equation (7) and we have:

$$N = \sqrt{\frac{665^2(1+2.28\left(\frac{0.5}{0.7}\right))}{0.22 \times 250(0.7-2.25 \times 0.1)}}$$

$$= \sqrt{\frac{665^2 \times 2.63}{0.04 \times 250 \times 0.475}}$$

$$= \sqrt{\frac{665^2 \times 2.63}{4.75}}$$

$$= 495 \text{ turns.}$$

Using the necessary formula, the inductance of this coil is about  $2,530 \mu\text{H}$ . As a matter of interest, it is found to agree very closely with data evolved from the charts and formulae given in Langford-Smith's *Radio Designer's Handbook*.\*

It now remains to choose the size of wire. The winding is 0.5 in long and 0.1 in deep, so the cross-sectional area is 0.05 sq. in. The turns per sq. in. is thus  $495/0.05=9,900$ . Taking the square root, this gives roughly 100 turns/sq. in. Either 36 s.w.g. SSC (105 turns/in.) or 37 s.w.g. DSC (102 turns/in) would be suitable. Other data would have to be consulted if it was necessary to use the optimum wire size for maximum Q.

#### Conclusion

There is no intention of claiming that a new method of calculating coil winding details has been evolved in this article. The writer's sole object has been to show the steps in developing an idea, and to present his findings in a way that he hopes makes a bit of maths a little easier (and maybe slightly amusing) to read.

\* *Radio Designer's Handbook*. F. Langford-Smith B.Sc., B.E. (1st Class Honours), Senior Member I.R.E., (U.S.A.), A.M.I.E. (Aust.). Iliffe & Sons Ltd.

## MEMO TO WIVES AND MOTHERS by J. E. KITCHIN

(Also, if applicable, to sisters and brothers and any other relative who thinks amateur radio men are "a queer lot.")

Does "he" give you the "willies" with his fiddling around with his gear? Does he never get the contraption working to his satisfaction? Does he wake you up at 2 a.m. to the hilarious shout of "I've got Bongo-Bongo in south-west Africa!"?

If so, you needn't take any pills or potions, or even give him any. Just leave him alone, occasionally say "Oh, that's good," and go back to sleep. To help you out, here are a few rules which will, it is hoped, ease the strain of being a wife, mother, guardian, or what have you, of a radio enthusiast.

1. Don't keep asking when "it" is going to be finished unless he mentions the subject first.

2. Don't even ask if it is ever going to be finished—it might never be! (That's part of the fun. In case you haven't already found out, nothing was ever made to the complete satisfaction of a radio man.)

3. Don't object to the hobby too strenuously; at least you know where he is at night.

4. If you like his company and the gear is in the cellar, why not suggest a small set upstairs? Lots of radio men have transmitters and receivers in boxes no larger than your sewing basket—and they make good "conversation pieces" too.

5. Don't ever suggest that he spends so much time with his gear that he hasn't the time to fix the fence, toaster, vacuum cleaner, washing machine, paint the room, mow the lawn, or take you out. Simply say off-handedly, "Now that reception conditions aren't too good, why not fix the fence to give you something to do?" (You can't possibly get caught in a jam with this one because reception conditions are always bad on some frequency or other).

6. Puzzled over what to give him for Christmas, birthday, or an anniversary, or a present for no good reason at all? Just look casually at some of his catalogues and say: "That's a nice (substitute neat, queer, odd, awful—as required) looking thing, what does it do?" You'll get your answer! (Caution! Look at the price first and if it is a foreign catalogue mentally add enough to cover import duty and shipping charges.)

7. Show this last suggestion to HIM. Why don't you fix the blinking fence or whatever it is? You've got lots of time and you can finish that wiring job tomorrow—it will give you something to look forward to, and remember that Amateur Radio is a hobby.

Good luck to you both!

Any 1, 2 or 3 books sent on 7 DAYS' FREE APPROVAL

FOR ENGINEER or AMATEUR - 3 NEW up-to-date, essential handbooks

Gordon J. King, Assoc. Brit. I.R.E., M.I.P.R.E., M.T.S., who is the author of all three of these thoroughly practical handbooks, is an experienced radio engineer, well known to amateurs and service engineers for his contributions to the technical press.

### TV SERVICING

Practical handbook of servicing and repair methods intended mainly for the service engineer, but will also prove invaluable to radio amateurs, students and apprentices. To give immediate assistance to the busy man are the Procedure Charts, which show at a glance all likely fault symptoms, possible causes, etc. Comprehensive survey of aerials and feeders. Beautifully bound in grey buckram, cash price 30/-.

- How to deduce from any fault symptom the most likely cause of trouble.
- How to locate the circuit section or component concerned and what action to take.
- Methods of converting single-channel receivers to Band III operation.

280 PAGES  
174 ILLUSTRATIONS

### FM SERVICING

A straightforward, non-mathematical, fully comprehensive coverage of both the theoretical and practical aspects of servicing, adjustment and construction of FM equipment. Invaluable to service engineers, amateur enthusiasts and radio students. Circuit arrangements are covered stage by stage. Many examples from current receivers are included. Beautifully bound in scarlet buckram, cash price 25/-.

- Circuit arrangements—combined AM/FM type of receiver; adaptors or tuners; audio problems.
- The alignment and servicing of FM equipment and FM-fed high-fidelity systems for domestic use.

192 PAGES  
over  
100 ILLUSTRATIONS

### PRACTICAL HI-FI

Up-to-date, practical survey of the many kinds of present-day hi-fi equipment—from disc and tape to loudspeaker. Circuits, fault-finding and servicing are fully covered together with a survey of the latest advances, including stereophonic sound. Invaluable for everyone concerned with the technicalities of hi-fi sound reproduction. Beautifully bound in scarlet buckram. Cash price 25/-.

- Pre-amplifiers and power amplifiers, loudspeakers, microphones and mixers.
- Record players, disc and tape recording.
- Stereophony.

224 PAGES  
over  
150 ILLUSTRATIONS

DO THIS NOW! Simply fill in envelope to Dept. H.J.42, People's Home Library, Basted, Sevenoaks, Kent. Offer applies U.K. and Eire only. Closes Nov. 30.

**'RADIO CONSTRUCTOR' READERS-POST FORM TODAY!**

To: Dept. H.J.42, People's Home Library (Odhams Press Ltd.), Basted, Sevenoaks, Kent. Please send me WITHOUT OBLIGATION TO PURCHASE the book(s) indicated below. Within 8 days of receipt I will either pay full cash price; or (for 2 or more books) I will send 10/- down payment and pay off balance (including credit charge of 1/- in £) at 10/- a month; or I will return unwanted book(s) in good condition, post paid.

Tick against book(s) required

TV Servicing	FM Servicing	Pract. Hi-Fi
--------------	--------------	--------------

Signature..... Age, if under 21.....  
(Persons under 21 will be sent a guarantor form)

Occupation.....  
Tick where applicable:

Cash  Terms  House owner   
Tenant in house or flat  Temporary resident

USE BLOCK LETTERS PLEASE

Name .....

Full Postal Address .....

H.J.42/NOV. 1959

Firmly affix 2d stamp in margin



**SCOTTISH INSURANCE CORPORATION LTD**



**62-63 Cheapside  
London EC2**

**TELEVISION SETS, RECEIVERS AND TRANSMITTERS**

Television Sets, Receivers and Short Wave Transmitters are expensive to acquire and you no doubt highly prize your installation. Apart from the value of your Set, you might be held responsible should injury be caused by a fault in the Set, or injury or damage by your Aerial collapsing.

A "Scottish" special policy for Television Sets, Receivers and Short Wave Transmitters provides the following cover:

- (a) Loss or damage to installation (including in the case of Television Sets the Cathode Ray Tube) by Fire, Explosion, Lightning, Theft or Accidental External Means at any private dwelling-house.
- (b) (i) Legal Liability for bodily injury to Third Parties or damage to their property arising out of the breakage or collapse of the Aerial Fittings or Mast, or through any defect in the Set. Indemnity £10,000 any one accident.
- (ii) Damage to your property or that of your landlord arising out of the breakage or collapse of the Aerial Fittings or Mast, but not exceeding £500.

The cost of Cover (a) is 5/- a year for Sets worth £50 or less, and for Sets valued at more than £50 the cost is in proportion. Cover (b) and (ii) costs only 2/6 a year if taken with Cover (a), or 5/- if taken alone.

Why not BE PRUDENT AND INSURE your installation—it is well worth while AT THE VERY LOW COST INVOLVED. If you will complete and return this form to the Corporation's Office at the above address, a proposal will be submitted for completion.

NAME (Block Letters).....  
If Lady, state Mrs. or Miss  
ADDRESS (Block Letters).....


/JB

**A REVOLUTIONARY NEW BRITISH INVENTION!**

- ★ Uses standard tapes
- ★ Plays at 7½" per. sec. or 3 other speeds
- ★ Records direct from radio or microphone

Results equal to a £50 recorder—yet only costs £13. 12s. (or £17. 11s. with special Moving Coil Microphone and 600ft. reel of tape.)

**EASY TERMS**

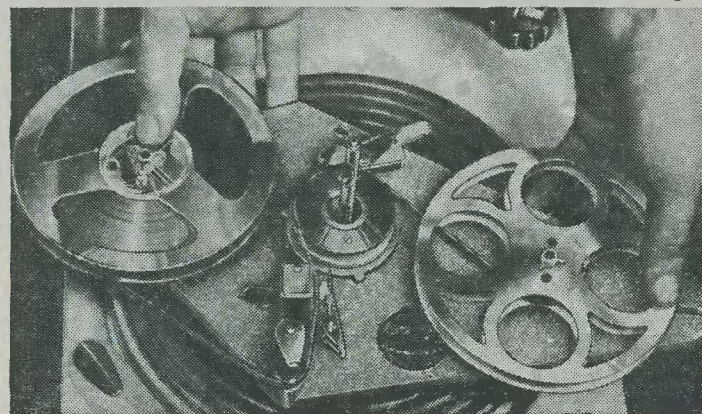

**Instantly turns any gramophone into a first-class Tape-Recorder and back into a record-player in a moment!**

Gramdeck is completely new . . . a revolutionary and ingenious invention that instantly turns your gramophone into a tape-recorder and back into a gramophone at will! Slip the Gramdeck on to your turntable and you have the finest tape-recorder you've ever heard! Lift it off . . . your gramophone is ready to play records again. There are no motors or valves to go wrong—and you get reproduction that has to be heard to be believed!

"Ingenious—simple . . . why on earth did no one think of it before!"—THE TAPE RECORDER.

"Ingenious and robust."—BRITISH SOUND RECORDING ASSOCIATION JOURNAL.

"Quality of reproduction excellent . . . real hi-fi results . . . potential is tremendous . . . both designer and manufacturer should be congratulated."—BRITISH RADIO & TV RETAILERS' REVIEW.

"Better than many so-called hi-fi recorders . . . robust . . . carefully designed . . . excellent value."—AMATEUR CINE WORLD.

Everyone is praising the Gramdeck. "The quality is at least equal to that obtained from a good microgroove disc," says a leading professional journal.

**WORKS FROM ANY RECORD PLAYER OR RADIOGRAM**

Gramdeck records and reproduces with a wonderful depth and breadth of tone. Because it uses equipment that is already in your gramophone it only costs a fraction of the high-quality tape-recorder you would normally require. Full details, specifications, photographs, easy terms, etc., are given in the Gramdeck Book. Send for your FREE copy, today.

**MADE BY THE FIRM THAT MAKES MICROWAVE WAVE-GUIDES FOR VISCOUNTS AND BRITANNIAS**

**FREE BOOK—POST NOW!**

I would like to know how to turn my gramophone into a first-class tape-recorder . . . please send me the Gramdeck Book—FREE and without obligation.  
(Write if you prefer not to cut coupon.)

NAME .....

ADDRESS .....

**GRAMDECK (Dept. RC/804)  
29 Wright's Lane Kensington London W8**

**Gramdeck**  
GRAMOPHONE TAPE RECORDER

**GRAMDECK TURNS A TURNTABLE INTO A TAPE-RECORDER**

**The Cooper-Smith, type B.P.I.  
HIGH FIDELITY AMPLIFIER  
and Mk. 2 CONTROL UNIT**

by Jack Cooper

One of our Radio Reprint series (RR6), this book of 24 pp., plus laminated plastic board cover, is a worth-while addition to the Hi-Fi enthusiast's bookcase.

In addition to the material reprinted from our December 1957, January and February 1958 issues, two new chapters have been included, these giving much useful information on Signal Sources for use with the amplifier and on Choosing a Loudspeaker.

Complete circuit and constructional details of the balanced phase inversion amplifier are given, including point-to-point diagrams.

PRICE 2/6 Postage 2d.

Published by

**DATA PUBLICATIONS LTD 57 Maida Vale • London W9**





Visit the City's new acoustically designed

# HI-FI Centre

COME AND HEAR THE LEADING MAKES IN AMPLIFIERS AND TUNERS

Amplifiers by  
VERDIK  
ARMSTRONG  
ROGERS  
DULCI

GOODSELL  
QUAD  
LEAK  
W.B., etc.

VHF Tuners by  
ARMSTRONG  
LEAK  
QUAD

ROGERS, etc.

T.S.L.  
DULCI  
GOODSELL

ROGERS, etc.

Hi-Fi Speakers by  
GOODMAN  
PLESSEY  
WHARFEDALE  
LORENZ, etc.

W.B.  
T.S.L.  
G.E.C.

**2 NEW BARGAINS FOR CONSTRUCTORS**  
The new **Cossor 6-valve FM receiver kit** comprising all components including 6 valves, Goodmans 10" x 6" speaker, printed circuit chassis, easy-to-follow instructions. Even to nuts and bolts. Manufacturer's price 15 gns. **Our price £8.19.6 complete.** P. & P. 2/6.  
**Cossor 3 watt printed circuit audio amplifier.** Main components mounted on printed circuit chassis, 3 Cossor valves, 10" x 6" speaker, 4" tweeter, and all components including easy-to-follow instructions. Cossor's price £9.15.0. **Our price complete £5.19.6.** P. & P. 3/6.

### BUILD THIS YOURSELF

The **Transette** medium wave, 2-transistor, pocket portable. Neatly designed, using 2 transistors and diode. Simple to assemble. Enlarged working diagram. All components colour coded. Ferrite wound aerial. Will play indoors and outside with self-contained aerial. All components and diagram complete, 62/6. Post and packing 1/6. Plug-in earpiece 12/6, single phone 4/6, battery 2/-. All components available separately.  
Stamped addressed envelope for details



### ANOTHER SNIP OFFER SLIGHTLY SOILED AT THE LOW PRICE 29/6

and 4/- post and packing Surplus to manufacturer's requirements, well made 2-tone colour portable player cabinets; will take non-auto player. Amplifier and 4" or 5" speaker.

**STOP PRESS**—Few only. Acos stereo and monaural turnover cartridge 73-1A. **Our price 42/6 post free.**

# Electronics FLEET ST Ltd

Dept. D. 152 FLEET STREET EC4 FLEet 3883  
Business Hours: Weekdays 9-6, Saturdays 9-1

## REPANCO MINI-3

A new local station pocket transistor Radio.

- Size 5in. x 3½in. x 1½in.
- Long and Medium Wave.
- Dual Ferrite Aerials.
- Loudspeaker reception.
- Regenerative RF Reflex Circuit.

Send Now! 1/6 (post free) for easy wiring plans, instructions and price list.

Mail Order and Trade:

**RADIO EXPERIMENTAL PRODUCTS LTD**


33 Much Park Street COVENTRY  
Telephone 62572

Wholesale Enquiries and Export:

**REPANCO LTD**

O'Brien's Buildings 203-269  
Foleshill Road COVENTRY  
Telephone 40594

## RADIOSETTE

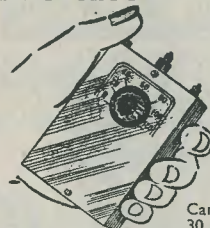


The ideal low cost transistor pocket radio for the beginner. The circuit utilises the new R.C.S. VARILoop-STICK transistor coil. A specially designed miniature .0004 tuning condenser permits the set to be in a case which fits the palm of your hand.

Can be built in 30 minutes **30/-**

All components are sold separately, full construction data including plan of parts, 2/-
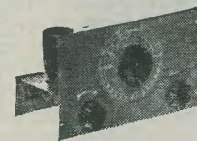
## ALL-WAVE RADIO 35/-

Ideal for the beginner or for those requiring a simple stand-by receiver




This 1 valve S.W. receiver can be built for 35/- from our list of components, which can be purchased separately. It includes valve and 1 coil covering 20-40 metres. Provision is made to increase to 2 or 3 valves if required, and all components are colour-coded so that the beginner can build this set quite easily. Send 2/- for specification, wiring diagram, layout and price list.  
Postage: under 10/-, 9d.; under 40/-, 1/6; over 40/-, post free

**R.C.S. PRODUCTS (RADIO) LTD**  
11 Oliver Road London E17 Mail Order only
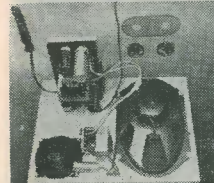
# Premier RADIO

23 TOTTENHAM COURT ROAD LONDON W1 Telephone MUSEum 3451/2



## THE FAMOUS COSSOR 3 watt Audio Amplifier Kit 562K

Original Price £9.15  
**Our Price £5.19.6**  
P. & P. 2/6

This Kit when assembled will provide a compact versatile amplifier which incorporates the most up-to-date printed circuit and is suitable for operation from radio, microphone and gramophone. The circuit design includes negative feedback and two high performance loudspeakers are used which ensures high quality output. All items are supplied including 10" x 6" loudspeaker, a 4" treble speaker and even solder

## POCKET TEST METER for the enthusiast: CABY MULTI-METER A-10

Ranges: DC/V 10-50-250-500-1kΩ (2kΩ/V); AC/V 10-50-250-500-1kΩ (2kΩ/V); DC/mA 0.5-25-250 (250 mV); OHM 0-10 kΩ-1MΩ.  
Complete with Test Leads **£4.19.6 p. & p. 2/6**

VISIT OUR NEW BRANCH AT  
309 EDGWARE ROAD · LONDON W2  
Telephone PADdington 6963


## THE BEREC

Battery Receiver for only £4.19.6 plus 5/- p. & p., or £1 deposit and 5 monthly payments of 19/-. This receiver is ideally suitable for use in the home or where normal electricity supply is not available, remarkable reception on both medium and short wavebands, incorporating the following latest type miniature battery valves: DK92, DF96, DAF96, DL96, and operates on an external B103 battery or equivalent. It is housed in an attractive two-tone metal case. Size 11½" x 7½" x 5½". Battery EXTRA, 18/6.


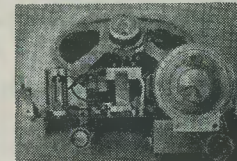
## THE COSSOR Printed Circuit Model 701K VHF/FM Radio Receiver Kit


Original Price 15 Gns.  
**Our Price £8.19.6**  
P. & P. 2/6



This Kit can be easily assembled and will provide a complete radio receiver for reception of transmission employing f.m. radiating from the VHF transmitters. This receiver utilises the latest type printed circuit method and is suitable for use on a.c. or d.c. mains. The Kit is supplied complete in every detail including a 10" x 6" Goodmans loudspeaker.

## MODERNISE YOUR RADIOGRAM

WITH AN *Armstrong* CHASSIS

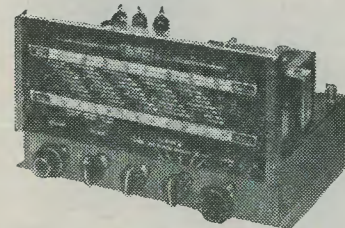

Post this coupon or write for descriptive literature and details of Home Trial facilities, Hire Purchase Terms and Guarantee. Demonstrations at our Holloway Showroom 9 a.m.-6 p.m. Sats. 9-5 p.m.

NAME \_\_\_\_\_  
ADDRESS \_\_\_\_\_  
CNC

**ARMSTRONG WIRELESS & TELEVISION CO. LTD**  
Walters Road · London N7 · NORth 3123

### STEREO 44 CHASSIS 27 GNS

(illustrated)  
8 watts output, 4 watts each channel ● 20dB negative feedback each channel ● Full FM band (87-108 Mc/s) and medium wave ● Stereo and monaural inputs for all crystal pick-ups, tape record and playback ● Separate bass and treble controls.

### STEREO-TWELVE CHASSIS 36 GNS

12 watts push-pull output, 6 watts each channel ● Full FM band, medium and long waves ● Stereo and monaural inputs for all pick-ups, radio, tape record and playback ● Separate bass and treble controls ● AFC on FM band, ferrite aerial and magic eye.

### JUBILEE CHASSIS 28 GNS

6 watts push-pull output, monaural ● Full FM band, medium and long waves ● Inputs for all pick-ups, tape record and playback ● Separate bass and treble controls ● AFC on FM band, ferrite aerial and magic eye.



## GET YOUR AERIALS RIGHT BEFORE WINTER

**HEADPHONES.** H.R. type, 4,000 ohms, very sensitive. Only 12/6 pair. P. & P. 1/6. C.L.R. (low res.) 8/6. P. & P. 1/6.

**RECORD CHANGERS.** Latest B.S.R. Monarch UA8 with manual and auto control, latest Ful-Fi Cartridge. List £9.15.0. OUR PRICE £6.19.6. Carr. paid.

**MULTI-WAY CABLE.**  $\frac{3}{8}$ " diam. 7 colour coded wires. Ideal for mobile or inter-chassis connection. Any length cut, 1/3 per yard. P. & P. 1/6 min.

**10-WAY CABLE** (5 pairs). Screened and plastic covered. Any length cut, 2/- per yard. P. & P. 1/6 min. 7-way (unscreened), 1/3 yard.

**DUAL RANGE VOLTMETERS.** Dual range 0-5V and 0-100 M.C. 1,000 $\Omega$ /V. Ranges easily extended. With test prods and leads. Complete in solid leather carrying case  $6\frac{1}{2}$ " x 5" x 2 $\frac{1}{2}$ ". A GIFT at 25/-. Post free.

**ABSORPTION WAVEMETERS.** 3.00 to 35.00 Mc/s in 3 switched bands, marked on scale. Complete with indicator bulb. A MUST for any ham shack. ONLY 19/6. Post free.

## SPECIAL OFFER ROTARY CONVERTERS

6V input, 250V, 125mA output. Only  $5\frac{1}{2}$ " x 3" x 3". 17/6 each. P. & P. 3/-.

**12V MINIATURE ROTARIES.** Only  $4\frac{1}{2}$ " x 2 $\frac{1}{2}$ " overall. Output 360V, 30mA or 310V, 70mA. NEW LOW PRICE 12/6 each or 22/6 for 2. P. & P. 1/6.

**100 KC/S CRYSTALS.** American 3 pin based crystals. New condition. Worth £3.10.0. Only 25/-. Post free.

**R.F. CHOKES.** 2.5mH, 120mA. Pye wound, 2/- each. Three or more post free.

**NATIONAL TYPE R-300 $\mu$ .** Type R-300 $\mu$  pillar mounting choke, 1mH, 300mA, 3/- each or 6 for 15/-.

**VARIABLE CONDENSERS.** All brass with Ceramic End Plates and Ball Race Bearings. 50pF, 5/9, 100 —6/6, 160—7/6, 240—8/6 and 300pF 9/6. Extension for ganging. P. & P. 1/-.

**RACK MOUNTING PANELS.** 9" x 5 $\frac{1}{2}$ ", 7", 8 $\frac{1}{2}$ ", or 10 $\frac{1}{2}$ " black crackle finish, 5/9, 6/6, 7/6 respectively, postage and packing 2/-.

## AERIAL EQUIPMENT

**COPPER WIRE.** 14g. h.d.: 140' 17/-; 70' 8/6; 7/25 stranded: 140' 10/-; 70' 5/- plus 2/- P. & P.

**RIBBED GLASS INSULATORS.** 3" 1/6 each or 6 for 7/6. P. & P. 1/6.

**TWIN FEEDER.** 300 ohm twin ribbon feeder, similar K25, 6d. per yard. K358 Telcon (round) 1/6 per yard. Post on above feeder and cable 1/6 any length.

**SUPER AERAXIAL CABLE** 1/8 per yard. P. & P. 1/6.

**CERAMIC FEEDER SPREADERS.** Type F.S. 6" 9d. each or 8/- doz. P. & P. 2/-.

**CERAMIC "T" PIECES.** Type AT for centre of dipoles, 1/5 each or 3 for 4/- P. & P. 1/6.

**MOSLEY TRI-BAND BEAMS**  
T33, JR, 3 EL ... £25  
TA32 JR. 2 EL ... £18  
V3 JR, Vertical 3 Band ... £8  
PLACE YOUR ORDER EARLY

**NEW MOSLEY POWER BEAMS.** Write for details. 300 watt, 50 ohm COAX,  $\frac{5}{8}$ " dia., very low loss, 1/6 yard or 20 yards 25/- P. & P. 1/9.

## CHAS H. YOUNG LTD (Dept. R)

110 DALE END BIRMINGHAM 4 (Tel. all departments) CEN 1635



### AMPLIFIER KIT


This is the famous Cossor 562K, 3-watt Audio Amplifier Kit, using 1 EF86, 6BQ5 and 5V4 valves, a 10" x 6" elliptical speaker and a 4" round speaker. This kit can be easily assembled to provide a compact and versatile printed circuit amplifier suitable for operation from radio microphone gramophone inputs. The circuit design includes negative feed-back and high performance loudspeakers, an easy-to-build instruction pamphlet. Original list price £9.15.0.

OUR PRICE £5-19-6 P. & P. 2/6


### VHF Radio Receiver Kit

This again is the famous Cossor printed circuit model 701/K. The kit may easily be assembled to provide a complete radio receiver suitable for the reception of transmissions employing f.m. (frequency modulation) radiating from the v.h.f. (very high frequency) transmitters now serving many different parts of the country. All parts, including loudspeaker and valves, are provided, together with the building instruction book.

Original list price 15 gns.

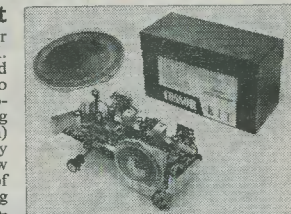

OUR PRICE £8-19-6 P. & P. 2/6

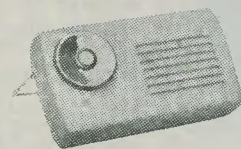

### Six Transistor Pocket Radio

can be built for £9.19.6, plus 3/6 post. Full medium and long wave superhet printed circuit construction using latest miniature components, 2 $\frac{1}{2}$ " moving coil speaker, Ferrite aerial. Choice of an attractive plastic cabinet in cream, blue or red. Complete easy-to-build instruction book included. All parts sold separately.

★ We hold large stocks of Condensers, Resistors, Ceramics, Volume Controls, Speakers, etc.  
PLEASE SEND FOR OUR CURRENT PRICE LIST


### RECORD CHANGERS

Collaro Conquest 4-speed auto-changers, turn-over styli, £7.19.6  
Garrard RC120/D Mark 2 4-speed auto and manual controls using GC2 cartridge, price £9.9.0 p. & p. 3/6

## WIRECOMP ELECTRONICS

378 HARROW ROAD LONDON W9 Telephone CUNningham 9530 Open 9-6. All day Saturday
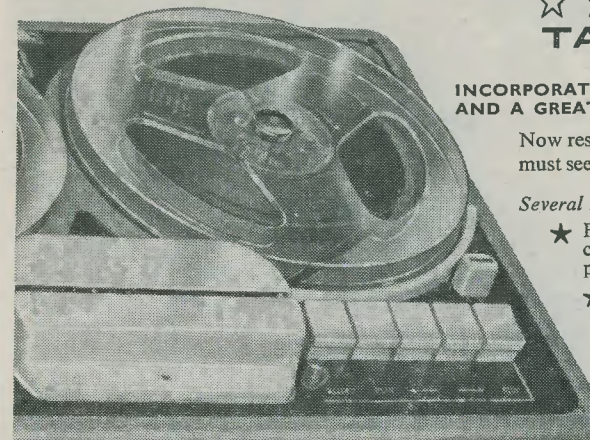
# Look at the NEW MOTEK K10 ☆☆☆☆☆ K10 TAPE DECK



INCORPORATING MANY NEW FEATURES  
AND A GREATER FREQUENCY RESPONSE

Now restyled in two tones of grey—you must see the new, attractive Motek K.10

Several new features include:

★ Enlarged drive wheel on the rev. counter ensures accurate tape positioning.

★ Non-slip push buttons.

Frequency response better than 40 c/s—  
★ 12,000 c/s at 7.5" per sec. with extremely low hum pick-up.

Patents pending

More and more manufacturers are installing Motek Tape Decks in their recorders.

Please send for brochure of K.10

21GNS

## MODERN TECHNIQUES

Wedmore Street, London, N.19 Tel. ARChway 3114

## Now... in your own home, LEARN

# RADIO - TELEVISION - ELECTRONICS

No previous technical experience needed!  
**PRACTICAL EQUIPMENT** (INCLUDING TOOLS)  
GIVES YOU A REAL LABORATORY TRAINING

"The trained electronics engineer has a great career ahead of him."

Valuable FREE book shows how E.M.I. Institutes

School of Electronics can train you for today's wonderful opportunities.

Radio, Television and Electronics provide an exciting field for the qualified man—high pay, a prosperous future, or independence in your own business. You train at home with E.M.I. Institute's specialists who know the quickest way to prepare you for one of the fine jobs open to trained electronics-men. Whether you are a beginner or an advanced student with an examination in mind, E.M.I. Institutes School of Electronics has a Course exactly suited to

your needs—with or without practical equipment—from electricity and magnetism to automation techniques.

We definitely Guarantee  
**"NO PASS - NO FEE"**

### FREE BOOK - POST NOW!

Please send me a free copy of your Guide to Careers in Electronics.

NAME

ADDRESS

Subject or Exam

Full details of the Courses, practical equipment, convenient monthly payments, our Employment and Advisory Depts. and much other helpful information is given in our Guide to Careers in Electronics. Write for your copy today. The book will be sent to you without obligation and free of charge.

Practical Radio  
Radio & Television  
Servicing

Practical

Electronics

Engineering

Automation

City & Guilds

R. A. Examination

R.T.E.B.

Certificate

P.M.G. Certificate


## E.M.I. INSTITUTES
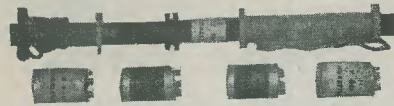
# SCHOOL OF ELECTRONICS

The Specialist Electronics Division of the British Institute of Engineering Technology  
(DEPT. SE/23) COLLEGE HOUSE 29-31 WRIGHT'S LANE KENSINGTON LONDON W8







### TELETRON MINIATURE TRANSISTOR 42/-

Superhet coil kit (as illustrated)

470 kc/s I.F. Transformers and Oscillator coil in screening cans  $\frac{3}{8}$ " x  $\frac{1}{2}$ " dia. Dual wave Ferrite rod aerial  $5\frac{1}{2}$ " x  $\frac{5}{16}$ " dia. Designed for the TRANSIDYNE miniature superhet receiver.

Descriptive folder with circuit and assembly instructions Price 9d.


**FERRITE ROD AERIALS** Wound on high permeability Ferroxcube rod. Medium wave, FRM 4" x  $\frac{5}{16}$ ", 8/9. Dual wave FRD, 8" x  $\frac{5}{16}$ ", 12/9.

Send 5d. in stamps for complete data and circuits. All types available from advertisers in this Magazine and local component stockists

## THE TELETRON COMPANY LIMITED

112b Station Road . Chingford . London E4 Telephone SIL 0836


### TELETRON TAPEJAK

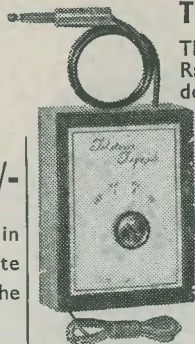

The first Transistorised Radio Tuner, specially designed for use with Tape Recorders. Converts your Recorder to a high quality Radio receiver. Direct recording on Tape. 5" x 3 $\frac{1}{2}$ " x 1 $\frac{1}{8}$ "

- High Sensitivity
  - Twin tuned circuits
  - Pre-setting for MW Programmes
  - Fxd. tuned for 1500 M
  - Switched prog. selector. ● Self Powered
- Tested and ready for use Battery extra


£5-9-0

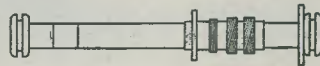

### ALL BAND RECEIVER R107

AMATEUR—SHIPPING—BROADCAST

This magnificent 9-valve 3-wave band receiver gives world-wide reception over 1.2-17 Mc/s (18-250 metres). The sensitivity is 1 microvolt on C.W., and 2-6 microvolts on R.T. Panel controls include Bandwidth switch ("Wide" or "Narrow"), choice of AVC and BFO, Audio Filter, R.F. Gain, Aerial Trimmer. Has built-in Output stage with internal speaker. Headphones sockets. Incorporates internal A.C. mains power unit (100-250V A.C.) and 12 volts D.C. Vibrator pack. Size 24" x 13" x 17". These sets are extensively tested prior to despatch.

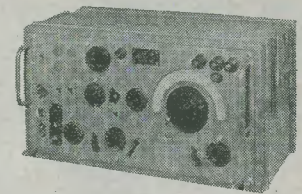

MODEL 1. Slightly used appearance £8.10.0 MODEL 2. Very good appearance £10.10.0 Carr. 20/- (England and Wales), rest of U.K. extra.

### ETCH YOUR OWN PRINTED CIRCUITS



ONLY 19/6

P.&P. 2/6 one hour. Fully guaranteed and complete with instruction book.

### SPECIALLY DESIGNED KITS FOR ETCH-YOUR-OWN CIRCUITS


- 1 Transistor/diode pocket radio 24/6 p.p. 1/6
  - 2 valve 3 watt mains amplifier 49/6 p.p. 2/6
  - 3 Transistor super pocket radio 72/6 p.p. 2/6
- All kits supplied entirely complete with full wiring and assembly details. Fully guaranteed

quickly and speedily at home with an Etch-Your-Own kit. Comprises over 60 sq. in. of laminate and enough chemicals to make dozens of printed circuits. Highest quality materials, easy to use and safe to handle. No special skill required—any mistakes can be corrected before etching. Can be completed in one hour. Fully guaranteed and complete with instruction book.
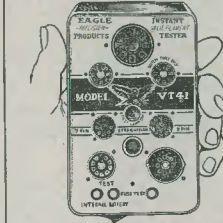
### INSTANT VALVE FILAMENT TESTER

MODEL VT-41

Pocket size Battery operated! GIVES INSTANT CHECK of



- All Receiver Valves\*
- All TV Valves
- All TV and Radio Set Fuses
- All Pilot Lamps


\*International octal, B8A, B9A, B7G battery and mains types.

● Has built-in miniature 7 and 9 pin valve straighteners and battery test.

Beautifully styled Precision made


Supplied complete, fully guaranteed ONLY 30/- P. & P. 1/6

### POCKET MULTI-METER

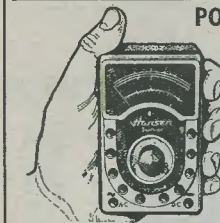

2,500 o.p.v. Multi-range. 6/30/120/300/1,200V a.c., ditto d.c. 0-1kΩ, 0-1 MΩ; 400μA, 12mA, 300 mA; —00 to +64dB; 5 ranges. 3" x 4 $\frac{1}{2}$ " x 1 $\frac{1}{2}$ ". Large clear dial, leads. List price £6.19.6. OUR PRICE £4.7.6. P. & P. 2/6. Saving you £2.13.0.


### AMERICAN LIGHT-WEIGHT HEADSET

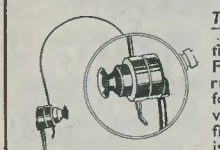

They're High & Low Impedance! These H.S.30 phones are the finest used by the U.S. Air Force. 250Ω imp. using soft rubber miniature ear moulds for maximum music and voice reproduction of the finest quality. Supplied free is a small transformer unit with cord and plug which steps impedance up to 4,000Ω. ONLY 15/-, P. & P. 2/6.


with cord and plug which steps impedance up to 4,000Ω. ONLY 15/-, P. & P. 2/6.

### HI-FI CO-AXIAL SPEAKERS

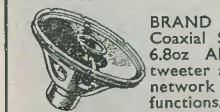


BRAND NEW—U.S.A. MADE. 12" Coaxial Speaker. The woofer uses 6.8oz Alnico 5 magnet. Has 3" tweeter and an electronic crossover network to separate the speaker functions. Freq response: ONLY 120/- 8 $\frac{1}{2}$ " cycles. Output 12 watts, imp 8ohms. ONLY 120/- 8 $\frac{1}{2}$ ", 2 $\frac{1}{2}$ " tweeter, 10 watts, etc., 90/-, P. & P. 4/- on each.

### WIRELESS SET No. 19 Mk. 11

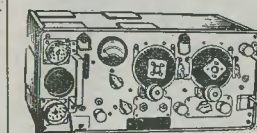

This famous Transmitter-Receiver incorporates "A" Set —TX/RX covering 2-8 Mc/s (37.5-150 metres); "B" Set—VHF TX/RX covering 230-240 Mc/s (1.2-1.3 metres) and intercom. amplifier. Complete with 15 valves, 500 micro-amp check and tuning meter, circuits and instruction book (American manufacture). In good condition. 65/-, carr. 10/-.

### COMPLETE MORSE TRAINING UNIT

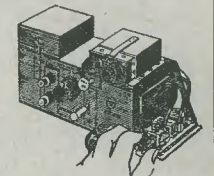

Complete Code Set, contains key, buzzer, headphones, pitch control, operating internal battery, housed in portable wooden case. Brand new, only 12/6. Carr. 5/-, Battery 1/6 extra.

### ★ VALVES NEW TESTED AND GUARANTEED ★

1R5	7/6	6V6G	7/6	DH76	8/6	EF92	5/6
1S5	7/6	6X4	7/6	DH77	7/6	EL41	9/-
1T4	6/-	6X5G	7/6	DK91	7/6	EL84	10/6
3S4	7/6	12AH8	10/6	PY82	7/-	EL91	7/6
3V4	8/-	12A7	7/6	DK96	8/-	EY51	9/6
5U4G	7/6	12AU7	7/6	DL92	7/6	EZ40	6/6
5Y3GT	8/6	12AX7	9/6	DL94	8/-	EZ80	6/6
5Z4G	9/-	12BH7	10/6	DL96	8/-	EZ81	7/-
6AM6	6/9	12K8GT	8/6	EB91	5/6	PL81	13/6
6AL5	5/6	12Q7GT	8/6	EBF80	10/6	PL82	10/6
6AT6	7/6	25A6G	10/6	ECC81	7/6	PY81	8/-
6BA6	8/6	25L6GT	9/-	ECC82	7/6	PCC84	10/6
6BE6	7/6	35Z4GT	8/6	ECC83	7/6	PCF80	10/6
6BR7	10/6	35L6GT	9/6	ECC84	10/6	PCF82	11/-
6BW6	8/6	53KU	11/6	ECC82	11/-	PCL82	10/6
6V5G	5/6	807	6/9	ECH81	10/6	U76	8/6
6I7GT	8/6	5763	10/6	ECH42	8/6	UBC41	10/-
6K7G	7/6	DAF91	7/6	ECL80	9/6	UCH42	10/6
6Q7G	8/6	DAF96	8/6	EF41	8/6	UF41	10/-
6SL7GT	8/-	DF91	7/6	EF80	8/-	UY41	8/-
6SN7GT	8/6	DF96	8/-	EF91	6/9	VY76	8/6

Matched Pairs. EL84, 23/-; 6V6G, 17/-; 6BW6, 18/-; KT33C, 19/6; KT66, 27/6; 807 14/6 pair

1R5, 1S5, 1T4, 3S4, 3V4, DAF91, DF91, DK91, DK92, DL92, DL94, any four, 27/6 per set.  
P.P. Op. Transformers. MR 3-15 ohms for EL84, 6V6, 6BW6, etc., 18/6; Op. Pen. 50mA, 5/6; 30mA, 4/6  
Volume Controls. All values, long spindle. L/S 3/-, s.p. 4/-, d.p. 4/9, ext. spkr. control 3/-  
W.W. Pots. Pre-set 3/-, 3W long spindle 5/6, s.p. 6/6  
P.M. Speakers. 3 ohm 5" 16/6, 6 $\frac{1}{2}$ " 17/6, 8" 21/-, 10" 25/-, 12" 30/-, Bakers 12" 15 ohm 15W, 90/-  
Coaxial Cable. 75 ohm  $\frac{1}{2}$ " stranded, 8d. yd; semi-air spaced, 9d. yd; screen cable single and twin, 9d. yd  
Coaxial Plugs 1/- each; Sockets 1/- each

C.R.T. Isolation Transformers with nil, 25% and 50% boost, low capacity a.c. mains 200/250V for 2V 4V, 6.3V and 13V tubes. All 10/6 each

Valveholders. 4, 5, 7 pin English and U.S.A. B7G, B9A, 10, M0, B8G, 9d. each; B7G, B9A with screening can, 1/6; B12A, 1/3. Aladdin formers  $\frac{1}{4}$ " with core, 8d. each

Scotch Boy Recording Tape, 1,200ft reels, 27/- Jack Plugs, miniature standard, 3/-; Sockets 3/- 2-Gang Condensers, 0.0005μF small size, 7/6 I.F. Transformers, 465 kc/s, small size, 7/6 pair

Capacitors, small mica, 5% 1pF to 100pF, 8d.; 120pF to 1,000pF, 9d.; 1,000V wkg. .01, .0015, .0025, .004, .005μF, 1/- each

Crystal Diodes, G.E.C., 1/6 each  
Headphones, lightweight, 4,000 ohm, 16/6 pair  
Ceramic Capacitors, close tol. 500V for V.H.F., 9d.

Paper Capacitors, tubular, 0.01μF 1,000V, 1/-; 0.1 to 0.5μF 500V, 10d.

Paper Blocks, 4μF, 1,000 wkg., 3/6  
Rectifiers, contact cooled, 250V 50mA, 7/6; 85mA, 9/6  
Reaction Condensers, .0001, .0003, .0005μF, 4/6 each  
Heater Trans. 200/240V, 6.3V, 1.5A, 7/6

Resistors,  $\frac{1}{2}$  and  $\frac{3}{4}$ W, insulated, 4d. and 6d.; 1W, 8d. 6W W.W., 1/-; 10W, 2/-

Electrolytics. Wire ends. 25/25V, 1/6; 50/50V, 2/-; 12/50V, 9d.; 8/450V, 2/-; 16/450V, 2/9; 16/500V, 3/6; 32/450V, 4/-; 8+8/450V, 4/6; 8+16/450V, 4/6; can types: 16/450V, 3/6; 16+16/500V, 6/-; 32/500V, 6/6; 32/450V, 6/6; 20+20/450V, 4/6; 64+120/275V, 7/6

Wavechange Switches, midget: 1p 12W, 2p 6W, 3p 4W, 4p 3W, 4p 2W, long spindles, 4/6

Toggle Switches. QMB, s.p.s.t., 2/-; s.p.d.t., 3/3; d.p.s.t., 3/6; d.p.d.t., 4/-

Chokes, 80mA, 15H, 8/6; 100mA 10H, 10/6; 150mA 10H, 14/6

Solder, Multicore, 4d. yd; Sleeving 2mm, 3d. yd

P. and P. 9d. to £1; 1/6 to £2; over £2 post free. C.O.D. 2/6

**R. COOPER G8BX** 32 SOUTH END CROYDON SURREY CROYDON 9186

Callers 87 Tottenham Court Road London W1  
Mail orders (Dept. C) 32a Coptic Street London WC1  
Telephone MUSEum 9607

**Relda Radio** Ltd.



## Build your own HI-FI!

At last! A specially selected and designed Hi-Fi Sound Installation for your home at really reasonable cost!



You save because you assemble everything yourself following our step by step instructions. You gain because you learn about the equipment as you build and are able to service and maintain it afterwards. Best of all—you'll have fun building it and be thrilled with the finished instrument which will bring you an entirely new experience in the enjoyment of sound. No previous skill or experience is needed. Post coupon now for full details, without any obligation. Easy terms available. Equipment includes:—Luxury Cabinets Top Quality Amplifier suitable for stereo or non-stereo reproduction · WFFM Radio Units · Record Player Tape Recorder · Hi-Fi Speaker System.

**FREE BROCHURE — POST TODAY**

To: RADIOSTRUCTOR, Dept. H-40  
46 Market Place, Reading, Berks.

Please send Brochure without obligation to:

Name..... BLOCK  
Address..... CAPS  
(317)..... PLEASE  
11-59

## RADIOSTRUCTOR

Britain's Leading Radio Training Organisation

**Broadway**  
ELECTRONICS

Hi-Fi Equipment — Radio Components

92 MITCHAM ROAD . LONDON . SW17

Telephone BALham 3984

### VALVES

1R5	7/-	*DF96	8/6	ECC81	7/6	MU14	7/6
1S5	7/-	*or 31/- set		ECC82	7/6	5Z4	9/-
1T4	6/6	EL41	8/6	ECC83	8/6	UL41	8/6
3S4	8/-	EZ40	7/6	ECC84	10/-	UY41	7/6
3V4	8/-	EL84	9/-	ECC85	7/6	PL81	11/6
*DK96	8/6	EZ80	7/6	EY51	12/-	PL82	8/6
*DAF96	8/6	EZ80	7/6	ECL80	10/-	PL83	8/6
*DL96	8/6	PY81	8/6	PY82	7/6	PY80	7/6

**4 SPEED E.M.I. PLAYER**, pick-up and motor mounted on metal plate, complete with Stereo Cartridge, turn over type plays either **Stereo, L.P. or Standard**. Well designed speed change mechanism. **£6.15.0** plus P. & P. 3/6.

**B.S.R. U.A.8.** Complete with TC8 cartridge. Limited number available. **£6.15.0** plus P. & P. 5/-.

**RECORD PLAYER AMPLIFIER**, complete on board with metal grill, 6 1/2" speaker, three valves, separate treble and bass controls. Ideal for fitting into record player case or bookshelves. **£5.10.0** plus P. & P. 3/6.

**SPECIAL OFFER.** Floor stand Crystal Mike. Black Crackle finish, Chrome stand. Extends to 5ft; heavy black crackle base. **£4.19.6** plus P. & P.

**PLESSEY 12" SPEAKERS**, Cloth Suspension, 15 ohms—handle 3 watts. Only 50/- plus 2/6 P. & P.

## REPANCO HIGH GAIN COILS

Dual Range Crystal Set Coil, Type DRX1	2/6		
Dual Range Coil with Reaction, Type DRR2	4/-		
Matched Pair Dual Range T.R.F. Coils, Type DRM3	8/-		
Pair Dual Range Superhet Coils, Type SH4	8/-		
Miniature Iron Dust Cored Coils, Type "R"	3/3		
Range	Aerial	H.F.	Osc.
800 2,000 m.	RA1	RHF1	RO1
190 550 m.	RA2	RHF2	RO2
70 230 m.	RA3	RHF3	RO3
15 50 m.	RA4	RHF4	RO4
Ferrite Rod Aerial, Dual Range Type FR1	12/6		
Miniature I.F. Transformers, Type MSE (465 kc/s)	pair 12/6		
Standard I.F. Transformers, Type TCG (465 kc/s)	pair 13/6		

Send S.A.E. for latest Repanco Component Catalogue

### Radio Experimental Products Ltd.

33 Much Park Street, COVENTRY  
Telephone 62572

## BUILD YOUR OWN



## MAYKIT TRANSISTORISED CAR RADIO

★ **HYBRID DESIGN—5 VALVE SUPERHET, TRANSISTOR AND PRINTED CIRCUIT**  
★ **STANDARD SIZE 7" x 2"—12V BATTERY**  
★ **ALL NEW COMPONENTS—AVAILABLE SEPARATELY OR IN COMPLETE PACK**

First and best DO-IT-YOURSELF Car Radio. Uses new Brimar low volt valves, no vibrator. Printed circuit and power transistor. Negligible "fade" and no "buzz." Only 1.5 amp. consumption. Complete with chassis assembly, filter box and output stage including elliptical loudspeaker and detailed instructions. Also Jason Car Radios. Send 3/6 for Car Radio booklet.  
Service facilities available

Can be built for **£13.10.0** plus 5/- p. & p.  
Cash with order  
or write for **BUY-AS-YOU-BUILD** details

Dept. D **MAYRA ELECTRONICS LTD**  
118 BRIGHTON ROAD . PURLEY  
Telephone Bywood 1263

## THE RADIO CONSTRUCTOR

### BOUND VOLUMES

Attractively bound in blue cloth, with gold-blocked spine


Vol. 11, August 57 to July 58 ... .. **£15.0**, postage 1/9

Vol. 12, August 58 to July 59 ... .. **£15.0**, postage 1/9

Where readers return all issues of a volume for exchange,  
the price is 12/6, plus postage 1/9

Please note:—Indexes are available for Volume 12, August '58 to July '59 inc., price 6d. postage 2d. A limited number of indexes are also available for volumes 4, 6, 8 and 11, at the same price.

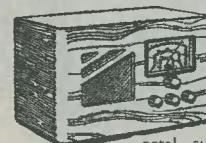**DATA PUBLICATIONS LTD** 57 MAIDA VALE LONDON W9



## HOME RADIO

79/6

A.C./D.C. Universal mains 5 valve octal superhet. 3 waveband receiver can be adapted to gram. p.u. In attractive wooden cabinet 9 1/2" x 18 1/2" x 11 1/2". Ins. carr. 4/6


**EXTENSION SPEAKER** . . . . . 19/9

Polished oak cabinet of attractive appearance. Fitted with 8" P.M. Speaker W.B. or Goodmans of the highest quality. Standard matching to any receiver (2-5 ohms). Switch and flex included. Ins. carr. 3/9



**SOLO SOLDERING TOOL** . 12/6

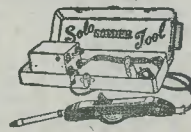110V, 6V or 12V (special adaptor for 200/250V 10/- extra). Automatic solder feed including a 20ft reel of Ersin 60/40 solder and spare parts. It is a tool for electronic soldering or car wiring. Revolutionary in design. Instantly ready for use and cannot burn. In light metal case with full instructions for use. Post 3/6



**TERMS DUKE & CO AVAILABLE**  
(DEPT. K.11) 621/3 ROMFORD ROAD  
MANOR PARK E12  
CATALOGUE FREE ILF 6001/3

## SMITH'S of Edgware Road

ELECTRONIC COMPONENT  
DISTRIBUTORS FOR OVER 25 YEARS

### BLANK CHASSIS

Precision made in our own works from commercial quality half-hard aluminium of 16 s.w.g. (1/16") thickness, these chassis go all over the world (and off it—in rockets!) Same day service for ANY SIZE, to nearest 1/16" and up to 17" of straightforward two, three or four-sided chassis. Specials dealt with promptly.

**SOLDERED CORNERS.** While these chassis, owing to their thickness, hardness and efficient folding, will carry components of considerable weight and normally require no corner strengthening, we can do this by a special soldering technique at 6d. extra for each corner.

**FLANGES.** 1/4", 3/8" or 1/2" flanges (inside or outside) 6d. extra for each bend.

**PRICE GUIDE (normal chassis only)**

Work out total area of material required, including waste, and refer to table below:

48 sq. in.	4/-	176 sq. in.	8/-	304 sq. in.	12/-
80 sq. in.	5/-	208 sq. in.	9/-	336 sq. in.	13/-
112 sq. in.	6/-	240 sq. in.	10/-	368 sq. in.	14/-
144 sq. in.	7/-	272 sq. in.	11/-	and pro rata	

Post 1/3 Post 1/6 Post 1/9  
Discount for quantities. Trade enquiries invited. Spray finished arranged for quantities of 25 or over.

**PANELS.** The same material can be supplied for panels, screens, etc. Any size up to 3ft at 4/6 sq. ft. (sq. in. x 3). Post, up to 72 sq. in. 9d., 108 sq. in. 1/3, 144 sq. in. 1/6, 432 sq. in. 1/9, 576 sq. in. 2/-.

287/289 EDGWARE ROAD LONDON W2  
Telephone PAD 5891/7595



# EDDY'S (NOTTM) LTD

116-118 Alfreton Road · Nottingham

**LUXEMBOURG EXPANDING AERIALS.** Compact and easy to fit. No technical knowledge required. Greatly improves reception. 3/11 ea., post 6d.

**DYNAMOTORS.** 200V d.c. to 12V d.c. Ideal for train sets. 19/11, post 2/6.

**MINIMOTORS.** 1.5V to 6V, 8/6, post 1/-

**VIBRATORS.** 12 volts 4 pin, 4/11, post 1/-.

**NIFE ACCUMULATORS.** Midget single unit size 3" x 2 3/4" x 3/8", 7 amp. hrs, 1/11, post 1/6.

**JACK PLUGS.** Standard type, 1/11, post 6d.

**GERMANIUM DIODES.** 1/- each, 10/- doz. post 4d.

**THROAT MIKES.** 1/-, post 6d. Could be used for electrifying musical instruments.

**ACOS CRYSTAL PICK-UPS.** Turnover head (2 sapphire styli), 29/11, post 2/6.

**DIMMER SWITCHES.** Ideal for train speed regulators. 1/11, post 6d.

**MORSE TAPPERS.** Plated contacts. Adjustable gaps, heavy duty, good quality. 3/6 each, post 9d.

**CONDENSERS.** Tubular wire end (not ex-Govt.) 8uF 450V 1/9, 8-8 450V 2/9, 16uF 450V 2/9, 16-8 450V 3/11, 16-16 450V 3/9, 32uF 450V 3/9, 32-32 350V 4/-, post 1/-.

**RECTIFIERS.** Contact cooled 250V 60mA 7/6, RM1 4/9, RM2 6/9, RM3 7/6, RM4 15/6, RM5 19/6, post 1/-.

**NEON MAINSTESTER/SCREWDRIVERS.** 3/11, post 6d

**ACOS CRYSTAL MICROPHONES.** Type MIC 35/1. 25/11, P. & P. 2/6.

ALL ABOVE ARE NEW AND GUARANTEED

### SPECIAL OFFER

**GRAM AMPLIFIERS.** High sensitivity, 3 watts output. Separate volume and tone controls. Printed circuit. 59/11 fully guaranteed P. & P. 4/-.

Size 8" x 2 3/4", max. height 5"

AZ1	12/6	EF50	1/6	1D5	9/6	6K7M	6/-
AZ31	9/-	EF50(R)	2/11	1R5	7/6	6K8G	6/6
DAF96	8/6	EF80	7/-	1L4	3/9	6P28	11/-
DH63	8/6	EF91	6/-	1T4	5/-	6SA7M	7/-
DH77	7/6	EF92	5/-	1S5	6/6	6SG7M	6/6
DK96	8/6	EL84	9/-	3V4	8/6	6SN7GT4	11/11
DL96	8/6	EL85	9/6	5U4G	6/6	6V6G	5/11
DF96	8/6	EY86	9/6	6AG5	5/-	6V6GT	6/-
DM70	7/6	EZ80	6/11	6AM6	4/-	6X5GT	5/-
EB34	1/6	GT1C	7/6	6B8G	2/11	10F1	9/6
EB91	4/-	KYW61	6/6	6BA6	6/-	10F9	10/6
EBF80	9/-	OZ4	5/6	6BJ6	7/-	12A6	6/6
ECC81	6/-	P61	2/6	6C4	3/6	25A6G	8/-
ECC82	7/-	PCC84	8/6	6CH6	9/6	35W4	7/6
ECC83	8/6	PCF80	9/-	6F1	9/-	90AV	4/6
ECC84	9/-	PEN36C	9/6	6F13	9/-	807(B)	3/9
ECC85	9/6	PL33	9/6	6F33	6/6	954	1/6
EFC80	11/6	PL81	12/6	6H6M	2/6	955	3/11
ECL82	11/6	PL82	8/6	6J5G	2/11	956	3/11
EF36	2/6	PL83	9/6	6J5GT	3/6	9001	2/11
EF37	4/6	PY31	8/6	6J5M	4/6	9004	4/6
EF42	9/6	U35	9/6	6K7G	2/6	9006	4/-

Surplus NEW AND GUARANTEED VALVES BY RETURN. ALL TESTED BEFORE DESPATCH

Any parcel insured against damage in transit for only 6d. extra per order. All uninsured parcels at customer's risk. Postage and packing 6d. per valve. Over £3, free. C.O.D. charge 3/- extra. S.A.E. with enquiries.

## It pays to go— to VIDIO

For value in Rebuilt Cathode Ray Tubes try Vidio. Each tube fully guaranteed for twelve months and fitted with a BRAND NEW Electron Gun Unit Free Delivery in the U.K. with an immediate, off-the-shelf service

### TRADE ENQUIRIES INVITED

Write direct to the  
**VIDIO REPLACEMENT  
COMPANY**

(THEY'RE TRADE ASSOC. APPROVED)


Hales Street  
Deptford High Street  
London S E 8

Telephone TIDeway 4506

Member of the Association of  
Tube Rebuilders



## Fully Guaranteed Components

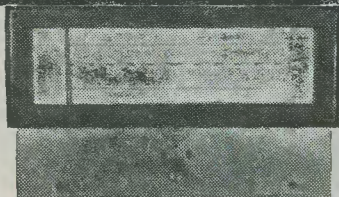

### S. L. 16 DRIVE

A general purpose slide rule drive for FM/VHF units, short-wave converters, etc. Printed in two colours on aluminium, with a 0-100 scale, and provision is made for individual calibrations. Complete with bronze escutcheon and glass.

PRICE 13/9

It's reliable if it's made by Jacksons

**JACKSON BROS**  
(LONDON) LTD.


Kingsway · Waddon · Surrey

Telephone CROydon 2754/5


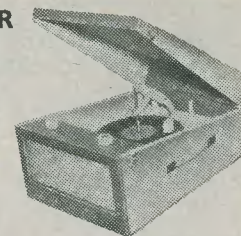
## RECORD PLAYER BARGAIN OFFER

A self-contained Portable unit comprising the latest Collaro 4-speed Auto Changer Record Player, incorporating the famous High Fidelity Studio "O" Xtal Pick-up with Turnover Cartridge, and fitted with L.P. and 78 Sapphire styli. An internal 2 valve amplifier of modern design with variable tone and volume controls is fitted. Quality 6" P.M. speaker Robust wooden cabinet attractively styled in maroon with polka dot relief.



This complete 3 unit Record  
Player Kit offered at

£12-19-6 carriage free.

Collaro 4-speed autochanger, £6.19.6 + 4/6 carr.

2-valve, 2-stage amplifier, ready wired, complete with speaker, etc., £3. 7.6 + 2/6 carr.

Cabinet with mounting board, etc. Size 18 1/2" x 13 3/4" x Ht. 8 1/2", £2.12.6 + 3/6 carr.

This is a recommended bargain buy and when present stock is exhausted cannot be repeated. Originally built to be sold at 17 gns.

### RECORD PLAYER BARGAINS

All Brand New and Latest 4-sp. Models

**SINGLE PLAYERS.** B.S.R. (TU9) 90/-; Collaro (4/564) 6 gns.; Garrard (4SP) £7.10.0; Garrard (TA Mk 2) £8.19.6. Carr. and ins. 3/6.

**AUTO CHANGERS.** B.S.R. (UA8) £6.19.6; Collaro (Conquest) £7.19.6; B.S.R. (UA12) with stereo and monaural cartridge, 10 gns. Garrard (RC121/4D/Mk 2) plug in head and stereo adapted, 10 gns. Carr. and ins. 4/6. Garrard GCS/10 stereo head £2 extra. Replacement Sapphire Styli available all units.

## RE-GUNNED TV TUBES new budget prices

... and now 12 months guarantee!

All tubes rebuilt with new heater, cathode and gun assembly-reconditioned virtually as new:

12"-£6, 14"-£7, 17"-£8.10.0 etc  
10/- part exchange allowance on old tube Carr. and ins. 10/- Comprehensive Stocks—quick delivery

### BAND III TV CONVERTER

180 Mc/s-205 Mc/s (Channels 6-13)

Suitable London, Birmingham, Northern, Scottish, Welsh and I.O.W. ITA transmissions.

**Mk. 2 Model.** Latest cascode circuit using ECC84 and EF80 valves giving improved sensitivity (18 dB) over standard circuits, built-in power supply a.c. 200-250V. Dimensions only 6 1/2" x 3", ht. 4". Simple and easy to fit—only external plug-in connections. Wired, aligned and tested ready for use. State channel required. Guaranteed. Bargain offer—good results or full refund. **ONLY £3.19.6** Carr. and pkg. 2/6

Recommended Addition—Band I/Band III changeover switch and B.B.C. aerial socket fitted and wired internal with converter 8/- extra.


### 7 VALVE AM/FM RADIOGRAM CHASSIS BARGAIN OFFER

MANUFACTURERS SURPLUS Latest type ECC85 series valves with 3 watt EL84 Output Med., Long and V.H.F. Wavebands with Switched Gram Position. Magic Eye Tuning, Illuminated glass dial 1 1/2" x 3 1/2". 4 controls. Chassis size 13 1/2" x 6 1/2" x 7 1/2" ht. A.C. 200/250V. Aligned and tested ready for use. Carr. **£13.10.0** and ins. 5/-.

Complete with 4 knobs—walnut or ivory to choice. P.M. speakers only required, 8" 20/-, 10" 25/-.

**TRANSISTORS—BVA 1st Grade** Mazda XB102, XB104, each 10/-; XA103, 15/-; XA104, 18/-; G.E.C. GET3, 10/6, etc. OA81, 3/6; GEX34, 4/-.

Mfrs. surplus (recommended and tested perfect), OC71, OC72, each 7/6; OC45, 12/6; OA70, 3/-.

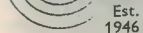

Est. 1946

## RADIO COMPONENT SPECIALISTS

70 Brigstock Road Thornton Heath Surrey

Telephone THO 2188

Terms: C.W.O. or C.O.D. Post and packing up to 1/2 lb 7d., 1 lb 1/1 3 lb 1/6, 5 lb 2/-, 10 lb 2/9

**COAX 80 ohm CABLE—Stand. 1/4" diam.**  
Low Loss Semi-Air Spaced AERAXIAL, polythene ins. SPECIAL REDUCED PRICES  
20 yds 12/6, P. & P. 1/6; 40 yds 22/6, P. & P. 2/-; 60 yds 32/6, P. & P. 3/-.

All other lengths 8d. yd. Coax Plugs 1/-, Coax Sockets 1/-, Couplers 1/3, Cable End Sockets 1/6, Outlet Boxes 4/6.

### C.R.T. Heater Isolation Transformers

New improved types—mains prim. 200/250V tapped

All isolation transformers now supplied with alternative no boost, plus 25%, and plus 50% boost taps, at no extra charge. All standard individual voltages available: 2V 2A-13V 0.3A (as previously advertised) each 12/6 P. & P. 1/6

Small size and tag terminated for easy fitting

**LOUDSPEAKERS.** P.M. 3 ohm, 2 1/2" Plessey, 17/6; 3 1/2" Goodmans, 18/6; 5" R. & A., 17/6; 6" Celest., 18/6; 7 1/2" x 4" Goodmans, 18/6; 8" Rola, 20/-; 10" R. & A., 25/-; 12" Plessey, 30/-, etc

**SPEAKER FRET.** Expanded bronze anodised metal: 8" x 8", 2/3; 12" x 8", 3/-; 12" x 12", 4/6; 12" x 16", 6/-; 24" x 12", 9/-, etc. TYGAN FRET (Contemp. pattern) 12" x 12", 2/-; 12" x 18", 3/-; 12" x 24", 4/-, etc.

### VOLUME CONTROLS

Log. or lin. ratios, 10,000 ohms-2 Megohms. Long spindles. 1 year guarantee. Midget Ediswan type, 1 1/2" dia. No sw. 3/-, d.p. sw. 4/6.  
**TWIN GANGED CONTROLS.** 1/2 Meg. 1/2 Meg. 1 Meg. less sw., each 8/9.

### SPECIAL OFFER

Superior type art leather-covered portable case. Well known manufacturer's surplus, in attractive tone colour with non-tarnish gilt fittings. Size 15 1/2" x 5 1/2". Knock-out price 15/6, p. and p. 2/6.

**CAR RADIO KIT.** This popular Hybrid printed circuit 12V Car Radio as recently featured in *The Radio Constructor* is now available. **£12.19.6** P. & P. Complete Kit incl. Speaker **ONLY £12.19.6** 3/6 Comprehensive Instruction Booklet 3/6 (free with kit)

**VALVES—NEW REDUCED PRICES.** 1R5, 1T4, 7/6; 1S5, 7/6; 3S4, 3V4, 8/-; 5Z4, 9/6; DAF96, 9/-; DF96, 9/-; DK96, 9/-; DL96, 9/-; ECL80, 10/6; ECL82, 11/6; EF80, 9/6; EF86, 13/6; EF91, 8/6; EL84, 9/6; EY51, 10/-; EY86, 10/-; EZ80, 7/6; MU14, 9/6; PCC84, 10/6; PCF80, 10/6; PCF82, 10/6; PCL83, 12/6; PL81, 12/6; PL82, 9/6; PL83, 11/6; PY80, 7/6; PY81, 9/6; PY82, 7/6; U25, 12/6, etc. Send for list.

**SPECIAL.** 1R5, 1T4, 1S5, 3S4 or 3V4, per set, 27/6; DK96, DF96, DAF96, DL96, 35/-; 6K8, 6K7, 6Q7, 6V6, 5Z4 or 6X5, 35/-.

Hours 9 a.m.-6 p.m., 1 p.m. Wed.



## New purchase of AC/DC PORTABLE RADIOS

- ★ 5 valve superhet
- ★ Built-in frame aerial
- ★ Size 10" x 10" x 4" deep
- ★ All Marconi valves
- ★ Med., long and short waveband
- ★ OR Med. and two short wavebands
- ★ Gram. sockets (for crystal or magnetic pick-ups)
- ★ 7" x 4" elliptical speaker
- ★ Slow motion tuning
- ★ Ideal for a radio-gram

ONLY £7.12.6 post 7/6

Portable polished cabinet ... .. 27/6  
Super portable rexine cabinet ... .. 37/6  
IDEAL SHORT WAVE RX

### TRANSMITTER/RECEIVER

**Army Type 17 Mk. 11.** Complete with valves, high resistance headphones, handmie and instruction book and circuit. Frequency range 44.0 to 61 Mc/s. Range approximately 3 to 8 miles. Power requirements: standard 120V h.t. and 2V i.t. Ideal for Civil Defence and communications.

BRAND NEW 45/- P.P. 5/-  
44-61 Mc/s calibrated wavemeter for same, 10/- extra

### WALKIE/TALKIE

**Type 38 Transmitter/Receiver.** Complete with 5 valves. In new condition. These sets are sold without guarantee, but are serviceable.

22/6 P.P. 2/6

Headphones 7/6 pair, Junction Box 2/6, Throat Mike 4/6, Canvas Bag 4/-, Aerial Rod 2/6.

### POCKET MULTIMETER

**MODEL A10: 500 Micro-amp Movement**  
★ AC/DC voltages, 2,000 ohms per volt; 10, 50, 250, 500 and 1,000 volts. ★ Resistance 10k ohms and 1 Megohm. ★ D.C. current 0.5mA; 25mA; 250mA.  
★ Decibel range. ★ DC ±2% accuracy; AC ±3%.  
**INCLUSIVE OF TEST PRODS, ILLUS-TRATION BOOK AND BATTERIES**

£4.17.6

Size 5 1/2" x 3 3/8" x 1 3/8". Weight 17 oz. P.P. 1/6  
BRAND NEW AND GUARANTEED  
Free Leaflet by Return

### 373 MINIATURE I.F. STRIPS 9.72 MC/S



The ideal f.m. conversion unit as described in P.W., April/May 1957. Complete with 6 valves, three EF91s, two EF92s and one EB91. I.F.T.s, etc., in absolutely new condition. With circuit and conversion data.

12/6 (less valves) 37/6 (with valves)  
Postage and packing 2/6 (either type)

### REDUCTIONS TO VALVE LISTS

OZ4	5/-	6AL5	5/-	6X5GT	5/-	CV140	5/-	DL96	9/-	EF40	11/6	PCC84	9/-	UBF89	9/-
1C5	10/-	6AM6	5/-	7Y4	7/-	723A/B	55/-	EB91	5/-	EF42	11/-	PCF80	9/-	UCC85	9/-
1R5	7/-	6C4	5/-	7Z4	7/-	2K25	65/-	EBC41	9/6	EF89	8/6	PCL82	12/-	UCH42	10/-
1S4	7/-	6F12	5/-	12A7	8/-	DAF91	7/-	EBF80	9/6	EF91	5/-	PY80	7/6	UCL82	12/-
1S5	6/6	813	65/-	12A7	7/6	DAF96	9/-	EBF89	9/6	EF92	5/-	PY81	8/6	UF80	9/6
1T4	6/-	GT1C	15/-	12A8GT	10/-	DF91	7/-	ECC81	8/-	EL42	7/6	PY82	7/6	UF85	9/6
3A5	9/-	6L6G	8/-	12K8M	10/-	DF96	9/-	ECC82	7/6	EM34	7/6	VR105/306	-	UF89	10/-
3Q5	9/-	6L6M	10/-	12SN7GT	10/-	DK91	7/-	ECC91	5/-	EY51	10/-	VR150/306	-	UL41	8/-
3S4	7/-	6Q7G	7/6			DL91	7/-	ECF80	12/-	EY86	10/-	U50	6/-	UL84	9/-
3V4	7/6	6SL7	6/-	12SL7GT	10/-	DK96	9/-	ECL80	10/-	EZ40	7/6	U52	6/-	UY41	7/6
5U4	6/-	6SN7	6/-			DL33	9/-	EF22	7/6	EZ80	7/-	UABC80	9/-	UY85	8/-
5Y3GT	6/-	6V6	6/-			DL35	10/-	VS70	6/-	EZ81	7/-	UAF42	9/-	VR54	2/6
6A7	9/-	6V6G	7/6	CV135	5/-	DL92	7/-	EF36	5/-	KT33C	8/6	UB41	10/-	CV188	6/-
6A8GT	9/-	6V6GT	6/6	CV136	5/-	DL94	7/6	EF39	5/-	MU14	7/6	UBC41	9/-	Z77	5/-
6AC7	5/-	6X4	6/-	CV138	5/-										

## HENRY'S RADIO LTD · 5 HARROW ROAD · LONDON W2

Opposite Edgware Road Tube Station

(DEPT. RCN)

Telephone PADDington 1008/9

## R.C.A. Valve-Voltmeter

Type 165-A

### D.C. ELECTRONIC VOLTMETER

6 Ranges, 3-1,000 Volts  
Input Res. 11,000,000 ohms  
Sensitivity 3,666,666 o.p.v. on 3V scale

### A.C. VOLTMETER

5 Ranges, 0-1,000 volts  
Sensitivity 1,000 o.p.v.

### ELECTRONIC OHMMETER

6 Ranges from 0.1 ohms to 1,000 Megohms  
Movement 200 Microamperes. D.C.  
Accuracy ±2%

BRAND NEW £12.10.0

With Instruction Book and Test Prods P.P. 3/6

LIMITED STOCKS — BUY NOW

### QUARTZ CRYSTALS

LARGE RANGE OF 500 DIFFERENT TYPES FOR ALL PURPOSES. SEND FOR FREE LIST.

### CAR RADIO 2-watt Amplifier

(See R.C. December 1959)

★ 7" x 4" high flux speaker ★ V15/10P power transistor. ★ Overall size 6" x 4" x 3" ★ Works off car 12-volt battery.

FOR USE WITH ANY BATTERY PORTABLE WITH 15-OHM OR 3-OHM OUTPUT TRANSFORMER.

Complete set of parts ... .. 65/- P. & P. 2/6  
Unit built up and tested ... .. 77/6 P. & P. 2/6

### IDEAL FOR TRANSISTOR-8

USE YOUR PORTABLE IN YOUR CAR!

### IF, RF, GENERATOR

★ Size 2 1/2" x 1 1/2" x 1". Harmonic output 450 kc/s to 2 Mc/s. Ideal for complete receiver alignment.

All Components 25/- P.P. 1/-

### AUDIO GENERATOR

Ideal for audio circuit checking or r.f. modulator. With XB104 transistor.

All Components 25/- P.P. 1/-

★ Size 2 1/2" x 1 1/2" x 1"

### AUDIO IF, RF SIGNAL TRACER

★ 2 Ediswan transistors. ★ Headphone output.

★ Size 4 1/2" x 3" x 1 1/2". All parts 37/6 P.P. 1/6

### "ADDON" 250mW OUTPUT STAGE

★ 2 Ediswan Transistors. ★ Push-pull up to 250 mW. ★ 3" ELAC Speaker. ★ Cabinet 5 1/2" x 3 1/2" x 1 1/2". A unit for use with Major 2 and 3 or any earpiece pocket-portable to give full speaker output. Complete set of parts with cabinet, 59/6. P.P. 1/6

## DO-IT-YOURSELF! NO EXTRAS NEEDED : FREE LISTS ON ANY MODEL AFTER SALES SERVICE : ALL PARTS SOLD SEPERATELY

All Components Guaranteed

★ IDEAL CHRISTMAS GIFTS ★

## TOP BAND TRANSISTOR TRANSMITTER

Pocket size 150 to 160 metre Transistor Transmitter. Range up to 100 ft. on 3ft. aerial. Ideal for short Range Communication, Car to Car, etc.  
Complete set of parts 57/6. P.P. 1/6.  
MICROPHONE INPUT: SEND FOR FREE CIRCUIT AND LIST. See 'RC' Jan., 1960.


## TRANSISTOR CRYSTAL MARKER (5.5 Mc/s to 9 Mc/s)

Uses new 25 Mc/s transistor, high efficiency oscillator. Complete with I-FT243 crystal between 5.650 Mc/s and 8.650 Mc/s.

30/- P.P. 1/- (7 to 7.3 and 8 to 8.3 2/6 extra)

FREE LIST AND DIAGRAM


## MINOR-1

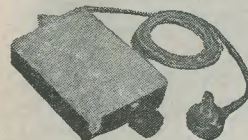

- ★ Variable tuning over medium waves
- ★ 3-stage reflex circuit
- ★ Highly sensitive
- ★ Internal ferrite aerial
- ★ Drilled chassis
- ★ Weight less than 2 oz.
- ★ Size only 3" x 2" x 2 1/2"

Complete, including transistor, personal miniature phone, case, battery and complete circuit and layout diagrams. Circuit and shopping list FREE.  
ONLY 49/6. P.P. 1/6

## MAJOR-3 Transistor Receiver

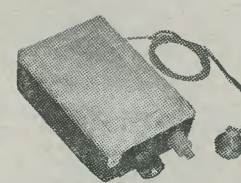

- ★ 5-stage Reflex Circuit
- ★ No Aerial or Earth
- ★ Min. Volume Control
- ★ 3 Ediswan Transistors
- ★ Medium Wave Tuning
- ★ Size 4 1/2" x 3" x 1 1/2"
- ★ Personal phone

(As described in R.C. Sept. '59)

Complete set of parts 87/6 P.P. 1/6

## TRANSISTORS RED SPOT 5/- EACH WHITE SPOT 8/6 EACH

NEW FREE LIST INCLUDING SHORT WAVE TYPES

## MAJOR-2 (Transistor Pocket Radio)



- ★ 4-stage reflex circuit
- ★ Tunable over medium waves
- ★ No aerial or earth
- ★ Over 6 months on one battery
- ★ Size 4 1/2" x 3" x 1 1/2"
- ★ Weight under 4 oz.
- ★ Layout diagrams

Complete set of components including 2 EDISWAN transistors, 69/6. P.P. 1/6


## "THE TRANSISTOR-8"

- ★ Tunable over medium and long wavebands
- ★ 250mW output push-pull
- ★ Internal Ferrite aerial
- ★ Highly sensitive and selective
- ★ 7" x 4" high flux speaker
- ★ All components identified and carded
- ★ EDISWAN transistors throughout
- ★ Easy-to-follow layout diagram

Car radio components 8/-; A.V.C. 4/3;

325mW version £11.11.6. P. & P. 2/6

Size 9" x 7" x 3 1/2". Weight 4 lb

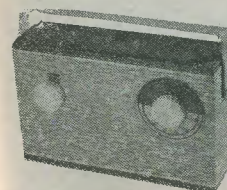

## "SUPER-SIX" Transistor Portable Superhet

- ★ Medium and Long Waves
- ★ 6 Mullard Transistors
- ★ Printed Circuit
- ★ Sensitive and Selective
- ★ Ferrite Rod Aerial
- ★ 3" 150Ω Speaker
- ★ Full Assembly Instructions
- ★ Size 7" x 2" x 1 1/2"

Complete set of parts including attractive cabinet

£9.10.0

P.P. 2/6

All parts sold separately

High sensitivity and selectivity combine to give excellent reception on both medium and long waves and this set is recommended by us as being the easiest-to-build printed circuit transistor set ever offered.

## HENRY'S RADIO LTD · 5 HARROW ROAD · LONDON W2

At junction of Edgware Road and Harrow Road

(DEPT. RCN)

Telephone PADDington 1008/9



Heavy duty 500pF differential condensers 3/-. Small solid dielectric variables, 0.0001µF 3/-; 0.0003µF 3/9; 0.0005µF 4/-. Resistors from 3d. each. Assd. carbon (many 5%). for 3/11, 50 for 7/6 Hi-Stabs 10% 1/2 watt 6d.; 10% 1 watt 9d.; 1% 1/2 watt 2/-. Many odd values. Send requirements for quotation Ajax Crystal Set complete, 14/6; L.W. 15/-. Case and chassis 5/9. Teletron HAX Coil 3/-. REP Dual Wave Xtal Coil 2/6. Germanium Diodes 1/-. Headphones, lightweight, 14/- and 16/-. Nuts, bolts, washers, tags. Well assorted: 25 1/-, 72 2/9, 144 5/-. Miniature Neons 1/10. "Litesold" Miniature Soldering Iron, battery or mains, 21/6. Multicore Solder 4d. yd., 19ft reel 2/6, 1lb reel 14/9. Fine gauge for printed circuits, 40ft reel, 2/6. Switches, s/p from 2/3, d/p from 3/6. Ferrite Rods 8" 2/-. 4" 1/6. Mains neon indicators with built-in resistor. Domed top, chrome bezel, 1" long 1/2" diam. Opal, red, amber, 3/10; green 4/7. Sub-miniature Electrolytics 8µF 6V, 16µF 12.5V, 32µF 3V, 5µF 12.5V 5µF 40V, 2.5µF 40V, 1.6µF 6V, 25µF 6V. All 3/- each. 100µF 6V, 3/- Paper 0.01, 0.001, 0.002, 0.005µF, all 8d. each. Transistor holders 1/- each, 6 for 5/9, 11/- doz. Ardente T.1065 transformers (page 911-

July), 12/-. Sub-miniature Speakers 1 1/2" round, 25/6; 2" x 3" elliptical, 30/6. Sub-miniature Output Transformers, single-ended or p/p, 12/6. Subminiature Germanium Diodes 1/10. Volume Controls, button type (totally enclosed), 47k and 1MΩ, 2/6; preset skeleton type 5k, 2/6; spindle type 1/2M, 1M, 2M, 4/3 (page 705-May, '58) Ardente Deaf Aid Earpieces E.R.100, with cord and earpiece. Limited number at 13/9. Ardente Catalogue 6d. Transistors: White Spot 14/-; Yellow/Green 7/6; Red Spot 7/-. Ediswan Transistors: XA104 R.F., 18/-; XA103 I.F., 15/-; XB104 A.F., XB102 A.F., 10/-. Pye Goltop Transistors of all types stocked.

### THE TRANSIDYNE RECEIVER

This proved 6-transistor circuit now supplied with  
**NEW EDISWAN TRANSISTORS**  
(as specified by Teletron)  
Complete Kit £11.15.6,  
or less transistors £8.15.6  
FREE—Special printed circuit solder with each kit  
Only genuine Teletron parts. Full details and price list 1/- post free

QUOTATIONS gladly given (S.A.E. please)

**R. FAGELSTON (MAIL ORDER)**

Please add Postage to above prices

46 HARDWICKE ROAD · LONDON N13



Patent No. 748811

Safety first every time with these patented spring-loaded AVO Prodclips.

Cleverly designed for use as insulated prods, they are invaluable for reaching and holding test points which are difficult of access.

Post Free  
**15/-**  
per pair

**AVO LTD** AVOCET HOUSE  
92-96 VAUXHALL BRIDGE RD LONDON SW1  
PC2 VICTORIA 3404 (12 lines)

## TRANSISTOR SUPPLIES

Teletron Transidyne Pocket Transistor Set. All parts £11.10.0. (Post 2/6.)

Mini-7 Transistor Pocket Receiver. Complete kit £9.2.6. (Post 2/6.) Limited supplies.

### BARGAINS

Red Spots 5/-; White Spots 7/6; Green/Yell. 5/9; Ediswan XB104 8/6; XA104 16/-; XA103 14/-; Moving Coil Earpiece (use as miniature speaker) 5/-. Super co-ax. 6d. yard; Var. Air Condenser 365pF 3/-. Subminiature electrolytics (15 volt) 2, 5, 8, 25, 50µF 3/-. Submin. Transformer interstage 5-1, 8-1 7/6.

Morco Reflex Circuit—Best 2 transistor design

Terms: Cash with order. Post extra.  
Send 8d. stamps for our Notes

**MORCO EXPERIMENTAL SUPPLIES**  
8 & 10 Granville Street, Sheffield 2  
Telephone 27461

## Teletron "Tapejak"—£5.9.0

(plus 1/6 post). RF/AF Signal Tracer (Page 831 June issue). Complete kit, with sub-miniature components and latest 2 1/2" plastic speaker (W.B.) £3.13.6. (S.A.E. for list) COAXIAL OFFER. High quality lead 6d yd., 6 yds 2/9, 12 yds 5/-. Sockets 1/-. Solderless plugs 1/3. Outlet Boxes, single 4/6, double 13/6. TRANSMITTING KEYS. With lead and heavy duty jack plug 1/6 (1/3 post). AMPLIFONE KIT. Telephone amplifier (R.C. March). All parts with 2 1/2" speaker £4.17.6. (S.A.E. list). SENSITIVE TRANSISTOR RECEIVER (R.C. Nov. 1958). Complete kit £4.18.9 (S.A.E. list). VOLUME CONTROLS. Long spindle, no switch 2/9; s/p 3/9; d/p 4/6. Most values. MIDGET W/W PRESETS: 1k, 2k, 3k, 3.5k, 5k, 10k, 20k, 25k. All at 2/9.

Alfa Multimeters—as reviewed on page 862 of June issue. 17 ranges, a.c./d.c., volts to 1,200; d.c. current to 300mA; resistance 0-2 Megohms. Price £5.19.6 plus 2/- post and packing. (Inclusive of batteries and test prods).

Microphone Cable: Black p.v.c. single screened: 3 yds 1/9, 6 yds, 3/- 12 yds 5/3. Amplifone Kit: Transistor Telephone Amplifier (R.C. March). All parts with 2 1/2" speaker (S.A.E. list).

## SMALL ADVERTISEMENTS

Readers' small advertisements will be accepted at 3d. per word, including address, minimum charge 2/-. Trade advertisements will be accepted at 9d. per word, minimum charge 6/-.

If a Box Number is required, an additional charge of 2/- will be made. Terms: Cash with order. All copy must be in hand by the 12th of the month for insertion in the following month's issue. The Publishers cannot be held liable in any way for printing errors or omissions, nor can they accept responsibility for the bona fides of advertisers.

## PRIVATE

SPUTNIK SPECIAL. R208, complete and in excellent condition. What offers?—P. Connell, 37 Toorack Road, Wealdstone, Middx. Telephone HAR 5096.

HI-FI OUTFIT. Mullard 3-3, £5; Jason Tuner, £5; BSR UA8 4-speed changer, £4 10s.; Whiteley Prelude cabinet, £4, lot £16. Minibeam Automatch, £3.—17 Harborough Road, Streatham, S.W.16.

FOR SALE. Magnaview power pack, receiver, time-base, spare valves, etc. First reasonable offer.—Telephone ACORN 0262 (London).

FOR SALE. 110 copies *The Radio Constructor* 1950-1959; 112 copies *Practical Television* 1950-1959; offers. 16 relays single, multi-contact, 25s. VCR97 6in, 3BP1 3in, for scopes, complete base shields, 15s. TV tubes 12in Mullard 31/74, Mazda CRM123, etc., 45s. L.O.P. transformers, Cossor 925, £2. Valves, mixed new old, ACTH1, 25L6, Y63, 1D5, 6P28, etc., ad infinitum, 4s 6d. each. S.a.e. enquiries.—O.D.B., 25 Ramshead Approach, Leeds, 14.

FOR SALE. Incomplete tape recorder, with Lane tapedeck, 4 valve push-pull amplifier, power supply, pre-amplifier, bias oscillator, speaker, Denco FM tuner, working but needs finishing mechanically, £15. R1155 with 6V6 output, 717A r.f., £3.—215 Amble-side Drive, Southend. Telephone 65026.

TELEVETT 877 for sale, 12 months old, seldom used and in perfect condition. Consists of Wobblulator, Scope, Pattern Generator, Valve Voltmeter etc., covers Bands 1 and 3. £45 o.n.o.—Green, 80 Victoria Road, Willesden Junction, London, N.W.10.

FOR SALE. Collaro tape pre-amp, complete, £6 10s. Cooper-Smith B.P.L. amplifier, Elac hi-fi speaker kit mounted on contemporary open baffle, would exchange w.h.y.—West, 24 Beechfield Gardens, Romford, Essex.

SELLING OUT. New surplus valves, components. At 3s. 6d. 6AK5, EF91, 6X5; at 5s. 12AT7, 5Y3, 6V6, 6F1; at 6s. 12AU7, 12AX7, 5R4; at 10s. EL38, B7G, B9G valveholders, 6d. Resistors, 1/2 watt 2d. each 1s. 6d. per dozen, 100 assorted 10s. S.a.e. for full lists to—W. Syme, 25 Brown Lane, Heald Green, Cheadle, Cheshire.

FOR SALE. Rogers Junior control unit and Cadet amplifier, perfect, 16 gns. Williamson mains transformer, 35s. B.J. Arm with Goldring 500 head, £2. G.E.C. octagonal twin speaker cabinet, walnut, £9. Hi-Fi News, vols: 2 and 3, 22s. 6d.—Vickers, 9 Brenda Crescent, Thornton, Liverpool, 23.

FOR SALE. Power pack, variable output, transformer 350V, 150mA and l.t.'s, large choke etc. G.E.C. Junior amplifier p.p. with selector, £5. Mullard 3-3 ditto, all unused. H.M.V. pre-war large radiogram cabinet, Murphy television cabinet with doors, both almost unmarked, £8, £4 buyer arranges collection.—Box No. E219

MULTIRANGE TEST METER. Scaled ohms, volts and milliamps, 35s. Hand type crystal microphone, 27s. 6d. 12in hi-fi speaker, £3 15s. All brand new and boxed. Will accept £5 for the lot.—Box No. E218.

## TRADE

VHF/FM front end, 85-102 Mc/s, 10.7 Mc/s i.f. output, new, British, small, compact, unique construction. Earthed grid r.f. stage. High sensitivity. Circuit and data included. Price, excl. valve (ECC85) £2 12s. 3d. plus 2s. postage. Delivered ex-stock. Trade enquiries invited. Dept. E/1 Rotopons Ltd, 54 Bedington Lane, Croydon, Surrey.

1000 AUTO and ELECTRONIC BARGAINS. List 3d.—Automaster, Haymarket, Birkenhead.

AFC KITS FOR FM. Page 213 October issue *The Radio Constructor*. Valve and components, 10s.—5 Burnside Crescent, Chelmsford, Essex.

continued on page 319

## NEW SURPLUS . . . BY RETURN

1L4	5/-	6S6G7M	6/6	DC70	7/6	EZ81	7/-
1R5	6/6	6SH7M	5/-	DET24	12/6	GT1C	7/6
1S5	6/6	6SJ7M	7/6	DF73	7/6	GZ32	11/6
1T4	5/-	6SK7M	6/6	DL70	7/6	HK24G	25/-
2A3	8/6	6SL7GT	6/-	EA50	1/6	KT33C	8/6
2X2	3/6	6SN7GT	4/6	EAB30	10/6	KT66	11/6
3A4	4/6	6SQ7M	7/6	EAC80	10/6	OA2	10/-
3A5	9/-	6ST7	8/6	EAC91	4/6	PCC84	8/6
3Q4	6/6	6V6G	7/6	EAF42	9/-	PCC85	9/-
3S4	8/6	6X4	5/6	EB34	2/-	PCF80	9/-
3V4	7/6	6X5GT	6/6	EB91	4/-	PCF82	9/-
5R4GY	9/6	7B7	8/-	EB33	5/-	PCL82	11/6
5Y3GT	7/6	7C5	8/-	EB41	8/6	PEN25	4/-
6AC7M	5/-	7C6	8/-	EBF80	9/-	PEN46	5/-
6AG5	3/6	7S7	9/6	EBF89	9/6	PL81	12/6
6AK5	5/-	7Y4	8/-	ECC80	12/6	PL82	8/6
6AL5	4/-	12A6M	6/6	ECC82	6/6	PL83	8/6
6AM6	4/-	12AT6	8/6	ECC83	7/6	PY80	7/6
6AQ5	8/6	12AT7	8/6	ECC84	9/6	PY81	8/6
6AT6	7/6	12AU7	6/6	ECC85	9/-	PY82	7/6
6AU6	7/6	12AX7	7/6	ECC80	11/6	PY83	8/-
6BB6	3/6	12AU6	9/-	ECF82	11/6	TT11	4/-
6BA6	7/6	12BE6	8/6	ECH42	9/-	U25	12/6
6BE6	7/6	12C8M	7/6	ECH81	10/-	UAF42	9/-
6BH6	6/6	12K7GT	6/6	ECL80	10/6	UBC41	9/6
6BJ6	7/6	12K8M	12/6	ECL82	11/6	UBF89	9/6
6BR7	11/6	12Q7GT	6/6	EF36	4/-	UCC85	9/6
6BW6	9/-	12SC7M	2/6	EF39	4/6	UCH82	9/6
6C4	4/-	12S17M	5/-	EF41	9/6	UCH81	9/6
6F32	6/6	12SK7M	5/-	EF50	2/6	UF41	9/-
6F6M	5/6	12SQ7M	8/6	EF50(S)	4/6	UF42	8/6
6ISGT	4/6	35L6GT	9/6	EF80	7/-	UF89	9/-
6ISM	5/-	35Z5GT	8/6	EF85	9/6	UL41	9/-
6I6	4/-	35Z4GT	7/6	EF86	11/6	UL84	9/-
6I7G	7/6	42	7/6	EF89	9/-	UY41	7/6
6K7G	3/6	50L6GT	9/6	EF91	4/-	UY85	8/6
6K8G	6/-	80	6/6	EL32	4/-	UABC80	
6K8M	10/6	446A	10/6	EL41	9/6		10/6
6H6M	2/6	830B	15/-	EL84	9/-	VL5631	12/6
6L6G	8/-	866A	15/-	EM80	9/6	VP23	5/-
6L6M	10/-	959	5/-	EY51	10/6	VR150/30	
6Q7G	7/6	1629	4/-	EY86	10/6		7/6
6Q7GT	9/6	5763	10/6	EZ40	7/-	VS70	3/-
6SA7M	7/6	ARP12	5/-	EZ80	7/-	Z77	4/-

Valveholders, moulded. B7G, B8A, B9A, I.O., 9d. each, 7/6 doz; B7G Ptfæ, B9A Micalax, 1/- each, 10/6 doz; screened B7G, B9A, 1/6 each, 15/- doz; B9A Micalax, 1/9 each, 18/- doz. B9A Cer. 2/6 each, 24/- doz. Special prices large quantities.

Fully Shrouded Chokes (U.S.A.) 10H 100mA 9/6. Post 9d. to £1, 1/6 to £2. S.A.E. enquiries

## JOHN ANGLIN

385 CLEETHORPE ROAD GRIMSBY LINCS  
Telephone 56315



# CLYNE RADIO LTD.



Specialists in Equipment for Home Construction  
(Send stamp for complete list)


ALL POST ORDERS AND CORRESPONDENCE TO  
162 HOLLOWAY ROAD · LONDON N7  
NOR 6293/5/7

18 TOTTENHAM COURT RD. LONDON W1  
MUS 5929/0095  
Callers welcome at both branches

## COSSOR KITS!

A unique opportunity to obtain a first class amplifier and/or the latest type VHF/FM receiver at the most reasonable price ever. Limited quantity—order now.

### COSSOR VHF/FM RECEIVER KIT 701K.

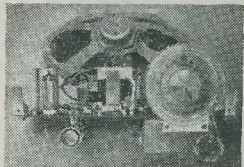

A first class receiver of the latest type for the reception of B.B.C. v.h.f./f.m. programmes, and suitable for use on a.c. or d.c. mains supply, supplied in kit form in manufacturer's original presentation carton, comprising: printed circuit (with all connections clearly marked); 6 valves (UCC85, UF89, UF89, UABC80, UL84, UY85). All necessary components including nuts, bolts, wiring wire, solder, etc., and an excellent quality Goodman 10" x 6" elliptical loudspeaker. A fully illustrated step-by-step instruction book is provided with the aid of which the receiver can be completed in approx. 9-10 hours.

Brand new and complete at only £8.19.6 plus 3/6 p. p. (List price £15 15.0)


**COSSOR AUDIO AMPLIFIER KIT 562K.** This excellent amplifier supplied in kit form in manufacturer's original presentation carton comprising: Pre-assembled printed circuit board; valves (6V4, 6BQ5, EF86); output transformer; two loudspeakers, 4" circular and 10" x 6" elliptical; wiring wire, nuts, bolts, attractive escutcheon and control knobs, mounting brackets and fully illustrated assembly instructions. With negative feedback incorporated, and the high performance loudspeakers provided, a really high quality output is assured. Suitable for use with radio tuners, microphone or gramophone units. For a.c. 200/250V operation. Brand new and complete at only £5.19.6 plus 3/6 p. and p. (list price £9.15.0)

London's leading stockists of valves, components and all electronic equipment, etc. We can supply all your needs! Enquiries welcomed.

**SUPER TRANSISTOR CRYSTAL RECEIVER** with ferrite aerial etc. (as advertised October issue) only 27/6, plus 2/- p. & p. Deaf aid earpiece for above 12/6. Full details, assembly instructions and price list, 1/- post free.
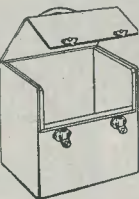
## RECORD PRESENTATION CASES

Beautifully made in various colours, covered in washable leatherette. Strong modern case and carry handle, hinged top, plated clip fasteners. P. & P. 2/6



To hold 30 E.P. 7" records 21/10  
To hold 40 E.P. 7" records 23/9  
To hold 20 10" or 12" records 22/6  
To hold 50 10" records 24/6  
To hold 50 12" records 27/6

## IDEAL FOR XMAS



Sturdy Case  
12/6  
(Ideal record case)

Covered in burgundy and grey washable rexine. Size 8 1/2" x 7 1/2" x 3 1/2" deep. Strong clasp, hinges and carry handle. Ideal for portable radio chassis or transistor set. Can be adapted as a record carrying case to hold eighteen 7" E.P. playing records. P. & P. 2/6

## DEPT. C XI COMPONENTS LTD.

219 ILFORD LANE ILFORD ESSEX  
Telephone: ILF 0295

**VOLUME CONTROLS** 2/6 doz. Assorted volume and tone controls stripped from working chassis. P. & P. 2/-

**FOCUS MAGNET** 9/9. Brand new 38mm. Incorporating picture shift control. P. & P. 1/3


**ELAC FOCUS MAGNET** 12/9. New 35/38mm. P. & P. 1/3

**TUNING CONDENSERS** 2/6. New 2-gang Std size. P. & P. 1/3

**INSULATING TAPE** 1/6. Good quality 75ft x 1/2" wide, in sealed metal tin. P. & P. 9d.

**O.P. TRANSFORMERS** 1/3. Std. size 2-5 ohms. P. & P. 1/-, 20 for £1. P. & P. 3/6

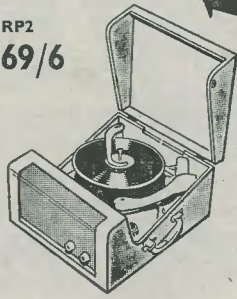**TV AERIAL** 7/9. Fitted with 9ft co-ax cable. For door rod or loft. For B.B.C. P. & P. 1/3



## XMAS SPECIALITY RECORD PLAYER CABINET

A beautifully styled cabinet. Made by a famous manufacturer. In two-tone contrasting colours with clipped lid and carrying handle. Size: 16" x 14 1/2" x 8 1/2" deep. Will take B.S.R. Monarch 4-speed auto-changer and 4" x 7" elliptical speaker and most of the modern portable amplifiers. Carr. & Ins. 4/6

- ★ **BATTERY PLAYER** 6 or 9 volt. 4 speed, 99/6. P. & P. 4/6
- ★ **VALVE BATTERY AMPLIFIER** 39/6 1.5V L.T. 60V or 90V H.T. Suitable for above P. & P. 3/6
- ★ **3 TRANSISTOR AMPLIFIER** 79/6 Ideal for use with player above. 9 volt. P. & P. 3/6

Send Stamp for FREE Catalogue

## SMALL ADVERTISEMENTS

continued from page 317

### TRADE—continued

**CATALOGUE No. 14.** Government surplus and model radio control, over 500 illustrated items. 2s. (refunded on purchase) p.p. 6d. —Arthur Sallis Radio Control Ltd., 93, (E) North Road, Brighton. Regret previous delays, due to printing dispute.

"**MEDIUM WAVE NEWS**" monthly during DX season.—Details from B. J. C. Brown, 196 Abbey Street, Derby.

**JOIN THE INTERNATIONAL S.W. LEAGUE.** Free Services to members including Q.S.L. Bureau, Amateur and Broadcast Translation. Technical and Identification Dept.—both Broadcast and Fixed Stations, DX Certificates, contests and activities for the SWL and transmitting members. Monthly magazine, "MONITOR" containing articles of general interest to Broadcast and Amateur SWLS, Transmitter Section and League affairs, etc. League supplies such as badges, headed notepaper and envelopes. QSL cards, etc., are available at reasonable cost. Send for League particulars. Membership, including monthly magazine, etc., 21s. per annum.—Secretary, ISWL, 86 Barringer Road, London, N.10.

**AT LAST**—at a reasonable cost—quality Hi-Fi in your home by building it yourself under our new system. FREE Brochure from: Dept. RC21, Radiostrutor, 46 Market Place, Reading, Berks.

**LEARN RADIO AND ELECTRONICS** the NEW Practical Way. Very latest system of experimenting with and building radio apparatus—"as you learn". FREE Brochure from: Dept. RC10 Radiostrutor, 46 Market Place, Reading, Berks.

**SERVICE SHEETS** from 1s. each, 100 TV Sheets, 18s. 6d. Cheap valves, components, lists free. Hamilton Radio, 237 Sedlescombe Road North, Hastings, Sussex.

**MORSE CODE TRAINING.** Special courses for Beginners. Full details from (Dept. R.C.) Candler System Company, 52 Abingdon Road, London, W.8.

**PANL**, recognised for many years as the unique one-coat black crackle finish. Brush applied, no baking. Available by post in 1/4 pint cans at 3s. 9d. from G. A. Miller, 255 Nether Street, London, N.3.

"**WORLD RADIO HANDBOOK.**" Copies available, 15s. 6d. inc. post and packing, from ISWL, 86 Barringer Road, London, N.10.

**1,000 INTERESTING ITEMS.** List 3d.—Rogers, 31/33 Nelson Street, Southport, Lancs.

**TECHNICAL WRITING IN ELECTRONICS,** Radio and TV Instruction Books, Service Manuals Brochures, Technical Drawings etc.—F. C. Judd, A.Inst.E., Rotech, 152 Maybank Road, London, E.18. Telephone BUCKhurst 9315.

**HIGH CLASS DUPLICATING,** Electronic Stencil Illustrations, circuits, etc. Sheets or booklets. —Rotech, 152 Maybank Road, London, E.18. Telephone BUCKhurst 9315.

**INCORPORATED** Practical Radio Engineers home study courses of radio and TV engineering are recognised by the trade as outstanding and authoritative. Moderate fees to a limited number of students only. Syllabus of Instructional Text is free. The Practical Radio Engineer, journal, sample copy 2s. 6,000 Alignment Peaks for Superhets, 5s. 9d. Membership and Entry Conditions booklet, 1s., all post free from the Secretary, I.P.R.E., 20 Fairfield Road, London, N.8.

## PROTECT YOUR CAR AT NIGHT

### PHOTOELECTRIC PARKING LIGHT SWITCH

will switch your lights on at dusk—off at dawn, automatically, while you are at work, in bed, or away from home. Controlled by light. Transistorised. Negligible consumption (.008 amp.). Avoid accidents, fines. Save your battery.

Kit of parts ... ..	52/6
Built and tested ... ..	57/6
Instructions only ... ..	1/-

Pat. applied for Money back guarantee

### ST. JOHN'S RADIO

156 ST. JOHN'S HILL SW11 BATtersea 9838

## WELL KNOWN FM TUNER KITS

**COMPLETE KIT:** chassis, dial, all components, etc., ready to assemble. Less valves, £3.15.0; complete with set of valves, £5.5.0. Easy to follow building and wiring plans and instructions, 3/6.

Few Only Left: spare sets of FM coils, 1Fs, R/Det., etc. £1.0.0 per set. S.A.E. for enquiries:

**R.C.R. 89 DERLEY ROAD SOUTHALL MIDD**

Callers Only to:

**R.T.V. 250 Goldhawk Road LONDON W12**

**12V D.C. Magnetic Switch.** Cuts out on 2 amp. overload or dead short. 13/6.

**Famous Make Lightweight Pencil Bit Soldering Iron,** 220/240V, 25W. Indicator light in handle (list price 24/6). Price 16/6.

**Scooter Batteries.** 6V 10 A.H. Hard rubber case. Size 5" x 5" x 1 1/2". Weight 3lb. 15/-.. Also ideal for model use.

**New and Boxed Collaro Conquest 4-speed Record Auto Changers.** 200/250V A.C. £7.4.6.

**Mains Transformers.** Input 200/250. Output tapped 3 to 30V 2A or 5, 11, 17V 5A. Each 24/6.

**F.W. Metal Rectifiers.** 12/6 volt 1A, 7/6; 3A, 13/-; 4A, 17/6; 6A, 27/6.

**Studio "O" P/U Cartridges** 21/-.

**12" Speaker,** separate tweeter in cabinet 22 1/2" x 8" x 13 1/2", £6.15.0.

**Mains Transformer and Rectifier,** giving 12V 1A D.C. output. 19/6.

**Relays.** We hold large stocks. Any contact combination and operating coil voltage supplied from 3/-.

**Key Switches** from 3/-.

**Cossor UHF/FM Kit,** model 701K, £8.19.6.

**Toggle Switches** DPDT 3/6.

**Micro Switches,** Make and Break, 5/6.

**Nickel NiFe Batteries.** 1.2V 2.5A. Size 3" x 2 1/2" x 1 1/2" 6/- or 3 for 16/-.

**Army Morse Keys.** 3/-.

**Light Weight H.R. Phones.** 17/6.

**H.S. Twist Drills.** Set 7. 1 1/2" - 1 1/4" 4/-.

All items post paid, new and guaranteed.

LISTS SENT ON REQUEST

Post orders only to

**THE RADIO & ELECTRICAL MART**  
29 STATION APPROACH, SUDBURY TOWN  
WEMBLEY MIDD



### TRANSFORMERS

Suppliers to B.B.C., I.T.A. and leading radio manufacturers, single or long runs, prompt delivery, home and export.

rewinds to all makes

**H. W. FORREST (TRANSFORMERS) LTD.,**  
Shirley, Solihull, Warwickshire  
Telephone SHirley 2483

**BRASS, COPPER, DURAL,  
ALUMINIUM, BRONZE**  
ROD BAR SHEET TUBE STRIP WIRE  
3,000 STANDARD STOCK SIZES  
No quantity too small List on application

**H. ROLLET & CO LTD**  
6 Chesham Place SW1 SLOane 3463  
Also at Liverpool Birmingham  
Manchester Leeds

Teleprinters, Perforators, Reperforators, Tape Readers, Terminals and V.F. Telegraph multi-channel units: Testing Equipment; Telephone Carriers and Repeaters; Signalling Rectifiers and Relays, Transformers, Transmit and Receive, Filters; Repeating and Retardation Coils; Racks, Relay Bases, Remote control transmitters; British, American, Italian and German Equipment.

**BATEY & CO.,**  
Gaiety Works Akeman Street Tring Herts  
Telephone Tring 2123 and 2310

### B.B.C. - I.T.V. - F.M. AERIALS

**B.B.C. (BAND 1).** Telescopic loft, 19/6. External, S/D, 26/3.  
**I.T.V. (BAND 3).** 3 Element loft array, 24/-, 5 Element, 32/6. Wall mounting, 3 Element, 33/9. 5 Element, 41/3.

**COMBINED B.B.C. + I.T.V.**  
Loft 1+3 Element, 41/3. 1+5 Element, 48/9. Wall mounting, 1+3 Element, 56/3. 1+5 Element, 63/9. Chimney and mast mounting units also available.

**F.M. (BAND 2).** Loft "H", 28/-, 3 Element loft, 52/6. S/D loft, 12/6. External S/D, 26/3. Send 6d. for illustrated lists. C.W.O. or C.O.D. P.P. 2/6. Coaxial cable, 8d. yd. Coaxial plugs, 1/3.  
**K. V. A. ELECTRONICS (Dept. RC)**  
3B Godstone Road Kenley Surrey

### NEW HI-FI PUBLICATIONS

MULLARD AMPLIFIER MANUAL	8/6
MULLARD TAPE PRE-AMP "C"	2/6
QUALITY AMPLIFIERS 7 designs	4/6
JASON FM TUNERS	2/6
MERCURY SWITCHED FM TUNER	2/-

Circuits for the Mullard 3-valve 3-watt amplifier, 2-valve pre-amp. tape amplifier free on request

Quality components and popular alternatives always in stock

52 page catalogue available on request

**J. T. FILMER** 82 DARTFORD ROAD  
DARTFORD KENT  
Telephone Dartford 4057

### H.A.C. THE ORIGINAL SUPPLIERS OF SHORT-WAVE KITS

One valve Super Sensitive All-dry Short-wave Receiver Model "K". Complete kit including valve and chassis 77/- (Other S.W. kits from 25/-) Before ordering call and inspect a demonstration receiver, or send stamped envelope for full specification, catalogue and order form.

**H.A.C. SHORT-WAVE PRODUCTS (DEPT. R)**  
11 OLD BOND STREET LONDON W1

### "GLOBE-KING"

WORLD-FAMOUS KITS AND RECEIVERS

for the Radio Amateur and S.W. Listener. Catalogue Free, enclose stamp for postage. Kits from 79/6 obtainable at your dealers or direct from sole manufacturers

**JOHNSONS (Radio)**  
ST. MARTINS GATE — WORCESTER

### VALVES GUARANTEED

6AM6 3/6, 6BA6 5/6, 6BE6 5/6, 6ALS 3/6, 6J6 3/6, 6X4 5/6, 6C4 3/6, 6BW6 7/6, 6CH6 10/-, 6F33 5/-, 6F13 9/-, 12AT7 5/6, 12AU7 7/-, 12AX7 6/6, 5763 9/6, 85A2 12/6, EF86 11/6, EY51 9/6, EL91 4/-, EC91 6/-, EAC91 4/6, EF92 5/-, R10 17/6, R18 16/-, R17 16/-, N78 10/-, EZ80 7/-, EM80 9/-, EL84 8/6, 1R5 6/-, 1T4 5/-, 1S5 6/-, 3V4 7/6, 6AT6 7/-

### SKILLMAN

79A FRANCHISE STREET WEYMOUTH

### RADIO AMATEURS...

get your Licence in

### Half The Usual Time!

You must be a good Morse operator! A "slap-dash" 12 w.p.m. neither satisfies the authorities, yourself, nor your operator friends. Morse operating is an exacting art unless your training is made simple and is based on sound fundamentals. For this reason, the Candler System was invented to take the "grind" out of Code tuition, turning a tricky subject into a pleasurable pursuit.

★ Send 3d. stamp for the "Book of Facts"

**CANDLER SYSTEM CO**  
(Dept. 55 RC) 52b Abingdon Rd London W8  
Candler System Company Denver Colorado U.S.A.

### Res/Cap Bridge

FOR

### 37/- ONLY

P. & P. 2/-

For checking all types of resistors and condensers  
**BUILT IN 1 HOUR! DIRECT READING!!  
READY CALIBRATED !!!**

Stamp for details of this and other instruments  
**RADIO MAIL** Dept CH Raleigh Mews  
Raleigh Street Nottingham

**INTEREST  
is at 3<sup>3</sup>/<sub>4</sub>%  
per annum**

(There is no deduction for income tax, as this is paid by the Society)



ESTABLISHED 1865

Savings in this old established Building Society combine sound investment with an attractive return

## The Duchess of Kent Permanent Building Society

Member of the Building Societies Association

Shares are in units of £25 each (maximum investment £5,000) . . . BUT, for the smaller saver, Subscription Share accounts may be opened with any sum from 1/- upwards. Interest is payable half-yearly on Fully Paid Shares—credited annually on Subscription Shares—all interest accrues monthly.

For further information apply to Mr. A. Neville Gillman, F.C.A.

**Duchess of Kent Permanent Building Society** 103 Cannon Street London EC4  
Telephone MANSion House 8011

Please send to me, without obligation, free brochure and a copy of the audited statement of accounts. (I understand that I shall not be troubled with circulars or calls by representatives)

Name .....  
(If lady, please state Mrs. or Miss)

Address..... R.C.  
(Please use Block Capitals for both name and address)

## SELRAY PUBLISHING & DISTRIBUTING CO

specialists in RADIO AND ALLIED PUBLICATIONS

**Electronic Gadgets for the Constructor.** By E. N. Bradley. 3s. 6d. Postage 4d.

**The Oscilloscope Book.** By E. N. Bradley. 5s. Postage 5d.

**Television Servicing.** By G. N. Patchett. Vol. 1, 5s. Vol. 2, 6s. Vol. 3, 5s. Vol. 4, 7s. 6d. Postage 5d. each.

**Radio Servicing.** 4 vols. 5s. each. Postage 4d. each.

Vol. 1: Basic Electrotechnology. By G. N. Patchett.

Vol. 2: Intermediate Radio Theory. By G. N. Patchett.

Vol. 3: Final Year Radio Theory. By B. Fozard.

Vol. 4: Fault Finding. By G. N. Patchett.

**Transistor and Crystal Diodes.** By B. R. Bettridge. 5s. Postage 4d.

**Electronic Novelties for the Constructor.** By E. N. Bradley 5s. Postage 4d.

**Radio Control of Models.** By G. Sommerhoff. 5s. Postage 4d.

**Suppressing Radio and TV Interference.** By B. L. Morley. 5s. Postage 5d.

**Television Test Equipment.** By E. N. Bradley. 5s. Postage 5d.

**British Transistor Manual.** E. N. Bradley. 224 pages. 200 diagrams. 12s. 6d. Postage 9d.

**Transistor Circuits for the Constructor.** Nos. 1 and 2. E. N. Bradley. 3s. 6d. each. Postage 4d.

Over 25 Years of Knowledge and Experience in Technical Publications at your disposal

**60 HAYES HILL · HAYES · BROMLEY · KENT · Telephone HURStway 1818**