

PUBLISHED IN CONJUNCTION WITH

THE

RADIO CONSTRUCTOR

★ *Data Book Series*

★ *Radio Reprint Series*

★ *Panel Signs Transfers*

Send stamped addressed envelope for
latest

BROCHURE

giving details of ALL PUBLICATIONS

DATA PUBLICATIONS LTD

57 MAIDA VALE LONDON W9

Telegrams Databux London

Telephone CUNningham 6141/2

Published in Great Britain by the Proprietors and Publishers

Data Publications Ltd 57 Maida Vale London W9

Printed by A. Quick & Co. (Printers) Ltd 125 High Holborn London WC1 England also at Clacton-on-Sea

Obtainable abroad through the following Collets Subscription Service Continental Publishers & Distributors Ltd
William Dawson & Sons Ltd Australia and New Zealand Gordon & Gotch Ltd South Africa Central News Agency
Holland "Radio Electronica"

Registered for transmission by Magazine Post to Canada (including Newfoundland)

NATIONAL HRO ALIGNMENT DATA

Over 1000

VOLUME 13
NUMBER 5
DECEMBER
1959

The RADIO Constructor



RADIO · TELEVISION · AUDIO · ELECTRONICS

A PERSONAL PORTABLE RECEIVER



Described by James Sinclair

Included in this issue

VERY SENSITIVE D.C. NULL INDICATOR
"TRANSITONE" SIMPLE ELECTRONIC ORGAN
COOPER-SMITH STEREO CONTROL UNIT
COMPREHENSIVE TRANSISTOR CHECKER
CAR RADIO 2-WATT TRANSISTOR AMPLIFIER
GOOD QUALITY AUDIO AMPLIFIER

DATA Publications 19

THE MODERN BOOK CO

Servicing Transistor Radios. By L. D'Airo 23s. Postage 1s.

TV Fault Finding. A Data Publication. 5s. Postage 6d.

How to Get the Best out of Your Tape Recorder. By P. J. Guy. 8s. 6d. Postage 6d.

Electronic Hobbyists' Handbook. By R. P. Turner. 20s. Postage 8d.

Quality Amplifiers for A.C. Mains. A Data Publication. 4s. 6d. Postage 6d.

Brimar Valve and Teletube Manual, No. 8. 6s. Postage 9d.

Radio Valve Data. Compiled by "WW". 6th Ed. 5s. Postage 9d.

Mullard Circuits for Audio Amplifiers. 8s. 6d. Postage 1s.

Television Servicing Handbook. By G. J. King. 30s. Postage 1s. 3d.

The All-in-One Tape Recorder Book. By J. M. Lloyd. 12s. 6d. Postage 8d.

Radio Engineering Formulae and Calculations. By W. E. Pannett. 17s. 6d. Postage 8d.

A Beginner's Guide to Radio. By F. J. Camm. 7s. 6d. Postage 6d.

Guide to Mobile Radio. By L. G. Sands. 22s. Postage 9d.

Elementary Telecommunications Examination Guide. By W. T. Perkins. 17s. 6d. Postage 9d.

We have the Finest Selection of British and American Radio Books in the Country

Complete catalogue 6d.

19-23 PRAED STREET (Dept RC) LONDON W2

Telephone PADdington 4185

INTEREST
is at **3 $\frac{3}{4}$ %**
per annum

(There is no deduction for income tax, as this is paid by the Society)



ESTABLISHED 1865

Savings in this old established Building Society combine sound investment with an attractive return

The Duchess of Kent Permanent Building Society

Member of the Building Societies Association

Shares are in units of £25 each (maximum investment £5,000) . . . BUT, for the smaller saver, Subscription Share accounts may be opened with any sum from 1/- upwards. Interest is payable half-yearly on Fully Paid Shares—credited annually on Subscription Shares—all interest accrues monthly.

For further information apply to Mr. A. Neville Gillman, F.C.A.

Duchess of Kent Permanent Building Society 103 Cannon Street London EC4
Telephone MANSion House 8011

Please send to me, without obligation, free brochure and a copy of the audited statement of accounts. (I understand that I shall not be troubled with circulars or calls by representatives)

Name

(If lady, please state Mrs. or Miss)


Address..... R.C.

(Please use Block Capitals for both name and address)



Mullard

CIRCUITS FOR AUDIO AMPLIFIERS

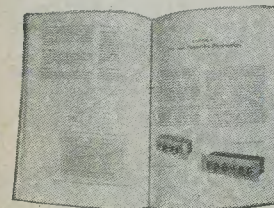

- a book every enthusiast will want!

This new Mullard publication is a practical manual for every audio enthusiast. In addition to describing twelve of the most popular Mullard circuits, it has introductory chapters on many of the theoretical and practical aspects of high quality sound reproduction.

Whether you are interested in disc or tape, monaural or stereo, you will find that "Circuits for Audio Amplifiers" gives just the sort of information you need.

This informative book costs only 8/6d. The demand for it is high, so get your copy now from your local radio dealer.



MULLARD LTD • MULLARD HOUSE • TORRINGTON PLACE • LONDON • W.C.1
MVM 422A

Here are our NEW kits designed to the same high technical standard

HI-FI FM TUNER



This model is available as two units which, for your convenience, are sold separately. They comprise a Tuner Unit, Model FMT-4U (£32.0 including Purchase Tax) with I.F. output of 10.7 mc/s and an Amplifier Unit complete with attractively styled cabinet, power supply and valves, Model FMA-4U (10.10.6) making a total cost for the equipment of £13.12.6.


ELECTRONIC SWITCH Model S-3U (Oscilloscope Trace Doubler)



This extremely useful low-priced device will extend the application of your single-beam oscilloscope by enabling it to give simultaneous traces of two separate and independent signals. £9.18.6

AMATEUR TRANSMITTER Model DX-100U

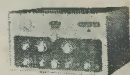This is the most popular Amateur transmitter in the world and requires no introduction to "Hams" the world over. Covers all bands from 160-10 metres. Self-contained, including power supply, Modulator and V.F.O. £78.10.0



DIRECT READING CAPACITANCE METER Model CM-1U.

Full-scale ranges of 100 micro-microfarad, 1,000 micro-microfarad, 0.01 microfarad and 0.1 microfarad. Easily built in a few hours. £14.10.0

TRANSCRIPTION RECORD PLAYER, Model RP-1U



This new RP594 Collaro Transcription Unit has a Ronette Stereo Pick-up, giving excellent results on stereo or mono (33, 45 or 78 r.p.m.) discs. Complete with furniture-grade wooden plinth. £12.10.0


THE "GLOUCESTER". It will house Tape Deck and/or Record Player—as well as FM Tuner and Stereo Amplifier, and storage space is provided for records, tapes and power amplifiers. Furthermore, to meet the needs of those with whom room-space is an overriding consideration, provision is made in the cabinet ends for matched Hi-Fi Stereo Speaker Systems.

- Mk. 1. Tape Deck or Record Player. £15.18.6
- Mk. 2. Tape Deck and Record Player. £17.8.6




THE "COTSWOLD"

THE "COTSWOLD". This is an acoustically designed enclosure 26" x 23" x 15½" housing a 12" bass speaker with 2" speech coil, elliptical middle speaker together with a pressure unit to cover the full frequency range of 32-20,000 c/s. Capable of doing justice to the finest programme source, its polar distribution makes it ideal for really Hi-Fi Stereo. Delivered complete with speakers, cross-over unit, level control, Tygan grille cloth, etc. All parts pre-cut and drilled for ease of assembly and left "in the white" for finish to personal taste. £19.18.6

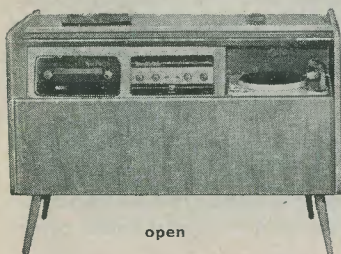

open


THE "GLOUCESTER"

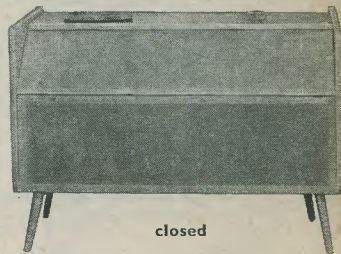

closed

DAYSTROM LTD DEPT. RC12 GLOUCESTER ENGLAND

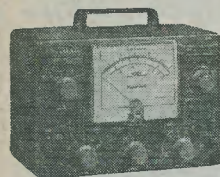Easily-built instruments of excellent quality at much lower cost



AG-9U

AUDIO GENERATOR: AG-9U. 10 volts, 10 c/s to 100 kc/s pure sine-wave. Switch-selected frequencies/attenuation. £19.3.0



USP-1

HI-FI SPEAKER SYSTEM: SSU-1. Ideal twin speaker/ducted-reflex cabinet for stereo/mono. in average room (left "in the white"). Legs £1.7.0 extra. £10.5.6

HI-FI STEREO 6 WATT AMPLIFIER: S-33. Low priced but high quality; less than 0.3% distn at 2½ watts per channel. £11.8.0

TRANSISTOR PORTABLE: UXR-1. In elegant solid hide case, with golden relief. Six transistors, dual-wave, fine reproduction, very easy to build. £15.18.6

HI-FI STEREO BOOSTER: USP-1. Input of 2 to 20mV gives output adjustable from 20mV to 2V. Negligible distn. Also suitable as a high gain monaural amplifier. £5.19.6

HI-FI STEREO 16 WATT AMPLIFIER: S-88. Superb reproduction for the man who wants the best in Hi-Fi. Only 0.1% distortion at 6 W/chnl. Many special features. £25.5.6

5" OSCILLOSCOPE: O-12U. "Y" sensitivity 10mV/cm., 3 c/s to over 5 Mc/s. Rise time, 0.08 µsecs or less. Sweep, 10 c/s to 500 kc/s. Electronically stabilised. £34.15.0

VALVE VOLTMETER: V-7A. The World's largest-selling VVM. Measures Volts to 1500 (DC & RMS) and 4,000 pk. to pk.; Resistance 0.1Ω to 1,000MΩ D.C. Sensitivity: 7,333,333 ohms per volt. £13.0.0

(Following models not illustrated)

CAPACITANCE/RESISTANCE BRIDGE C-3U. Measures capacity, 10pF to 1,000µF, Resistance, 100Ω to 5MΩ; Pwr. Fctr. £7.19.6

"HAM" TRANSMITTER: DX-40U. 75 W. CW; 60 W. pk. c/c phone; 40 W. into Aerial. £29.10.0

VARIABLE FREQUENCY OSCILLATOR: VF-1U. 10V output; covers 10 to 160 metres. £10.12.0


AUDIO WATTMETER: AW-1U. Up to 25 W. continuous, 50 W. intermittent. £13.18.6

AUDIO VALVE-MILLIVOLTMETER: AV-3U. 1mV to 300V A.C. 10 c/s to 400 kc/s. £13.18.6


COMPLETE MATCHED STEREO OUTFIT

★ comprising record player, amplifier and twin speaker systems. £42.10.0 ★

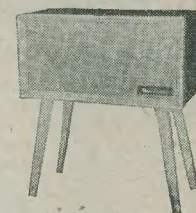All prices include free delivery in U.K. Deferred terms available on orders above £10.



SSU-1

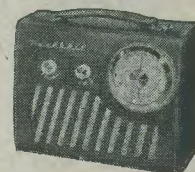

UXR-1



V-7A



S-33

★ SEND THIS COUPON NOW FOR FURTHER INFORMATION

(Please write in BLOCK CAPITALS)

NAME _____

ADDRESS _____

Without obligation please send me (Tick here)

BRITISH HEATHKIT CATALOGUE

FULL DETAILS OF MODEL(S)

DAYSTROM LTD DEPT. RC12 GLOUCESTER . ENGLAND

A member of the Daystrom Group, manufacturers of the WORLD'S LARGEST-SELLING ELECTRONIC KITS

LASKY'S RADIO

THE LARGEST AND MOST COMPREHENSIVE
STOCKS FOR ALL CONSTRUCTORS AND
HIGH FIDELITY ENTHUSIASTS

TAPE DECK OFFERS

Latest B.S.R. "MONARDECK." Single speed, 3½ i.p.s. Takes 5½" spools. Simple controls, £9.19.6.

Latest COLLARO Studio Tape Transcriber, 3-spd., 1½, 3½ and 7½, fitted with digital counter. Takes 7" spools. Push-button controls, £15.19.6.

COLLARO Mk. IV Tape Transcriber, 3-spd., fitted digital counter, £17.19.6.

Carr. and Insur., all Tape Decks, 12/6, Tape extra.

TURRET TUNER SCOOP

12-channel Tuner. New and unused. Complete with PCC84 and PCF80 valves and coils for 5 Band I channels and channels 8, 9, 10 Band III. I.F. 33-38 Mc/s. Limited number. Today's value over £7.

Lasky's Price 49/6 Post 3/6.

FINE GIFT FOR A BOY

The "DIODEON"—a highly efficient 2-stage receiver using crystal diode detector and transistor in cascade. Covers 200-500 metres (medium wave) Chassis shows pictorially all components and connections. Built in minutes! Complete parcel including two U16 batteries, 25/10 post free.

EARPHONES. High imp., 14/6. Low imp., 7/6. Post 1/6.

SEND FOR OUR NEW COMPONENTS CATALOGUE

The finest ever produced for the "ham" and hi-fi fan. 100 pages, 8½" x 5½", copiously illustrated.

PRICE 2/- Post 6d.

Our latest "BARGAIN BULLETIN" free with each copy.

207 EDGWARE ROAD, LONDON, W.2.

Few yards from Praed Street. PADDINGTON 3271/2

42 TOTTENHAM COURT ROAD, W.1.

Nearest station Goodge Street MUSSEUM 2605

Both addresses open all day Saturday, close 1 p.m. Thurs.

Please address Mail Orders and enquiries to Lasky's (Harrow Rd) Ltd, Dept. RC, 207 Edgware Road, London W2

4-Spd. AUTO-CHANGERS

Brand new in maker's cartons.

Latest B.S.R. UA12, wired for STEREO and complete with stereo cartridge.

£8.19.6

Ditto, monaural cartridge, £7.19.6.


B.S.R. type UA8, complete with latest "ful-fi" pick-up. £6.19.6. Post 5/-.

Ditto, wired for STEREO, and complete with stereo cartridge, £7.19.6.

COLLARO, complete with Studio crystal p.u. and sapphire stylus, £7.19.6. Post 3/6.

GARRARD RC121 Mk. II, with plug-in head. £10.19.6

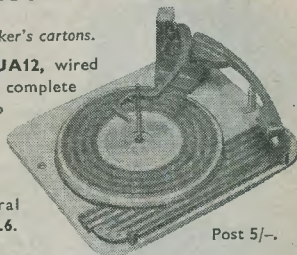Ditto, wired for STEREO and with stereo cartridge. £11.19.6. Post 5/-.



Post 5/-.

TRANSISTORS

AUDIO P.N.P. Junction type (yellow/green) 7/6; 3 for 20/-; 6 for 37/6. Post free.

R.F. P.N.P. Junction type (yellow/red) 15/-; 3 for 40/-; 6 for 75/- Post free. Special prices for larger quantities.

TS/1. Audio P.N.P. Transistor, well known make 5/-.

SPECIAL OFFER. Set of 7 latest types EDISWAN Transistors: XA/101, XA/102, two XB/102, XB/103, two matched XC/101. Price 79/6.

All other makes and types. List post free or see our new Components Catalogue.




BUILD THE CRYSTAL CONTROLLED CALIBRATOR

with an
authentic

Jason Kit

Designed by G. G. Blundell and described in the November issue (page 274), the Crystal-Controlled Calibrator C.C.10 enables signal generators from 100 kc/s to 200 Mc/s to be accurately checked by a system of audio marker "pips" with a basic accuracy of 0.01%. Self-powered unit. Complete kit with valves, case and loud-speaker.

£16.19.0

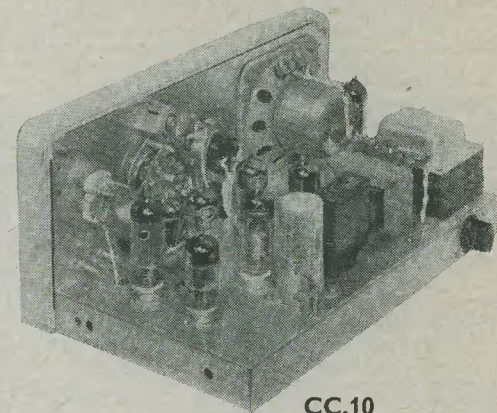

CC.10

OTHER KITS IN THE JASON PROGRAMME

AUDIO GENERATOR AG.10

Excellent stability with output held constant over entire band. Tunes from 10 c/s to 100 kc/s over four switched stages and two scales. Switch for square or sine wave. Square wave rise time less than 2 microseconds. at all frequencies. Min. calibrated output 100mV. With case, valves and meter. £14.5.0

WOBBULATOR W.11

Enables FM signals, IF signals for AM sets and TV sound and vision channels to be correctly aligned. RF circuits may also be aligned from the 40-70 Mc/s output, the second and third harmonics of which serve for Bands II and III respectively. Return trace is blanked when using a 50 c/s sine wave sweep frequency to provide a reference base line not found on most commercial instruments. £14.15.0. (Built £19.10.0.)

OSCILLOSCOPE OG.10

Push-pull scan on X and Y plates with an X bandwidth from 10 c.p.s. to 1.5 Mc/s, ±1dB. Sensitivity—10mV/cm. As described in The Radio Constructor exact to spec. with valves and Mullard C.R.T. kit. £22.10.0.

STABILISED POWER PACK PP.10M


175mA at 300V Mains variation of ±10% produces output charge of less than 0.15% Ripple less than one millivolt. Available with or without meter. Polarity change switch. With valves, meter and case, £22.10.0.

Radio Hobbies Exhibition, Stand 14, Royal Horticultural Old Hall, Nov. 25-28th.

Details of the above instruments and others in the Jason range, including audio and radio units gladly sent on request. Please quote this journal when writing.

THE JASON MOTOR & ELECTRONIC COMPANY

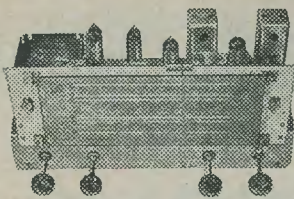3-4(E) GREAT CHAPEL ST. OXFORD ST. LONDON W1 Telephone GERrard 0273/4



1959 RADIOGRAM CHASSIS

THREE WAVEBANDS S.W. 16 m-50 m. M.W. 200 m-550 m. L.W. 800 m-2,000 m. FIVE VALVES LATEST MULLARD ECH81, EF89, EBC81, EL84, EZ80 12 month Guarantee. A.C. 200/250V, 4-way switch. Short-Medium-Long-Grass. A.V.C. and negative feedback. 4.2 watts. Chassis 13 1/2" x 5 1/2" x 2 1/2". Glass dial, horizontal or vertical, size 10" x 4 1/2", 2 pilot lamps. Four knobs, walnut or ivory, aligned and calibrated. Chassis isolated from mains. Leaflet S.A.E.

BRAND NEW £9.10.0 Carr. 4/6
 TERMS: Deposit £5.5.0 and 5 monthly payments of £1
MATCHED SPEAKERS: 8" 17/6. 10" 25/-, 12" 30/-
 New 6V AM/FM model. £18.19.6

LATEST "E.M.I." 4 SPEED SINGLE RECORD PLAYER

Acos 73 Hi-Fi Stereo and Normal Xtal Pick-up for 7", 10" and 12" records Silent Motor, Heavy Turntable
 Special offer **£6.19.6** post 3/6

BUILD THIS REPRODUCER BARGAIN SPECIAL SINGLE PLAYER KIT

COLLARO 4-speed Gram-Pick-up Unit £4.10.0
 Handsome portable case 17 1/2" x 13 1/2" x 7" with room to play 12" records £2.5.0
 Ready built 3-watt amplifier with two valves and 7" ellip speaker, printed circuit £3.12.6
 or **£9.15.0** complete kit post free

I.F. TRANSFORMERS 7/6 pair

465 kc/s slug tuning miniature can 2 1/2" x 1" x 1". High Q and good band width. By Pye Radio. Data sheet supplied.
 Wearite M800 Midget I.F.S. 465 kc/s 12/6 pair
 Wearite 550 Standard I.F.S. 465 kc/s 12/6 pair

New boxed VALVES 90-day Guarantee

1R5	8/6	16K8G	8/6	EA50	1/6	EZ80	8/6
1S5	8/6	16L6	10/6	EABC8010/6	1/6	E1148	1/6
1T4	8/6	6N7M	7/6	EB91	6/6	HABC80	12/6
2X2	2/6	6Q7G	10/6	EBC33	8/6	HVR2A	7/6
3S4	8/6	6SA7	10/6	EBC41	10/6	MU14	10/6
3V4	8/6	6S17M	10/6	EBF80	10/6	P61	6/6
5U4	8/6	6SN7	8/6	ECC84	12/6	PCCR84	12/6
5Y3	8/6	6V6G	7/6	ECF80	11/6	PCC80	11/6
5Z4	10/6	6X4	7/6	ECH42	10/6	PCF82	11/6
6AM6	8/6	6X5	7/6	ECL80	12/6	PCL82	11/6
6B8	5/6	757	10/6	ECL82	12/6	PEN25	6/6
6BE6	7/6	12AT7	10/6	EF39	7/9	PL82	10/6
6BH6	10/6	12AU7	9/6	EF41	10/6	PY80	8/6
6BW6	10/6	12AX7	9/6	EF50	5/6	PY81	10/6
6D6	7/6	12BE6	9/6	EF50	8/6	PY82	8/6
6F6	7/6	12K7	8/6	Sylv.		SP61	5/6
6H6	3/6	12Q7	8/6	EF80	10/6	UBC41	10/6
6I5	6/6	35L6	9/6	EF92	5/6	UCH42	10/6
6I6	7/6	35Z4	9/6	EL32	5/6	UF41	10/6
6I7G	8/6	80	10/6	EL84	10/6	UL41	10/6
6K6GT	6/6	807	6/6	EY51	12/6	UY41	8/6
6K7G	5/6	954	1/6	EZ40	8/6	UZ22	10/6

B.B.C. Pocket Transistor. M.W. & L.W. Radio Kit 32/6. 'Phones 7/6. Ardente deaf aid earpiece with special lead and plug 15/-.

Our written guarantee with every purchase

C.R.T. ISOLATION TRANSFORMERS

For Cathode Ray Tubes having heater cathode short circuit and for C.R. Tubes with falling emission, full instructions supplied. Type A. Low leakage windings. Optional 25% and 50% boost on secondary: 2V, or 4V, or 6.3V, or 10.3V, or 13.3V, with mains primaries, 12/6. Our Latest Superior Product. Mains Input Type A2. High quality low capacity 10-15pF. Optional boost 25%, 50%, 75%, 16/6 each. Type B. Mains input. Low capacity. Multi output 2, 4, 6.3, 7.3, 10 and 13V. Boost 25% and 50%. This transformer is suitable for all TV tubes. 21/- each.

RESISTORS. Preferred values. 20% 10 ohms to 10 meg. 1/4W 4d., 1/2W 4d., 1W 6d., 1 1/2W 8d., 2W 1/-, HIGH STABILITY. 1/4W 1/2-, 2/-. All preferred values 100Ω-10MΩ. Ditto 5% 100Ω-5MΩ 9d. each.
 5 watt }
 10 watt }
 15 watt }

WIRE-WOUND RESISTORS 1/3 1/6 2/-
 15,000 ohms-50,000 ohms, 5W, 1/9; 10W, 2/3.
WIRE-WOUND POTS 3W Lab. Colvern, etc. Pre-set min. TV type. Standard size Pots, 2 1/2". Knurled slotted knob. Spindle, high grade. All values, 100 ohms to 50k, 3/- each, 30k, 50k, 4/-, 6/6; 100k, 7/6. Ditto 1/4W Carbon Track W/W EXT. SPEAKER CONTROL 10Ω, 3/-

MAINS TRANSFORMERS-200/250 AC
STANDARD 250-0-250, 80mA, 6.3V tapped 4V 4A, 22/6
 Rectifier 6.3V 1A tapped 5V 2A and 4V 2A 22/6
 Ditto 350-0-350 10/6
MINIATURE. 200V 20mA, 6.3V 1A 15/6
MIDGET. 250V 45mA, 6.3V 2A 19/6
SMALL. 250-0-250V 100mA, 6.3V 3.5A 17/6
STANDARD. 250-0-250, 65mA, 6.3V 3.5A 17/6
HEATER TRANS. 6.3V 1 1/2A 7/6
 Ditto tapped sec. 2, 4, 6.3V 1 1/2A 8/6
 Ditto, sec. 6.3V 3A 10/6
 Mullard "510" Osram "912" 300-0-300, 120mA, 6.3V 4A c.t., 6.3V 2A tapped 5V 38/6

O/P TRANSFORMERS. Heavy duty 50mA, 4/6. Multi-ratio push-pull, 7/6. Miniature 3V4, etc., 4/6. Small pentode, 4/6. Hygrade push-pull 7 watts, 15/6. Heavy duty 10/20W 6k or 8k c.t., 30/-.
L.F. CHOKES 15/10H 60/65mA, 5/-; 10H, 85mA, 10/6; 10H 150mA, 14/-.

CRYSTAL MIKE INSERT by Acos 6/6 Precision engineered. Size only 1 1/2" x 3/8" **ACOS CRYSTAL HAND or DESK MIKE, 35/-**

ALADDIN FORMERS and cores. 1/2" 8d., 3/8" 10d. 0.3" FORMERS 5937 or 8 and cans TV1 or 2. 3/8" sq. x 2 1/2" or 3/8" sq. x 1 1/2", 2/- with cores.
SLOW MOTION DRIVES. Epicyclic ratio 6-1, 2/3. TYANA. Midget Soldering Iron. 230V 40W, 16/9.
REMPLOY INSTRUMENT IRON, 230V 25W, 17/6.
MAINS DROPPERS. 3" x 1 1/2". Three adj. sliders, 0.3A, 750 ohms, 4/3; 0.2A, 1,000 ohms, 4/3.
LINE CORD. 0.3A 60 ohms per foot, 0.2A 100 ohms per foot, 2-way, 6d. per foot; 3-way, 7d. per foot.
MIKE TRANS. 50:1, 3/9; 100:1, potted, 10/6.
LOUDSPEAKERS. P.M. 3 ohm. 5", Rola 17/6; 6" x 4" Rola, 18/-; 4" Hi-Fi Tweeter, 25/-; 8" Plessey, 19/6; 6 1/2" Goodmans, 18/6; 10" R.A., 30/-; 12" Plessey, 30/-; 10" x 6" R.A., 27/6; 12" Baker 15W 3 ohm or 15 ohm models, 105/-; Stentorian HF1012 10", 95/-.
CRYSTAL DIODES. G.E.C., 2/-; GEX34, 4/-.
40 CIRCUITS FOR GERMANIUM DIODES, 3/-.
H.R. HEADPHONES 4,000 ohms, brand new, 16/6 pr.
SWITCH CLEANER FLUID, squirt spout, 4/3 tin.
TWIN GANG CONDENSERS. 365pF, miniature. 1 1/2" x 1 1/2" x 1 1/2", 10/-; 0.0005 standard with trimmers, 9/-; less trimmers, 8/-; Midget, 7/6; 50pF single, 2/6.
SHORT WAVE Single 75pF, 100pF, 160pF, 7/- each.
TUNING AND REACTION CONDENSERS. 100pF, 300pF, 500pF, 3/6 each, solid dielectric.

HIGH GAIN TV PRE-AMPLIFIERS BAND I B.B.C.—See page 852 June issue

Tuneable channels 1 to 5 Gain 18dB. ECC84 valve. Kit price 29/6 or 49/6 with power pack. Details 6d.

BAND III I.T.A.—Same prices

Tuneable channels 8 to 13. Gain 17 dB ECC84 valve.

Volume Controls Midget size. Long spindles. Guaranteed 1 year. All values 5,000 ohms to 2 Meg. No Switch D.P. Switch 3/- 4/9 Linear or Log Tracks
80Ω Coaxial Cable Post 1d. per yard Semi-air spaced Polythene Ideal Band III 6d yd. Losses cut 50% FRINGE QUALITY Air spaced Coaxial 1/- yd.

Coaxial Plugs 1/- Lead Socket 2/-
 Panel Sockets 1/- Outlet Boxes 4/6
 Balanced Twin Feeder, per yd 6d., 80Ω or 300Ω.
 Twin Screened Balanced Feeder, 1/6 yd, 80 ohms. Trimmers. Ceramic 30, 50, 70pF, 9d.; 100pF, 150pF, 1/3; 250pF, 1/6; 600pF 750pF, 1/9; Philips, 1/- each. **BLACK CRACKLE PAINT.** Air drying, 3/- tin. **P.V.C. CONN. WIRE,** 8 colours, single or stranded, 2d. yd. Sleeving 1, 2mm, 2d., 2, 3 mm, 3d., 6 mm, 5d. yd. **NEON MAINS TESTER SCREWDRIVERS,** 5/-, **SOLDER RADIOGRADE,** 4d. yard 1 1/2 lb 2/6.

Aluminium Chassis. 18 s.w.g. Plain, undrilled, 4 sides, riveted corners, lattice fixing holes, 2 1/2" sides. 7" x 4", 4/6; 9" x 7", 5/9; 11" x 7", 6/9; 13" x 9", 8/6; 14" x 11", 10/6; 15" x 14", 12/6; 18" x 16" x 3", 16/6.

Miniature Contact Cooled Rectifiers. 250V 50mA 7/6; 250V 85mA, 9/6. Selenium Rect. 300V 85mA, 7/6. Coils. Wearite "P" type, 3/- each. Osmor Midget "Q" type, adj. dust core, from 4/- each. All ranges. **Teletron D.W.R. L. & Med. T.R.F.** with reaction, 3/6. **Ferrite Rod Aerials.** M.W., 8/9; M. & L., 12/6. **T.R.F. Coils A/HF, 7/- pair. H.F. Chokes, 2/6.** **Speaker Fret.** Gold cloth, 17" x 25", 5/-; 25" x 35", 10/-; Tygan, 4" 6" wide, 10/- ft; 2" 3" wide, 5/- ft. Samples, S.A.E.

Condensers. 0.001μF 7kV T.C.C., 5/6; ditto 20kV, 9/6; 0.1μF 7kV, 9/6; 100pF to 500pF Micas, 6d.; Tubular 500V 0.001 to 0.05, 9d.; 0.1, 1/-; 0.25, 1/6; 0.1/350V, 9d.; 0.5, 1/9; 0.01/2,000V, 1/9; 0.1/2,000V, 3/6. **Ceramic Condensers.** 500V 0.3pF to 0.01μF, 9d. **Silver Mica.** 10% 5pF to 500pF, 1/-; 600pF to 3,000pF, 1/3; close tolerance (plus or minus 1pF), 1.5pF to 47pF, 1/3; ditto 1% 50pF to 815pF, 1/9; 1,000pF to 5,000pF, 2/-.
NEW ELECTROLYTICS FAMOUS MAKES

TUBULAR	TUBULAR	CAN TYPES
1/350V 2/-	64/350V 5/6	8/500V 3/-
2/450V 2/3	100/25V 2/-	16/500V 4/-
4/450V 2/3	250/25V 2/6	32/350V 4/-
8/450V 2/3	500/12V 3/-	100/270V 5/6
8/500V 2/9	8+8/450V 4/6	2,500/3V 4/-
16/450V 3/6	8+8/500V 5/-	6,000/6V 5/-
16/500V 4/-	8+16/450V 5/-	32+32/350V 4/6
32/450V 5/6	8+16/500V 5/6	50-50/350V 7/-
25/25V 1/9	16+16/450V 5/6	64+120/275V 7/6
50/25V 2/-	32+32/500V 4/6	64+120/350V 11/6
50/50V 2/-	32+32/500V 7/6	100+200/275V 12/6

Full Wave Bridge Selenium Rectifiers. 2, 6 or 12V 1 1/2A, 8/9; 2A, 11/3; 4A, 17/6. Free charger circuit. **Charger Transformers.** Tapped input 200/250V for charging at 2, 6 or 12V 1 1/2A, 15/6; 2A, 17/6; 4A, 22/6.

LONG PLAY "GEVAERT GEVASONOR" Plastic tape 50% extra 1,700ft 7" reel, 35/-; 850ft 5" reel, 21/-; MSS 225ft, 3" reel, 7/6. Spare reels, 3/-.
SUPERIOR 1,200ft plastic tape, 24/-; 7" plastic reel. 600ft plastic tape on 5" plastic reel, 15/-.
LONG PLAY 1,200ft, 5 1/2" reel, 28/-.
INSTANT bulk tape eraser, and Head Defluxer, 200/250V a.c., 27/6.

BRAND NEW AND BOXED Model UA8 OUR PRICE £6.19.6

STEREO MODELS UA8 £7.19.6 UA12 £10.10.0

★ COLLARO ★
HI-FI ATUOCHANGER £7.19.6
 4 SPEEDS—10 RECORDS
 or with Cabinet, Amplifier and Speaker
OUR PRICE £11.19.6 Carr. 5/6

★ GARRARD 4-SPEED RECORD CHANGERS RC121/D MK II MODELS ★
 With Plug-in Normal Head £10.10.0
 Stereo Head £2 extra

AUTOCHANGER ACCESSORIES
 Suitable player cabinets (uncut boards) 49/6
 Amplifier player cabinets with cut boards 63/-
 2-valve amplifier and 6 1/2" speaker for above 79/6
 3-valve amplifier and 6 1/2" speaker for above 95/-
 Wired and tested ready for use

★ GARRARD 4-SPEED SINGLE RECORD PLAYER 4SP ★
£7.10s. AUDIO PERFECTION POST FREE
MODEL TA MK 11 £8.10.0 { Stereo Heads £2 extra.
MODEL 4 HF £18

Wavechange Switches. 2 p. 2-way, 3p. 2-way, short spindle, 2/6; 5p. 4-way 2 way, long spindle, 6/6; 2 p. 6-way, 4 p. 2-way, 4 p. 3-way, long spindle, 3/6; 3 p. 4-way, 1 p. 2-way, long spindle, 3/6; wavechange "MAKITS." 1 wafer, 8/6; 2 wafer, 12/6; 3 wafer, 16/-; 4 wafer, 19/6; 5 wafer, 23/-; 6 wafer, 26/6.
Toggle Switches, s.p., 2/-; d.p., 3/6; d.p.d.t., 4/-.

JASON FM TUNER COIL SET, 26/-. H.F. coil, aerial coil, oscillator coil, two i.f. transformers 10.7 Mc/s, detector transformer and heater choke. Circuit and component book using four 6AM6, 2/6. **Complete Jason FM Kit,** with valves and Jason Chassis with calibrated dial, £6.15.0, post free.

Valveholders. Pax. int. oct., 4d. EA50, EF50, 6d. B12A, CRT 1/3. Eng. and Amer. 4, 5, 6 and 7 pin, 1/- **MOULDED Mazda** and int. oct., 6d., B7G, B8A, B8G, B9A, 9d. B7G with can, 1/6. B9A with can, 1/9. **Ceramic, EF50, B.G. B9A,** int. oct., 1/-; B7G, B9A Cans, 1/- each.

TV Fault Finding, 5/-. **Quality Amplifiers, 4/6.** **Radio Valve Guide.** Books 1, 2 or 3 5/- each **TRANSISTORS.** Ediswan Audio XB102, 10/- R.F. XA103, 15/-; XA104, 18/-; OC71, 7/6. **Sub-miniature Electrolytics (15V),** 1μF, 2μF, 4μF, 5μF, 8μF, 25μF, 50μF, 3/-.

TELETRON POCKET RADIO Transidyne Superhet Six 6" x 4" x 1 1/2"
 T.C.C. Printed Circuit, internal Ferrite aerial, Rola loudspeaker push-pull output. All parts, cabinet, 6 Ediswan or Mullard transistors.
£11.19.6 Details 9d.

RADIO COMPONENT SPECIALISTS 337 WHITEHORSE ROAD WEST CROYDON Catalogue 1/6 Telephone THO 1665

48 hour postal service 1/-, over £2 post free. C.O.D. 1/6 (Export welcome. Send remittance and extra postage)

NEW! DO-IT-YOURSELF TRAINING TECHNIQUE in RADIO & ELECTRONICS

You LEARN while you BUILD...

SIMPLE...PRACTICAL...FASCINATING...

ANNOUNCING—after many years of highly successful operation in the U.S.A. and in Europe—the latest system in home training in electronics is now introduced by an entirely new British training organisation.


AT LAST—a comprehensive and simple way of learning—by practical means—the basic principles of radio and electronics, with a minimum of theory.

YOU LEARN BY BUILDING actual equipment with the components and parts which we send you. You advance by simple steps using high quality equipment and performing a whole series of interesting and instructive experiments. No mathematics!

INSTRUCTION MANUALS and our teaching staff employ the latest techniques for showing clearly how radio works in a practical and interesting manner. You really have fun whilst learning! And you end by possessing a first rate piece of home equipment with the full knowledge of how it operates and—very important—how to service and maintain it afterwards. A full library of magnificent illustrated textbooks is included with the courses.

IN FACT for the "Do-it-Yourself" enthusiast, the hobbyist or those wanting help with their radio career training, or to set up their own full or part-time servicing business—then this new and exciting instructional system is exactly what is needed and it can all be provided at very moderate cost. Easy payments available. Post the coupon now, for full details. There is no obligation of any kind.

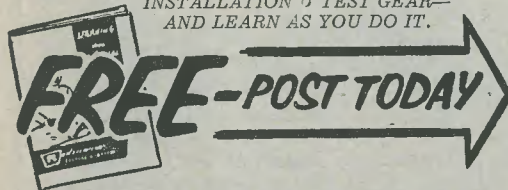
BUILD YOUR OWN: • RADIO EQUIPMENT • HI-FI INSTALLATION • TEST GEAR—AND LEARN AS YOU DO IT.




RADIOSTRUCTOR
BRITAIN'S LEADING RADIO TRAINING ORGANISATION.

LOTS OF INSTRUCTIVE EXPERIMENTS AT HOME!



Power supply circuits

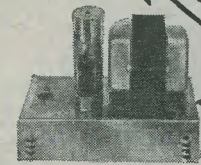


Test equipment supplied

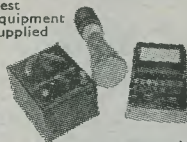

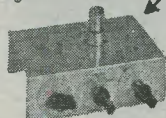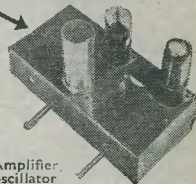Amplifier, oscillator and detector circuits



Basic 1st stage receiver

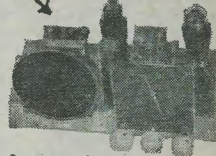

Servicing of commercial receivers


No Mathematics!

To: RADIOSTRUCTOR (Dept. G31)
46 Market Place, Reading, Berks.

Please send full details of your Radio Equipment Courses without any obligation to:

Name.....
Address.....
BLOCK CAPS PLEASE
(802) We do not employ representatives 12.59

Touch-down!

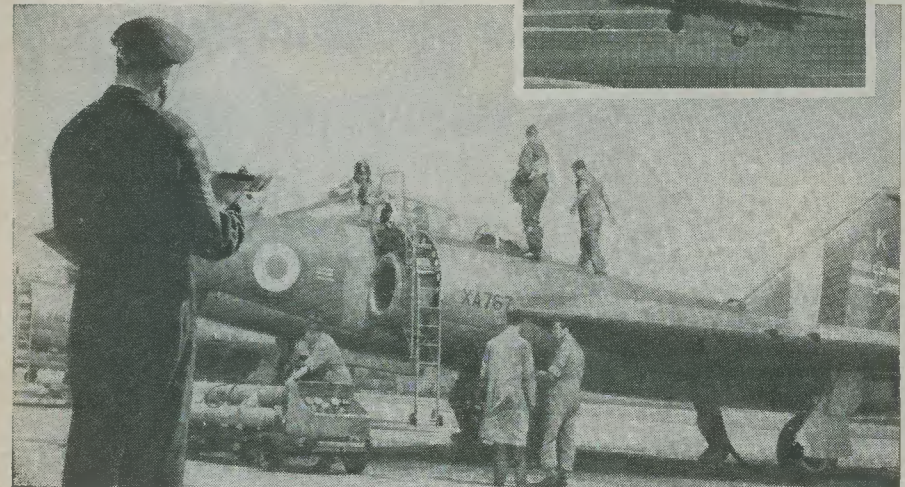

7 minutes to go!

Their sortie completed—two Javelins return—only two aircraft—only four men—but it takes a large team of technicians to get them back into the air without delay.

A Javelin's ground crew works at top speed. They can rearm and refuel the aircraft and have it back on the runway fully serviced in seven minutes. Here, the Master Radar Station takes over. Once again a technical team . . . air operations staff, teleprinter operators, radar specialists. In the R.A.F., every man counts.

You'll get more out of life in the

R.A.F.

The R.A.F. will train you for a key post and a planned career in electronics, radio, radar or one of many other trades. For full details, post this coupon today.

To: Royal Air Force Central Recruiting Office (ECA 18),
Victory House, Kingsway, London WC2

NAME DATE OF BIRTH.....
STATE TRADE PREFERENCE.....
ADDRESS



As part of their servicing recharged batteries are hoisted into the Javelin's fuselage. These provide a reserve source of electric power.



In seven minutes, two more Javelins are ready on the runway. From the Control Tower, it's . . . "All clear for take-off".

The Television Tube with the All-Star Performance

- ★ **A**pproved by the Highest Standard
- ★ **L**onger Life
- ★ **T**welve Months Guarantee
- ★ **O**utstanding Quality
- ★ **N**ew Mullard and S.E. Electron Guns

12"	£5.10.0	15"	£6.5.0	17"	£6.15.0
14"	£5.15.0	16"	£6.5.0	21"	£9.0.0

All Mullard, Mazda, G.E.C. Types or Equivalents

Cash with order. Plus 10/- carriage and insurance. Terms to the Trade

ALTON-ELECTRO (HIGH VAGUUMS) LIMITED


Cray Works Leeson's Hill St Mary Cray Kent
or Telephone Orpington 27751

Main Distributors

HAMILTON & HORSMAN LTD
199 Becontree Avenue
Dagenham Essex
Telephone Seven Kings 2306

TELELECTRIC SERVICES
34 Sussex Street
St. Philips Bristol 2
Telephone Bristol 56103

MOTEK

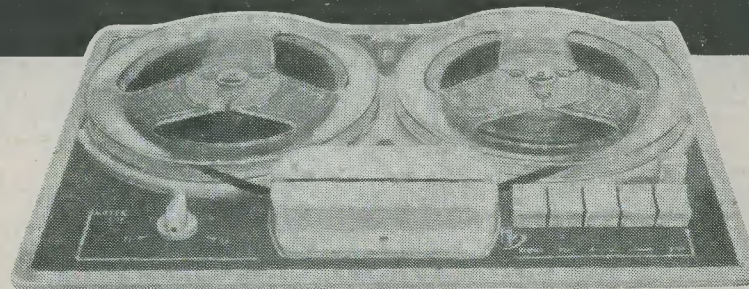

THREE SPEED TAPE - DECK

The Motek tape deck is both the heart and backbone of a multitude of recording machines. Confidence in Motek, felt by manufacturers and enthusiasts alike, grows with the technical excellence of Motek equipment.

Three speeds, pause control, push button operation, accidental erasure prevention, positioning counter . . . these are a few of the outward signs of internal quality.

List 21 gns.

Patents Pending.

Details on request.

MODERN TECHNIQUES


WEDMORE STREET LONDON N19 Telephone Archway 3114

HOME RADIO OF MITCHAM

Dept. AC 187 LONDON ROAD MITCHAM SURREY
Shop hours: 9-6.30 (Weds. 1.0 p.m.) Telephone MIT 3282


We are short wave specialists. Consult us for EDDYSTONE receivers, KW Electronic transmitters, Mosley antennas, etc. Latest Data Book "Short Wave Receivers for the Beginner," price 6/6 post paid.

"GLOBE KING" SHORT WAVE RADIO KITS

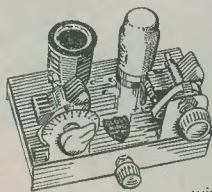

"The finest hobby of all." Explore the world on short waves. News from America, music from Brazil, sport from South Africa, and all the amateurs in every corner of the world. Real long-distance reception at minimum cost consistent with high quality components. Complete kit for 1 valver with three matched coils covering 10 to 100 metres, price 79/6. Illustrated leaflet on request.

LINEAR L3/3 STEREO

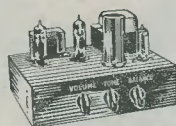

The best value ever for a full two-channel stereo amplifier. 3 watts each channel, response 50 to 15,000 cycles. Output for 3 ohm speakers. Size 9" x 7" x 5". For a.c. mains 200/250V (110V to order) Attractive stoved enamel finish. A quality product at a reasonable cost providing remarkably realistic reproduction. PRICE 7 gns. plus 2/6 post. S.A.E. for leaflet.

CIRCUITS FOR AUDIO AMPLIFIERS

Latest book by Mullards with constructional data for over 12 different designs including amplifiers, pre-amplifiers, mixers, tape amplifiers, stereo amplifiers, etc. PRICE 8/6 plus 1/- post

HI-FI EQUIPMENT

We stock a comprehensive range of hi-fi equipment including Pye, Mozart, Leak, Dulci, Armstrong, Tripletone, etc. Demonstration room now open and a range of sensible high quality systems both ready-made and in kit form are available to hear. S.A.E. for leaflet.

"INSTANT" BULK ERASER




Enables a complete reel of magnetic recording tape to be effectively erased of all traces of recorded matter in a few seconds leaving tape as new. Also can be used for defluxing tape heads giving silent background and elimination of hiss. Highly praised by tape recording journals. S.A.E. for leaflet. PRICE 27/6, post 1/-.

CADENZA MICROPHONE




The most elegant desk microphone ever produced now available with high quality crystal insert. High impedance, response 30 to 8,000 cycles. Ideal for tape recorders, public address, etc. S.A.E. for leaflet. PRICE £3.13.6, post 1/-.

UNIVERSAL MIXER

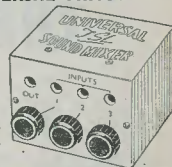


An essential accessory for everyone who uses a tape recorder or audio amplifier. Permits controlled fading in and out of up to three separate signal sources, giving the final result that professional touch. S.A.E. for detailed leaflet. PRICE 2 gns. post 1/-.

STEREO RADIOGRAM CHASSIS

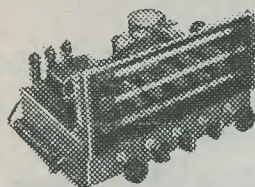

Dulci H35 Long, med. and v.h.f. 8 valves. 8 watts total £27.16.6.
Armstrong Stereo 44. Med. and v.h.f. 9 valves. 8 watts total. £28.7.0.
Armstrong Stereo 12. Long, med. and v.h.f. 12 valves. 12 watts total push-pull. £38.17.0.
All other Armstrong and Dulci Chassis in stock.

REPANCO 1 VALVE DUAL RANGE

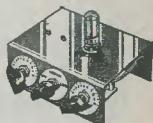



Wonderful little medium and long wave battery receiver. Easy to build and gives excellent results. Ideal constructional gift for any youngster. Complete kit with valve 32/6. Combined h.t. and l.t. battery 8/3. Headphones 15/-. Please add 1/- postage. Full constructional data 1/- post paid.

BARGAIN OFFER

Don't Miss This! 12 new assorted volume controls including switched and pre-set types for ONLY 6/- post paid. Wonderful value for engineers and home constructors.

CABY SUPREME

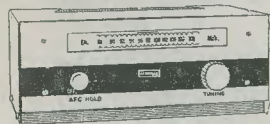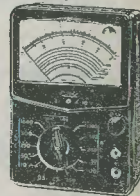Empire made Multi-Range Test Meters. Supplied complete with leads and instructions. S.A.E. for leaflet. Model A.10, a.c. and d.c. 15 ranges. Sensitivity 2,000 ohms per volt. PRICE £4.17.6, post 1/6.
Model B.20, a.c. and d.c. 19 ranges. Sensitivity 4,000 ohms per volt. PRICE £6.10.0, post 1/6.
Also full range of test meters by AVO, Taylor, Pullin, etc.



JASON FM2 TUNER

Enjoy crystal clear hi-fi reception this winter with a JASON FM tuner. Modern slide rule scale and neat case. Self-contained power unit. Full constructional data and price list 2/9 post paid. Complete kit £9.8.0, post 1/-.

RECORDING TAPES

Special purchase of high grade recording tapes enables us to offer at below normal trade price. 3" 250ft L.P., 7/-; 5" 850ft L.P., 20/-; 5 1/2" 1,200ft L.P., 25/-; 7" 1,700ft L.P., 32/6; also 7" 1,200ft Std., 22/6. Add 1/- post.

The Radio Constructor

Incorporating THE RADIO AMATEUR



Vol. 13 No. 5 DECEMBER 1959 ANNUAL SUBSCRIPTION 25/- (including postage)

CONTENTS

- 334 Suggested Circuits: A Very Sensitive D.C. Null Indicator, by G. A. French
- 336 Can Anyone Help?
- 337 In Your Workshop
- 342 Understanding Television, Part 23 by W. G. Morley
- 348 The Cooper-Smith Stereo Control Unit, Part 1
- 354 Radio Topics, by Commentator
- 356 A Good Quality Audio Amplifier by A. J. Sercombe
- 358 National HRO, HRO-M and HRO-MX Alignment Data, including Circuit and Component Values
- 364 A Personable Portable Receiver described by James Sinclair
- 369 Getting Started on RTTY by Arthur C. Gee, G2UK, Hon. Sec., British Amateur Radio Teletype Group
- 372 Car Radio 2-watt Transistor Amplifier
- 374 A Transistor Voltmeter, by L. Baker
- 378 Balance Indicator for Stereo Amplifiers by D. J. Linsey, A.M.I.P.R.E.
- 379 A Vertical Trapped Dipole Antenna by Arthur C. Gee, G2UK
- 380 The "Transitone," a simple Transistorised Electronic Organ, by J. G. Ransome
- 382 A Comprehensive Transistor Checker by J. Anderson
- 383 A Utility Infinite Baffle, by A. H. Strange

Editor
C. W. C. OVERLAND, G2ATV

Associate Editor
A. C. GEE, G2UK

Business Manager
J. H. BURROWS, A C A

Advertising Manager
F. A. BALDWIN, A M I P R E

Offices
57 MAIDA VALE LONDON W9

Telephone
CUNNINGHAM 6141
(2 lines)

Telegrams
DATABUX, LONDON

NOTICES

THE CONTENTS of this magazine are strictly copyright and may not be reproduced without obtaining prior permission from the Editor.

ARTICLES appearing in this magazine which describe kits are inserted only on condition that such kits, or special components thereof, are freely available at a trade discount to all retail advertisers.

OPINIONS expressed by contributors are not necessarily those of the Editor or proprietors.

THE EDITOR invites original contributions on construction of radio subjects. All material used will be paid for. Articles should preferably be typewritten, and photographs should be clear and sharp. Diagrams need not be large or perfectly drawn, as our draughtsmen will redraw in most cases, but all relevant information should be included.

ALL MSS must be accompanied by a stamped addressed envelope for reply or return. Each item must bear the sender's name and address.

TRADE NEWS. Manufacturers, publishers, etc., are invited to submit samples or information of new products for review in this section.

TECHNICAL QUERIES should be submitted in writing. We regret that we are unable to answer queries, other than those arising from articles appearing in this magazine; nor can we advise on modifications to the equipment described in these articles.

ALL CORRESPONDENCE should be addressed to THE RADIO CONSTRUCTOR 57 Maida Vale London W9. REMITTANCES should be made payable to "DATA PUBLICATIONS LTD."

suggested

circuits

The Circuits presented in this series have been designed by G. A. FRENCH, specially for the enthusiast who needs only the circuit and essential data

TWO VERY INTERESTING ARTICLES HAVE recently come to the writer's notice. The first of these¹ describes a light-operated relay unit which possesses some unusual design features. The unit, which was installed at an Industrial Fair in Wellington, New Zealand, causes a buzzer to sound whenever the trigger of a rifle, fitted with an internal light bulb and pointing directly at the centre of a target, is pulled. The trigger operates a shutter in the barrel of the rifle, thereby illuminating a photocell immediately behind the target centre. The most interesting design feature of this device is that the photocell is connected to a fairly conventional a.f. amplifier and that this amplifier handles the pulse resulting from the sudden illumination of the photocell. The amplified pulse energises a relay with a "hold-on" contact in the output anode circuit and this relay, in its turn, causes the buzzer to sound. The device does not respond to slow-changing variations in ambient illumination and no special shielding of the photocell against incident light is required.

The second article² describes the new

¹ "A Special-Purpose Light-Operated Relay," *Radio and Electrical Review* (New Zealand), May, 1959.

² "The Marconi TF.868B," by E. C. Crawford, *Marconi Instrumentation*, September, 1959. *Marconi Instrumentation* is published by Marconi Instruments Ltd., St. Albans, Herts.

No. 109

A very sensitive D.C. Null Indicator

TF.868B Universal Impedance Bridge manufactured by Marconi Instruments Ltd. Part of this second article deals with the balance indicator employed for the resistance-measuring bridge circuits. The bridge is energised by direct current and the voltage between its two balance arms is converted to a.c. by a mechanical vibrator, or chopper, which runs at 80–120 c/s. The a.c. from the chopper is then amplified by an a.f. amplifier, the output of which is detected and fed to an indicating meter. Care is taken to ensure that hum and high frequency components do not reach the detector. The device is capable of considerable sensitivity, and can give useful indications with only a few millivolts d.c. from the bridge.


Both these designs have the feature that effective amplification of a direct voltage is achieved by a.c. amplifier techniques. In the first case it is a pulse which is handled and, in the second, it is a square-wave a.c. which is handled.

The writer felt that it would be interesting to see whether the principles employed in the two devices could be combined together in a form suitable for home-constructor use; and this month's circuit provides the result he arrived at.

The circuit discussed in this article is intended to operate as a very sensitive d.c. null detector. The direct voltage applied to

the detector input terminals is chopped by mechanical means at a frequency of some 5 to 20 c/s. The resultant square wave is then applied to an amplifier which, by differentiation, causes each cycle to be converted to one positive-going and one negative-going spike. The spikes are then passed to a loud-speaker which reproduces them as a series of closely-spaced "clicks," indication of null being given by minimum volume from the speaker. A loudspeaker method of null indication has been chosen here because of its cheapness and also because it takes advantage of the ear's ability to distinguish between the distinctive noise given by the spikes and any background noise, such as hum, which may be present.

years ago,³ and which is capable of offering a very high level of gain. Especially of interest in the amplifier circuit, so far as its present application is concerned, are the low-value coupling condensers C_2 and C_4 . The original purpose of these condensers was that of reducing hum and low-frequency response, but they now serve the additional function of differentiating the square wave applied to T_1 . In consequence each cycle applied to T_1 appears on the grid of V_2 in the form of two successive spikes of opposite polarity, each being capable of causing a "click" to be heard from the speaker. The amplitude of the spikes is limited at the grid of V_2 , incidentally, by the fact that an excessive positive-going spike causes grid current

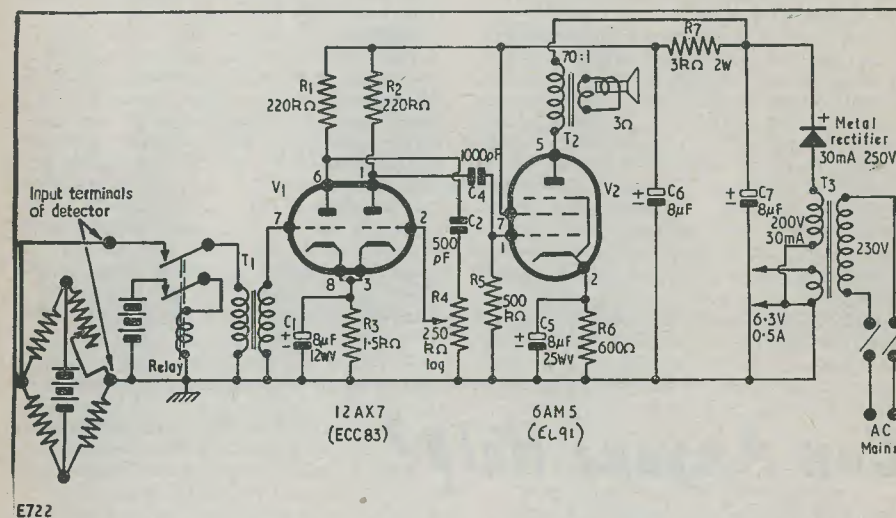

The Circuit

The circuit of the detector accompanies this article, and it may be seen that the input voltage (obtained for purposes of illustration here from a Wheatstone bridge) is applied to a contact set on a relay. A second contact set on the relay is connected between its coil and a battery in such a manner that the relay energises and de-energises continuously in the manner of an electric bell or buzzer. Thus, the first contact set causes the input voltage to be interrupted at the frequency at which the relay operates, this interrupted voltage being passed to the primary of an a.f. transformer, T_1 . The secondary of T_1 couples to an a.f. amplifier and, thence, to the speaker.

The circuit of the amplifier is similar to one used very successfully by the writer some

to flow and that an excessive negative-going spike takes the grid beyond cut-off.

If, when the device is connected up and operating, a d.c. voltage is applied to the input terminals, a succession of closely spaced "clicks" should be heard from the loud-speaker. As the d.c. diminishes in value so, also, does the volume of the "clicks." When the d.c. voltage is zero there should be no "clicks" from the speaker.

Practical Points

There are a number of practical points to clear up. The first of these concerns the relay. No specific type is recommended here as the constructor may wish to take advan-

³ Suggested Circuits No. 71, "A Very High Gain Low-Cost Amplifier," *The Radio Constructor*, October, 1956.

tage of whatever components he may have on hand. The relay is shown in the diagram as being operated from a battery but the latter may, of course, be replaced by a suitable mains power unit. It would be undesirable to attempt to operate the relay from the amplifier h.t. supply unless heavy decoupling was used to prevent coil switching impulses from appearing on the h.t. line. If it is found difficult to make the relay operate at the requisite frequency and with adequate movement of the armature, it should be electrically "slugged" by connecting a resistor across its coil. The value of this resistor will have to be found by experiment, but it will be commensurate with coil resistance.

Transformer T_1 needs to be a high-impedance a.f. type having a ratio lying between 1:1 and 1:5. An "inter-valve" transformer would be ideal here.

The amplifier proper needs little comment, as its operation is simple and straightforward. A 6AM5 is not essential for the V_2 position, as any output pentode with similar power capability will cope in this position. Alternative output valves may, however, make greater demands upon the simple power supply arrangements shown in the circuit. It will be noted that the decoupling circuits are extremely rudimentary. This was a feature of the original amplifier and is possible because of the reduced low frequency response.

The greatest precaution which needs to be taken in the circuit is the avoidance of hum

pick-up in the circuit around T_1 . Because of this it may be necessary to screen the lead from the primary of the transformer to the upper contact set of the relay and, also, the lead from this contact set to the bridge itself. Care should also be taken to prevent hum injection due to inductive coupling between T_1 and T_3 . If these two components are kept well spaced from each other this coupling should cause no trouble. Care needs to be taken, also, to prevent pick-up of the noise generated in the energising circuit of the relay. This trouble, if it appears, should be cleared by fitting screening between the two contact sets and by earthing the metal work of the relay to chassis.

A gain control is provided by R_4 . This should be brought out to the front panel, whereupon it can be employed as a sensitivity control.

Sensitivity

The sensitivity of the indicator should be very high. A spike of one volt amplitude on the primary of T_2 —which should cause a clearly audible "click" from the speaker—corresponds to an input voltage (assuming no losses, and a 1:1 ratio in T_1) of 0.0063mV only. It is doubtful if such a high sensitivity can be achieved in practice due to losses, especially in T_1 , and also because some rounding-off of the spikes will occur in the amplifier, thereby reducing their audible effect. Nevertheless, it should be possible to achieve a sensitivity of at least several millivolts quite readily.

Can Anyone Help?

CR100 Modifications, etc.—D. Bowers, 24 Home Park Road, Saltash, Cornwall, a disabled S.W.L., would like any amateur or enthusiast to loan or sell him any modifications or improvements to the CR100 receiver. Also wanted are copies of *QST*, *CQ*, *Radio Handbook*, by Editors and Engineers, since 1953, cheap if possible.

* * *

Monitor Type 61.—D. M. Macphee, 22 Birch Avenue, Upton, Wirral, Cheshire, would be extremely grateful if any reader could supply him with circuit diagram and modification details to convert the above unit into an oscilloscope suitable for t.v. servicing.

* * *

A.M. Crystal Filter Unit type 53 and 1172 Receiver.—H. L. Braham, 25 Chiltern Road,

Requests for data are inserted free of charge. Enquirers undertake to answer all correspondence and defray all expenses


Newbury Park, Ilford, Essex, is trying to find some information on the two items of equipment above. Can any reader help?

* * *

MCR1 Receiver.—K. F. Gosling, "Melville Cottage," Park View Road, Woldingham, Surrey, would like to receive a circuit diagram and any other information on this receiver. All expenses met.

* * *

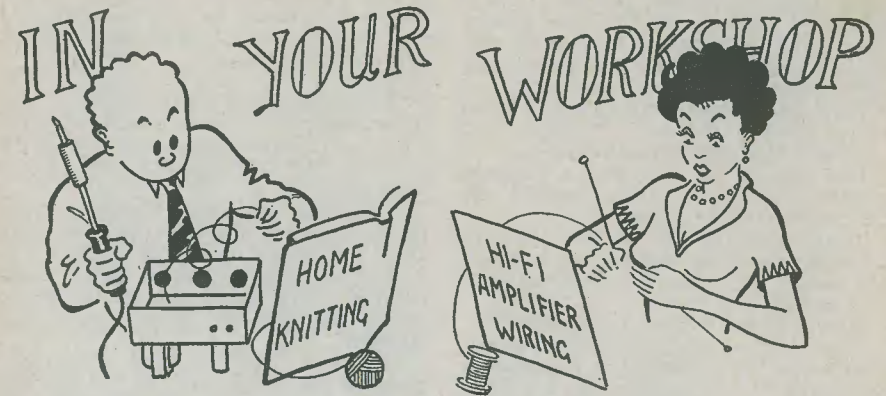BC221 Frequency Meter.—G. A. Bould, 27 Horsford Street, Weymouth, Dorset, would like any information on adding an LF modulator, valve or transistor, to this unit. In particular, has any reader used with the BC221 the Transistor Audio Signal Generator described in the August 1959 issue of *The Radio Constructor*?



This month Smithy the Serviceman discusses with his able assistant, Dick, the vagaries of frame output stages, and introduces him to the ever-present problem of tolerances

THERE IS A TENDENCY, STRONGLY CONDEMNED by the literary critics, for the Modern Novel to become more and more Symbolic in character. Whatever the literary critics might have had to say about the state of affairs existing in the Workshop one early winter's morning, there is little doubt that many Modern Novelists might have readily employed it to illustrate a direct connection between Symbol and Emotion.

In front of Smithy was a television receiver displaying a circle of immaculate roundness and symmetry; and Smithy was chirpily happy in consequence. In front of Smithy's assistant, Dick, was a second television receiver. This exhibited a circle which was round only over its lower 270 degrees, the uppermost section being elongated to at least twice its normal height. And, because of this, Dick was fretful and miserable.

A Modern Novelist who was really on the ball would have taken this situation firmly in hand by defining Smithy's perfectly round circle as being representative of self-sufficient and cheerful maturity; and by equating Dick's egg-shape in terms of youth still controlled, subconsciously, by the ovum. Or something of that order, anyway; and certainly to the extent of a good few hundred words.

Dick, whose idea of the Modern Novel encompassed only the works of Hank Jansen and who would say that Symbols were what

the local Salvation Army used when they had the full band out, was not a person to remain depressed for very long—even when confronted by the ovate. Turning away from his receiver he suddenly cheered up rapidly, and inflated his lungs.

"Smithy," he yelled out, "please give me a hand, will you?"

Frame Output Fussiness

"What's up?" said the Serviceman.

"It's this darned t.v. set," replied Dick, bitterly. "It's got a bad attack of vertical non-linearity and I've spent ages trying to clear it. Right now, I'm stumped for ideas."

The Serviceman did not move from his chair or, even, turn his face away from his own work.

"Are you getting sufficient height?" he said, over his shoulder.

"Stacks."

"And have you checked the condensers, particularly the paper ones, in the frame output stage for leakiness?"

"Every one, and they're all as sound as a bell."

"Are you absolutely sure? A 10MΩ leak in a condenser in the frame output stage, especially if it's in the feedback circuits, can sometimes cause havoc, you know."

"I've checked them thoroughly," replied Dick confidently, "and they're all perfect."

"Resistors O.K. and on value?"

"Whereabouts?"

"Again, in the output stage."

Dick hesitated.

"They should be now," he remarked at length. "I had one that had gone high in value, but I've swapped it for a brand new one. I must admit, though, that the new one didn't improve the linearity very much."

The Serviceman grunted, and left his bench to look at Dick's chassis.

"Where is the one you took out?"

Dick showed the Serviceman a half-watt replacement. Smithy then examined the replacement on the chassis.

"Well," he remarked, "the very first thing I can see is that you've taken out a 1.2MΩ 5% resistor and replaced it with a 1.2MΩ 20% resistor."

"Is that liable to cause much trouble?"

"It might do. Manufacturers don't usually fit expensive 5% resistors if they can get away with cheaper low-tolerance units. See if you can find another 1.2MΩ resistor of the right tolerance."

Dick hunted around and soon found a component of the right type. Under Smithy's watchful eye he carefully removed the component he had already fitted, and soldered in the new one.

"Right," said Smithy, as Dick switched on, "let's see how this one behaves."

As soon as the set warmed up and Test Card "C" appeared, Dick tackled the linearity controls. To his considerable surprise he found that he was able to achieve frame linearity which was perfectly acceptable.

"Well, I'm dashed," he remarked. "So it was that resistor after all."

"So it was," repeated Smithy a little drily, "and I hope this brings home the lesson that close-tolerance components should always be replaced by components of similar tolerance."

"You must admit," said Dick, on the defensive, "that you didn't sound too certain, yourself, that the new 5% resistor would clear the bad linearity."

"I wasn't," confessed Smithy. "Firstly, because frame output stages are notoriously fussy on component values so far as linearity is concerned and some other equally abstruse fault might have been in existence; and, secondly, because the value of the 20% resistor might have fallen within the 5% tolerance in any case!"

Dick considered these two points for a moment.

"Why," he asked, "do you say that frame output stages are temperamental with regard to linearity?"

"Because of the job they have to do," replied the Serviceman promptly. "They have to ensure that a sawtooth waveform

having a very low frequency is fed into the deflection yoke at quite a high power and with low distortion. Also, the feeding has to be done via an iron-cored transformer whose mutual inductance, between primary and secondary, is liable to change quite considerably during the cycle."

"Hey?"

"I'm quite serious," said Smithy. "The permeability of the iron core decreases as the output valve draws more current through the primary, and this reduces the mutual inductance."

"I still can't see why all this should make the frame output stage so touchy," remarked Dick. "A square wave is probably just as hard, if not harder, to amplify than is a sawtooth, and yet a square wave can be handled almost distortion-free by any good hi-fi amplifier."

"That's a different thing altogether," protested the Serviceman. "A hi-fi amplifier employs output valves having plenty of power in reserve, and it uses a pretty massive output tranny. Also, it's designed to have considerably more gain than is really needed, so that plenty of negative feedback can be applied. If you started putting hi-fi circuitry into the frame section of a t.v. set its price would go up by another twenty to thirty quid."

"What you have to do in the frame output stage instead is to keep costs to a sensible level by using an output valve which has just enough beef for the job and an output tranny which is just big enough to cope. It's true that you use n.f.b. circuits in a frame output stage but, since you haven't got much gain in hand, these circuits are not able to exert a high level of control. All they can do is 'trim up' the linearity."

"Fair enough," said Dick, ruminatively. "I must say that it all sounds very reasonable. What you've told me explains also why all your questions just now were concerned with the frame output stage."

"That's right," confirmed Smithy. "If you get bad frame linearity and the frame oscillator seems to be giving plenty of whack, always suspect the frame output stage."

"What about the frame output valve?"

"That's a good suspect. If the frame output valve is getting weary of life you usually get trouble around the bottom of the picture because that corresponds to maximum anode current through the primary. A tired bottle will have trouble drawing sufficient current."

"Do you have to select valves to get best results from the frame output stage?"

"Not normally. Frame output valves seem to be much of a muchness provided they can pass the requisite current. You may

quite probably find, however, that different valves need slightly different linearity control settings."

A Question of Tolerance

"Okey dokey," said Dick. "Now what about your second point? That of tolerance? You said that I might have fitted a resistor which fell within 5% tolerance even if it was marked 20%."

"So I did," said Smithy, "and such a thing could quite easily occur. However, in your case it so happened that the component you fitted was well outside the 5% tolerance range, and it was that which caused you all your trouble. And I must say again," Smithy added, "that you should always try to replace a low tolerance component in a fussy circuit with one of the same tolerance. I might add that, if you haven't got the low tolerance type available, you should measure those you have got in order to find one that falls into the required range of values."

"Well, I suppose you're right," conceded Dick, "and I admit that I dropped a clanger in this particular instance. Nevertheless, I think that most people, nowadays, have got into the habit of fitting replacement components of an old tolerance. They seem to get away with it."

"Well, I certainly wouldn't agree with sweeping generalisations such as that," said Smithy, "because I don't think you're correct. I feel we have a more personal problem here—your own inability to visualise how wide a 20% tolerance is. Let me give you an example."

Smithy unearthed a piece of paper and proceeded to sketch out a circuit.

"Now here," he remarked, "we have a simple a.f. phase-splitter of the type you encounter very frequently in ordinary amplifier work. (Fig. 1.) There is a resistor between h.t. plus and the triode anode, and another between chassis and the triode cathode. The function of the phase-splitter is to pass equal voltages of opposite phase to the push-pull output stage which follows. O.K. so far?"

"Surely."

"Right. Now let's give these two resistors a value and a tolerance. The value could quite comfortably be 100kΩ, and for the purpose of my argument, we'll make the tolerance 20%. Still O.K.?"

"Yep."

"Fine. Now, at any given instant of time, the same current flows through both these resistors; so that we may say that the a.f. voltage appearing across each will be directly proportional to its resistance. Any questions?"

"Nope."

Dick was beginning to look a little bored.

"Fair enough," said the Serviceman. "If we were unlucky, it could quite easily happen that the upper resistance was on bottom tolerance, making it 80kΩ, and that the lower resistance was on top tolerance, making it 120kΩ. With the consequence that the ratio between the a.f. voltages developed across the two resistors will be 80:120. When you cancel things down this is the same as 1:1.5. Still with me?"

"Definitely," said Dick, his boredom vanished.

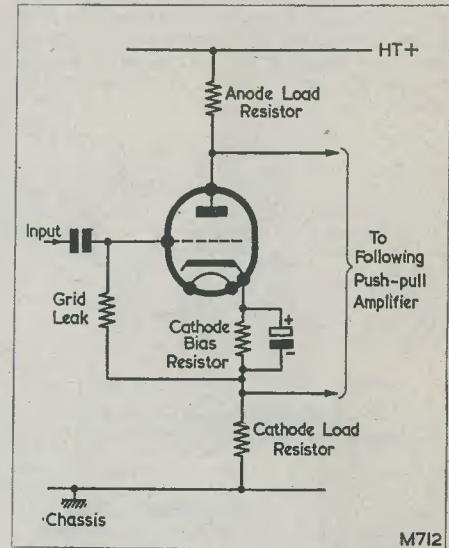


Fig. 1. A typical phase-splitter. If the anode and cathode load resistors have equal values the a.f. volts built up across them should be equal in amplitude

"And the final result," said Smithy, grandiosely, "is that by the use of the 20% resistors in the phase-splitter circuit you have achieved a state of affairs where the voltage passed to the output stages by the lower resistor is no less than 50% higher than that passed by the upper resistor."

"Golly," said Dick, impressed, "I hadn't realised that the error could blow up to as high a proportion as that."

"Well, it does do so," chuckled the Serviceman. "In this instance the error is the result of two tolerances working in opposite directions, with the result that you get an effect which is twice as bad."

"That's funny," said Dick, puzzled. "If it were twice as bad, the difference between the two voltages would have been 40 and not 50%."

Mechanical Tolerances

"The question of tolerances," said Smithy carrying on hurriedly, "is usually far more troublesome when mechanical dimensions are being looked into. I think, now that I'm getting you tolerance-minded, we ought to look into a simple design problem where mechanical tolerances assume considerable importance." Smithy scribbled away on his piece of paper. "For instance, how would you dimension the two parts I've drawn here if they were to be mass-produced? One part is a bush, and the other is a spindle which passes through it and must be free to rotate in it. (Fig. 2 (a).) These two pieces could easily be the part of a cord drive tuning mechanism on to which the tuning knob fits."

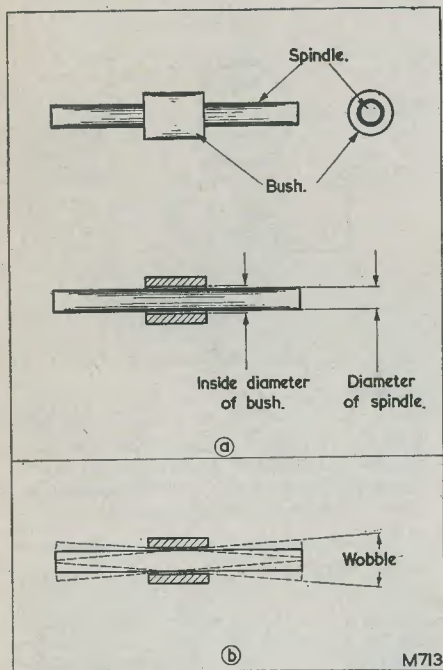


Fig. 2 (a) A typical bush and spindle assembly. The lower diagram shows a section through the centre of the assembly. (b) The amount of spindle wobble is proportional to the clearance between spindle diameter and bush inside diameter

"How d'you mean, dimension them?"

"Their diameters."

"Oh," said Dick, thoughtfully. "Well, I suppose that if the spindle is going to have a knob put on it I might as well give it a diameter of quarter of an inch."

"And the inside diameter of the bush?"

"Well, slightly above quarter of an inch." Smithy chuckled.

"It's not as easy as all that," he said. "A spindle and bush assembly of this nature is a notoriously difficult thing to handle. If the spindle is too tight in the bush it won't turn. If it's too loose you get a wobble effect. Like this. (Fig. 2 (b).) I know, incidentally, that the length of the bush will affect wobble but we'll ignore that for the time being."

Smithy stopped for a moment, as he lit a cigarette.

"To get you started," he resumed, "I'll say that the sort of tolerance you find in practice on parts of this nature is something like this. The spindle could have a diameter of 0.250 inch—that's your quarter-inch—with a tolerance, say, of plus or minus 0.0015 inch. This gives you a minimum of 0.2485 inch and a maximum dimension of 0.2515 inch. It should be possible to hold the inside diameter of the bush to the same tolerance or, even, significantly better. Let's say we can make it plus or minus 0.001 inch. Now, the clearance we need between bush and spindle to enable the latter to turn nicely and freely is, rough check, 0.001 inch again. So what do you think we should make the inside diameter of the bush?"

"Well," said Dick thoughtfully, "the spindle is 0.2515 inch on top tolerance. We need 0.001 inch clearance, so we should make the bush inside diameter 0.2525 inch."

"But I've just said," interjected Smithy, "that the tolerance on the bush inside diameter is plus or minus 0.001 inch. Your 0.2525 bush on bottom tolerance will be 0.2515 inch, whereupon it will seize up solid if you put a top tolerance spindle into it."

"Ah," said Dick quickly. "But how often will that happen?"

Smithy's eyes turned despairingly to the ceiling.

"If you've a good designer it should never happen. What you have to do is to make the bush inside diameter 0.2535 inch. Then, when it is on bottom tolerance it will still be 0.001 inch up on a top tolerance spindle."

"That's all very well," said Dick, scribbling figures on Smithy's paper, "but what happens if you're the other way round? A spindle on bottom tolerance will be 0.2485 inch and a bush on top tolerance will be 0.2545 inch. There's all of 0.006 inch clearance there. Won't that give you a lot of wobble?"

"Ah," said Smithy, satisfied, "now you're beginning to get the right idea! If you're designing a bush and spindle assembly such as that we're discussing here, you have to take two limiting factors into consideration. The first, and most important, limiting factor is that there must always be 0.001 inch clearance between the two diameters if the

spindle is not going to be tight. After that you have to find your second limiting factor—how far can you go the other way before wobble becomes unacceptable. If the wobble given by 0.006 inch clearance is just as bad as we can go, then the tolerances we have just quoted will work very nicely. Alternatively, it may happen that a clearance of as much as 0.01 inch between diameters is acceptable, whereupon we could ease the tolerance figures we spoke of just now."

"You know," confessed Dick. "This is opening up an entirely new world to me. I've never even *thought* of mechanical tolerances before now. I just accepted the fact that most things fit! But, *must* we have tolerances? Why can't people make things *exact*?"

"Because it's impossible," said Smithy. "There must inevitably be tolerances somewhere. If you look at any engineering manufacturing drawing you will see tolerances on all its dimensions."

"Yes," persisted Dick, "but suppose I asked you to make something which was exactly one inch long. Couldn't you make it *exactly* one inch long, as measured by, say, a micrometer?"

"Even were I to attempt the job," said Smithy, "I would ask for tolerances, if only to take up errors in reading the micrometer! In any case the manufacturer of the micrometer would never guarantee that it was measuring *exactly* one inch. He would say it was measuring one inch plus or minus the tolerance he allowed in its manufacture."

"I give up," said Dick, disgustedly. "At any rate, I can definitely forget this tolerance business during my normal servicing work, if nowhere else. I do at least know that if I read 100 volts with my testmeter it *is* 100 volts."

"You don't, you know. The testmeter calibration accuracy is only guaranteed within a certain percentage of full scale deflection!"

"Oh, come off it, Smithy," protested Dick, "if what you say is true then there's *nothing* exactly correct in electronics at all. Everything is an approximation."

"Everything we measure is an approximation," said Smithy, correcting him. "And it is a salutary exercise of the mind to realise that it *is* an approximation."

"Some of the dimensional tolerances we were talking about just now were pretty small, weren't they?" questioned Dick, returning to the previous subject. "I mean such things as 0.001 and 0.0015 inch. 0.0015 inch is only one and a half thousandths of an inch, isn't it?"

"That's right," said Smithy, cheerfully, "but you quite often have to chase the odd half a 'thou' in things of this nature. You

wouldn't normally require such tight tolerances if you were, say, dealing with the positioning of holes on a chassis. Something like plus or minus 10 or 20 'thou' would cope here."

Juggling Figures

Dick seemed satisfied with this and Smithy left him to carry on with his work.

After some minutes, however, Dick called out again.

"I *knew* there was something fishy in those figures of yours."

"What figures?" said Smithy defensively.

"The figures you quoted when you did that explanation with the phase-splitter. You said that one voltage was 50% higher than the other."

"So it is," said Smithy, trying to suppress a grin.

"But," said Dick, aggressively, "if you take it the other way round, you could also say that one voltage was 33⅓% lower than the other. Which is a lot less than your 50% figure!"

Smithy laughed.

"I wondered how long it would be before you twigged it," he chuckled. "I'm afraid I couldn't resist using the higher figure to put my point over. Still, there's no harm done, I hope."

But Dick was lost in a further puzzle.

"I seem to have stumbled on something new here," he remarked thoughtfully. "Now, if I had to specify that the two voltages were within a certain percentage of each other I could get quite different results if I based the percentage on the higher instead of the lower voltage." He scribbled away furiously. "Now let's assume x % difference on either voltage and work out . . ."

His voice died away to an intermittent mutter as he struggled with his figures. The grinning Serviceman left him to it, realising after a glance at the clock that it was very nearly time for elevenses. Dick's mind would soon be diverted from his problem by the soothing action of a cup of tea.

The tea being, of course, Symbolic of Refreshment and Spiritual Restoration.

The Editors and Staff of The Radio Constructor

wish all their readers

A Merry Christmas
and a
Happy New Year

UNDERSTANDING TELEVISION

PART 23

By W. G. MORLEY

The twenty-third in a series of articles which, starting from first principles, describes the basic theory and practice of television

IN LAST MONTH'S ARTICLE WE COMMENCED an examination of the deflection circuits of the television receiver. We saw that the line and frame deflection sections usually consist of sawtooth generators, output valves and output transformers which couple directly into the appropriate deflection coils. We then discussed a capacitive "sawtooth-forming circuit" and showed the relationship between sawtooth linearity and amplitude and the component values employed in the circuit.

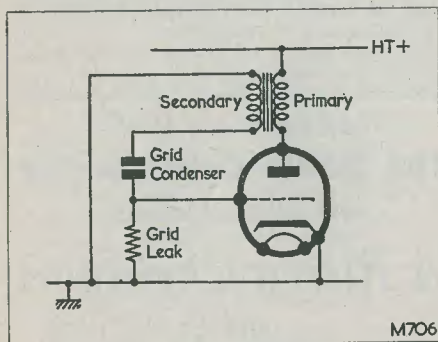


Fig. 124. The basic circuit of the blocking oscillator

Deflection Oscillators

In order that the "sawtooth-forming circuit" of Fig. 123 (a)¹ may be employed in a practical manner it is necessary that the condenser be made to charge and discharge at regular intervals by means of an oscillator, the frequency of the latter being easily controllable. In television receiver design two basic types of oscillator are employed to carry out this function. One basic type is known as a *blocking oscillator*, and the other as a *multivibrator*. We shall consider the blocking oscillator first.

The Blocking Oscillator

A typical blocking oscillator is illustrated in Fig. 124. In this diagram we have a triode valve in whose anode circuit is connected the primary winding of a transformer. The secondary winding of the transformer connects to the grid of the triode via a grid condenser and grid leak.

In order to describe the functioning of the blocking oscillator, it is useful to commence at a point in its oscillatory cycle when the anode commences to draw current through the primary winding. The inductance of the primary winding opposes the flow of current, with the result that this does not rise to a maximum value instantaneously. Instead it increases at a rate governed by the inductance.

¹ Accompanying last month's article.

The increasing current in the primary winding causes an expanding magnetic field to be produced in the transformer, the lines of force of which pass through the secondary winding and induce a voltage therein. The secondary winding is connected to grid and cathode such that this induced voltage causes a positive potential (with respect to chassis) to be applied to the grid via the grid condenser. Since the grid and cathode of the triode form an effective diode, the grid goes only slightly positive of the cathode, and the secondary voltage causes the grid condenser to become charged, its left-hand plate being positive. At the same time, the fact that the valve grid is slightly positive of its cathode ensures that the only hindrance to flow of maximum possible anode current is presented by the inductance of the primary winding.

After a period, the current flowing in the primary of the transformer ceases to increase, either because the valve has become saturated or because the transformer has become saturated.² In consequence the magnetic field becomes stationary and the induced voltage across the secondary winding commences to drop. The drop in secondary voltage results in the grid going negative, with a consequent reduction in anode current. This reduction, in its turn, causes the field in the transformer to contract, thereby inducing a voltage in the secondary having opposite polarity to that resulting from the expanding field. The grid, in consequence, rapidly goes further negative. The valve, by this time, is biased far beyond cut-off and anode current is nil.

During the time when anode current was increasing and before saturation occurred, the grid condenser was charged by the secondary such that its left-hand plate was positive. The condenser still holds this charge (or most of it) and it now causes a negative potential, well beyond cut-off, to be applied to the grid of the triode. The grid condenser cannot retain its charge, however, because the grid leak, in series with the secondary winding, is connected across it; and it discharges slowly. After a period, the charge on the condenser falls below cut-off value, with the result that the valve is able to draw anode current once again. Flow of anode current causes an expanding magnetic field in the transformer to be produced by the primary winding, whereupon the voltage induced in the secondary causes the grid to go positive once more and another cycle commences.

In order to understand the operation of

² A valve is saturated when it passes the maximum current which the cathode is capable of emitting. Saturation in a transformer can only occur when it is iron-cored (as are all conventional television blocking oscillation transformers) and it happens when the iron core is capable of no further magnetisation.

the blocking oscillator more fully, it will be helpful to look at the voltage waveforms which appear on grid and anode of the triode. The grid waveform is shown in Fig. 125 (a). Before point A of this waveform we have the case where the grid condenser is slowly discharging into the grid leak, thereby causing the grid to become progressively less negative. At point A, the grid voltage becomes equal to the cut-off voltage for the valve, and anode current commences to flow. Due to the voltage induced in the transformer secondary the grid goes positive very rapidly, and it stays positive until point B is reached. At point B saturation occurs, and it is after this point that the violent negative swing of grid voltage, to point C, occurs. After point C there is a small positive excursion to point D, caused by the secondary voltage returning to zero, and this is followed by the slow decrease in negative voltage which results from the grid condenser discharging into the grid leak. At point E we reach cut-off potential once more and another cycle starts.

The corresponding anode voltage waveform is shown in Fig. 125 (b). (The letters in this diagram correspond to those in Fig. 125 (a).) As we approach point A we have the case where the grid is biased beyond cut-off and the anode draws no current. In consequence anode potential is the same as that of the h.t. supply. At point A we obtain the sudden increase in anode current initiated by the grid voltage falling below cut-off, this increase causing the anode voltage to decrease until it reaches a minimum at point B. After point B we get the rapid negative excursion of grid voltage. The anode at once ceases to draw current and, due to the collapse of the field in the transformer, its voltage actually goes positive of that on the h.t. rail to point C. The anode returns to h.t. positive potential at point D, and remains at this potential until the next cycle commences at point E. It is important to note that the anode only draws current between point A and a point situated shortly after point B. The anode current waveform is illustrated in Fig. 125 (c).

It is desirable, when blocking oscillators are employed in television receivers, to make the periods when anode current flows short, and the periods when the grid is beyond cut-off, or is "blocked,"³ long. The length of time during which the anode draws current is dependent mainly upon the design of the blocking oscillator transformer, together with the characteristics of the valve. The length of the cut-off period, on the other hand, is mainly dependent upon the values of the grid condenser and grid leak.

In a television receiver it is necessary for us to couple the blocking oscillator to a

³ Hence the term blocking oscillator.

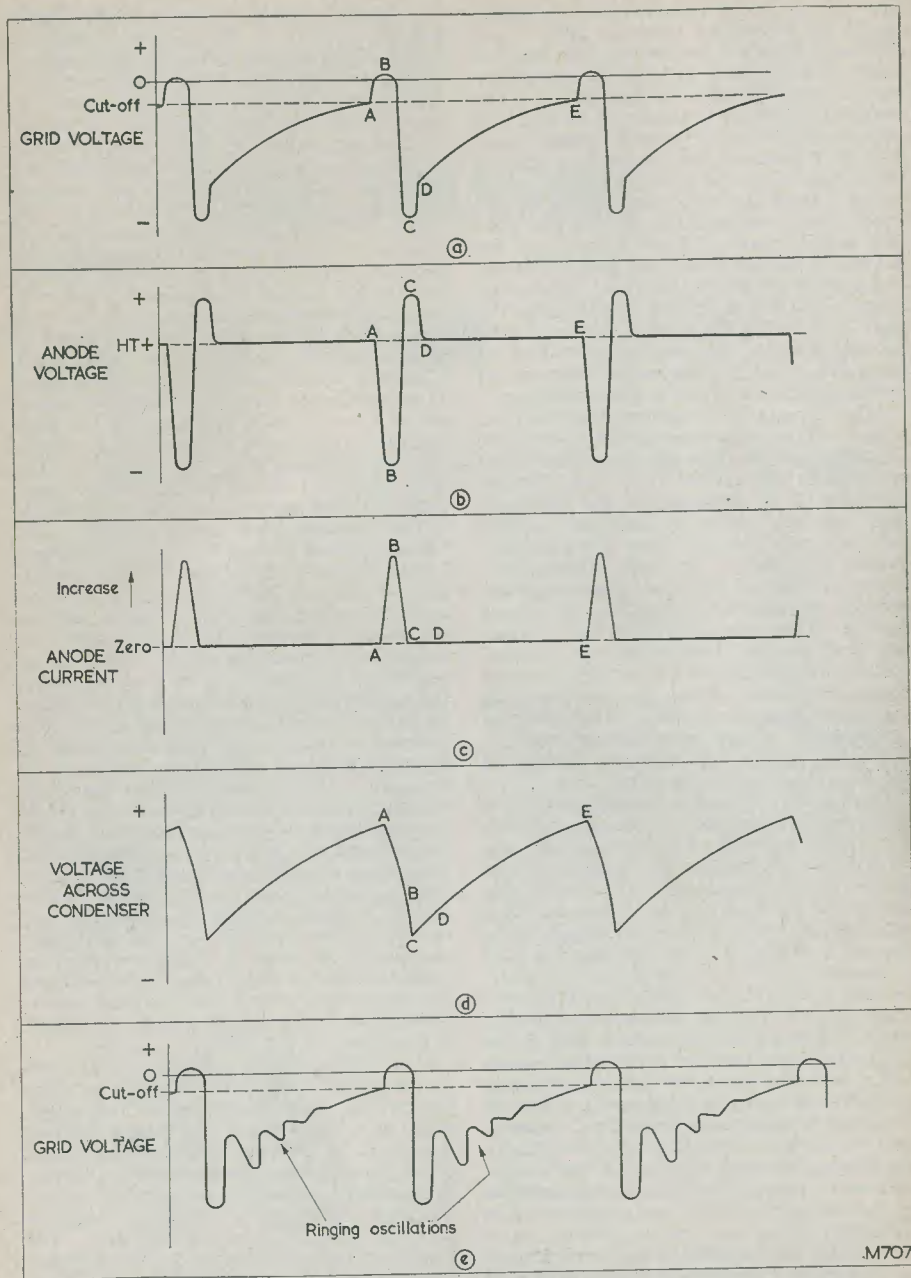



Fig. 125 (a) The voltage waveform appearing at the grid of a blocking oscillator. (b) The voltage waveform at the anode. (c) The anode current waveform. (d) The sawtooth waveform given by either circuit of Fig. 126. (e) If ringing occurs in the blocking oscillator transformer, the grid voltage waveform could look like this.

“sawtooth-forming circuit” such as that we examined in Fig. 123 (a). A simple method of doing this is illustrated in Fig. 126 (a). In this diagram we introduce a second triode whose grid is directly connected to the grid of the blocking oscillator triode. A resistor couples the anode of this second triode to the h.t. positive rail, and a condenser connects between the anode and chassis. The valve then functions as did the switch and series resistor of Fig. 123 (a). It is assumed that the second triode has a cut-off voltage equal to, or less than, that of the oscillator triode.

more and the second triode becomes non-conductive, allowing the condenser to commence charging up slowly again. The result, as seen in Fig. 125 (d), is a sawtooth waveform.

It is possible to dispense with the second triode by using the circuit device illustrated in Fig. 126 (b). In this diagram the condenser connected between the anode of the second valve and chassis now appears between the h.t. positive end of the blocking oscillator primary and chassis. Also, a resistor is interposed between this point and the h.t.

Fig. 126 (a) Connecting the grid of the blocking oscillator valve to the grid of another triode enables a sawtooth waveform to be formed at the anode of the latter. The condenser between chassis and the anode of the second valve discharges rapidly when the valve is conductive and charges slowly, via the resistor coupling it to the h.t. positive rail, when the valve is non-conductive. (b) In this circuit the blocking oscillator valve also causes the formation of the sawtooth waveform

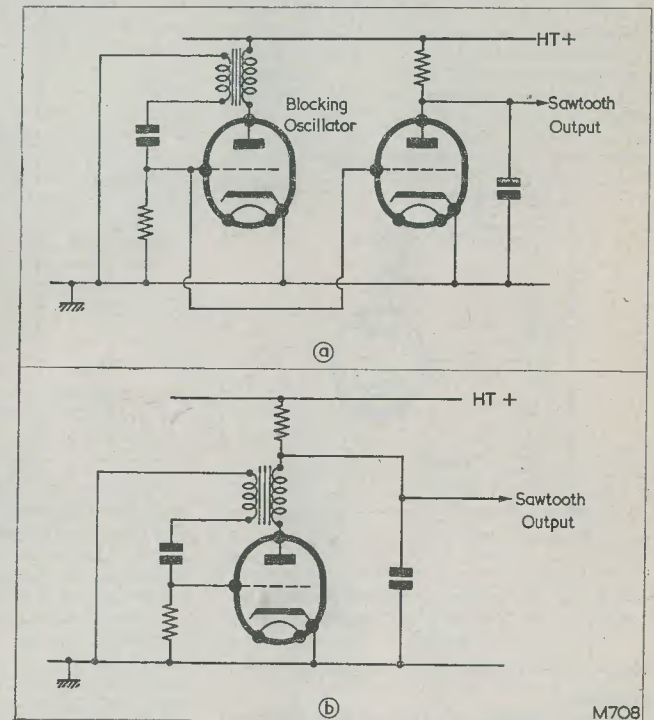

The anode waveform of the second triode is shown in Fig. 125 (d). (Again, the lettered points correspond to those in the previous waveforms). Before point A, the second triode is cut off, with the result that the condenser between its anode and chassis is able to charge up, slowly, via the resistor coupling its upper plate to the h.t. positive rail. After point A the grid of the blocking oscillator valve goes rapidly positive, and so, also, does the grid of the second triode. This valve then conducts heavily, causing a rapid discharge in the condenser. At point C the grids of both valves are beyond cut-off once

positive rail. The action of this circuit is similar to that of Fig. 126 (a). When the blocking oscillator valve draws current, the condenser discharges quickly; when the oscillator valve is cut off, the condenser charges slowly via the series resistor. Once more, a sawtooth waveform results.

Ringing and Squegging

Due to the fact that the blocking oscillator transformer is an inductive component possessing stray capacities, there is a tendency for it to ring after the shock-excitation caused during the period when the anode draws

current.⁴ If ringing is severe, it may cause the grid voltage waveform of the blocking oscillator valve to take up the appearance illustrated in Fig. 125 (e). The ringing effect is not a very desirable design feature, but it will not upset the operation of the oscillator provided that the ringing cycles are not so large as to cause the grid voltage to fall below cut-off before its proper time. Should this happen, the next cycle will be initiated too soon, and the operation of the blocking oscillator will become erratic.

The ringing effect just described should not be confused with *squegging*. A squegging oscillator functions in rather the same manner as does a blocking oscillator, but the transformer in this circuit is such that markedly more than one oscillation takes place before the grid becomes blocked. Squegging oscillators are not employed in television deflection circuits.

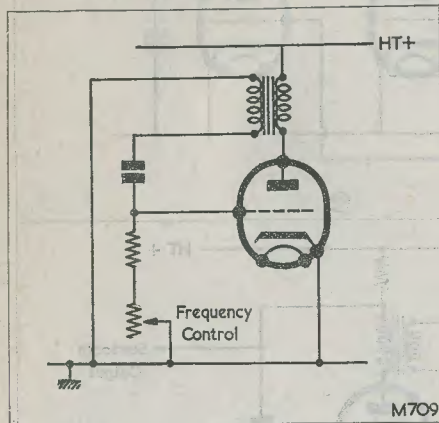


Fig. 127. A variable grid leak provides a control over the blocking oscillator frequency

Frequency

An examination of the sawtooth produced by the blocking oscillator and a "sawtooth-forming circuit" shows that the short discharge section (flyback) occurs during the period when the oscillator valve passes anode current, and that the long charge section (scan) corresponds to the period when the valve is cut off. We have noted, also, that the period when the valve passes anode current is dependent upon the design of the blocking oscillator transformer together with the characteristics of the valve, and that the length of the cut-off period is dependent upon the

⁴ The question of ringing was discussed in "Understanding Television," part 15 (March 1959 issue) when the i.f. amplifier was being dealt with.

values of the grid leak and condenser. In a practical blocking oscillator intended for use in a television receiver the transformer is always designed in such a manner that, with its valve, the flyback period it controls is always shorter than the blanking period after the leading edge of the sync pulse passed on by the sync separator. At the same time, control of frequency is achieved by varying the period of time taken up by the cut-off period. Thus, whatever the frequency, the length of the flyback period, within each cycle, remains fixed.

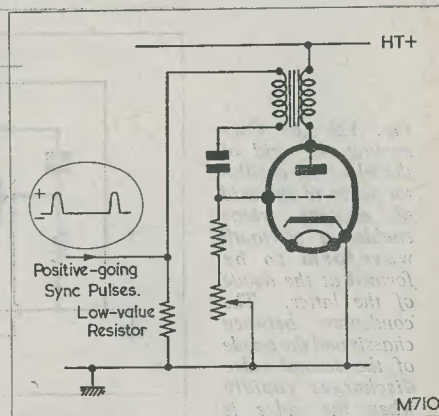


Fig. 128. Injecting positive-going sync pulses into the blocking oscillator

A typical method of controlling blocking oscillator frequency is shown in Fig. 127. In this diagram the grid leak consists of a fixed resistor in series with a variable resistor. Adjusting the variable resistor varies the time taken for the grid condenser to discharge to cut-off potential and, therefore, controls the frequency of the oscillator. The relative values of the two resistors determine the range of frequency control which may be achieved. If the variable resistor has a low value compared with the fixed resistor the range of control is low, and vice versa. An alternative, and much less convenient, method of control could consist of making the grid condenser variable.

Synchronising

In order to keep the deflection circuits of the television receiver in step with those at the transmitter it is necessary for the former to be synchronised. Synchronising pulses appear at the end of each line and frame and these are separated from the signal and passed, in suitable form, to the receiver deflection circuits by the sync separator stage.

A simple method of synchronising the

blocking oscillator of Fig. 127 would consist of injecting positive-going sync pulses into its grid circuit. Fig. 128 shows how the circuit may be modified in order to allow such sync pulses to be injected. In Fig. 128 a low-value resistor is connected in series with the transformer secondary. The positive-going sync pulses are applied to the junction of this resistor and the secondary winding.

Fig. 129 (a) illustrates the grid waveform of the oscillator and shows how the pulses cause the oscillator to be synchronised. In this diagram each sync pulse arrives at a point just before the grid condenser discharges to cut-off voltage, and it causes the grid to go positive. The grid rises above cut-off level, causes anode current to flow, and thereby initiates the flyback part of the cycle. The same occurs in the following cycle, the sync pulse once more forcing the oscillator to go through the flyback part of the cycle before it would otherwise do so.

which the sync pulses appear. If it ran at a higher frequency the flyback period would have commenced before the sync pulse arrived and the latter would have no effect.

The oscillator will also fall out of synchronisation if the sync pulse could not force the grid above cut-off potential. Such a state of affairs would occur if the sync pulse were too small and/or if it appeared too early after the previous flyback period. A typical instance is shown in Fig. 129 (b). In this diagram the sync pulse arrives at a time when the grid condenser has a large negative charge. The sync pulse cannot carry the grid above cut-off potential, and so it has no effect.

We may now see that our blocking oscillator circuit may only be kept in synchronism if its natural running frequency is kept within two extremes. The highest frequency at which it may run is one which is just slightly lower than that of the pulses themselves, and the lowest frequency at which it may run is

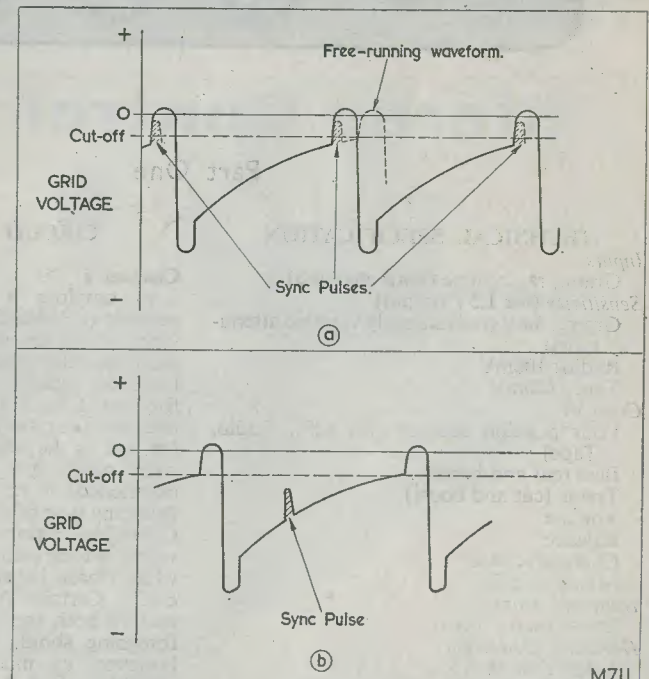


Fig. 129 (a) How the sync pulse forces the grid above cut-off potential, thereby initiating the flyback part of the cycle. (b) If the sync pulse is too small, or if it arrives too early, it cannot initiate the flyback period

Thus, the frequency of the blocking oscillator is held at the frequency of the sync pulses, and flyback, in each cycle, commences immediately after the appearance of the sync pulse leading edge.


It will be noted that, for synchronisation to occur, the blocking oscillator must operate at a frequency lower than that at

that which just allows the sync pulses to force the grid above cut-off potential.

In Fig. 127 we introduced a variable resistor which controlled the frequency of the blocking oscillator. Since this resistor, by changing the frequency, also enables the oscillator to be brought in and out of

Continued on page 373

The Cooper-Smith

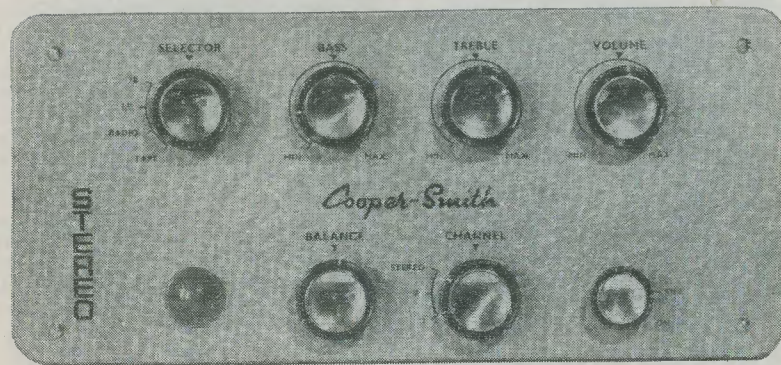

Stereo 'Control' Unit

Part One

TECHNICAL SPECIFICATION

Inputs

- Gram., radio, tape (both channels)
- Sensitivity (for 1.5V output)
- Gram.: 3mV (continuously variable attenuators)
- Radio: 100mV
- Tape: 100mV

Controls

- Four position selector (78, L.P., Radio, Tape)
- Bass (cut and boost)
- Treble (cut and boost)
- Volume
- Balance
- Channel selector
- Mains on-off

Hum and Noise

- Better than -60dB

Harmonic Distortion

- Better than 0.15%

Power Requirements

- 6.3V at 1.3A
- 150-200V at 8-10mA

Dimensions (approx.)

- Length 10½ in
- Height 4½ in
- Depth 3½ in
- Panel 10⅞ in x 4⅞ in

Weight

- 3½ lb. approx.

CIRCUIT DESCRIPTION

Channel 1

V₁ employs a low noise, high slope pentode (EF86/6267) with negative feedback from anode to grid. On the two gram. positions the negative feedback becomes frequency selective, providing equalisation for both L.P. and 78 r.p.m. records. Only one curve for each speed has been provided for, but as the tone controls used are of the wide range type, no trouble should be experienced in obtaining satisfactory results from any type of disc. E.M.I. discs (H.M.V., Columbia, Parlophone) are normally played with the tone controls in the "flat" position, while Decca benefit from a degree of "top cut." Certain American discs, however, require both top cut and bass boost. The foregoing should not be taken as gospel, however, as much depends on listening conditions and the type of speakers used. The correct settings are those which sound best to you! The correction networks are formed by C₁, C₂, C₃, C₄ and C₅ and R₁, R₂ and R₃. On radio and tape the negative feedback is used purely for attenuation and the stage is "flat." The gram. input is fed via a potentiometer VR₁; this enables the control unit to handle practically any kind of pick-up.

The output of V₁ is fed via a fixed potentiometer P₁/P₂ to the grid of

V₂(a). This uses one half of a double triode (12AT7) and is a simple voltage amplifier providing a comparatively low impedance source for the Baxendall tone control circuit (see "Low Cost High Quality Amplifiers," by P. J. Baxendall, B.SC.(ENG.) page 16). This is one of the best tone control circuits ever designed and is eminently suitable for stereo application as it uses linear potentiometers, these being more suitable for ganging. Furthermore, the circuit is of the negative feedback type and introduces a minimum amount of distortion. The small capacitor C₁₄ across the treble control has been included to improve stability at maximum treble boost. This in no way impairs the action of the control.


V₂(b) provides negative feedback for the tone control, and the output of this is fed to the main amplifier via the volume control and channel selector switch. The latter enables either channel 1 or 2 to be selected individually and fed to both main amplifiers in parallel, or on "Stereo" to be connected each to its own amplifier and speaker.

enable the optimum stereo effect to be obtained, as the correct positioning of the stereo "image" depends on the relative sound intensity of each channel one with the other.

With equal input signals the gain of Channel 2 may be adjusted so as to be above or below that of Channel 1, the gain of which is fixed by potentiometer P₁/P₂. When VR₂ is set at about two-thirds of maximum rotation the sound from the two loudspeakers should be approximately equal and the "image" in its correct place. If this is not so, it may be made to move to right or left by corresponding rotations of VR₂.

CONSTRUCTION

The main consideration when designing a unit of this sort is to keep leads as short as possible. This makes the positioning of components of paramount importance, and for this reason the usual chassis and group-board has been, somewhat regretfully, departed from. Instead, the controls and valveholders are mounted on a skeleton framework and the capacitors and resistors strung point-to-point between them, thus reducing wiring to a minimum.

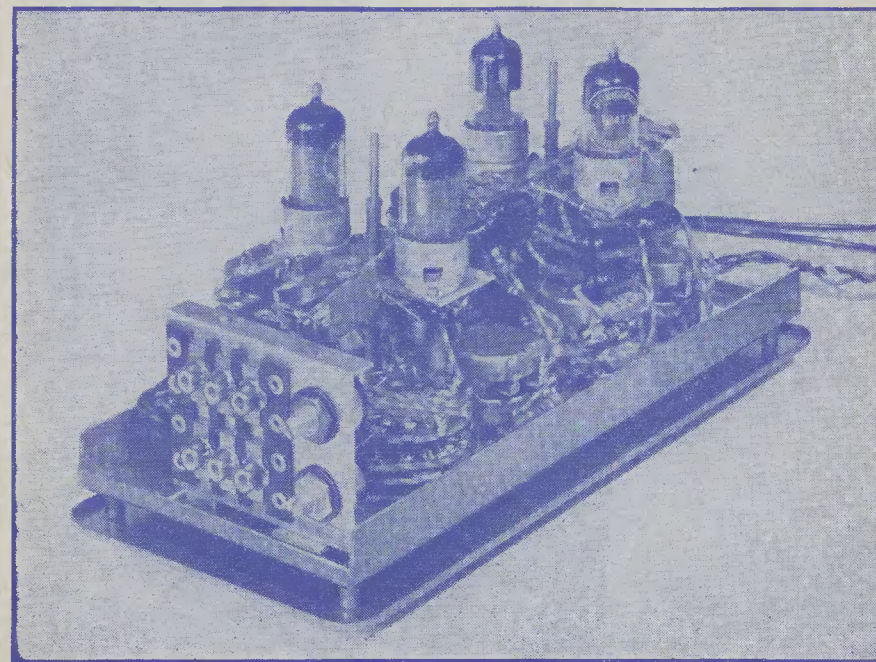

Three-quarter view of the Stereo Control Unit, less case

Channel 2

is identical except for the "Balance" control VR₂. The latter component is necessary to

The result is a piece of apparatus which, though somewhat complicated-looking, can be viewed and worked on from any angle and

Much care and experience has gone into the design of this unit and the writing of these instructions; and, faulty components being very rare, when built it should work. Many hours are spent trying to find the reason for the failure of home-constructed apparatus to do so, and in ninety-nine cases out of a hundred it will be one or more of the following:

1. Wrong connection. (Check and re-check as you go along.)
2. Connection omitted. (Tick off each as made.)
3. Wrong component. (Make sure you have identified each correctly.)
4. Short-circuit. (Use sleeving where necessary. Watch for solder getting in the wrong places. See that components touch only at connections.)

To those with little experience in soldering as applied to electronic apparatus these hints will be of much value and will save them (and probably us!) a lot of trouble.

The first essential is a small but efficient soldering iron such as the Solon 625, Remploy MH/4, Adcola or Litesold 930, all of which are 25 watts, or a solder gun such as the Primax 60 watt. A pair of thin-pointed pliers is also necessary for bending wires into position, and we recommend the small shears type of cutters for snipping off the ends. Use only resin-cored solder of the type specially made for this kind of work, such as Ersin Multicore 18 s.w.g. containing 60% tin and 40% lead. **DO NOT USE A LIQUID FLUX.** We have seen amateur-constructed apparatus so badly corroded owing to its use that most of the components have had to be scrapped.

The requirements of a good electrical joint are these:

1. The parts to be soldered *must* be clean. The wire, tags, etc., should be quite bright in appearance when received; if they are at all dull or the solder does not "take" immediately, scrape clean with a sharp blade.
2. Endeavour to join the parts together so that they will remain in position until soldered (e.g. bend wire round soldering tags and squeeze with pointed pliers).
3. Bring the point of the clean, properly tinned bit to the work and allow a second or two for the heat to flow into it.
4. Apply solder, allowing just sufficient to melt on to the work. Wait until this flows round the joint and remove bit. (Don't keep it on long enough to damage the component.)
5. Watch for solder to "freeze" before allowing any movement between joint.

If the solder takes the form of a blob it is not a good joint and should be cleaned off

and done again; it should *flow* round the work. A crystal-like appearance indicates that the parts have moved at the moment of cooling, and a lumpy appearance that insufficient heat has been applied. Reheat. Use gravity to get solder to run where you want it, but see that it doesn't run where you don't. Too much solder may result in a short-circuit, especially between valveholder tags. Take a second or two to check each joint; it may be very difficult to locate and rectify one after the unit has been completed. Remember, even experts slip up sometimes!

Now to commence.

Stage One

Select the rear tagstrip (the one with the valveholders on) and the associated components, and referring to Fig. 1, place this the correct way round with the valveholder tags uppermost. The tag numbers may be scratched on the strip for easy reference. The valveholder tags number clockwise starting from the blank position. Wire up as follows and in this order (both channels):

- V₁ (2)—spigot—V₁ (7)
 - V₁ (3)—V₁ (8)
 - V₂ (4)—V₂ (5)
 - TS (3) (either tag)—earth tag on valve bracket
 - TS (5)—V₂ (1)
 - TS (9)—V₁ (6)
 - TS (10)—V₁ (2 or 7)
 - TS (6)—TS (11)
 - TS (7)—R₁₇ (brown/red/red)—V₂ (2)
 - TS (8)—C₆ (0.25μF)—V₁ (1)
 - V₁ (9)—R₇ (120kΩ)—V₁ (2 or 7)
- Solder 3-4in wire to V₂ (3 & 8) and V₁ (8) and RH V₂ (7)

Using the twisted flex:

- TS (1) (both)—V₂ (both) (4 & 9)—V₁ (both) (4 & 5)

Now take the front tagstrip, solder tags uppermost, and referring to Fig. 2, wire up as follows (both channels):


- TS (15)—TS (19)
- TS (18)—R₁₀ (blue/grey/orange)—TS (19)
- TS (14) (one wire only)—TS (18) (solder tags together)

Next take the input panel and fit the two VR₁ (100kΩ) as in Fig. 3. Use one nut each side of panel and adjust so that the thread projects no more than necessary to secure.

- VR₁ (2) (both) to Gram. input sockets
 - VR₁ (3)—VR₁ (3)—all earth tags on input sockets, leaving about 5in loose wire from bottom RH tag
- Solder 3-4in wire to both Radio and Tape sockets

Lastly, take Selector Switch (S₁) and refer to Fig. 4. Viewed from rear with nuts horizontal and blank position at 8.30 o'clock, number tags 1 to 11 starting at 3.30 o'clock. Wire up as follows (both wafers):

- S₁ (1)—R₃ (yellow/mauve/orange)—S₁ (6)

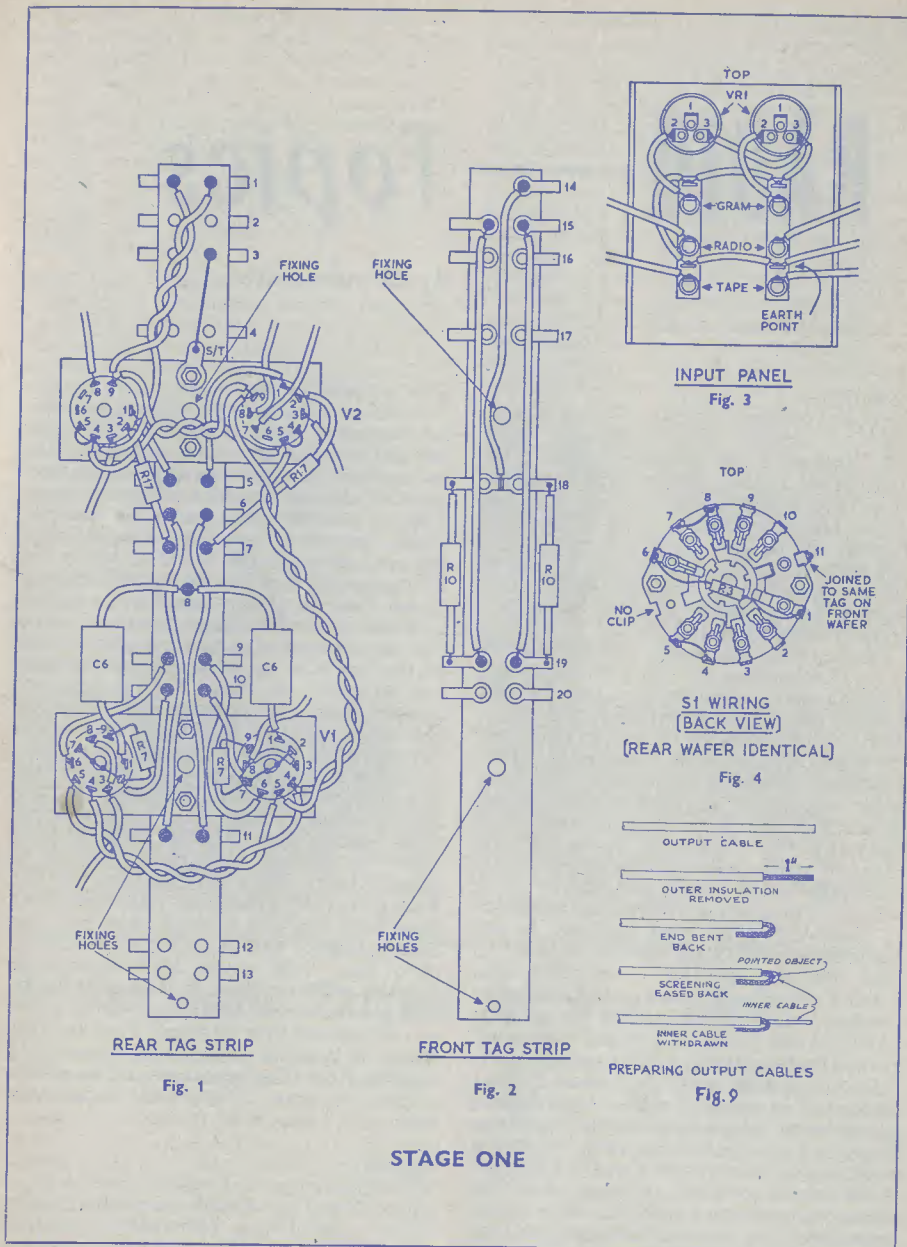

Join 4 to 5 and 7 to 8

Join 11 on rear wafer to 11 on front wafer

Now prepare for Stage Two by building up the framework as shown in Fig. 5. This is shown without the components already

fitted for the sake of clarity. Take care not to break tagstrips by over-tightening or bending.

To be continued

By Commentator

First QSOs

YOUR COMMENTATOR HAS NEVER CEASED to wonder what motivates those operators of amateur radio C.W. transmitters who churn out CQs by the string, often never stopping even to insert their call signs. The phenomenon is still as prevalent as ever, and no amount of publicity against this futile practice seems to stop it. But at last an explanation of its cause has appeared in print, an explanation which in the writer's opinion seems quite feasible.

Dealing with this problem in his editorial in the October issue of "CQ", Wayne Green, W2NSD, makes the suggestion that the root cause of this age-old vice is Fear! He writes: "I'm sure that everyone of you can remember the petrification of your first unaided QSO. This fear is so strong that many novices have never conquered it and have let their licences lapse rather than go on the air. Most of us get over our fears gradually, easing the early pangs by stereotyped contacts which require practically no thinking, and allow us to proceed through the trauma as painlessly as possible." Well, that certainly is one explanation and it's the best we've heard to date. Pity they don't try a few QSOs with a friend who can give them an understanding hearing, instead of putting half the amateur fraternity into a state of frenzied frustration, waiting for the call sign which never comes!

In the same issue of "CQ" there appears an account of a most ingenious legal defence put up by an "automobile mobiler" who was caught in a speed cop's radar trap. Producing evidence that his transmitter was "on-the-air" at the time of the check, he maintained that it caused interference with the radar equipment, producing an inaccurate speed reading. He succeeded in his defence. This seems to be one more good reason for "going mobile"! Will it, we wonder, lead to the production of yet more gadgetry, this time one which will turn the Tx on every time the speedometer reads over 30 m.p.h. in a built-up area?

RTTY—First Contacts

At the time of writing (late October) news has reached us of the first RTTY QSOs in the British Isles. G3CQE in Norwich and G2UK in Lowestoft have been having regular skeds and G3CQE has already worked the States. This is certainly good going; in fact the whole project of getting amateur radio teletype started in this country, which was the reason for forming the British Amateur Radio Teletype Group, seems to have been pushed ahead with such speed and enthusiasm that its organisers deserve the success, which on the face of it, appears to have come their way so easily. In actual fact, an immense amount of work has been put into the project and much opposition from many, who should have been the first to encourage such enterprise, has had to be overcome. It is strange how frequently progress is held up by "The Establishment"—those who by reason of their position and influence could help so much to further progressive ideas. It happened with Single Side Band and with the Radio Amateur Emergency Network. Both these were similarly frowned upon by "The Establishment" and in each case it was left to a keen little group of enthusiasts to conceive and nurture the growing child. Both SSB and the RAEN now enjoy every possible encouragement from all sides. They are "the thing" in amateur radio circles today. We wish the BARTG every success in their efforts to take the spirit of enterprise in amateur radio yet another stage further.

Friendly

Commercially, a magazine's success is judged from its monthly circulation; and, taking a broad view, presumably if tens of thousands of people buy it it must be giving them what they want, and the editorial staff are assured that their policy is correct. Sometimes, however, rather more personal evidence of having satisfied the customer comes in, in the form of letters to the Editor appraising his activities. Where this journal

is concerned, a frequent remark from such correspondents is to the effect that "your magazine has such a friendly spirit about it". This perhaps is one of the reasons for its success. Formality is an outdated mode; nowadays a more personal relationship is sought between all sections of the community, and if a magazine manages to convey this outlook through such an impersonal medium as the printed page, those who direct its policy must be congratulated on their up-to-date outlook.

Valve Type Numbers

Talking of letters from readers, one picks up some good hints from some of these from time to time. I must thank Mr. J. Hockley for one suggestion which he says is not fool-proof but may occasionally help in that very irritating situation where one finds that valve type numbers have become worn off the glass envelope. Try smearing a minute amount of grease—there is usually enough natural grease on the hand for this—on to the glass and then rub it off until there is just a faint rainbow of light reflected when looking across the glass. The remains of the numbers can occasionally be seen as a duller area in the brighter reflection. Ring the place round with a chinagraph pencil and recheck, marking the number prominently on the Bakelite base subsequently.

Electrified Air

Has the thought ever occurred to you that, besides the temperature, the humidity, the dustiness or clearness of the atmosphere in which we live, its electric state may affect our comfort and perhaps even our health? It appears that scientists have given this matter considerable attention ever since Benjamin Franklin demonstrated the fact that the atmosphere was at times electrified. In 1780,

the Abbé Bertholan published a book on the therapeutic properties of atmospheric electricity. In later years the evil traditions associated with such natural phenomenon as the Fohn and Sirocco winds were ascribed to their electrical characteristics. But only recently has it been possible to put these theories to practical tests.

From the Naval Medical Research Unit, University of California, comes a communication based on a considerable amount of research work done by Drs. Albert P. Krenger and Richard F. Smith. It appears that ions, that is the particles of atmospheric gases having positive or negative charges, are continually formed in the atmosphere by such causes as radiation, electric discharges and frictional electricity produced by rainfall and sand blown in the wind. They have shown that these ions do affect living tissues, particularly those of the throat, nose and lungs. Negative ions have a favourable influence on these tissues; positive ions an unfavourable one. They predict that, at some future date, atmospheric electricity control may become an essential part of air-conditioning plants. They even suggest that some respiratory diseases, e.g. asthma, may possibly be treated by adjusting the atmospheric electricity.

The B.R.C.

The British Recording Club has reached an agreement with the British Tape Recording Society whereby the latter has been absorbed, so that the B.R.C. now becomes the largest organisation of its kind in the world. It has representation in thirty-six countries, and publishes a journal—*The Amateur Tape Recording Magazine*. It is reckoned that there are now 400,000 tape recording users in Great Britain alone.

British Audio Exhibit for New York

A composite exhibit of British audio equipment is being arranged for the British Exhibition in New York in June 1960. This is being organised by the Audio Manufacturers' Group of B.R.E.M.A., which was formed early this year, and the possibility of developing other overseas markets by concerted Group action is under consideration.

Apart from export promotion, other Group activities cover technical standards and codes of practice designed to benefit the industry, the trade and the general public, and to avoid confusion caused by the vague term "high fidelity" and its exploitation. A statistical service has also been started.

The Group reminds companies not at present members that any British company engaged in the audio industry in the widest sense is welcome to apply for membership of the Group, which is already representative of a wide section of the industry ranging from very small manufacturers to some of the much larger companies. The management body is elected by members of the Group and is autonomous in respect of all matters concerning audio equipment in the official schedule.

The present chairman is Major J. F. E. Clarke; the vice-chairman Mr. D. A. Lyons, and the secretary Mr. S. E. Allchurch, O.B.E., 49 Russell Square, London, W.C.1.

A GOOD QUALITY AUDIO AMPLIFIER

By A. J. Sercombe

THE AMPLIFIER TO BE DESCRIBED WAS built around an EF86 and an EL84 used in conjunction with an f.m. tuner. The results were found to be very pleasing and rather better than that generally obtained with commercial a.m./f.m. receivers. There is, of course, no reason why a gram input should not be used with suitable matching arrangements.

The circuit is quite straightforward. An alternative method to earthing one side of the heaters would be to use a potential divider arrangement across the heaters and earth the centre-tap. In either case a separate heater winding should be used for the rectifier.

It may be found convenient to omit C₄, and if the bass cut is too severe C₆ should be lowered, the final value being found by trial.

There is little to say about the circuit except that RV₁ and C₁ were incorporated in the f.m. tuner in the prototype; but they could be fitted to the main chassis if desired, or if a gram input were to be used. The circuit diagram shows a coax lead between tuner and amplifier. This lead should be not more than 12in in length.

If the tuner has not got its own power supply, power can be taken from the amplifier at the points as follows:

HT—T (on circuit diagram).
HT—Chassis.

Heaters—Parallel with amplifier heaters. Good quality components should be used as much as possible for trouble-free operation. All resistors are 1/4W except R₈ which is 6W and R₇ which is 4W, and all are ±10%. The capacitors were of the mold seal type in the

COMPONENTS LISTS

Capacitors

- C₁ 0.01μF 400V
- C₂ 0.01μF 400V
- C₃ 8μF 350V
- C₄ 100pF ceramic
- C₅ 0.02μF 350V
- C₆ 0.005μF 400V
- C₇ 50μF 12V d.c. wkg.
- C₈ 50+50μF 350V
- C₉ 50+50μF 350V
- C₁₀ 0.01μF 400V
- C₁₁ 0.01μF 400V

Resistors

- RV₁ 1MΩ 10% 1/4W
- RV₂ 500kΩ 10% 1/4W
- R₁ 1MΩ 10% 1/4W
- R₂ 1kΩ 10% 1/4W 56kΩ
- R₃ 220kΩ 10% 1/4W
- R₄ 1.2kΩ 10% 1/4W
- R₅ 470kΩ 10% 1/4W
- R₆ 10kΩ 10% 1/4W
- R₇ 180Ω 10% 4W
- R₈ 180Ω 10% 6W 1kΩ 4W


Miscellaneous

- Chassis 6in x 8in, see text
- T₁ Mains transformer 250-0-250V, 6.3V at 0.5A, Rectifier heater winding to suit.
- T₂ O/P Transformer Sec. to suit L/S Primary 6,000Ω 10in L/S
- 1 EF86
- 1 EL84
- 1 EZ80 or suitable to T₁

Voltage Table

- EF86—{ V₁ Anode 2 volts approx.
Grid 2, 1/2 volt approx.
Cathode 0.2 approx.
- EL84—{ V₂ Anode 105 volts approx.
Grid 2, 120 volts approx.
Cathode 3 1/2 volts approx.

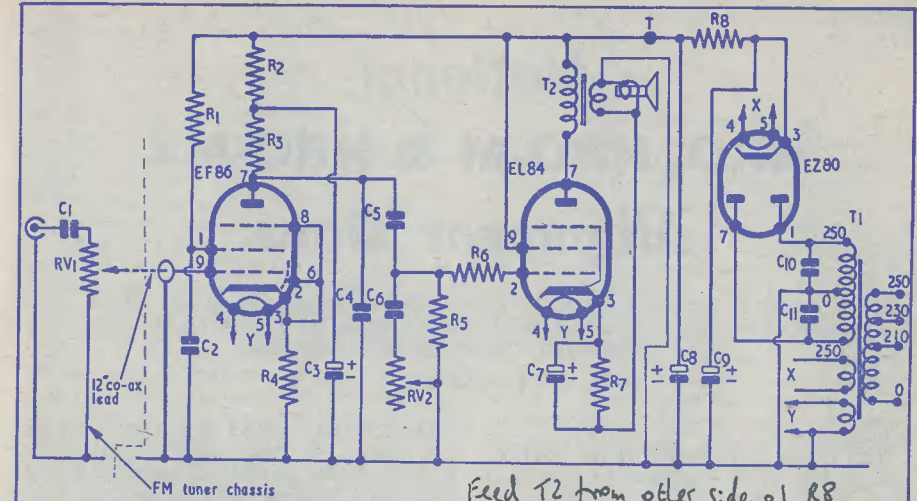- EZ80—V₃ Anodes 250 volts approx.
Cathode 125 volts approx.
Junction of P₈ and C₈ 120 volts approx.



Feed T₂ from other side of R₈.

prototype, but almost any type would be suitable. The mains transformer secondaries used should be 250-0-250 volts 6.3V at 0.5A and 6.3V at 0.5A.

The output transformer should be of generous proportions as this is a very critical component of any audio amplifier, and it should match the R_a of an EL84 which is 4.5kΩ.

A layout drawing is given, but it must be pointed out that it has NOT been scaled as many types of mains and output transformers may be used which are suitable and available to constructors. It would be unwise to use a chassis smaller than 6in x 8in as shown in the components list.


Voltage measurements are given to help the constructor in case faults should occur.

Operation

It should be noted that the tone and on/off controls are on the amplifier chassis and the volume control on the f.m. tuner chassis, but

if the latter control has been fitted to the amplifier the procedure is the same. Switch on, but do not rotate the tone control. Allow 60 seconds for warm-up, inject a signal, or connect a gram or f.m., etc., input.

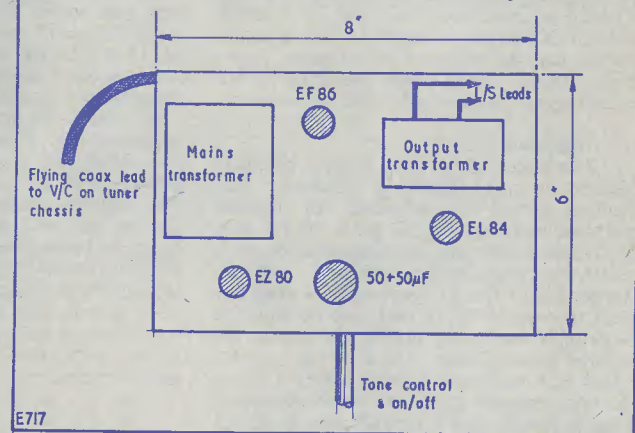See that volume varies as the volume control is varied, and rotate the tone control and note that bass response increases with increased rotation; if not, reverse the connections on the potentiometer.



E717

RIGIDEX — THE POLYETHYLENE PLUS

The impact now being made on modern industry by the introduction of Rigidex high density polyethylene is well demonstrated in a new publication issued by British Resin Products Ltd., Devonshire House, Piccadilly, London, W.1 (telephone Hyde Park 0151).

Entitled "Rigidex—the Polyethylene Plus", the booklet outlines the increasing use of Rigidex in many different industries and walks of life and shows how the superior properties of this new rigid polyethylene are making more things possible in plastics.

356 fit 120Ω in each anode lead of EZ80.

see Feb. 1960 p496 for important modifications. S.B.S. Dec. 54.

National HRO, HRO-M & HRO-MX Alignment Data

In answer to numerous enquiries for such information, we give in this article alignment data for the ex-WD HRO receivers which are so popular, and also include the circuit diagram with component values

I.F.=456 kc/s.

Crystal Filter

With crystal filter switch in off position, receiver bandwidth is approx. 3 kc/s at 2 times down. Switching crystal filter into circuit gives bandwidth of approx. 2.5 kc/s in broad position and about 200 c/s in sharp position of selectivity control. The phasing control can be adjusted to suppress interfering signal frequencies differing from desired signal frequency by 300 c/s or more.

I.F. Alignment

1. The alignment of the I.F. may be easily checked in the following manner. The receiver should be adjusted for normal operation with no antenna, a.v.c. off, r.f. gain at 9, crystal filter on, phasing control at 5, selectivity maximum and the c.w. osc. on. The setting of the a.f. gain control does not affect the measurement and may be adjusted to provide sufficient output to make the required observations. The c.w. osc. control should be turned until a point is found where the predominant pitch of the background noise is lowest and a crystal ring is heard. This setting of the c.w. osc. control should occur near 9 on the scale and the exact setting should be noted.

The crystal filter should then be disconnected from the circuit by turning the phasing control to 0 on the scale and the selectivity control adjusted for maximum background noise. The c.w. osc. control should again be adjusted for lowest predominant pitch of background noise and this new setting noted.

If the i.f. amplifier is properly aligned, the setting of the c.w. osc. control should be the same for both tests mentioned above.

2. When it is found necessary to align the i.f. amplifier, the following procedure should be used.

(a) Adjust receiver as explained above, with crystal filter connected into circuit and set for maximum selectivity.

(b) Connect antenna and tune in steady c.w. signal, or inject unmodulated signal from generator, so that it is tuned exactly on the crystal peak response frequency.

(c) Adjust the c.w. osc. to provide a beat note well within the audio range.

(d) Adjust i.f. amplifier trimmers, numbers 10, 11, 12, 13 and 14 for maximum response. Avoid second detector or audio overload by reducing the signal input as necessary.

(e) Check the alignment as outlined in 1 to ensure that alignment is correct.

3. After the i.f. amplifier has been aligned, the tuning of the c.w. osc should be checked. This may be readily accomplished by repeating the test of 1 with the crystal filter disconnected and the selectivity control adjusted for maximum background noise. If the setting of the c.w. osc. control does not occur at or near 9, with this test, turn the c.w. osc. control to 9 and adjust trimmer No. 15 or 16, or both, for the lowest pitch of background noise.

High Frequency Oscillator Alignment

B-1. The need for re-alignment of the high frequency oscillator is indicated when the frequency calibration of the receiver dial is in error by more than $\pm 3\%$ at the high frequency end of the band in question.

B-2. If the error is more than $\pm 3\%$, it should be corrected in the following manner:

(a) Adjust the receiver for normal operation as follows: r.f. gain at 9, c.w. osc. off, a.v.c. off, crystal filter off, (phasing control at 0), selectivity control at the position of maximum background noise, and the a.f. gain set to provide a suitable signal level.

(b) Adjust an accurately calibrated test oscillator, frequency meter or signal generator to provide a signal which should be tuned in near 490 on the receiver dial according to the general coverage calibration chart for the coil set in use.

(c) Tune the receiver to the test signal and compare the dial reading with the calibration chart.


(d) When the dial reading is too low, more circuit capacity is required and is supplied by adjustment of trimmer No. 8. When the receiver dial reading is too high, less circuit capacity is required and is supplied by adjustment of the same trimmer.

B-3. It is particularly important that the high frequency oscillator circuits operate at a higher frequency than that of the r.f. amplifier circuits. This can be checked by tuning in the test signal as an image which is normally 912 kc/s lower on the receiver dial. The image signal should be considerably weaker if the r.f. amplifier is correctly aligned, and a stronger test signal may be required before the image can be found. If the image signal appears at a higher dial setting rather than a lower setting, the h.f. osc. circuit is incorrectly adjusted and the capacity of trimmer No. 8 must be decreased until the real signal and image signal appear at the proper points on the dial.

imum background noise, which is the setting for maximum gain.

Tracking of the H.F. Osc. and R.F. Amplifier Circuits

D-1. Tracking of the h.f. osc. and r.f. amplifier circuits may be readily checked by observing the background noise while tuning throughout the range of the coil set in use. The background noise should not vary greatly as the dial is turned toward the low frequency end of the tuning range. The actual tracking of each stage near the low frequency limit of the range may be checked by pressing the outside rotor plates of the main tuning section toward or away from the stator, but not far enough to short the condenser or to permanently bend the rotor plates. Any change in capacity should decrease the background noise, indicating decreased sensitivity, if the stage is properly tracking. Coil sets which may require precise adjustment of circuit elements are provided with adjustable series padders in the high frequency oscillation portion of the coil

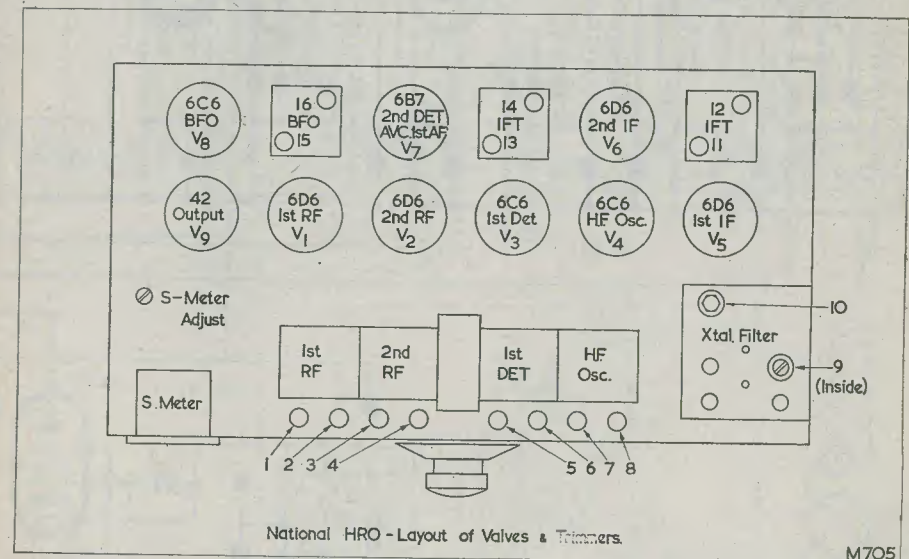

R.F. Amplifier Alignment

C-1. The term "r.f. amplifier alignment," as used in this section, includes alignment of both r.f. amplifier and mixer circuits.

C-2. The r.f. amplifier may be aligned as follows:


(a) Adjust the receiver as explained in (a) of para. B-2. No antenna is needed.

(b) Turn the receiver dial to 490.

(c) Adjust trimmers 2, 4 and 6 for maxi-

set, which can be adjusted to track with the average adjustment of the r.f. amplifier coils. This series padder is mounted inside the coil and is adjustable from the rear by means of a screwdriver. It should be remembered that the series padders found in the coils of the coil sets type A, B, C and D are Bandsread series padders and should not be adjusted except during bandsread alignment.

D-2. After calibration and alignment at

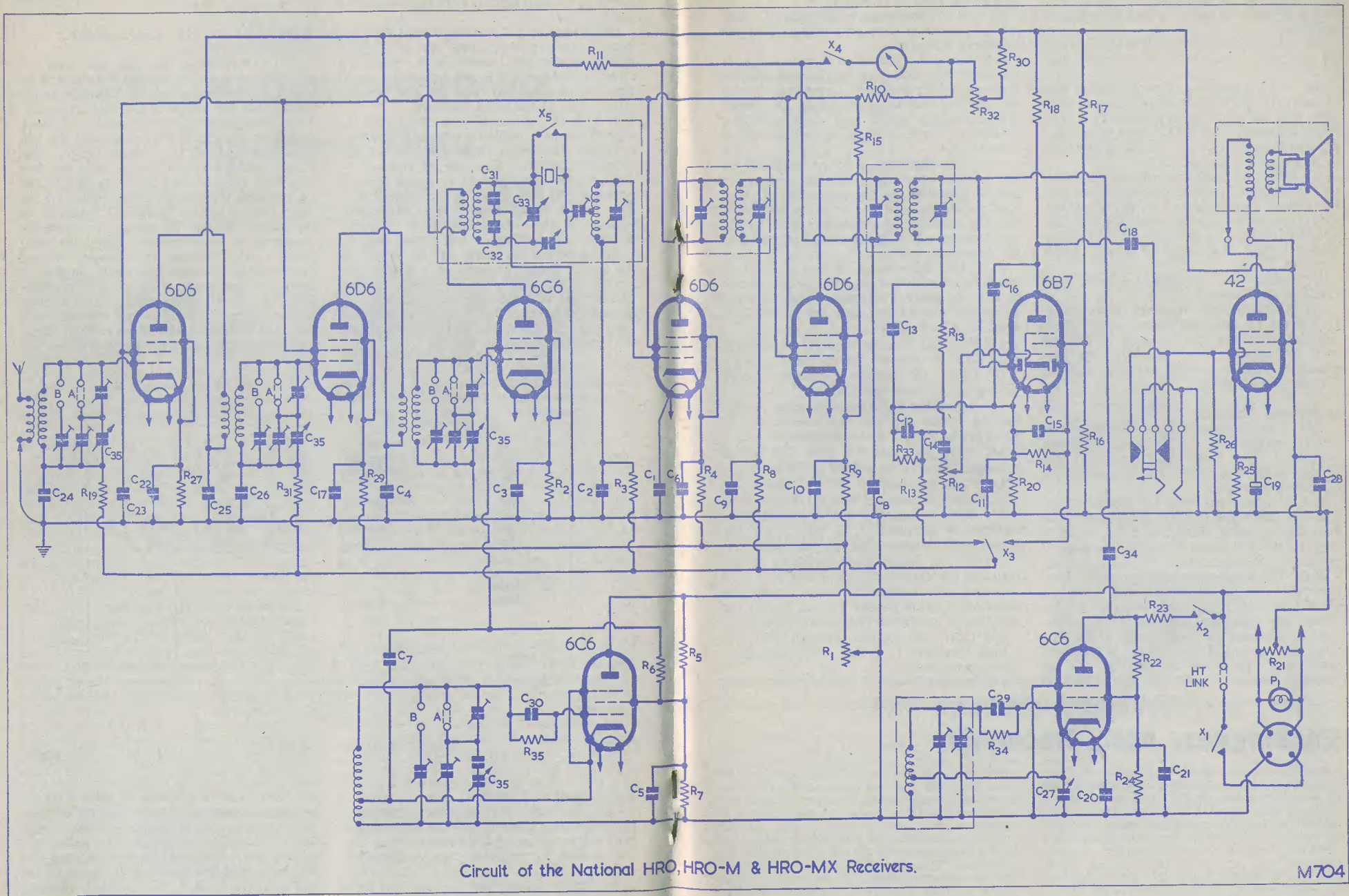

Presented for readers' convenience as an addition to the HRO alignment article. For component values see page 363

the high frequency end of the coil set have been adjusted as explained in paragraphs B-2 and C-2, the tracking may be adjusted as follows:

(a) With the receiver adjusted as in part (c) of para. C-2, turn the receiver dial to 20.

(b) Test the tracking of each stage in turn by bending the outside rotor plate of each section of the main tuning gang and note any maladjustment. Do NOT bend any rotor plate to the extent that it will not spring back to its original position.

(c) Adjust the high freq. osc. series padder to its optimum tracking position when step (b) (above) gives indication of poor tracking.

(d) Turn the receiver dial to 490 and adjust trimmer 8 to give the proper calibration with the new value of series padder capacity.

(e) Repeat (a), (b) and (c) until best tracking is obtained.

(f) Note any slight tracking errors occurring in the r.f. amplifier stages so that if the same error occurs in a majority of the coil sets, the outside rotor plate may be permanently bent to provide the best tracking for the stage involved.

Bandspread Alignment

E-1. The bandspread feature may or may not be included in the particular coil sets supplied. The following alignment data applies only to coil sets which include the bandspread feature.

E-2. Adjustments made for general coverage will affect the bandspread adjustments, but the separate bandspread adjustments may be made without changing the general coverage coil alignment.

E-3. The four screws used to change from general coverage to bandspread must be shifted to the right-hand terminal blocks before any alignment adjustments are made.

E-4. The need for re-alignment of the high freq. osc. section of any coil set is indicated when the frequency calibration of the receiver dial is in error by more than 30

divisions (plus or minus) at the high frequency end of the band in question.

E-5. If the frequency calibration of a coil set is in error, it should be corrected in the following manner:

(a) Repeat the procedure of para B-2 with the exceptions that a test oscillator frequency is chosen which should be tuned in at 450 on the receiver dial as indicated by the bandspread tuning chart, and correction for calibration error is made by adjustment of trimmer 7.

E-6. The alignment of the r.f. amplifier for bandspread operation is similar to that for general coverage, so the procedure of para. C-2 should be repeated with the exception that the receiver dial should be turned to 450 and trimmers 1, 3 and 5 should be adjusted for maximum noise.

E-7. The adjustment of and method of checking bandspread tracking is not similar to that for general coverage. The following procedure should be used for bandspread tracking adjustments:

(a) With the receiver adjusted as in para. E-6, turn the receiver dial to 50.

(b) Check the receiver calibration at 50 against an accurate test oscillator.

(c) Adjust the high freq. osc. series padder located inside the h.f. osc. coil shield to provide the correct dial calibration.

(d) Turn the dial to 450 and adjust trimmer 7 to give the proper calibration.

(e) Turn the dial to 50 and check the calibration. Repeat (c) and (d) if necessary.

(f) With the receiver dial at 50 check the settings of trimmers 1, 3 and 5 for the position of maximum background noise.

(g) If it is found that increasing or decreasing the capacity of trimmers 1, 3 or 5 increases the background noise, adjust the associated series padder located inside the coil shields to provide the desired capacity.

(h) Turn the receiver dial to 450 and adjust trimmers 1, 3 and 5 for maximum background noise.

(i) Repeat (f) and (h), also (g), if necessary.

COMPONENTS LIST

for National HRO, HRO-M & HRO-MX Receivers

see circuit on pages 360-361

Resistors

R ₁	10,000Ω variable
R ₂	5,000Ω ½ watt
R ₃	500,000Ω ½ watt
R ₄	300Ω ½ watt
R ₅	50,000Ω ½ watt
R ₆	100,000Ω ½ watt
R ₇	100,000Ω ½ watt
R ₈	500,000Ω ½ watt
R ₉	1,000-5,000Ω ½ watt
R ₁₀	15,000Ω 2 watt
R ₁₁	250-2,500Ω ½ watt
R ₁₂	500,000Ω variable
R ₁₃	500,000Ω ½ watt
R ₁₄	250,000Ω ½ watt
R ₁₅	30,000Ω 2 watt
R ₁₆	20,000Ω ½ watt
R ₁₇	100,000Ω 2 watt
R ₁₈	100,000Ω 2 watt
R ₁₉	500,000Ω ½ watt
R ₂₀	800Ω ½ watt
R ₂₁	60Ω centre tapped
R ₂₂	250,000Ω ½ watt
R ₂₃	100,000Ω ½ watt
R ₂₄	100,000Ω ½ watt
R ₂₅	500Ω 2 watt
R ₂₆	500,000Ω ½ watt
R ₂₇	300Ω ½ watt
R ₂₈	500,000Ω ½ watt
R ₂₉	300Ω ½ watt
R ₃₀	0-2,000Ω ½ watt
R ₃₁	500,000Ω ½ watt
R ₃₂	1,000Ω variable
R ₃₃	500,000Ω ½ watt
R ₃₄	50,000Ω ½ watt
R ₃₅	20,000Ω ½ watt

Capacitors

C ₁	0.1μF
C ₂	0.01μF
C ₃	0.1μF

C ₄	0.1μF
C ₅	0.1μF
C ₆	0.1μF
C ₇	0.01μF
C ₈	0.25μF
C ₉	0.01 μF
C ₁₀	0.1 μF
C ₁₁	10μF electrolytic
C ₁₂	100pF mica
C ₁₃	250pF
C ₁₄	0.1μF
C ₁₅	0.01μF
C ₁₆	500pF mica
C ₁₇	0.1μF
C ₁₈	0.1μF
C ₁₉	10μF electrolytic
C ₂₀	0.1μF
C ₂₁	0.1μF
C ₂₂	0.1μF
C ₂₃	0.1μF
C ₂₄	0.01μF
C ₂₅	0.1μF
C ₂₆	0.01μF
C ₂₇	30pF variable
C ₂₈	0.01μF
C ₂₉	0.001μF mica
C ₃₀	100pF mica
C ₃₁	100pF mica
C ₃₂	100pF mica
C ₃₃	50pF variable
C ₃₄	2pF
C ₃₅	250pF 4-gang variable

Miscellaneous

X ₁	H.T. (stand-by) switch
X ₂	C.W. Oscillator switch
X ₃	A.V.C. on-off switch
X ₄	S-meter push-switch
X ₅	Crystal filter switch
P ₁	Lamp 6.5V 0.3 amp.

Catalogues, etc., Received

Designing for Diecasting—this is the title of a very well produced 32-page booklet now being issued, free of charge to readers, by Fry's Diecastings Ltd., of Merton Works, Prince George's Road, Merton Abbey, London, S.W.19. The booklet contains many line illustrations, in two colours, showing the desirable and undesirable methods of producing and planning diecasts.

1960 Component Catalogue—Home Radio Ltd., 187 London Road, Mitcham, Surrey, now have in stock their latest catalogue. This current production is attractively produced and printed in clear easy-to-read type. This square-backed production, of 128

pages, printed on fine quality Cotone paper, lists just about everything that one could possibly think of pertaining to radio retailing. Nothing is listed in this catalogue unless Home Radio Ltd. have the item in sufficient stock to last a considerable period and available to purchasers by return. Containing over 4,000 differing items and more than 400 illustrations—including full details of the Eddystone range of receivers and components—this well-produced production is priced at 2s. plus 9d. postage. What we particularly liked about this catalogue: complete index at the front, useful formulae at the rear, and the "How to reach Home Radio" feature on the rear cover.

NEW LABGEAR PRODUCTS

Labgear Limited has recently introduced new aerial accessories. First and by far the most important is the exclusive Labgear 3-station Diplexer Model CN.911. In many parts of the country, stations are so sited that it is now possible for viewers to receive one B.B.C. and two I.T.V. programmes, and the use of this Diplexer, the only one of its kind on the market, makes it possible to receive these programmes on one feeder lead. It is housed in a round watertight case which has a special bracket for fitting either to the chimney lashings or the fascia board, saving therefore, the cost of an extra down lead, and alternatively the inconvenience of changing plugs at the receiver end, or using a switching device with its attendant

losses. Channels must be specified when ordering. This very important unit retails at only 30s.

Another new unit is the Picture Equaliser Model PE.31. In areas where the I.T.V. signal is stronger than the B.B.C. this unit avoids the necessity of adjusting sensitivity and contrast controls when changing programmes, as it automatically reduces the Band III signal to the level of the Band I signal. It is an adaptation of the already familiar model PE.13 which is for areas where the B.B.C. signal is stronger than the I.T.V. No installation problems are involved as these models merely plug in between the feeder lead and the receiver and both retail at 10s. 6d.

A PERSONAL PORTABLE RECEIVER

described by James Sinclair

THE R.C.S. PRODUCTS (RADIO) LTD. personal portable receiver, about to be described, has proved to be extremely popular with the home constructor. It is essentially simple in design, effective in operation and reasonably inexpensive initially. From the front cover illustration it will be noted that the receiver is compact and, contained within a bronze hammer finished metal case, is attractive in appearance.

The receiver as such may be first constructed as a one-valve circuit, which makes the project of some appeal to the young beginner in radio work. Consequent upon this, the successful construction of the first stage may be followed by the addition of an added audio stage. Relatively simple to

Circuit (1-Valve)

This is shown in Fig. 1, from which it will be seen that the circuit is built around the 954 acorn type valve, the anode and suppressor grid of which are not used. The screen grid is used here as the anode, the valve therefore functioning as a triode. The circuit as a whole is simple and basic, thus keeping the cost low and making the construction simple. The condenser CR is used for reaction, whilst CT is used for tuning purposes. The aerial, composed of three sections of aluminium rod, each being some 10½ in in length, is fed directly to the grid winding, C1 and R1 being the grid condenser and leak respectively. The h.t. positive supply is taken, via the headphones, to the "anode."

Assembly Instructions

Secure into position, as shown in Fig. 2, the condenser CR and the tuning condenser CT, making sure that the aluminium washers supplied with these two components are fitted to the fixing bushes before placing them into the case apertures. Place the phone socket (paxolin strip) into position as shown, ensuring that the two sockets coloured red and yellow are nearest to the condenser CR. Fix the strip into position by means of the screws and nuts provided, not overlooking the inclusion

of the earthed soldering tag shown. Fasten the aerial input terminal in position on the top of the case so that the solder tag is inside and nearest to the rear. (See Fig. 2.) Secure the coil in such a manner that the

red locating spot is nearest the open rear of the case. Check that all fixing screws and condenser bush nuts are fixed tightly against the metal casing.

This completes the assembly of the case.

Wiring of the One-Valve Receiver

Note: All wiring must be insulated with the sleeving supplied.

Step No. 1.—Connect one end of a length of wire to the aerial input solder tag and from there to the blue tag of CT. From the latter tag solder a further length to the blue tag of the coil. Do not forget the insulated sleeving.

Step No. 2.—Solder one end of a length of bare 22 s.w.g. wire to the solder tag coloured white on the phone strip and also to the earthed solder tag mounted with this strip.

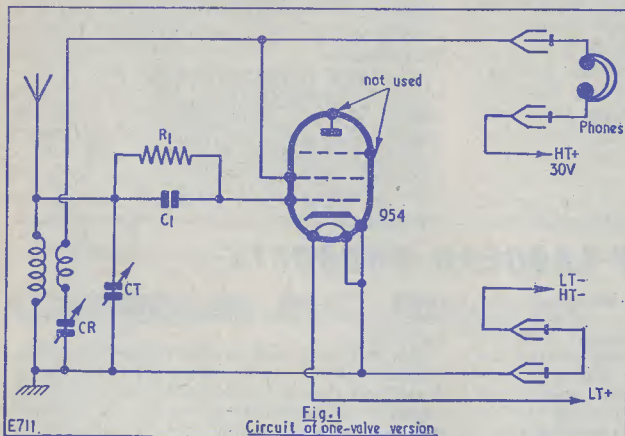


Fig. 1
Circuit of one-valve version.

assemble and construct, and bearing in mind the low cost involved, this receiver should prove popular with those of the older radio enthusiasts who have a Christmas gift problem on their hands!

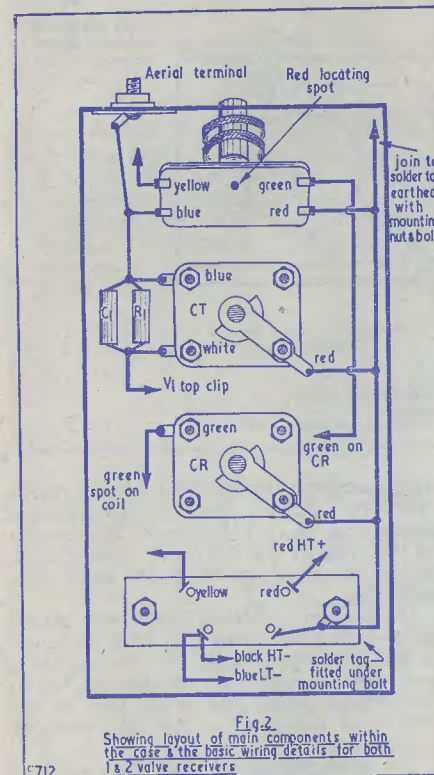


Fig. 2
Showing layout of main components within the case & the basic wiring details for both 1 & 2 valve receivers

Continue from there, leaving all of this wire bare, and solder, at a suitable point along this wire, to the red tag of CR. From this latter point leave sufficient wire to finally solder to an earthed tag which will be mounted later.

Step No. 3.—With a suitable length of wire, join together yellow on the coil to yellow on the phone strip.

Step No. 4.—Connect together green tag of the coil to the green tag on the condenser CR.



Showing arrangement of batteries within the case

Step No. 5.—Detach C1 and R1 from the marked card on which they are mounted and, suitably shortened, solder one end of each to the blue tag of CT, the other end of each of these components now being connected to the white tag of CT.


Step No. 6.—Solder one end of a 4 in length of wire to the white tag of CT, suitably cover with systoflex and connect to the other end the small metal spring clip which is

eventually to be secured to the valve top connection at a later stage.

Step No. 7.—Cut approximately 9in of black wire and 4in of black wire and solder one end of each to the green tag of the phone strip.

Step No. 8.—Cut approximately 4in of red wire and connect one end to the red tag of the phone strip. Leave the other end free for the time being.

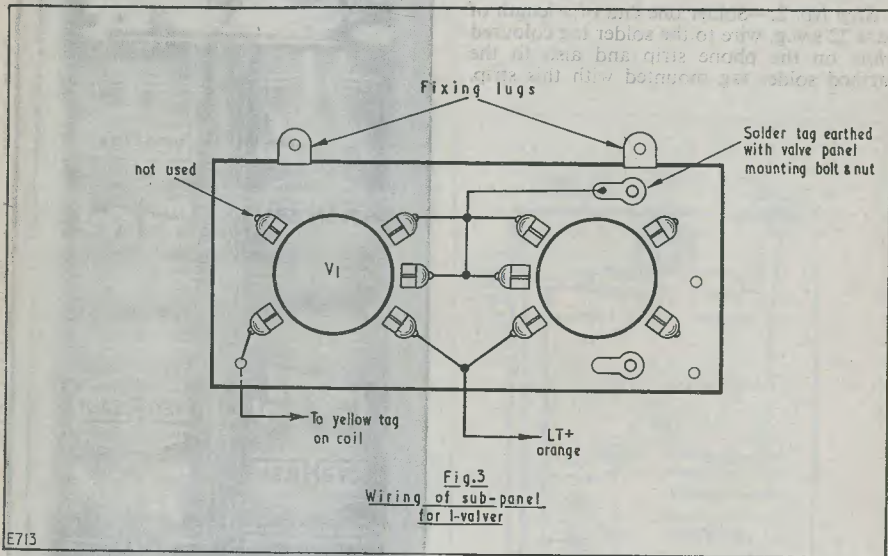We must now commence to wire the sub-panel on which are mounted the valve or valves as the case may be—the valveholders already being in position as received. (See Fig. 3.)



Step No. 9.—Solder together the red tag of V₁ to the red tag of V₂. To this latter point, solder a short length of bare wire to connect with the white tags of both V₁ and V₂. Secure the sub-panel to the case by means of the screws and nuts, ensuring that an earthed tag is fitted under that screw on the right-hand side looking at the receiver from the rear. To this solder tag connect the end of the bare wire left from Step No. 2. Note here that although the red tags of both V₁ and V₂ are in physical contact as received, they must be soldered together as outlined above.

Step No. 10.—From the blue tag of V₁ connect one end of a length of wire, the other end of which is now soldered to the blue tag of V₂. Also solder to one of these blue tags one end of a 4in length of orange flex as shown in Fig. 3.

Step No. 11.—Solder one end of a length

of red flex to the yellow tag of V₁, the other end of which is now connected to the yellow tag of the coil. From this latter tag solder a further length of red flex to the yellow tag of the phone strip.

The valve may now be inserted into the valveholder. Care must be taken to support the sub-panel at the same time, handling the valve itself gently as it is somewhat fragile. The elongated red end of the valve should be placed into the circular aperture in the centre of the valveholder and the valve pins then clipped into their respective seatings. The spring clip connection to the top pin of the valve should now be placed into position, this

latter connection being left from Step No. 6. The wire which is connected to this clip should now be tucked into the cut-out slot on the edge of the sub-panel. There is no connection, of course, to the red, or bottom, valve pin.


The aluminium battery tray is now placed in the case with the red and black terminals at the sub-panel end of the case, allowing both the red and black lengths of flex to protrude on either side of the tray, at the bottom of the case, so that they may be connected to the h.t. battery.

The short length of black flex which is soldered to the blue tag on the phone strip is now brought up under the tray and connected to the black terminal on the tray soldering strip. The orange flex from the blue tag of V₁ is now soldered to the red tag of the tray. Next, connect the h.t. battery by soldering the red flex to the h.t. + brass battery tag and the

black flex to the h.t. - brass tag of the battery.


The h.t. battery should now be inserted at the bottom of the case, together with a small piece of cardboard at either end in order to

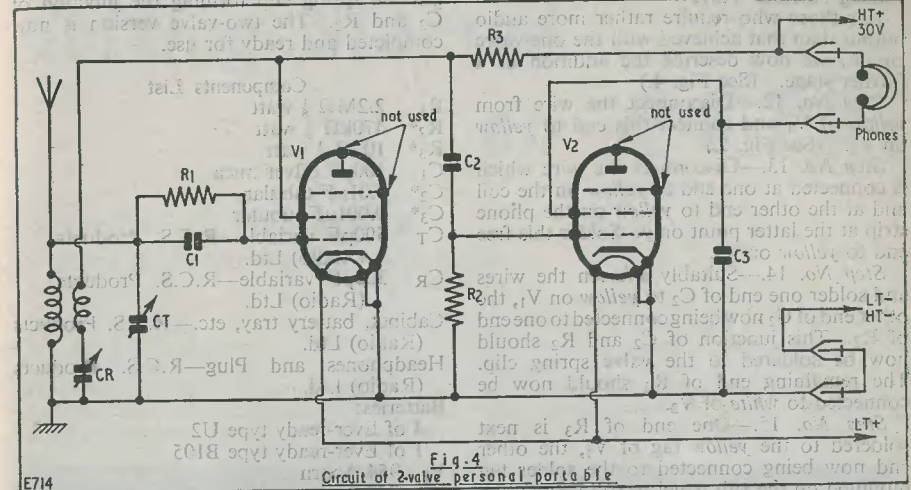Lastly, connect the phones to the phone plug. The insertion of this plug automatically causes both the l.t. and h.t. currents to flow, and these should therefore be removed when



prevent the battery contacts touching the metal casing. Next, fit the cardboard strips supplied in the case, one on either side, and then position the four U2 type batteries as shown in the photograph. The spring clip

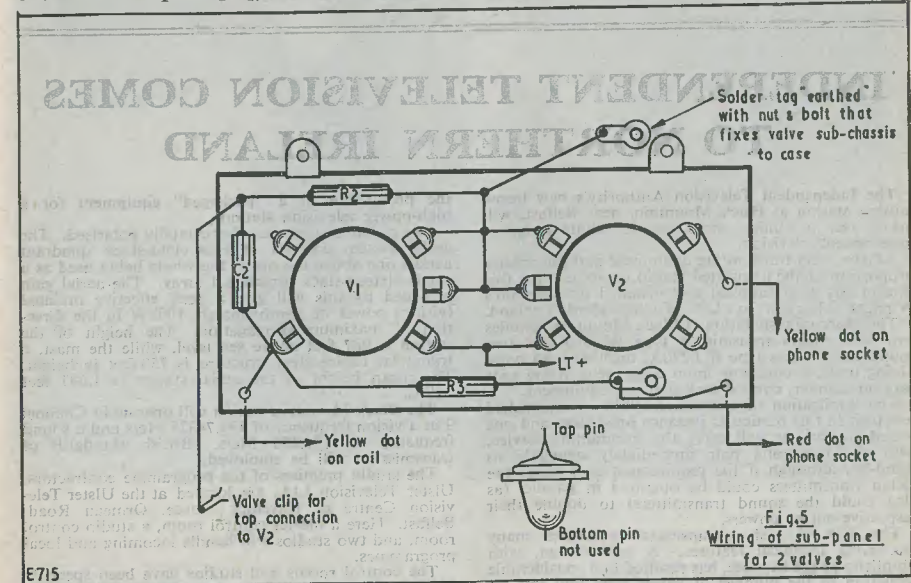the set is not in use, i.e. remove the headphones. The headphone leads themselves are connected to the two wide spaced pins, the remaining two pins being shorted, i.e. connected together with a short length of



attached to the paxolin board should now be fitted underneath the four batteries in order to firmly press these batteries against the terminals at the top of the tray.

bare wire. Having connected the phones to the plug, place the latter into the socket on the front panel, when the valve should "light-up". Screw the aerial rods to the

Getting Started on RTTY

by Arthur C. Gee, G2UK

Hon. Sec., British Amateur Radio Teletype Group

Part 2

ANY THOUGHT OF STARTING AMATEUR RTTY in this country had to be put right out of mind until a source of teleprinters could be found. Whilst the electronic gear can be easily built by the enthusiastic amateur, no amount of enthusi-

teleprinters to part with them at a price which would appeal to the average radio amateur.

And then, quite out of the blue, through a series of events which at first seemed most unlikely to go in the direction one wished,



Teleprinters galore! Members of the B.A.R.T.G. examine the first of the Type 3 teleprinters which the Group has managed to acquire

asm could conjure up a ready supply of the "machinery" side of the matter, nor did it seem able to persuade those concerns who were in a position to supply second-hand

the opportunity came to the writer of acquiring a reasonable number of ex-G.P.O. machines of the type known as Creed Type 3's. Now, as was indicated in the first article

DECEMBER 1959

369

aerial input fixture, and the set should now be in working order. For increased gain, advance the reaction control clockwise.

Adding Another Valve

For those who require rather more audio output than that achieved with the one-valve circuit, we now describe the addition of a further stage. (See Fig. 4.)

Step No. 12.—Disconnect the wire from yellow of V_1 and connect this end to yellow on V_2 . (See Fig. 5.)

Step No. 13.—Disconnect the wire which is connected at one end to yellow on the coil and at the other end to yellow on the phone strip at the latter point only. Solder this free end to yellow on V_1 .

Step No. 14.—Suitably shorten the wires and solder one end of C_2 to yellow on V_1 , the other end of C_2 now being connected to one end of R_2 . This junction of C_2 and R_2 should now be soldered to the valve spring clip. The remaining end of R_2 should now be connected to white of V_2 .

Step No. 15.—One end of R_3 is next soldered to the yellow tag of V_1 , the other end now being connected to the solder tag mounted on the sub-panel paxolin assembly. Also to this latter tag solder one end of a 7in length of wire. Pass this wire through the adjacent hole in the paxolin and connect at the other end to red on the phone strip.

Step No. 16.—Solder one end of C_3 to

yellow on the phone strip and the other end to the red tag of the condenser C_R .

Place the second valve into position, as previously described, and secure to the top pin the spring clip forming the junction of C_2 and R_2 . The two-valve version is now completed and ready for use.

Components List

R_1	2.2M Ω $\frac{1}{2}$ watt
R_2^*	470k Ω $\frac{1}{2}$ watt
R_3^*	10k Ω $\frac{1}{2}$ watt
C_1	100pF Silver mica
C_2^*	0.01 μ F tubular
C_3^*	0.001 μ F tubular
C_T	500pF variable—R.C.S. Products (Radio) Ltd.
C_R	300pF variable—R.C.S. Products (Radio) Ltd.
	Cabinet, battery tray, etc.—R.C.S. Products (Radio) Ltd.
	Headphones and Plug—R.C.S. Products (Radio) Ltd.
	Batteries:
	4 of Ever-ready type U2
	1 of Ever-ready type B105
V_1	954 Acorn
V_2^*	954 Acorn
	Valveholders/Sub-panel—R.C.S. Products (Radio) Ltd.
	Aerial input socket, phone strip, aerial rods, etc.—R.C.S. Products (Radio) Ltd.
	* 2-valve version only.

INDEPENDENT TELEVISION COMES TO NORTHERN IRELAND

The Independent Television Authority's new transmitting station at Black Mountain, near Belfast, will bring over a million more people within range of independent television.

All the main transmitting equipment and the greater proportion of the associated studio equipment for this station has been supplied and installed by Marconi's Wireless Telegraph Co., Ltd. of Chelmsford, England.

The Marconi installation at Black Mountain includes two 4kW vision transmitters type BD.366 and two sound transmitters type BD.270A, together with combining units, programme input equipment, flying spot caption scanner, control desk and test equipment.

The duplication of transmitters follows established practice; in this particular instance one vision and one sound transmitter will carry the programme service, with the remaining pair immediately available as stand-by, although if the requirement ever arose the vision transmitters could be operated in parallel (as also could the sound transmitters) to double their respective output powers.

The BD.366 vision transmitter embodies many interesting technical features. A new design, with simplicity as the keynote, has resulted in a considerable reduction in the number of valves used and this, in turn, has made possible an extremely clean, straightforward layout and the incorporation of a simple yet thoroughly efficient cooling system which needs no sub-floor ducting. The transmitter represents the nearest approach yet made by any manufacturer to

the production of a "packaged" equipment for a high-power television station.

The radiated signals are horizontally polarised. The aerial system consists of two eight-stack quadrant aerials one above the other, the whole being used as a single sixteen-stack directional array. The aerial gain provided by this will give a peak effective radiated (vision) power of approximately 100kW in the direction of maximum propagation. The height of the station is 987 feet above sea level, while the mast, a triangular lattice steel structure, is 750 feet in height. The mean height of the aerial system is 1,687 feet A.S.L.

The Black Mountain station will operate in Channel 9 at a vision frequency of 194.74325 Mc/s and a sound frequency of 191.230 Mc/s. British standards of transmission will be employed.

The studio premises of the programme contractors, Ulster Television Ltd., are located at the Ulster Television Centre at Havelock House, Ormeau Road, Belfast. Here a master control room, a studio control room, and two studios will handle incoming and local programmes.


The control rooms and studios have been specially designed by Marconi's in conjunction with Ulster Television Ltd.'s technical advisers. The larger studio is equipped with two Marconi Broadcast Vidicon cameras while the other, which is an announcers' studio, has a smaller Marconi Vidicon camera. Telecine equipment is installed in an adjacent room.

in this series, there are two standards in common use in the field of teleprinter communication, the English or Creed System and the American system. Quite frankly, if one had had the choice, one would have preferred to have acquired American teleprinters rather than English ones, because most of the amateur RTTY going on at present is taking place in America, Canada and one or two other countries, all of whom have acquired their machines from civil or Services U.S.A. sources. As amateur RTTY operators will want to work into these countries, it would have been better to have adopted the American standard and kept just the one standard as far as amateur radio was concerned. However, American machines are rarely offered for sale in this country, and when they are, the price asked is far above

the Creed system, not the American, so that their signals are intelligible on our machines.

This point has been laboured somewhat in order to warn those who may acquire teleprinters through sources other than the B.A.R.T.G. to be sure they work on the Creed system. There are to be had, at times, various ex-U.S.A. Services teleprinters. These will not work into the British net, without modification.

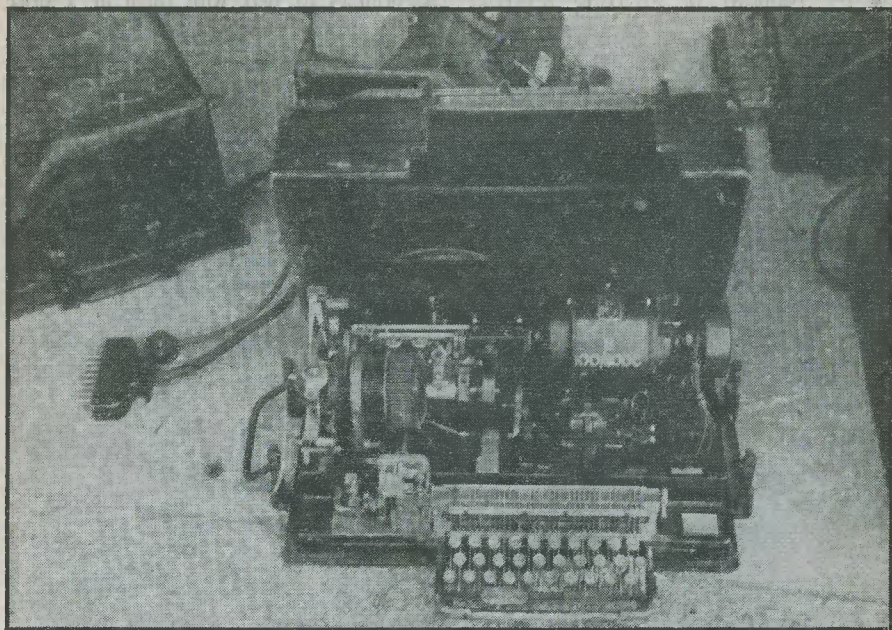Generally speaking, there are two types of teleprinter. The older type, of which the Type 3 is an example, type on to a long paper tape. This will be familiar to most readers as the type used for those telegrams in which the message was printed on to gummed paper tape which was subsequently stuck on to message forms. The newer



Ex-G.P.O. Creed Type 3 Teleprinter. Typing head, with paper tape transport mechanism is to the left. The governor is to the right of the motor

that which an amateur can afford. With such an offer as came the B.A.R.T. Group's way, the obvious course was to take it, get a British—and perhaps European—net going, and sort out the difficulties of working American-equipped stations later.

As it happens, this decision has proved a wise one from another point of view, viz., that many of the European Shortwave Commercial Stations, whose signals have proved so useful in lining up one's gear, use

models type directly on to message forms or paper rolls about 8in. wide in the form of a "page." These are designated "page printers."

Whilst the tape printer produces yards of paper tape on which the message is recorded and obviously hasn't the advantages in this direction which the page printer has, it has a number of advantages over the page printer, particularly in relation to simplicity of operation, which is a valuable feature for

those acquiring their first experience of this mode of communication.

So much for the generalities. Let's turn to some details of the Type 3 machine.

As can be seen from the photos, it is quite a compact unit, being 20½in long, 14½in back-to-front and, with its cover on, 10in high. It weighs about 60lb, which is not too bad for one-man handling. Of those acquired by the B.A.R.T.G., some had 100-110V d.c. motors; others 150-170V d.c. motors, and the remainder 200-220V d.c. motors.

The motor is maintained at a constant speed of 2,520 r.p.m. by a centrifugal governor mounted on the end of the motor shaft. As has already been explained, these teleprinters work on the "start-stop" system and the speed of one machine does not, therefore, have to be accurately timed to that of another, as is the case with the synchronous systems. Even so, the permissible speed difference between machines must not be too great and a tolerance of not more than 0.5% is usually aimed at. The amount of speed error permissible before errors show up depends on circuit characteristics and so on, but generally speaking a difference in speed between two machines of 2% or more will produce gross errors in printing between the two machines.

The speed of the teleprinter can be checked in a number of ways. One can, of course, check the motor speed with a speedometer in the normal way, if one has access to this type of instrument. A revolution counter can be similarly used. The manuals on these machines usually give a table of the various shaft speeds. In practice, rapid checking is carried out by using a stroboscope. This is a most ingenious little gadget consisting of a metal reed fixed to the bottom of a brass tube, up which it extends. At the top of the tube, the reed is attached to a metal weight. When this is made to vibrate, by pulling quickly to one side and releasing, it does so at a rate depending on the length of the reed. As it does so, it covers and uncovers a narrow aperture through which one can watch a white line marked on one of the gear wheels of the teleprinter. Various stroboscopes are available, each with different speed characteristics. Examination of the Type 3 machine will reveal a gear wheel with a well marked white line or segment on it. If this is viewed through the appropriate stroboscope, with

the machine running at its correct speed, the line or segment will appear stationary. If the line appears to be rotating clockwise, the motor is running too fast; if anti-clockwise, too slow. In the case of the Type 3 teleprinter, the wheel carrying the white mark should rotate at 630 r.p.m. and the stroboscope required to check it is the No. 1.

Adjustment of the motor speed is done by adjusting the governor. Its cover is removed, the clamp screws holding the base plate are loosened, and the governor spring adjusting screw is turned in a clockwise direction to increase the motor speed or an anti-clockwise direction to slow the motor. One complete turn of the governor adjusting screw should alter the motor speed—not the gear wheel speed—by about 30 r.p.m.

Direct current supplies for the motor can be obtained in a variety of ways. For those who wish to buy a suitable unit, the Type 43 is the thing to look for, if you have a motor of the 100-110V range. These are rather large units, massively built, of the metal rectifier type. They can be obtained very cheaply from various firms who deal in surplus of this type. However, as most of these motors do not take much current—from ½-¾ amp—most members of the B.A.R.T.G. appear to have devised their own d.c. supplies from receiver type transformers and metal rectifiers which they already had on hand. Similarly with the 150 and 200V motors, for which at the time of writing the author has found no reasonably priced surplus unit.

It is not possible in the limited space available for this feature to deal with the mechanics of the teleprinter. For those who are interested, the various service manuals on this topic should be consulted.

The primary purpose of these articles is to show how to "join the equipment together and get it going," although in subsequent articles we shall deal with the construction of a receiving FSK converter, or "terminal unit" as it is called, and with FSK conversions for amateur transmitters.

Next month we shall deal with various matters relating to the circuitry of the machines and show how to wire them up so that they can be made to "self-print," a procedure which will indicate quite well whether or not your machine is suffering from any gross faults.

RADIO SHOW 1960

The National Radio and Television Exhibition is to be held at Earls Court, London, from 24th August to 3rd September

with a preview for overseas and other specially invited visitors on 23rd August.


This will be the 27th National Radio Show.

Car Radio 2-Watt Transistor Amplifier

THERE MUST BE MANY READERS OF THIS magazine who own a car radio and require just that little extra "punch" so often required when located in a notoriously poor reception area, or whose existing installations do not deliver sufficient audio output. Also, for those fortunate enough to have a trailer caravan, where usually more output is required, this amplifier should prove to be "just the job".

should now be connected to the input of the amplifier via a twin screened lead. The screening of this lead should only be connected at the amplifier end to positive, the other end being left free.

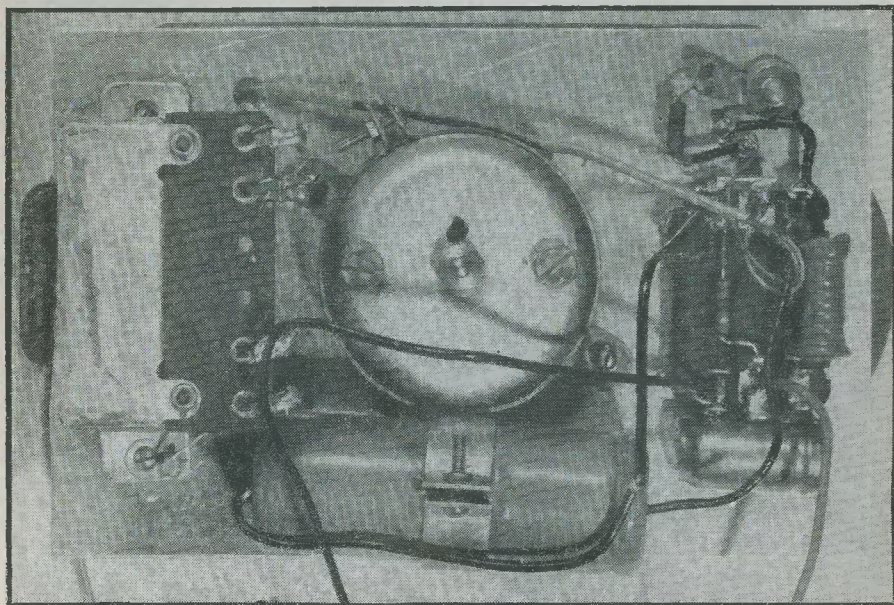The collector of the Newmarket V15/10P power output transistor is the OBA nut—in effect the transistor casing. This must be bolted directly to the amplifier metal chassis in order to dissipate heat and obviate



Layout of the car radio amplifier chassis

The circuit is shown in Fig. 1 and is self-explanatory, being the normal a.f. amplifier design met with power transistors. To connect the amplifier into circuit, disconnect the speaker voice coil from the existing output transformer of the receiver and connect to the output transformer TT12 of the amplifier. The output transformer of the receiver


thermal runaway. This being so, the chassis of the amplifier must *NOT* come into contact with the car chassis; indeed should this occur, a blown transistor and/or a flat car battery will result!

Connection to the car chassis in order to obtain a positive supply should be obtained by a lead soldered to the appropriate end of

the 1Ω resistor inserted in the emitter supply. The negative supply should be obtained either direct from the car battery or a suitable nearby source and via the switch shown.

connected directly to the transistor base. The total current consumption of this amplifier is some 300mA.

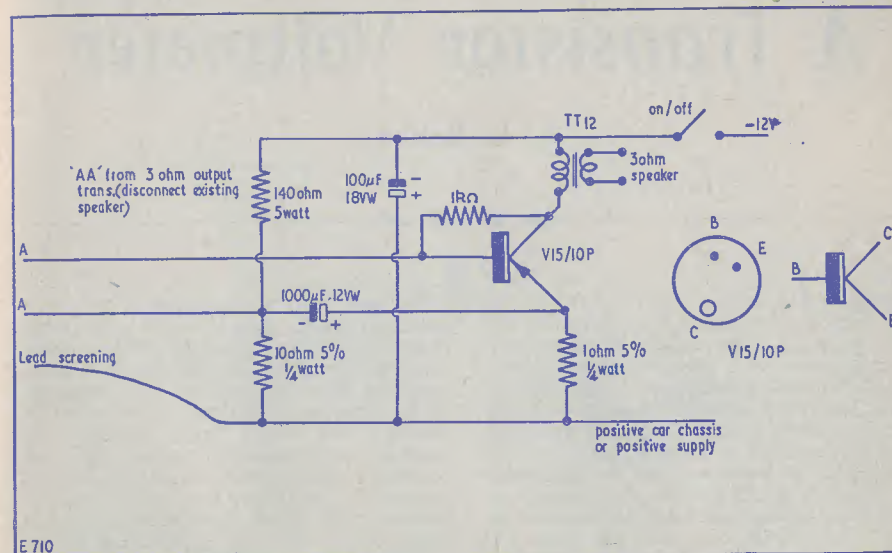The great advantage of this amplifier is that



E710

Components List

Transistor, Newmarket V15/10P
 1,000μF condenser 12V wkg.
 100μF condenser 18V wkg.
 Metal chassis—Henry's Radio Ltd.
 7in x 4in high flux 3Ω speaker
 Single pole On/Off switch
 TT12 O/P transformer—Henry's Radio Ltd.

Resistors:
 1kΩ, 56Ω, 1/4 watt
 10Ω 5%, 1/4 watt
 140Ω 5 watt
 1Ω 5% 1/4 watt
 Tagboard, clips, etc.—Henry's Radio Ltd.

The output power obtained from this amplifier is some 2 watts maximum, and volume control is effected by using the existing control on the receiver. Should the output obtained prove to be an overload on the amplifier input, a 56Ω resistor should be inserted in series with the input con-

with a suitably modified portable radio, the amplifier may be left within the car on such occasions when the portable is required for use elsewhere. The much greater audio output obtained, with no extra current drain on the portable batteries, is an advantage also not to be overlooked.

UNDERSTANDING TELEVISION Continued from page 347

synchronism it is described as the oscillator "hold," or "lock," control.

In Fig. 128 the sync pulse is applied to the grid with the aid of a low-value resistor in series with the secondary of the transformer. There are other ways in which a positive-going pulse may be applied. A typical instance is given when the pulse is applied direct to the grid via a condenser (which should have a capacity markedly lower than

that of the grid condenser). A *negative*-going pulse may also be used to synchronise the oscillator. In this case it would be applied to the anode, whereupon the necessary positive-going pulse at the grid would be obtained via the transformer.

Next Month

In next month's article we shall carry on to discuss the multivibrator.

A Transistor Voltmeter

By L. Baker

THE TRANSISTOR VOLTMETER TO BE described measures from 1 volt to 800 volts d.c. The use of a transistor in a circuit similar to a valve voltmeter enables the instrument to operate at a high value of input resistance which will give results which are comparable to that of the valve voltmeter. Voltages as small as 0.5 of a volt or less are easily read on the meter, and the instrument is especially useful for the measurement of very small voltages such as, for instance, the a.v.c. line voltage of a radio receiver. The number of components is kept to a minimum, the 100 μ A meter M₁ being the most expensive part.

The instrument can be built into a small case; in the original instrument this measured 5 $\frac{3}{4}$ in x 4 $\frac{3}{8}$ in. However, since the only deciding factor as regards the size of the finished instrument is the meter itself, it could be made smaller if so desired, the actual size being left to the intending constructor to suit whatever meter parts he has on hand.

The actual ranges covered by the instrument are:

- Range 1. 0 to 1 volt full-scale
- Range 2. 0 to 10 volts full-scale
- Range 3. 0 to 100 volts full-scale
- Range 4. 0 to 200 volts full-scale
- Range 5. 0 to 400 volts full-scale
- Range 6. 0 to 600 volts full-scale
- Range 7. 0 to 800 volts full-scale

Within the scope of these ranges will be found all d.c. volts encountered in radio receivers, amplifiers, and such like equipment. Both the penlite 1.5 volt dry batteries are housed in the case of the instrument itself. The penlite type is especially suitable for this instrument on account of its small size. The switch S_{3A/B} is ganged with R₉, and serves the purpose of switching off both batteries when the instrument is not in use. It is recommended that both R₁₀ (sensitivity) and R₉ (zero set) are of the wire-wound type. These give better stability and wear than carbon types.

The switch S_{1A/B} is included as a polarity reversing switch. This is useful in the event of connecting the instrument the wrong way round to the voltage to be measured, in which event the meter will attempt to move in the wrong direction. This can be corrected by throwing the switch S_{1A/B} to the other position, whereupon the meter will read correctly. On the front panel this switch is engraved + ground in one position and - ground in the other. With this system it is possible to tell the polarity of the test voltage without tracing the test leads, etc.

The only precision components are the voltage dividers R₁, 2, 3, 4, 5, 6, 7. It is recommended in the interest of accuracy that these be of the 1% type. TR₁ is a Mullard OC71 junction transistor; the use of this Mullard type is advised. However, it is likely that the red spot surplus type of transistor will work equally well in this position. It is probable that some adjustment will have to be made to R₈ in this case. R₈, in any event, is critical and may need some adjustment up or down even with the OC71. The nominal value of 47k Ω is given in the parts list as this was found to be the best value in the prototype instrument.

Construction

All parts are mounted behind the front panel, which in the prototype was of Formica. The actual size of the panel is, of course, dependent on the type of case the intending constructor has in mind. The Formica is drilled to suit the mounting bushings of R₉, R₁₀, S_{1A/B}, S₂ and S_{3A/B}. A hole is cut centrally in the panel to take the flush-fitting 2in microammeter. Holes should also be drilled in the Formica panel for the input socket strip. The clips for holding the batteries B₁, 2 are made from brass strip and are held on the front panel by means of 8BA screws and nuts. Connection to these batteries is made by soldering the appropriate leads directly to each cell electrode, and care

should be taken to see that they are wired properly as shown in the circuit diagram. It is most important that these batteries are properly connected to avoid damage to the meter and transistor.

be a good quality plastic insulated type, and the thin coloured type is advisable. Having installed all parts (less TR₁) and soldered all joints with a good clean soldering iron, TR₁ can be mounted on the tagstrip. Small pieces

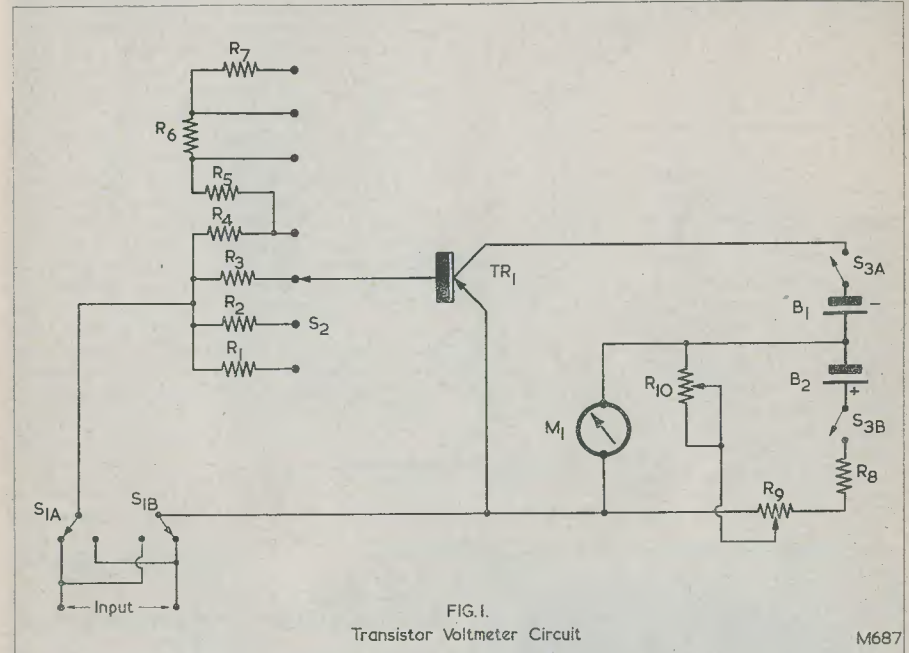


FIG. 1. Transistor Voltmeter Circuit

Components List

- | | |
|---|---|
| Resistors | Meter |
| R ₁ 150k Ω $\frac{1}{2}$ W 1% | M ₁ 100 μ A f.s.d. |
| R ₂ 1.5M Ω $\frac{1}{2}$ W 1% | |
| R ₃ 15M Ω $\frac{1}{2}$ W 1% | Switches |
| R ₄ 30M Ω $\frac{1}{2}$ W 1% | S _{1 a-b} Double-pole, double-throw |
| R ₅ 30M Ω $\frac{1}{2}$ W 1% | S ₂ Single-pole, seven or more-way |
| R ₆ 30M Ω $\frac{1}{2}$ W 1% | S _{3 a-b} Double-pole, single throw |
| R ₇ 30M Ω $\frac{1}{2}$ W 1% | |
| R ₈ 47k Ω $\frac{1}{2}$ W, see text | Batteries |
| R ₉ 50k Ω w.w. potentiometer | B ₁ , B ₂ Ever Ready Penlite |
| R ₁₀ 10k Ω w.w. potentiometer | |
| Transistor | Miscellaneous |
| TR ₁ Mullard OC71, see text | Input sockets, cabinet, screws, nuts, wire, Formica panel, sleeving, etc. |

When all components have been mounted, wiring can be commenced, leaving the wiring-in of the transistor TR₁ until last to avoid damage to this part. The resistors R₁ to R₇ are mounted on the 11-tag strip as shown. Care should be taken when soldering these parts not to apply the hot soldering iron to the leads for long periods; this will avoid their values altering. The wire used should

of sleeving are slipped over the leads of TR₁ leaving enough room to grip the bare lead with small pliers when soldering to conduct away the heat and so avoid damage to the transistor. The batteries should be left out until the actual testing of the completed instrument.

Having installed TR₁, it is now advisable to check and double check the wiring for

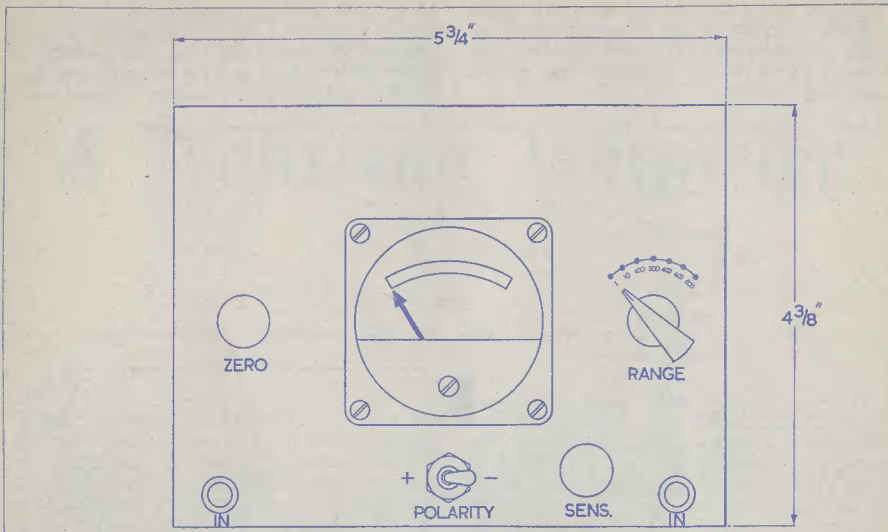


FIG. 2.
Transistor Voltmeter-Front.

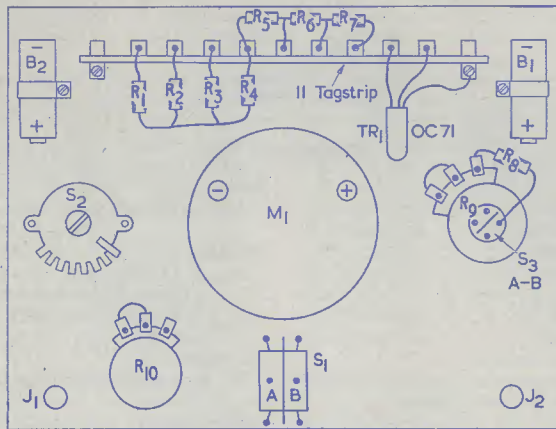


FIG. 3.
Transistor Voltmeter-Rear of Front Panel.

M688

possible errors before connecting the batteries. If all is in order, the batteries can be installed with the instrument switched off.

For the initial testing, a known accurate voltmeter is required plus a source of several voltages such as a radio high tension battery. The resistors R_9 and R_{10} should be roughly

set in the following manner. R_9 should be set so that all the resistance element is in circuit. R_{10} should be set approximately halfway through its travel. Test leads should be connected to the instrument and this switched on. The meter may now be made to read zero volts (with the input leads

shorted) by rotating R_9 in the appropriate direction. R_{10} can be adjusted by rotating it so that as much of its resistance as possible is left in circuit consistent with steady zero on the meter with the test leads still shorted. Once R_{10} (sensitivity control) is set it will not be necessary to move it except occasionally. With a small single dry cell, and using the separate temporary circuit shown, set up one volt exactly as indicated by the known accurate voltmeter. This voltage may now be applied to the transistor voltmeter on range 1. The meter should now move to full scale indicating one volt. Range 2 may be tested using a grid-bias battery, and 4.5 volts and 9 volts checked on this range. The 100 volt range may be checked at several points by means of the h.t. battery, always comparing the readings on the transistor instrument to the known accurate instrument. For the other ranges use can be made of voltages encountered in, for instance, a domestic radio receiver. Check first of all with the known accurate instrument then compare with the transistor instrument, when all the higher ranges of volts should be within, say, 3 or 4 volts.

The instrument may be housed in a small

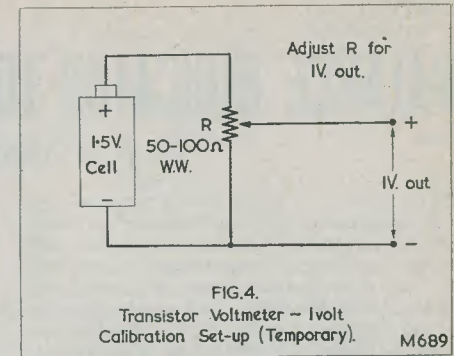


FIG. 4.
Transistor Voltmeter - 1 volt
Calibration Set-up (Temporary).

M689

case made especially for the meter. The writer used one made from 5-ply wood stained and polished, and especially made to suit the $5\frac{3}{4}$ in x $4\frac{3}{8}$ in Formica panel. Formica is obtainable at most hardware stores, and most places have scrap pieces of various colours which can be bought for a few pence. This material has a hard shiny surface which will resist damage and for appearance alone is worth including in the instrument. Other materials such as paxolin are also suitable.


Trade Review

The Heathkit Transistorised Portable Receiver, Model UXR.1

One of the most popular of the Heathkit range must surely be the personal receiver UXR.1. This is a six-transistor superhet receiver, using a printed circuit, and housed in a really good quality leather case; the whole, when completed, presenting an appearance of quality and elegance.

The writer recently had the opportunity of building up one of these kits and has used the receiver extensively since. In spite of it being his first experience of transistor circuits and incidentally of printed circuit construction, the unit worked straight away on completion and a minimum of lining-up was required. No special instruments were required for this process, alignment being carried out without the aid of a signal generator as outlined in the instruction manual for those not possessing such equipment. Everything worked out as detailed, and the receiver was working perfectly a few minutes after the final constructional step was completed. It has given faultless service since.

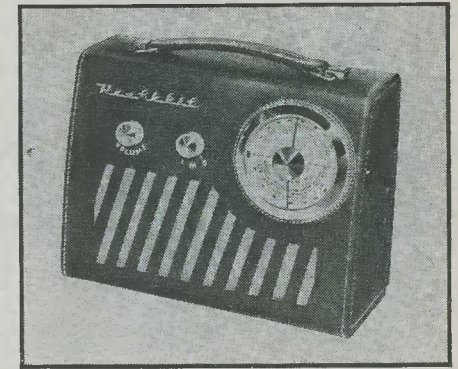The layout of the printed circuit is sufficiently open to give easy construction, and



every component fits nicely into its allotted place. As with all Heathkit equipment, each step has been carefully worked out so that an ideal sequence of construction is followed. Beginners need have no fear that the construction of what, at first, appears to be a somewhat complicated receiver will be beyond their capabilities. Provided they can make a soldered joint cleanly and quickly, the "step-by-step" procedure will keep them on the straight and narrow path to success. This kit is an excellent one which we can thoroughly recommend, and is one which will give the constructor a personal receiver of which he can be really proud.

BALANCE INDICATOR FOR STEREO AMPLIFIERS


By D. J. LINSEY, A.M.I.P.R.E.

TO OBTAIN THE BEST RESULTS FROM ANY equipment, whether it be mechanical or electrical, it is essential that each part of that equipment should function correctly.

In a stereophonic system the two volume levels should be equal. This can be done by fitting a balance control which varies the gain of each channel. Unfortunately, if the balance control cannot be adjusted from the listening position it is impossible to get the two levels equal.

To overcome this some means of level

indication is required, and the diagram shows a circuit of such an indicator. Two out-of-phase and equal-in-amplitude signals are applied to the inputs of the amplifier, the two speakers being strapped together. (This is done so that the two out-of-phase signals are applied to each of the speakers simultaneously—two out-of-phase signals equal in amplitude give little or no output.) The balance control is adjusted for minimum signal, the speakers are next unstrapped, and the equipment is then set up.

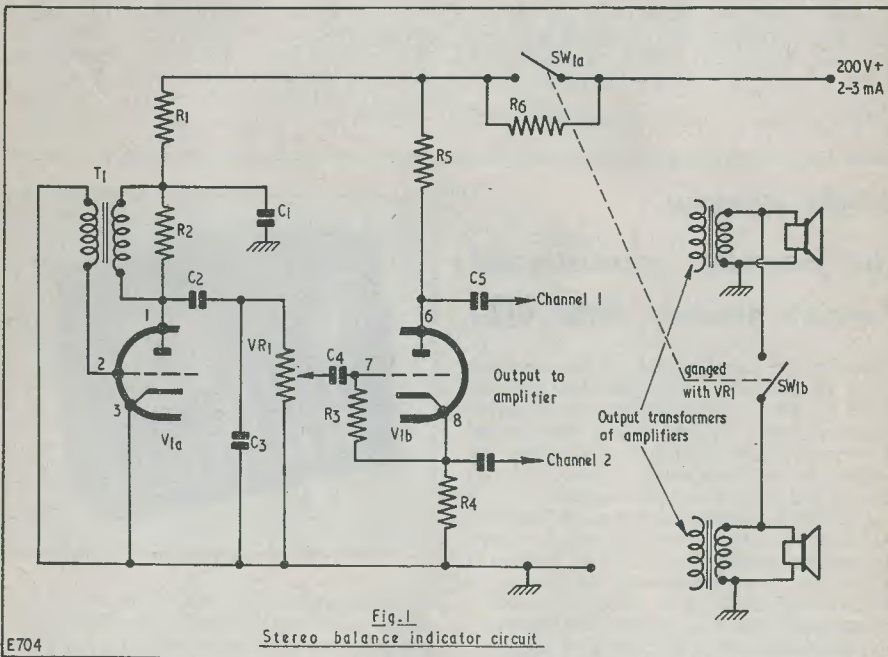

Components List

Resistors—all $\frac{1}{4}$ W

R ₁	100k Ω
R ₂	10k Ω
R ₃	10M Ω
R ₄	100k Ω $\pm 2\%$
R ₅	100k Ω $\pm 2\%$
R ₆	1M Ω

Transformer

T ₁	Radiospares FB5
----------------	-----------------

Capacitors

C ₁	0.1 μ F
C ₂	0.002 μ F
C ₃	0.001 μ F
C ₄	0.002 μ F
C ₅	0.002 μ F
C ₆	0.002 μ F

Valve

V _{1a-b}	ECC82 or equivalent
-------------------	---------------------

Operation

The circuit consists of a twin triode (ECC82). The first triode operates as a simple transformer-coupled oscillator, working at a frequency of approximately 600 c/s, the output being fed via VR₁ output control to a concertina phase-splitter. The two out-of-phase outputs are fed into the pick-up terminals of the stereo amplifier.

The volume control is fitted to vary the output to the amplifier, thus allowing the unit to be used for high or low settings of the amplifier volume control. It should be noted

that the indicator can be used for either single-ended or push-pull amplifiers since the balancing is done by the output from the speakers.

Component values are not at all critical except those of R₄ and R₅, which should be matched to within 2% to give the equal outputs required.

The double-pole switch is ganged to the volume control, SW_{1a} being shunted by R₆ (1 M Ω) thus allowing a low anode current to flow during non-operation, which extends the life of the valve. SW_{1b} is connected across the speakers as shown.

MISCELLANEOUS

A VERTICAL TRAPPED DIPOLE ANTENNA

By ARTHUR C. GEE, G2UK

THE SEARCH FOR THE "PERFECT AERIAL" WILL NO DOUBT continue for as long as radio amateurs exist. The aerial to be described fulfils the author's requirements more satisfactorily than any other which he has so far used. Briefly, his requirements were: for use on 14-21-28 Mc/s primarily, freedom from unwanted directional effects, good Dx characteristics, ease of erection and an ability to stand heavy weather, rapidity of band-changing facilities and a compact, neat appearance.

The type of aerial which meets most of these requirements is, of course, the vertical dipole. However, these are too long to be readily put up by the amateur with the usual facilities. The ground plane is the next best thing, but the radials present a problem in space requirements and erection.

Turning over the advertisement pages of one of the radio periodicals, Mosley's range of aerials caught my interest. Could one use two "top-half" elements of their multiband ground plane antennas, mounted end to end up the side of a thirty foot wooden pole, feed the arrangement at the centre with twin feeder or coax, thus getting a rigid, stormproof, all-round-the-compass, low angle of radiation, compact antenna? There seemed no reason why it should not work. So Mr. O. J. Russell, G3BHJ, Mosley's British manager, was consulted and he agreed that the idea was a most interesting one, particularly as on first principles it would seem that it should work well and also because such an arrangement should appeal to the many amateurs whose space limitations are severe and whose "neighbour-reaction" is not favourable to elaborate aerial systems. He carried out some initial tests, which appeared to confirm that the idea was feasible and that approximately 80 ohm twin feeder seemed to produce the best compromise match. The necessary components were delivered to G2UK's QTH and the aerial erected as indicated in the accompanying illustration.

Results have passed all expectations. The centre of the aerial is approximately 22 feet above ground. It has been tested out with a home-built 60 watts transmitter and with an LG.300, both with pi-couplers coupled straight into the twin feeder so that switching from band to band is instantaneous. Excellent Dx contacts have been consistently maintained.

Mosley's have now decided to market this antenna as one of their standard lines. It has been designated Type TA31 Jr., and is available at £10. Their address is 15 Reepham Road, Norwich, Norfolk.



The TRANSITONE

A simple transistorised electronic organ

By J. G. Ransome

THIS LITTLE ELECTRONIC ORGAN IS VERY simple to construct and should meet the demands of the one-finger pianists who want to "go electric." Alternatively, it would make an ideal birthday or Christmas gift for a child. The inclusive cost of the electronic side of the instrument need not be more than 30s. even if every component is purchased new. The organ consists of two parts, the note generator and the output stage. The output stage is very simple and needs no explanation.

The note generator is shown in its basic form in Figure 1. The "old hands" will, of course, recognise it as our old friend, the multivibrator, but for the less experienced a word or two of explanation will not be out of place. Two waveforms are available from this type of oscillator, and these are depicted in Figure 1. The operation of the circuit is as follows: consider initially that TR₁ is fully conducting and TR₂ is cut-off (i.e., not conducting). When TR₁ is fully conducting it offers practically zero impedance and so almost all of the battery voltage appears across the collector load resistor R₁. C₁ then begins to charge and, as it does so, the base of TR₂ is driven negative until TR₂ conducts; C₂ then discharges, biasing off the base of TR₁ and cutting it off; but as TR₂ conducts C₂ charges through R₂ and slowly drives the base of TR₁ negative until it conducts, C₂ then discharging and cutting off TR₂. The cycle of operations then repeats itself producing a continuous oscillation.

The frequency of operation is given by the following expression:

$$f = \frac{1}{0.7 C_1 R_1 + 0.7 C_2 R_2}$$

where the capacitance is in farads and resistance is in ohms.

If we make C₁=C₂, we may simplify the expression to:

$$f = \frac{1}{0.7 C (R_1 + R_2)}$$

Using the above formula, we may now proceed to the final circuit. The complete circuit for the electronic organ is shown in Fig. 2.

As will be seen the oscillator section does not depart very far from the basic circuit

outlined in Fig. 1, save that the timing resistor associated with C₁ now consists of two parts R₁ and R_x. R₁ is fixed and has a fairly low value and is used to prevent damage to TR₂ should any trouble occur on the keyboard. R₂ has a fixed value and a value of about 27kΩ is chosen for the final design. The oscillator may be keyed by switching in various pre-set variable resistors in series with R₁ to "h.t."

The output stage consisting of TR₃ is fairly conventional and any audio output transistor may be used. T₁ will have to be matched to the transistor used.

R₅ is an h.t. compensation resistor. Since the frequency of the oscillator is dependent upon the h.t. applied, the frequency of the oscillator will tend to drift as the h.t. battery ages—R₅ is incorporated to compensate for this drift. It is set to maximum resistance with a new battery and then is gradually reduced in value as the battery ages and the organ goes out of tune.

The value of R_x may be calculated from the above formula and the final value found by experiment.

For instance;

taking C₁=C₂=0.1μF or 1 x 10⁻⁷ farad and R₂=27kΩ

then for a note of middle C (f=256 c/s) R_x will be

$$f = \frac{1}{0.7 C (R_1 + R_x)} \text{ or } R_1 + R_x = \frac{1}{0.7 C f}$$

$$\therefore R_x = \frac{1}{0.7 C f} - R_1 \text{ ohms}$$

$$\text{or } R_x = \frac{1}{0.7 \times 1 \times 10^{-7} \times 256} - 27,000 \approx 33k\Omega$$

or for a note two octaves above (i.e., f=1,024 c/s)

$$\text{taking } C_1=C_2=0.05\mu\text{F or } 5 \times 10^{-8} \text{ farad } R_1=27k\Omega$$

$$R_x = \frac{1}{0.7 C f} - R_1 \text{ ohms}$$

$$\text{or } R_x = \frac{1}{0.7 \times 5 \times 10^{-8} \times 1,024} - 27,000\Omega \approx 1k\Omega$$

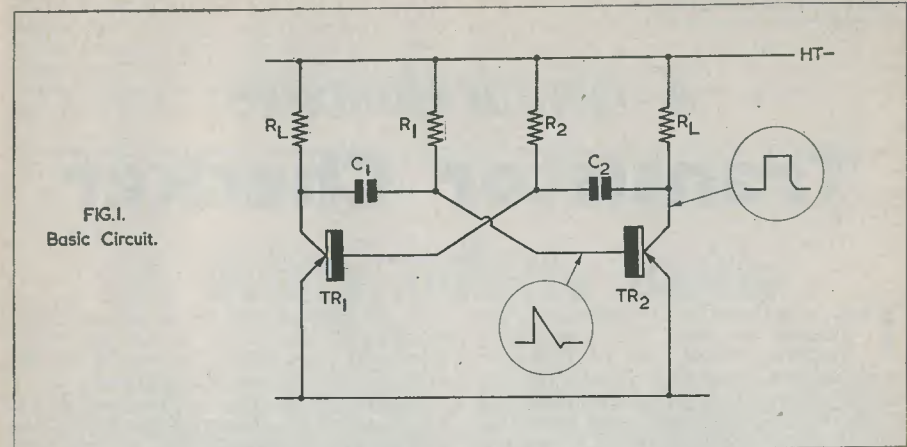


FIG. 1. Basic Circuit.

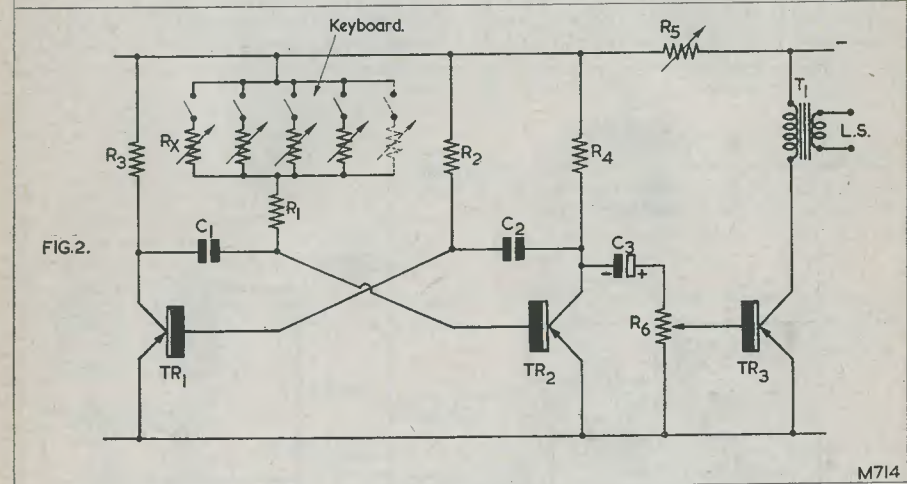


FIG. 2.

M714

Components List

Resistors

- R₁ 500Ω
- R₂ 27kΩ
- R₃ 1kΩ
- R₄ 1kΩ
- R₅ 10kΩ variable
- R₆ 1MΩ variable

Capacitors

- C₁ See text
- C₂ See text
- C₃ 2μF 6V wkg. electrolytic

Miscellaneous

- TR₁ and TR₂—any audio transistor (Red Spot, etc.)
- TR₃ Output transistor
- T₁ Transformer to match
- R_x Variable resistors, quantity according to number of notes to be produced.

All other values may be calculated as above. The value calculated will not be exact because the calculation depends on the value of R₁ and if a 20% resistor is used in this position the value of R_x will only be approximate; but it is sufficiently accurate for our purposes.

The layout is in no way critical and any form may be adopted. The mechanical side is left to the reader but the original unit was constructed inside a small toy piano, the keys being used to make off a series of contacts to bring in the various note producing resistors.


A Comprehensive Transistor Checker

By J. Anderson

THIS INSTRUMENT WAS DESIGNED WITH economy in mind, but economy in transistors rather than of parts, for admittedly it is rather more complex than the majority of testers. It provides rough checks, characteristic measurements, and gain readings, as well as collector current values, and is suitable for the majority of both point-contact and junction transistors.

type the increase will be in the region of 1.5mA. (It should be noted that some transistors may require only 4.5V in the collector line and not 10V as shown).

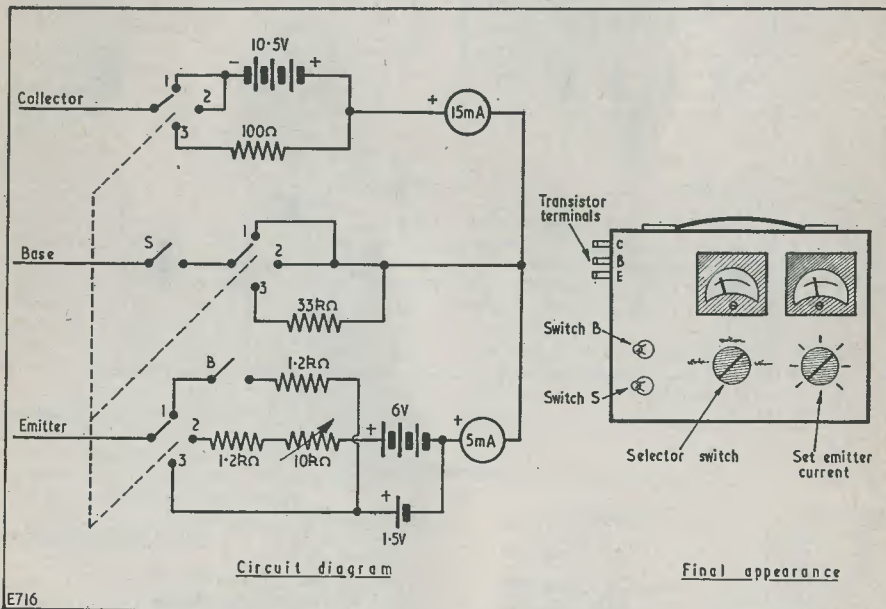In position 2, the modification of the circuit allows the emitter current to be controlled and measured, and a group of characteristics to be plotted ($I_c:V_c$ for various values of I_e). During this test switch "S" is,



E716

The selection of these facilities is, as will be seen, provided by a three-bank rotary switch.

When this is in position 1, a transistor may be checked by the fact that when switch "B" is open the current will be less than 1mA for a point-contact transistor, and less than 20μA for most junction types. If transistor action is occurring when "B" is closed, then for a point-contact transistor the current will rise by from 2 to 4mA, whilst for a junction

of course, closed.

When the rotary switch is in position 3, then, with switch "S" open, the meter will read I_{co} which should be in the region of 150μA or $\frac{1}{30}$ full scale. On closing "S" the meter will read current gain or α , which will be found by multiplying the reading by 10—that is, an f.s.d. of 150 units.

The unit is very safe to use, as with wrong connections (if made) the current will be limited, for the most part, by the resistances

in the collector and base lines. The author constructed his instrument in a plastic box (easily obtained under the pseudonym of a "lunch box") 6in x 8in x 2½in, with three spring terminals as well as a transistor holder on one end, and a small handle on top.

Current drain is so low that the batteries were wired in, but the experimenter may wish to substitute wander plug sockets for the 4.5/10.5 collector battery; the voltage of this battery can be checked at switch position 1, terminals B and C.

MISCELLANEOUS

A Utility Infinite Baffle

By. A. H. Strange

The small speaker enclosure is becoming increasingly popular, for which there is good reason, since the sound produced is pleasing; also, its size conforms with modern homes, and therefore generally meets with the approval of the lady of the house. However, it will be admitted that its compactness is dictated by necessity and economy, and that the large enclosure remains superior and the true infinite baffle unsurpassed.

Bearing this in mind, I suggest that many have almost a ready-made infinite baffle in the shape of a fireplace which perhaps is no longer used for heating as a more modern method is now employed. If this be so, a speaker could be mounted on a substantial

baffle board large enough to fit tightly into the opening of the fireplace, with felt glued to the four edges to ensure an airtight enclosure. An infinite baffle has now been produced, which when finished by covering the whole board with speaker fabric is very much cheaper and less likely to cause dissension than cutting the legendary hole in the wall.

It may be argued that a resonance could be set up by the air column of the chimney; if this was so, the frequency would be below cut-off of the speaker due to the column length, and it would be damped by the porous nature of the bricks and soot.

Trade Review

TELETRON "TAPEJAK"



The Teletron "Tapejak", illustrated herewith, is a transistorised a.m. tuner unit powered by a 9V battery (Ever Ready PP4). It is the first transistorised radio tuner specially designed for use with tape recorders, and simply connects to the latter by inserting the jack plug into the microphone socket, the aerial lead then being uncoiled. The signal pick-up from this aerial energises a high-Q ferrite-cored input coil coupled to an r.f. transistor. The resultant amplified signal output from this stage is matched to a crystal diode by means of a tuned r.f. transformer, the rectified signal then being conducted, via a screened cable, to the terminating jack plug.

Internal pre-set condensers permit the unit to be adjusted for the reception of any two Medium wave local programmes, plus the permanent reception of the 1500 metre Long wave programme.


The standard type of jack plug, as illustrated, is fitted to all units, but alternatives can be fitted on request.

The Teletron "Takejak," which permits the recording of radio programmes directly on to tape, is modestly priced at £5 9s. 0d., tax paid, less battery. A high-gain version of the Tapejak, with an additional built-in pre-amplifier, is also available at £6 13s. 9d., tax paid, less battery. Both types are, of course, completely built and tested before despatch. The "Tapejak" is available direct from the manufacturers—The Teletron Co. Ltd., 112b Station Road, London, E.4, or from most radio retailers advertising in this magazine. Trade enquiries should be directed to Sam Mozer Ltd., 288 Hedge Lane, London, N.13. Telephone: PALmers Green 1748.

*** Ideal Xmas Present

PHOTOGRAPHIC SLIDE CASE 17/6

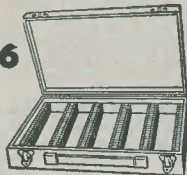Size 8" x 12 3/4" x 2 1/2" deep. Will hold 150 of those expensive coloured transparencies in separated partitions. This is the answer to that aggravating search for that particular photograph and will, of course, keep them safe from damage. Post 2/6.



HOME RADIO 79/6

AC/DC. Universal mains 5 valve octal superhet 3 waveband receiver can be adapted to gram. p.u. In attractive wooden cabinet 9 1/2" x 18 1/2" x 11 3/4". Carr. and Ins. 4/6.



EXTENSION SPEAKERS 19/9

Polished oak cabinet of attractive appearance. Fitted with 8" p.m. speaker W.B. or Goodmans of the highest quality. Standard matching to any receiver (2-5 ohms) Switch and flex included. Carr. and Ins. 3/9.

DUKE & CO

(DEPT. K.12) 621/3 ROMFORD ROAD
MANOR PARK E12 ILF 6001/3

Deferred terms to suit all pockets

Monthly credit terms or weekly easy payments—
Details on request.


AS FEATURED IN THIS ISSUE

POWERFUL! PERSONAL! PORTABLE!

(Trade Enquiries invited)

- ★ Sturdy metal case
- ★ No holes to drill
- ★ Detachable rod aerial
- ★ All batteries self-contained
- ★ Can be built in 1 hour—
- ★ Covers medium waves
- ★ Loud clear tone
- ★ Selective tuning
- ★ All parts are sold separately

FOR ONLY **35/-**

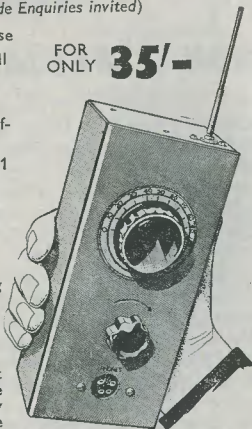

This delightful set is designed to give you a completely personal portable radio.

Bronze-finished case. Ideal for the beach, the bedroom, the office—in fact, anywhere.

Send 2/- for wiring diagram and component price list

R.C.S. PRODUCTS (RADIO) LTD
11 Oliver Road London E17 Mail Order only

REPANGO HIGH GAIN COILS

Dual Range Crystal Set Coil, Type DRX1	2/6		
Dual Range Coil with Reaction, Type DRR2	4/-		
Matched Pair Dual Range T.R.F. Coils, Type DRM3	8/-		
Pair Dual Range Superhet Coils, Type SH4	8/-		
Miniature Iron Dust Cored Coils, Type "R"	each 3/3		
Range	Aerial	H.F.	Osc.
800 2,000 m.	RA1	RHF1	RO1
190 550 m.	RA2	RHF2	RO2
70 230 m.	RA3	RHF3	RO3
15 50 m.	RA4	RHF4	RO4
Ferrite Rod Aerial, Dual Range Type FR1	12/6		
Miniature I.F. Transformers, Type MSE (465 kc/s)	pair 12/6		
Standard I.F. Transformers, Type TCG (465 kc/s)	pair 13/6		

Send S.A.E. for latest Repango Component Catalogue

Radio Experimental Products Ltd.

33 Much Park Street, COVENTRY
Telephone 62572

Ask "ARTHURS" First

NOTE NEW ADDRESS AT
125 Tottenham Court Road
London WC1

Close to Warren Street Station

You will have the same service and obtain all your requirements in Radio Components, Electrical Goods, Accessories and Television as previously.

Test Instruments in stock include Avo, Advance, Cossor and Taylor. List on request

VALVE MANUALS AVAILABLE
Mullard 10/6 Brimar No. 7 6/-
Osram Part 1, 2nd Edition 7/6
Post and packing 9d. each extra

Arthurs first

Est. 1919

Proprietors ARTHUR GRAY LTD


Gray House
125 Tottenham Court Road
London WC1

Telephone EUSton 5802/3/4



RECORD PLAYER BARGAIN OFFER

A self-contained Portable unit comprising the latest Collaro 4-speed Auto Changer Record Player, incorporating the famous High Fidelity Studio "O" Xtal Pick-up with Turnover Cartridge, and fitted with L.P. and 78 Sapphire styli. An internal 2 valve amplifier of modern design with variable tone and volume controls is fitted. Quality 6" P.M. speaker Robust wooden cabinet attractively styled in maroon with polka dot relief

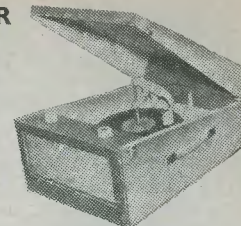

Collaro 4-speed autochanger, 2-valve, 2-stage amplifier, ready wired, complete with speaker, etc., Cabinet with mounting board, etc. Size 18 1/2" x 13 3/4" x Ht. 8 1/2"	£6.19.6 + 4/6 carr.
	£3. 7.6 + 2/6 carr.
	£2.12.6 + 3/6 carr.

This is a recommended bargain buy and when present stock is exhausted cannot be repeated. Originally built to be sold at 17 gns.

This complete 3 unit Record Player Kit offered at

£12-19-6 carriage free.

RECORD PLAYER BARGAINS

All Brand New and Latest 4-sp. Models

SINGLE PLAYERS. B.S.R. (TU9) 90/-; Collaro (4/564) 6 gns.; Garrard (4SP) £7.10.0; Garrard (TA Mk 2) £8.19.6. Carr. and ins. 3/6.
AUTO CHANGERS. B.S.R. (UA8) £6.19.6; Collaro (Conquest) £7.19.6; B.S.R. (UA12) with stereo and monaural cartridge, 10 gns. Garrard (RC121/4D/Mk 2) plug in head and stereo adapted, 10 gns. Carr. and ins. 4/6. Garrard GCS/10 stereo head £2 extra. Replacement Sapphire Styli available all units.

RE-GUNNED TV TUBES new budget prices

and now 12 months guarantee!

All tubes rebuilt with new heater, cathode and gun assembly-reconditioned virtually as new:

12"-£6, 14"-£7, 17"-£8.10.0 etc
10/- part exchange allowance on old tube
Carr. and ins. 10/- Comprehensive Stocks—quick delivery

BAND III TV CONVERTER

180 Mc/s-205 Mc/s (Channels 6-13)

Suitable London, Birmingham, Northern, Scottish, Welsh and I.O.V. ITA transmissions.
Mk. 2 Model. Latest cascade circuit using ECC84 and EF80 valves giving improved sensitivity (18 dB) over standard circuits, built-in power supply a.c. 200-250V. Dimensions only 6 1/2" x 3" x 4". Simple and easy to fit—only external plug-in connections. Wired, aligned and tested ready for use. State channel required. Guaranteed. Bargain offer—good results or full refund. **ONLY £3.19.6** Carr. and pkg. 2/6
Recommended Addition—Band I/Band III changeover switch and B.B.C. aerial socket fitted and wired internal with converter 8/- extra.

7 VALVE AM/FM RADIOGRAM CHASSIS BARGAIN OFFER MANUFACTURERS SURPLUS

Latest type ECC85 series valves with 3 watt EL84 Output Med., Long and V.H.F. Wavebands with Switched Gram Position. Magic Eye Tuning. Illuminated glass dial 1 1/2" x 3 1/2". 4 controls. Chassis size 13 1/2" x 6 1/2" x 7 1/2" ht. A.C. 200/250V. Aligned and tested ready for use. Carr. **£13.10.0** and ins. 5/-. Complete with 4 knobs—walnut or ivory to choice. P.M. speakers only required, 8" 20/-, 10" 25/-.
TRANSISTORS—BVA 1st Grade
Mazda XB102, XB104, each 10/-, XA103, 15/-, XA104, 18/- G.E.C. GET3, 10/6, etc. OA81, 3/6. GEX34, 4/-, Mrs. surplus (recommended and tested perfect). OC71, OC72, each 7/6. OC45, 12/6. OA70, 3/-.



Est. 1946

RADIO COMPONENT SPECIALISTS

70 Brigstock Road Thornton Heath Surrey

Telephone THO 2188

Terms: C.W.O. or C.O.D. Post and packing up to 1/2 lb 7d., 1 lb 1/1 3 lb 1/6, 5 lb 2/-, 10 lb 2/9

COAX 80 ohm CABLE—Stand. 1/4" diam.

Low Loss Semi-Air Spaced AERAXIAL, polythene ins.

SPECIAL REDUCED PRICES

20 yds 12/6, P. & P. 1/6; 40 yds 22/6, P. & P. 2/-; 60 yds 32/6, P. & P. 3/-. All other lengths 8d. yd. Coax Plugs 1/-, Coax Sockets 1/-, Couplers 1/3 Cable End Sockets 1/6, Outlet Boxes 4/6.

C.R.T. Heater Isolation Transformers

New improved types—mains prim. 200/250V tapped

All isolation transformers now supplied with alternative no boost, plus 25%, and plus 50% boost taps, at no extra charge. All standard individual voltages available: 2V 2A—13V 0.3A (as previously advertised)

each 12/6 P. & P. 1/6

Small size and tag terminated for easy fitting

LOUDSPEAKERS. P.M. 3 ohm, 2 1/2" Plessey, 17/6; 3 1/2" Goodmans, 18/6; 5" R. & A., 17/6; 6" Celes., 18/6; 7 1/2" x 4" Goodmans, 18/6; 8" Rola, 20/-; 10" R. & A., 25/-; 12" Plessey, 30/-, etc

SPEAKER FRET. Expanded bronze anodised metal: 8" x 8", 2/3; 12" x 8", 3/-; 12" x 12", 4/6; 12" x 16", 6/-; 24" x 12", 9/-, etc. TYGAN FRET (Contemp. pattern) 12" x 12", 2/-; 12" x 18", 3/-; 12" x 24", 4/-, etc.

VOLUME CONTROLS

Log. or lin. ratios, 10,000 ohms-2 Megohms. Long spindles. 1 year guarantee. Midget Ediswan type, 1 1/2" dia. No sw. 3/-, d.p. sw. 4/6.
TWIN GANGED CONTROLS. 1/2 Meg. 1/2 Meg. 1 Meg. less sw., each 8/9.

SPECIAL OFFER

Superior type art leather-covered portable case. Well known manufacturer's surplus, in attractive tone colour with non-tarnish gilt fittings. Size 15" x 11 1/2" x 5 1/2". Knock-out price 15/6, p. and p. 2/6.

CAR RADIO KIT. This popular Hybrid printed circuit 12V Car Radio as recently featured in *The Radio Constructor* is now available.

Complete Kit incl. Speaker **ONLY £12.19.6** P. & P. 3/6

Comprehensive Instruction Booklet 3/6 (free with kit)

VALVES—NEW REDUCED PRICES. 1R5, 1T4, 7/6; 1S5, 7/6; 3S4, 3V4, 8/-; 5Z4, 9/6; DAF96, 9/-; DF96, 9/-; DK96, 9/-; DL96, 9/-; ECL80, 10/6; ECL82, 11/6; EF80, 9/6; EF86, 13/6; EF91, 8/6; EL84, 9/6; EY51, 10/-; EY86, 10/-; EZ80, 7/6; MU14, 9/6; PCC84, 10/6; PCF80, 10/6; PCF82, 10/6; PCL83, 12/6; PL81, 12/6; PL82, 9/6; PL83, 11/6; PY80, 7/6; PY81, 9/6; PY82, 7/6; U25, 12/6, etc. Send for list.

SPECIAL. 1R5, 1T4, 1S5, 3S4 or 3V4, per set, 27/6; DK96, DF96, DAF96, DL96, 35/-; 6K8, 6K7, 6Q7, 6V6, 5Z4 or 6X5, 35/-.

Hours 9 a.m.-6 p.m., 1 p.m. Wed.

SMITH'S of Edgware Road

ELECTRONIC COMPONENT
DISTRIBUTORS FOR OVER 25 YEARS

BLANK CHASSIS

Precision made in our own works from commercial quality half-hard aluminium of 16 s.w.g. (1/16" thickness, these chassis go all over the world (and off it—in rockets!). Same day service for ANY SIZE, to nearest 1/16" and up to 17" of straightforward two, three or four-sided chassis. Orders for specials dealt with promptly if sent with clear instructions.

SOLDERED CORNERS. While these chassis, owing to their thickness, hardness and efficient folding, will carry components of considerable weight and normally require no corner strengthening, we can do this, if required, by a special soldering technique at 6d. extra for each corner.

FLANGES. 1/4", 3/8" or 1/2" flanges (inside or outside) 6d. extra for each bend.

PRICE GUIDE (normal chassis only)

Work out total area of material required, including waste, and refer to table below:

48 sq. in.	4/-	176 sq. in.	8/-	304 sq. in.	12/-
80 sq. in.	5/-	208 sq. in.	9/-	336 sq. in.	13/-
112 sq. in.	6/-	240 sq. in.	10/-	368 sq. in.	14/-
144 sq. in.	7/-	272 sq. in.	11/-	and pro rata	
	Post 1/3		Post 1/6		Post 1/9

Discount for quantities. Trade enquiries invited. Spray finish arranged for quantities of 25 or over.

PANELS. The same material can be supplied for panels, screens, etc. Any size up to 3ft at 4/6 sq. ft. (sq. in. x 8). Post, up to 72 sq. in. 9d., 108 sq. in. 1/3, 144 sq. in. 1/6, 432 sq. in. 1/9, 576 sq. in. 2/-.

287/289 EDGWARE ROAD LONDON W2
Telephone PAD 5891/7595

BUILD YOUR OWN



MAYKIT TRANSISTORISED CAR RADIO

- ★ HYBRID DESIGN—5 VALVE SUPERHET, TRANSISTOR AND PRINTED CIRCUIT
- ★ STANDARD SIZE 7" x 2"—12V BATTERY
- ★ ALL NEW COMPONENTS—AVAILABLE SEPARATELY OR IN COMPLETE PACK

First and best DO-IT-YOURSELF Car Radio. Uses new Brimar low volt valves no vibrator. Printed circuit and power transistor. Negligible "fade" and no "buzz." Only 1.5 amp. consumption. Complete with chassis assembly, filter box and output stage including elliptical loudspeaker and detailed instructions. Also Jason Car Radios. Send 3/6 for Car Radio booklet.

Service facilities available

Can be built for **£13.10.0** plus 5/- p. & p.

Cash with order

or write for BUY-AS-YOU-BUILD details

Dept. D MAYRA ELECTRONICS LTD

118 BRIGHTON ROAD . PURLEY


Telephone Bywood 1263

A REVOLUTIONARY NEW BRITISH INVENTION!

- ★ Uses standard tapes
- ★ Plays at 7 1/2" per. sec. or 3 other speeds
- ★ Records direct from radio or microphone

Results equal to a £50 recorder — yet costs only £13 12s. (or £17. 11s. complete with special moving-coil microphone and 600 ft. reel of tape).

EASY TERMS

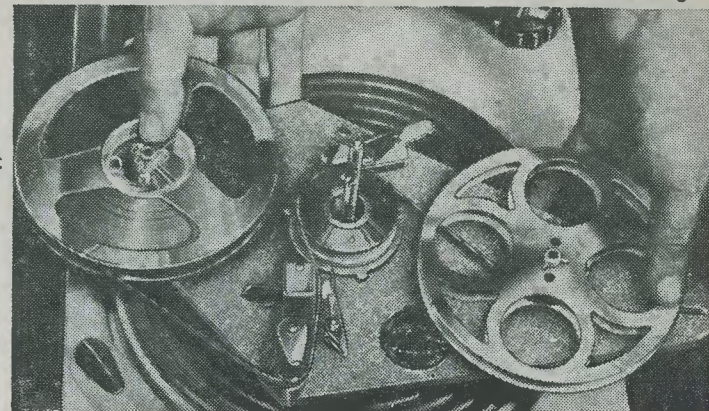

Instantly turns any gramophone into a first-class Tape-Recorder and back into a record-player in a moment!

Gramdeck is completely new . . . a revolutionary and ingenious invention that instantly turns your gramophone into a tape-recorder and back into a gramophone at will! Slip the Gramdeck on to your turntable and you have the finest tape-recorder you've ever heard! Lift it off . . . your gramophone is ready to play records again. There are no motors or valves to go wrong—and you get reproduction that has to be heard to be believed.

"Ingenious—simple . . . why on earth did no one think of it before!"—THE TAPE RECORDER.

"Ingenious and robust."—BRITISH SOUND RECORDING ASSOCIATION JOURNAL.

"Quality of reproduction excellent . . . real hi-fi results . . . potential is tremendous . . . both designer and manufacturer should be congratulated."—BRITISH RADIO & TV RETAILERS' REVIEW.

"Better than many so-called hi-fi recorders . . . robust . . . carefully designed . . . excellent value."—AMATEUR CINE WORLD.

Everyone is praising the Gramdeck. "The quality is at least equal to that obtained from a good microgroove disc," says a leading professional journal.

WORKS FROM ANY RECORD PLAYER OR RADIOGRAM

Gramdeck records and reproduces with a wonderful depth and breadth of tone. Because it uses equipment that is already in your gramophone it only costs a fraction of the high-quality tape-recorder you would normally require. Full details, specifications, photographs, easy terms, etc., are given in the Gramdeck Book. Send for your FREE copy today.

MADE BY THE FIRM THAT MAKES MICROWAVE WAVEGUIDES FOR VISCOUNTS AND BRITANNIAS

FREE BOOK—POST NOW!

I would like to know how to turn my gramophone into a first-class tape-recorder . . . please send me the Gramdeck Book—FREE and without obligation.

(Write if you prefer not to cut coupon.)

NAME

ADDRESS

Gramdeck
GRAMOPHONE TAPE RECORDER

GRAMDECK (Dept. RC/805)
29 Wright's Lane Kensington London W8

GRAMDECK TURNS A TURNTABLE INTO A TAPE-RECORDER

Radio Amateur Operator's Handbook

Indispensable to the Amateur Transmitter
and Short Wave Listener


More than ever, now that the Dx season is in full swing, will the latest edition of this essential aid to operators be in constant demand and use. This extremely handy and informative book should be readily to hand at every operating position—containing as it does, complete details of all information which is constantly required.

The contents include complete Amateur Band Prefix Lists, both Alphabetically and by Country, the 40 Radio Zone Areas, Call Areas, Mileage Tables of over 200 cities and towns throughout the world, the latest amended list of QSL Bureau addresses, the "Q" and other radio codes, WVVV and MSL schedules, Record Charts for scoring and QSL purposes of (a) World Prefixes on 5 Bands, (b) American States, (c) the 40 Zones and (d) British Isles Counties Heard/Worked on 4

Bands, Maps of Dx Areas, Morse Code, Amateur Transmitting Licence details, Amateur Abbreviations, Local Time Conversion List, Amateur Bands Frequency Allocations, Directional Bearings, Frequency/Wavelength Conversion Chart, as well as articles on working the VHF Bands and Amateur Bands Dx Operating Techniques.

PRICE 3/6 Postage 4d.

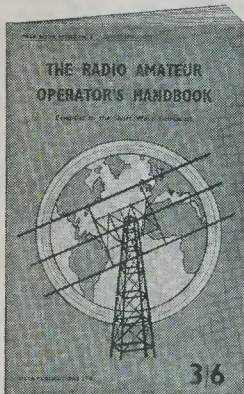DATA PUBLICATIONS LTD 57 Maida Vale London W9



Tuning Condensers. Small twin, 500pF, 7/11; Standard twin, 500pF, 5/11; a.m./f.m. twin 500/twin 27pF with geared 8:1 drive, bargain 8/9; **small dielectric .0001µF, 3/-; 0.0003µF, 3/9; 0.0005µF, 4/-.** Extra small 500pF, 4/6.

Trimmers. Air spaced 3/50pF, ceramic variables, 1/6. 20pF ceramic preset, 11d. 3 x 100pF on metal plate, 1/-; 2 x 60pF +2 x 200pF, or 4 x 60pF (separable into pairs), 3/-; Single postage stamp (various values), 1/-.

Resistors. ½ and ¼ watt carbon, 9d. each Well mixed assortment (many close tolerance), 25 for 3/11; 50 for 7/6. **High Stabs.** 10% ½W, 6d.; 10% 1W, 9d.; 1% ½W, 2/-; Other types available. **Wire-wound** 10% 5W., 1/3; 10W, 1/6; 15W, 1/9.

Capacitors. Electrolytic, 32+32+8µF, 275V, 2/8; 32+32µF 450V, 4/-; 16+16µF 500V can, 4/6; 8+16µF 500V can, 4/-; 8µF 450V 2/3; 50 +50µF 450V, 4/6. Many other values (electrolytic and paper) in stock. **Subminiature electrolytic** 8µF 6V, 16µF 5V, 32µF 3V, 5µF 12.5V, 5µF 40V, 16µF 6V, 25µF 6V, 8µF 25V, etc., all 3/-; **Silver Mica** from 8d. **Paper** from 10d.

GIFT IDEAS

All these are popular items which would be appreciated by the hobbyist. Those starred are especially suitable for the younger constructor.

★**Preset Crystal Receiver Kit.** For home and light on medium waveband. No case or chassis, 8/-.

★**Dual Wave Crystal Receiver Kit.** Tuneable over long and medium waveband. With metal chassis having printed dial, 12/-.

★**"Ajax" Crystal Set Kit.** The well-known receiver designed by Teletron. Complete with case and chassis. M.W., 15/-.

★**Valve Receiver Kit.** Excellent 'phone reception. Complete with battery but less phones, £2.10.0.

★**R.E.P. Beginners' Transistor Kits.** L & M.W. with reaction, 25/3 complete. L & M.W. Feeder Unit, 22/9 complete. L & M.W. Band-pass feeder, 32/6 complete.

★**Headphones** for all above, 14/-, or superior type, 17/-.

Teletron "Tapejak." Ready to plug in to any tape recorder, to give radio reception. Fully transistorised in attractive cabinet, £5.9.0. (See review on page 383).

Teletron "Transidyne." Six transistor pocket receiver of proved design. With printed circuit and attractive cream plastic cabinet, £11.15.0.

Caby Test Meter. 2,000 ohms per volt, 10V to 1,000V a.c./d.c., d.c. current to 250mA. Resistance to 1Megohm, also decibels, 15 ranges. Complete, £4/17/6.

Alfa Test Meter. 3,300 ohms per volt. 6V to 1,200V a.c./d.c., d.c. current 300 microamps to 300mA, 15 ranges. Versatile and well reviewed, £5.19.6.

Tools. A large selection available in wallets and individually.

Transistors. White Spot, 14/-; Yellow/Green, 9/6; Red Spot, 7/-; Ediswan XA 104 R.F., 18/-; XA 103 I.F., 15/-; XB 102, 10/-; **Transistor Holders,** 1/- each, 6 for 5/9, 11/- per doz.

Ardente Deaf Aid Earpieces with cord and earrip, 13/9. **Subminiature volume controls,** less switch, 7/6; D/P, 12/6. All Ardente components stocked. **Catalogue 6d.**

Connecting Wire. 50ft assorted colours, 1/9. **Coaxial Lead,** high quality, 6d. yd., 12 yds, 5/-; **Microphone Cable,** single, 3 yds, 1/9; 6 yds 2/9; 12 yds, 5/-; **Sleeving.** Assorted colours and sizes, 15ft, 8d. Enquiries invited for all types wire and sleeving.

Teletron Hax Coil, 3/-; **R.E.P. Dual Range Xtal Coil,** 2/6. **R.E.P. Dual Range T.R.F. Coil DRR2,** 4/-; **All Teletron and Repanco coils and components in stock.**

Headphones. Lightweight 14/- and 16/6. **Special type matched to transistor output,** 14/-; **Germanium Diodes GEX 34,** 4/-; **OA71 OA79 G.D.3.,** 5/6. **Glass type,** 1/-; **Subminiature Glass,** 1/10.

Speakers. **Subminiature** 1½" round, 25/6; 2" x 3", 30/6. **Plastic Chassis,** 2½" (only ⅜" thick), 22/6. **Rola C.25,** 26/9. **T.S.L. Tweeter,** L.P. H 65, 30/-; Other sizes and types stocked. **Output Transformers** Subminiature single end or p/p 12/6. **Others** from 7/6.

QUOTATIONS gladly given (S.A.E. please)

R. FAGELSTON (MAIL ORDER)

Please add Postage to above prices

46 HARDWICKE ROAD • LONDON N13

L. F. HANNEY
77 LOWER BRISTOL ROAD BATH
TRANSISTORS

Red Spot, 5/-; White Spot, 6/6; Brimar TS1 6/- (Audio). Ediswan XA104, 18/-; XA103, 15/-; XB102, 10/-; XB104, 10/-; Genuine Mullard OC44, 26/-; OC45, 23/-; OC71, 14/-; OC72, 17/-; 2 x OC72 (matched), 34/-; (All post free.)

All Repanco, Teletron, Ardente components in stock, and miniature resistors, condensers, speakers, etc.

Shopping List available for Mullard Amplifiers described in "Circuits for Audio Amplifiers." S.A.E. for LIST please.

PROTECT YOUR CAR AT NIGHT
PHOTOELECTRIC PARKING LIGHT SWITCH

will switch your lights on at dusk—off at dawn, automatically, while you are at work, in bed, or away from home. Controlled by light. Transistorised. Negligible consumption (.008 amp.). Avoid accidents, fines. Save your battery.


Kit of parts 52/6
Built and tested 57/6
Instructions only 1/-

Pat. applied for Money back guarantee

ST. JOHN'S RADIO
156 ST. JOHN'S HILL SW11 BATtersea 9838

Premier RADIO

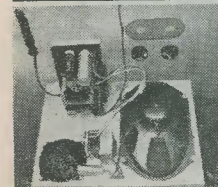23 TOTTENHAM COURT ROAD LONDON W1 Telephone MUSeum 3451/2




THE FAMOUS COSSOR
3 watt Audio Amplifier Kit 562K
Original Price £9.15
Our Price £5.19.6
P. & P. 2/6

This Kit when assembled will provide a compact versatile amplifier which incorporates the most up-to-date printed circuit and is suitable for operation from radio, microphone and gramophone. The circuit design includes negative feedback and two high performance loudspeakers are used which ensures high quality output. All items are supplied including 10" x 6" loudspeaker, a 4" treble speaker and even solder

THE BEREC
Battery Receiver for only £4.19.6 plus 5/- p. & p., or £1 deposit and 5 monthly payments of 19/-; This receiver is ideally suitable for use in the home or where normal electricity supply is not available, remarkable reception on both medium and short wavebands, incorporating the following latest type miniature battery valves: DK92, DF96, DAF96, DL96, and operates on an external B103 battery or equivalent. It is housed in an attractive two-tone metal case. Size 11½" x 7½" x 5½" Battery EXTRA, 18/6.



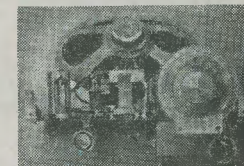THE COSSOR
Printed Circuit Model
701K VHF/FM Radio Receiver Kit
Original Price 15 Gns.
Our Price £8.19.6
P. & P. 2/6



This Kit can be easily assembled and will provide a complete radio receiver for reception of transmission employing f.m. radiating from the VHF transmitters. This receiver utilises the latest type printed circuit method and is suitable for use on a.c. or d.c. mains. The Kit is supplied complete in every detail including a 10" x 6" Goodmans loudspeaker.

POCKET TEST METER for the enthusiast:
CABY MULTI-METER A-10

Ranges: DC/V 10-50-250-500-1kΩ (2kΩ/V); AC/V 10-50-250-500-1kΩ (2kΩ/V); DC/ma 0.5-25-250 (250 mV); OHM 0-10 kΩ-1MΩ.
Complete with Test Leads £4.19.6 p. & p. 2/6

VISIT OUR NEW BRANCH AT
309 EDGWARE ROAD • LONDON W2

Telephone PADdington 6963

Build your own HI-FI!

At last! A specially selected and designed Hi-Fi Sound Installation for your home at really reasonable cost!



You save because you assemble everything yourself following our step by step instructions. You gain because you learn about the equipment as you build and are able to service and maintain it afterwards. Best of all—you'll have fun building it and be thrilled with the finished instrument which will bring you an entirely new experience in the enjoyment of sound. No previous skill or experience is needed. Post coupon now for full details, without any obligation. Easy terms available. Equipment includes:—Luxury Cabinets Top Quality Amplifier suitable for stereo or non-stereo reproduction · VHF/FM Radio Units · Record Player Tape Recorder · Hi-Fi Speaker System.

FREE BROCHURE — POST TODAY

To: RADIOSTRUCTOR, Dept. H.40
46 Market Place, Reading, Berks.

Please send Brochure without obligation to:

Name } BLOCK
Address } CAPS
(317) } PLEASE
12-59

RADIOSTRUCTOR

Britain's Leading Radio Training Organisation

For Safety's Sake
use
AVO Proclips

Patent No. 748811
... with Trigger-Action Spring-Loaded Clips
PRESS TRIGGER TO OPEN
RELEASE TO GRIP

Safety first every time with these patented spring-loaded AVO Proclips.

Cleverly designed for use as insulated prods, they are invaluable for reaching and holding test points which are difficult of access.
Post Free
15/-
per pair

AVO LTD AVOCET HOUSE
92-96 VAUXHALL BRIDGE RD LONDON SW1
VICtoria 3404 (12 lines)

A member of the Metal Industries Group of Companies
PC2



THE COOPER - SMITH HIGH FIDELITY STEREO CONTROL UNIT

COMPONENT PRICE LIST

Buy direct from the
Designers to ensure
100% results

All enquiries promptly
dealt with


Carriage free in U.K.

Complete resistor kit	21/6
Complete capacitor kit	37/2
Set of potentiometers	42/6
Set of switches	17/-
Case, tagstrips, valveholders, input panel, control carrier, plugs, rods and spacers, control panel with lens	70/-
Panel light holder and bulb	2/3
Set of knobs	8/6
EF86, pair (inc. P.T.)	34/10
12AT7, pair, (inc. P.T.)	28/6
Wire and flex	3/-
Instructions	2/6
<i>We regret that single components cannot be supplied.</i>	
Total	£13.7.9

Inclusive price for complete kit £12.12.0
Laboratory built and tested £15.0.0

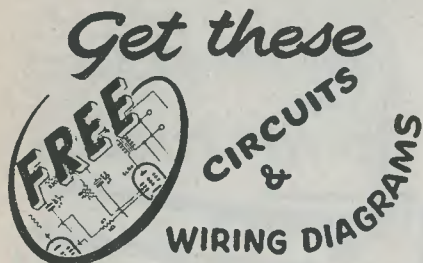H. L. SMITH & CO. LTD

287/9 EDGWARE ROAD · LONDON W2 Telephone Paddington 5891 & 7595



T.R.F. Circuits Mains Circuits Send
Battery Circuits Filter Circuits 1/-
Portable Circuits TV Converter Circuits (stamps)
S'het Circuits etc., etc.

OSMOR COILS are regularly used and recommended by designers writing in "Practical Wireless," "Wireless World" and "Radio Constructor." Why not follow the experts?

"Q COILS" All ranges • POTTED COILS • FM COILS

SPEAKER CROSS-OVER COILS

TAPE COILS • ROD AERIALS
SUB MINIATURE COILS

COILS and I.F.s for MIDGET I.F. TRANS
Transistor Circuits With ferrite cores



418 Brighton Road
South Croydon
Telephone CRO 5148/9

REPANCO MINI-3

A new local station pocket transistor Radio.

- Size 5in. x 3½in. x 1½in.
- Long and Medium Wave.
- Dual Ferrite Aerials.
- Loudspeaker reception.
- Regenerative RF Reflex Circuit.

Send Now! 1/6 (post free) for easy wiring plans, instructions and price list.

Mail Order and Trade:

**RADIO EXPERIMENTAL
PRODUCTS LTD**
33 Much Park Street COVENTRY
Telephone 62572

Wholesale Enquiries and Export:

REPANCO LTD
O'Brien's Buildings 203-269
Foleshill Road COVENTRY
Telephone 40594

Just Released . . .

Short Wave Receivers for the Beginner

with Preface and Introduction by Frank A. Baldwin, A.M.I.P.R.E.

In this, our latest production, most of the queries constantly put in letters to us are answered in the opening chapter. In addition, the book as a whole contains no fewer than 10 versions of 5 basic receiver designs, 3 of these including step-by-step building instructions. Each of the versions are complete with point-to-point wiring diagrams and/or photographs, panel and chassis drilling instructions, etc.

A glance at the contents will show that the book has been logically arranged in progression from the Introduction to the final chapter.

CONTENTS

Introduction to the Short Waves. (Radio Wave Propagation Conditions, The Aerial & Earth, The Broadcast Bands, Identifying Broadcast Stations, The Amateur Bands, CW or Phone?, Clubs & Societies, QSL'ing, Receiver Calibration, Operating your Short Wave Receiver). Soldering Notes. Beginner's Short Wave Receiver (1 valve 1T4, battery). Adding an Audio Stage (2 valve 1T4, DL96). Simple All-Wave Receiver (2 valve 6SL7GT, 6V6GT with 5Y3GT separate power supply). Simple All-Wave Receiver (2 valve 12AT7, 6BW6 with EZ41 separate power supply). The "Meteor" Mini-Receiver (1 & 2 valve, EF41, EL42 with separate metal rectifier power supply). The PUI Power Unit. The "Centurion", A Beginner's All-Wave Progressive Receiver, (1, 2 & 3 valve battery receiver with conversion to a.e. mains unit, DF91, DL96). Battery Eliminator for Short Wave Receivers.

PRICE 6s. 0d. postage 5d. 72 pages, plus cover

DATA PUBLICATIONS LTD 57 Maida Vale London W9

Now . . . in your own home, **LEARN**

RADIO - TELEVISION - ELECTRONICS

No previous technical
experience needed!
**PRACTICAL
EQUIPMENT
INCLUDING TOOLS)**
GIVES YOU A REAL
LABORATORY
TRAINING

"The trained electronics engineer has a great career ahead of him."

Valuable FREE book shows how E.M.I. Institutes School of Electronics can train you for today's wonderful opportunities.

Radio, Television and Electronics provide an exciting field for the qualified man—high pay, a prosperous future, or independence in your own business. You train at home with E.M.I. Institute's specialists who know the quickest way to prepare you for one of the fine jobs open to trained electronics-men. Whether you are a beginner or an advanced student with an examination in mind, E.M.I. Institutes School of Electronics has a Course exactly suited to your needs—with or without practical equipment—from electricity and magnetism to automation techniques.

We definitely Guarantee
"NO PASS - NO FEE"

Full details of the Courses, practical equipment, convenient monthly payments, our Employment and Advisory Depts, and much other helpful information is given in our Guide to Careers in Electronics. Write for your copy today. The book will be sent to you without obligation and free of charge.

FREE BOOK - POST NOW!

Please send me a free copy of your
Guide to Careers in Electronics.

NAME _____

ADDRESS _____

Subject or Exam _____




Practical Radio
Radio & Television
Servicing
Practical
Electronics
Engineering
Automation
City & Guilds
R. A. Examination
R.T.E.B.
Certificate
P.M.G. Certificate

E.M.I. INSTITUTES

SCHOOL OF ELECTRONICS

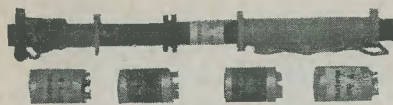The Specialist Electronics Division of the British Institute of Engineering Technology
(DEPT. SE/23) COLLEGE HOUSE 29-31 WRIGHT'S LANE KENSINGTON LONDON W8



TELETRON MINIATURE TRANSISTOR 42/-

Superhet coil kit (as illustrated)

470 kc/s I.F. Transformers and Oscillator coil in screening cans $\frac{3}{8}$ " x $\frac{1}{2}$ " dia. Dual wave Ferrite rod aerial $5\frac{1}{2}$ " x $\frac{5}{16}$ " dia. Designed for the TRANSIDYNE miniature superhet receiver.

Descriptive folder with circuit and assembly instructions Price 9d.

FERRITE ROD AERIALS


Wound on high permeability Ferroxcube rod. Medium wave, FRM 4 " x $\frac{5}{16}$ ", 8/9. Dual wave FRD, 8 " x $\frac{5}{16}$ ", 12/9.

Send 5d. in stamps for complete data and circuits. All types available from advertisers in this Magazine and local component stockists

THE TELETRON COMPANY LIMITED

112b Station Road . Chingford . London E4 Telephone SIL 0836


TELETRON TAPEJAK

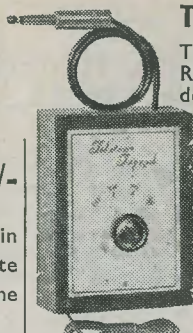

The first Transistorised Radio Tuner, specially designed for use with Tape Recorders. Converts your Recorder to a high quality Radio receiver. Direct recording on Tape. 5 " x $3\frac{3}{4}$ " x $1\frac{3}{8}$ "

- High Sensitivity
- Twin tuned circuits
- Pre-setting for MW Programmes
- Fxd. tuned for 1500 M

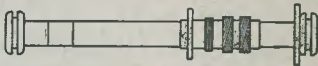● Switched prog. selector. ● Self Powered
 Tested and ready for use Battery extra
£5-9-0



★ VALVES NEW TESTED AND GUARANTEED ★

1R5	7/6	6V6G	7/6	DH76	8/6	EF92	5/6
1S5	7/6	6X4	7/6	DH77	7/6	EL41	9/-
1T4	6/-	6X5G	7/6	DK91	7/6	EL84	10/6
3S4	7/6	12AH8	10/6	PY82	7/-	EL91	7/6
3V4	8/-	12AT7	7/6	DK96	8/-	EY51	9/6
5U4G	7/6	12AU7	7/6	DL92	7/6	EZ40	6/6
5Y3GT	8/6	12AX7	9/-	DL94	8/-	EZ80	6/6
5Z4G	9/-	12BH7	10/6	DL96	8/-	EZ81	7/-
6AM6	6/9	12K8GT	13/6	EB91	5/6	PL81	13/6
6AL5	5/6	12K9GT	13/6	EBC41	9/6	PL82	10/6
6AT6	7/6	12Q7GT	8/6	EBF80	10/6	PY81	8/-
6BA6	8/6	25A6G	10/6	ECC81	7/6	PCC84	10/6
6BE6	7/6	25L6GT	9/-	ECC82	7/6	PCF80	10/6
6BR7	10/6	35Z4GT	8/6	ECC83	7/6	PCF82	11/-
6BW6	8/6	35L6GT	9/6	ECC84	10/6	PCL82	10/6
6J5G	5/6	53KU	11/6	ECC82	11/-	U76	8/6
6J7GT	8/6	807	6/9	ECH81	10/6	UBC41	10/-
6K7G	7/6	5763	10/6	ECH42	8/6	UCH42	10/6
6Q7G	8/6	DAF91	7/6	ECL80	9/6	UF41	10/-
6SL7GT	8/-	DAF96	8/-	EF41	8/6	UL41	8/-
6SN7GT	8/6	DF91	7/6	EF80	8/-	UY41	8/-
		DF96	8/-	EF91	6/9	W76	8/6

Matched Pairs. EL84. 23/-; 6V6G. 17/-; 6BW6. 18/-; KT33C. 19/6; KT66. 27/6; 807 14/6 pair

1R5, 1S5, 1T4, 3S4, 3V4, DAF91, DF91, DK91, DK92, DL92, DL94, any four, 27/6 per set
 P.P. Op. Transformers. MR 3-15 ohms for EL84, 6V6, 6BW6, etc., 18/6; Op. Pen. 50mA, 5/6; 30mA, 4/6
 Volume Controls. All values, long spindle. L/S 3/-, s.p. 4/-, d.p. 4/9, ext. spkr. control 3/-
 W.W. Pots. Pre-set 3/-, 3W long spindle 5/6, s.p. 6/6
 P.M. Speakers. 3 ohm. 5" 16/6, 6 $\frac{1}{2}$ " 17/6, 8" 21/-, 10" 25/-, 12" 30/-, Bakers 12" 15 ohm 15W, 9/-
 Coaxial Cable. 75 ohm $\frac{1}{4}$ " stranded, 8d. yd; semi-air spaced, 9d. yd; screen cable single and twin, 9d. yd
 Coaxial Plugs 1/- each; Sockets 1/- each

P. and P. 9d. to £1; 1/6 to £2; over £2 post free. C.O.D. 2/6


R. COOPER G8BX 32 SOUTH END CROYDON SURREY CROYDON 9186

★ C.R.T. Isolation Transformers with nil, 25% and 50% boost, low capacity a.c. mains 200/250V for 2V 4V, 6.3V and 13V tubes. All 10/6 each

Valveholders. 4, 5, 7 pin English and U.S.A. B7G, B9A, 10, M0, B8G, 9d. each; B7G, B9A with screening can, 1/6; B12A, 1/3. Aladdin formers $\frac{1}{4}$ " with core, 8d. each
 Scotch Boy Recording Tape, 1,200ft reels, 27/-
 Jack Plugs, miniature standard, 3/-; Sockets 3/-
 2-Gang Condensers, 0.0005 μ F small size, 7/6
 I.F. Transformers, 465 kc/s, small size, 7/6 pair
 Capacitors, small mica, 5% 1pF to 100pF, 8d.; 120pF to 1,000pF, 9d.; 1,000V wkg. .01, .0015, .0025, .004, .005 μ F, 1/- each
 Crystal Diodes, G.E.C., 1/6 each
 Headphones, lightweight, 4,000 ohm, 16/6 pair
 Ceramic Capacitors, close tol. 500V for V.H.F., 9d.
 Paper Capacitors, tubular, 0.01 μ F 1,000V, 1/-; 0.1 to 0.5 μ F 500V, 10d.
 Paper Blocks, 4 μ F, 1,000 wkg., 3/6
 Rectifiers, contact cooled, 250V 50mA, 7/6; 85mA, 9/6
 Reaction Condensers, .0001, .0003, .0005 μ F, 4/6 each
 Heater Trans. 200/240V, 6.3V, 1.5A, 7/6
 Resistors, $\frac{1}{2}$ and $\frac{1}{4}$ W, insulated, 4d. and 6d.; 1W, 8d. 6W W.W., 1/-; 10W, 2/-
 Electrolytics. Wire ends. 25/25V, 1/6; 50/50V, 2/-; 12/50V, 9d.; 8/450V, 2/-; 16/450V, 2/9; 16/500V, 3/6; 32/450V, 4/-; 8+8/450V, 4/6; 8+16/450V, 4/6; can types: 16/450V, 3/6; 16+16/500V, 6/-; 32/500V, 6/6; 32/450V, 6/6; 20+20/450V, 4/6; 64+120/275V, 7/6
 Wavechange Switches, midget: 1p 12W, 2p 6W, 3p 4W, 4p 3W, 4p 2W, long spindles, 4/6
 Toggle Switches. QMB, s.p.s.t., 2/-; s.p.d.t., 3/3; d.p.s.t., 3/6; d.p.d.t., 4/-
 Chokes, 80mA, 15H, 8/6; 100mA 10H, 10/6; 150mA 10H, 14/6
 Solder, Multicore, 4d. yd; Sleeving 2mm, 3d. yd

HI-FI SNIP Infinite Wall Baffle

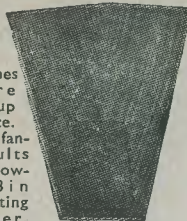Nicely veneered and polished. Corner fitting (attaches to picture rail). Takes up no floor space. Gives really fantastic results with only low priced 8in speaker. Fitting for tweeter. Only 45/- each. Carriage and insurance 3/6.





Speaker Bargain

12in high fidelity Loudspeaker. High flux. Permanent magnet type with standard 3 ohm speech coil. Will handle up to 12 watts. Brand new by famous maker. Price 32/6, plus 3/6 post and insurance.



Crystal Mike by Acos

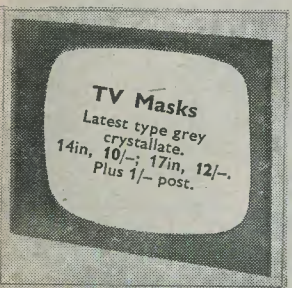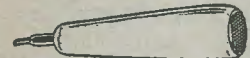Model 39/1 this is ideal for tape or general amplifiers, complete with screened lead 39/6, plus 1/- post.



TV Masks
 Latest type grey crystallate.
 14in, 10/-; 17in, 12/-.
 Plus 1/- post.


R1155 for Spares

These are less valves but otherwise reasonably complete—ideal for spares—prices £2 to £4 depending on condition. Carriage 7/6.



Transistor Set Parcel

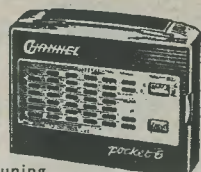Cabinet as illustrated—w i t h handeand motifs—2 gang tuning condenser—printed circuit—tuning scale—full circuit diagram showing other necessary parts—separate value £3—will all be sent for 29/6 plus 2/6 post and insurance.



For the Record Enthusiast

New four speed playing deck by E.M.I. has the following features: Velocity operated auto trip; Pick-up on switch, cannot be damaged; Remarkably low rumble achieved by single ball thrust and magnetic screen on motor; Anti-microphony mounting. The ideal unit to renovate old equipment or to build into new. Size $11\frac{1}{2}$ " wide, $1\frac{1}{4}$ " deep, $2\frac{1}{2}$ " high, depth $2\frac{1}{4}$ ". Mains model with stereo cartridge £17.6. Or with monaural cartridge, £6.18.6, post and insurance 3/6. H.P. terms on request

Components Would Cost More

Car Battery Charger—ready-made high output battery charger in stove-enamelled sheet steel louvered case. New, complete and ready to work, rated at 12V 4 amps. And variable rate selector for trickle charging, also a meter to show charging rate. Suitable for 230/250 A.C. mains. Special snip price of 55/-, plus 3/6 post and ins.



Six Useful Articles

Our 1960 catalogue now ready gives you a host of constructional hints and circuits for the following items: Moisture-operated switch; Simple but clever signal tracer; Versatile power pack costing only 10/-; Instantaneous heater for workshop or den; Six transistor pocket superhet; Simple bed warmer; Photo-flood controller. Send for this catalogue today—price 2/6 refundable from purchases.

Avo Prodclips

The advantage of these test prods is that by pressing the trigger at the side they become crocodile clips and can be left in circuit. This is a great time saver when servicing. Price 15/- pair.



Thermostats



- 1 $\frac{1}{2}$ amp Q.M.B. ... 3/6
- 2 amp Q.M.B. ... 5/6
- 5 amp ... 8/6
- 15 amp ... 15/-
- 15 amp—wall mounting... 27/6

Note all are skidion type similar to illustration except the wall mounting type which is encased in metal box with scale and pointer.

Yaxley Switches

- 1 pole 3 way, 1/6; 1 pole 5 way, 2/-;
- 1 pole 11 way, 2/6; 2 pole 2 way ceramic, 2/6; 2 pole 4 way, 2/-; 2 pole 6 way, 2/6; 2 pole 8 way, 3/6; 2 pole 11 way, 3/6; 2 pole 12 way, 4/6; 3 pole 3 way, 1/6; 3 pole 6 way, 3/6; 4 pole 4 way, 3/-; 6 position shorting, 2/-;
- 6 pole 3 way, 2/6; 6 pole 3 way ceramic, 3/6; 8 pole 2 way, 2/-; 9 pole 3 way, 2/6; 12 pole 2 way, 2/-.

Radio Stethoscope

This can be slipped into the pocket rather like a fountain pen. With it in most districts a receiver can be checked from the grid of the first valve right through to the output without a signal generator, the stethoscope will operate in both L.F. and R.F. circuits without alteration. It is a complete fault-finder. All the necessary parts to make this tracer, 9/6, post 1/-.



Band III Converters

Suitable for Wales, London, Midlands, North, Scotland etc. All the parts including 2 EF80 valves, coils, fine tuner, contrast control, condensers and resistors. (Metal case available as an extra.) Price only 19/6, plus 2/6 post and insurance. Data free with parts or available separately, 1/6.



Please send two more kits, the one you sent last week is performing magnificently. We receive this sort of letter every day of the week, so if you have hesitated because you thought our kits too cheap you need hesitate no longer.

<p>Electronics (Ruislip) Ltd. 42/46 Windmill Hill Ruislip Middlesex Telephone RU1slip 5780 Half-day Wednesday</p>	<p>If ordering by post, address to the Company nearest to you</p>	<p>Electronics (Croydon) Ltd. 266 London Road Croydon Telephone CROYdon 6558 Half-day Wednesday</p>	<p>Electronics (Finsbury Park) Ltd. 29 Stroud Green Road Finsbury Park N4 Telephone ARChway 1049 Half-day Thursday</p>
---	---	---	--

VALVES—VALVES!

OZ4	5/-	12SN7GT	10/-	EF42	11/-
IC5	10/-	12SL7GT	10/-	EF89	8/6
IR5	7/-	DAF91	7/-	EF91	5/-
IS4	7/-	DAF96	9/-	EF92	5/-
IS5	6/6	DF91	7/-	EL42	10/-
IT4	6/-	DF96	9/-	EY51	10/-
3A5	9/-	DK91	7/-	EY86	10/-
3Q5	9/-	DL91	7/-	EZ40	7/6
3S4	7/-	DK96	9/-	EZ80	7/-
3V4	7/6	DL92	7/-	EZ81	7/-
5U4	6/-	DL94	7/6	MU14	7/6
5Y3GT	6/-	DL96	9/-	PCC84	9/-
6AL5	5/-	EB91	5/-	PCF80	9/-
6AM6	5/-	EBC41	5/-	PCL82	12/-
6C4	5/-	EBF80	9/6	PY80	7/6
6SL7	6/-	EBF89	9/6	PY81	8/6
6SN7	6/-	ECC81	8/-	PY82	7/6
6V6G	7/-	ECC82	7/6	UAF42	9/-
6V6GT	6/6	ECC91	5/-	UB41	10/-
6X4	6/-	ECF80	12/-	UBC41	9/-
6X5GT	5/-	ECL80	10/-	UCH42	10/-
7Y4	7/-	EF36	5/-	UF89	10/-
12AT7	8/-	EF39	5/-	UL41	8/-
12AU7	7/6	EF40	11/6	UL84	9/-
				UY41	7/6

Full list on request

American Valve Voltmeter

R.C.A. TYPE 165-A (110 to 250V A.C. Input)

D.C. ELECTRONIC VOLTMETER

6-Ranges. 3-10-30-100-300 and 1,000 volts. Input res: 11-meg. constant on all ranges. Sensitivity: 3,666,666 ohms per volt on 3V scale.

A.C. VOLTMETER

5-Ranges. 0-10-30-100-300-1,000 volts. Sensitivity: 1,000 ohms per volt.

ELECTRONIC OHMMETER

6-Ranges, from 0.1 ohms to 1,000 megohms. Movement. 200 microamperes. D.C. accuracy $\pm 2\%$.

Complete with Instruction Book and Test Prods. Brand New

ONLY £12.10.0 P.P. 3/6

SPECIAL PURCHASE — LIMITED STOCKS — BUY NOW

CAR RADIO 2-watt Amplifier

(See page 372 this issue)

★ 7" x 4" high flux speaker ★ V15/10P power transistor. ★ Overall size 6" x 4" x 3". ★ Works off car 12-volt battery.

FOR USE WITH ANY BATTERY PORTABLE WITH 15-OHM OR 3-OHM OUTPUT TRANSFORMER.

Complete set of parts ... 65/- P. & P. 2/6
Unit built up and tested ... 77/6 P. & P. 2/6

IDEAL FOR TRANSISTOR-8, ETC. USE YOUR PORTABLE IN YOUR CAR!

AUDIO GENERATOR

Transistor Oscillator, ideal for audio circuit checking or RF modulator. Size 2½" x 1½" x 1". All components 25/- P.P. 1/- (See "R.C." Aug. 59)

FREE LIST AND DIAGRAM

IF AND RF GENERATOR

Transistor Oscillator, for receiver alignment, etc. Harmonic output 450 kc/s to 2 Mc/s. Size 2½" x 1½" x 1". All components 25/- P.P. 1/-

FREE LIST AND DIAGRAM

SIGNAL TRACER

2-Transistor and Diode; RF, IF and Audio general purpose Signal Tracer for receivers, monitors, etc. Size 4½" x 3" x 1½". All parts with phones, etc., 37/6. P.P. 1/6.

FREE LIST AND DIAGRAM

TRANSISTOR TRANSMITTER

★ Top Band 150 metres ★ 3-Transistor
★ Size 4½" x 3" x 1½"
★ Voice Modulated ★ Low Consumption
★ Ideal for short range communication

ALL PARTS 57/6 P. & P. 1/6

FREE LIST AND DIAGRAMS

(See "R.C." Jan. 1960)

TRANSISTORS AND MINIATURE COMPONENTS A SPECIALITY

FREE LISTS, DATA AND CIRCUITS ON REQUEST

CRYSTAL OSCILLATOR

Transistor Crystal Controlled Test Oscillator.


★ 3 to 12 Mc/s
★ Choice of 400 frequencies

All components including new 20 Mc/s Transistor.

22/6. P.P. 1/- (Less Crystal) FREE LIST AND DIAGRAM

ALL WAVE PORTABLE RADIO

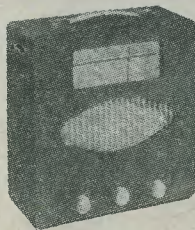★ 5 valve superhet. ★ Built-in frame aerial. ★ Size 10" x 10" x 4" deep. ★ All Marconi valves. ★ Med., long and short waveband OR med. and two short wavebands. ★ Gram. sockets (for crystal or magnetic pick-ups). ★ 7" x 4" elliptical speaker. ★ 200-250 V a.c./d.c. ★ Slow motion tuning. ★ Ideal for a radiogram.



ONLY £7.12.6 P.P. 7/6

Inclusive of Cabinet and Speaker

To the Manager

HENRY'S RADIO LTD

5 HARROW ROAD LONDON W2

Please add my name to your list to receive all FREE lists available now and in the future, without obligation.

(Block capitals please)

NAME

ADDRESS

RC3

HENRY'S RADIO LTD · 5 HARROW ROAD · LONDON W2

Opposite Edgware Road Tube Station

Telephone PADDington 1008/9

DO-IT-YOURSELF! NO EXTRAS NEEDED : FREE LISTS ON ANY MODEL AFTER SALES SERVICE : ALL PARTS SOLD SEPARATELY


All Components Guaranteed

★ IDEAL CHRISTMAS GIFTS ★

ANNOUNCING: Entirely New Design in Transistor Portable Radios! The "CONTINENTAL—6" Combined Portable / Car Radio-M & LW Superhet.

Superseding the popular "Transistor—8"

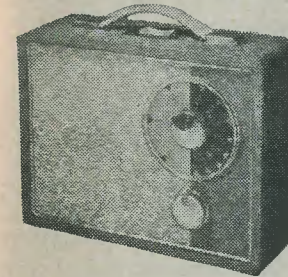For Style, Quality Performance and Value for Money




- ★ Plessey Printed Circuit
- ★ 6 Ediswan Transistors
- ★ 5" High Fidelity Speaker
- ★ 400mW Push-Pull Output
- ★ Internal Ferrite Aerial
- ★ Slow Motion Tuning
- ★ Step-by-Step Instructions

Total Cost of all Components
£11.10.0
including Cabinet, Car & AVC Components
(P.P. 3/6)

All parts available separately. Size 9½" x 7½" x 3½". Weight 4½ lb. This superb receiver has been designed to produce maximum sensitivity, selectivity, ample volume and tonal quality on both Medium and Long waves. Its performance, style and quality have combined to make the "Continental-6" a top flight portable in the 20 guinea class.

MAJOR—3 (3-Transistor Radio)

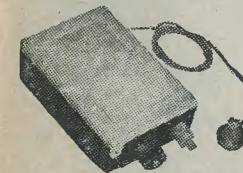

(As described in R.C., Sept. '59)

- ★ 5-stage Reflex Circuit
- ★ No Aerial or Earth
- ★ Min. Volume Control
- ★ 3 Ediswan Transistors
- ★ Medium Wave Tuning
- ★ Size 4½" x 3" x 1½"
- ★ Personal phone

Complete **87/6** P.P. 1/6

NEW EASY-TO-FOLLOW BOOKLET RECEPTION GUARANTEED ANYWHERE

MAJOR—2 (Two-transistor Pocket Radio)



- ★ 4-stage reflex
- ★ Medium wave; tuneable!
- ★ Very sensitive
- ★ No aerial or earth
- ★ Complete layout
- ★ Over 6 months on one battery
- ★ 4½" x 3" x 1½"
- ★ Weight only 4 ozs
- ★ Personal phone

Complete **69/6** P.P. 1/6

NEW EASY-TO-FOLLOW BOOKLET All components sold separately GOOD RECEPTION ANYWHERE

MINOR—1 (Transistor Pocket Radio)



- ★ 3" x 2" x ¾"
- ★ Medium Wave
- ★ 3-Stage Reflex
- ★ Internal Aerial
- ★ Smallest yet
- ★ Personal phone

All components with case and phone **49/6** P.P. 1/6 THE SMALLEST WORKING RECEIVER WITH BUILT-IN FERRITE AERIAL EVER OFFERED

All parts sold separately

Diagram and List Free

250 mW "ADDON" STAGE


2-Transistor Power Amplifier for use with Major—2 or 3 or similar units to give 250mW. Push-pull from 3" Speaker.

- ★ 2—XB104 transistors
- ★ 3" Elac Speaker
- ★ Size 5½" x 3½" x 1½"

All components complete **59/6** P.P. 1/6

FREE LIST AND DIAGRAM

"SUPER-SIX" Transistor Portable Superhet

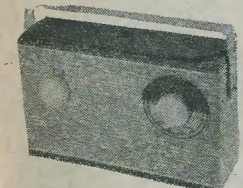

- ★ Medium and Long Waves
- ★ 6 Mullard Transistors
- ★ Printed Circuit
- ★ Sensitive and Selective
- ★ Ferrite Rod Aerial
- ★ 3" 150Ω Speaker
- ★ Full Assembly Instructions
- ★ Size 7" x 2" x 1½"

Total cost of all components (including washable rexine cabinet)

£9.10.0 P.P. 2/6

All parts sold separately

High sensitivity and selectivity combine to give excellent reception on both medium and long waves, this set is recommended by us as being one of the easiest-to-build printed circuit transistor sets ever offered.

HENRY'S RADIO LTD · 5 HARROW ROAD · LONDON W2

At junction of Edgware Road and Harrow Road

Telephone PADDington 1008/9

EDDY'S (NOTTM) LTD

172 Alfreton Road · Nottingham

LUXEMBOURG EXPANDING AERIALS. Compact and easy to fit. No technical knowledge required. Greatly improves reception, 3/11, post 6d.
HEADPHONE CORDS. High quality, 6ft, 1/11 pair. Post 6d.
SPEAKER GOLD GRILL. 6½" x 4", 1/- each. Post 6d
CRYSTAL SETS. Complete 2 wave bands. High gain. Good quality, 19/11. P. & P. 2/-
THROAT MIKES. 1/- Post 6d. Could be used for electrifying musical instruments.
DIMMER SWITCHES. Ideal for train speed indicators, 1/11. Post 6d.
NEON MAINSTEATER/SCREWDRIVERS 3/11. Post 6d.
MORSE TAPPERS. Plated contacts. Adjustable gaps. Heavy duty. Good quality, 3/6 each Post 9d.
MINIMOTORS. For model makers. High speed, 1.5V to 6V, 8/6. Post 1/-.

SPECIAL OFFER

GRAM AMPLIFIERS. High sensitivity, 3 watts output. Separate volume and tone control. Printed circuit, 59/11. Post 4/-. Fully guaranteed. Size 8" x 2½" Max. height 5"

GERMANIUM DIODES, 1/- each, 9/6 dozen. Post 4d.
DYNAMOTORS. 200V d.c. to 12V d.c. Ideal for train sets, etc., 19/11. Post 2/6.
ACOS CRYSTAL MIKES. Type MIC/35/1, 25/11. P. & P. 2/6.
NIFE ACCUMULATORS. Midget single unit, size 3" x 2½" x ½", 7 amp. hrs., 1/11. Post 1/6.
ACOS CRYSTAL PICK-UPS. Turnover head (2 sapphire styli), 29/11. Post 2/6.
CONDENSERS. Tubular wire end (not ex-govt.) 8u.F 450V 1/9, 8-8 450V 2/9, 16u.F 450V 2/9, 16-8 450V 3/11, 16-16 450V 3/9, 32u.F 450V 3/9, 32-32 450V 4/- Post 1/-
RECTIFIERS. Contact cooled, 250V 60mA, 7/6; RM1, 4/9; RM2, 6/9; RM3, 7/6; RM4, 15/6; RM5, 19/6. Post 1/-
VIBRATORS. 12 volts, 4 pin, 4/11. Post 1/-
JACK PLUGS. Standard type, 1/11. Post 6d.
RELAYS. Siemens high speed suitable for model control, 8/11. P.O. 3,000 type, assorted values, 5/11 each.
ALL ABOVE ARE NEW AND GUARANTEED

1D5	9/6	6SN7GT	4/9	AZ1	12/6	EF91	4/-
1L4	3/9	6V6GT	6/6	CY31	12/6	EL84	8/3
1S5	6/6	6X4	6/-	DAF96	8/6	EY51	9/6
1T4	4/9	6X5GT	6/-	DF96	8/6	EY86	9/6
5U4G	5/9	7C5	7/6	DH63	7/6	EZ80	6/11
5Z4G	9/6	7C6	7/6	DK96	8/6	GT1C	7/6
6AG5	5/-	7S7	9/6	DL96	8/6	PY31	8/6
6BB8	2/11	7Y4	7/6	DM70	7/6	PY80	7/-
6BA6	6/6	10F1	9/6	EB91	4/-	PCF80	9/-
6BJ6	6/6	12A6	6/6	ECC81	6/-	PL33	9/-
6C4	3/6	25A6G	8/-	ECC84	9/-	PL83	8/9
6F33	5/6	25L6GT	9/-	ECC85	8/6	U31	7/9
6J5G	2/6	25Z4G	7/9	ECL82	11/-	U35	8/6
6J5GT	3/6	35W4	6/9	EF36	2/6	UBC41	8/3
6J5M	4/3	807(B)	3/9	EF37	4/-	9001	4/6
6K7G	2/3	954	1/6	EF41	8/9	9004	4/-
6K8G	6/6	955	3/11	EF42	8/6	9006	4/-
6P28	9/6	956	2/11	EF50	1/9	9006	4/-

Surplus NEW AND GUARANTEED VALVES —ALL TESTED BEFORE DESPATCH

Any parcel insured against damage in transit for only 6d. extra per order. All uninsured parcels at customers' risk. Postage and Packing 6d. per valve extra. Over £3 free. C.O.D. or C.W.O. only. C.O.D. charge 3/- extra. S.A.E. with enquiries.

Now **VIDIO** offers even better value with a new service

CATHODE RAY TUBES RE-SCREENED & ALUMINISED

All type of tubes available, each fitted with new Gun Units and completely guaranteed for a year, and delivered anywhere in the United Kingdom—now.

For full details write direct to

VIDIO REPLACEMENT Co Ltd


R.T.R.A. APPROVED

Hales Street
Deptford High Street
London SE8

or
Telephone TIDeway 4506



DALY MINIATURE ELECTROLYTICS

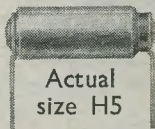

Actual size H5

Send for descriptive leaflet giving full details of complete new range

DALY (CONDENSERS) LTD

West Lodge Works The Green
Ealing London W5

Telephone EALing 3127/8/9

SMALL ADVERTISEMENTS

Readers' small advertisements will be accepted at 3d. per word, including address, minimum charge 2/-. Trade advertisements will be accepted at 9d. per word, minimum charge 6/-. If a Box Number is required, an additional charge of 2/- will be made. Terms: Cash with order. All copy must be in hand by the 12th of the month for insertion in the following month's issue. The Publishers cannot be held liable in any way for printing errors or omissions, nor can they accept responsibility for the bona fides of advertisers.

PRIVATE

FOR SALE. Eddystone 358X receiver, coverage 40-31,000 Kc/s with 10 plug-in coil units, with power pack, 8in speaker, in good condition, £12 10s. o.n.o. Berec "Skyscraper" battery receiver, covers 28, 21, 14, 7 & 3.5 Mc/s amateur bands, plus 190-550 metres, magic eye plus 7 valves, wonderful job, £7. Meter, centre zero, scaled 0-20 either side, FSD 2.5mA, 70 ohm resistance, 10s. Another meter, centre zero, unscaled, made by Elliott, 10s. Jason "Argonaut" chassis with escutcheon and drive plus i.f.t.s and valves. Has been used, £2 10s. Bunch of relays, various, one mounted on mains switch, another 3 relays in one unit mounted on 13-way miniature Jones plug and socket, German made, beautiful job, the lot, £2. Power pack MON8356 for P38 set, 230 mains input with input/output meter, £2. Any morning or Weds, evenings.—A. Melhuish, 31 Shepherds Bush Green, London, W.12.

FOR SALE. Multirange test meter, scaled ohms, volts & milliamms, 35s. Hand type crystal microphone, 27s. 6d. 12in Hi-Fi speaker, £3 15s. All above brand new and boxed, accept £5 the lot.—Box No. E218.

FOR SALE. R1155, trawler band, rebuilt 1950, complete with new power pack, speaker and output stage, has been modified to improve signal to noise ratio, £10.—M. James, 1 Chequers End, Gaddesden Row, Hemel Hempstead, Herts.

***THE RADIO CONSTRUCTOR*.** April 1953 to May 1959 inclusive, 5 missing, best offer the lot.—Evans, 109 Tansley Road, Kingstanding, Birmingham.

FOR SALE. EMI 2 valve battery short wave receiver, first offer over 50s. secures. Guaranteed working well.—Dando, 11 Whitepost Hill, Redhill, Surrey.

FOR SALE. Condensers, resistors, transformers, switches, etc. All new, s.a.e. for lists.—448 East Prescott Road, Liverpool.

HAMBANDER. 7 valve receiver with matching speaker, also Radiovision pre-selector, both in excellent condition.—Box No. E220.

AMATEUR. Selling unwanted components in genuine Gs. bargain parcels. At least two useful valves, pots, resistors, condensers, etc. Money back if not satisfied. Three parcels 15s.—Smith, 29 Pickford Road, Bexleyheath, Kent.

AMATEUR. Selling up has for disposal Taylor signal generator model 65B, s/b ex-Government scope, Primax solder gun. £15 the lot, buyer must collect (London Area).—Box No. E221

FOR SALE. Goodman Axiom 300, new. Nearest offer £8 15s.—Lawrence, 1 Gladstone Terrace, Raunds, Northants.

COLLAR MKIV. Complete recorder and R/P amps portable case etc., as new. £24.—Telephone GRA 2862 (London).

JASON JTV. FM/TV sound tuner, assembled, tested, £14 o.n.o.—76 Sladedale Road, S.E.18. Telephone WOO 7975.

FOR SALE. 750 service sheets, £7 10s. 10 TV pre-amps, converters, turrets, less valves, 50s. FM tuning heart, £1. Six valve push-pull gramophone amplifier, volume, treble, bass controls, £5. Mullard optical unit, 30s. Denco FM tuner kit, less capacitors, £3. Wire recorder amplifier with valves and speaker, 50s. Many other items. Exchanges.—

Hall, 24 Nevyn Mansions, Warwick Road, London, S.W.5. Telephone FREmantle 9631.
TEST METER. New Taylor 122A, bargain, £5.—Box No. E222
AR88D. Communication receiver complete with S-meter, also Elizabethan transmitter in matching cabinet, £40 the pair. S.a.e. for particulars.—Bowen, 31 The Crescent, Donnington, Wellington, Shrops.
FOR SALE. 1958 model, Industrial Electronics 3in oscilloscope with AM wobulator attachment, £10. Heathkit electronic testmeter, good condition, £7 10s.—A. Clark, 36 Malm Street, Boulevard, Hull.
FOR SALE. Taylor multimeter, model 71, guaranteed perfect working order, new condition, ranges up to 3000V. AC/DC ohms ranges only, £7 10s.—Telephone CLI 6335 (London) after 6 p.m.
FOR SALE. ITV converters, Sterlings, Pennine, Acrialite, Wolsey, etc., 55s. each, p. & p. please. Newnes Radio & Television Engineers Reference Book, mint condition. Offers.—O.D.B., 25 Ramshead Approach, Leeds, 14.

continued on page 399

NEW SURPLUS . . . BY RETURN

1L4	5/-	6SG7M	6/6	DC70	5/-	EZ81	7/-
1R5	6/6	6SH7M	5/-	DET24	12/6	GT1C	7/6
1S5	6/6	6SJ7M	7/6	DF73	5/-	GZ32	11/6
1T4	5/-	6SK7M	6/6	DL70	5/-	HK24G	25/-
2A3	8/6	6SL7GT	6/-	EA50	1/6	KT33C	8/6
2X2	3/6	6SN7GT	4/6	EAB8010	-	KT66	11/6
3A4	4/6	6SQ7M	7/6	EAC91	4/6	OA2	8/6
3A5	9/-	6S7	8/6	EAF42	9/-	PCC84	8/6
3Q4	6/6	6V6G	7/6	EAF42	9/-	PCC85	9/-
3S4	7/6	6X4	5/6	EB34	2/-	PCF80	9/-
3V4	7/6	6X5GT	6/6	EB91	4/-	PCF82	9/-
5R4GY	9/6	7B7	8/-	EBC33	5/-	PCL82	11/6
5Y3GT	7/6	7C5	8/-	EBC41	8/6	PEN25	4/-
6AG7M	5/-	7C6	8/-	EBC80	9/-	PEN46	5/-
6AK5	3/6	7S7	9/6	EBC89	9/6	PL81	12/6
6AK5	5/-	7Y4	8/-	ECC80	12/6	PL82	8/6
6AL5	4/-	12A6M	6/6	ECC82	6/6	PL83	8/6
6AM6	4/-	12AT6	8/6	ECC83	7/6	PY80	7/6
6AQ5	8/6	12AT7	8/-	ECC84	9/6	PY81	8/6
6AT6	7/6	12AU7	6/6	ECC85	9/-	PY82	7/6
6AU6	7/6	12AX7	7/6	ECC80	11/6	PY83	8/-
6B8G	3/6	12AU6	9/-	ECC82	11/6	TT11	4/-
6BA6	7/6	12BE6	8/6	ECH42	9/-	U25	12/6
6BE6	7/6	12C8M	7/6	ECH81	10/-	UAF42	9/-
6BH6	6/6	12K7GT	6/6	ECL80	10/6	UBC41	9/6
6B16	7/6	12K8M	12/6	ECL82	11/6	UBF89	9/6
6BR7	11/6	12Q7GT	6/6	EF36	4/-	UCH85	9/6
6BW6	9/-	12SC7M	2/6	EF39	4/6	UCC42	9/6
6C4	4/-	12S17M	5/-	EF41	9/6	UCH81	9/6
6F32	6/6	12SK7M	5/-	EF50	2/6	UF41	9/6
6F6M	5/6	12SQ7M10	-	EF50(S)	4/6	UF42	8/6
6J5GT	4/6	35L6GT	9/6	EF80	7/-	UF89	9/6
6J5M	5/-	35Z5GT	8/6	EF85	9/6	UL41	9/6
6J6	4/6	35Z4GT	7/6	EF86	11/6	UL84	9/6
6I7G	7/6	42	7/6	EF89	8/6	UY41	7/6
6K7C	3/6	50L6GT	9/6	EF91	4/-	UY85	8/6
6K8G	6/-	80	6/6	EL32	4/-	UABC80	-
6K8M	10/6	446A	10/6	EL41	9/6	-	10/6
6H6M	2/6	830B	15/-	EL84	9/-	VLS631	12/6
6L6G	8/-	866A	15/-	EM80	9/6	VP23	5/-
6L6M	10/-	959	5/-	EY51	10/6	VR150/30	-
6Q7G	7/6	1629	4/6	EY86	10/6	-	7/6
6Q7GT	9/6	5763	10/6	EZ40	7/-	VS70	3/-
6SA7M	7/6	ARP12	5/-	EZ80	7/-	Z77	4/-

Valveholders, moulded. B7G, B8A, B9A, I.O., 9d. each, 7/6 doz; B7G Prfe, B9A Micalex, 1/- each, 10/6 doz; screened B7G, B9A, 1/6 each, 15/- doz; B9A Micalex, 1/9 each, 18/- doz. B9A Cor, 2/6 each, 24/- doz. Special prices large quantities.

Fully Shrouded Chokes (U.S.A.) 10H 100mA 9/6. Post 9d. to £1, 1/6 to £2. S.A.E. enquiries

JOHN ANGLIN

385 CLEETHORPE ROAD GRIMSBY LINCS
Telephone 56315

CLYNE RADIO LTD.




Specialists in Equipment for Home Construction (Send stamp for complete list)

ALL POST ORDERS AND CORRESPONDENCE TO
162 HOLLOWAY ROAD · LONDON N7
NOR 6295/6/7

18 TOTTENHAM COURT RD. LONDON W1
MUS 5929/0095
Callers welcome at both branches

CLYNE CATHODE RAY OSCILLOSCOPE

FOR HOME CONSTRUCTION

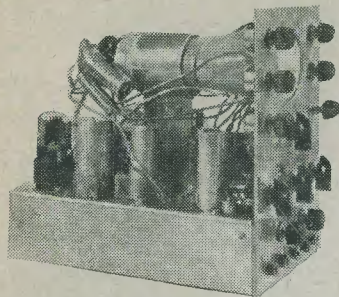

The latest addition to our comprehensive stocks of quality equipment for the constructor. This is an exceptionally sound and robust instrument of the most versatile type, that will be a boon to the seriously minded amateur, serviceman or constructor. Specifications: 8-Range Time Base, switched from 20 c/s to 160 kc/s. Y-Plate Amplifier has a sensitivity of 50mV and frequency response of 20 c/s to 600 kc/s with a gain of 150. A calibrating voltage of 6.3V 50 c/s is provided. Employs ECR30 2 $\frac{1}{2}$ " Cathode Ray Tube and 4 valves: 2/ECF80, 1/EF91, 1/EZ35 (6X5). Controls: X-shift, Y-shift, Focus, Width, Brilliance, ON/OFF, Time Base Frequency (Fine) Time Base Frequency (Coarse), Sync. Selector, Sync. Amplitude, Y-input selector, X-input selector, Amplifier Gain. Operates from 200/250V or 110V A.C. Mains. All required components for the construction of this wonderful instrument, including comprehensive assembly instructions, available at a SPECIAL INCLUSIVE PRICE OF ONLY £12.19.6 plus 5/- carriage and packing.

COSSOR KITS!

ORDER NOW!

COSSOR VHF/FM RECEIVER KIT 701K. A first class receiver of the latest type for the reception of B.B.C. v.h.f./i.m. programmes. Brand new and complete at only £8.19.6 plus 3/6 P. & P. (List price £15.15.0.)

COSSOR AUDIO AMPLIFIER KIT 562K. An excellent amplifier suitable for use with radio tuners, microphone or gramophone units. Brand new and complete at only £5.19.6 plus 3/6 P. & P. (List price £9.15.0.)
See November issue, page 318, for fuller details.


CHRISTMAS OFFER

(Exclusively by us)

PORTABLE 1960 "PERTH" SHOW MODEL

In two-tone colours. Extension speaker cabinet to match which is secured in lid. Size 18" x 14" x 8 $\frac{1}{2}$ " high. Carr. and ins. 5/6. This stereophonic player complete retails in the shops at 35 gns.

RP2
69/6

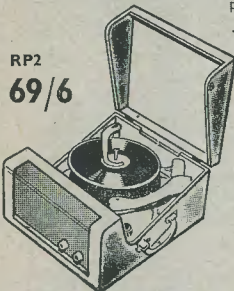

★ ★ ★ ★ ★ ★ ★ ★
IDEAL CHRISTMAS GIFT

Record Player Cabinet

A beautifully styled cabinet in two-tone polka dot. Clipped lid and strong carry handle. Size 16" x 14 $\frac{1}{2}$ " x 8 $\frac{1}{2}$ " high. Takes B.S.R. Monarch 4-speed auto-changer, elliptical speaker and modern portable amplifier. Carr and ins. 4/6.


★ ★ ★ ★ ★ ★ ★ ★
Bakelite Cabinet

Brand new. Attractive design. Size 5/9
12" x 7" x 5 $\frac{1}{2}$ ". Ideal for small receivers, etc.



STEREO
CABINET

ONLY 99/6

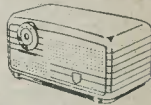

SPEAKER BARGAINS. 8" p.m. at 5/9. Slight cone repair, not affecting the quality. Tested and guaranteed. Limited quantity. P. & P. 2/9.
8" p.m. 8/9. Ideal for extensions. Standard 2-5 ohms. Good quality. P. & P. 2/9.
Elliptical Speakers 19/6. 10" x 4 $\frac{1}{2}$ ". Ideal for record players. P. & P. 2/6.

TRANSFORMERS

REVISED LIST. Mains Auto. 8/9. 0-205-225-245 volts at 300mA. Isolated windings 6.3V-6.3V-2V. P. & P. 2/9.
MAINS TRANS. 5/9. 200-250 volt at 150mA. Sec. 0-100-250. Suitable small amplifiers. Size 2 $\frac{3}{4}$ " x 1 $\frac{1}{2}$ ". P. & P. 1/9.
MAINS TRANS. 7/9. 300-0-300 volts. 6.3V at 0.3A. Prim. 200-250V. P. & P. 2/9.
MAINS TRANS. 6/9. 300-0-300 volt at 80mA. Prim. 200-250V 6.3V-5V. P. & P. 2/9.
O.P. TRANS. 1/3. Standard size 2-5 ohms. P. & P. 1/- 20 for £1. Carr. 5/6.
FRAME O.P. TRANS. 1/9. 500 ohms Prim. 18 ohms sec. P. & P. 1/6.



COMPONENTS LTD.

219 ILFORD LANE ILFORD ESSEX
Telephone ILF 0295 Stamp for FREE Catalogue

SMALL ADVERTISEMENTS

continued from page 397

PRIVATE—continued

WANTED. "Spectone" Mullard 5-10 amplifier.—G. Bidmead, 150 Shakespeare Crescent, Manor Park, London, E.12. Telephone LEYtonstone 1906.
TO CLEAR. Box capacitors, approx. 30, high values, 12s. 6d. Box assorted audio transformers, approx. 20, 17s. 6d. Box assorted meters, amp. and mA. 30s. Box assorted switches, plugs, sockets, 10s. Labgear coils, DSL/14 and 21. 5s. 6d. each G.E.C. Bell Transformers, 200-250V. in 4-8-12V. out; 10s. Mains transformer, 350-0-350; 5V2A; 5V2A; 6.3V2A; 2V2A; £1. Rotary, 12V in 285V 60mA out; 12s. 6d. Rotary, 12V in 480V 40mA out; 12s 6d. Ext. speaker; wood cabinet 14 x 14 x 7in.; 12s. 6d. VHF Wavemeter Type W. 1549; 10s. Valves; 6V6, 6K6, 12AT7, DL92, 807, 6BW6, 6BR7, 6AG7, 6SA7, 6SK7, VT136, 6AG5, 6AT7; at 5s. 6d. each. 36 assorted QSTs, mostly pre-1952; 10s. Ditto, mixed QST, CO & R.S.G.B. Bulletin; 10s. 50 assorted Bulletins, pre-1953; 10s. Bound Vols. Bulletin, 15-19 & 21; 5s. each. Gyro demonstration model with rotary, 12V input £1. UG 9 High Speed Marconi Morse Recorder, new, £10. Model 9W Morse Code Perforator, keyboard, 230V A.C. £10. Fractional H.P. A.C. motor, £1. Postage and packing included in above prices.—"East Keal", Romany Road, Oulton Broad, Lowestoft, Suffolk.

TRADE

150 TAPE JACKS. Receives any two local stations on Medium Wave, Switch tuned, fit any make of recorder. S.a.e. details, 12 months guarantee. A gift at 27s. post free—Jackson Recording Service, 68 Hartford Road, Boreham Wood, Herts.

TRANSISTOR BARGAINS. Red Spot 5s., White Spot 6s. 3d. Yellow/Green 6s., Red/Yellow 13s., XA104 18s., XA103 15s., XB104 10s. LIGHT-WEIGHT HEADPHONES. 14s., miniature ear-piece, 13s. 6d. SCOTCHBOY TAPE. 3 $\frac{1}{2}$ in 200ft, 6s. 9d. 3 $\frac{1}{2}$ in 300ft, 9s. 6d. 5in 600ft, 18s. 5in 900ft, 28s. 7in 1200ft, 30s. 7in 1800ft, 50s. All post free. Postal Orders only.—Pearson Radio, 46 Hill Rise, Sundon Park, Luton, Beds.

CATALOGUE No. 14. Government surplus and model radio control, over 500 illustrated items. 2s. (refunded on purchase) p.p. 6d.—Arthur Sallis Radio Control Ltd., 93, (E) North Road, Brighton. "MEDIUM WAVE NEWS" monthly during DX season.—Details from B. J. C. Brown, 196 Abbey Street, Derby.

JOIN THE INTERNATIONAL S.W. LEAGUE. Free Services to members including Q.S.L. Bureau, Amateur and Broadcast Translation, Technical and Identification Dept.—both Broadcast and Fixed Stations, DX Certificates, contests and activities for the SWL and transmitting members. Monthly magazine "MONITOR" containing articles of general interest to Broadcast and Amateur SWLs, Transmitter Section and League affairs, etc. League supplies such as badges, headed notepaper and envelopes. QSL cards, etc., are available at reasonable cost. Send for League particulars. Membership, including monthly magazine, etc., 21s. per annum.—Secretary, ISWL, 86 Barringer Road, London, N.10.

AT LAST—at a reasonable cost—quality Hi-Fi in your home by building it yourself under our new system. FREE Brochure from: Dept. RC21, Radiostructor, 46 Market Place, Reading, Berks.

LEARN RADIO AND ELECTRONICS the NEW Practical way. Very latest system of experimenting with and building radio apparatus—"as you learn". FREE Brochure from: Dept. RC10 Radiostructor, 46 Market Place, Reading, Berks.

SERVICE SHEETS from 1s. each, 100 TV Sheets, 18s. 6d. Cheap valves, components, lists free, Hamilton Radio, 237 Sedlescombe Road North, Hastings, Sussex.

MORSE CODE TRAINING. Special courses for Beginners. Full details from (Dept. R.C.) Candler System Company, 52 Abingdon Road, London, W.8. PANL, recognised for many years as the unique one-

coat black crackle finish. Brush applied, no baking. Available by post in 4th pint cans at 3s. 9d. from G. A. Miller, 225 Nether Street, London, N.3

"WORLD RADIO HANDBOOK." Copies available. 15s. 6d. inc. post and packing, from ISWL, 86 Barringer Road, London, N.10.

1,000 INTERESTING ITEMS. List 3d.—Rogers, 31/33 Nelson Street, Southport, Lancs.
TECHNICAL WRITING IN ELECTRONICS, Radio and TV Instruction Books, Service Manuals Brochures, Technical Drawings etc.—F. C. Judd, A.Inst.E., Rotech, 152 Maybank Road, London, E.18. Telephone BUCKhurst 9315.

HIGH CLASS DUPLICATING, Electronic Stencil Illustrations, circuits, etc. Sheets or booklets.—Rotech, 152 Maybank Road, London, E.18. Telephone BUCKhurst 9315.

INCORPORATED Practical Radio Engineers home study courses of radio and TV engineering are recognised by the trade as outstanding and authoritative. Moderate fees to a limited number of students only. Syllabus of Instructional Text is free. The Practical Radio Engineer, journal, sample copy 2s. 6.000 Alignment Peaks for Superhets, 5s. 9d. Membership and Entry Conditions booklet, 1s., all post free from the Secretary, I.P.R.E., 20 Fairfield Road, London, N.8.

SMALL ADVERTISEMENTS

Readers' small advertisements will be accepted at 3d. per word, including address, minimum charge 2/- Trade advertisements will be accepted at 9d. per word, minimum charge 6/- If a Box Number is required, an additional charge of 2/- will be made. Terms: Cash with order. All copy must be in hand by the 12th of the month for insertion in the following month's issue. The Publishers cannot be held liable in any way for printing errors or omissions, nor can they accept responsibility for the bona fides of advertisers.

12V D.C. Magnetic Switch. Cuts out on 2 amp. overload or dead short. 13/6.

Famous Make Lightweight Pencil Bit Soldering Iron, 220/240V, 25W. Indicator light in handle (list price 24/6). Price 16/6.

Scoter Batteries. 6V to 10 A.H. Hard rubber case. Size 5" x 5" x 1 $\frac{1}{2}$ ". Weight 3lb. 15/- Also ideal for model use.

New and Boxed Collaro Conquest 4-speed Record Auto Changers. 200/250V A.C. £7.4.6.

Mains Transformers. Input 200/250V. Output tapped 3 to 30V 2A or 5, 11, 17V 5A. Each 24/6.

F.W. Metal Rectifiers. 12/6 volt 1A, 7/6; 3A, 13/-; 4A, 17/6; 6A, 27/6.

Studio "O" P/U Cartridges 21/-
12" Speaker, separate 4" tweeter, in floorstand cabinet 22 $\frac{1}{2}$ " x 8" x 13 $\frac{1}{2}$ ", £6.15.0.

Mains Transformer and Rectifier, giving 12V 1A d.c. output. 19/6. Ideal for model supply.

Relays. We hold large stocks. Any contact combination and operating coil voltage supplied from 3/-

Key Switches from 3/-
Cossor UHF/FM Kit, model 701K, £8.19.6.

Toggle Switches d.p.d.t. 3/6.
Micro Switches, make and break, 5/6.

Nickel NiFe Batteries. 1.2V 2.5A. Size 3" x 2 $\frac{1}{2}$ " x 1". Practically everlasting, 6/- or 3 for 16/-

Army Morse Keys 3/-
Lightweight H.R. Phones 17/6.

H.S. Twist Drills. Set 7. $\frac{1}{16}$ "- $\frac{1}{4}$ ". 4/-

All items post paid, new and guaranteed
LISTS SENT ON REQUEST

Post orders only to

THE RADIO & ELECTRICAL MART
29 STATION APPROACH SUBBURY TOWN
WEMBLEY MIDDX

TRANSFORMERS

Suppliers to B.B.C., I.T.A. and leading radio manufacturers, single or long runs, prompt delivery, home and export.

rewinds to all makes

H. W. FORREST (TRANSFORMERS) LTD.,
Shirley, Solihull, Warwickshire
Telephone SHIRley 2483

NYLON • P.T.F.E.

ROD BAR SHEET TUBE STRIP WIRE
No quantity too small List on application

BRASS COPPER BRONZE
ALUMINIUM LIGHT ALLOYS
H. ROLLET & CO LTD

6 Chesham Place SW1 SLOane 3463
Also at Liverpool Birmingham
Manchester Leeds

Teleprinters, Perforators, Reperforators, Tape Readers, Terminals and V.F. Telegraph multi-channel units, Testing Equipment, Telephone Carriers and Repeaters, Signalling Rectifiers and Relays, Transformers, Transmit and Receive Filters, Repeating and Retardation Coils, Uniselectors, Racks, Relay Bases, Remote Control Transmitters: British, American, Italian and German Equipment.

BATEY & CO.

Gaiety Works, Akeman Street, Tring, Herts
Telephone Tring 2183 and 2310

FACTORY REBUILT . . . SUPER . . .

TELEVISION TUBES

Fully Guaranteed 12 months

12" MW or CRM £6.10.0 14" MW or CRM £7.0.0
17" MW or CRM £8.0.0
Carriage, Packing & Ins. 10/-

NOW AVAILABLE . . .

Line Output Trans. Frame Output Trans. Deflector Coils. Frame & Line Blocking OSC Trans.

Please state make and model number of receiver
S.A.E. for all Enquiries. C.W.O. or C.O.D.

K.V.A. ELECTRONICS (DEPT R.C.)
3B GODSTONE ROAD KENLEY SURREY

NEW HI-FI PUBLICATIONS

MULLARD AMPLIFIER MANUAL	8/6
MULLARD TAPE PRE-AMP "C"	2/6
QUALITY AMPLIFIERS 7 designs	4/6
JASON FM TUNERS	2/6
MERCURY SWITCHED FM TUNER	2/-

Circuits for the Mullard 3-valve 3-watt amplifier, 2-valve pre-amp. tape amplifier free on request

Quality components and popular alternatives always in stock

52 page catalogue available on request

J. T. FILMER 82 DARTFORD ROAD
DARTFORD KENT
Telephone Dartford 4057

H.A.C. THE ORIGINAL SUPPLIERS OF SHORT-WAVE KITS

One valve Super Sensitive All-dry Short-wave Receiver Model "K". Complete kit including valve and chassis 77/- (Other S.W. kits from 25/-) Before ordering call and inspect a demonstration receiver, or send stamped envelope for full specification, catalogue and order form.

H.A.C. SHORT-WAVE PRODUCTS (DEPT. R)
11 OLD BOND STREET LONDON W1

"GLOBE-KING"

WORLD-FAMOUS KITS AND RECEIVERS

for the Radio Amateur and S.W. Listener. Catalogue Free, enclose stamp for postage. Kits from 79/6 obtainable at your dealers or direct from sole manufacturers

JOHNSONS (Radio)
ST. MARTINS GATE — WORCESTER

WANTED

Wireless Sets 31 ZA31385 or ZA39058.
Aerials Vertical 14ft (folding aerial 7ft x 2ft secs.) PS and LF Amplifiers Units No. 3 ZA39057.

R. GILFILLAN & CO. LTD

29 South Street Worthing Telephone 30181

RADIO AMATEURS . . .

get your Licence in

Half The Usual Time!

You must be a good Morse operator! A "slap-dash" 12 w.p.m. neither satisfies the authorities, yourself, nor your operator friends. Morse operating is an exacting art unless your training is made simple and is based on sound fundamentals. For this reason, the Candler System was invented to take the "grind" out of Code tuition, turning a tricky subject into a pleasurable pursuit.

★ Send 3d. stamp for the "Book of Facts"

CANDLER SYSTEM CO
(Dept. 55 RC) 52b Abingdon Rd London W8
Candler System Company Denver Colorado U.S.A.

Res/Cap Bridge

FOR

37/- ONLY

P. & P. 2/-

For checking all types of resistors and condensers
BUILT IN 1 HOUR! DIRECT READING!!
READY CALIBRATED !!!

Stamp for details of this and other instruments
RADIO MAIL Dept CJ Raleigh Mews
Raleigh Street Nottingham

THE RADIO CONSTRUCTOR

BOUND VOLUMES

Attractively bound in blue cloth, with gold-blocked spine

Vol. 11, August 57 to July 58 £1.5.0, postage 1/9

Vol. 12, August 58 to July 59 £1.5.0, postage 1/9

Where all issues of a volume are returned for exchange 12s. 6d. postage 1/9

"Easibinders" for temporary or permanent binding 12s. 6d. postage 1/9

Please note:—Indexes are now available for Volume 12, August '58 to July '59 inc., price 6d. postage 2d. A limited number of indexes are also available for volumes 4, 6, 8 and 11, at the same price.

DATA PUBLICATIONS LTD 57 MAIDA VALE LONDON W9

SELRAY PUBLISHING & DISTRIBUTING CO

specialists in RADIO AND ALLIED PUBLICATIONS

Grundig Book. New Edition including The Cub, etc. 12s. 6d. Postage 9d.

Guide to Broadcasting Stations. 1958-59. Wireless World. 2s. 6d. Postage 3d.

Radio Engineer's Pocket Book. F. J. Camm. Twelfth Edition. 6s. Postage 4d.

Everyman's Wireless Book. F. J. Camm. Thirteenth Edition. 17s. 6d. Postage 9d.

Beginner's Guide to Radio. F. J. Camm. Fourth Edition. 7s. 6d. Postage 6d.

Beginner's Guide to Television. F. J. Camm. 7s. 6d. Postage 6d.

F.M. Radio Servicing Handbook. Gordon J. King. 25s. Postage 1s.

Electronic Novelties for the Constructor. E. N. Bradley. 5s. Postage 4d.

Radio Control of Models. G. Sommerhoff. 5s. Postage 4d.

Electronic Gadgets for the Constructor. E. N. Bradley. 3s. 6d. Postage 4d.

Transistor Circuits for the Constructor. E. N. Bradley. Nos. 1 and 2. 3s. 6d. each. Postage 4d.

Television Servicing. By G. N. Patchett. Vol. 1 5s., Vol. 2 6s., Vol. 3 5s., Vol. 4 7s. 6d. Postage 5d. each

Radio Servicing. By G. N. Patchett and B. Fozard. 4 volumes. 5s. each. Postage 4d. each

Over 25 Years of Knowledge and Experience in Technical Publications at your disposal

60 HAYES HILL · HAYES · BROMLEY · KENT · Telephone HURstway 1818