

# RADIO & ELECTRONICS CONSTRUCTOR

SEPTEMBER 1976

35p

THE  
ACADEMY




PART ONE  
(2 PARTS)

STEREO F.M. TUNER



TOYTOWN

TRAFFIC LIGHT CONTROLLER

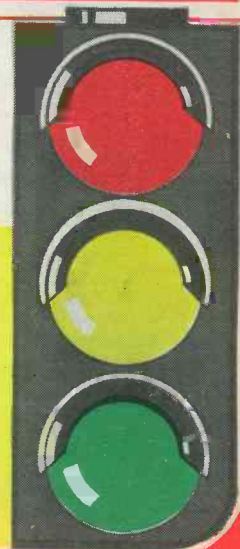

ALSO  
FEATURED

TONE-CANCELLING  
CAPACITANCE BRIDGE



## Each £3 unit of Home Unit Insurance gives you protection up to the limit shown

This is the simplified insurance you have been waiting for. Not just cover on the contents of your home but a package of personal protection you and your family need. And it's how we save you so much money: just ONE policy to issue instead of nine! You can build up to the cover you need by additional units

(or 1/4 units after the first) up to a maximum of five. So simple. So easy. Apply to your Broker, Agent or local office of a General Accident company. The Home Unit Policy can replace your existing insurances And remember - as you buy more possessions just add more Home Units at any time. *Quote Ref. 20/9468*

## THE GENERAL ACCIDENT FIRE & LIFE ASSURANCE CORPORATION LTD

Metropolitan House, 35 Victoria Avenue,  
Southend-on-Sea, Essex, SS2 6BT

It pays to be protected by a **General Accident** company

Please send me further particulars of the Home Unit Insurance.

Name.....

Address.....

20/9468

# RADIO & ELECTRONICS CONSTRUCTOR

SEPTEMBER 1976  
Volume 30 No. 2

Published Monthly (1st of Month)  
First Published 1947

*Incorporating The Radio Amateur*

*Editorial and Advertising Offices*  
57 MAIDA VALE LONDON W9 1SN

Telephone 01-286 6141      Telegrams  
Databux, London

© Data Publications Ltd., 1976. Contents may only be reproduced after obtaining prior permission from the Editor. Short abstracts or references are allowable provided acknowledgement of source is given.

**Annual Subscription:** £5.00 (U.S.A. and Canada \$11.00) including postage. Remittances should be made payable to "Data Publications Ltd". Overseas readers please pay by cheque or International Money Order.

**Technical Queries.** We regret that we are unable to answer queries other than those arising from articles appearing in this magazine nor can we advise on modifications to equipment described. We regret that such queries cannot be answered over the telephone; they must be submitted in writing and accompanied by a stamped addressed envelope for reply.

**Correspondence** should be addressed to the Editor, Advertising Manager, Subscription Manager or the Publishers as appropriate.

**Opinions** expressed by contributors are not necessarily those of the Editor or proprietors.

**Production.**—Web Offset.

Published in Great Britain by the Proprietors and Publishers, Data Publications Ltd, 57 Maida Vale, London W9 1SN

The *Radio & Electronics Constructor* is printed by Swale Press Ltd.

## CONTENTS

TOYTOWN TRAFFIC LIGHT CONTROLLER by J. R. Davies	78
CONSTRUCTOR'S CROSSWORD Compiled by J. R. Davies	85
NEWS AND COMMENT	86
RELAY TRIGGER CIRCUIT (Suggested Circuit 310) by G. A. French	88
TRADE NEWS	90
AUDIO CONTROL CIRCUITS — 3 AUTOMATIC FADER by P. R. Arthur	91
UNIUNCTION SIGNAL INJECTOR by N. R. Wilson	94
THE 'ACADEMY' STEREO F. M. TUNER — Part 1 by R. A. Penfold	96
THE NOR GATE by C. F. Edwards	102
SHORT WAVE NEWS — For DX Listeners by Frank A. Baldwin	104
3-BAND SHORT WAVE RADIO — Part 2 A. P. Roberts	106
SOME ELECTRONIC PUZZLES by R. River	108
TONE-CANCELLING CAPACITANCE BRIDGE by W. R. Jenkins	110
RADIO TOPICS by Recorder	113
SOME ELECTRONIC PUZZLES — Solutions	115
IN YOUR WORKSHOP — Rejuvenating Early Radios	116
ELECTRONICS DATA No. 14 (For the Beginner — Transistor Configurations)	iii

OCTOBER ISSUE WILL BE  
PUBLISHED ON 1st OCTOBER



# Stirling Sound Products


FROM BI-PRE-PAK

## UNIT 1 PRE-AMP/CONTROL

SUPERB VALUE AT

**£7.80**

WITH ACTIVE TONE CONTROL CIRCUITRY

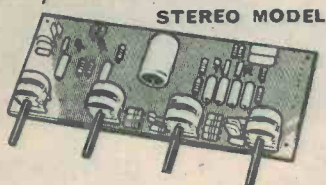

UNIT 1, latest addition in the Stirling Sound range of realistically priced constructional modules is going to assure many many more constructors of obtaining quality where price has prevented it before. UNIT 1 offers full stereo facilities, is guaranteed and easy to connect up.

- Input sensitivity—50 mV, adjustable
- Output—200 mV for 50 mV in
- Bass control—±15 dB at 30 Hz
- Treble control—±15 dB at 10 kHz
- Balance control; volume control; 1/2" spindles throughout
- Operating voltage—10 to 16V

MADE IN OUR OWN FACTORY IN ESSEX


## MORE POWER—LESS SPACE

### GREATER VALUE

**SS.140 MK.3**

**POWER AMP.**

**Built for hard work**

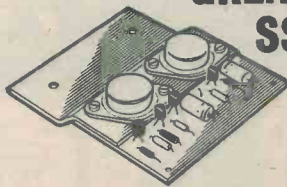

40 WATTS

R.M.S.

INTO 4Ω

**£3.95**

+ 8% V.A.T.

Resulting from research and development, the Mk.3 version of this most popular power amp. now includes built-in output capacitor with improved stability under severest working conditions. Greatly used for P.A., disco and similar work, SS.140 offers fantastic value for the price.

## Build and save with Stirling Sound

BASIC MODULES FOR BUILDING UP TO A STEREO TUNER-AMP

### ★ POWER AMPS

- |          |  |       |
|----------|--|-------|
| SS.103   | 3W r.m.s. amplifier incorporating I.C./SL60745. With current, short-circuit and thermal protection | £1.75 |
| SL.103-3 | Stereo version of above  | £3.25 |
| SS.105   | 5W amplifier to run from 12V (3 1/2" x 2" x 1")  | £2.25 |
| SS.110   | Mk. 3 Similar to SS.105 but more powerful giving 10W into 4 ohms, using 24 volts                   | £2.75 |
| SS.120   | Mk. 3 20W module when used with 34 volts into 4 ohms   | £3.00 |



SS.125

### ★ CONTROL

- |        |   |       |
|--------|---|-------|
| SS.100 | Active tone control, stereo, ± 15dB cut and boost with suitable network   | £1.60 |
| SS.101 | Pre-amp for ceramic p.u., radio & tape with passive tone control details  | £1.60 |
| SS.102 | Stereo pre-amp with R.I.A.A. equalisation, mag., p.u., tape and radio in. | £2.25 |



SS.203

### ★ POWER STABILISER

- |           |   |        |
|-----------|---|--------|
| SS.300    | Add this to your unstabilised supply to obtain a steady working voltage from 12 to 50V for your audio system, workbench etc. Money saving and very reliable | £3.25* |
| SS.310/50 | Stabilised power unit with infinitely variable output from 10 to 50V D.C. with protection against shorting and full size heat sink (p/p 50p)                | £11.00 |

### ★ F.M. TUNING

- |        |   |       |
|--------|---|-------|
| SS.201 | Front end, geared drive capacitor tuning, 88-108 MHz. AFC facility  | £5.00 |
| SS.202 | I.F. amp A meter and/or A.F.C. can be connected (size 3" x 2")  | £2.85 |
| SS.203 | Stereo decoder<br>For use with Stirling Sound modules, or with any other good mono F.M. tuning section. A L.E.D. beacon can be added to indicate when a stereo signal is tuned in (3" x 2") | £3.85 |




SS.202

## Stirling Sound

### POWER PACKS

with low volt take off point

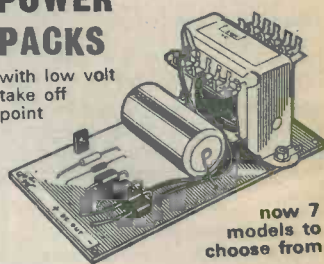

now 7 models to choose from

Not only do these excellent power packs stand up unflinchingly to hard work, inclusion of a take off point at around 13-15 V adds to their usefulness and once again price value is outstanding.

Add 50p for p/p any model.

Made to serve for years

SS.312	12V/1A	£3.75*
SS.318	18V/1A	£4.15*
SS.324	24V/1A	£4.60*
SS.334	34V/2A	£5.20*
SS.345	45V/2A	£6.25*
SS.350	50V/2A	£6.75*

Direct from the makers and obtainable only from Bi-Pre-Pak Ltd. Stirling Sound products are designed by professional experts and made in our own factory. They are distributed exclusively through Bi-Pre-Pak Ltd.

### TERMS OF BUSINESS:

VAT at 12 1/2% must be added to total value of order except for items marked \* or (8%) when VAT is to be added at 8%. No VAT on overseas orders. POST & PACKING add 30p for UK orders unless marked otherwise. Minimum mail order acceptable—£1 Overseas orders, add £1 for postage. Any difference will be credited or charged. PRICES subject to alteration without notice. AVAILABILITY All items available at time of going to press when every effort is made to ensure correctness of information.

### NEW SHOWROOM

We have extended our premises and opened up a new demonstration showroom. All welcome.

Order your Stirling Sound products from  
**BI-PRE-PAK LTD**

Co Reg No 820919

222-224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX SSO 9DF.

TELEPHONE: SOUTHBEND (0702) 46344

CHEQUES/MONEY ORDERS PAYABLE TO BI-PRE-PAK LTD.

TO STIRLING SOUND (BI-PRE-PAK LTD.), 220/222 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX SSO 9DF

Please send .....

..... for which I enclose £ .....

Inc. V.A.T. ....

NAME .....

ADDRESS .....

REC9

RADIO & ELECTRONICS CONSTRUCTOR



# WILMSLOW AUDIO

## THE Firm for speakers!

### SPEAKERS

Baker Group 25, 3, 8 or 15 ohms  
 Baker Group 35, 3, 8 or 15 ohms  
 Baker Group 50/12 8 or 15 ohms  
 Baker Group 50/15 8 or 15 ohms  
 Baker Deluxe 12" 8 or 15 ohms  
 Baker Major 3, 8 or 15 ohms  
 Baker Superb 8 or 15 ohms  
 Baker Regent 12" 8 or 15 ohms  
 Baker Auditorium 12" 8 or 15 ohms  
 Baker Auditorium 15" 8 or 15 ohms

Castle BRS/DD 4/8 ohms  
 Celestion G12M 8 or 15 ohms  
 Celestion G12H 8 or 15 ohms  
 Celestion G12/50 8 or 15 ohms  
 Celestion G12/50TC 8 or 15 ohms  
 Celestion G15C 8 or 15 ohms  
 Celestion G18C 8 or 15 ohms  
 Celestion HF1300 8 or 15 ohms  
 Celestion HF2000 8 ohms  
 Celestion MH1000 8 or 15 ohms  
 Celestion CO3K

Decca London ribbon horn  
 Decca London CO1000/8 Xover  
 Decca DK30 ribbon horn  
 Decca CO1/8 Xover (DK30)

EMI 14 x 9 Bass 8 ohms 14A770  
 EMI 8 x 5, 10 watt, d/cone, roll surr.  
 EMI 6 1/2" d/cone; roll surr. 8 ohms  
 Elac 59RM109 (15) 59RM114 (8)  
 Elac 6 1/2" d/cone, roll surr. 8 ohms  
 Elac 10" 10RM239 8 ohms  
 Eagle Crossover 3000hz 3, 8 or 15 ohms  
 Eagle FR4  
 Eagle FR65  
 Eagle FR8  
 Eagle FR10  
 Eagle HT15  
 Eagle HT21  
 Eagle MHT10  
 Eagle FF28 multicell. horn

Fane Pop 15, 8 or 16 ohms  
 Fane Pop 33T, 8 or 16 ohms  
 Fane Pop 50, 8 or 16 ohms  
 Fane Pop 55, 8 or 16 ohms  
 Fane Pop 60, 8 or 16 ohms  
 Fane Pop 70, 8 or 16 ohms  
 Fane Pop 100, 8 or 16 ohms  
 Fane Crescendo 12A, 8 or 16 ohms  
 Fane Crescendo 12BL, 8 or 16 ohms  
 Fane Crescendo 15/100A, 8 or 16 ohms  
 Fane Crescendo 15/125, 8 or 16 ohms

### SPEAKERS

f9.00 Fane Crescendo 18, 8 or 16 ohms  
 f10.75 Fane 910 Mk.II horn  
 £14.00 Fane 920 Mk.II horn  
 £18.62 Fane HPX1 crossover 200 watt  
 £12.38 Fane 13 x 8, 15 watt dual cone  
 £10.69 Fane 801T 8" d/c, roll surr.  
 £16.31 Goodmans Axent 100

£9.00 Goodmans Audiom 200 8 ohms  
 £14.85 Goodmans Axiom 402 8 or 15 ohms  
 £19.41 Goodmans Twinaxiom 8, 8 or 15 ohms  
 £9.28 Goodmans Twinaxiom 10, 8 or 15 ohms  
 f13.50 Goodmans 8P 8 or 15 ohms  
 f16.75 Goodmans 10P 8 or 15 ohms  
 £16.50 Goodmans 12P 8 or 15 ohms  
 £18.00 Goodmans 12PG 8 or 15 ohms  
 £26.95 Goodmans 12PD 8 or 15 ohms  
 £34.50 Goodmans 12AX 8 or 15 ohms  
 £6.98 Goodmans 15AX 8 or 15 ohms  
 £8.55 Goodmans 15P 8 or 15 ohms  
 £13.50 Goodmans 18P 8 or 15 ohms  
 £4.46 Goodmans Hifax 750P  
 Goodmans 5" midrange 8 ohms

f29.95 Gauss 12"  
 f6.95 Gauss 15"  
 f19.95 Gauss 18"  
 f4.75 Jordan Watts Module, 4, 8 or 15 ohms

£11.92 Kef T27  
 £3.56 Kef T15  
 £3.93 Kef B110  
 £3.38 Kef B200  
 £3.83 Kef B139  
 £3.83 Kef DN8  
 £1.75 Kef DN12  
 £5.51 Kef DN13 SP1015 or SP1017

£8.95 Lowther PM6  
 £11.95 Lowther PM6 Mk.I  
 £14.06 Lowther PM7  
 £3.96 Peerless KQ10DT 4 or 8 ohms  
 £4.95 Peerless DT10HFC 8 ohms  
 £4.00 Peerless KQ40MRF 8 ohms  
 £5.95 Peerless MT225HFC 8 ohms  
 £5.50 Richard Allan CA12 12" bass

f5.50 Richard Allan HP88  
 f9.75 Richard Allan LP88  
 £12.50 Richard Allan DT20  
 £15.50 Richard Allan CN8280  
 £17.95 Richard Allan CN820  
 £18.75 Richard Allan Super Disco 60W.12"  
 £27.95 STC 4001G  
 £37.95 Tannoy 10" Monitor HPD  
 £39.95 Tannoy 12" Monitor HPD  
 £49.95 Tannoy 15" Monitor HPD  
 £57.95 Wharfedale Super 10 RS/DD 8 ohms

### SPEAKER KITS

£67.95 Baker Major Module 3, 8 or 15 ohms each £13.28  
 £15.75 Goodmans DIN 20 4 or 8 ohms each £13.28  
 £39.95 Goodmans Mezzo Twin kit pair £46.50  
 £2.50 Helme XLK 20 pair £17.50  
 £5.50 Helme XLK 30 pair £21.95  
 £8.96 Helme XLK 35 pair £26.75  
 £7.60 Helme XLK 40 pair £38.50  
 £13.46 KEFkit 1 pair £51.00  
 £19.80 KEFkit III each £46.00  
 £9.50 Peerless 1060 pair £54.00  
 £9.86 Peerless 1070 each £46.50  
 £6.20 Peerless 1120 each £54.00  
 £6.50 Peerless 2050 pair £39.50  
 £14.95 Peerless 2060 pair £53.00  
 £16.50 Richard Allan Twin assembly each £13.46  
 £16.95 Richard Allan Triple 8 each £20.25  
 £39.00 Richard Allan Triple 12 each £25.16  
 £45.00 Richard Allan Super Triple each £29.25  
 £22.50 Richard Allan RAB Kit pair £37.80  
 £39.00 Richard Allan RA82 Kit pair £59.40  
 £16.00 Richard Allan RA82L Kit pair 65.70  
 £4.05 Wharfedale Linton II Kit pair £21.50  
 £95.00 Wharfedale Glendale 3XP Kit pair £47.70  
 £110.00 Wharfedale Dovedale III Kit pair £59.40  
 £121.00 Denton 2XP Kit pair £23.25

### HI-FI ON DEMONSTRATION

in our showrooms:  
 Akai, Armstrong, Bowers & Wilkins, Castle,  
 Celestion, Dual, Goodmans, Kef, Leak, Pioneer,  
 Radford, Richard Allan, Rotel, Tandberg, Trio,  
 Videotone, Wharfedale, etc.

—Ask for our HiFi price list—

### THIS MONTH'S SPECIALS (Carr. £2.00)

Pioneer SX737 £179.00  
 Rotel RD20 £135.00 Rotel RA312 £58.00  
 Videotone Saphir 1 pr. £52.00  
 Videoton Minimax 2 pr. £43.00

We stock the complete Radford range of amplifiers, preamplifiers, power amplifiers, tuners etc., and also Radford Audio Laboratory equipment, low distortion oscillator, distortion measuring set, audio noise meter etc.

ALL PRICES INCLUDE VAT

(Prices correct as of 5/8/76)

Send stamp for free 32-page booklet  
 "Choosing a Speaker"

All units guaranteed new and perfect  
 Carriage and Insurance: Speakers 55p each,  
 12" and up 85p each, Kits £1 each  
 (£2 per pair), Tweeters & crossovers 33p each.  
 (£1.60 per pair), Tweeters & crossovers

# WILMSLOW AUDIO

DEPT REC  
 LOUDSPEAKERS, MAIL ORDER AND EXPORT:  
 SWAN WORKS, BANK SQUARE, WILMSLOW  
 HIFI, RADIO & TV: SWIFT OF WILMSLOW, 5  
 SWAN STREET, WILMSLOW CHESHIRE  
 PA, HIFI & ACCESSORIES: WILMSLOW  
 AUDIO, 10 SWAN STREET, WILMSLOW  
 CHESHIRE  
 TELEPHONE: LOUDSPEAKERS, MAIL ORDER  
 AND EXPORT WILMSLOW 29599  
 HIFI, RADIO ETC., WILMSLOW 26213

Access & Barclaycard Orders  
 accepted by phone

### COMPLETE KITS IN STOCK FOR

**RADFORD STUDIO 90, RADFORD MONITOR 180,  
 RADFORD STUDIO 270, RADFORD STUDIO 360,  
 HIFI ANSWERS MONITOR (Rogers), HIFI NEW NO  
 COMPROMISE (Frisby), HI FI NEWS, STATE OF THE  
 ART, WIRELESS WORLD, TRANSMISSION LINE  
 (Bailey), PRACTICAL HIFI & AUDIO MONITOR (Giles),  
 PRACTICAL HIFI & AUDIO TRIANGLE (Giles),  
 POPULAR HIFI (Colloms) ETC.**

**On Dem. Answers Monitor, State of Art, etc.  
 Construction leaflets for Radford, Kef, Jordan Watts,  
 Tannoy, HiFi Answers Monitor, Free on request**

**PA Amplifiers, microphones etc. by  
 Linear, Shure, Eagle, Beyer, AKG etc.**

**FREE with orders over £10**

**"Hi-Fi Loudspeaker Enclosures" Book**



**"I MADE IT MYSELF"**

*Imagine the thrill you'll feel! Imagine how impressed people will be when they're hearing a programme on a modern radio you made yourself.*

**Now! Learn the secrets of radio and electronics by building your own modern transistor radio!**

Practical lessons teach you sooner than you would dream possible.

What a wonderful way to learn - and pave the way to a new, better-paid career! No dreary ploughing through page after page of dull facts and figures. With this fascinating Technatron Course, you learn by building!

You build a modern Transistor Radio - a Burglar Alarm. You learn Radio and Electronics by doing actual projects you enjoy - making things with your own hands that you'll be proud to own! No wonder it's so fast and easy to learn this way. Because learning becomes a hobby! And what a profitable hobby. Because opportunities in the field of Radio and Electronics are growing faster than they can find people to fill the jobs!

No soldering - yet you learn faster than you ever dreamed possible.

Yes! Faster than you can imagine, you pick up the technical know how you need. Specially prepared step-by-step lessons show you how to read circuits - assemble components - build things - experiment. You enjoy every minute of it!

You get everything you need. Tools. Components. Even a versatile Multimeter that we teach you how to use. All included in the course. **AT NO EXTRA CHARGE!** And this is a course anyone can afford. (You can even pay for it by easy instalments).


So fast, so easy, this personalised course will teach you even if you don't know a thing today!

No matter how little you know now, no matter what your background or education, we'll teach you. Step by step, in simple easy-to-understand language, you pick up the secrets of radio and electronics.

You become somebody who makes things, not just another of the millions, who don't understand. And you could pave the way to a great new career, to add to the thrill and pride you receive when you look at what you have achieved. Within weeks you could hold in your hand your own transistor radio. And after the course you can go on to acquire highpowered technical qualifications, because our famous courses go right up to City & Guilds levels.

Send now for **FREE** 44-page book - see how easy it is - read what others say!

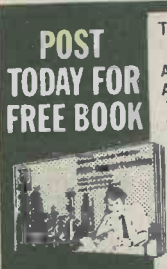Find out more now! This is the gateway to a thrilling new career, or a wonderful hobby you'll enjoy for years. Send the coupon now. There's no obligation.



To: ALDERMASTON COLLEGE  
DEPT. CRE 21, READING RG7 4PF CRE 21

Also at our London Advisory Office, 4 Fore Street  
Avenue, Moorgate, London, EC2Y 5EJ Tel: 01-628 2721  
Yes, I'd like to know more about your course. Please send me free details - plus your big, 44-page book that tells about all your courses.

NAME: .....

ADDRESS: .....

POSTCODE: .....

HOME OF BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

**LATEST BOUND VOLUME No. 28**

of

**"Radio & Electronics Constructor"**



AUGUST 1974 to JULY 1975

Comprising 768 pages **PRICE £2.75 P&P 75p** inc. index

**BOUND VOLUME No. 25**  
(August 1971 to July 1972)

**BOUND VOLUME No. 27**  
(August 1973 to July 1974)

**PRICES**

**VOL. 25**  
£2.00 per volume P&P 75p

**VOL. 27**  
£2.40 per volume P&P 75p

Limited number of these volumes still available.

We regret all earlier volumes are now completely sold out.

Available only from  
**DATA PUBLICATIONS LTD.,**  
57 MAIDA VALE, LONDON, W9 1SN

RADIO & ELECTRONICS CONSTRUCTOR



# THE MODERN BOOK CO

## AUDIO AMPLIFIERS FOR THE HOME CONSTRUCTOR

By I. R. Sinclair

Price: £2.50

**ELECTRONICS: AN ELEMENTARY INTRO. FOR BEGINNERS** by L. W. Owers **PRICE: £1.65**  
**MAKING YOUR OWN ELECTRONIC GADGETS: A BEGINNERS' GUIDE** by R. H. Warring **PRICE: £2.55**  
**INTRODUCING AMATEUR ELECTRONICS** by I. R. Sinclair **PRICE: £1.45**  
**20 SOLID STATE PROJECTS FOR THE CAR & GARAGE** by R. M. Marston **PRICE: £2.15**  
**ELECTRONICS SELF-TAUGHT WITH EXPERIMENTS & PROJECTS** by J. Ashe **PRICE: £2.20**  
**SOLID STATE HOBBY CIRCUITS** by RCA **PRICE: £1.95**  
**20 SOLID STATE PROJECTS FOR THE HOME** by R. M. Marston **PRICE: £2.15**  
**TRANSISTOR AUDIO & RADIO CIRCUITS** by Mullard **PRICE: £3.00**  
**MAKING & REPAIRING TRANSISTOR RADIOS** by W. Oliver **PRICE: £2.15**  
**BASIC THEORY & APPLICATION OF TRANSISTORS** by Dover **PRICE: £2.25**  
**AMATEUR RADIO TECHNIQUES** by P. Hawker **PRICE: £2.50**

**THE OSCILLOSCOPE IN USE** by I. R. Sinclair **PRICE: £2.75**  
**HI-FI CHOICE CASSETTE DECKS** by A. McKenzie **PRICE: £1.25**  
**HI-FI CHOICE RECEIVERS** by A. McKenzie **PRICE: £1.25**  
**FOUNDATIONS OF WIRELESS & ELECTRONICS** by M. G. Scroggie **PRICE: £4.25**  
**COLOUR TV WITH PART. REF. TO THE PAL SYSTEM** by G. N. Patchett **PRICE: £5.50**  
**SERVICING WITH THE OSCILLOSCOPE** by G. J. King **PRICE: £4.90**  
**TRANSISTOR ELECTRONIC ORGANS FOR THE AMATEUR** by A. Douglas **PRICE: £4.90**  
**THE ELECTRONIC MUSICAL INSTRUMENT MANUAL** by A. Douglas **PRICE: £8.00**  
**VHF-UHF MANUAL** by D. S. Evans **PRICE: £5.85**  
**RADIO VALVE & SEMI-CONDUCTOR DATA** by A. M. Ball **PRICE: £2.50**  
**ARRL ELECTRONICS DATA BOOK** by ARRL **PRICE: £3.05**

PRICES INCLUDE POSTAGE

We have the Finest Selection of English and American Radio Books in the Country

**19-21 PRAED STREET (Dept RC) LONDON W2 1NP**

Telephone 01-723 4185

## 1. Understand electronics.


Step by step, we take you through all the fundamentals of electronics and show you how easily the subject can be mastered using our unique Lerna-Kit course.



- (1) Build an oscilloscope.
- (2) Read, draw and understand circuit diagrams.
- (3) Carry out over 40 experiments on basic electronic circuits and see how they work.
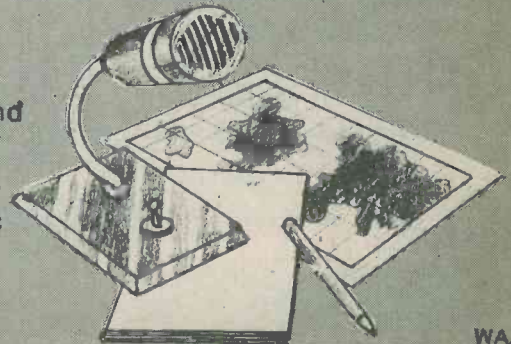
## 2. Become a radio amateur.

Learn how to become a radio-amateur in contact with the whole world. We give skilled preparation for the G.P.O. licence.



WAA

**Free!**

Brochure, without obligation to:  
**BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL,**  
 P.O. Box 156, Jersey, Channel Islands.

NAME \_\_\_\_\_

REC 96

ADDRESS \_\_\_\_\_ Block caps please



**FABULOUS**  
**EASY TO CONSTRUCT**



**DORAM  
 KITS  
 CONTAIN  
 EVERYTHING  
 DOWN TO  
 THE LAST  
 NUT!**

**AM-FM-MPX Stereo TUNER**

★ Output 100mV ★ Compliments audio separates

**£44.95 +H**

**CAR PUSH-BUTTON MW/LW RADIO**

★ Output 4W  
 ★ Dual Polarity  
 ★ Short Circuit Proof

COMPLETE WITH FITTING KIT & SPEAKER

**£16.95 +H**

**Available NOW!**

**POWER SUPPLY**

0-30V and 0-1A with a variable current limit

**£19.95 +S**

**SOIL MOISTURE METER**

Indicates whether water is needed for plants and lawns

**£2.00 +S**

**TRANSISTOR TESTER**

Measures hFE leakage for PNP, NPN, silicon or germanium transistors - includes battery check facility

**£9.95 +S**

- ★ New 16-page brochure contains complete details of kit range.
- ★ Big range of kits to interest Radio, Electronic and Hi-Fi enthusiasts.
- ★ Kits sent by return-of-post.
- ★ Each kit designed by specialists - only highest quality and reliable components included.

**SEND FOR YOUR NEW KIT BROCHURE TODAY**  
 only **25p** inc. post and packing.

**S - 8% V.A.T.**  
**H - 12½% V.A.T.**

**DORAM**

**DORAM ELECTRONICS LTD**  
**P.O. Box TR8,**  
**Leeds LS12 2UF.**

I enclose 25p please send me by return my new Doram kit brochure. Overseas orders except for N.Ireland please add 10p for post and packing surface only.

CUSTOMERS WHO ORDER THIS KIT BROCHURE TOGETHER WITH DORAM'S NEW EDITION 3 COMPONENT CATALOGUE CAN SAVE 15p ON THE INDIVIDUAL PURCHASE PRICE FOR BOTH AND OBTAIN TWO 25p VOUCHERS.

COMBINED PRICE 70p.

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

\_\_\_\_\_

\_\_\_\_\_

POST CODE \_\_\_\_\_

An Electrocomponents Group Company

# COMPONENTS

HOBBYIST - PROFESSIONAL - DOMESTIC - SURPLUS - INDUSTRIAL  
JUST A FEW BARGAINS ARE LISTED - SEND STAMPED ADDRESSED  
ENVELOPE FOR A QUOTE ON OTHER REQUIREMENTS. PAY A VISIT.  
OVER 90% OF STOCK BELOW QUANTITY WHOLESALE PRICE.  
RETURN POSTAL SERVICE UNLESS CHEQUE.

Goods sent at customer's risk, unless sufficient payment for registration (1st class letter post) or compensation fee (parcel post) included.

VALVE BASES	
Printed circuit B9A-B7G	7p
Chassis B7-B7G	9p
Shrouded chassis B7G-B9A-B8A	10p
B9A chassis-B12A tube	9p

Speaker 6" x 4" 5 ohm ideal for car radio £1.25

TAG STRIP - 6 way	3p	5 x 50pF or 2 x 200pF	20p
9 way	5p	Single	1p

BOXES - Grey polystyrene 61 x 112 x 31mm, top secured by 4 self tapping screws 32½p

Clear perspex sliding lid, 46 x 39 x 24mm 10p

ABS, ribbed inside 5mm centres for P.C.B., brass corner inserts, screw down lid, 50 x 100 x 25mm orange 48p; 80 x 150 x 50mm black 70p; 109 x 185 x 60mm black £1.04

### ALUMINIUM

3" x 2" x 1"	39p	4" x 2½" x 2"	44p	8" x 6" x 3"	£1.02
2½" x 5¼" x 1½"	45p	4" x 5½" x 1½"	45p	10" x 4½" x 3"	£1.02
4" x 4" x 1½"	45p	6" x 4" x 2"	65p	12" x 5" x 3"	£1.20
4" x 2½" x 1½"	45p	7" x 5" x 2½"	79p	10" x 7" x 3"	£1.22
				12" x 8" x 3"	£1.50

TO3 or TO66	
Mica Washer	2p
18 volt 4 amp charger, bridge rectifier	79p
GC10/4B	£3.00

Telescopic aerial  
Closed 9½", open 38½"  
Fitted right angle TV plug, 50p

JAP 4 gang min. sealed tuning condensers New 35p  
Ex-eqpt. 2 or 4 gang 20p

ELECTROLYTICS MFD/VOLT. Many others in stock 70- 200-300-450-  
Up to 10V 25V 50V 75V 100V 250V 350V 500V MFD

10	4p	5p	6p	8p	10p	12p	16p	20p
25	4p	5p	6p	8p	10p	15p	18p	20p
50	4p	5p	6p	8p	13p	18p	25p	—
100	5p	6p	10p	12p	19p	20p	—	—
250	9p	10p	11p	17p	28p	—	85p	£1
500	10p	11p	17p	24p	45p	—	—	—
1000	13p	22p	40p	75p	—	—	£1.50	—
2000	23p	37p	45p	—	—	—	—	—

As total values are too numerous to list, use this price guide to work out your actual requirements  
8/20, 10/20, 12/20 Tubular tantalum 15p each  
16-32/275, 32-32/275, 100-100/150, 100-100/275 50-50/300 20p each  
50/50-385 30p  
12,000/12, 32-32-50/300, 700/200 100-100-100-150-150/320 50p each  
20-20-20/350 40p each

RS 100-0-100 micro amp null indicator  
Approx. 2" x ¾" x ¾" £1.50

### INDICATORS

Bulgin D676 red, takes M.E.S. bulb 30p  
12 volt or Mains neon, red pushfit 18p  
R.S. Scale Print, pressure transfer sheet 10p

### CAPACITOR GUIDE - maximum 500V

Up to .01 ceramic 3p. Up to .01 poly 4p.  
.013 up to .1 poly etc. 5p. .12 up to .68 poly etc. 6p. Silver mica up to 360pF 8p, then to 2,200pF 11p, then to .01 mfd 18p.  
Many others and high voltage in stock.

8p. 1/600: 12p. .01/1000, 1/350, 8/20, .1/900, .22/900, 4/16. .25/250 AC (600vDC) .1/1500 40p. 5/150, 9/275AC, 10/150, 15/150, 40/150.

### FORDYCE DELAY UNIT

240 volt A.C./D.C. Will hold relay, etc., for approx. 15 secs after power off. Ideal for alarm circuits, etc. £1.50

### CONNECTOR STRIP

Belling Lee L1469, 4 way polythene. 6p each

1½ glass fuses 250 mA or 3 amp (box of 12) 24p  
Bulgin. 5mm Jack plug and switched socket (pair) 8p

1" or 1½" or 2" or ¾" CAN CLIPS 6p

### MAINS DROPPERS

36+79 ohm	25p
66+66+158 ohm, 66+66+137 ohm	
17+14+6 ohm, 266+14+193 ohm	30p
50+40+1k5 ohm	
285+575+148+35 ohm	40p
25+35+97+59+30 ohm	

5½" x 2½" Speaker, ex-equipment 3 ohm 30p  
2 Amp Suppression Choke 8p

3 x 2½ x 1½" PAXOLINE 4p  
4½ x ½ x 1½" 1p  
PCV or metal clip on MES bulb Holder 4p  
VALVE RETAINER CLIP, adjustable 2p

### OUTPUT TRANSFORMERS

Sub-miniature Transistor Type 25p  
Valve type, centre tapped or straight 40p

12 volt 250M/A or 6 volt ½ A Transformers £1.00  
Whiteley Stentorian 3 ohm constant impedance volume control way below trade at 80p  
Drive Cord 2p per yd.

Pole	Way	Type	
4	2	Sub. Min. Slide	18p
6	2	Slide	20p
4	2	Lever Slide	15p
2	2	Slide	10p
1	3	13 amp small rotary	12p
2	2	Locking with 2 to 3 keys	£2.00
2	1	2 Amp 250V A.C. rotary	28p

Wafer Rotary, all types 30p  
S.P.S.T. 10 amp 240v. white rocker switch with neon. 1" square flush panel fitting 65p  
S.P.S.T. dot 13 amp, oblong, push-fit, rocker 18p

### AUDIO LEADS

5 pin din plug 180° both ends 1½ Mtr., £1.20  
3 pin din to open end, 1½ yd twin screened 35p  
Phono to Phono plug, 6ft. 35p

### COMPUTER AND AUDIO BOARDS

VARYING PANELS WITH ZENER, GOLD BOND, SILICON, GERMANIUM, LOW AND HIGH POWER TRANSISTORS AND DIODES, HI STAB RESISTORS, CAPACITORS, ELECTROLYTICS, TRIMPOTS, POT CORES, CHOKES ETC.

3lb for 85p + 85p post and packing  
7lb for £1.95 + £1.20 post and packing

Skeleton Presets	3" Tape Spools	8p
Slider, horizontal or vertical standard or submin. 5p	1" Terry Clips	4p
	12 Volt Solenoid	30p

### KNOBBS

SILVER METAL PUSH ON WITH POINTER, OR WHITE PLASTIC GRUB SCREW WITH GOLD CENTRE 8p EACH

ENM Ltd. cased 7-digit counter 2½ x 1½ x 1½" approx. 12V d.c. (48 a.c.) or mains £1.00

### ZM1162A INDICATOR TUBE

0-9 Inline End View. Rectangular Envelope 170V 2.5M/A £2.67

### REGULATED TAPE MOTOR

9v d.c. nominal approx 1½" diameter 80p

12v 8 amp transformer £4.00 (p&p 85p)

Ferric Chloride, Anhydrous mil. spec. 1lb. bag 65p

### RESISTORS

¼ ½ 1 watt 1p  
1 watt 3p  
Up to 5 watt wire 11p  
10 watt wire wound 12p  
15 watt 12p  
1 or 2% five times price.

Semiconductor Data Book 263 pages. Covers 2N21 through to 2N5558 plus some 3N's. Type/connection/parameter details £1.95  
No VAT

### POTS

Log or Lin carbon 16p  
Switched 31p  
Dual Pots 50p  
Dual & switch 69p  
Lin wirewound 25p  
Slider Pot 43p  
Dual Slider 55p  
1.5m Edgetype 8p

### THERMISTORS

VA1008, VA1034, VA1039, VA1040, VA1055, VA1066, VA1082, VA1100 } 10p  
VA1077, VA1005, VA1026 } 15p

### RELAYS

12 volt S.P.C.O octal mercury wetted high speed 75p  
P.O. 3000 type, 1,000, OHM coil, 4 pole c/o 60p

Mains or 12v d.p.c.o heavy duty octal £1

Boxed GEC KT88 valve £2

## THE RADIO SHACK

161 ST. JOHNS HILL, BATTERSEA, LONDON S.W.11

Open 10 a.m. till 7 p.m. Monday to Saturday

Terms: Payment with order Telephone: 01-223 5016



# Sparkrite mk2

Capacitive discharge  
electronic ignition kit

VOTED BEST  
OF 8 SYSTEMS  
TESTED BY  
'POPULAR  
MOTORING'  
MAGAZINE



- \* Smoother running
- \* Instant all-weather starting
- \* Continual peak performance
- \* Longer coil/battery/plug life
- \* Improved acceleration/top speeds
- \* Up to 20% better fuel consumption

Sparkrite Mk. 2 is a high performance, high quality capacitive discharge, electronic ignition system in kit form. Tried, tested, proven, reliable and complete. It can be assembled in two or three hours and fitted in 15/30 mins.

Because of the superb design of the Sparkrite circuit it completely eliminates problems of the contact breaker. There is no misfire due to contact breaker bounce which is eliminated electronically by a pulse suppression circuit which prevents the unit firing if the points bounce open at high R.P.M. Contact breaker burn is eliminated by reducing the current to about 1/50th of the norm. It will perform equally well with new, old, or even badly pitted points and is not dependent upon the dwell time of the contact breakers for recharging the system. Sparkrite incorporates a short circuit protected inverter which eliminates the problems of SCR lock on and, therefore, eliminates the possibility of blowing the transistors or the SCR. (Most capacitive discharge ignitions are not completely foolproof in this respect). All kits fit vehicles with coil/distributor ignition up to 8 cylinders.

### THE KIT COMPRISES EVERYTHING NEEDED

Ready drilled pressed steel case coated in matt black epoxy resin, ready drilled base and heat-sink, top quality 5 year guaranteed transformer and components, cables, coil connectors, printed circuit board, nuts, bolts, silicon grease, full instructions to make the kit negative or positive earth, and 10 page installation instructions.

### OPTIONAL EXTRAS

Electronic/conventional ignition switch. Gives instant changeover from "Sparkrite" ignition to conventional ignition for performance comparisons, static timing etc., and will also switch the ignition off completely as a security device, includes: switch connectors, mounting bracket and instructions. Cables excluded. Also available RPM limiting control for dashboard mounting (fitted in case on ready built unit).

CALLERS WELCOME. For Crypton tuning and fitting service - phone (0922) 33008.

PRICES INCLUDE VAT, POST AND PACKING.

Improve performance & economy NOW

**POST TODAY!**

**Quick installation**  
No engine modification  
required

Electronics Design Associates, Dept., REC/9  
82 Bath Street, Walsall, WS1 3DE. Phone: (0922) 33652

Name .....  
Address .....

Mk. 2 DIY Ass. Kit @ £11.80	QUANTITY NEEDED	enclose cheque/PO's
Mk. 2 Ready Built Negative Earth @ £14.97		for £
Mk. 2 Ready Built Positive Earth @ £14.97		Cheque No.
Ignition Changeover switches @ £4.30		Send SAE if brochure
R.P.M. Limit systems in above units @ £2.42		only required.

# DESIGNED BY TEXAS



30,000  
ALREADY  
SOLD

Texan Amplifier as  
featured by PRACTICAL WIRELESS  
SOLE U.K. DISTRIBUTORS - HENRY'S

Build it yourself for only

**£32** KIT PRICE INC. VAT + £1.00 p&p  
Built and tested £42.00 inc. VAT + £1.00 p&p.

Build the Texan stereo amplifier, then you can be doubly proud! For a start, you'll own a superb home entertainment unit. And have had all the pleasure of doing it yourself, with the Henry's kit.

### Look at the Texan specification

Incorporating fully integrated stereo preamp and power amp, with 6 ICs, 10 transistors, 6 rectifiers and zener diodes. Plus stabilised, protected circuitry, glass fib pcb; Gardener's low-field low-line mains transformer; all facilities and controls. Slim design, chassis 14 1/2" x 6" x 2" overall, 20 watts per channel RMS, less than 0.1% distortion at 1 kHz.

- ★ Can be built Stage by stage
- ★ Ask for leaflet 5.
- ★ Everything necessary supplied.
- ★ Full after sales service and guarantees.

TEXAN FM  
TUNER KIT **£23.50**  
inc. VAT + 50p p&p

Built and tested £28.50 inc. VAT +50p p&p.

Build the matching Texan stereo tuner!

Features advanced varicap tuning! Phase lock loop decoder. Professionally designed circuit. Everything you need is in the kit. From the glass fibre pcb to the cabinet itself. Excellent spec: 2.5 uV aerial sensitivity, 500 mV output (adjustable). Tuning range 87-102 MHz. Mains powered.

### THE NATURAL FOLLOW-ON

DIGITAL  
24 HOUR  
CLOCK



WITH BUILT-IN ALARM!  
NORMALLY £24.00 WITH CASE

EXCLUSIVE HENRY'S PRICE **£16** LOTS OF 3 £16.50 INC. V.A.T. and P&P

All you have to do is make a casing and you're got a £24.00 Digital Unit.

Also from Henry's MISTRAL DIGITAL CLOCK KIT £11.50 inc. VAT, 30p p&p

## VIDEO SPORT



An up-to-the-minute game. Plugs into your own TV aerial socket. Switch on. And you're away! Choose your game - football, tennis or hole-in-the-wall. Absolutely safe. For you, Your children. And your TV. Mains powered. List Price £42.50

HENRY'S PRICE **£25.00**  
inc. VAT + 50p p&p

- ★ OVER 10,000 ALREADY SOLD
- ★ IDEAL GIFT

- SILENT RUNNING ● LARGE ILLUMINATED NUMERALS
- A.C. MAINS ● SIZE 6 1/2" x 2 1/2" x 2 1/2"

HENRY'S LATEST ELECTRONIC CATALOGUE

50p + 20p carr/pack.

TRANSISTOR & VALVE DISCOUNT PRICE LIST  
over 2000 types  
SEND FOR YOUR FREE COPY

**HENRY'S**  
RADIO

All mail to: Henry's Radio  
303 Edgware Rd. London W2

LONDON W2:  
404/6 Edgware Road. Tel: 01-402 8381  
LONDON W1:  
(lower sales floor) 231 Tottenham Court Road.  
Tel: 01-636 6681



**PRECISION PETITE LTD**

**119a High Street  
Teddington, Middx.**

**Tel: 01-977 0878**

Have pleasure in introducing their Precision Tools from France for all types of electronic design and development, professional or amateur

**THE ABOVE KIT IS AVAILABLE  
AS SEPARATES**


	£ p	p&p
● Kit Complete as above .....	30.50	1.15
● Mk.II Drill Stand .....	4.00	35
● Mk.II Drill Only .....	8.00	35
● Flexible Shaft.....	5.00	25
● Transformer .....	5.50	70
● S.30 Kit (30 tools).....	16.00	85
● S.10 Kit (10 tools).....	12.50	65

*(Any Quantity)*

Replacement accessories ....	40p each	15p
Circular Saw Blade Sets (4).....	£2.40	15p
Spare Collets.....	£0.40	15p
Spare Chuck & 3 Collets .....	£2.50	15p

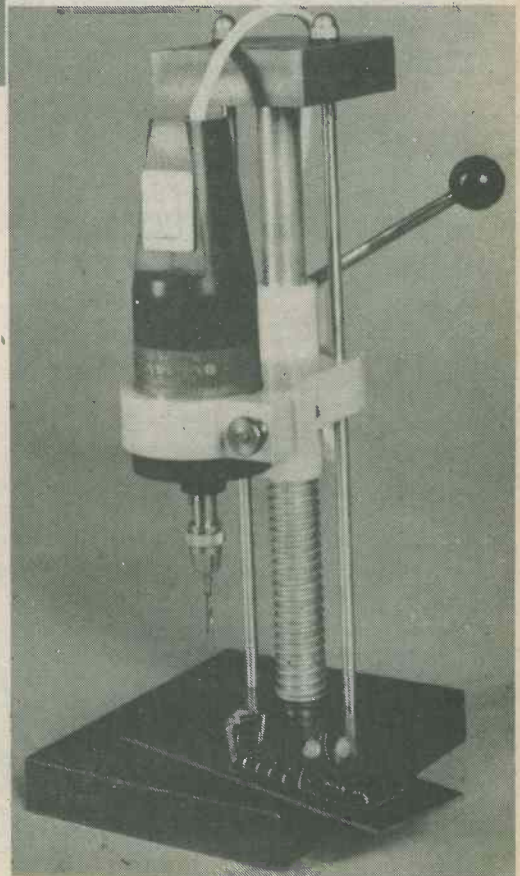**ALL ABOVE PRICES INCLUDE V.A.T.**

**S.A.E.** FOR ILLUSTRATED LEAFLET  
& ORDER FORM



# TAKE AN S-DeC

## No 19 Simple Electronic Organ


David Gibson

This miniature organ emits a series of musical notes in accordance with the positioning of a probe lead between hole 56 and a chain of resistors, and between hole 1 and the same chain. A range of musical scales is available dependant on the selection of the appropriate resistors at various parts of the chain.

The circuit is an example of an astable multivibrator. The left-hand transistor obtains its base current via the resistance chain. The total value of the resistance in circuit at any time determines the pitch of the oscillator note. Since the resistance can be varied by means of the probe lead, so can the pitch of the note.

Many developments are possible. For example, by substituting a 30kΩ potentiometer between hole four and hole 35 (wiper to hole 56) and omitting the resistors in the chain between holes four and 35, a swanee whistle type effect can be produced complete with vibrato (waggle the pot spindle slightly backwards and forwards!).

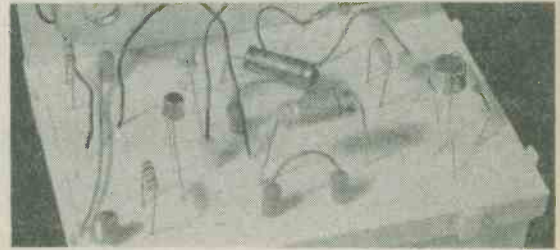Building circuits like this is simple if you use an



S-DeC (see photograph). Component leads are plugged into the relevant numbered holes (see circuit diagram) and are automatically connected into circuit.

Beneath the holes are special sockets connected together in a pattern which is shown on the upper surface of the S-DeC. When you have finished building the Simple Electronic Organ, simply unplug your components and use them again.

If you want to keep a circuit permanently wired, then for only a few pence you can buy a Super Solder Board. These printed circuit boards have holes and copper tracks which exactly match those on the S-DeC. To preserve your circuit, simply transfer the components from the S-DeC to exactly the same matching holes on the Super Solder Board and solder a permanent circuit. Holes on both S-DeC and Super Solder Board have the same letter/number marking. Making mistakes is almost impossible.

When you have built your Simple Electronic Organ you can build other exciting projects on your S-DeC. Many of the circuits featured in the popular electronics construction journals can be built on your S-DeC. In addition, P.B. Electronics is writing a special projects handbook for the S-DeC experimenter. The book will contain 48 different projects to build. These include record player amplifiers, emotion meter, radio jammer, electronic tug-of-war, strength meter, radio microphone and dozens of others — and you can build every one on your S-DeC.

The S-DeC costs only £1.98 plus 37p post, packing and VAT. It also includes a booklet giving 9 S-DeC circuits you can build.

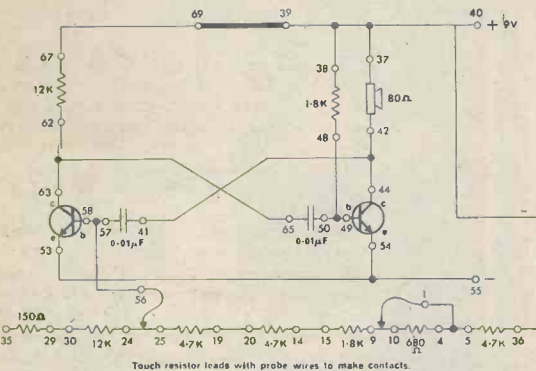


Fig. 1 Circuit diagram of Simple Electronic Organ showing relevant hole numbers of S-DeC.

Please rush me ..... S-DeC's at £1.98 plus 37p p. & p. and VAT each.

I enclose a postal order/cheque for .....

Name .....

Address .....



**P.B. ELECTRONICS (SCOTLAND) LTD.**

RC2

57 HIGH STREET • SAFFRON WALDEN • ESSEX CB10 1AA • ENGLAND

**Random FLASHER UNIT**



Wired ready for use. Complete with three 100 watt coloured lamps that flash independently at random.


**£18.95**

**TWIN BANK 6 LIGHT UNIT**  
(less lamps) LENGTH 14 1/2 inches



B.C. Fitting **£9.55** EACH  
E.S. Fitting **£10.35** EACH

**Sound to Light MASTER UNIT** 600 WATTS PER CHANNEL



**£30.95**

INCLUDING CHANNEL OUTPUT PLUGS AND MAINS INPUT SOCKET

**TYPE A SPOT** (less lamp)



B.C. Fitting **£1.95** EACH | E.S. Fitting **£2.12** EACH

**TYPE B 3 BANK UNIT** (Less Lamps)



B.C. Fitting **£6.90** EACH | E.S. Fitting **£7.26** EACH

**TWIN BANK 12 LIGHT UNIT** Length 31 3/4 (less lamps)



B.C. Fitting **£15.60** EACH | E.S. Fitting **£17.00** EACH

100 WATT SPOT LAMPS  
RED, YELLOW, GREEN, BLUE, CLEAR

Minimum 3 lamps each **£3.54**

B.C. or E.S. Fitting

ALL PRICES INCLUDE V.A.T. and POST & PACKING (These prices apply to the United Kingdom only)

Send 20p for illustrated leaflet & price list


**ALBEN ENGINEERING CO. LTD.,**  
DEPT. RE THE CRESCENT, WORSTHORNE,  
BURNLEY, LANCs. Tel: Burnley 20940

# SPECIAL ANNOUNCEMENT


We are adding a further 800 new items to our stock list of components. Watch for our advertisement in next month's issue! Better still, write NOW for our NEW 1976 Catalogue. It shows our complete range of Electronic Components, Semiconductors, Audio Modules, Hi-Fi Accessories etc., in fact, everything for the electronic enthusiast. AND all at unbeatable bargain prices! Order your copy NOW. ONLY 50p plus 15p postage.

## BI-PAK

P.O. BOX 6, WARE, HERTS

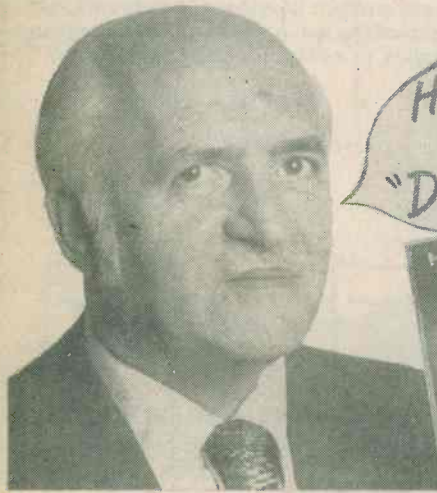

HOME RADIO have a "Double Feature"

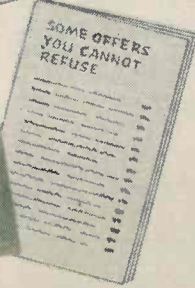

Perhaps you have to be of my vintage to know the phrase "a Double Feature," but up to a few years ago cinemas always ran a main film and a supplementary film. I was reminded of it because with their new catalogue Home Radio Components are now giving away a supplementary catalogue of bargain lines.

It sounds a very practical and sensible idea. After all, most electronic component firms accumulate surplus stocks of various items, and rather than dispose of them, why not offer them to customers at exceptionally low prices? I'm told that this bargain list will continue for several months and be up-dated from time to time.

No constructor should be without the Home Radio Components Catalogue (it contains 5,000 items clearly listed plus about 2,000 illustrations) but now you have a double incentive for buying one. In addition to getting one of the finest component catalogues available, you also receive a list of bargains at unbelievably low prices. For example, Gemini Mains Transformers: normal price £11.48, bargain list price £5, saving £6.48! This means that with a single purchase from the bargain list you can save the price of your catalogue several times over!

Please write your Name and Address in block capitals

NAME .....

ADDRESS .....

HOME RADIO (Components) LTD., Dept. RC  
234-240 London Road, Mitcham, Surrey CR4 3HD  
Regd. No. 912966, London

**POST THIS COUPON**  
with cheque or p.o. for **£1.25**

By the way, the price of the catalogue is 90p plus 35p for postage and packing. Why hesitate? Send off your cheque or Postal Order for £1.25 today, together with the coupon on the left.

The price of £1.25 applies only to customers in the UK and to BFPO Addresses.

**HOME RADIO (Components) LTD. Dept. RC, 234-240 London Road, Mitcham, CR4 3HD. Phone: 01-648 8422**

# TOYTOWN TRAFFIC LIGHT CONTROLLER

by J. R. Davies

By taking advantage of three 555 timer integrated circuits, this controller offers the four switching steps needed for lighting up a toy traffic light system.

The author was recently browsing through a catalogue of electronic components when he encountered a range of light-emitting diodes in red, yellow and green. It occurred to him that, as these colours correspond to the familiar red, amber and green of traffic control lights, it would be an amusing exercise to set up a switching system which automatically turned on two sets of l.e.d.'s in the standard traffic light sequence. The completed project could form an attractive gift for a youngster interested in model cars, and could also provide an entertaining and attention-catching display for the not-so-young whose professional or spare time pursuits are concerned with cars.

The sequence switching device described in this article is the outcome of the author's idea, and it employs three 555 timer i.c.'s, three transistors and a small number of other components, together with the red, yellow and green l.e.d.'s which function as the traffic lights. The circuit will accommodate any number of l.e.d.'s between one and four in each section by the choice of suitable series resistor values. For maximum realism, at least two l.e.d.'s per section will be required so that the traffic lights can face in four directions.

## LIGHT SEQUENCE

Fig. 1 shows two sets of traffic lights at a crossroad junction, one set facing the North-South road and the other facing the West-East road. Starting with Red, each set will light up in the following sequence: Red, Red-and-Amber, Green, Amber, Red. Obviously, the North-South lights will be at Red when the West-East lights are at Green, and vice versa. In practice, there may be a delay after the lighting up of Red at one set before the appearance of Red-and-Amber and then Green at the other set but, at the risk of a few Toytown pile-ups, the switching can be considerably

simplified by the exercise of a little judicious bending. With the present circuit it is assumed that the Amber after Green in one set of lights is coincident with the Red-and-Amber in the other set. Thus, Red (with Amber) becomes present at one set of lights when the other set changes from Green to Amber, and so a reasonable replica of actual working is achieved.

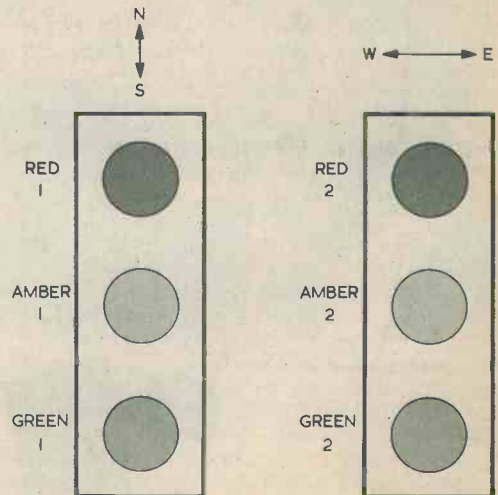


Fig. 1. Two sets of traffic lights at a crossroad junction





*Toytown traffic hold up, as the cement carrier and ambulance wait for the green*

Fig. 2 shows the sequences for the two sets of lights, and it will be noted that there are four switching steps in the cycle before it reverts to its initial state. From now on, we shall give the North-South lights the suffix 1, and the West-East lights the suffix 2. We shall also ascribe the colour Amber to yellow l.e.d.'s.

STEP	N-S LIGHTS	W-E LIGHTS
1	RED 1	GREEN 2
2	RED 1-AMBER 1	AMBER 2
3	GREEN 1	RED 2
4	AMBER 1	RED 2-AMBER 2
1	RED 1	GREEN 2

*Fig. 2. Suitable switching steps for the two sets of lights*

### BASIC CIRCUIT

Fig. 3 shows a simplified circuit of the sequence switcher. Here, the blocks identified as "Red 2", "Grn 1", etc., represent the l.e.d. or l.e.d.'s in each set, together with their series resistors. IC1 is in a standard 555 multivibrator circuit and produces a near-square wave at its pin 3 which changes state at relatively long intervals. IC2 and IC3 are also 555 i.c.'s, and are employed without their discharge function. Pins 2 and 6 connect to the internal comparators and all that has to be remembered here is that when these two pins are taken lower than one-third of VCC the output at pin 3 goes high (i.e. close to the positive rail), and that when the two pins are taken above two-thirds of VCC the output at pin 3 goes low (i.e. close to the negative rail).

Let us commence examination at an instant when the output of IC1 goes high. This at once causes Red 1 to light up. Green 2 also lights up since TR2 is conductive. TR2 is conductive because, prior to the change at IC1 output, capacitor C3 had been held discharged via D1 and the output at pin 3 of IC3 is consequently high, causing base current to flow into TR2. As IC1 output goes high, a base current flows into TR3 and this turns on, discharging C2 and causing IC2 output to go high.

The circuit is now at Step 1 of Fig. 2, with Red 1 and Green 2 alight.

Since IC1 output is high, diode D1 is reverse biased and C3 commences to charge via VR3. VR3 has been previously set up such that the voltage across C3 reaches two-thirds of VCC a short time before the output of IC1 goes low. When the voltage across C3 has risen to two-thirds of VCC, the output of IC3 goes low, removing the base bias from TR2 and causing this transistor to become cut off. Green 2 extinguishes. The output of IC3 also causes both Amber 1 and Amber 2 to light up via D3, with D2 being reverse biased.

We have now reached Step 2 of the sequence. Red 1 and Amber 1 are lit up, as also is Amber 2.

The circuit remains in this state until the output of IC1 changes and goes low. At once Red 1 extinguishes and Red 2 lights up. C3 is rapidly discharged by way of D1, which is now forward biased, and the output of IC3 goes high. This causes a base current to flow into TR2, but Green 2 cannot be illuminated because its upper terminal is low. Since IC3 output goes high, Amber 1 and Amber 2 extinguish. Before the change in IC1 output, the output at pin 3 of IC2 was high. TR1 now becomes turned on, and Green 1 lights up.

We are now at Step 3 of the sequence, with Green 1 and Red 2 illuminated.

The charging of C2 was previously inhibited because TR3 was turned on. But TR3 is now turned off, allowing C2 to charge via VR2 (which has been previously set up in the same manner as VR3). A short time before the next change in output from IC1, the voltage across C2 reaches two-thirds of VCC and the output of IC2 goes low. Base bias for TR1 ceases and Green 1 extinguishes in consequence. Also,

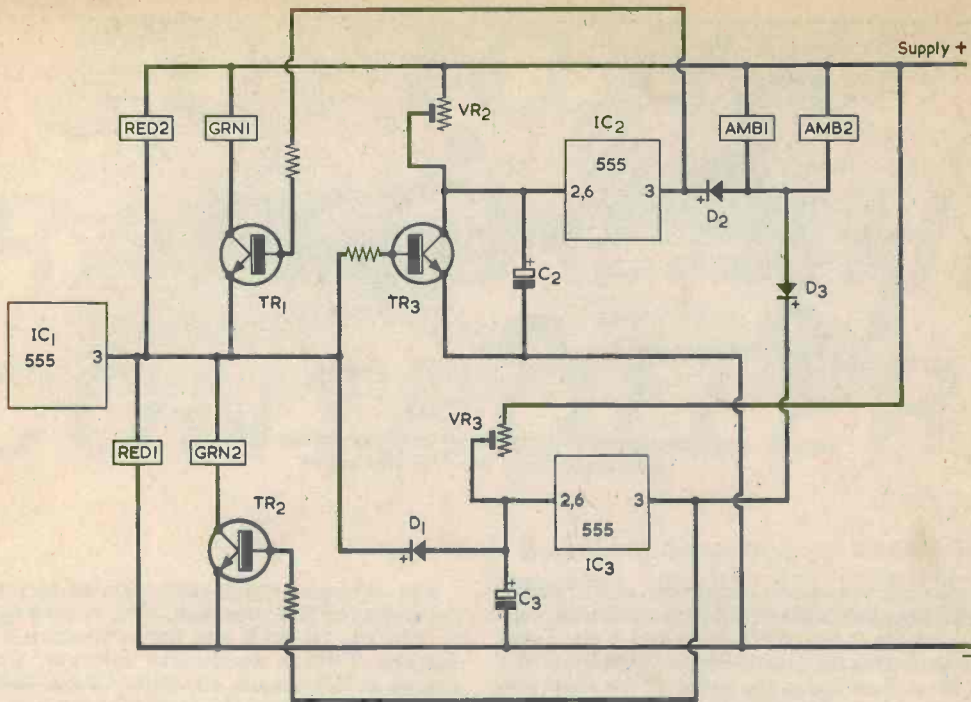


Fig. 3. Simplified circuit demonstrating the operation of the traffic light controller

Amber 1 and Amber 2 are lit up via D2, with D3 reverse biased.

Thus we now have Amber 1 lit up, together with Red 2 and Amber 2, this constituting Step 4 of the switching cycle.

The circuit stays in this state until the output from IC1 goes high again. Red 1 lights up, Red 2 extinguishes and TR3 is turned on. C2 discharges rapidly and the output of IC2 goes high with Amber 1 and Amber 2 extinguishing as a result. Green 2 also lights up because, with C3 previously inhibited via D1, the output of IC3 is high and TR2 is turned on.

Which is where we came in.


### FULL CIRCUIT

The full circuit diagram appears in Fig. 4. This is the same as Fig. 3 with components added for practical operation.

IC1 appears in an astable multivibrator circuit, with C1 charging via R1, R2 and VR1, and discharging via R2 and VR1. Since R1 is much lower in value than R2 and VR1 the output approaches a 50:50 square wave, this being particularly the case when VR1 inserts a high resistance into circuit. The cycle length can be adjusted by VR1 from roughly 7 seconds to 70 seconds. The shorter time periods are useful for circuit testing, and in practice a cycle length of about 30 to 40 seconds is adequate to demonstrate the changing of the lights without excessive waiting.

The blocks of Fig. 3 which represented the lights are now replaced by the actual l.e.d.'s. Two are shown at each position but, as already mentioned, there may be any number from one to four. The l.e.d.'s at each position are connected in series as indicated. The diagram also shows the series resistor values for different numbers of l.e.d.'s. These resistor values assume a forward voltage per l.e.d. of around 2.2 volts with a forward current of the order of 20mA.

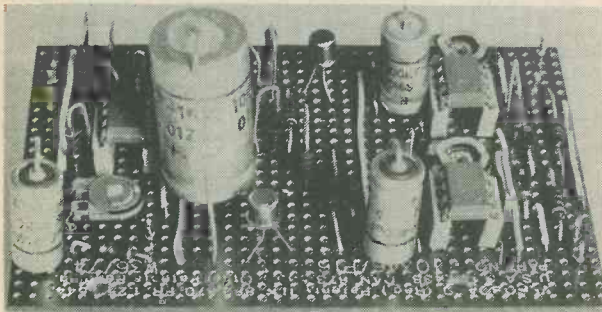TR1, TR2 and TR3 are switched in the same manner as in Fig. 3, but an extra 1kΩ resistor is added across each base and emitter. These extra resistors ensure that each transistor is fully cut off when the associated 555 output goes low, and guards against the (admittedly unlikely) possibility of an i.c. output not being adequately negative when in the nominal low state.



The controller components are assembled on a standard size Veroboard panel. The traffic lights are switched by three 555 timers and three transistors

## COMPONENTS

### Resistors

(All fixed values  $\frac{1}{4}$  watt 5% unless otherwise stated)

- R1 4.7k $\Omega$
- R2 47k $\Omega$
- R3-R6 See Fig. 4
- R7 4.7k $\Omega$
- R8 1k $\Omega$
- R9 1k $\Omega$
- R10 4.7k $\Omega$
- R11 4.7k $\Omega$
- R12 100 $\Omega$
- R13 1k $\Omega$
- R14 22k $\Omega$
- R15 100 $\Omega$
- R16 See Fig. 4
- R17 See Fig. 4
- R18 22k $\Omega$

- VR1 470k $\Omega$  pre-set potentiometer, 0.1 watt, miniature horizontal
- VR2 220k $\Omega$  pre-set potentiometer, 0.1 watt, miniature horizontal
- VR3 220k $\Omega$  pre-set potentiometer, 0.1 watt, miniature horizontal

### Capacitors


- C1 100 $\mu$ F subminiature electrolytic, 25V Wkg. (Mullard)
- C2 100 $\mu$ F subminiature electrolytic, 25V Wkg. (Mullard)
- C3 100 $\mu$ F subminiature electrolytic, 25V Wkg. (Mullard)
- C4 1,000 $\mu$ F subminiature electrolytic, 16V Wkg. (Mullard)

### Semiconductors

- IC1 555
  - IC2 555
  - IC3 555
  - TR1 BC107
  - TR2 BC107
  - TR3 BC107
  - D1 1N4002
  - D2 1N4002
  - D3 1N4002
- Light-emitting diodes, red, yellow and green (see text)
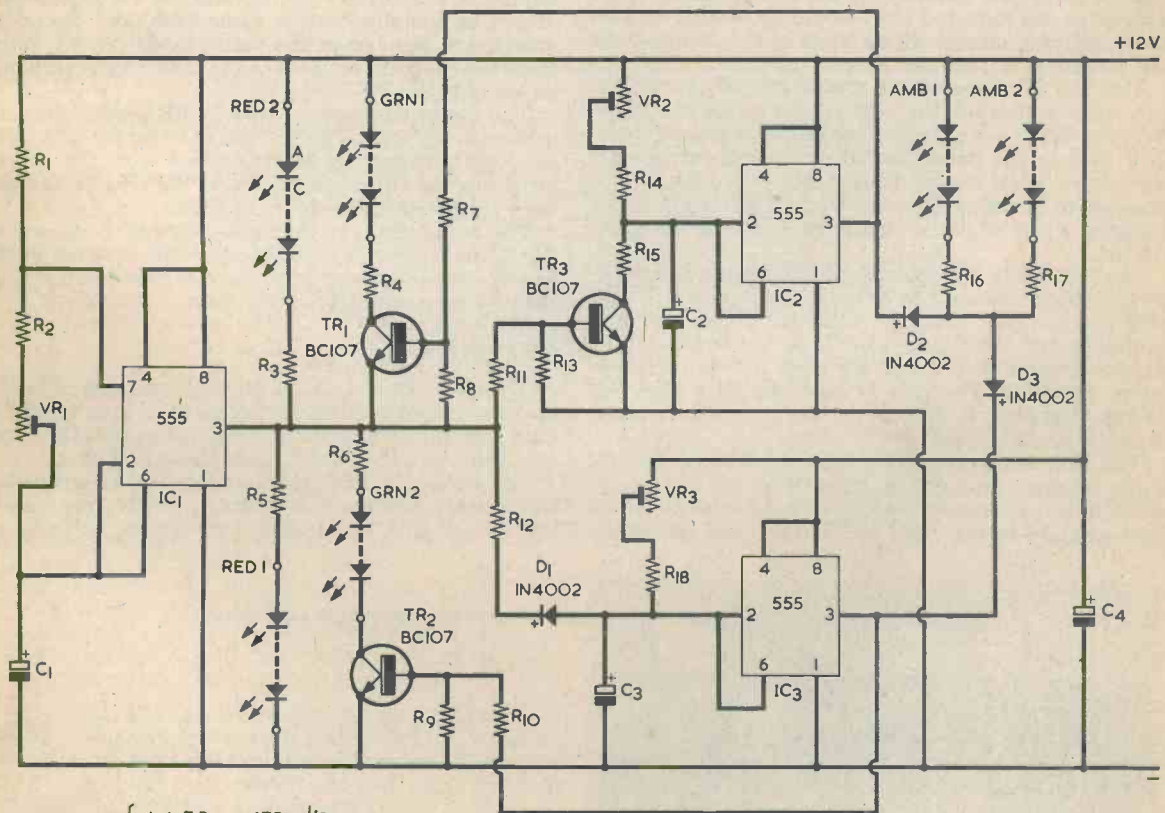
### Miscellaneous

- Veroboard, 0.1in. matrix, 2.5 x 3.75in.
- Veropins, 0.1in. (9 required)
- Hardware for light standards (see text)
- Wire, solder, etc.



- |                                   |  |
|-----------------------------------|--|
| R <sub>3</sub> , R <sub>4</sub>   | { 1 L.E.D. - 470 $\Omega$ 1/2 watt<br>2 L.E.D.'s - 390 $\Omega$ 1/4 watt<br>3 L.E.D.'s - 270 $\Omega$ 1/4 watt<br>4 L.E.D.'s - 150 $\Omega$ 1/4 watt |
| R <sub>5</sub> , R <sub>6</sub>   |  |
| R <sub>16</sub> , R <sub>17</sub> |  |
|                                   |  |

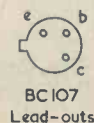


Fig. 4. The full working circuit of the controller

Resistors R12 and R15 are surge limiting resistors. R12 ensures that the maximum surge current which flows when C3 is discharged is about 110mA. Similarly, R15 limits discharge current to about the same value when TR3 discharges C2. VR2 and VR3 now have R14 and R18 in series to limit their range and to prevent excessive current flow in their tracks if they are set to insert a low resistance into circuit. R2, incidentally, performs a similar function in relation to VR1.

A low supply source impedance is essential, as a number of switching operations occur simultaneously, or nearly simultaneously, during the cycle. The low impedance is provided by C4. Constructors who like to build projects in stages, checking each stage when it is complete, are advised to ensure that C4 is in circuit at the outset.

No connections are made to any of the i.c. pins which do not appear in the circuit of Fig. 4.

### VEROBOARD ASSEMBLY

The complete circuit fits comfortably on a piece of 0.1in. matrix Veroboard measuring 2.5 by 3.75in. This is a standard size and does not need to be cut from a larger piece. It should have 24 strips by 37 holes.

The component and copper sides of the board appear in Fig. 5. Since large sections of the circuit change from one polarity to the other, rather more link wires are required than would be needed in, say, an amplifying circuit where most of the components are straddled across two supply rails.

The two 6BA clear holes should initially be drilled out, after which all the cuts in the strips are made with the aid of a Vero spot face cutter or a small twist drill held in the hand. Visually check the cuts after they have been made. With 0.1in. Veroboard it is possible to occasionally miss a small sliver of copper bridging a cut which is fondly imagined to be open-circuit.

Next fit 0.1in. Veropins at all the points where external connections are to be made to the board. These pins are virtually essential with this project, as it is probable that the flying leads from the board will be moved around to a relatively large extent in subsequent handling. The copper could be torn from the s.r.b.p. backing if the flying leads were soldered directly to the strips.

The link wires are fitted after the Veropins. Link wires bridging more than three holes should be insulated, but shorter wires can be bare tinned copper. Immediately to the right of VR3 are two link wires

which lie alongside each other. These two wires must both be insulated.

The three diodes, the three potentiometers and all the resistors and capacitors are next soldered in. Note that the potentiometers are miniature types having 0.2in. spacing between track tags and 0.4in. spacing between track and slider tags. After these, the three transistors are connected to the board. Finally to be mounted are the integrated circuits. The author fitted these to short 4-way lengths of 0.1in. connection strip in the prototype, these effectively forming i.c. holders, but the integrated circuits can alternatively be soldered directly to the board.

When assembly has been completed, check for short-circuits between the supply rails by connecting an ohmmeter across the supply rail pins. After an initial charging surge in C4, the resistance reading should rise well above 1k $\Omega$  if the ohmmeter test prods are applied with a polarity that agrees with that of C4. In other words, check with the test leads connected one way round and then transpose them; the higher reading is the correct one. A careful visual examination should also be made, looking in particular for short-circuits between strips.

The completed board may be housed in any convenient plastic or home-made wooden case. If it is to be powered by a battery, an on-off s.p.s.t. toggle switch may be inserted in series with the positive supply lead. Should it be desired that a mains power supply be employed both this and the Veroboard panel can be installed in the same case, and the on-off switch will then be in the mains input circuit. Wires from the case will connect to the traffic light standard or standards.


The board can be mounted by 6BA bolts and nuts at the two 6BA clear holes. It is in order for 6BA nuts, used for spacing, to be in contact with the copper strips, as the three strips around the 6BA clear holes have no connections made to them.

The connections to the light-emitting diodes are as illustrated in Fig. 5. Four connections external to the board are taken from a positive supply point, and a fifth from a negative supply point.
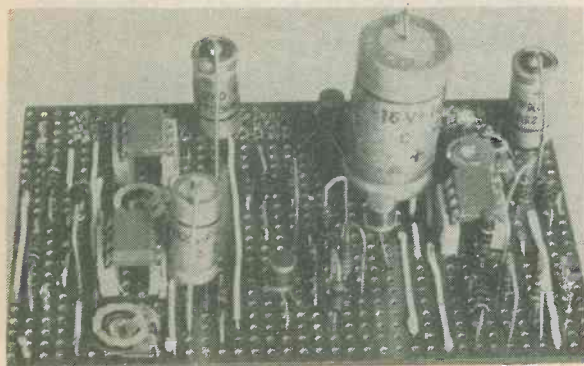
### SETTING UP

To check the circuit the requisite number of l.e.d.'s may be temporarily connected up to it. It is helpful to have the l.e.d.'s soldered to tagstrips so that they take up positions approximating to those in Fig. 1.

The three pre-set potentiometers are all connected into circuit such that the timing periods they control increase as they are adjusted clockwise. Initially set



*The Veroboard panel, as seen from the other side*

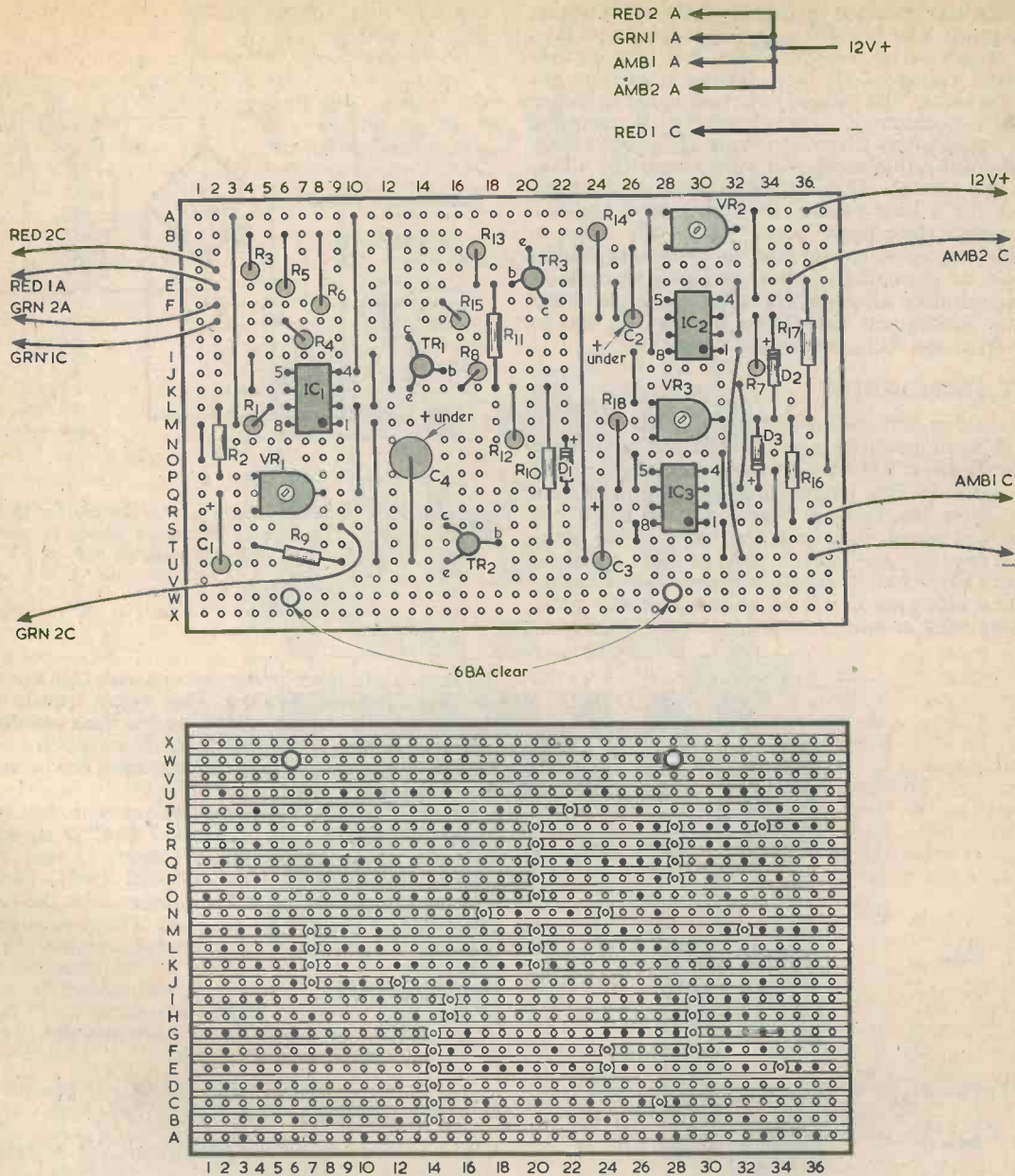


Fig. 5. The controller is assembled on a Veroboard panel as shown here

VR1 nearly fully anti-clockwise and set VR2 and VR3 to approximately mid-travel, then switch on. After an initial charging period for C1, during which Red 1 and Green 2 will light up, the circuit will settle down to alternate illumination of Red and Green l.e.d.'s.

VR2 is next adjusted. This controls the start of illumination in Amber 1 and Amber 2 after Green 1. As this control is adjusted anti-clockwise, Green 1 will be followed by Amber 1 and Amber 2, and a final setting is needed in VR2 which gives the Amber period the

correct length.

VR3 may next be adjusted, and this controls the lighting of Amber 1 and Amber 2 after Green 2. It is adjusted in the same manner, and for the same length of Amber period, as VR2.

These adjustments will check that the circuit is working satisfactorily. As the switching will now be relatively rapid, VR1 may be adjusted for the final cycle period, after which VR2 and VR3 are adjusted for the corresponding Amber periods.

To take up variations within tolerance of the timing capacitances, VR1 is given a slightly larger value than would otherwise be required. Should it happen that the actual values of all three timing capacitors are about the same, VR1 should not be adjusted to higher than three-quarters of its maximum value, since the Amber periods may then be too long. However, a little experimental adjustment will soon reveal the situation in this respect. If the timing capacitors have been in stock for a long period, they may need about a dozen runs before they "form" and settle down to their final capacitance and internal resistance values. It should be remembered that the first half-cycle in IC1 immediately after switching on is always longer than the subsequent half-cycles because C1 has to charge from the fully discharged condition.

## LIGHT STANDARDS

The making and scaling of the standards on which the l.e.d.'s are mounted is left to the constructor's ingenuity. "Lantex" (s.r.b.p.) tubing is available from Home Radio in 6in. lengths with outside diameters ranging from  $\frac{1}{2}$ in. to more than 1in., and lengths of such tubing could well form the basis of the standards. They will need to be painted with alternate white and black bands. Another approach can consist of putting alternate bands of white and black p.v.c. insulating tape around the standards. The wiring to

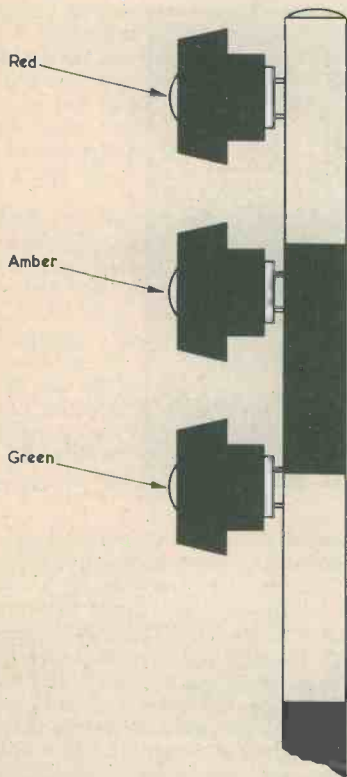


Fig. 6. As is explained in the text, l.e.d.'s with panel mounting bushes offer a fair approximation to actual traffic lights

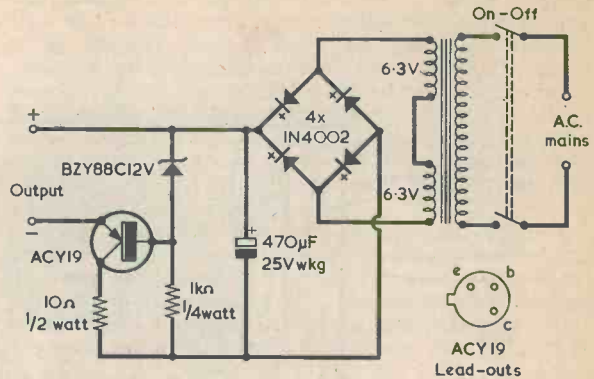


Fig. 7. A suitable mains power supply for the controller. The output connects direct to the positive and negative rails of Fig. 4

the l.e.d.'s can then be carried out with thin enamelled wire of around 30 s.w.g. This wiring travels down the *outside* of each standard, and is then covered by the tape. Wiring in this manner will be much simpler than is given by passing the wires down the centres of the standards.

The l.e.d.'s may be of any size considered suitable. A possible choice here is the "L.E.D.4" types with a diameter of 5.1mm. available from Doram Electronics under Code Nos. 586-475 (red), 586-481 (green) and 586-497 (yellow). These have the anode connected to the shorter lead-out. They are supplied with panel mounting bush assemblies which, if fitted over the l.e.d.'s, approximate to the appearance of traffic light hoods, as in Fig. 6. As mentioned earlier, all the l.e.d.'s in each section are wired up in series. Thus, all the North-South l.e.d.'s are in series circuits, as are all the West-East l.e.d.'s.

## POWER SUPPLY


The current drawn by the circuit varies between approximately 50mA and 70mA during the cycle, and this is rather high for continuous operation from dry batteries, although the use of dry batteries for initial checking may be found convenient.

Any small mains power supply offering 12 volts at the current required may be used, and a suitable circuit is given in Fig. 7, in which the pass transistor is an inexpensive germanium type having a high collector current rating. Other transistors in the ACY19 "family" of ACY17 to ACY22 will function equally well. The 10Ω resistor in the collector circuit limits surge current after switch-on when C4 on the Veroboard panel charges.

The mains transformer is a small heater transformer having two 6.3 volt secondaries. These are connected in series to produce a total voltage of 12.6 volts.

# CONSTRUCTOR'S CROSSWORD

Compiled by J. R. Davies

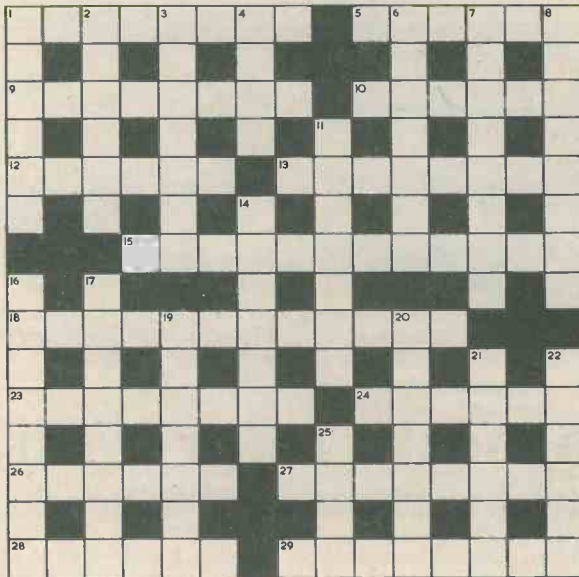

## Clues Across

1. Southern coven can turn things on. (8)
5. Acid and alcohol form these compounds. (6)
9. Emission of brilliance. (8)
10. Hustler which soaks up valve gas. (6)
12. This clock now governs the six radio pips. (6)
13. Descriptive of ion emitted by positive plate. (5, 3)
15. Muddled voter and American anode put metal on metal. (12)
18. The Ancient Mariner could have found a use for this. (5, 7)
23. NOR gate plus pole produces particle. (8)
24. In chalk a litmus paper turns blue. (6)
26. What TO5 has and TO1 has not. (6)
27. Keeping ganged tuned circuits in tune. (8)
28. Shoran spells out these Indian trees. (6)
29. SN7400 enabled in the countryside? (4, 4)

## Clues Down

1. Cliff-hanging transfer of computer bits. (6)
2. Not the aerial for stereo f.m. (6)
3. Encourage one, Capone, along this cable. (7)
4. Confused ache, 1-off. (4)
6. These flip-flop capacitors get things moving. (5-2)
7. Feedback quite opposite to 2. (8)
8. Atomiser output and what produces it. (5,3)
11. Physics term for available energy. (7)
14. Resonant radar testing device. (4, 3)
16. These parameters relate output to input. (8)
17. Electronic map tracer fitted in a vehicle. (8)
19. Go on, act out this eight-sided piece! (7)
20. Son of germanium. (7)
21. Singular laminae. (6)
22. This sideband takes up less space. (6)
25. Excess voltage could cause an excursion. (4)

For Solution see page 109

## Dust-off air blast cleaner



Immediately available from importers Pelling & Cross Ltd., 104 Baker Street, London W1., a very useful cleaning device for the hi-fi and electronics enthusiast. Dust-Off is a 14 oz. can containing a liquified gas (freon) which emerges as a pressurised, super dry but inert gas, capable of dislodging even well engrained dust and oxide from delicate tape recorder mechanisms, tape heads, and record stylus without the danger of creating static by conventional forms of wiping or brushing.

Do it yourself enthusiasts will also find it invaluable for cleaning printed circuit boards, switches and relays as well as those awkward places where no brush has access. With suitable care the can can be inverted and liquid freon made to emerge from the nozzle causing instant freezing where sprayed. This can be utilized to check faulty circuit boards and other soldered connections for 'dry joints.' Poor joints will either 'make' or 'break' under this treatment making the task of fault finding easier.

A flexible hose and extension nozzle is available so that the jet may be most precisely directed where required.

The cost of the initial Dust-Off can and trigger nozzle is £8.57 inclusive of VAT, plus post and packing at 65p. Flexible extension nozzle £1.49 plus post and packing 35p.

## Scotch cassette improvements

Compact cassettes, like cars, are continually being refined to improve their performance, although the detail improvements are seldom noticeable on cursory examination; indeed, some are visually undetectable.

3M, which is top of the sales league in the U.K. with its range of cassettes, has recently put into full-scale operation its new tape manufacturing facility at Gorseinon, near Swansea. The £34m. scheme includes an automatic cassette assembler known as the 'Snowflake,' and an impressive number of cassette winders known as 'Raindrops.' These, coupled with what is probably the world's most sophisticated tape coating machine, are now producing a range of cassettes which exhibit marked improvements over the previous hand-assembled models.

Scotch Dynarange, New High Energy, Chrome and dual-layer Classic cassettes are now all manufactured on 3M's automatic assembly lines. The mechanics are common to each range within the Scotch family, and have been designed with reliability and consistent performance in mind. In fact, 3M's Recording Materials Division is so confident about the trouble-free operation of its cassettes that it is currently calling them 'The Jambusters' in a national retail campaign which highlights their jam-free properties.

Detailed improvements in Scotch cassette design include the following:

(1) Larger, permanently fixed one-piece pressure pad for better head-to-tape contact and signal uniformity; (2) Posi-Track backing — a tape back-coating process for a smooth wind and reduction of static-induced dust attraction which can lead to annoying

drop-outs; (3) Fixed polished metal guideposts which eliminate the mechanical movement associated with nylon wheels and so reduce wow and flutter.

Improvements have also been made to tape formulations: the popular Scotch Dynarange tapes, for example, have a new oxide formulation, which gives an improvement of some 4dB over the tape previously used in Dynarange cassettes.



*Taking the "lid" off a new Scotch High Energy cassette reveals the large one-piece pressure pad and polished metal guideposts which contribute towards good wow and flutter performance.*



# COMMENT

## International Broadcasting Convention 1976

The Sixth International Broadcasting Convention will be held at Grosvenor House, London, from 20-24 September 1976 and will be opened by the Admiral of the Fleet the Earl Mountbatten of Burma, Chairman of the National Electronics Council.

Lord Mountbatten has taken a keen active interest in the art and science of radio and television for many years. He is a Past-President of the Institution of Electronic and Radio Engineers, one of the IBC sponsors.

The aims of IBC, since it was launched in 1967 have been to provide an international forum for people with interests in the wide field of broadcast engineering, to discuss developments and to exhibit and demonstrate their latest equipment and to assist the all important objective of exporting UK products and expertise. With the support of world broadcasting organisations and equipment manufacturers, these aims have been achieved and IBC is now firmly established in the international broadcasters calendar.

IBC 76, to be held at Grosvenor House, London, from 20-24 September is the sixth of the biennial conventions, each one of which has attracted an increasing number of participants from all over the world. At IBC74 more than 2,000 delegates from 44 countries attended. Today the indications are that the number will again increase with an even higher percentage from overseas.

All available exhibition space has been sold. Most of the leading world manufacturers are represented.

Running concurrently with the Exhibition will be a Technical Programme consisting of 60 papers written by leading international experts.

## Earl Mountbatten at the HEDA Exhibition



*Earl Mountbatten listens to the new Hacker portable stereo radio at the HEDA Exhibition, at NEC Birmingham. On the left are Mr. R. H. Hacker, Managing Director, and Mr. H. A. McGhee, Chairman.*

Earl Mountbatten of Burma visited the all British Stand of Hacker Radio Ltd., at the HEDA Exhibition held in the New Exhibition Centre, Birmingham.

On his whistle stop show tour, the Earl was able to listen to the third programme 'Stereo Style' on Hacker's new stereo portable radio.

One of the highlights at HEDA, it incorporates acoustic principles not previously used in portable radios. In genuine Rio Rosewood, it has a black leather and matt silver finish.

## Growing up with television


Children aged between five and 15 in Britain watch an average of 24 hours of television a week, a recent survey reported.

It is not surprising, therefore, that they in turn are constantly watched by psychologists, whose findings are read by anxious parents. A book by Grant Noble, a specialist in this field, was recently published in London and reviewed on BBC World Service. The book, called *Children in Front of the Small Screen*, is based on original research carried out with children in Britain, Ireland and Canada.


Central to the author's theme is the idea that television satisfied those needs of children which were met long ago by the village community. It was as a member of that community that the child saw enacted before him the whole pattern of social relationships which he was likely to encounter later. Through television he can learn, for example, what it is like to be a policeman or a butcher, a painter or an artisan, and to recognise people he might never

otherwise have a chance to meet.

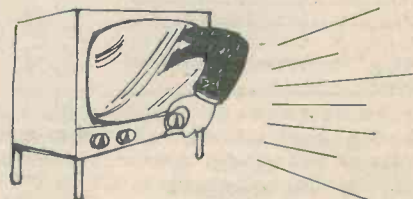On the thorny problem of television and violence, Grant Noble's view is that in nine cases out of ten televised violence has no effect on the normal child. His studies show that when children watch programmes in which violence is shown in a stylised way, as in Westerns, they do not subsequently behave in an anti-social way.



*"You're not that grown up!"*

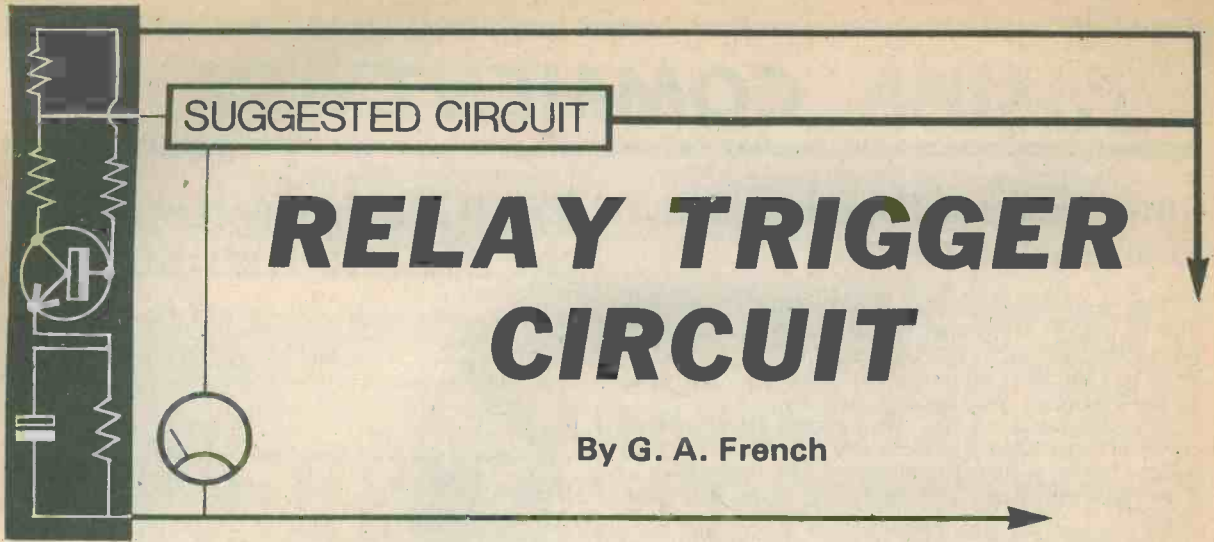

In some electronic devices it is desirable to have a very short closure of a circuit when a push-button is pressed. Typical applications are given by the starting of a timer cycle and the testing of power supplies having instant short-circuit shut-down. A very simple means of obtaining the short closure of the circuit is by means of a relay, and this offers the advantage that the contacts which provide the closure are completely isolated from the circuit which energises the relay coil. Incidentally, the technique to be discussed in this article plays an important part in a more complex device on which the author is currently working, and which he hopes to describe in a future article in the "Suggested Circuit" series.

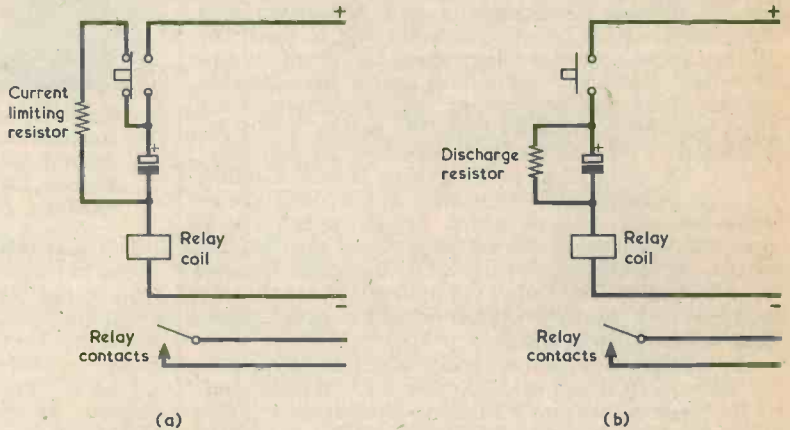


Fig. 2 (a). A development from Fig. 1 which allows the capacitor to discharge between operations (b) An alternative capacitor discharge circuit

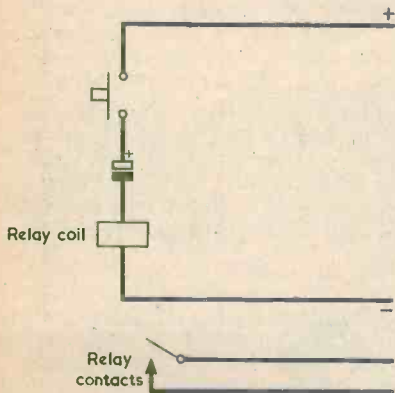


Fig. 1. The basic relay circuit. When the button is pressed the relay energises momentarily as the capacitor charges

### BASIC CIRCUIT

The basic relay trigger circuit appears in Fig. 1. Here, a discharged electrolytic capacitor is connected in series with a push-button and the coil of a relay. The relay contacts, which are normally open, couple to the circuit requiring the short closure. On pressing the button a charging current for the capacitor flows through the relay coil, causing the relay to energise and its contacts to close. If the capacitor has a low value it charges very quickly, whereupon the voltage available for the relay coil falls below the release level and the relay de-energises. Thus, pressing the button causes a very short closing of the relay contacts, the period during which they

remain closed being independent of the time the push-button is pressed. The series capacitor is shown as an electrolytic component because it is found in practice that the capacitance required is higher than can be economically provided by a non-polarised capacitor.

It is necessary to have the capacitor discharge after the push-button is opened, so that the relay will again energise when the button is pressed. One method of discharging the capacitor is shown in Fig. 2 (a). Here, the push-button is made a double-throw component, and has two extra contacts which close when pressure on the button is removed. The capacitor then discharges by way of these two contacts and the current

limiting resistor. The latter may have a value of  $10\Omega$  and, under the circuit conditions to be described, can be a  $\frac{1}{2}$  watt component.

An alternative means of discharging the capacitor is shown in Fig. 2 (b). In this circuit the push-button is the same as in Fig. 1, and the capacitor discharges, when the push-button is opened, by way of a parallel resistor permanently connected across it. This resistor must have a value significantly higher than that which would allow the relay to remain energised with the capacitor out of circuit.

If the current limiting resistor of Fig. 2 (a) or the parallel discharge resistor of Fig. 2 (b) is given a high value which does not permit quick discharge of the capacitor, relay energising after one operation is inhibited until the capacitor has discharged to the level at which a sufficiently high voltage is available for the relay coil when the push-button is pressed a second time. This effect has the result that, after the circuit has been operated once, it cannot be operated again until a pre-determined period of time has elapsed.

The relay type employed is of considerable importance, and it is necessary that it has a light mechanical action. An excellent choice here is the popular 'Miniature Open P.C. Relay' with  $410\Omega$  coil which is available from Doram Electronics Ltd. This has a single pole changeover contact set, and the armature is integral with the moving contact. Also, the armature retaining spring imparts only a small amount of tension. Relays of more common construction, in which the armature is L-shaped and pivots on a knife-edge or hinge, would be much too sluggish for use in the present application. The Doram Electronics relay was employed in all the tests next to be discussed.

## TEST CIRCUIT

The relay was initially connected in the test circuit shown in Fig. 3 (a). The relay contacts were coupled to a thyristor gate circuit, which monitored their closure. The thyristor, TH1, fired even when contact closure was virtually instantaneous, causing a forward reading to be given in the voltmeter connected across the thyristor anode load. This technique was particularly helpful during the later timing experiments, when it would otherwise have been difficult to observe the actuation of the relay as well as the second hand of a watch. After it had fired, the thyristor was returned to the non-conductive state by momentarily opening the switch S1. The push-button circuit in Fig. 3 (a) is the same as that of Fig. 2 (a). The push-button is shown as S2, the series electrolytic capacitor as C1 and the current limiting resistor as R3.

The first task was to find the minimum value required in C1 for reliable operation of the relay. Ob-

viously, the lower the value of C1 the shorter the period of closure of the relay contacts. Various values were checked and the requisite capacitance was found to be  $20\mu\text{F}$ .

The test circuit was then changed to that in Fig. 3 (b), in which the capacitor has a parallel resistor across it, as in Fig. 2 (b). This resistor is now shown as R4, and the push-button as S3.

R4 was at first given a value of  $2.2\text{k}\Omega$  and it was found that the capacitor discharged almost immediately after the push-button was opened, resulting in a performance which was virtually the same as that of Fig. 3 (a). Higher values were then

checked. With R4 at  $100\text{k}\Omega$  it was necessary to wait for 5.5 seconds after opening the push-button before the relay could be made to operate again. As is to be expected, the time delay was proportional to the value of the resistance. With R4 at  $200\text{k}\Omega$  the delay was approximately 11 secs., and with R4 at  $47\text{k}\Omega$  the delay was between 2.5 and 3 seconds. These delays would also be given with the circuit of Fig. 3 (a) if R3 were given similarly high values. Note that the delay starts after the last release of the push-button: if the button is pressed during a delay period the electrolytic capacitor becomes charged and another delay period commences.

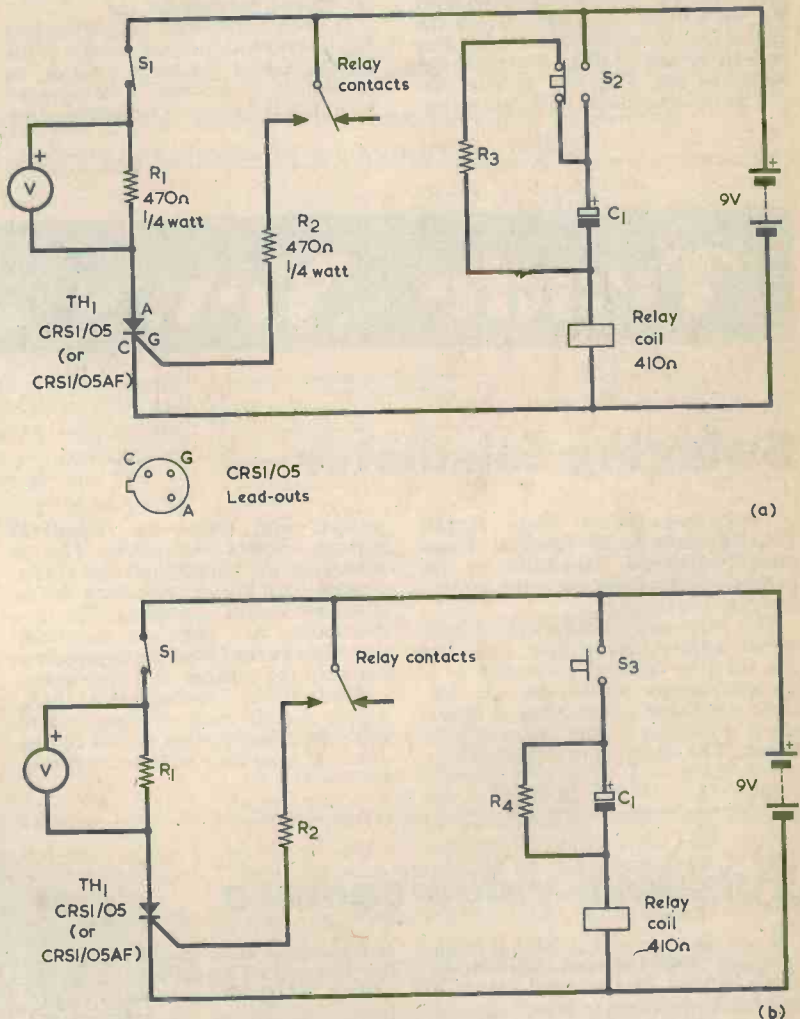


Fig. 3 (a). Simple test circuit for finding the value required in the capacitor. The thyristor circuit is helpful in monitoring relay contact operation since the thyristor turns on with even a momentary closure of the relay contacts. The voltmeter is a multi-testmeter switched to an appropriate volts range (b) The circuit of Fig. 2 (b) with thyristor monitor

## COMPONENT VALUES

The component values just mentioned were those obtained with the particular relay employed by the author. There are bound to be variances between one relay of the type specified and the next, whereupon the constructor who wishes to use the circuit has to find the value required in the electrolytic capacitor by experiment. The value required will also vary with supply voltage, which can lie in the range of 9 to 12 volts. If delays are to be incorporated the value of the discharge resistor is also found experimentally.

The constructor should first decide whether he is to use the push-button circuit of Fig. 2 (a) or that of Fig. 2 (b). The circuit is then wired up without the electrolytic capacitor. With the Fig. 2 (a) circuit the current limiting resistor should be  $10\Omega \frac{1}{2}$  watt; with the circuit of Fig. 2 (b) the parallel discharge resistor should be  $2.2k\Omega \frac{1}{2}$  watt.

Starting at around  $100\mu\text{F}$ , various values of electrolytic capacitor are then tried, reducing these until a value is reached at which the relay fails to energise when the push-button is pressed. A capacitance value slightly higher is installed. There is no necessity for a thyristor monitor circuit with this procedure as the operation of the relay can be observed visually. If a capacitor with too low a value of capacitance has been in stock for a considerable period it may initially cause the relay to energise. Such capacitors should be allowed to "form" by keeping the push-button pressed for several seconds, after which their functioning can be more accurately assessed. When no delay periods are needed, the circuit is then set up and is ready for use.

If delay periods are required either the  $10\Omega$  current limiting resistor or the  $2.2k\Omega$  parallel discharge resistor, as applicable, is removed, to be replaced by a  $100k\Omega$  resistor. The length of the

discharge period offered by this is then found with the aid of a watch having a sweep second hand or digital second display. The discharge period is the shortest time after the push-button is released at which the relay energises when the button is pressed again. When this period has been found the resistance value finally required may be calculated and the resistor installed. Thus, if the  $100k\Omega$  resistor gives a delay of four seconds when a delay of six seconds is required, the resistor finally installed may have a value of  $150k\Omega$ . Resistor values greater than  $470k\Omega$  are best avoided. The thyristor monitor circuit in Figs. 3 (a) and (b) is not essential for finding delay periods but it will in practice ease the process considerably.

For consistent performance the supply voltage for the push-button and relay circuit should be reasonably well stabilized, and regulation should be no worse than, say, plus or minus 0.5 volt of the nominal value. ■

# Trade News . . .


## Swinging calculator

Introduced by West Hyde Developments Ltd., Ryefield Crescent, Northwood, Middlesex, is the pocket calculator shown in the accompanying photograph.

This has a card sliding inside a plastic sheath approximately 6½ in. long. On one side the calculator operates as a straightforward slide rule. On the other side it has a cursor free to rotate about an eyelet at the centre of the sheath. The sliding card underneath is

printed with scales for resistance, voltage, current and power. This is moved in the sheath and the cursor rotated until the cursor centre line is over two known quantities. The corresponding two unknown quantities may then be read from the appropriate scales in the manner of a nomogram.

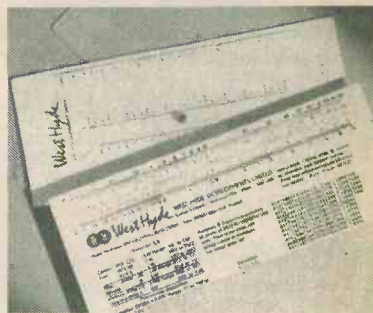West Hyde Developments, Ltd., supply a wide range of resistors and capacitors, and further details can be obtained from their address, as above.



The West Hyde Developments calculator.

## Tubeless video camera

A new development by RCA is given by their TC1155 tubeless video camera. This uses a c.c.d. (charge coupled device) image sensor instead of the traditional vidicon pick-up tube. The silicon image radiation sensor uses 163,840 elements which enable the camera to provide sharp clear highlights with anti-blooming characteristics. Image retention due to trace persistence in electron beam tubes is thereby eliminated.

The image sensor incorporates a

self-scanning technique in which electric charges are transferred along the surface of the silicon wafer which forms the heart of the image sensor. Varying intensities of visible or infrared light impinging on the wafer surface produce proportional changes in the charge in discrete silicon elements. These changes are digitised and encoded with timing data for transmission to the receiver.

The light-weight (2.5lb.) TC1155 camera takes advantage of the

reliability and operation benefit of solid-state technology and operates over a range of  $-12^{\circ}\text{C}$  to  $+50^{\circ}\text{C}$ . The camera is suited to uses such as industrial process control or scientific instrumentation where non-contact measurement based on precision image geometry is advantageous.

Additional information may be obtained by writing to RCA Electro-optics and Devices, Sunbury-on-Thames, Middlesex.

# AUDIO CONTROL CIRCUITS — 3

## AUTOMATIC FADER

By P. R. Arthur

This concluding article in our 3-part series describes how the MC3340P integrated circuit may be employed in an automatic fader.

In the preceding two articles of this series, circuits have been described which incorporate the Motorola MC3340P electronic attenuator, these circuits consisting of a compression amplifier, an audio squelch unit and a dynamic noise limiter. As was stated in the first article of the series, the MC3340P is a new device which supersedes the MFC6040. Both these i.c.'s are electrically identical and are different only in the number of pins and pin spacing. The pin connections for both types were given in the first article.

We now proceed to the final audio control circuit to be dealt with, this being an automatic fader.


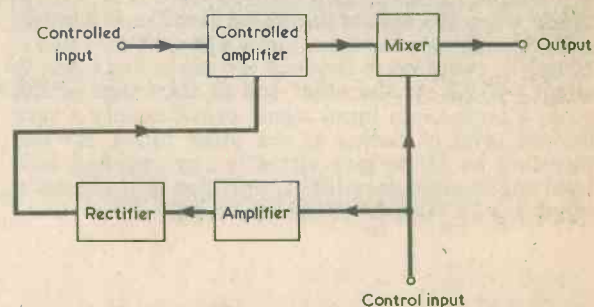


Fig. 14. Block diagram illustrating the operation of the automatic fader

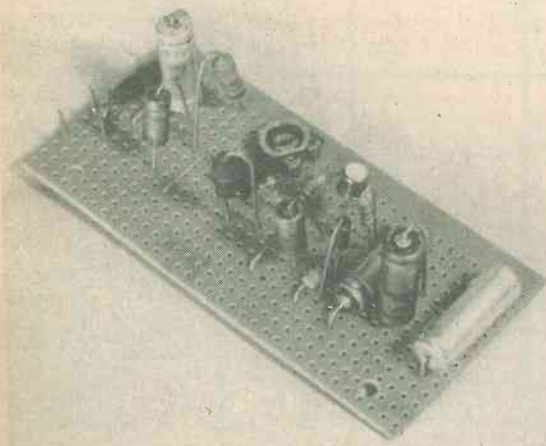

The components of the automatic fader are wired up on a Veroboard panel

### AUTOMATIC FADER

An automatic fader is a type of 2-channel audio mixer, but it has the additional facility that when a signal is fed to the main input the secondary input is automatically attenuated or faded out. This type of circuit can be employed in the production of electronic music, in home movie equipment and at discotheques. There are, no doubt, other uses to which it may be put.

Fig. 14 shows the stages of the fader in block diagram form. The main, or control, input is fed straight to the mixer, whilst the secondary controlled input is fed to the mixer via a controlled amplifier (the MC3340P). Part of the main input signal is amplified, rectified and smoothed, and the d.c. potential thus produced is applied as a control voltage to the controlled amplifier. The circuit is arranged such that the greater the control voltage, the lower the gain of the controlled amplifier. Feeding an input signal to the main input thus fades out the secondary input.

## THE CIRCUIT

As can be seen from the circuit of Fig. 15, only a single active device is needed in addition to the MC3340P.

R5 and R6 form a simple passive mixer which combines the control input and the output from the controlled amplifier. The controlled input is fed to the input terminal (pin 1) of the i.c. via C5. R4 sets the gain of the device at about unity, and C6 is the roll-off capacitor.

The control input signal is also fed via C2 to the base of TR1. TR1 is used as a common emitter amplifier with R1 as the collector load resistor and R2 as the base bias resistor. A pre-set variable resistor, R3, is connected in the emitter circuit of TR1 and is unbypassed.

The amplified signal appearing at the collector of TR1 is fed to a voltage doubling rectifier and smoothing circuit consisting of C3, D2, D1 and C1. The positive bias produced at the positive terminal of C1 is then applied to the control terminal (pin 2) of the MC3340P. Thus, a signal input at the control input produces a positive bias of proportional value at pin 2 of the i.c., and fades out the secondary input accordingly.

The voltage gain of TR1 is controlled by R3, which is a simple feedback gain control. Gain is at a maximum when R3 inserts minimum resistance into circuit. At this gain level an input signal of only about 100mV is required to fade out the controlled input to about -40dB. At the other end of the range of R3, quite a large main input signal provides only a very limited level of fading at the other input. R3 can therefore be set to give virtually any required fade level to the secondary input, provided that the main input is at a level of 100mV or more.

## COMPONENTS

### Resistors

(All fixed values  $\frac{1}{2}$  watt 5 or 10%)

R1 4.7k $\Omega$  R2 2.2M $\Omega$

R3 2.2k $\Omega$  skeleton potentiometer, 0.1 watt, horizontal mounting (see text)

R4 6.8k $\Omega$

R5 10k $\Omega$

R6 10k $\Omega$

### Capacitors

C1 100 $\mu$ F electrolytic, 10 V Wkg.

C2 1 $\mu$ F electrolytic, 25 V Wkg.

C3 10 $\mu$ F electrolytic, 16 V Wkg.

C4 25 $\mu$ F electrolytic, 16 V Wkg.

C5 10 $\mu$ F electrolytic, 16 V Wkg.

C6 560pF polystyrene

C7 10 $\mu$ F electrolytic, 16 V Wkg.

### Semiconductors

IC1 MC3340P

TR1 BC108C

D1 OA91

D2 OA91

### Switch

S1 s.p.s.t. toggle

### Miscellaneous

Veroboard, 0.1in. matrix, 34 holes x 14 strips

Veropins (as required)

Wire, etc.


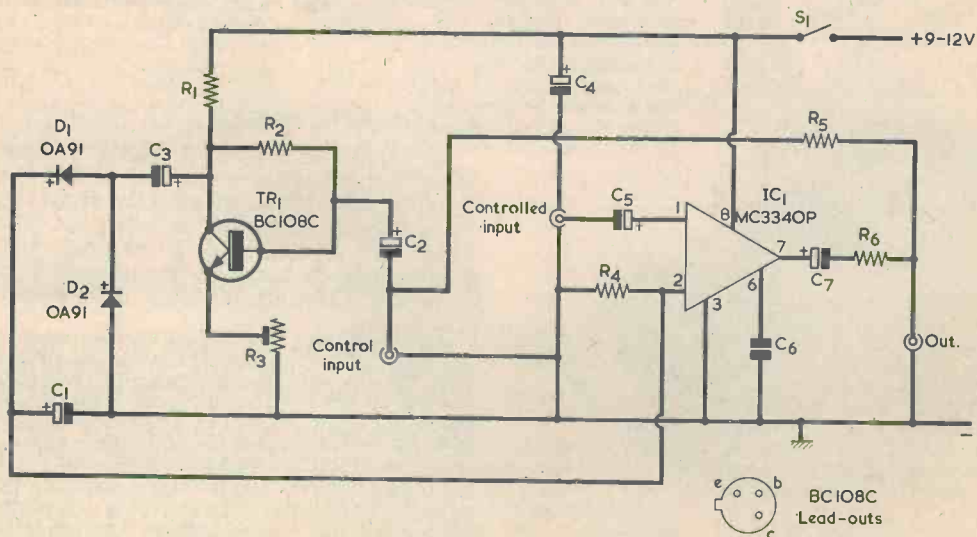


Fig. 15. Full circuit diagram for the automatic fader

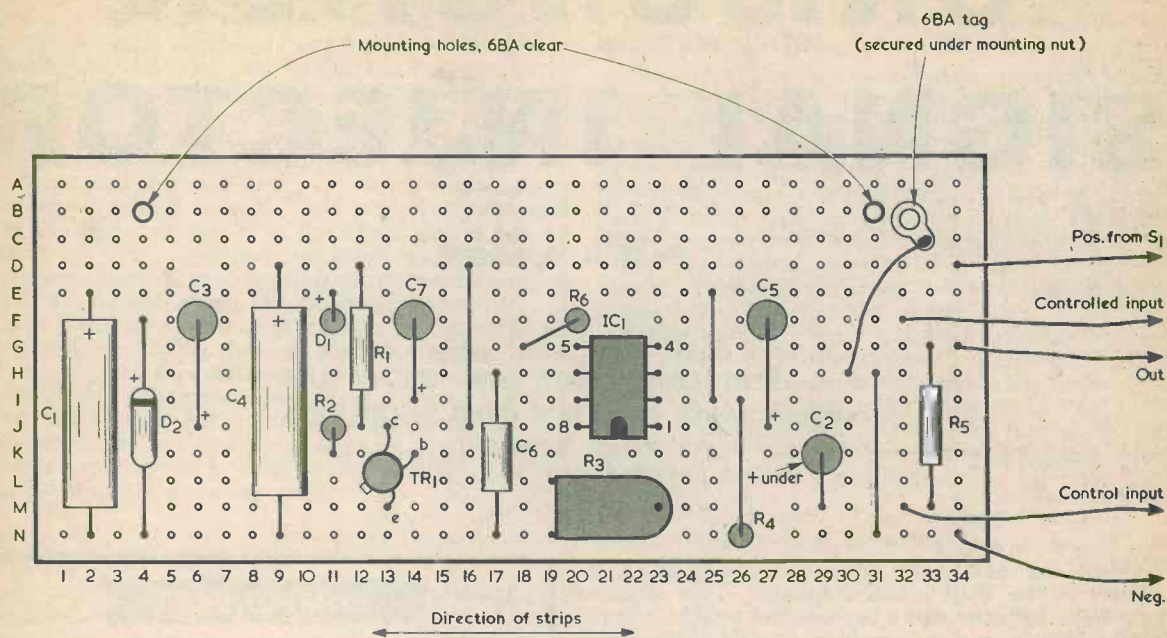

Cut strips at : F12,F24,H21,I21,J21,J14 and M26

Fig. 16. Component side of the Veroboard assembly. (Pins 4 and 5 of the integrated circuit are 'NC' pins.)

The input impedance at the control input is dependent upon the setting of R3 and the input impedance of the circuit into which the output couples. A low input impedance would be given if R3 inserted zero resistance into circuit, but in practice this resistor will probably insert a few ohms at its minimum resistance setting. The control signal input impedance may therefore be looked upon as ranging between some 1k $\Omega$  to 10k $\Omega$  or more. The input impedance at the secondary input is of the order of 50k $\Omega$ .


The current consumption is approximately 8mA from a 9 volt supply and 12mA from a 12 volt supply.

## CONSTRUCTION

The automatic fader components are assembled on a 0.1in. matrix Veroboard panel having 34 holes by 14 copper strips. Fig. 16 gives full details of this panel.

First, cut out the panel to the correct size with a small hacksaw, then drill out the 6BA clear mounting holes. Next cut the copper strips at the points specified, using a Vero spot face cutter or a small twist drill held in the hand. Then fit and solder the components to the panel as illustrated. Note that R3 is a pre-set potentiometer having its two track tags spaced at 0.2in. and its slider tag spaced 0.4in. from the track tags. Fit 0.1in. Veropins to the circuit points where external connections to the supply, etc., are made.

The panel can be fitted in a small metal case which is connected to the negative rail by a solder tag under one of the securing nuts. The input and output sockets may be phono or coaxial types, or jacks, according to preference, and they take up their chassis connection by way of the metal case. The leads from the panel to their non-earthly contacts need not be screened but should be kept reasonably short. If a battery is used for the supply this may also be housed in the metal case.

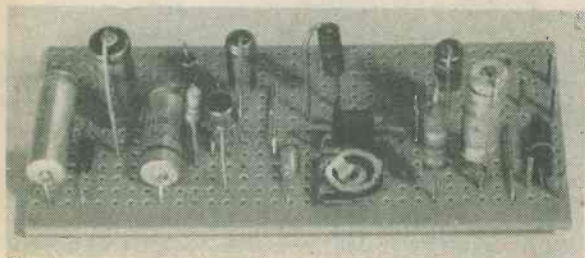

Another view of the Veroboard assembly

(Concluded)

# UNIUNCTION SIGNAL INJECTOR

By N. R. WILSON

A low cost instrument which offers a modulated test signal over all of the medium wave band and most of the long wave band.

One of the most useful devices for use as an a.f. oscillator is the unijunction transistor. This requires only three resistors and a capacitor to enable it to oscillate at any audio frequency, and it can operate without the necessity of bypassing the supply rails. A further advantage is that it produces a waveform which is rich in harmonics, these extending well over 2MHz.

## SIGNAL INJECTOR

A unijunction transistor, TR1, appears in Fig. 1 and in conjunction with R1, R2, R3 and C4 functions as an oscillator running at around 800Hz. Oscillation takes place in conventional manner; after on-off switch S2 is closed C4 charges by way of R3 until the

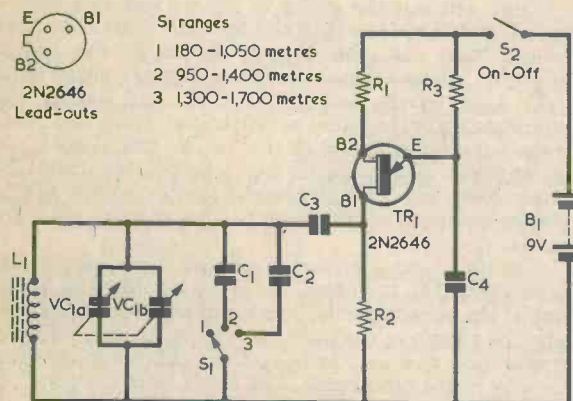


Fig. 1. The circuit of the unijunction signal injector. This produces a modulated r.f. signal over the ranges indicated

## COMPONENTS

### Resistors

(All  $\frac{1}{4}$  watt 10%)

R1 470  $\Omega$

R2 150  $\Omega$

R3 22k  $\Omega$

### Capacitors

C1 750pF polystyrene or silvered mica (see text)

C2 1,500pF polystyrene or silvered mica

C3 See text

C4 0.047 $\mu$ F plastic foil

VC1(a)(b) 500+500pF variable air-spaced, 2-gang.

### Coil

L1 Home-wound on ferrite rod (see text)

### Transistor

TR1 2N2646

### Switches

S1 Single pole 3-way, rotary

S2 S.P.S.T., toggle

### Battery

B1 9 volt battery

potential on its upper plate reaches triggering level, whereupon it discharges abruptly via the emitter and base 1 of the transistor into R2. The capacitor then charges again by way of R3 until the triggering level is once more reached, and so the cycles proceed.

A series of abrupt pulses at oscillator frequency is present at the base 1 of the transistor. In Fig. 1 these are loosely coupled via C3 to the tuned circuit given by L1 and VC1(a)(b), together with C1 or C2 when range switch S1 is adjusted accordingly. The pulses passed via C3 shock-excite the tuned circuit and cause



damped oscillations to be produced at its resonant frequency. If the coupling provided by C3 is loose enough, and if the tuned circuit has a reasonably high Q, the frequency range over which the damped oscillations appear is nearly as sharply defined as occurs with a conventional r.f. oscillator having positive feedback. Since the damped oscillations are produced by the pulses from the unijunction transistor, the r.f. signal at the tuned circuit is effectively amplitude modulated at unijunction oscillator frequency.

L1 can be a coil wound on a ferrite rod whereupon a further advantage accrues. This is given by the fact that the signal produced in the tuned circuit can be picked up on a transistor superhet receiver whose ferrite rod aerial is held parallel with the rod on which L1 is wound and about six inches away from it.

The purpose of the signal injector is to provide an amplitude modulated signal of known frequency which can be coupled to a medium and long wave superhet without any interconnecting wires. It may then be used for tuning and padding adjustments in the receiver aerial and oscillator circuits, for frequency calibration of a newly constructed receiver, and for general receiver servicing work.

## FREQUENCY RANGES

In order to obtain a wide frequency range, the capacitance in the tuned circuit is capable of being varied from a low to a relatively very high value. When range switch S1 is set to position 1, L1 is tuned by VC1(a) and (b) in parallel. VC1(a)(b) is a 2-gang 500+500pF air-spaced variable capacitor, offering a maximum capacitance of 1,000pF. Variable 2-gang capacitors of this type were commonly used in the earlier valve radio receivers, and they are still available in several styles from many of the mail order houses. They tend to be somewhat more bulky in size than the variable capacitors encountered in modern transistor receivers.

With the prototype, the coverage given by VC1(a)(b) on its own is 180 to 1,050 metres. When S1 is set to Range 2, C1 is connected across the 2-gang capacitor, and the range given by adjusting the capacitor then becomes 950 to 1,400 metres. Setting S1 to position 3 gives a range of 1,300 to 1,700 metres. C1 and C2 should be polystyrene or silvered mica capacitors. C1 in the prototype is 750pF but this value may be a little difficult to obtain from retailers, and if necessary the more readily available value of 680pF may be employed instead. Should it be found that this value does not give an overlap with the low wavelength end of Range 3, a further capacitor of around 68pF may be connected in parallel. Since L1 is home-wound, the actual ranges obtained may vary slightly from those shown in Fig. 1, but they should agree in general and have a small amount of overlap between them.

Coil L1 consists of 75 turns of 30 s.w.g. enamelled wire close-wound at the centre of a ferrite rod having a length of 7in. and a diameter of  $\frac{3}{8}$ in. Shorter rods down to a length of 5in. may also be employed and these will require proportionately more turns. It is a simple matter to find the number of turns required with such rods. First wind on too many turns (say 90) then remove these, as required, until the tuned circuit resonates at 200 metres with VC1(a)(b) vanes nearly fully out of mesh and S1 at position 1.

The current consumption of the circuit is only

1.4mA, and B1 may be a small battery such as the Ever Ready PP3.

## CONSTRUCTION

The circuit can be assembled in any small wooden or plastic case with L1 mounted on the outside. The rod should be several inches clear of the battery and the metal frame of the 2-gang capacitor. The leads to L1 should be kept reasonably short, as these will also radiate r.f. energy and it is desired to have as much as possible of the radiation given by L1 only. The 2-gang capacitor needs to be fitted with a pointer knob or cursor and a scale which can be calibrated over the three ranges. There is no necessity for a slow motion drive if a reasonably large knob is fitted.

Capacitor C3 is not a physical capacitor but consists of the capacitance between a short insulated wire and the lead of R2 which connects to the base 1 of the transistor. The arrangement is shown in Fig. 2. The degree of coupling can be varied by moving the wire and it should be sufficiently loose to ensure that a sharp well-defined signal is given.


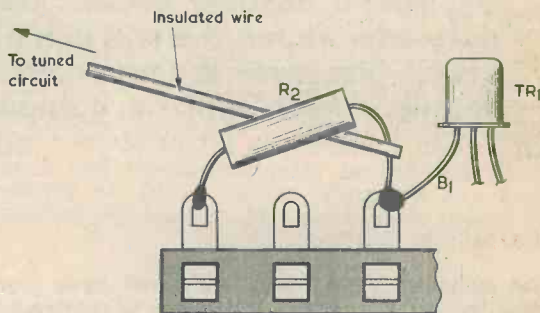


Fig. 2. C3 is given by positioning an insulated wire from the tuned circuit against or near to the non-earthly lead-out of R2

After the circuit has been assembled it may be checked out with a standard medium and long wave superhet. The latter is positioned with its ferrite rod parallel with L1, and VC1(a)(b) is adjusted until the modulating tone is picked up. The tone may be heard weakly at frequencies other than the resonant frequency but the presence of the latter will be obvious when it is tuned in. The tone tunes in about as sharply as a broadcast station on both medium and long waves. It is a little weaker on long waves due to the high tuning capacitance in the unit. The optimum spacing between the receiver ferrite aerial rod and L1 will soon become apparent after a little experience.

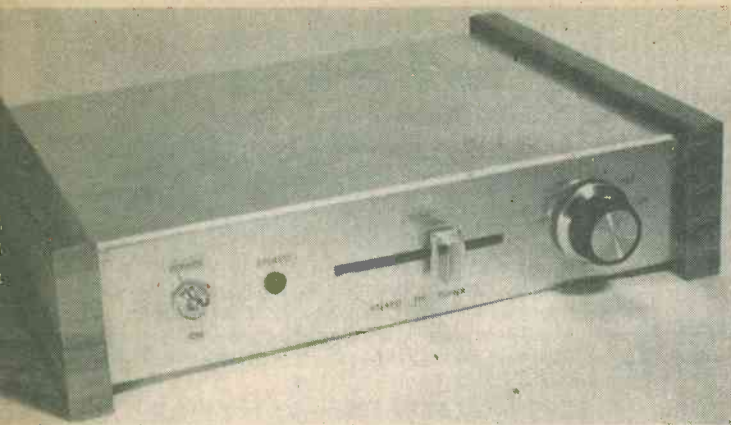The unit is then calibrated in terms of wavelength with the aid of a receiver having a reliably calibrated tuning scale, checking against stations of known wavelength when these appear. There will, of course, be a gap in the calibration between about 600 metres on the medium wave band and about 1,000 metres on the long wave band. ■



# The 'Ac

## Part 1

By R. A. Penfold

Incorporating two integrated circuits and a pre-aligned front-end module, this f.m. tuner is far simpler to construct than would be one employing discrete components throughout. If desired, the stereo decoder section may be omitted or added at a later date whereupon the unit can then function as a mono tuner. This article discusses the tuner circuit and commences constructional details, which will be completed in next month's concluding article.

Not so many years ago it may well have been beyond the scope of many constructors to complete a stereo f.m. tuner project. This was not necessarily due to the complexity of the circuitry involved, but was mainly because of the complications incurred in aligning the finished tuner.

The setting up problem can be overcome these days by the use of modern circuitry which, although originally developed to reduce and simplify the test and alignment procedure for commercially made tuners, also has the effect of enabling the home constructor to carry out a successful alignment even when no test equipment is available.

### TUNER STAGES

Fig. 1 gives a block diagram of the various stages which comprise the tuner to be described. The front end is based on a ready made module, the Mullard LP1186. This is pre-aligned by the manufacturer and needs no further adjustment. The module is coupled aperiodically to a single transistor i.f. amplifier, which is in turn coupled to an integrated circuit i.f. amplifier and quadrature detector via a ceramic filter. The only conventional L-C tuned circuit used in this combination is the quadrature detector coil, and this can be given the correct adjustment very simply without the need for any test equipment.

The stereo decoder is based on a modern integrated circuit employing a phase locked loop (p.l.l.). This

requires only the adjustment of a single pre-set potentiometer for alignment, and again no test equipment is required for this. All stages are supplied by a stabilized and well smoothed mains power supply unit.

The tuner has been designed primarily as a relatively simple unit and is not quite as sensitive as

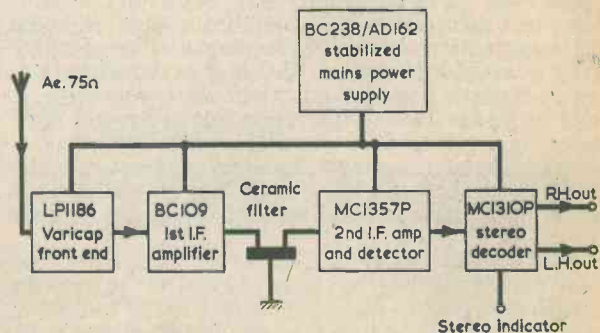


Fig. 1. Block diagram illustrating the stages of the stereo f.m. tuner. If desired, the stereo decoder section may be omitted, whereupon the unit can be used as a mono f.m. tuner

# Academy' Stereo

## F.M. Tuner


some of the more elaborate modern tuners. It does, however, have enough sensitivity to provide good reception of the ordinary national v.h.f. B.B.C. transmissions in most areas, as well as reception of B.B.C. and commercial local radio stations where these are in operation.

The use of integrated circuits enables a high quality output to be given despite the relative simplicity of the overall circuit. The i.f. amplifier-detector i.c. gives a typical distortion level of only 0.5% at an i.f. of 10.7MHz, and the stereo decoder has an even lower distortion figure of typically 0.3% at the maximum permissible input level.

The building of the tuner should not prove to be too troublesome provided the constructor has some ex-

perience in etching his own printed circuit boards. Most of the circuitry is contained on three printed boards, one for the power supply, one for the tuner and one for the stereo decoder.

The unit is housed in an attractive case of the "book-ends" type, which is made by slightly modifying a ready-made chassis. Switch tuning is employed, giving five pre-set tuning positions together with a sixth position which enables variable tuning to be accomplished by means of a slider potentiometer on the front panel. Frequency coverage is from approximately 87 to 104MHz. The output level is about 250mV r.m.s., and should preferably be fed into an impedance of about 100k $\Omega$ . Virtually any stereo amplifier will have at least one suitable input.

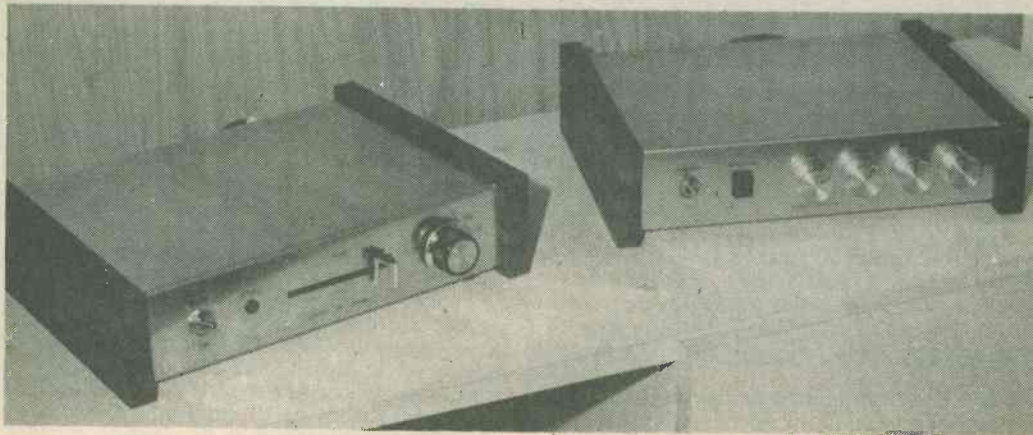

*The tuner employed in conjunction with the Stereo I.C. Amplifier described in our March 1976 issue*

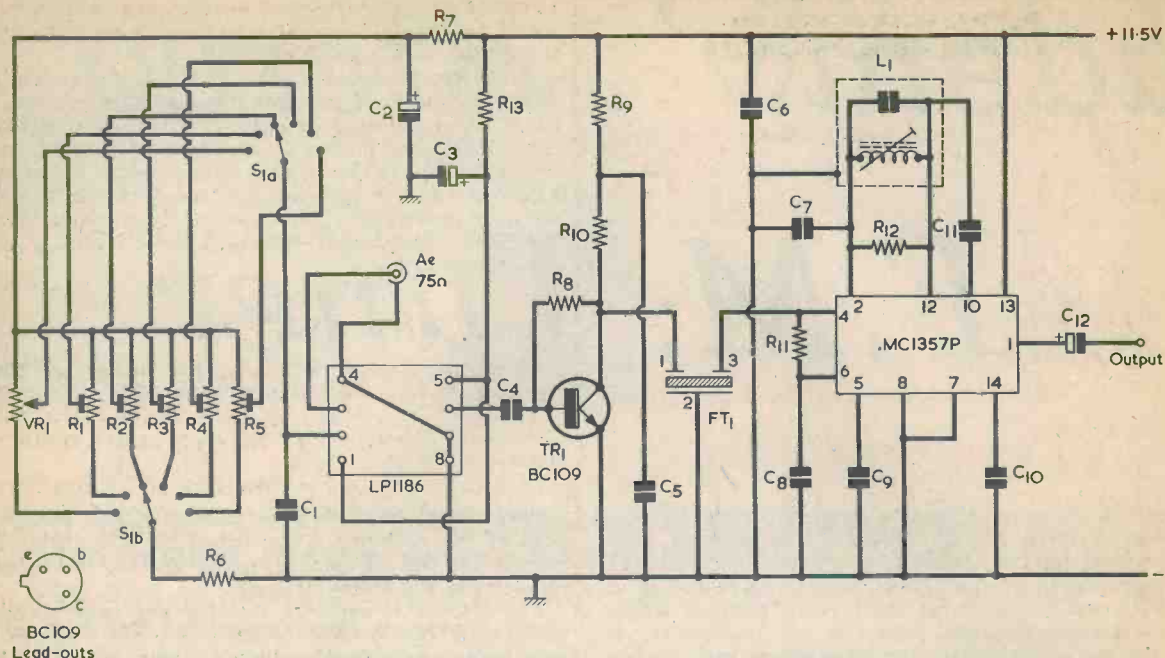


Fig. 2. The basic tuner section of the unit. This provides a mono output via C12 and incorporates a Mullard controlled f.m. module type LP1186

## THE CIRCUIT

The circuit diagram of the tuner, less the power supply and stereo decoder sections, is shown in Fig. 2.

S1(a)(b) is the tuning switch and selects one of six potentiometers, according to its position. VR1 is a front panel manual tuning potentiometer, whilst R1 to R5 are pre-set tuning potentiometers. R6 forms part of the potential divider at all settings of S1 (a)(b), and limits the minimum voltage which can be fed to pin 2 of the LP1186 module.

This module incorporates variable capacitance diodes for tuning and requires only a single tuning voltage. The aerial couples to pin 3, and pins 4, 7 and 8 are the aerial earthy input, i.f. earthy output and negative supply connections respectively. These are all connected to chassis. Pin 5 is the positive supply input, and the basic 11.5 volt supply is reduced to about the required level of 8 volts by R13. C3 provides decoupling. The tuning voltage must obviously be extremely well smoothed in order to ensure that mains hum is not introduced by modulation of the local oscillator, and so extra smoothing is provided by R7 and C2.

Pin 1 is the a.f.c. connection to the module. Since frequency stability was found to be quite adequate without a.f.c. this facility has been omitted from the present design and pin 1 connects to the positive supply.

The i.f. output from the module is coupled via C4 to the base of TR1, the first i.f. amplifier. This is connected in the common emitter mode, and is fed from the positive supply via the decoupling components R9 and C5. The value of R10 is chosen to match the input impedance of the ceramic filter, FT1.

Pin 4 of the Motorola MC1357P i.c. connects to the other side of the ceramic filter. This i.c. comprises an i.f. amplifier and quadrature detector. R11 completes part of the bias circuit of the i.c. and also largely determines the input impedance, which matches the output impedance of the filter. It is important that the impedances of the circuits at the input and output of the filter provide a good match, as otherwise the shape of the i.f. passband will deteriorate.

C6 to C9 are all decoupling capacitors. There are relatively few decoupling capacitors required here when compared with discrete component amplifiers. This is due to the use of three long-tailed pairs coupled via emitter followers to form the i.f. amplifier inside the i.c., these being fed from an internal voltage regulator. The long-tailed pairs, at 53dB, provide the bulk of the gain of the tuner, although the LP1186 front-end adds a useful further gain of 30dB. The i.f. transistor, TR1, does little more than make up for the 6dB loss in the ceramic filter.

L1, C11 and R12 are in the tuning circuit for the quadrature detector. The capacitor shown connected across L1 is an integral part of the ready-made coil unit. The output of the quadrature detector connects to pin 1 of the i.c. via an internal emitter follower. C12 provides d.c. blocking at the output.

C10 is the de-emphasis capacitor, as is required for mono reception, and is connected between the output of the quadrature detector and chassis. It has the effect of reducing the treble content of the audio output signal. This is necessary because the signal is given a degree of pre-emphasis (treble boost) at the transmitter, and a compensatory reduction in the treble response is required in the receiver. The overall

## COMPONENTS

### Resistors

(All fixed values  $\frac{1}{4}$  watt 5%)

R1-R5 100k $\Omega$  pre-set potentiometer, horizontal skeleton, standard size

R6 15k $\Omega$

R7 270 $\Omega$

R8 220k $\Omega$

R9 100 $\Omega$

R10 330 $\Omega$

R11 390 $\Omega$

R12 3.9k $\Omega$

R13 680 $\Omega$

R14 4.7k $\Omega$

VR1 100k $\Omega$  potentiometer, linear, slider (see text)

### Capacitors

C1 0.1 $\mu$ F type C280 (Mullard)

C2 10 $\mu$ F electrolytic, 16 V Wkg.

C3 50 $\mu$ F electrolytic, 16 V Wkg.

C4 0.01 $\mu$ F type C280 (Mullard)

C5 0.022 $\mu$ F plastic foil

C6 0.022 $\mu$ F plastic foil

C7 0.1 $\mu$ F plastic foil

C8 0.1 $\mu$ F plastic foil

C9 0.1 $\mu$ F plastic foil

C10 5,600pF polystyrene (see text)

C11 4.7pF silvered mica or ceramic

C12 10 $\mu$ F electrolytic, 16 V Wkg.

C13 100 $\mu$ F electrolytic, 16 V Wkg.

C14 220 $\mu$ F electrolytic, 16 V Wkg.

C15 1,500 $\mu$ F or 1,600 $\mu$ F electrolytic, 30 V Wkg.

### Inductors

L1 Coil assembly type KACS K586 HM (see text)

T1 Mains transformer, miniature, secondary 9-0-9 V at 100mA (see text)

### Semiconductors

IC1 MC1357P

TR1 BC109

TR2 BC238

TR3 AD162 (with insulating kit)

D1-D4 1N4001

D5 BZY88C12 V

### Module

Voltage controlled f.m. tuner module type LP1186 (Mullard)

### Filter

FT1 Ceramic filter type CFSA 10.7. no colour (see text)

### Switches

S1 (a) (b) 2-pole 6-way rotary

S2 (a) (b) D.P.S.T. toggle

### Miscellaneous

Control knob

Coaxial socket

3-way DIN socket

Mains lead

18 s.w.g. aluminium chassis with base plate, 9 x 7 x 2in. (see text)

Chipboard (see text)

Materials for printed boards

Nuts, bolts, etc.

effect of pre-emphasis and de-emphasis is to give a small but worthwhile improvement in the signal-to-noise ratio of the received signal.

It is important to note that C10 is only needed for mono reception. The tuner can easily be built as a mono unit by simply omitting the stereo decoder, connecting the output from C12 to the output socket, and including C10 on the printed circuit board. When the stereo decoder is included C10 must be omitted, as stereo reception will otherwise not be possible. With the stereo decoder, de-emphasis is provided at the decoder outputs.

## POWER SUPPLY SECTION

Since any changes in the supply voltage will alter the frequency to which the unit is tuned, it is absolutely essential that a well stabilized power supply be employed. The circuit of the power supply section is shown in Fig. 3.

The output from the secondary of T1 is fed to a bridge rectifier consisting of D1 to D4. T1 is a transformer having a 9-0-9 volt secondary with the 0 volt centre-tap ignored. The output from the bridge rectifier is smoothed by C15.

A stabilized potential of 12 volts is provided by the simple shunt regulator formed by R14 and zener diode D5. C13 smooths out any mains hum or noise present across D5.

TR2 and TR3 are wired as common emitter amplifiers, with a 100% negative feedback loop between the collector of TR3 and the emitter of TR2. This combination gives a voltage gain of almost exactly unity. Therefore the voltage at the collector of TR3 is virtually fixed relative to that at the base of TR2. About 0.5 volt is dropped between the base and emitter of TR2, and so the output stabilizes at about 11.5 volts.

Since the combined current gain of TR2 and TR3 is very high a low output impedance is achieved, and the supply is easily able to handle the necessary output current of about 35 to 40mA. C14 provides final smoothing of the supply, and S2 is the on-off switch.


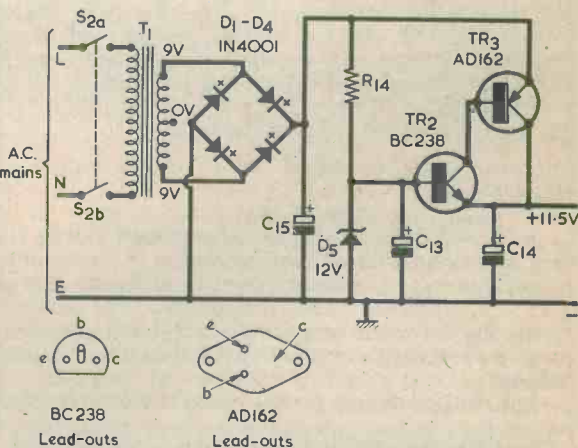


Fig. 3. The power supply section. This gives a well stabilized output voltage, thereby ensuring that there are no shifts in tuning due to supply voltage changes

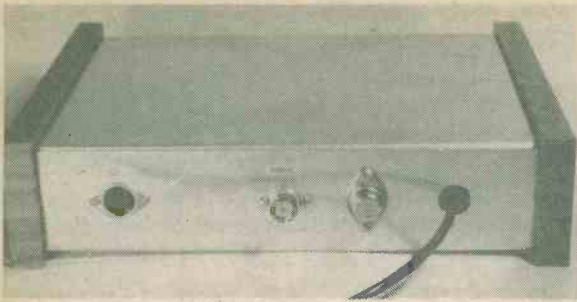

Mounted on the rear panel are the aerial and output sockets, together with the power transformer incorporated in the stabilized mains power supply

The circuit of Fig. 3 gives an extremely well smoothed and stabilized output, and quite large variations in the output load current and mains input voltage have no significant effect on the output voltage. This assumes, of course, that D5 is a good-quality component.

## COMPONENTS

Some notes on the components so far encountered will be helpful. The MC1357P integrated circuit is listed by Chromasonic Electronics, 56 Fortis Green Road, Muswell Hill, London, N10 3HN. The coil assembly specified for L1 is available from Ambit International, 25 High Street, Brentwood, Essex, CM14 4RH, as also is the ceramic i.f. filter type CFSA 10.7. These filters have five frequency groupings around 10.7MHz identified by a colour code, and filters centred on 10.7MHz are identified by no colour. A filter of this type is to be preferred. R1 to R5 are standard sized horizontal skeleton pre-set potentiometers, and not miniature types.

The mains transformer must be a miniature type, and the component employed in the prototype was obtained from M. Dziubas, 158 Bradshawgate, Bolton, BL2 1BA. The slider potentiometer has an overall length of 87mm. and can be obtained from several suppliers including Electrovalue Ltd., 28 St. Judes Road, Englefield Green, Egham, Surrey, TW20 0HB. Its knob has to be ordered separately.

## THE CASE

A 16 s.w.g. aluminium chassis measuring 9 by 7 by 2in. and fitted with a baseplate forms the basis of the case. This can be obtained from H. L. Smith and Co. Ltd., 287 Edgware Road, London W2. The baseplate forms the lid of the unit and, when this is completed, may be secured in place with small self-tapping screws.

The drilling details for the case are shown in Fig. 4, where the front and rear panels and the two sides are shown flat for ease of presentation.

The cut-out for VR1 can be made by first drilling a  $\frac{1}{8}$ in. diameter hole, and then using a miniature round file to lengthen this to the dimensions shown. A miniature flat file can finally be used to square up the ends of the cut-out, and to remove any irregularities

which may be evident. The easiest method of mounting VR1 is to glue it in position with an epoxy adhesive. Great care must be taken to ensure that no adhesive gets onto the track. The component must be aligned accurately behind its cut-out.

The hole for D6 will take a panel mounting light-emitting diode functioning as a stereo beacon with the stereo decoder. D6 can be any l.e.d. offering a reasonably bright light at a forward current of around 10mA, and a relatively large l.e.d. will give a good appearance to the front panel. If the unit is to be constructed as a mono tuner, the l.e.d. may be powered from the 11.5 volt supply via a 1k  $\Omega$  resistor and employed as an on-off indicator.

The aerial and output sockets are mounted on the rear panel, the former being a standard coaxial socket and the latter a 3-way DIN socket. There is also a hole which takes a  $\frac{1}{2}$ in. grommet for the mains lead. Further required are four holes for TR3, the body of which is on the outside of the chassis. TR3 is insulated from the chassis by means of the usual mica washer and insulating bushes, and the washer may be used as a template for marking out the holes required. The holes must be free of burrs and, when the transistor is mounted, a solder tag inside the chassis under the upper securing nut provides the collector connection. A continuity tester or ohmmeter is employed to make quite certain that the transistor is fully insulated from the chassis.


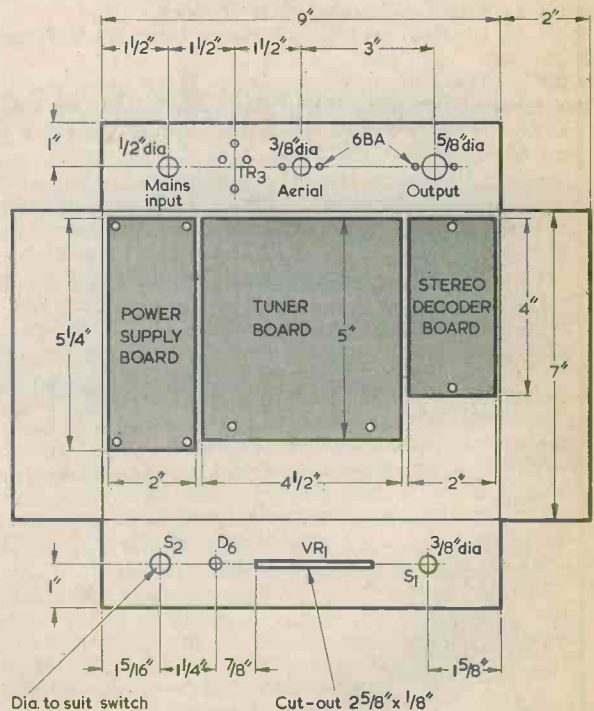



Fig. 4. Drilling details for the tuner chassis. The sides, and the front and rear panels are shown opened out to simplify presentation. Also illustrated are the positions taken up by the three printed circuit boards

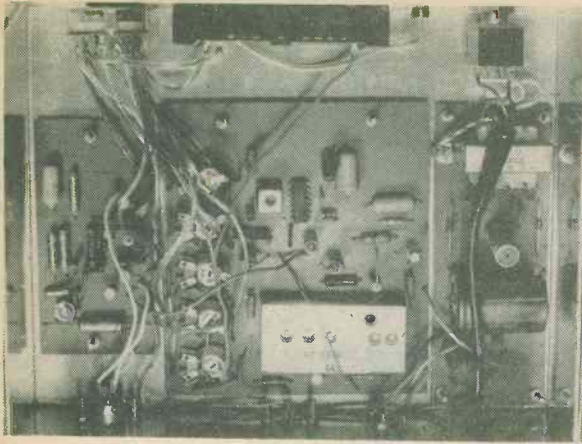

*The tuner circuitry is carried on three separate printed circuit boards*

The mounting holes on the chassis bottom for the printed circuit boards can be marked out with the aid of the boards themselves after they have been made up. Their positions and outside dimensions are shown in Fig. 4.

Two pieces of chipboard, each measuring  $2\frac{1}{2}$  by  $7\frac{1}{2}$  by  $\frac{1}{8}$  in. are glued to the ends of the chassis to give a case having a "book-ends" appearance. The chipboard is first covered with a self-adhesive material, such as Fablon or Contact, over its surface apart from most of the inside area which will be against the aluminium. Material having a woodgrain pattern offers what is probably the most attractive finish. The two pieces of chipboard are then glued to the ends of the chassis by means of epoxy resin applied to the uncovered sections of the chipboard.

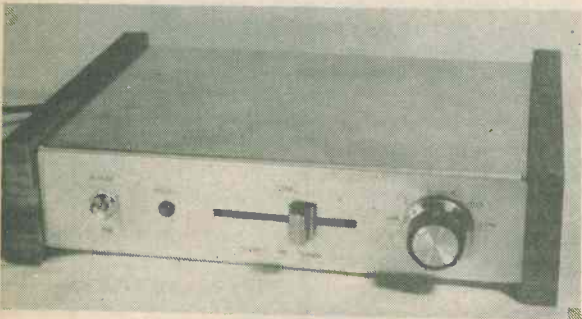

*A further look at the front panel of the tuner, showing its neat and simple finish*

#### NEXT MONTH

In next month's concluding article constructional details will be given for the power supply and tuner printed boards, after which the stereo decoder circuit and its assembly will be described. The accompanying Components List specifies the parts required for the power supply and tuner sections. A further Components List for the decoder section will appear in Part 2.

*(To be concluded)*

SEPTEMBER 1976

# RADIO & ELECTRONICS CONSTRUCTOR

## SPECIAL FEATURE IN OCTOBER ISSUE



### REGENERATIVE SHORT WAVE SUPERHET, Part 1 (2 parts)



Covering 1.6 to 25MHz, or 190 to 12 metres, this battery operated superhet will function both with a speaker or headphones. The coils and mixer transistor are wired up in a compact coil pack module, and an attractive feature is the provision of adjustable regeneration at the detector. Constructional details will be completed in the concluding article in the November issue.



## Many other articles

on sale 1st October

35p

*Copies may also be obtained direct from the Publishers, 46p including postage. Published by Data Publications Ltd., 57 Maida Vale, London*

# RADIO & ELECTRONICS CONSTRUCTOR

# THE NOR GATE

by C. F. Edwards

A swift sojourn with a neglected member of the t.t.l. family.

For some reason, NOR gates do not appear to have the popularity that is enjoyed by NAND gates and the more complex t.t.l. (transistor-transistor logic) i.c.'s which are so readily available these days. Perhaps this is because they don't fit so readily into quickly designed logic systems. In consequence, it will do no harm to briefly examine a commonly encountered

NOR gate, such as that which is incorporated in the SN7402 integrated circuit.

## SN7402 GATE

The SN7402 has the internal circuitry shown in block form in Fig. 1, and it contains four 2-input NOR

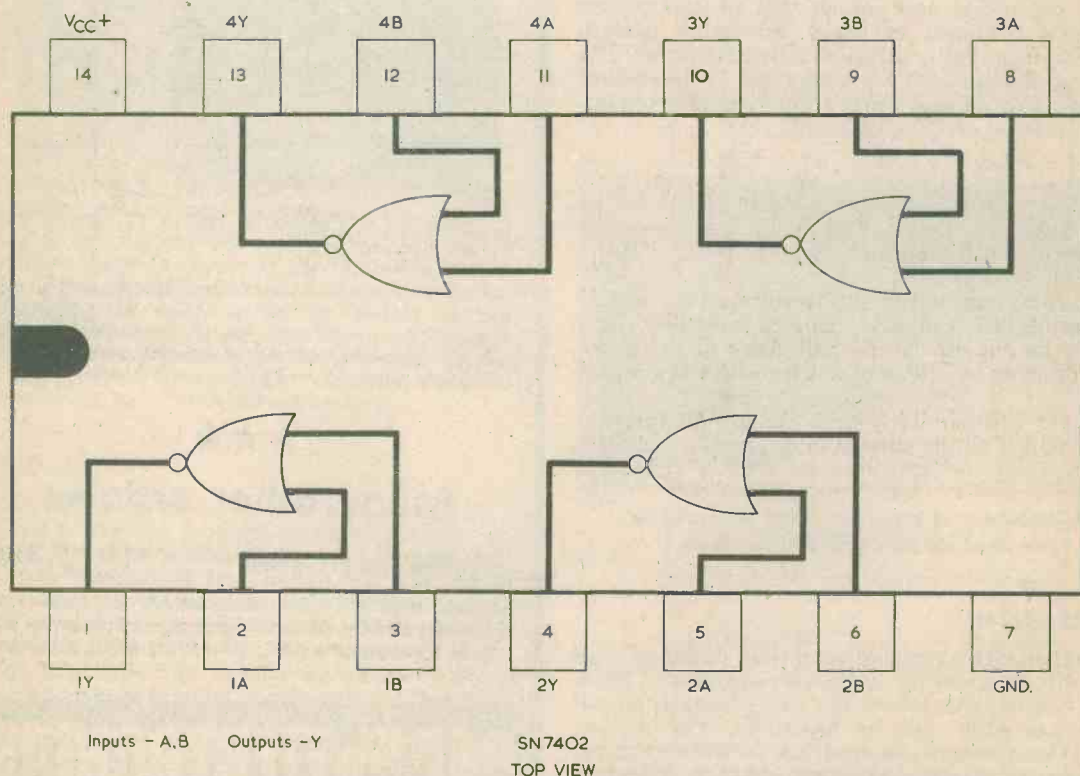


Fig. 1. Block diagram illustrating pin allocation and internal functions of the SN7402. As is common with integrated circuit pin layout diagrams, the pins point away from the reader



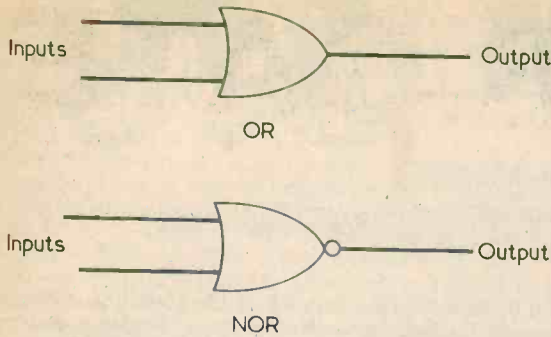


Fig. 2. Adding a circle at the output of an OR gate symbol changes it to a NOR gate symbol

gates. The gates are shown as OR gates (in which the input lines pass to a curved concave outline) having a circle at the output to indicate inversion. See Fig. 2. With t.t.l. positive logic, in which 1 is represented by a high positive voltage with respect to ground or earth and 0 by a low positive voltage, an OR gate will give an output 1 when any one or more of its inputs is raised from 0 to 1. With a NOR gate the output is inverted. The NOR gate output falls from 1 to 0 when any one or more of its inputs rises from 0 to 1.

Fig. 3 shows the truth table for a 2-input NOR gate. The input columns are headed A and B and the output column is headed Y. When both the inputs are at 0, as occurs in the first line, the output is at 1. As is shown in the second, third and fourth lines, the output falls to 0 when A is 1, when B is 1 and when both A and B are 1.

The circuit of one of the SN7402 NOR gates appears in Fig. 4. If both inputs A and B are at 0 they are only slightly positive of ground potential, and transistors TR1 and TR4 are turned hard on. Resistors R1 and R3 allow the bases of TR1 and TR4 to be about 0.6 volt positive of the emitters. The collectors of the two transistors will be just slightly positive of the emitters.

These collectors, with their low voltages, connect to the bases of TR2 and TR3, causing these two transistors to be cut off. No current flows in the base-emitter junction of TR6, and this transistor is also cut off.

TR2 and TR3 similarly draw no current through R2, whereupon all the current in this resistor flows to the base of TR5, which turns on. The voltage at its emitter and, hence, that at the gate output is high, representing 1.

A	B	Y
0	0	1
1	0	0
0	1	0
1	1	0

Fig. 3. Truth table for a 2-input NOR gate

## INPUT CHANGE

If input A goes up to 1, the emitter of TR1 is taken positive of its base and it cuts off. A current now flows through R1 and the forward biased base-collector junction of TR1 to the base of TR2, turning TR2 on. The emitter current of TR2 flows into the base-emitter junction of TR6 whereupon this transistor also turns on. At the same time, the collector of TR2 falls to a voltage which is only slightly positive of its emitter and consequently takes the base of TR5 negative. Thus the output goes low, representing 0.

Transistor TR3 takes no part in this process because it remains cut off.

If it had been input B instead of input A which changed from 0 to 1 the same process would have occurred, with TR4 and TR3 performing the same functions as TR1 and TR2 respectively. If both inputs rise to 1 the output again falls to 0, as TR2 and TR3 merely duplicate each other's function.


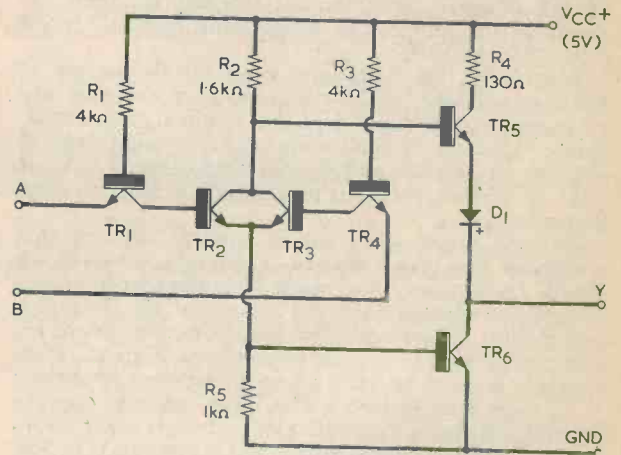


Fig. 4. The internal circuit of one of the 7402 NOR gates. The resistor values shown are nominal

The purpose of diode D1 is to ensure that TR5 is fully cut off when TR6 is hard on. Under this condition, the collector of TR6 is about 0.2 to 0.3 volt positive of its emitter. TR5 can then only pass current if the voltage at its base is about 1.2 volts positive of TR6 collector, the 1.2 volts being made up of an 0.6 volt drop in D1 and a further 0.6 volt drop in the base-emitter junction of TR5. The voltage delay given by D1 takes up the border-line case, which can occur during transition from one state to the other, where TR2 (or TR3) is not turned fully on and its emitter-collector voltage approaches some 0.8 to 0.9 volt.

# SHORT WAVE NEWS

## FOR DX LISTENERS

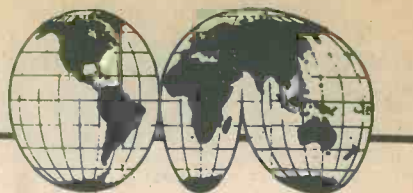

By Frank A. Baldwin

Times = GMT

Frequencies = kHz

Scanning the higher frequency bands recently we noted a few stations of interest to the S. W. Listener. The Holy Qur'an Station at Riyadh, Saudi Arabia on 15245 at 2000 signing-off with the National Anthem after readings from the Qur'an (westernised incorrectly as Koran) and station identification in Arabic. The schedule of this programme, which consists entirely of readings from the Holy Qur'an is from 1700 to 2000.

Another Arabic transmitter is that of Radio Kuwait, which was logged at 2010 on 9715 when radiating the Domestic Service on this channel, the schedule being from 1830 to 2215.

A further Arabic station, Radio Baghdad, was logged at 1803 on 9745 with a talk in Arabic in the "Voice of the Masses" programme directed to Arab expatriates in Europe, the programme schedule being from 1500 to 1930.

Also for S. W. Listeners, we noted Jerusalem at 2025 on 15100, OM with identification and announcements at the end of the English programme; Radio Grenada at 2032 with cricket commentary in English on 15105, and W1NB Red Lion, U.S.A., at 2035 on 15185, religious programme in English after identification.

For the Dxr, the item of possible interest this month is Voz del Caqueta, Colombia, at 0445 on 5035. Local music and songs then the identification with three chimes followed by chord on Hawaiian guitar both before and after identification which, incidentally, has an added echo-effect. Sign-off after trumpet fanfare at 0457 without National Anthem.

In very general terms, the Dxr tends to operate from 6000 down to 2200 kHz although often resorting to the HF bands in search of Dx stations. The SW Listener mostly uses bands from 6000 kHz upwards to 21750 or so, hence the division of schedules listed under China — see Current Schedules.

### CURRENT SCHEDULES

Readers are reminded that all short wave schedules are liable to be altered at short notice, those published here are correct at the time of writing.

#### ● U.S.S.R.

From the regional centre of Kiev, "Radio Kiev" operates an External Service in English to Europe from 1930 to 2000 on 7205, 7390 and on 11890. The service is transmitted via the technical facilities of Radio Moscow.

"Radio Vilnius" presents a programme in English on Saturdays and Sundays directed to North America and Europe from 2230 to 2300 on 9655, 9720 and on 11900. This service is also transmitted by the technical facilities of Radio Moscow.

Dxers may be interested in listening for the "Pacific Ocean Radio Station", Vladivostock which, according to the BBC Monitoring Service, operates

from 0700 to 0800 in Russian to the Pacific and North America on Sundays, Wednesdays, Fridays and on Saturdays and daily to the Far East, Middle East and South Asia on 5015, 9520, 9600, 9645, 9770, 9810, 11740, 15100, 15130, 15190, 17745, 17765, 17805 and 17835. The above transmission is relayed by Magadan on 4030, 5940 and 12240, Petropavlovsk-Kamchatka on 4485, Yuzhno-Sakhalinsk on 4050 and by Kharbarovsk on 7210. From 1430 to 1530 in Russian to the Pacific and the Middle East on Sundays, Wednesdays, Fridays and Saturdays and daily to the Far East and South Asia on 7245, 7290, 9590, 9690, 9735, 11795, 11820, 11835 and on 12010. From 1900 to 2000 in Russian to the Pacific and North America on Sundays, Wednesdays and Fridays, to the Far East and South Asia on Saturdays on 5015, 6060, 6150, 6200, 7100, 7160, 7170, 7280, 7295, 7315, 9710, 9735 and on 12010.

"Radio Tashkent" has an External Service in English for South Asia from 1200 to 1230 and from 1400 to 1430 on 11730, 11925, 15115 and on 15460.

#### ● CZECHOSLAVAKIA

"Radio Prague" radiates an External Service in English for Africa, South East Asia and Europe from 1530 to 1630 on 6055, 7345, 9605, 11990, 15110, 17840 and on 21670. To the U.K. and Eire from 1630 to 1700 on 5930 and 7345; from 1900 to 1930 on 5930, 7245 and on 7345; from 2000 to 2030 on 5930 and 7345 and from 2130 to 2200 on 5930, 7345, 9540, 11990 and 17840. "Radio Prague" also operates an "Inter-Programme" to Europe in English as follows — from 0745 to 0800, 0845 to 0900, 0945 to 1000, 1045 to 1100, 1145 to 1200 on 6055 and on 9505, transmissions consisting of either a news bulletin or a commentary or a short feature programme.

#### ● CUBA

"Radio Havana" offers an English programme directed to Europe from 2010 to 2140 on 17885.

#### ● SPAIN

"Radiotelevision Espanola", Madrid, has an External Service in which is featured an English transmission to Europe from 2130 to 2230 (not Sundays) on 6075 and on 9505.

#### ● CHINA (FOR S.W. LISTENERS)

"Radio Peking" schedules English programmes to Europe from 2030 to 2130 on 6590, 6860, 7590, 9030 and on 9880; from 2130 to 2230 on 5090, 6590, 6860, 9030 and on 9840.

The Domestic Service (First Programme) in Standard Chinese can be heard on 7935 from 1518 to

1735, 2000 to 2300; 10245 from 1100 to 1230, 2202 to 0100; 12120 from 2300 to 0800 (except Wednesdays and Fridays when 0500 to 0800); 12420 from 0829 to 1735, 2203 to 0415; 15230 from 2338 to 1130; 15550 from 0103 to 1040; 15590 from 2303 to 1515 and on 17605 from 0418 to 0828.

The Domestic Service (Second Programme) in Standard Chinese may be logged on 7770 from 1203 to 1600, 2100 to 2330; 9670 from 0700 to 1200; 9745 from 0700 to 1428; 11040 from 2333 to 1400 (on Tuesdays 0600 to 0800 only); 11505 from 2333 to 1200 (on Tuesdays 0600 to 0900 only); 12200 from 0003 to 1100 and on 15030 from 2300 to 0800.

"Radio Peking" also operates an External Service in Standard Chinese, Amoy and Hakka directed to Taiwan as follows — on 9170 and 11100 from 0830 to 1900 and from 2000 to 0610 (Sundays to 0655); on 15710 from 0830 to 1429 and from 2316 to 0610; on 15880 from 0830 to 1225 and from 0016 to 0610. This service (to Taiwan) is also relayed by the PLA Fukien Front Station from 1200 to 1215, 2100 to 2130 and from 0400 to 0415 (also see below).

#### ● CHINA (FOR THE DXER)

The Domestic Service (First Programme) in Standard Chinese on 3450 from 1233 to 1735, 2000 to 2200; 4460 from 1133 to 1735, 2000 to 2335; 4800 from 1100 to 1735, 2000 to 0100; 4905 from 2000 to 2200; 5320 from 1043 to 1735, 2000 to 0100; 5860 from 100 to 1735, 2000 to 0100 and on 6665 from 1100 to 1735 and 2000 to 0100.

The Second Programme in Standard Chinese may be located on 4250 from 1333 to 1500, 2100 to 2240; 4850 from 1403 to 1600, 2100 to 2400; 5075 from 1103 to 1600, 2100 to 2400; 5163 from 1203 to 1600, 2100 to 2400; 6345 1403 to 1600, 2100 to 2330 and on 7190 from 2243 to 1330.

To Taiwan in Standard Chinese, Amoy and Hakka ("Radio Peking") on 5125 from 1430 to 1900, 2000 to 2315 and on 6890 from 1226 to 1900 and from 2000 to 0015.

The PLA (People's Liberation Army) Fukien Front Station operates its own schedule in Standard Chinese and Amoy in addition to the relays shown above. Transmissions may be tuned in on the following channels — 2490 from 1000 to 0025; 3000 from 1201 to 2400; 3535 from 1413 to 2241; 3640 from 1415 to 2241; 4045 from 1000 to 0530; 4330 from 1000 to 0144; 5240 from 1000 to 1412, 2242 to 0530; 5265 from 1000 to 1414, 2242 to 0530; 5900 from 1000 to 1200, 0001 to 0530; 6765 from 0026 to 0530 and on 7850 from 0145 to 0530.

#### ● CHINA (FOR ALL LISTENERS)

"Radio Peking" operates an extensive round-the-clock service in Russian, a convenient time to log these would be from 2130 to 2225 on 6545, 6645, 6900, 6930, 6990, 7035, 9340, 9370, 9390, 9440 and on 9696. However, a word of warning, to avoid interference some channels may vary by as much as 10kHz. Or why not listen to a reversed tape transmission on 5220 and 8260 which may be logged from 0900 to 0955, or even a reversed tape single-sideband signal on 6550 from 1830 to 1925! (All this information according to the BBC Monitoring Service).

#### ● BANGLADESH

"Radio Bangladesh", Dacca, transmits an External Service in English to Europe from 1230 to 1300 on 15270; from 1815 to 1915 on 9550 and 11970.

#### ● PAKISTAN

"Radio Pakistan", Karachi, features a newscast in English at slow speed directed to Europe from 1100 to 1155 on 15110 and 17665 and transmissions in the World Service directed to the U.K. as follows — in Urdu from 0830 to 1100 on 15110 and on 17665; from 1915 to 2145 on 9445 and 11672 (1915 to 2045 in Urdu; 2045 to 2100 in Sylheti; 2100 to 2145 in English).

#### ● GERMANY (EAST)

"Radio Berlin International" schedules a service in English to Europe from 1830 to 1915 on 6080, 6115, 7185, 7300 and on 9730; from 2115 to 2200 on 7260.

#### ● PORTUGAL

"Radiodifusao Portuguesa", Lisbon, currently lists a broadcast in English to Europe from 2030 to 2100 on 6025 and on 9740.

#### ● CLANDESTINE

"Voice of the Malayan Revolution", in Malay "Inilah Suara Revolusi Malaya", is a pro-communist transmitter attacking the governments of both Malaysia and Singapore and is thought to be located near Changsha in Hunan Province of China. The schedule commences at 0430 and ends at 0005 in various time-periods throughout the day, probably the best chances of logging this one would be from 2200 to 2245 in Malay, 2245 to 2320 in Standard Chinese and from 2330 to 0005 in Tamil on 7305 and on 15790, at which times this month the short signal path will be mostly in darkness. Transmissions in English are made from 0930 to 1015 and from 1450 to 1530 on 11830 and on 15790, the latter period being best for U.K. reception.

"Voice of the People of Thailand", in Thai "Thi Ni Sathani Vithayu Sieng Prachachon Heang Prathet Thai", is controlled by the Communist Party of Thailand and the transmitters are thought to be located in the Kunming area of Yunnan Province in China. The transmissions are in Thai, Laotian and White Meo and may be located on 6033 and on 9423. Try for the 1530 to 1610 or the 2300 to 2340 transmissions in Thai.

"Voice of the People of Burma", in Burmese "Myama-pye Pey-thu Ah-than" in Chinese "Mien-tien Jen-min Chih Sheng Kuang-po Tien-tai", is pro-Burmese Communist Party and is thought to be located on, or very near, the Burma/China border. The frequency is 5110 and the transmissions are as follows — from 0030 to 0130 in Burmese (Tuesdays, Thursdays, Fridays, Sundays), Standard Chinese (Saturdays), Shan (Wednesdays), Jingpaw (Mondays); from 1200 to 1300 in Burmese (Tuesdays, Thursdays, Fridays, Saturdays), Standard Chinese (Saturdays), Shan (Wednesdays) and Jingpaw (Mondays). All according to the BBC Monitoring Service.


#### AROUND THE DIAL

#### ● INDIA

Air Delhi on 3365 at 1730, local music, OM in vernacular then suddenly off without National Anthem.
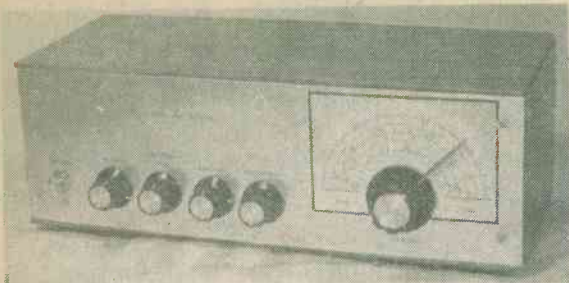
#### ● COLOMBIA

Ecos del Atrato, Quibdo, on 5020 at 0335, YL with songs in Spanish, local music under some commercial interference. The schedule of this one is reportedly from 0100 to 0515 variable — as is the frequency, it can be sometimes be logged on, or near, 5016!



# -BAND

# SHORT WAVE RADIO

Part 2 By A. P. Roberts

In the article which appeared last month the circuit and construction of this t.r.f. design were described. Notes on operation are given in this concluding article, together with details of the a.f. output stage which enables the receiver to drive a loudspeaker.

In last month's issue a description was given of the circuit and construction of this receiver with the exception of the optional a.f. output stage. The latter is covered in the present concluding article, but details will be given first of the aerial and earth required, and of receiver operation.

## AERIAL AND EARTH

The receiver is intended for use with an external long wire aerial. As it has good sensitivity, a short indoor aerial will provide reception of a large number of transmissions, including many quite distant ones. However, for best results a long outdoor aerial is required. This should preferably be about 20 metres or more long and set up as high as possible. It will be more efficient if it is positioned well clear of any buildings or similar obstructions. It should be insulated from its supports and from anything else with which it comes into physical contact.

An earth connection is not essential, and is only likely to add significantly to signal strength when the Range 3 coil is in use. An earth merely consists of a metal plate or pipe buried in moist soil, this being connected to the receiver by way of a wire which should be as short as is reasonably possible. In general, the larger the surface area of the metal plate or pipe the more efficient the earth will be.

In the receiver circuit (published last month) the aerial has a d.c. coupling to the gate of TR1, the r.f. amplifier, by way of the r.f. gain control VR1. Unless suitable precautions are taken a very long wire aerial is capable of picking up a static voltage under certain conditions, but the relatively low resistance to earth offered by VR1 should be more than adequate to discharge any static voltages which might appear when the receiver is used in the U.K. If the receiver is employed overseas with a long aerial in areas where static may be produced, an isolating plastic foil capacitor of  $0.01\mu\text{F}$  may be inserted between socket

SK1 and the slider of VR1, and a  $22\text{k}\Omega$   $\frac{1}{2}$  watt resistor connected between SK1 and SK2. Under these conditions an earth connection must be provided.

## USING THE RECEIVER

A little practice will probably need to be gained with the receiver before optimum results are obtained.

S1 is an ordinary on-off switch, The aerial connects to SK1, the earth (if used) to SK2, and the headphones to SK3. It is best to use the Range 4 coil when initially testing the receiver, as this will provide a large number of very strong signals.

Start with VR1 fully advanced, VR2 about two-thirds advanced, and VC3 at minimum capacitance. As supplied, the cores of the coils are fully screwed into the formers. The core of each coil should be unscrewed so that about 10mm. of the brass thread protrudes from the top of the former.

VC1 is used to search the band for signals, fine tuning being carried out by VC2. If a whistle of varying pitch is heard as the receiver is tuned across a station, this means that too much regeneration is being applied and VR2 should be backed off slightly. The set is most sensitive when the regeneration is adjusted to just below the point at which the circuit breaks into oscillation (causing the characteristic whistle in the headphones).

It will usually be necessary to advance the regeneration control VC3 (i.e. increase its capacitance) in order to bring the receiver to just below the threshold of oscillation. For best results VR2 should always be well advanced, with VC3 advanced as far as is necessary to produce an output of good volume. If the set oscillates even with VC3 at minimum capacitance, then VR2 is backed off a little to bring the circuit just below the point of oscillation.

S.S.B. (single sideband) and c.w. (morse) signals are the main modes of transmission in use on the amateur bands, and these can be resolved by adjusting

the circuit so that it is just beyond oscillation point and, for s.s.b., adjusting VC2 to produce an intelligible output. Strong s.s.b. signals may overload the detector, resulting in a very distorted audio signal. Advancing VC3 further, or backing off VR1, should prevent this. For c.w. signals, VC2 is adjusted for a tone of the required frequency.

Very strong a.m. signals may also overload the detector. The effect given is a high level of background noise accompanied by several stations which cannot be tuned out and which occupy an excessively large part of the band. For correct reception under these circumstances it is necessary for VR1 to be turned back slightly.

## OUTPUT STAGE

The optional a.f. output stage is added if it is required that the receiver drive a loudspeaker. The circuit of the stage is given in Fig. 7, and it provides an output of up to about 200mW into a 25Ω speaker. Speakers with impedances below 25Ω must not be used, but it is in order to employ speakers with higher impedances. However, these will cause the maximum available output power to be reduced. The speaker is installed in its own case, external to the receiver.

The circuit of Fig. 7 is fairly conventional, and comprises a common emitter Darlington pair (TR5 and TR6) driving two complementary emitter follower output transistors (TR7 and TR8). R13 provides the usual base bias for the output transistors, the bias voltage being a little lower than would normally be employed. This does not result in any noticeable crossover distortion as a high level of negative feedback is provided over the amplifier as a whole. The second a.f. amplifier in the receiver, TR4, provides quite a high level of drive, and so the output stage is called upon to offer only a very low voltage gain. The prototype uses the high gain BC109C for TR5 and TR6. Standard BC109's could alternatively be used, but there might be a slight loss of performance with these.

C13 and C14 have values which prevent problems with low frequency instability. C12 is the output d.c.


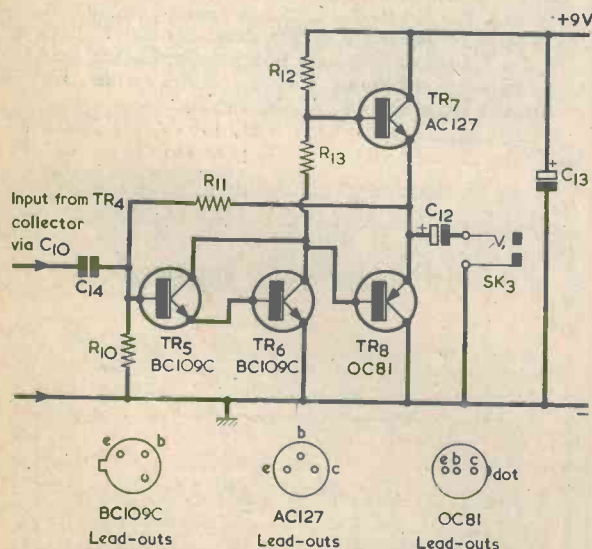


Fig. 7. The circuit of the a.f. output stage

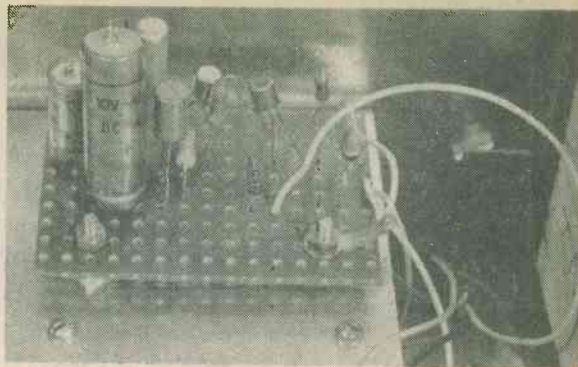

The Veroboard panel on which are assembled the a.f. output stage components

blocking capacitor. The quiescent current drawn by the output stage is about 5mA, whereupon the quiescent current taken by the complete receiver with output stage is approximately 11mA.

The parts required for the output stage appear in the accompanying Components List.

## CONSTRUCTION

The output stage components are assembled on a piece of 0.15in. matrix Veroboard having 15 by 10 holes. The layout is given in Fig. 8.

First cut out a board of the required size and drill out the two 6BA clear mounting holes. Next cut the strips at the two points indicated with crosses, using a small twist drill or the special Vero spot face cutter tool. Next fit and solder the components. Take care to ensure that the connections to TR7 and TR8 are made fairly quickly. These are germanium transistors and are more liable to be damaged by heat than are the other silicon transistors.

The output stage panel is fitted above the chassis in the position indicated in Fig. 4 (published last month). Using the panel as a template mark out, and then drill, the two 6BA clear holes required in the

## COMPONENTS

### Resistors

(All ½ watt 10%)

- R10 10kΩ
- R11 33kΩ
- R12 1.8kΩ
- R13 180Ω

### Capacitors

- C12 100μF electrolytic, 10 V. Wkg.
- C13 470μF electrolytic, 10 V. Wkg.
- C14 0.022μF type C280 (Mullard)

### Semiconductors

- TR5 BC109C
- TR6 BC109C
- TR7 AC127
- TR8 OC81

### Miscellaneous

- Veroboard, 0.15in. matrix
- Speaker, 25Ω impedance


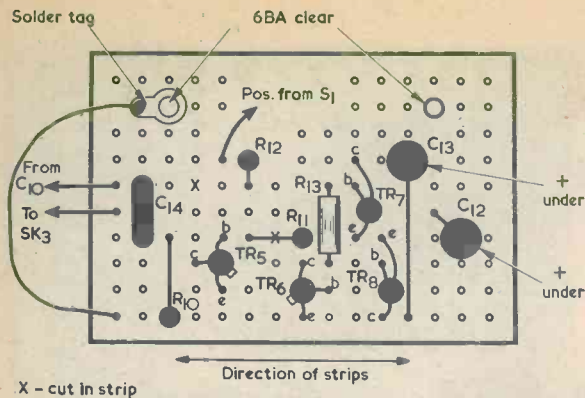


Fig. 8. Component layout and wiring on the output stage Veroboard panel. The solder tag is secured under one of the mounting nuts and provides the chassis connection for the panel

chassis. After it has been wired to the other sections of the receiver the panel is mounted, with spacing washers, in the same way as was the receiver panel.

The lead which now connects C10 of the receiver panel to SK3 is removed from SK3 and connected to C14 on the output stage panel. A lead from the output stage panel now connects to SK3, whilst a third lead connects to the tag of S1 which is remote from the battery. (If desired, the input lead to C14 may be connected direct to the collector of TR4 on the receiver panel, whereupon C10 is not required and can be removed.)

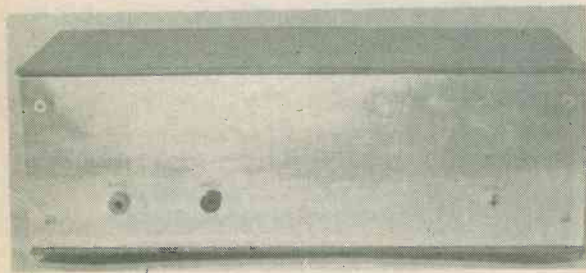It should be noted that the receiver will still feed medium to high impedance headphones with the output stage fitted. These are plugged into SK3, just as before, and a little more gain and volume will be available.




The output jack socket, together with the aerial and earth sockets, is mounted on the rear panel of the receiver
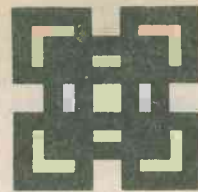
## FINAL POINTS

A finishing touch consists of adding a wire pointer to the tuning knob for VC1 by means of a suitable adhesive, and of fitting a tuning scale to the panel behind it. The tuning scale visible in the photograph of the prototype front panel is taken from "Panel Signs" Set No. 5. The controls were marked with legends indicating their functions, these being taken from "Panel Signs" Set No. 4. "Panel Signs" are available from the publishers of this journal.

If a calibrated signal generator is to hand, the scale can be marked up in terms of frequency. Should no calibration source be available the scale is marked with the position of the amateur and broadcast bands, as received.



# SOME

By R. River

1. Charlie comes into the workshop with a box containing resistors.

He says to Jack, Fred, Jim and Joe: "I have no further use for these resistors, take what you want."

Jack takes half the total number of resistors plus half a resistor.

Fred takes half the remainder plus half a resistor.

Jim takes a quarter of the remainder plus half a resistor.

Joe takes the remaining resistor.

What is the lowest number of resistors that Charlie gave away? (No resistors were broken in two.)

2. A computer is made up with integrated circuits. There are 100 different types of i.c. in the computer, the types being numbered from 1 to 100 inclusive.

The whole circuit requires 100 of type 1, 99 of type 2, and so on to 1 of type 100.

What is the total number of i.c.'s used in the computer?

3. A service manager is hard pressed and his two best repair men are off work due to illness. There are 32 colour sets which must be repaired as soon as possible.

A free-lance service engineer offers to repair the 32 sets at the following rates:  $\frac{1}{2}p$  for the first set,  $1p$  for the second set, and so on, doubling the charge for each set. The service manager agrees to this.

Why did the service manager faint when he received the repair bill?

4. In an electronic calculation a certain parameter,  $x$ , is equal to the cube root of the sum of the cubes of the other circuit quantities,  $L$ ,  $R$  and  $C$ . The relationship is shown in Fig. 1.

If  $L$  is 3,  $R$  is 4 and  $C$  is 5, what is the value of  $x$ ?

$$x = \sqrt[3]{L^3 + R^3 + C^3}$$

Fig. 1. The equation encountered in problem 4

# ELECTRONIC PUZZLES

Here are some problems which merit a period away from the work bench. The puzzles are mainly of a mathematical nature and include an acknowledged oldie together with one or two minor stinkers. Solutions are given on page 115.

5. You have seven precision resistors with values respectively of  $1\Omega$ ,  $2\Omega$ ,  $4\Omega$ ,  $8\Omega$ ,  $16\Omega$ ,  $32\Omega$  and  $64\Omega$ . How many values of resistance in  $1\Omega$  steps between  $1\Omega$  and  $100\Omega$  can be produced by single resistors or series combinations of two or more of these resistors?

6. The first line in Fig. 2 illustrates that  $\frac{1}{4}\text{MHz}$  is equal to  $250,000\text{Hz}$ . The square roots must also be equal, as shown in the second line, but this leads to the obviously untrue third line. What has gone wrong?

$$\frac{1}{4}\text{MHz} = 250,000\text{Hz}$$

$$\sqrt{\frac{1}{4}\text{MHz}} = \sqrt{250,000\text{Hz}}$$

$$\frac{1}{2}\text{MHz} = 500\text{Hz}$$

Fig. 2. The first equation is obviously true, as also is the second equation which follows from it. But we then arrive at the very peculiar relationship which appears on the third line

7. Fig. 3 illustrates a venerable puzzle which continues, nevertheless, to have traumatic effects amongst those who have not yet encountered it. The cube is made up of 12 resistors, and each resistor has a value of  $1\Omega$ . What is the resistance between the opposite corners X and Y?

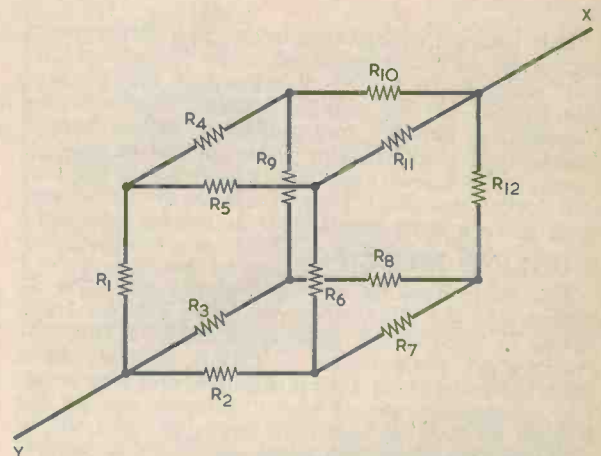


Fig. 3. A cube is made up of equal value resistors

## Constructor's Crossword Solution

### Across

1, Switches. 5, Esters. 9, Radiance. 10, Getter. 12, Atomic. 13, Anode Ray. 15, Electroplate. 18, Radio Compass. 23, Negatron. 24, Alkali. 26, Flange. 27, Tracking. 28, Rohans. 29, Open Gate.

### Down

1, Serial. 2, Indoor. 3, Coaxial. 4, Each. 6, Speed-Up. 7, External. 8, Spray Jet. 11, Entropy. 14, Echo Box. 16, Transfer. 17, Odograph. 19, Octagon. 20, Silicon. 21, Lamina. 22, Single. 25, Trip.

8. A resistor and a capacitor cost 11p. The capacitor costs 10p more than the resistor.

How much does the resistor cost?

9. A serviceman in a radio controlled van is out on a call. After travelling at 15 m.p.h. he is 1 mile from base when he is redirected to go to the home of the service manager's mother-in-law, which is 2 miles from base in the same direction.

How fast must he drive the extra 1 mile to average 30 m.p.h. for the total 2 mile trip?

For solutions see page 115.

# TONE - CANCELLING CAPACITANCE BRIDGE

by  
W. R. Jenkins

A novel design in which the capacitance to be measured is balanced against another of equal value.

This unusual capacitance bridge is a development from a design which appeared in the "Suggested Circuit" series by G. A. French in the July 1974 issue of this journal. In the original article, "Multivibrator Capacitance Bridge", two opposing outputs from a symmetrical multivibrator were applied to the unknown and a known capacitance in series. In the present design, two amplifying transistors are added and these allow a more identifiable null to be achieved.

## WORKING PRINCIPLE

The basic working principle of the circuit is illustrated in Fig. 1(a), where TR1 and TR2 are transistors in a 50:50 a.f. multivibrator. At a first approximation, the collector of TR1 is always positive when the collector of TR2 is negative, and vice versa. The consequent out of phase collector signals are applied to CX, the unknown capacitor, and VC, a calibrated capacitor. When the values of CX and VC are equal, there should theoretically be zero signal at the junction of the two capacitors. A pair of high resistance headphones is connected between this junction and the lower supply rail, whereupon VC can be adjusted for a null signal in the phones and the value of CX read from the VC calibration.

In practice, the signals at the collectors of TR1 and TR2 are not always out of phase with each other. For instance, at the period in the multivibrator cycle when TR1 turns off its collector potential does not rise immediately to that of the upper supply rail. Instead, it rises relatively slowly as the cross-coupling capacitor connected to the collector charges. Similarly, the collector potential of TR2 rises relatively slowly after the instant in the cycle when this transistor turns off. In consequence, the signal voltages applied to CX and VC are not exactly opposite to each other and the null given when these two capacitances are equal consists of a change in the character of the tone in the headphones rather than a marked diminution of its amplitude.


The null given by the arrangement of Fig. 1(a) is still quite detectable, but an improvement can be obtained by adding two transistors in the manner shown in Fig. 1(b). Here, TR3 and TR4 have their base-emitter junctions inserted in the emitter circuits of TR1 and TR2. Since these base-emitter junctions are connected to be forward biased they have no effect on multivibrator operation apart from a slight lowering in frequency. At the same time, the circuit allows TR3 to turn on and off at the same times as does TR1, and allows TR4 to turn off at the same times as does TR3. There are no cross-coupling capacitors to the collectors of TR3 and TR4 and so the collector potentials of these two transistors rise almost immediately to that of the upper supply rail after the instants of changeover which turn off TR1 or TR2. As a result, the signals obtained at the collectors of TR3 and TR4 are more truly opposite to each other throughout the multivibrator cycle than are those at the collectors of TR1 and TR2.

In Fig. 1(b) the collectors of TR3 and TR4 are applied to CX and VC, and VC is once again adjusted for a null in the headphones. Even with this circuit there is not a complete cancellation of the multivibrator tone at balance, but the reduction in amplitude and change in tone character are significantly more evident than occurs with the circuit of Fig. 1(a).


There are several advantages in the circuit of Fig. 1(b) when compared with a more conventional type of bridge of simple design. The first of these is that one of the headphone leads is at chassis potential, with the result that bridge readings are not affected by changing capacitances between the headphone leads and earth. Second, the collector resistors of TR3 and TR4 can be given low values, whereupon one terminal of CX and one terminal of VC connect to low impedance points in the circuit.

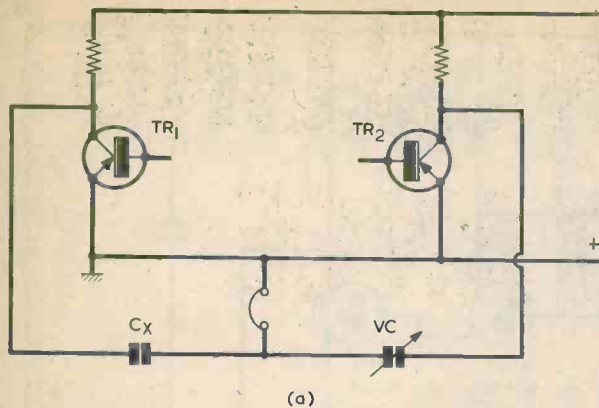There is one disadvantage in the circuit, this being that the maximum capacitance which can be





(a)

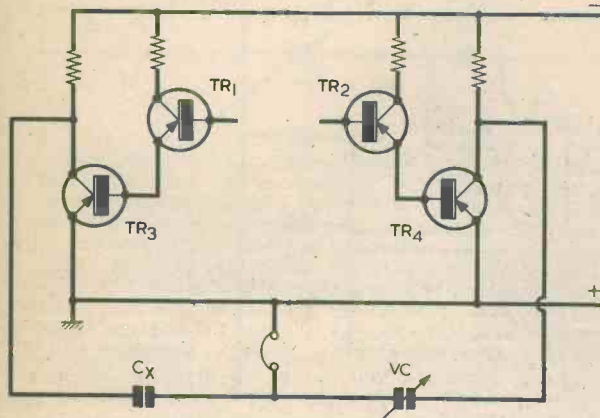

(b)

Fig. 1(a). Basic circuit illustrating the functioning of the capacitance bridge  
 (b). An improvement in performance is given by adding the transistors TR3 and TR4

measured is limited to the maximum capacitance which can be given to VC, whilst the minimum capacitance is limited by circuit strays and the reactance at a.f. of the two capacitances. In the author's circuit the total range of measurements is from 20pF to 2,300pF. In mitigation, it can be stated that this range takes in very many of the capacitances that need to be measured in the amateur workshop, including variable capacitors and small silvered mica and ceramic capacitors whose markings have become smudged or erased.

### FULL CIRCUIT

The full circuit of the bridge appears in Fig. 2. Here, TR1 and TR2 appear in a standard multivibrator circuit which runs at approximately 1.3kHz. A pre-set potentiometer is inserted in the base circuit of TR2 to enable the multivibrator to be set up for 50:50 operation. TR3 and TR4 couple to TR1 and TR2 in the same manner as in Fig. 1(b), and a second pre-set potentiometer in the collector circuit of TR3 enables the outputs of TR3 and TR4 to be balanced.

## COMPONENTS

### Resistors

(All fixed values  $\frac{1}{4}$  watt 5%)

- R1 470 $\Omega$
- R2 2k $\Omega$
- R3 15k $\Omega$
- R4 10k $\Omega$
- R5 2k $\Omega$
- R6 1k $\Omega$
- R7 100 $\Omega$
- VR1 1k $\Omega$  pre-set potentiometer, skeleton
- VR2 10k $\Omega$  pre-set potentiometer, skeleton
- VR3 25k $\Omega$  potentiometer, log

### Capacitors

- C1 0.047 $\mu$ F plastic foil
- C2 0.047 $\mu$ F plastic foil
- C3 50pF silvered mica or polystyrene
- C4 1,000pF silvered mica or polystyrene
- C5 100 $\mu$ F electrolytic, 10 V. Wkg.
- VC1(a)(b)(c) 500+500+500pF variable, 3-gang (see text)

### Transistors

- TR1 ACY19
- TR2 ACY19
- TR3 BC214L
- TR4 BC214L

### Switches

- S1 3-pole 4-way, rotary
- S2 s.p.s.t., toggle

### Battery

- B1 9 volt battery

### Miscellaneous

- Headphones, 4,000 $\Omega$
- 2 insulated terminals
- 2 control knobs.

VC of Fig. 1(b) can consist of any variable capacitance offering the required range, and constructors can use whatever components they may have on hand here. The metal frame of the variable capacitor should be connected to the low impedance output at TR4 collector, and should also, of course, be insulated from chassis. The author employed a 3-gang capacitor with a nominal value of 500pF in each section in conjunction with the range switching circuit shown. When range switch S1 is in position 1, it selects C3 in series with one section of the capacitor. In position 2, the single section of the capacitor is switched into circuit on its own. At position 3 all the sections of the capacitor are in circuit in parallel, and in position 4 C4 is added to this parallel combination. If this circuit is employed, care is needed in the wiring to keep stray capacitances low, and it helps if fairly thin connecting wire is used.

A testmeter having a resistance on its voltage ranges of 10,000 ohms per volt or more is required for setting up the multivibrator. The meter is switched to a low d.c. volts range (say 0-10 volts) and is connected across the collectors of TR1 and TR2. The meter may

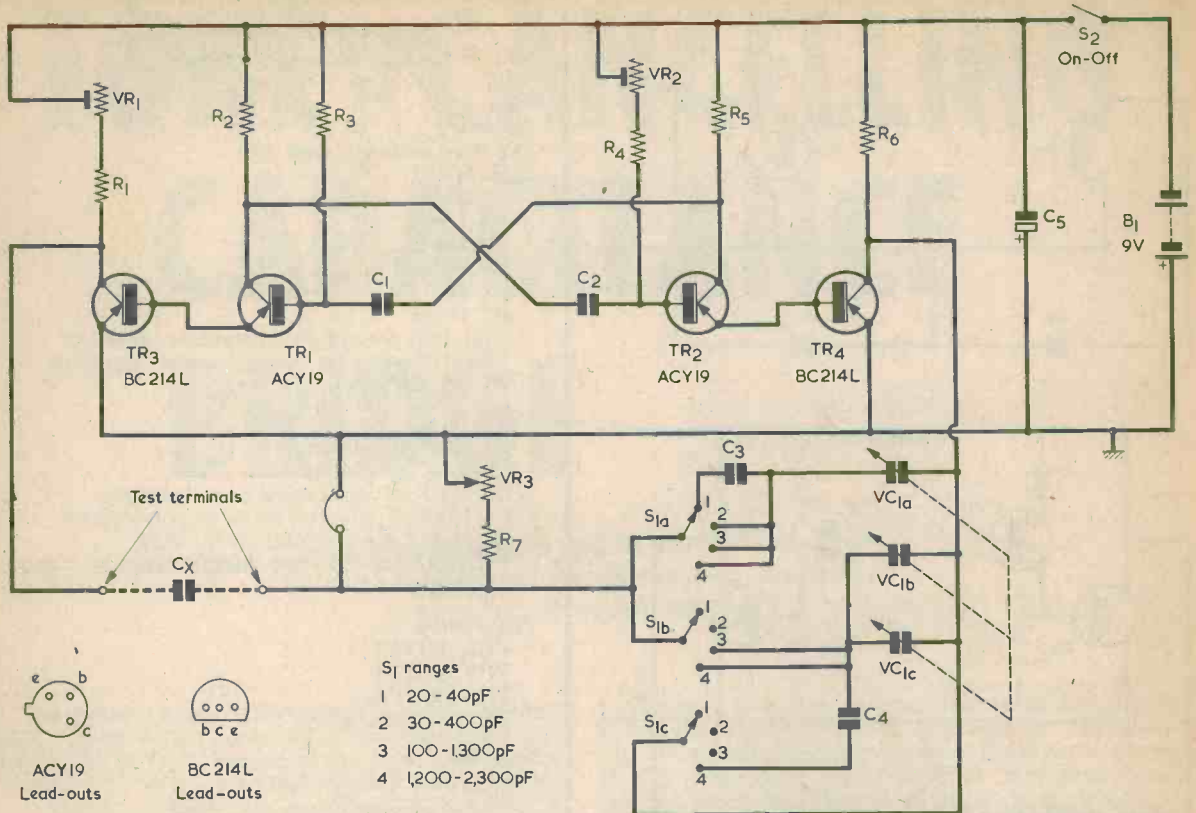


Fig. 2. Complete circuit of the tone-cancelling capacitance bridge. Alternative means of providing the VC arm may be employed if desired

give a forward or a reverse reading, and VR2 is then adjusted for a zero reading. This reading indicates that the transistors are turned on for equal periods during the cycle. The voltmeter is then removed and is connected across the collectors of TR3 and TR4. This time, VR1 is adjusted for a zero reading, and it will probably be necessary to finally switch the meter to a lower volts range than was needed with TR1 and TR2.

VR3 is included to vary the amplitude of the tone heard in the headphones. When measuring high values of capacitance it may be adjusted to reduce the volume level of the tone. With low values of capacitance it is adjusted to insert maximum

resistance into circuit. It is wired such that the resistance it inserts increases as its spindle is turned clockwise. The headphones are standard magnetic types with a resistance of 2,000Ω in each phone.

The null given when the variable capacitor is adjusted is quite noticeable. The amplitude of the tone in the headphones decreases and changes from a "full" sound to one having a thin and reedy character. There is also the impression of a rise in pitch.

The bridge is calibrated with the aid of known values of capacitance connected to the test terminals. The current drawn from the 9 volt battery is 14mA.

## BACK NUMBERS

For the benefit of new readers we would draw attention to our back number service.

We retain past issues for a period of two years and we can, occasionally, supply copies more than two years old. The cost is the cover price stated on the issue, plus 11p postage.

Before undertaking any constructional project described in a back issue, it must be borne in mind that components readily available at the time of publication may no longer be so.

We regret that we are unable to supply photo copies of articles where an issue is not available. Libraries and members of local radio clubs can often be very helpful where an issue is not available for sale.

# Radio Topics

## By Recorder



I live and learn.

Until recently I had assumed in my innocence that, for an oscillator to work, it required positive feedback in phase from an amplifier output back to its input. But I find you can also have a perfectly respectable oscillator in which the amplifier output is out of phase with the input. And how is this magic wrought?

By hysteresis.

### SCHMITT TRIGGER

If you couple the output of a t.t.l. Schmitt trigger back to its input via resistor, and add a capacitor between the input and ground, the set-up will oscillate away quite happily. A suitable Schmitt trigger is one of the two triggers in the SN7413. This actually has four inputs going to an AND gate so in practice the four inputs are joined together to form a single input.

When this input is at ground level the Schmitt trigger output is high. If the input is taken slowly positive and reaches a voltage of typically 1.7 volts above ground the output suddenly goes negative and stays negative for all further positive excursions of the input. If now we start to take the input negative towards ground the output suddenly goes high again when the input reaches a level of, typically, 0.9 volt. Thus, the Schmitt trigger exhibits a hysteresis effect which, with the SN7413, occupies a range of approximately 0.8 volt.

It is now fairly easy to see how oscillation may be obtained. Let's say that at an instant in the oscillatory cycle the input has been negative-going, has just reached 0.9 volt, and the output has in consequence just gone high. The output at once forces the input to go high via the resistor coupling them together, but the rise of voltage at the input is delayed by the capacitor between the input and ground. After a

period it reaches 1.7 volts above ground whereupon the output at once goes low. The output draws the input low too, but there is again the delay resulting from the capacitor between the input and ground. When the input does reach 0.9 volt the output goes high once more; which is where we came in.

Neat, isn't it?

The resistor coupling the output back to the input needs a fairly low value because of the relatively heavy current needed to hold a t.t.l. input down, and a suitable value is of the order of 360Ω. The capacitor between input and ground can be 0.1μF to 1μF.

The time constant of 360Ω and 1μF is 360 microseconds, and the capacitor is swinging between 1.7 and 0.9 volts. A very rough guess at the time taken to drop from 1.7 to 0.9 volts would be about 300 microseconds, arguing a frequency, with 360Ω and 1μF, of around 1.6kHz. But the situation is complicated by the current drawn by the Schmitt trigger input: when it is taken negative and so the actual frequency of oscillation may vary quite a bit from any easily calculated figure.

### STEERING BY A STAR

Marconi Space and Defence Systems Limited, one of the GEC-Marconi Electronics Companies, continue to report 100% success for their star-pointing systems which are incorporated in upper-atmosphere research rockets. The star-pointing system complements the Marconi sun-pointing control system which has already made more than 50 successful flights.

The fifth Skylark research rocket carrying the star-pointing equipment was successfully launched from Woomera Rocket Range recently. The 330kg. (720lb.) payload was carried to a peak altitude of 250km. (154 miles).

During the flight the rocket acquired the target star Zeta Taurus (visual magnitude 3.0) and remained "locked on" to this star with an accuracy of six arcseconds for a period of four minutes.

The mission objective of this, a Leicester University experiment, was to measure the abundance of oxygen, helium and neon in the vicinity of the Crab Nebula by observing the absorption of low energy X-rays.

### LINE OUTPUT SNAG

Coming down to earth with rather a bump I must next recount the sad plight of an acquaintance who has to switch his television set off every time he goes to the toilet.

He lives on his own and has used for many years a beat-up old valve monochrome television receiver which, he insists, he is going to hang on to until it finally breaks down. Which may occur in the fairly near future, as it has now developed an intermittent fault in the line output stage.

What happens is that every now and again the picture suddenly disappears and a quite frightening sizzling noise becomes audible from the inside of the set. My acquaintance switches it off and then leaves it for about five minutes before turning it on again. Amazingly enough, the set then resumes normal working and continues to do so until the fault appears once more. The shortest time between the occurrence of the fault has been two days and the longest time a fortnight.

As he complains, my acquaintance is scared of leaving the TV set for any period of time whilst it is switched on in case the fault comes on whilst he is away, so that he would return to a receiver with a completely burnt-out line output stage. I must say that this is the hardest hard-luck TV story I've heard yet.

## DIGITAL MULTIMETER

I also have photographs this month of the recently introduced Hewlett-Packard fully autoranging digital multimeter type 3476A, which is available from Hewlett-Packard Limited, King Street Lane, Winnersh, Wokingham, Berkshire. Claimed to offer comprehensive facilities at very competitive cost, this multimeter is a.c. mains operated and has dimensions of 2.3in. high, 6.6in. wide and 8.1in. deep. There is also a model 3476B which can be powered by the mains or by its own rechargeable nickel cadmium batteries.

Readout is by way of a  $3\frac{1}{2}$  digit l.e.d., and voltages can be measured from 0.0001 to 1,000 volts d.c., and 0.0003 to 700 volts a.c. Resistance measurements are from  $1\Omega$  to  $1M\Omega$ . D.C. current range is 0.0001 to 1.1 amp, and a.c. current range is 0.0003 to 1.1 amp. Autozero and autopolarity are built in.

The manufacturers state that the low price of the digital multimeter has been achieved through a major technological advance. Development of fine-line tantalum nitride technology has eliminated the use of more costly discrete precision resistors. The tantalum nitride resistors are contained in a small pack and are matched to 0.02% by means of a laser-trim process.

## FIRE SURPRISE


And finally a rather disturbing little incident which happened to me personally and which has to do with quite simple electricity.

In my workroom I have a standard 2-bar portable electric fire, each bar consisting of a ceramic rod having a spiral groove in which is wound the element resistance wire. Two terminals at the ends enable the bars to be quickly fitted or removed, as required.

I switched on one bar of this fire one chilly morning and noticed several minutes later that there was a bright, almost white-hot, glow at one point of the element. Thinking that a spot of dust had fallen onto the wire I dismissed the effect from my mind and started work. When I turned round several minutes later the excessive glow was still there.

This was beginning to become interesting. It was evident that there must be a thin point in the wire at the bright glow, and that the element was on the verge of expiry. I assumed that the wire would soon melt at the weak spot whereupon, since an alternating current breaks its own arc, the element would simply become open-circuit and that would be that. But I was mistaken.

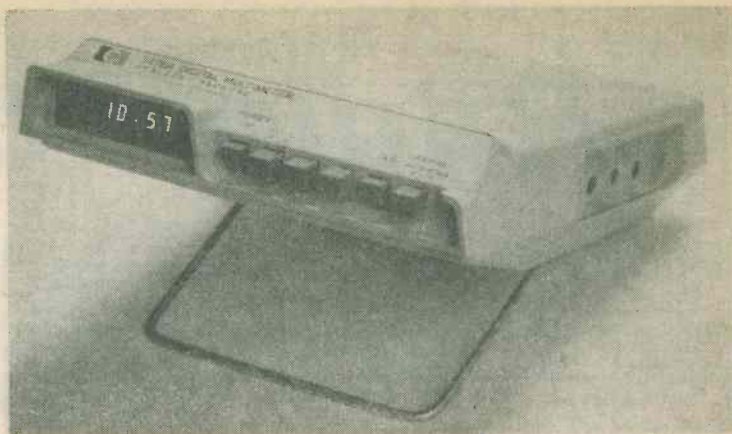Shortly afterwards the glow increased in intensity and size. What was more, the ceramic itself now seemed to be cooking up. And then not only did the glow get even wider and brighter but the bar started throwing out sparks onto the floor, crackling



*The Hewlett-Packard digital multimeter type 3476A. This features autoranging, autozero and autopolarity selection.*



*Sorting out the voltages in a complex experimental breadboard layout with the aid of the Hewlett-Packard digital multimeter*

away like a miniature fireworks display. Enough is enough and I switched off. When I examined the offending rod later I found that the ceramic had actually melted and re-set at the area of the glow.

Now, this was completely unexpected. That element had a fair amount of grime on its surface and so I presume that this broke down to some form of conductive material when the wire finally became open-circuit. Molten glass, believe it or not, passes electricity so, alternatively, could the

ceramic material become conductive if it was hot enough? There was no change in the brightness of the glow from the rest of the bar so about the same current was still flowing after the wire parted. The element, incidentally, registered as an open-circuit when I checked it with a testmeter after it had cooled.

Quite a mystery. But, at any event, that little episode is going to make me think very carefully before I leave a fire of this nature unattended anywhere in the future. ■

# SOME ELECTRONIC PUZZLES

Solutions to the puzzles set on page 108.

1. 27 resistors.
2. 5,050 integrated circuits.
3. The repair bill was for:  
£21,474,836.47½ plus VAT.

Disregarding the initial ½p, the series 1, 2, 4p ... has 31 terms and its sum is equal to 2 to the 31st power minus 1. (Try this with shorter series: the sum of 1 and 2 is 2 squared minus 1, the sum of 1, 2 and 4 is 2 cubed minus 1.)

2 to the 31st power is:  
2,147,483,648.

Subtracting 1, dividing by 100 to produce pounds and pence, and then adding the initial ½p gives the solution above.

4. 6.  
5. All the values can be made up, and also values up to 127Ω. This is a use of the binary system.

6. The error is that the square root of a MHz should also be taken. The square root of a MHz is a kHz, so that the third line should read:  
½kHz = 500Hz.

7. The resistance between X and Y is five-sixths of an ohm.

The easiest way of solving the problem consists of first assuming that a voltage is applied across X and Y and then finding points of equal potential in the cube. The cube can be redrawn in the manner illustrated in Fig. 4, whereupon inspection shows that points A, B and C are at the same potential. Since no current can flow between points having equal potential, A, B and C may be joined together without altering the overall resistance of the cube. Points D, E and F are similarly at the same potential and can also be joined. The cube may then be redrawn as in Fig. 5. (The circular presentation of Fig. 4 was first suggested to us by D. Graves, and appeared on page 640 of our April 1964 issue. — Ed.)

8. The resistor costs ½p.

9. It is impossible for the serviceman to average 30 m.p.h. for the 2 mile trip. To do this he would have to cover the 2 miles in 4 minutes, but he has already spent 4 minutes on the first mile.


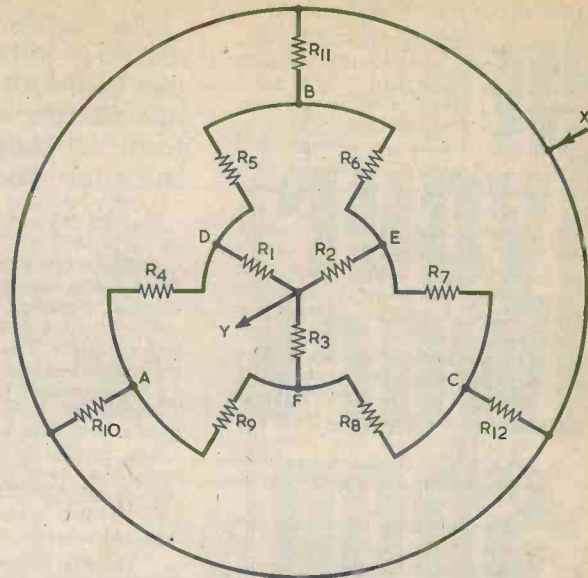


Fig. 4. The cube of resistors can be redrawn in the manner shown here

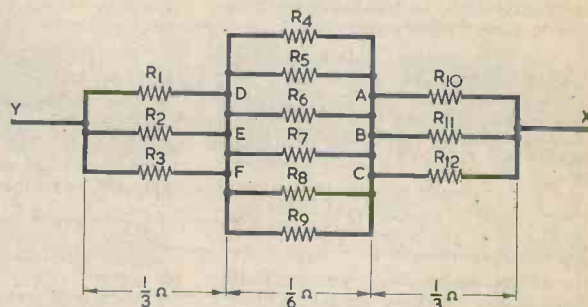

$$\text{Resistance (X-Y)} = \frac{1}{3} + \frac{1}{6} + \frac{1}{3} = \frac{5}{6} \Omega$$

Fig. 5. If equal potential points in the cube are joined together it becomes possible to arrive at this simplification



## AUDIO AMPLIFIERS

Edited by J. R. Davies

16 Transistor and Valve Designs for the Home Constructor

124 pages

Amplifiers for Tuner Units, Record Players, Tape Recorders, Public Address, etc., etc.


Includes contributions by such well-known authors as

A. S. Carpenter, A. Kinloch, E. Govier,  
G. A. French, F. G. Rayer, P. F. Bretherick,  
K. Jones, D. Aldous, R. Murray-Shelley,  
C. Swires, G. A. Stevens and V. E. Holley.

**PRICE**  
**53p**  
p&p 14p

DATA PUBLICATIONS LTD, 57 MAIDA VALE, LONDON W9 1SN.

# In your work-shop



"Cardboard boxes," complained Smithy. "Nothing else but cardboard boxes!"

"Dash it all," protested Dick. "I've got to keep things somewhere."

"Normal people," stated Smithy, "keep things in cupboards and drawers. But not you. You keep things in cardboard boxes. It baffles me how you can get your legs under your bench even."

The Serviceman glared at the heterogeneous collection of dusty cardboard boxes ranged on the floor underneath his assistant's bench.

"What you must do," went on Smithy accusingly, "is wait until you find a cardboard box that takes your fancy and then use it for hoarding junk. A fetish for cardboard boxes, that's what you've got."

"Hey," said Dick indignantly. "There's no call for remarks like that."

"Well," responded Smithy, "we can't have all these boxes of yours cluttering up the Workshop. Let's see what's in this one."

## CARDBOARD BOXES

Smithy pulled out the box nearest him, placed it on Dick's bench and opened it up.

"Blimey," he remarked, surprised. "This is full of nothing else but control knobs. I don't think I've ever seen so many different types of control knob all together in my life."

"I never," stated Dick proudly, "throw away a control knob. Whenever we dispose of a set I always keep the knobs. You never know when you'll need one with a particular style and colour."

As Smithy says, there must be many old valve radios stored in lofts and attics which can be brought back into use again after a few simple repairs. This month, Dick and Smithy stumble on a medium and long wave radio from the early 1950's, and Smithy demonstrates some of the basic faults liable to occur in the sets of this era.

But Smithy's curiosity was now fully aroused and he ignored his assistant's comments as he pulled out more of the boxes and placed them on Dick's bench. These contained, respectively, a quantity of loose mains transformer laminations, resistors with short leads, a selection of 465kHz i.f. transformers, a further quantity of transformer laminations, capacitors with short leads, four small reels of 36 s.w.g. enamelled wire, several loose coils of unused electric fire element wire, a large package of six inch nails, and a third quantity of transformer laminations.

"Ye gods," snorted Smithy, surveying the boxes which now covered most of Dick's bench. "What d'you want all these laminations for?"

"I never know if I might not want to make up a special transformer for myself some day," responded Dick quickly. "Have you ever tried to buy laminations?"

"Well, what's the electric fire element wire for?"

"For making up very low values of resistance," replied Dick. "You can easily make up temporary resistors with the wire if you want values below about half an ohm or so."

"I suppose," conceded Smithy, "that you have a point there. There's only two more boxes left now. What's in them?"

"Search me," said Dick. "They've been here as long as I can remember."

Smithy reached down, pulled out the box which was further from the wall and placed it on Dick's bench. He opened it, gave a startled gasp and commenced searching feverishly through its contents.

"There just seems to be a lot of old mags in it," commented Dick dispassionately.

"Old mags?" repeated Smithy incredulously. "Do you know that all the issues of *The Radio Constructor* from January 1955 to December 1956 are in here? I thought I'd lost them for ever."

He looked happily at the magazines. "This makes my collection complete all the way back to 1950 now. Blow me, that's the best find I've had for ages. This brings us to the last box of all. I wonder what we'll find in that."

Purposefully, Smithy reached down, picked up the remaining box and placed it on the bench. He wiped the dust from its surface with a rag then opened it up. His face took on a puzzled expression as he peered inside and drew out an object which he plac-

ed on the surface of Dick's bench.

It was a medium and long wave valve radio in a neat and relatively small two-tone plastic case. Its mains lead, terminated in an old-fashioned 2-pin 2-amp mains plug, was held in a neat bundle with an elastic band.

## VALVE RADIO

"Stap me," breathed Dick. "Where on earth did that come from?"

"What is more to the point," stated Smithy, "is how long has it been there?"

"Well," said Dick. "I've never ever looked inside either of those last two boxes. When did you lose the 1955 and 1956 issues of *The Radio Constructor*?"

"I don't even remember keeping them," replied Smithy, scratching his head. "They must have found their way into that box after I'd read them, and they've been there ever since."

"That means," said Dick slowly, "that the mags have been down there for around twenty years. And if the box with the radio in it was behind the one with the mags in . . ."

"That means," broke in Smithy, "that the radio has been there for at least as long as the magazines have been."

Dick gazed at the set with reluctant respect.

"If that set originally came in for a repair," he remarked, "it's certainly had to wait a long time for it! What do we do with it now Smithy, chuck it out?"

"Certainly not," retorted Smithy. "If it's got a fault, we'll fix it. The cabinet has got a few scratches on it so it wasn't brand-new when it came in. Funnily enough, this situation is much the same as occurs in quite a few households. I bet there are no end of old mains radios stored away in lofts and attics which require only a little work to get them going again. The trouble these days is that everybody is so preoccupied with solid state equipment that they've completely forgotten that you can still get an excellent performance from a valve radio. Hello, what's this?"

Smithy looked into the cardboard box and took out a folded piece of paper.

"Stone me," he remarked. "The service sheet for the radio was put in the box with it. Well, that makes our job a lot easier. There's a bit more space on



## Your Local Supplier

LONDON

### THE MODERN BOOK CO.

Largest selection of English & American radio and technical books in the country.

19-21 PRAED STREET,  
LONDON, W2 1NP  
Tel: 01-723 4185/2926

HAMPSHIRE

### BOURNEMOUTH

LARGEST HI-FI AND  
RADIO COMPONENT  
STORE IN THE SOUTH

FORRESTERS NATIONAL  
RADIO SUPPLIES LTD.

70-72 Holdenhurst Road

Bournemouth

Telephone 25232

Closed all day Wednesday

SUSSEX

### JEFFRIES

For  
Hi-Fi Equipment  
Tape Recorders  
Television  
Transistor Radios

6A Albert Parade  
Victoria Drive,  
EASTBOURNE SUSSEX

EIRE

### PEATS for PARTS ELECTRONIC COMPONENTS RADIO & TELEVISION

For the convenience of Irish enthusiasts we supply  
Radio & Electronics  
Constructor  
Data Books and  
Panel Signs Transfers  
Also a postal service

Wm. B. PEAT & Co. Ltd.  
25/26 PARNELL STREET  
DUBLIN 1

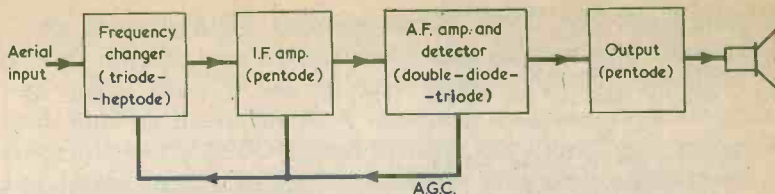


Fig. 2. An alternative signal stage line-up encountered in a.m. radios.

And, of course, the bias increases considerably when a signal is being received because of the a.g.c. action. So far as the triode section of the UCL82 is concerned you'll see that the grid resistor has the high value of 10MΩ. This allows an effect which was described as 'grid current bias' to take place and the triode works quite satisfactorily under these conditions. "Is the valve line-up here a standard one?"

"Oh yes," stated Smithy. "About the only variation you'll find is when the output pentode is a single valve. You then have a separate triode a.f. voltage amplifier, and this will have the two signal diodes with it to make it a double-diode-triode. The i.f. amplifier is a simple pentode on its own without diodes." (Fig. 2.)

#### STARTING TESTS

"Shall I," asked Dick, "connect this set up to the mains and switch it on?"

"Not yet," replied Smithy. "I want to check first that it hasn't got an h.t. short down to chassis. That may have been what was wrong with the set in the first place, but there is also a very slight possibility that the h.t. electrolytics have gone low resistance over the last twenty years. Better to be safe than sorry."

Dick applied himself to the receiver and was soon able to draw the chassis from its case.

"Blimey," he remarked, "there isn't even a printed circuit. All the parts are wired up on a chassis with tagstrips."

"That seems reasonable enough," commented Smithy. "Many receiver manufacturers hadn't changed over to printed circuits in the earlier 1950's. Okay, Dick, check the resistance between the positive tag of the reservoir capacitor and chassis."

Dick applied his test prods and watched the meter needle. This moved fairly swiftly to a reading of around 20kΩ. (Fig. 3.)

"Not so good," remarked Smithy. "If the h.t. electrolytics were in good condition, that meter needle would have swung over a lot more slowly. Still, there isn't by any means a dead short between the h.t. line and chassis so it should be safe to apply the mains. Before we do that, however, fit the knobs back on the control spindles. This will make it easier to operate them. And also, of course, don't forget that the chassis is connected to one side of the mains and that you can get

a dangerous shock from it if you aren't careful."

"Hey Smithy," grumbled Dick, "take it easy. I have been fixing live-chassis TV's for quite a time now, you know."

"Sorry," chuckled Smithy. "This radio is taking me back over the years so much that I got carried away for the moment! I should set your testmeter to a high voltage range now and connect it between chassis and the positive tag of the reservoir electrolytic again. This will enable us to monitor the h.t. voltage."

Dick connected the receiver to the mains. He then adjusted the range switch of the testmeter, clipped its negative lead to the receiver chassis and applied its positive prod to the reservoir capacitor tag. He put his hand out towards the combined volume control and switch.

"Don't have your face too close to the chassis for the first few minutes," stated Smithy. "After twenty years out of service there is just a very slight risk

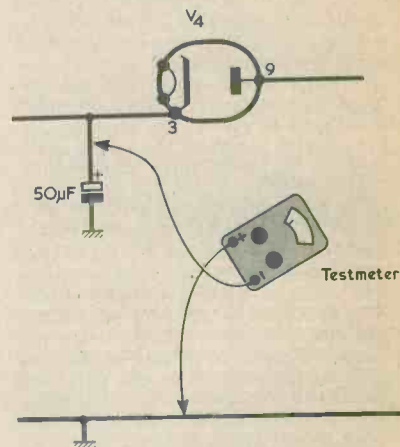


Fig. 3. Checking for h.t. short-circuits to chassis at the reservoir capacitor by means of a testmeter switched to read ohms. With normal testmeters, connecting the test leads in the manner shown causes the testmeter battery to have the same polarity as the electrolytic capacitor.



of the reservoir capacitor going pop when the rectified voltage gets to it. I know I'm a bit of a fuddy-duddy so far as things like this are concerned but I believe in safety first. Okay, switch on now."

There was a click as Dick turned on the switch. The dial lamp lit up weakly, then rose to full brightness as the resistance of the series thermistor in the heater chain dropped. The valve heaters began to glow cheerfully.

Dick glanced at the meter. "Hey, Smithy," he called out, "there's no voltage across the electrolytic. The rectifier must be duffy."

"Give it a chance," retorted Smithy. "It's got an indirectly heated cathode and that cathode has got to warm up just the same as all the other cathodes. Hello, the meter needle's starting to move now."

Slowly, the meter needle rose to indicate a reading of 190 volts. It stayed at this level for a short moment then continued to a steady reading of 210 volts. Dick removed the positive test prod.

"That's beautiful," said Smithy. "Now we'll just leave it like that for a few moments to give the electrolytics a chance to form and start working properly. All we've got to do for the moment is keep a visual check to ensure that no resistors are cooking up. So far, we've discovered two good things."

"What are those?"  
 "First," said Smithy, "the heater chain is all right. Second, so is the rectifier. Well, I think we've given those h.t. electrolytics enough time now to get back into working order. See what happens when you turn up the wick."

### NO OUTPUT

Dick advanced the volume control and the pair listened.

"It's dead," stated Dick shortly. "There's no background noise, no hum, no nothing."

"Fair enough," commented Smithy. "We've got h.t. at the reservoir capacitor. Check if there's h.t. at the smoothing capacitor."

Obligingly, Dick applied his testmeter prod to the positive tag of the smoothing capacitor. (Fig. 4 (a).)

"I'm getting about 180 volts here," he called out.

"That seems all right," said Smithy. "Try the anode of the UCL82 triode. It's pin 9."

"Okey-doke," replied Dick. "I'm putting the prod on pin 9 now. And the voltage is 100 volts." (Fig. 4(b).)

"There doesn't seem to be anything wrong there, either," said Smithy. "But there's certainly a fault in the circuit following that triode anode."

"Why's that?"  
 "Because there should have been a crackle from the speaker when you put the test prod on the anode. Try the voltage on the pentode anode. It's pin 6."

Dick placed the test prod on the

anode pin. (Fig. 4(c).)

"The meter says 210 volts," he called out.

"Does it now?" said Smithy. "That's the same reading as we got at the reservoir capacitor. Normally, there's about 20 volts dropped across the primary of these valve output transformers, so either the primary is short-circuit or the pentode isn't drawing any anode current through it. We can see if the pentode is passing cathode current at any event by measuring the voltage across its cathode bias resistor. So check the voltage at pin 2, Dick."

Once more Dick took up the test prod and, this time, he applied it to pin 2 of the UCL82 valveholder. He glanced at the meter then selected a lower voltage range. (Fig. 4(d).)

"There's 18 volts there," he announced.

"18 volts?" repeated Smithy. "That

seems a bit high. These output pentodes usually run with a cathode bias of around 12 volts. At any rate, the voltage shows that the pentode is passing current so it looks as though there's a short across the output transformer primary. Switch the set off, Dick, and measure the resistance of the primary."

Dick carried out Smithy's instructions. After setting his testmeter to an ohms range and zeroing it, he applied his test prods to the transformer tags. (Fig. 5(a).)

"You were right," he announced cheerfully, "there seems to be a dead short here. There's certainly a zero resistance reading in the meter."

"Good show," commented Smithy. "My guess is that the 5,000pF capacitor across the primary has broken down. Snip one of its leads and check it."

The capacitor was mounted on the transformer tags and it took Dick no


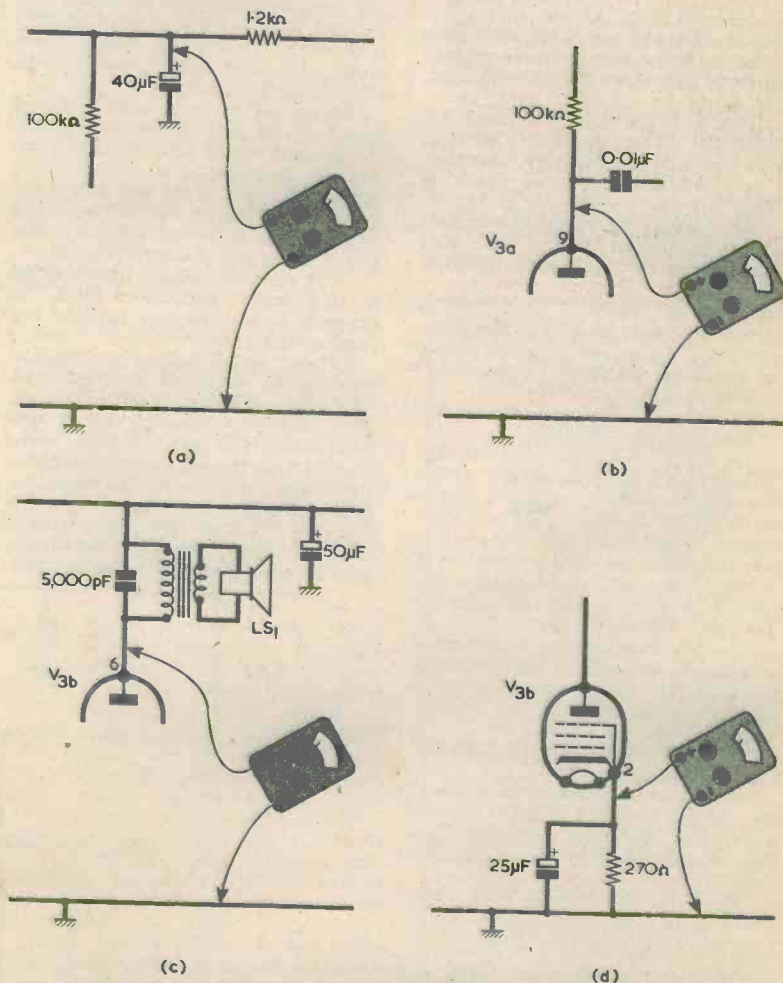


Fig. 4. Successive steps in tracing a fault in the radio. Dick checked the voltage at (a) the smoothing capacitor, (b) the a.f. triode anode, (c) the output pentode anode and (d) the output pentode cathode.

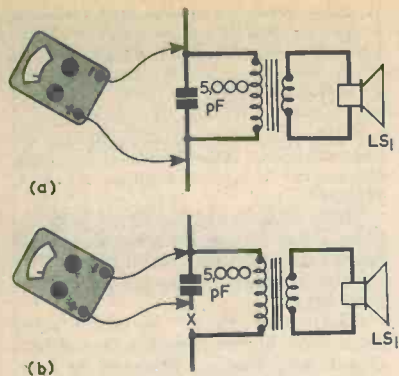

**Fig. 5 (a).** Checking the resistance at the output transformer primary. (b) One lead of the capacitor has to be disconnected before its condition can be checked.

time at all to cut one of its leads close to the tag it connected to. He applied his testmeter leads to the capacitor. (Fig. 5(b).)

"That's it, Smithy," he called out jubilantly. "The capacitor's shorted. Let's see what the primary resistance is now. Blow me, it's as much as 300Ω!"

"That would be about the correct value," confirmed Smithy. "So your next job is to fit a new 5,000pF capacitor."

"Righty-ho, Smithy," said Dick, as he rose and made his way to the spares cupboard. "I suppose a modern plastic foil capacitor will be all right. What working voltage — 250?"

"750 volts would be nearer the mark."

"Hey?"

"I'm quite serious," said Smithy. "The alternating a.f. voltage across that transformer primary can rise to nearly 200 volts peak if the receiver volume is turned up high. Believe it or not, but some set makers used to fit 1,000 volt capacitors across the speaker primary in output circuits like this one."

After a little searching, Dick located a suitable capacitor. He returned, removed the faulty component and commenced to solder in the replacement.

"What," he asked, "is this capacitor supposed to do, anyway?"

"It's simply a brute-force treble-cut component," replied Smithy. "It cuts down the shrillness resulting from third harmonic distortion in the pentode."

"Stap me," exclaimed Dick, as he absorbed this information. "Couldn't they have used negative feedback instead?"

"Negative feedback?" repeated Smithy. "You've got to be joking, Dick. Feedback was only appearing in hi-fi amplifiers in the days when that set was made. Set-makers would have had kittens at the thought of losing

gain by introducing negative feedback!"

"Well, I've got the new capacitor soldered in," announced Dick. "So let's try out this set again."

Once more he turned the volume control switch. There was silence for some moments as the valves warmed up then a quiet hiss became audible from the speaker. Dick turned the tuning control experimentally. Almost immediately he found a station and tuned it in carefully. A voice from the speaker announced a record by Carol Gibbons and the Savoy Orpheans, to be followed by the record itself. Both the voice and the record were noticeably distorted.

"I think," remarked Smithy, "that we have what is a very common snag in these old radios."

"What's that?"

"I think that the 0.01μF coupling capacitor between the triode and pentode sections of the UCL82 has gone leaky and is causing the signal grid of the pentode to go positive. This would explain the unusually high cathode bias voltage, too. Well, we can soon check this. Put that meter on the cathode again, Dick."

Smithy picked up a spare test lead and held the plug at one end against the chassis. Whilst Dick measured the cathode voltage, the Serviceman applied the prod of the test lead to the signal grid of the pentode. There was a loud crackle from the speaker, after which it remained silent. (Fig. 6).

"The cathode voltage has dropped to 12.5 volts," announced Dick. "It dropped as soon as you put that test prod on the grid."

"Then," stated Smithy in a satisfied tone as he removed the test lead, "we've found another fault in this set. That coupling capacitor *must* have been leaky. The fact that there was a crackle from the speaker also confirms that there's leakiness in the capacitor. If the capacitor had been all right the signal grid would have been held at chassis potential by way of the 470kΩ grid resistor, whereupon connecting it

directly to chassis would merely have stopped the sound without causing any crackle. So you've got another capacitor to change now, Dick."

"As you wish," said Dick obligingly, making his second trip to the spares cupboard. "What working voltage does this one need?"

"350 volts will be more than adequate," stated Smithy. "Incidentally, you have to keep an eye on the working voltage of replacement capacitors for these old valve sets. We've got used to plastic foil capacitors having working voltages below 200 volts in transistor equipment, and these could well break down in some of the circuits in a valve set."

## NEW CAPACITOR


Dick had no trouble in locating a new 0.01μF 350 volt capacitor. He sat down at Smithy's bench and removed the faulty component so that it could be replaced by its much less bulky modern equivalent.

"Are these capacitors always liable to give trouble in old sets, Smithy?"

"Oh definitely," confirmed Smithy.

"All the tubular capacitors from around 0.001μF to 0.1μF had paper dielectric with wax impregnation, and it is very common for these to become leaky after some ten to twenty years simply due to the ingress of moisture. If they're used as cathode bypass capacitors they don't usually cause much trouble until their leakage resistance becomes very low, because they're connected across low value resistors. But they only need to have a leakage resistance of 10MΩ or less to cause trouble when they connect an anode to a following grid. So whenever you want to refurbish an old valve radio the components you want to check are firstly, h.t. electrolytics and secondly, paper dielectric capacitors. After that the next components to suspect are fixed resistors of 1MΩ or more. These have a tendency to go high in value."

"Apart from the faults we've

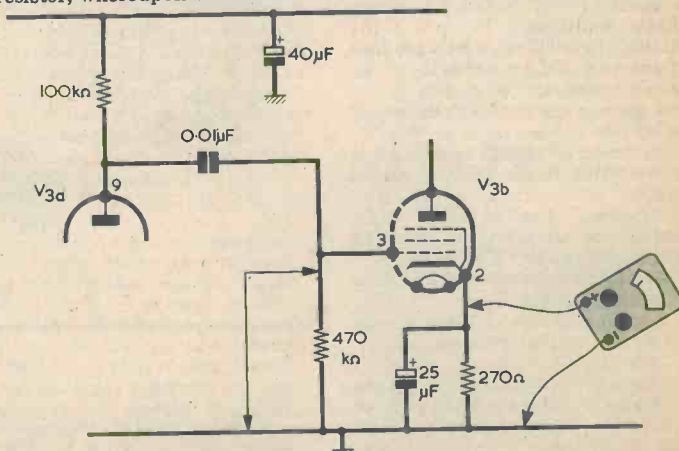

**Fig. 6.** Checking the voltage at V3(b) cathode with the grid resistor short-circuited.

bumped into today," said Dick, "what are the main troubles you are likely to encounter?"

"Instability is the most common one," replied Smithy. "If you look at the circuit of the set we've got here you'll see that the absolute bare minimum of decoupling components is used. For instance, the 40 $\mu$ F smoothing capacitor is the h.t. bypass component for the anode circuits of the frequency changer, the i.f. amplifier and the a.f. triode. In some sets it may also be the anode bypass component for the output pentode as well. The capacitor only needs to develop a very small impedance for all these circuits to couple together, whereupon you get instability. This can happen even when the capacitor still seems to be working all right as a smoothing component."

"Are there any other forms of instability?"

"A very common one is given when the bypass capacitor at the screen-grid of the frequency changer or the i.f. amplifier goes open. The screen-grid prevents capacitive coupling between the anode and the signal grid and, if it isn't reliably held at chassis potential for r.f. by its bypass capacitor, the stage simply oscillates. Usually, you get a heterodyne beat with stations as you tune them in. In the set we have here, both the frequency changer and the i.f. amplifier screen-grids are bypassed to chassis by one capacitor and, once again, it only needs a little unwanted impedance in the bypass circuit for the whole receiver to become unstable." (Fig. 7.)

"D'you know, Smithy," said Dick, as he put Smithy's soldering iron back on its rest, "going back to valves is like entering a new world again."

"You can have a lot of fun with these old valve radios," agreed Smithy. "One would hardly suggest that somebody constructed a valve radio in these present times. On the other hand there can be a lot of pleasure in servicing an old valve radio and getting it to go again."

"Well," said Dick. "I've put in the new 0.01 $\mu$ F capacitor, so let's see how this particular old set works."

He switched it on again. They waited once more for the valves to warm up. As the set came to life, the same voice was heard announcing Henry Hall and his B.B.C. Dance Orchestra. This was followed by "The Teddy Bears' Picnic".

"There's something fishy going on here," remarked Dick a little uneasily. "We've repaired an old radio and all it plays is old records."

"I must confess that it's a bit odd," commented Smithy. "Still that distortion has cleared up. There's no noticeable hum either, so we'll assume that the reservoir and smoothing electrolytics are all right. Indeed, the set sounds jolly good."

"It isn't bad at all," agreed Dick. "In fact the quality is a darned sight better than the noises we've got used to with present-day transistor radios. For

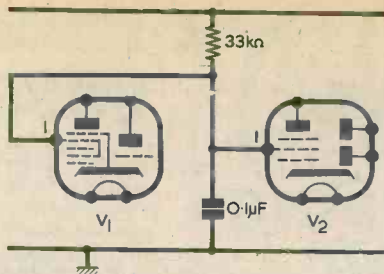


Fig. 7. A common bypass capacitor couples the screen-grids of both the frequency changer heptode and the i.f. amplifier pentode to chassis.

a start, there's a bit of bass to it."

"True," confirmed Smithy.

They listened critically as "The Teddy Bears' Picnic" came to a close. Then followed an interview with a civic dignitary in what was obviously a repeat of "Down Your Way". The dignitary chose a comfortingly modern recording.

"Well," said Dick, his brow clearing, "that clears up the old records mystery. The previous people in the programme must have been elderly geysers."

"Let's put this set through its paces," suggested Smithy.

Dick rotated the tuning control, to be rewarded by a good selection of stations, both on medium and long waves.

## UNEXPECTED PRESENT

"Seeing," remarked Smithy, "that we found this set under your bench, you might as well keep it for yourself. I can't see anyone coming to claim it after all these years."

"Gosh Smithy, thanks. This will be just the job for my bedroom. I must say that I've really enjoyed the repair job we've done on it. Are there any other hints you can pass on about fixing old sets?"

"Only the obvious ones. For instance there's not much point in tackling an old set if the cabinet is broken beyond repair or if the set has been stored in a damp place. Also, the job is probably not worth the trouble if there's a mechanical snag in the wave-change switching arrangements or in the tuning drive which is difficult to clear. Again, I'd think twice about tackling some of the earlier sets with printed circuits as there's a fairly high risk of leakage between copper sections on the board. The best sets to play with are those where the parts are assembled on a chassis."

Dick looked fondly at the radio which he had now so unexpectedly acquired, then glanced over at the cardboard boxes on the surface of his bench.

"If," he remarked cheerfully, "this is what happens when we have a clear-out of my junk, then I'm all for having a clear-out every day!"

## GAREX

**Modulation transformers**  
Valve type 747, for 30W Tx £2.60

**Transistor type, p/p NKT404 to QQV03-20a**  
(or QQV03-10), with driver transformer to match - special offer - the two £1.30

**Mains transformer (multitap primary)**  
250-0-250V 200mA, 6.3V 5A, 5V 2A, fully shrouded, (suitable for 30W Tx - matching style to mod. transf.) £5.95

Connection data supplied with transformers.

**H.T. chokes** 5H 80mA, 1.8H 125mA £1.25

**Relays** GPO type 2400, 12V coil, 8A contacts, 4PCO or 2P make 40p each; 5+ : 25p

**Neons** min. wire end, 55p/10; £4/100

**Slide Switches** min. DPDT 15p ea; 5+ : 12p

**2 pole, 3 position** 22p each; 5+ : 18p

**PL259 UHF Plug & Reducer** 60p; 5+ : 50p

**SO239 UHF Socket panel mtd.** 45p; 5+ : 36p

**BNC cable mtg Socket** 50 $\Omega$  15p; 5+ : 12p

**Resistor Kits** 10E12 5% C-Film, 10 each value 22 $\Omega$  to 1M (570 pcs)  $\frac{1}{2}$  or  $\frac{1}{4}$ W £4.75

**Numericators** ZM1080 75p each; 5+ : 63p

**I.C.'s (new, full spec.)** CD4001AE 40p

**SN76680 FM Quad. detector** £1.12

**723 Voltage reg. TO5 metal case** 90p

**NE555 Timer** 75p

**709 (TO5); 741 (DIL-8) Op. amps** 25p each

**5+ I.C.'s (any mix) at 20% discount**

**Nicad rechargeable cells** HP7 size £1 each

**4+ : 90p; 10+ : 85p.** New, recent manufacture.

Prices include UK Post, Packing & VAT

Mail order only Sole Address:

**GAREX ELECTRONICS**  
7 NORVIC ROAD, MARSWORTH,  
TRING, HERTS HP23 4LS  
Cheddington (STD 0296) 686884

## MORSE MADE EASY



### BY THE RHYTHM METHOD!

These courses, which have been sold for over 23 years, have been proved many times to be the fastest method of learning Morse. You start right away by learning the sounds of the various letters, numbers, etc., as you will in fact use them. Not a series of dots and dashes which later you will have to translate into letters and words.

Using scientifically prepared 3-speed records you automatically learn to recognise the code RHYTHM without translating. You can't help it. It's as easy as learning a tune. 18-V.P.M. in 4 weeks guaranteed.

The Complete Course consists of three records as well as instruction books.

For Complete Course send £5.00 including P.P.I. etc. (overseas surface mail £1 extra).

### THE MORSE CENTRE

Box 8, 45 Green Lane, Purley, Surrey.  
I enclose £5.00 or large s.a.e. for explanatory booklet.

Name.....

Address.....

# TV

## FAULT FINDING MANUAL for 405/625 LINES



**90p**  
P. & P. 18p

### REVISED & ENLARGED

EDITED BY J. R. DAVIES

132 pages

Over 100 illustrations, including 60 photographs of a television screen after the appropriate faults have been deliberately introduced.

Comprehensive Fault Finding Guide cross-referenced to methods of fault rectification described at greater length in the text.

# UNDERSTANDING TELEVISION



by  
J. R. DAVIES

Over 500 pages  
300 diagrams

**£3.25**  
P. & P. 60p

UNDERSTANDING TELEVISION deals with:

- Principles of 405 line reception
- Principles of 625 line reception
- Nature of the television signal
- Receiver tuner units
- A.F. and video amplifiers
- Deflector coil assemblies
- Automatic gain and contrast control
- Receiver aerials
- The cathode ray tube
- Receiver i.f. amplifiers
- Vertical and horizontal timebases
- Synchronising
- Power supply circuits
- Colour television
- **COLOUR TELEVISION** – 80 page comprehensive introduction to the subject

The reader is required to have only a basic knowledge of elementary radio principles. The treatment is non-mathematical throughout, and there is no necessity for any previous experience in television whatsoever. At the same time UNDERSTANDING TELEVISION is of equal value to the established engineer because of the very extensive range it covers and the factual information it provides.

To Data Publications Ltd., 57 Maida Vale, London, W9 1SN

Please supply the 4th revised edition of TV FAULT FINDING, Data Book No. 5.....

Please supply UNDERSTANDING TELEVISION, Data Book No. 17.....

I enclose cheque/crossed postal order for.....(Tick which book is required)

NAME.....

ADDRESS.....

(BLOCK LETTERS PLEASE)

# SMALL ADVERTISEMENTS

Rate: 8p per word. Minimum charge £1.00  
Box No. 20p extra

Advertisements must be prepaid and all copy must be received by the 4th of the month for insertion in the following month's issue. The Publishers cannot be held liable in any way for printing errors or omissions, nor can they accept responsibility for the *bona fides* of Advertisers. (Replies to Box Numbers should be addressed to: Box No. — **Radio and Electronics Constructor**, 57 Maida Vale, London, W9 1SN.

**SERVICE SHEETS** for Radios/TV's etc. 50p and s.a.e. Catalogue 20p and s.a.e. Hamilton Radio, 47 Bohemia Road, St. Leonards-on-Sea, Sussex.

**VINTAGE WIRELESS:** For:— valves, circuits, components, receivers, books, magazines, repairs and nostalgia in radio 1920 to 1950, contact Tudor Rees (Vintage Services). Send s.a.e. for newsheet or 50p for full 1976 catalogue. 64 Broad Street, Staple Hill, Bristol, BS16 5NL. Telephone: 0272 565472.

**COMPONENTS AND HARDWARE — FAST. FREE** Catalogue and samples. Includes transistor tester data. Send 2 x 6½p stamps. Magenta Electronics Ltd., R9, 61 Newton Leys, Burton-on-Trent, Staffs., DE15 0DW.

**WANTED TO PURCHASE:** All early books on radio preferably before 1925. Box No. 282.

**TREASURE HUNTERS!** Construct, inexpensively, metal detector giving £300 performance. 10 pages, illustrated plans, £1. C. H. Lucas, 241 Upminster Road South, Rainham, Essex.

**WANTED TO PURCHASE:** large and small quantities of transistors, diodes, I.C.s, etc. Immediate requirement for 10,000 BC109 transistors. Send samples/lists of any surplus components. Elekon Enterprises, 224a St. Paul's Road, Highbury Corner, London N1 2LJ. Telephone: 01-359 4224.

**FOR SALE:** ORP12 48p, BPX25 £1.10, TBA625B 90p, TBA625C £1.05, LM309K £1.40, TIL108L £1.70, 2N3055 40p, MAN64A, com. anode 0.4" 7 segment & d.p. £1.60. Silicon solar cells .5 volts 40mA, £2.10. Cybertone audio tone generator, variable rate/pitch, 12 volt operation, £3.50. DIL sockets 8, 14 or 16 pin, 12p. Clock crystal 32.768kHz, £2.40. Precision resistor pack, 1/8W -1% -100ppm, 120-200k, 18 different resistors in each pack, £1.44. P & P 25p extra. For unpriced parts list please send s.a.e. Box No. G308.

**PHOTO-COPIES** of articles in *Radio & Electronics Constructor* back to 1963. 20p per page plus large s.a.e. Evison, 6 Pondcroft Road, Knebworth, Herts.

(Continued on page 125)

## WHAT'S ON VLF?

EXPLORE 10-150 KHz with a VLF TUNER. Listen to time signals, CW weather forecasts, DX beacons, standard frequencies, etc. RF in -audio out. EASY TO MAKE, all parts, case, PCB, instructions, money back assurance. ONLY £9.70, £11.20 airmail.

**Cambridge Kits**

45 (EJ) Old School Lane,  
Milton, Cambridge

# Components?

The firm you need is  
**HOME RADIO**  
publishers of the famous



## HOME RADIO COMPONENTS CATALOGUE



For full details see the separate advertisement in this issue.

**HOME RADIO COMPONENTS LTD.**

240 London Rd, Mitcham, Surrey, CR4 3HD.  
Phone 01-648 8422

## REVOR OPTICAL & TECHNICAL

42 TAVISTOCK STREET  
LONDON W.C.2  
Tel. 01-836 4536

**£8.50**

**POST FREE**

**4"** dia. lens

**FLEXIBLE  
MAGNIFIER**

WITH CAST IRON BASE,  
PRECISION GROUND AND  
POLISHED LENS, CHROME PLATED  
FRAME AND FLEXIBLE TUBE.  
IDEAL FOR HOBBIES, AND  
DETAILED WORK WHICH REQUIRES  
BOTH HANDS FREE.

CALLERS WELCOME

(Subject to price ruling at the time of issue)



## PRECISION

### POLYCARBONATE CAPACITORS

ALL HIGH STABILITY - EXTREMELY LOW LEAKAGE

440V AC (+-10%)	63V DC Range	+1%	+2%	+5%
0.1µF (1" x 3") 68p	0.47µF	£1.32	77p	51p
0.22µF (1" x 3") 86p	1.0µF	£1.56	91p	60p
0.25µF (1" x 3") 92p	2.2µF	£1.98	£1.32	75p
0.47µF (1" x 3") £1.10	4.7µF	£2.82	£1.88	£1.23
0.5µF (1" x 3") £1.16	6.8µF	£3.48	£2.32	£1.47
0.68µF (2" x 3") £1.25	10.0µF	£4.98	£3.32	£2.01
1.0µF (2" x 3") £1.37	15.0µF	£7.14	£4.76	£2.88
2.0µF (2" x 1") £1.95	22.0µF	£9.66	£6.44	£3.90

**TANTALUM BEAD CAPACITORS** - Values available: 0.1, 0.22, 0.47, 1.0, 2.2, 4.7, 6.8µF at 15V/25V or 35V; 10.0µF at 16V/20V or 25V; 22.0µF at 6V/10V or 16V; 33.0µF at 6V or 10V; 47.0µF at 3V or 6V; 100.0µF at 3V. ALL AT 12p EACH: 10 for £1.10; 50 for £5.00.

#### TRANSISTORS:

BC107/8/9 9p	BC183/183L 11p	BF194 12p	BFY51 20p
BC114 12p	BC184/184L 12p	BF196 13p	BFY52 20p
BC147/8/9 10p	BC212/212L 12p	BF197 13p	OC71 20p
BC157/8/9 12p	BC547 12p	AF178 40p	2N3055 50p
BC182/182L 11p	BC558A 12p	BFY50 20p	*2N3702/411p

1N914 6p; 8 for 45p; 18 for 90p. 1N916 8p; 6 for 45p; 14 for 90p. IS44 5p; 11 for 59p; 26 for £1.00. IN4148 5p; 6 for 27p; 12 for 48p.

**LOW PRICE ZENER DIODES:** 400mW; Tol. +-5% at 5mA. Values available: 3V; 3.6V; 4.7V; 5.1V; 5.6V; 6.2V; 6.8V; 7.5V; 8.2V; 9.1V; 10V; 11V; 12V; 13V; 13.5V; 15V; 16V; 18V; 20V; 22V; 24V; 27V; 30V. All at 7p each; 5 for 33p; 10 for 65p. SPECIAL: 100 Zeners for £6.00.

**RESISTORS:** High stability low noise carbon film 5%, 1/2 W at 40°C; 1/4 W at 70°C. E12 series only - from 2.2Ω to 2.2MΩ ALL AT 1p EACH; 8p for 10 of any one value; 70p for 100 of any one value. SPECIAL PACK: 10 of each value 2.2Ω to 2.2MΩ (730 resistors) £5.00.

**SILICON PLASTIC RECTIFIERS** - 1.5 Amp - Brand new wire ended D027: 100 P.I.V. - 7p (4/26p); 400 P.I.V. - 8p (4/30p).

**BRIDGE RECTIFIERS:** 2 1/2 Amp. 200V - 40p; 350V - 45p; 600V - 55p.

**SUBMINIATURE VERTICAL PRESETS** - 0.1W only; ALL AT 5p each; 50Ω, 100Ω, 220Ω, 470Ω, 680Ω, 1K, 2.2K, 4.7K, 6.8K, 10K, 15K, 22K, 47K, 100K, 220K, 680K, 1M, 2.5M, & 5M.

PLEASE ADD 8% VAT TO ALL ITEMS EXCEPT THOSE MARKED WITH \* WHICH ARE 12 1/2%. PLEASE ADD 20p POST AND PACKING ON ALL ORDERS.

Send S.A.E. for lists of additional ex-stock items. Wholesale price lists available to bona-fide companies. ALL EXPORT ORDERS PLEASE ADD COST OF SEA/AIR MAIL.

### MARCO TRADING

Dept. P1, The Old School, Edstaston, WEM, Salop. Tel: WHIXALL (Salop) 464/5 (STD 094872) (Props: Minicost Trading Ltd.).

# RADIO MODELLER

## ELECTRONIC BOOKS


#### MODEL RADIO CONTROL

Detailing both Theory and Practice, this book, by leading authority Paul Newell, has become the standard reference work. A brief historical survey leads up to a detailed description of proportional systems, with over 100 illustrations, including theoretical circuits and p.c. layouts for an advanced digital system. 134 pages Price £2.25

U.K. Packing & Postage 32p

ON SALE NOW  
at all leading shops  
or direct from:-

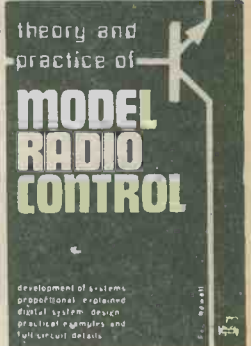RADIO MODELLER  
BOOKS DIVISION,  
64 Wellington Road,  
Hampton Hill, Middx.



## SMALL ADVERTISEMENTS

Use this form for your small advertisement

To: The Advertisement Manager, Data Publications Ltd., 57 Maida Vale, London W9 1SN

Please insert the following advertisement in the ..... issue of RADIO & ELECTRONICS CONSTRUCTOR

➔			

15 words at 8p  
= £1.20

ALL WORDING  
IN  
BLOCK LETTERS  
PLEASE

I enclose remittance of ..... being payment at 8p a word. MINIMUM £1.00  
Box Number, if required, 20p extra

NAME .....  
ADDRESS .....

Copy to be received four weeks prior to publication. Published on the 1st of every month.

## SMALL ADVERTISEMENTS

(Continued from page 123)

**THE RADIO AMATEUR INVALID & BEDFAST CLUB** is a well established Society providing facilities for the physically handicapped to enjoy the hobby of Amateur Radio. Please become a supporter of this worthy cause. Details from the Hon. Secretary, Mrs. Rita Shepherd, 59 Paintain Road, Loughborough, Leics., LE11 3LZ.

**WANTED:** Buy or hire. Service manual for contamination meter 5CG0012. Forrester, 4 Beechcombe, Corringham, Essex.

**WANTED TO PURCHASE:** American "Popular Electronics" magazine for January, 1973. Good price paid. Box No. G314.

**UNIQUE "GLOBE-KING" VHF KITS.** 80-180MHz. Receiver, tuner, converter. World wide sales. Send £6.00 or s.a.e. for free literature. Johnsons Radio (C), 17 Solitaire Avenue, Worcester, WR2 5PP.

**FOR SALE:** Brand new grade one transistors. Surplus to requirements. Manufactured by well-known company. 170-BF180, 180-BF181, 180-BF182, 180-BF183, 190-BF184, 190-BC187, 1090 transistors in all. Best offer over £50 secures. Box No. G315.

**JOIN THE INTERNATIONAL S.W. LEAGUE.** Free services to members including Q.S.L. Bureau, Amateur and Broadcast Translation, Technical and Identification Dept. — both Broadcast and Fixed Stations, DX Certificates, contests and activities for the SWL and transmitting members. Monthly magazine, *Monitor*, containing articles of general interest to Broadcast and Amateur SWLs, Transmitter Section and League affairs, etc. League supplies such as badges, headed notepaper and envelopes, QSL cards, etc., are available at reasonable cost. Send for League particulars, Membership including monthly magazines, etc., £3.75 per annum. (U.K. and British Commonwealth), overseas \$10.00 or £4.00. Secretary ISWL, 1 Grove Road, Lydney, Glos., GL15 5JE.

**MULLARD COMPONENTS.** Send s.a.e. for free list to P.M.S. Dept. REC1, P.O. Box 6, Crawley, Sussex, RH10 6LH.

**VALVES, RADIO, TV, Transmitting, Industrial.** 1930 to 1976. 2,500 types. Many obsolete. List 20p. S.A.E. for quotation. We wish to buy all types of new and boxed valves. Wholesalers, dealers, etc., stocks purchased. Cox Radio (Sussex) Ltd., The Parade, East Wittering, Sussex. Telephone: West Wittering 2023.

(Continued on page 126)

### TAPETALK THE CLEVER WAY TO LEARN

TWO C60 CASSETTES ENTITLED  
**'INTRODUCING TRANSISTORS'**  
will be sent to you by return of post for only  
£5.44 plus 55p. VAT/P.Pkg.

**TAPETALK, P.O. BOX 99 (C),  
MILTON KEYNES MK3 5BR.**  
Tel: Milton Keynes (0908) 77710

# ELECTRONI-KIT

**BUILD, DISMANTLE AND REBUILD  
OVER 100 DIFFERENT PROJECTS  
AND DESIGN YOUR OWN  
CIRCUITS TOO**

Radio Receivers & Transmitters, Telephone Amplifiers, Time Buzzers, Battery Checkers, Computer Circuits, Amplifiers, Directional Transmitters, Metal Detectors, Continuity Testers, Electronic Birds, Guns, Metronomes, Sirens, Roulette, etc., etc. **ALL IN ONE KIT**

"... educational kits of exceptional quality" (AUDIO mag)

"... worthwhile ... good value for money" (EVERYDAY ELECTRONICS mag)


Educational manuals included with each kit. No previous experience required. Suitable for beginners and experts too.

**100 project kit £19.60** (Add-on kits available too)  
**45 project kit £15.60**  
**25 project kit £12.10**

Prices include Manuals, Batteries, VAT and p&p  
Cheque/PO (or 11p for illustrated literature) to DEPT. REC.

Satisfaction guaranteed.

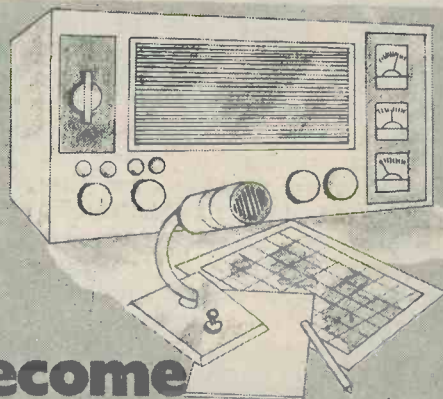**ELECTRONI-KIT LTD, 408 St. John's Street,  
London, EC1. (01-278 4579)**



## Become a radio amateur.

Learn how to become a radio-amateur in contact with the whole world. We give skilled preparation for the G.P.O. licence.

Free!

Brochure, without obligation to: **REK 96**


**BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL, Dept**  
P.O.Box 156, Jersey, Channel Islands.

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_ (Block caps please)
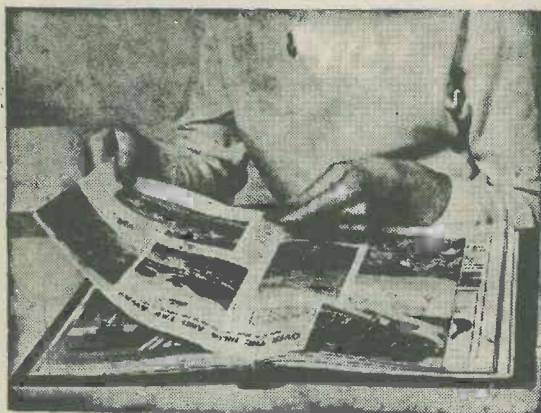
# PLAIN-BACKED NEW STYLE SELF-BINDERS

for your other magazines  
(max. format 7½" x 9½")



The "CORDEX" Patent Self-Binding Case will keep your copies in mint condition. Issues can be inserted or removed with the greatest of ease. Specially constructed Binding cords are made from Super Linen of great strength, very hard twisted and twice doubled. They are attached to strong RUSTLESS Springs under tension, and the method adopted ensures PERMANENT RESILIENCE of the Cords. Any slack that may develop is immediately compensated for, and the Cords will always remain taut and strong. It is impossible to overstretch the springs, as a safety check device is fitted to each.

**COLOURS: MAROON OR GREEN**

(If choice not stated, colour available will be sent)

**PRICE 95p** P. & P. 25p

Available only from:—

**Data Publications Ltd.**  
57 Maida Vale London W9 1SN

## SMALL ADVERTISEMENTS

(Continued from page 125)

**FREQUENCY LIST TRANSFERS.** We have a limited supply of sheets of Dial Frequency Transfers in black. Short Wave frequencies 1.8Mc/s to 32Mc/s and 144Mc/s and 146Mc/s. Includes amateur band marker frequencies at 100kc/s points and other short wave frequencies from 2 to 32 Mc/s at every 500Kc/s points. Each frequency is repeated. Two sheets for 5p., five sheets for 10p., postage 6p. Data Publications Ltd., 57 Maida Vale, London, W9 1SN.

**BOOKS TO CLEAR.** 110 Operational Projects by R. M. Marston, 1975, £1.50; *Popular Electronics and Computers* by F. G. Rayer, 1968, £1.00; *Radio Experiments* by F. G. Rayer, 1968, 50p; *Beginners Guide to Transistors* by J. A. Reddihough, 1975, £1.00; *Television Engineering* by Amos, Birkinshaw & Green, 1969, £2.00; *Radio & Line Transmission* by Danielson & Walker, 1969, £1.50; *Electric Model Car Racing* by D. J. Laidlaw-Dickson, 1965, 60p; *Radio Communication* by J. H. & P. J. Reyner, 1962, £2.00. All prices include Postage and Packing. Box No. G316.

**FOR SALE:** Selected range of popular transistors, diodes and I.C.s. For free price list write to: Leo's Electronics, 147 Millais Road, London E11 4EZ. No callers please.

**PRACTICAL TEST EQUIPMENT.** Build your own test equipment with this exciting new book by G. C. Dobbs. Complete constructional details for seven reliable instruments. 75p plus 10p P&P. Georgian Press, 8 Redgates Court, Calverton, Nottingham.

**POSTAL ADVERTISING?** This is the Holborn Service. Mailing lists, addressing, enclosing, wrapping, facsimile letters, automatic typing, copy service, campaign planning, design and artwork, printing and stationery. Please ask for price list. — The Holborn Direct Mail Company Capacity House, 2-6 Rothsay Street, Tower Bridge Road, London. S.E.1. Telephone: 01-407 6444.

**UFO (FLYING SAUCER) CIRCUITS.** Interesting projects for the purely scientific experimenter, including valve and transistor set ups for the observer. Circuit diagrams are complete and cost £1.30 per set. **RADIO CONTROL.** Transistor and valve circuits and building plans for radio control models, including model ships or boats, aircraft models, etc. Also some plans for additional equipment for pleasure boat owners, to instal in their own craft. D. G. Harrington, 'Carnbrae', 25 Poynter Road, Bush Hill Park, Enfield, Middlesex.

## PERSONAL

**JANE SCOTT FOR GENUINE FRIENDS.** Introductions to opposite sex with sincerity and thoughtfulness. Details free. Stamp to: Jane Scott, 3/Con North St. Quadrant, Brighton, Sussex, BN1 3GJ.

**DISABLED YOUNG MAN** looking for electronic wiring assembly (outwork) for assembly in his home workshop. Box No. G307.

(Continued on page 127)

RADIO & ELECTRONICS CONSTRUCTOR



## SMALL ADVERTISEMENTS

(Continued from page 126)

**IF YOU HAVE ENJOYED A HOLIDAY** on the Norfolk Broads, why not help to preserve these beautiful waterways. Join the Broads Society and play your part in determining Broadlands future. Further details from: - The Hon. Membership Secretary, The Broads Society, "Icknield," Hilly Plantation, Thorpe St. Andrew, Norwich, NOR 85S.

**ESSEX GARDENERS.** Buy your Bedding and rock plants, shrubs, etc., also cacti from May's Nurseries, 608 Rayleigh Road, Hutton, Brentwood, Essex. Callers only. Monday to Saturday.

**SPONSORS** required for exciting scientific project. Norwich Astronomical Society are building a 30" telescope to be housed in a 20' dome of novel design. All labour being given by volunteers. Already supported by Industry and Commerce in Norfolk. Recreational. Educational. You can be involved. Write to: NAS Secretary, The Manse, Back Lane, Wymondham, Norfolk.

### Give for those who Gave

#### WINGS APPEAL



During September



**TAPETALK**  
The  
**CLEVER**  
way  
to  
**LEARN**

*This Month's Special Offer:*  
*TWO C60 Cassettes entitled*  
**INTRODUCING ELECTRONICS**  
will be sent to you by return of post for only  
**£5.44** plus 55p VAT/P. Pkg.

**TAPETALK, P.O. Box 99 (C)**  
**Milton Keynes MK3 5BR**  
**Tel: Milton Keynes (0908) 77710**

OVER 2,000 ELECTRONIC COMPONENTS IN A

# BIG NEW FREE

## 100 PAGE CATALOGUE

**YOURS BY  
POSTING  
TODAY**

Please send me  
the 100 page  
Tandy catalogue

Name \_\_\_\_\_

Address \_\_\_\_\_

**40  
PAGES IN  
COLOUR**

# TANDY

Nationwide supermarket of sound!

REC/2

Tandy Corporation (Branch UK), Bilston Road,  
Wednesbury, W. Midlands WS10 7JN.

**MULLARD FERRITE CORES** — LA3 100 to 500 kHz, 54p; LA5 30 to 100 kHz, 81p; LA7 < 10 kHz, 81p; LA13 for W.W. Oscilloscope, £1.50.

**SPECIAL OFFER** — Metallised Polyester Capacitors by Erie, Mullard, etc. Values include: .01/160V, .01/250V, .015/160V, .022/160V, .033/160V, .047/160V, .068/160V, .1/160-250V, .22/160V, etc. This is a bargain not to be missed. 100 for £2.00.

1N4148 **SWITCHING DIODES**, 10 for 30p; 50 for £1.25; 100 for £1.50; 1,000 for £10.00

**TRANSISTORS** — All branded. BC147, BC148, BC149, BC157, BC158, BC159, BF194, BF195, BF196, BF197, 8p each or 100 for £6.00.

*Please note all prices include UK Postage and appropriate VAT @ 8% or 12½%*

**MAIL ORDER ONLY**  
**XEROZA RADIO**

1 EAST STREET, BISHOP'S TAWTON, DEVON

**express component service**  
**same day turn round**  
**High Spec Components**  
**FAST**

S.A.E. Stocklist  
Post Free Order Service  
Super Express Phone Service  
Shop 6 Days Per Week


*Example Price: BC108 - 10p*

**orchard electronics** 

Flint House, High Street,  
Wallingford, Oxon  
Tel: (0491) 35529. Telex: 4SP WALFRD 849349.



# THE OPEN DOOR TO QUALITY

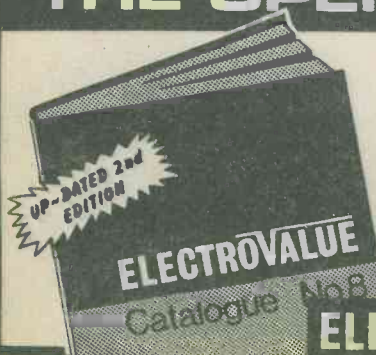

This catalogue — Electrovalue Catalogue No. 8 (Issue 2, updated) offers items from advanced opto electronic components to humble (but essential) washers. Many things listed are elsewhere very difficult to obtain. The company's computer is programmed to expedite delivery and maintain customer satisfaction. Attractive discounts are allowed on many purchases. Access and Barclaycard orders are accepted. **+FREE POSTAGE** on all C.W.O. mail orders over £2.00 list value (excluding V.A.T.) in U.K. If under, add 15p handling charge.

**144 pages**

Post paid

**40p**

inc. refund  
voucher  
worth  
**40p**

All communications to Dept REC3  
28 St Johns Rd, Enfield Green, Enfield, Surrey TW20 0HD. Phone: Enfield 3803.  
Telex: 264475. Shop hours: 9.30-5.1 pm Sat.  
Northern Branch: 880 Burnage Lane, Burnage, Manchester M19 1NA. Phone: (061) 432 4946.  
Shop hours: 9.30 am-5.1 pm Sat. In U.K. you are invited to contact  
ELECTROVALUE AMERICA PO.337, Peterborough NH03458.

## ELECTROVALUE LTD

# RADIO & ELECTRONICS CONSTRUCTOR

## Single Copies

Price **35p** each, postage 11p

Issue(s) required .....

## Annual Subscription

Price **£5.00**, post free, commence with .....issue

## Bound Volumes:

Vol. 25. August 1971 to July 1972.	Price <b>£2.00</b> , post & pkg 75p
Vol. 27. August 1973 to July 1974	Price <b>£2.40</b> , post & pkg 75p
Vol. 28. August 1974 to July 1975	Price <b>£2.75</b> , post & pkg 75p

## CORDEX SELF-BINDERS

With title, 'RADIO & ELECTRONICS CONSTRUCTOR' on spine, maroon only	Price <b>£1.00</b> , post & pkg 25p
With no title on spine, maroon	Price <b>95p</b> , post & pkg 25p
With no title on spine, green	Price <b>95p</b> , post & pkg 25p

*Prices include V.A.T.*

## DATA BOOK SERIES

DB5 TV Fault Finding, 132 pages	Price <b>90p</b> , P. & P. 18p
DB6 Radio Amateur Operator's Handbook, 88 pages	Price <b>70p</b> , P. & P. 12p
DB17 Understanding Television, 504 pages	Price <b>£3.25</b> , P. & P. 60p
DB18 Audio Amplifiers, 124 pages	Price <b>53p</b> , P. & P. 15p
DB19 Simple Short Wave Receivers 140 pages	Price <b>80p</b> , P. & P. 18p

## STRIP-FIX PLASTIC PANEL SIGNS

Set 3: Wording — White	Price <b>75p</b> , P. & P. 7p
Set 4: Wording — Black	Price <b>50p</b> , P. & P. 7p
Set 5: Dials	Price <b>38p</b> , P. & P. 7p

*Prices include V.A.T. on Panel Signs*

I enclose Postal Order/Cheque for.....in payment for.....

NAME .....

ADDRESS .....

(BLOCK LETTERS PLEASE)

*Postal Orders should be crossed and made payable to Data Publications Ltd.  
Overseas customers please pay by International Money Order.  
All publications are obtainable through your local bookseller*

**Data Publications Ltd., 57 Maida Vale, London W9 1SN**

**PLEASE MENTION THIS MAGAZINE WHEN WRITING TO ADVERTISERS**