

# RADIO & ELECTRONICS CONSTRUCTOR

**APRIL 1980**  
**Volume 33 No. 8**

Published Monthly

First published in 1947

Incorporating *The Radio Amateur*

Editorial and Advertising Offices  
57 MAIDA VALE LONDON W9 1SN

Telephone  
01-286 6141

Telegrams  
Databux, London

© *Data Publications Ltd.*, 1980. Contents may only be reproduced after obtaining prior permission from the Editor. Short abstracts or references are allowable provided acknowledgement of source is given.

**Annual Subscription:** £8.50, Eire and Overseas £9.50 (U.S.A. and Canada \$20.00) including postage. Remittances should be made payable to "Data Publications Ltd". Overseas readers, please pay by cheque or International Money Order.

**Technical Queries.** We regret that we are unable to answer queries other than those arising from articles appearing in this magazine nor can we advise on modifications to equipment described. We regret that queries cannot be answered over the telephone, they must be submitted in writing and accompanied by a stamped addressed envelope for reply.

**Correspondence** should be addressed to the Editor, Advertising Manager, Subscription Manager or the Publishers as appropriate.

**Opinions** expressed by contributors are not necessarily those of the Editor or proprietors.

**Production**— Web Offset.

THE "40-20" GAME — Suggested Circuit — by G. A. French	464
RECENT PUBLICATIONS	467
NEWS AND COMMENT	468
MICRO CURRENT ICM7555 CIRCUITS — by A. P. Roberts	470
TRADE NOTE — Magnetiser/Demagnetiser for the Workbench	473
SEED PROPAGATOR HEATER — Electronic Control of Soil Temperature — by J. K. Owen	474
NEW PRODUCTS	478
IN NEXT MONTH'S ISSUE	479
AMPLIFYING INTERCOM — Useful Addition to any Household — by R. A. Penfold	480
ELECTRONIC CATALOGUE	487
THE STATUS REGISTER — Databus Series No. 9 — by Ian Sinclair	488
MEDIUM-LONG WAVE REFLEX PORTABLE — Part 1 (2 parts) — by R. F. Haigh	491
THE RIGHT CONNECTION — Reliable Soldering in the Electronics Industry	496
SHORT WAVE NEWS— For DX Listeners — by Frank A. Baldwin	498
MONOCHROME VIDEO FAULT — A Lack of Vision — In Your Workshop	500
COMPUTER BASIC COURSE REVIEW	505
TRACKING — Electronics Data No. 56	iii

Published in Great Britain by the Proprietors and Publishers, Data Publications Ltd, 57 Maida Vale, London W9 1SN.

The *Radio & Electronics Constructor* is printed by Swale Press Ltd.

**THE MAY ISSUE  
WILL BE PUBLISHED  
EARLY IN APRIL**


# BEWARE! RADIO ACTIVITY



The new MK III FM tuner sitting under the Dorchester multiband AM/FM tuner

Revisions to the Mark III include: a centre zero tuning indicator meter and silent preset switching

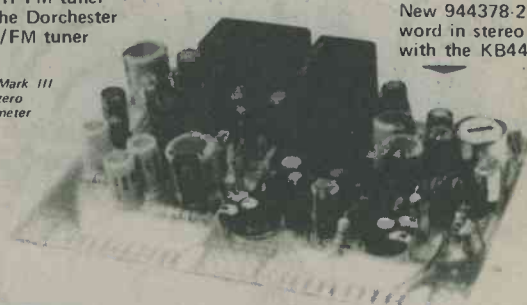New 944378-2, the last word in stereo decoders with the KB4437/4438.



Choosing the products to advertise each month can be quite a task at AMBIT, since we tend to introduce at least one new line per week. So it is nearly impossible to say all we would like in this space - other than to bring you as far up to date as possible with current events. The major medium for finding out about what we have to offer is our unique catalogue system, and we ask that you invest in a copy of parts 1, 2 & 3 since many questions we are asked can be readily answered by reference to these.

Each part costs 60p, or £1.60 for all three current editions.

We are also launching a new and greatly elongated version of our PRICE LIST, which now includes a large number of quantity listings, and many items not previously listed. The new style price list is a quick reference short form to our general catalogues - available FOC with a large (A4) SAE please.

As a result of the soaring price of oil - and the subsequent huge increases in the cost of wax for Mr Tom Jackson's famous moustache, the Post Office have increased their charges (Feb. 4th). Accordingly, our standard cover charge has been increased to 35p per order (CWO).

## COMPONENTS

### DIGITAL FREQUENCY READOUTS / SYNTHESISER SYSTEMS

Ambit has the biggest range of digital frequency readout systems for various applications in Broadcast and Communications. Prices range from £18.50 for a complete AM/FM broadcast frequency display (kit of DFM2). Most are detailed in the latest catalogue.

TUNING SYNTHESIZERS are also heavily featured, and we offer our first complete system covering MW/LW/SW2 and FM based on Hitachi parts. The unit is retrofittable to voltage tuned radio systems - and will shortly be incorporated in a complete tuner project. Cost for the synthesiser will be circa £40. A versatile communications system based on the new Mullard 2 IC system is nearing completion, together with 16 station CMOS memory and optical shaft encoder system with fast tune facility. Synthesiser circa £70, memory £50.

### Latest semiconductor news:

CMOS, TTL and LPSN TTL are in stock (ask for our OSTs price leaflet). Some of the very popular types are still "difficult" but we have things like 4011s, 4017s at the time of writing.

RADIO ICs - interesting developments here, we now have the Hitachi HA11225 and the HA12412 ultra high specification members of the CA3089E family. The PLESSEY SL1600 range now includes the SL6600 high performance PLL NBFM IF and detector.

CA3089E	2.11	HA1197	1.61	SD6000	4.31	SL1610	1.84	SL1626	2.80
CA3189E	2.53	CA3123E	1.61	TDA4420	2.59	SL1611	1.84	SL1630	1.86
HA1137W	1.95	TDA1072	3.09	MC1330P	1.38	SL1612	1.84	SL1640	2.17
HA11225	2.47	TBA651	2.53	MC1350P	1.38	SL1613	2.17	SL1641	2.17
HA12412	2.81	TDA1090	1.61	KE4412	2.24	SL1620	2.50	SL6600	4.31
KB4420	1.95	TDA1220	1.61	KB4413	2.24	SL1623	2.80	SL6640	3.16
TBA120S	1.15	TDA1083	2.24	KB4417	2.53	SL1624	3.77	SL6690	3.68
KB4406	0.80	TDA1062	2.24	MC3357P	3.16	SL1625	2.50	MC1496	1.44

TRANSISTORS - New lower prices, wider range, large stocks. Also the world's lowest noise audio devices (2SC2546E and 2SA1084E) first from AMBIT of course. Power MOSFETs & all sorts of other devices. Our 3SK51 MOSFET replaces the 408XX and 40673 families.

BC237-8-9	0.092	2SC1775	0.207	2SA1084E	0.368	BF256	0.437	BFY90	1.03
BC237-8-9	0.092	2SA872A	0.207	2SC2547E	0.391	2SK55	0.368	BFY224	0.253
BC413-5	0.116	2SD666A	0.345	2SA1085E	0.391	2SK168	0.402	BFY274	0.207
BD414-6	0.126	2SB666A	0.345	2SK133	6.32	3SK51	0.62	BFY95	1.138
BC546-556	0.138	2SD760	0.52	2SK48	8.32	3SK60	0.667	VN66AF	1.092
BC550-560	0.138	2SB720	0.52	2SK135	7.29	BF960	1.426	2N4427	0.977
BC639-640	0.265	2SC2546E	0.368	2SK150	7.29	3SK48	1.426	J176	0.747

RADIO CONTROL: A special section for all RC fans. New and exciting stuff: KB4445/KB4446 - complete 4 channel RX/TX dig.prop IC pair RF&control in one 4.75p MSL9362/MSL9363 - logic section of a four channel dig.prop link, with switch opt. 3.75p NE5044 - Signetics versatile 7 channel encoder, suitable for mixing etc. £2.14 ea NE544 Signetics famous servo driver IC £2.07 MC3357P as used in RCME design £3.16 ea AMBIT RCRX4 - RCME FM system compatible, complete RX kit with box/connector and AMBIT design screened front end with 27MHz ceramic filter £16.10 (kit) XTALS: FM pairs £3.74 (no splits) TX is fund. 1/2 op frequency, RX 3rd OT-455kHz AM pairs £3.57 (no splits). Both 3rd OT types, again RX IF at 455kHz

CATALOGUES 60p ea, all three for £1.60  
PRICES SHOWN HERE INCLUDE VAT  
POST/PACKAGE CHARGE NOW 35p

### MODULE NEWS


We are at last able to quote for quantities of our modules, following a program of standardization and revision to speed manufacture and test. The following types are the results of the standardization program:

UM1181	5 varicap MOSFET input VHF band 2 tunerhead	£12.00 inc
911225 A	High Performance FM IF system, with switched BW	£23.95 inc
911225 B	Single BW filters, single tuned detector	£14.95 inc
91072 A	DC tuned and single pole switched MW LW tuner	£14.43 inc
91072 B	As type 'A' but with either SW1 or SW2 band	£15.90 inc
92242 A	Combined LW/MW tuner, with FM IF detector section	£29.00 inc
92242 B	As 92242A but with 5-10MHz SW section	£34.00 inc

All are supplied housed in screened metal cases 97x56x24mm, with all connections along a single edge, suitable for verticle or horizontal mounting.

Previously advertized units are still available - although there may have been some price changes in the latest edition of the Price List (Date Feb.80). A separate leaflet covering the new range of modules is available from April 80, with an A4 SAE please.

NEW LINE: ALPS switches and rotary potentiometers. With a general catalogue that's over 3 inches thick, we cannot begin to offer a comprehensive list of what we can offer - but we are already stocking the keyboard switches, keyswitches, pushbutton switches etc. In particular, the pushbutton switches really put all others in the shade (shadow?) when it comes to quality and price. A special new shortform is being prepared (and may be ready when you read this). All the potentiometers and switches you could ever need from a single source. Keypad switches cost as little as 15p ea (1 off), with a range of two part caps for easy ledging. You must see the shortform catalogue (30p) and our new pricelist for full details of this huge range of components

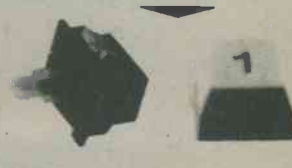

Keyboard switch  
SCK41505  
typ 6m ops  
23p each (1-24)

### AMBIT SHOP NOW OPEN

We are gradually getting our caller sales area sorted out, with displays of the products on offer and a browsers corner to sit and study data/catalogues. Call in next time you are in the area - parking outside the door.

### COMPUTER CAPABILITIES

Ambit has been keeping a low profile on the subject of the MPU and its applications. Interestingly enough, the first project we offer with MPU content does rather more in the way of processing than simply playing a daft game, or looking like an enormous calculator. Our MPU facility and expertise is now for hire on a fully commercial basis. Z80, 6800, 6809, 2650 etc.



NEW LINE: DC/OC+AC converters for fluorescent displays. TOKO CPS series 12v IN, -20 and 3v AC out at 65mA. Thick film design £2.34 ea Qty. prices OA



### GENERAL INFORMATION

Ambit stocks the following ranges of components for ex-stock volume delivery: SIGNAL COILS, CERAMIC, MECHANICAL and CRYSTAL FILTERS. RADIO ICs for AM/FM/SSB, TOROID CORES FOR RADIO and EMI FILTER CIRCUITS, INICATING ANO PANEL METERS, AUDIO ICs, RF TRANSISTORS, FETS, MDSFETS, OIGOES (PIN, VARICAP, SCHOTTKY), PASSIVE OBM (like MD108 etc), IC SOCKETS, LEDS, TRIMMER CAPS, SWITCHES, KEYBOARD SWITCHES, TUNERHEADS, IF AMPS, AM RADIO MODULES, etc etc

NEW LINE: DVM176 - the definitive ICM7106 LCD DVM module. 3 1/2 digit £22.37 ea.

CM161: LCD 12/24hr alarm clock/day/date/backlight (eq.RS308-499) 7mm digits £11.44 each  
CM174: LCD 12hr alarm clock/stopwatch/backlight with 30mm height digits £14.32 each

**ambit**  
INTERNATIONAL

CWO PLEASE: Commercial MA terms on application  
Goods are offered subject to availability, prices subject to change - so please phone and check if in doubt.

200 North Service Road, Brentwood, Essex

TELEPHONE (STD 0277) 230909 TELEX 995194 AMBIT G POSTCODE CM14 4SG

# MAPLIN

## ELECTRONIC SUPPLIES




### PRINTED CIRCUIT DRILLS

Miniature 12V DC drills designed for drilling pcb's. Small drill: Order as BW03D Price £6.75. Large drill: Order as BW02C Price £10.83


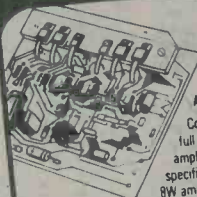
### ANTI-STATIC MAT & GUN

Turntable mat removes static from discs while they are playing. Order as LX10L Price £2.95. Gun removes static charge from discs. After use dust no longer clings and may be easily brushed off. Order as LX04E Price £4.99



### AMP KITS

Complete kits of parts with full instructions to make hi-fi amplifiers with excellent specifications.

8W amp kit: Order as LW35P Price £3.83. 50W amp kit: Order as LW35Q Price £13.73. 150W amp kit: Order as LW32K Price £14.89



### HEADPHONES

High quality stereo headphone with large padded headband and slider volume controls. Order as WF14Q Price £7.99




### CONDUCTIVE PAINT

Repair pcb's, car demisters, etc., with this silver paint. Phial contains 3gm. Order as FY72P Price £2.69


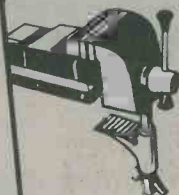
### McKENZIE POWER SPEAKERS

High quality, high power speakers. 12in. 50W 8Ω Order as XQ79L Price £18.79. 12in. 50W 16Ω Order as XQ80B Price £18.79. 12in. 80W 8Ω Order as XQ81C Price £26.32. 12in. 80W 16Ω Order as XQ82D Price £26.32. 15in. 150W 8Ω Order as XQ83E Price £57.80. 15in. 150W 16Ω Order as XQ84F Price £57.80



### MINIATURE VICE

Small modellers vice in tough plastic with metal faced jaws. Clamps to bench. Jaws width 41mm, maximum opening 30mm. Order as FY53H Price £2.78



### 20,000 OHM/VOLT MULTIMETER

A 20,000 ohms per volt multimeter at an incredibly low price. DC volts 5, 25, 125, 500, 2,500; AC volts 10, 50, 250, 1,000; DC amps 0 to 0.05mA, 0 to 250mA; Resistance 0 to 50k, 0 to 5M ohms; Decibels -20 to +22dB. Complete with test leads, battery and instruction leaflet. Order as YB83E Price £13.70



### ELECTRET MICROPHONES

Super quality genuine electret microphones operating on 1.5V battery (HP7 type) supplied. Cassette type with miniature jack plugs. Order as YB33L Price £3.84. Omnidirectional low-cost with standard jack plug. Order as YB34M Price £3.75. Unidirectional 600Ω with standard jack plug. Order as YB35Q Price £9.75. Unidirectional 600Ω/150kΩ dual with standard jack plug (pictured). Order as WF34M Price £16.77



### WIRING TOOLS

Miniature box-jointed wiring pliers with insulated handles and return spring. Order as BR68A Price £4.52. Miniature box-jointed side-cutters with insulated handles, return spring and precision cutting edges. Order as BR70M Price £4.45. End action wire strippers, fully adjustable, insulated handles. Order as BR76H Price £5.85



### CLOCK MODULE

Module requires only transformer and two push switches to

operate 4-digit, 0.7in red LED display. Alarm and radio outputs. Battery back-up when mains fail. Sleep and snooze timer. Seconds display. Just add speaker for alarm tone. Full details on page 267 of our catalogue. Order as XL14Q Price £8.41



### MEGAPHONE

High quality megaphone with differential microphone. Requires eight HP11 batteries (not supplied). Shoulder strap for portable operation. Order as XQ72P Price £49.50




### DEMAGNETISER

Tape head demagnetiser with curved probe ideal for cassette tape heads. Cures hiss due to permanently magnetised heads. Amazing low price. Order as FO62S Price £4.15


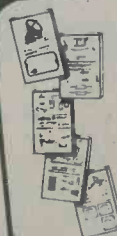
### CAR AERIAL BOOSTER

High gain car aerial booster for long, medium, short and VHF bands. Negative earth cars only. Very easy to fit - just plugs in plus one wire to +12V. We have measured gains of 20dB at 90MHz! Order as XX37S Price £5.93



### TEACH YOURSELF ELECTRONICS

There is no better way of learning basic electronics than by practical experience and this set of books is undoubtedly the very best basic course for doing just that. Set of five Basic Electronics books. Order as XX10L Price £8.30



### MULTIMETER & TRANSISTOR TESTER

Superb high sensitivity multimeter and transistor tester in one. Sensitivity 100,000 ohms per volt DC. Ranges DC volts 0.5, 2.5, 10, 50, 250, 1,000; AC volts 5, 10, 50, 250, 1,000; AC current 0.01, 0.025, 0.5, 5, 50, 500mA, 10A; AC current 10A; Resistance 5k, 50k, 5M, 50M ohms; Decibels -10dB to +62dB. Complete with test leads, three leads for transistor tester batteries and instruction leaflet. Order as YB87U Price £39.30



### TURNTABLES

Autochanger complete with stereo ceramic cartridge and circuit to make a complete low cost record player ideal for the young pop fan.

Order as XQ00A Price £18.48. Single play nm drive turntable with stereo ceramic cartridge. Order as XB23A Price £24.79. Single play belt drive turntable 'S'-shaped tone arm. Order as XB25C Price £30.63



### TRANSISTOR TESTER

Accurate transistor tester measures dynamic gain, identifies unknown transistors, also ideal for matching transistors into pairs. Order as LH05F Price £12.28



### QUICKTEST

A safe and quick way to connect to the mains. Just snap the wires under the sprung keys and close the lid. Completely safe both open and closed. Order as YB21X Price £6.54

All prices include VAT and postage and packing, but if total under £4 please add 30p handling charge. Prices guaranteed until 1 May 8th 1980. Export customers deduct 13% and export postage will be charged extra at cost.

Please use order code. All items in stock at time of going to press.

FOR FULL CATALOGUE DETAILS SEE BACK COVER

# MAPLIN

## ELECTRONIC SUPPLIES LIMITED

All mail to PO Box 3, Rayleigh, Essex SS6 8LR. Telephone: Southend (0702) 554155. Shop: 284 London Road, Westcliff-on-Sea, Essex (closed on Monday). Telephone: Southend (0702) 554000.

ALL PRICES INCLUDE V.A.T. AND P. & P.

**AXIAL CAPACITORS**

1/25v	4p	150/25v	6p
2.2/63v	4p	160/25v	6p
3.3/50	4p	220/16v	8p
4.7/40v	4p	220/25v	8p
10/25v	4p	220/63v	9p
15/16v	5p	330/10v	9p
22/10v	5p	330/25v	9p
22/16v	5p	330/63v	12p
22/25v	5p	470/6.3v	9p
33/35v	5p	470/16v	12p
33/50v	5p	470/40v	15p
47/25v	5p	680/6.3v	12p
47/16v	5p	1000/6.3v	15p
47/50v	6p	1000/16v	20p
100/10v	5p	1500/25v	20p
100/16v	5p	2200/10v	20p
100/63v	8p	3300/16v	25p

**RADIAL CAPACITORS**

.47/50v	4p	220/50v	9p
1/50v	4p	220/63v	9p
2.2/25v	4p	330/10v	8p
10/40v	4p	330/25v	8p
10/50v	5p	330/50v	9p
15/16v	5p	330/63v	9p
22/25v	5p	470/6.3v	8p
22/50v	6p	470/16v	9p
33/63v	6p	470/25v	10p
47/16v	6p	1000/16v	20p
47/35v	6p	1000/25v	21p
100/35v	6p	2200/10v	23p
220/16v	8p	2200/10v	23p
220/40v	8p	3300/6.3v	24p

**C280. POLYESTER CAPACITORS**

.01uF	4p	.15uF	6p
.015uF	4p	.22uF	6p
.022uF	4p	.33uF	6p
.033uF	4p	.47uF	8p
.047uF	4p	.68uF	12p
.068uF	5p	.68 F 630v	15p
.1uF	5p	1.0uF	15p

**AXIAL POLYESTER**

.001uF	400v...3p	.047uF	160v.....4p
.0015uF	400v...3p	.1uF	160v.....5p
.0022uF	160v...3p	.1uF	400v.....5p
.0022uF	400v...3p	.15uF	160v.....6l
.0027uF	400v...3p	.18uF	160v.....6p
.0068uF	400v...3p	.22uF	160v.....6p
.01uF	160v...4p	.22uF	400v.....6p
.022uF	160v...4p	.47uF	400v.....8p
.033uF	400v...4p	1uF	160v...15p
.039uF	400v...4p		

**CERAMIC DISC**

.047 24v 9mm dia	3p
.1uF 30v 13mm dia	5p

**CAN CAPACITORS**

1250/50v.....	50p	10,000/10v.....	60p
2500/35v.....	70p	15,000/10v.....	60p

**TANTALUM BEAD**

22/35v.....	8p	10/16v.....	11p
33/35v.....	8p	15/16v.....	14p
47/35v.....	8p	22/6.3v.....	14p
2.2/35v.....	8p	47/16v.....	16p
4.7/25v.....	11p	100/3v.....	16p
6.8/35v.....	11p		

**HIGH VOLTAGE CAPS**

Polystyrene	.1uF 10% 1000v	.....8p
Paper	.1uF	10% 1000v .....10p

**DISPLAYS**

TLR302 .3 inch Common Cathode	70p
TLR308 .6 inch Common Anode	£1.10
DL500 .5 inch Common Cathode	75p
FND507 .5 inch Common Anode	£1.20
Red L.E.D's .2 inch	8p
Green L.E.D's .2 inch	12p

**DIODES**

IN914.....	3p	IN4006.....	6p
IN4001.....	4p	IN4150.....	3p
IN4002.....	4p		
IN4003.....	5p	IN4148.....	2p
IN4004.....	5p	OA91.....	4p
IN4005.....	6p	OA200.....	6p

**LINEAR I.C.'s**

LM380.....	50p	TBA820.....	70p
LM741.....	19p	TCA270SQ.....	55p
NE555.....	22p	SN70613N.....	£1.20
CA1310Q.....	£1.20	SN76023N.....	£1.20
CA3089Q.....	75p	SN76033N.....	£1.20
TAA350.....	£1.00	SN76110N.....	75p
TBA120A.....	50p	SN76131N.....	£1.30
TBA120S.....	70p	SN78660N.....	75p
TBA800.....	70p	711.....	40p

**SUB-MIN PRESETS**

Horizontal:  
100Ω, 220Ω, 470Ω, 1k, 1k5, 2k2, 4k7, 10k, 47k, 100k.  
Vertical:  
470Ω, 2k2, 4k7, 47k.  
All price 5p each

**SWITCHES**

Push to make switches 16p  
Sub-min DPDT Slide switches 14p  
Standard DPDT Slide switches 12p  
Standard DPDT Toggle switches 49p  
Rotary switches 1p 12w, 2p 6w, 3p 4w, 4p 3w All 41p each

**VARIOUS ITEMS**

P.C. Board  
Approx. 2½" x 8½" 10p  
Approx. 4½" x 9" 25p  
Etch Resist Pen 85p  
PP3 battery clips 6p  
PP9 battery clips 14p  
Din Plugs 5 pin 180° 10p  
Din Sockets 5 pin 180° 10p  
Standard metal type 10p  
Green Phono Plugs 6p  
Latch switches 2p 2w 10p  
20mm chassis mounting fuseholders 6p

**SPECIAL OFFER**

(While stocks last)

100	IN4001	£3.00
100	IN4003	£3.50
100	IN4005	£4.00
100	IN4006	£4.00
100	BC107	£7.50
100	BC109	£7.50
100	BC183L	£5.50
25	High Quality CA741 8 pin (metal can)	d.i.l. £3.25
IN148	100 off	£1.75
	1000 off	£15.00

**TTL**

7400	10p	7474	23p
7401	12p	7475	24p
7402	12p	7476	19p
7404	12p	7485	50p
7405	12p	7486	21p
7406	25p	7489	£1.25
7408	14p	7490	32p
7409	14p	7491	30p
7410	10p	7492	30p
7411	15p	7493	25p
7412	16p	7494	43p
7414	42p	7495	37p
7416	22p	74107	20p
7420	12p	74121	26p
7421	20p	74122	34p
7427	20p	74123	42p
7430	13p	74132	48p
7432	17p	74141	56p
7437	18p	74151	38p
7438	19p	74153	38p
7440	12p	74154	60p
7441	50p	74160	45p
7442	38p	74164	60p
7448	51p	74174	55p
7447	43p	74175	55p
7450	12p	74192	48p
7451	12p	74193	48p
7470	26p	74194	43p
7472	22p	74198	48p

**CMOS**

4000	15p	4027	48p
4001	18p	4028	78p
4002	15p	4030	48p
4006	91p	4035	93p
4007	15p	4040	80p
4008	78p	4041	80p
4009	41p	4042	76p
4010	36p	4043	78p
4011	19p	4044	78p
4012	15p	4046	£1.10
4013	42p	4049	42p
4014	73p	4050	42p
4015	70p	4052	65p
4016	40p	4053	65p
4017	76p	4066	48p
4018	78p	4068	15p
4019	43p	4069	15p
4020	80p	4070	22p
4021	80p	4071	20p
4022	85p	4072	20p
4024	64p	4078	20p
4025	15p		

**TRANSISTORS**

AD161/		BD116	45p
162 MP	75p	BD131	30p
OC36	47p	BD183	90p
BC107	9p	BF185	19p
BC107B	10p	BF194	12p
BC108	9p	BF195	12p
BC108A	10p	BF198	12p
BC108C	11p	BF200	25p
BC109	9p	BF240	8p
BC109C	11p	BF241	7p
BC142	21p	BF244	14p
BC147	7p	BF245	14p
BC148	7p	BF255	10p
BC149C	8p	BF336	16p
BC149S	9p	BFX88	28p
BC153	8p	BFY50	15p
BC154	8p	BFY51	20p
BC171B	10p	BSX21	10p
BC172B	10p	BU208	90p
BC182L	9p	BF256	15p
BC183A	10p	TIP29	38p
BC183L	8p	TIP30	38p
BC207B	11p	TIP31A	45p
BC212L	10p	TIP32A	45p
BC213LB	10p	TIP32B	31p
BC308	10p	TIP41A	65p
BC338	10p	TIP42A	65p
BC455	7p	2N2905	20p
BC456	9p	2N2906	16p
BC547	11p	2N2907	18p
BC548	9p	2N3055	45p
BC549	9p	2N3702	9p
BCY70	11p	2N3703	9p
BCY72	12p	2N3704	9p
BCY79	12p		

SAME DAY SERVICE

QUALITY COMPONENTS

Write or telephone for free pamphlet

**HARRISON BROS. P.O. Box 55, Westcliff-on-Sea**  
**Essex SS0 7LQ**

Telephone: Southend-on-Sea (0702) 32338

**TRADE ENQUIRIES WELCOME**

# BI-PAK

# SEMICONDUCTORS

DEPT. RC4, PO Box 6 WARE, HERTS.

Visit our Shop at: 3 Baldock Street, Ware, Herts.

TEL: 0920 3182

TELEX: 817861

### CERAMIC PAK

16160 - 24 - 3 of each value - 22pf  
27pf 33pf 39pf 47pf 68pf 82pf £0.69  
16161 - 24 - 3 of each value - 100pf  
120pf 150pf 180pf 220pf 270pf 330pf  
390pf £0.69  
16162 - 24 - 3 of each value - 470pf  
560pf 680pf 820pf 1000pf 1500pf  
2200pf 3300pf £0.69  
16163 - 24 - 3 of each value - 4700pf  
6800pf 01uf 015uf 022uf 033uf  
047uf £0.69

### ELECTROLYTIC PAKS

A range of paks each containing 18  
first quality, mixed value miniatures

16201 - 47mFD-10mFD £0.69  
16202 - 10mFD-100mFD £0.69  
16203 - 100mFD-680mFD £0.69

### CARBON RESISTOR PAKS

16213 - 60 mixed 1/4w 100 ohms - 820  
ohms £0.69  
16214 - 60 mixed 1/4w 1K ohms - 82K  
ohms £0.69  
16215 - 60 mixed 1/4w 10K ohms - 83K  
ohms £0.69  
16216 - 60 mixed 1/4w 100K ohms -  
820K ohms £0.69  
16217 - 40 mixed 1/4w 100 ohms - 820  
ohms £0.69  
16218 - 40 mixed 1/4w 1K ohms - 82K  
ohms £0.69  
16219 - 40 mixed 1/4w 10K ohms - 82K  
ohms £0.69  
16220 - 40 mixed 1/4w 100K ohms - 820K  
ohms £0.69  
16230 - 80 mixed 1/4w 1 Meg 10 Meg  
ohms £0.69  
16231 - 40 mixed 1/4w 1 Meg - 10 Meg  
ohms £0.69

### COMPONENT PAKS

16164 - 20 Resistor mixed value approx  
(Count by weight) £0.69  
16165 - 150 Capacitors mixed value  
approx (Count by weight) £0.69  
16166 - 80 Precision resistors. £0.69  
values  
16167 - 80 1/4w resistors. Mixed  
values £0.69  
16168 - 5 pieces assorted ferrite  
rods £0.69  
16169 - 2 Tuning gangs MW LW  
VHF £0.69  
16170 - 1 Pack wire 50 metres  
assorted colours single strand £0.69  
16171 - 10 Reed switches £0.69  
16172 - 3 Micro switches £0.69  
16173 - 15 Assorted pots £0.69  
16174 - 5 metal jack sockets 3 x  
3.5mm 2 x standard switch types £0.69  
16175 - 30 Paper condensers - mixed  
values £0.69  
16176 - 20 Electrolytics trans  
types £0.69  
16177 - 1 Pack assorted hardware  
Nuts, bolts, Gromets etc £0.69  
16178 - 5 Mins slide switches,  
assorted £0.69  
16179 - 20 Assorted tag strips and  
panels £0.69  
16180 - 15 Assorted control  
knobs £0.69  
16181 - 3 Rotary wave change  
switches £0.69  
16182 - 2 Relays 6-24v  
operating £0.69  
16183 - 1 Pak copper laminate approx  
200 sq inches £0.69  
16184 - 15 Assorted Fuses 100mA 5  
amp £0.69  
16185 - 50 metres PVC sleeving  
assorted size and colours £0.69

### METAL FOIL CAPACITORPAK

16204 - Containing 50 metal foil  
capacitor like Mullard C280 series -  
Mixed values ranging from 0.1uf-2.2uf.  
Complete with identification  
sheet £1.38

### SLIDER PAKS

16180 - 6 slider mixed £0.69  
16191 - 6 slider 470 ohms £0.69  
16192 - 6 slider 10K ohms 1in£0.69  
16193 - 6 slider 22K ohms 1in£0.69  
16194 - 6 slider 47K ohms 1in£0.69  
16195 - 6 slider 47K log £0.69

### TRANSISTORS

AC107	£0.28	AD182	£0.40	BC151	£0.28	BC441	£0.35	BF165	£0.85	2N1305	£0.21
AC113	£0.23	AD161/162	£0.81	BC152	£0.23	BC460	£0.44	BF167	£0.28	2N1306	£0.29
AC115	£0.23	AD1140	£0.83	BC153	£0.28	BC461	£0.44	BF173	£0.23	2N1307	£0.29
AC117	£0.35	AF124	£0.35	BC154	£0.22	BC477	£0.23	BF176	£0.44	2N1308	£0.35
AC117K	£0.39	AF125	£0.38	BC157	£0.12	BC478	£0.23	BF177	£0.30	2N1309	£0.35
AC121	£0.23	AF126	£0.38	BC158	£0.14	BC479	£0.23	BF178	£0.32	2N1711	£0.23
AC122	£0.18	AF127	£0.37	BC159	£0.12	BC547	£0.12	BF179	£0.35	2N2219	£0.23
AC125	£0.21	AF139	£0.40	BC160	£0.30	BC548	£0.12	B0239A	£0.32	2N2221	£0.23
AC126	£0.21	AF178	£0.89	BC161	£0.44	BC549	£0.12	240AMP	£1.15	2N2222	£0.23
AC127	£0.21	AF179	£0.89	BC167	£0.14	BC550	£0.18	BF180	£0.35	2N2369	£0.18
AC128	£0.18	AF181	£0.89	BC168	£0.14	BC557	£0.18	BF181	£0.35	2N2371	£0.25
AC128K	£0.30	AF182	£0.38	BC169	£0.12	BC558	£0.18	BF182	£0.35	2N2714	£0.25
AC132	£0.23	AF186	£0.58	BC169C	£0.12	BC559	£0.14	BF183	£0.35	2N2904	£0.21
AC134	£0.23	AF239	£0.44	BC170	£0.10	BC559	£0.16	BF184	£0.23	2N2905	£0.21
AC137	£0.23	AL102	£1.38	BC171	£0.10	BC559	£0.16	BF185	£0.23	2N2906	£0.21
AC141	£0.24	AL103	£1.38	BC172	£0.10	BC559	£0.16	BF186	£0.30	2N2907	£0.23
AC141K	£0.35	AU104	£1.81	BC173	£0.10	BC559	£0.16	BF187	£0.30	2N2908	£0.23
AC142	£0.23	AU110	£1.81	BC174	£0.17	BC559	£0.16	BF188	£0.30	2N2923	£0.17
AC142K	£0.35	AU113	£1.81	BC175	£0.40	BC559	£0.16	BF189	£0.30	2N2924	£0.17
AC151	£0.23	BC107	£0.09	BC176	£0.18	BC559	£0.16	BF190	£0.30	2N2925	£0.17
AC153	£0.26	BC107A	£0.09	BC178	£0.18	BC559	£0.16	BF191	£0.30	2N2926	£0.17
AC153K	£0.35	BC107B	£0.12	BC180	£0.29	BC559	£0.16	BF192	£0.30	2N2927	£0.17
AC154	£0.23	BC107C	£0.12	BC181	£0.29	BC559	£0.16	BF193	£0.30	2N2928	£0.17
AC155	£0.23	BC108	£0.08	BC182	£0.25	BC559	£0.16	BF194	£0.30	2N2929	£0.17
AC156	£0.23	BC108A	£0.08	BC182E	£0.10	BC559	£0.16	BF195	£0.30	2N2930	£0.17
AC157	£0.23	BC108B	£0.12	BC183	£0.10	BC559	£0.16	BF196	£0.30	2N2931	£0.17
AC158	£0.23	BC108C	£0.09	BC183L	£0.10	BC559	£0.16	BF197	£0.30	2N2932	£0.17
AC165	£0.23	BC109	£0.10	BC184	£0.10	BC559	£0.16	BF198	£0.30	2N2933	£0.17
AC167	£0.23	BC109C	£0.12	BC184L	£0.10	BC559	£0.16	BF199	£0.30	2N2934	£0.17
AC169	£0.23	BC113	£0.18	BC188	£0.25	BC559	£0.16	BF200	£0.30	2N2935	£0.17
AC171	£0.23	BC114	£0.18	BC187	£0.25	BC559	£0.16	BF201	£0.30	2N2936	£0.17
AC179	£0.23	BC125	£0.20	BC207	£0.18	BC559	£0.16	BF202	£0.30	2N2937	£0.17
AC178	£0.23	BC126	£0.25	BC208	£0.18	BC559	£0.16	BF203	£0.30	2N2938	£0.17
AC178	£0.23	BC132	£0.21	BC209	£0.14	BC559	£0.16	BF204	£0.30	2N2939	£0.17
AC179	£0.23	BC134	£0.21	BC212	£0.10	BC559	£0.16	BF205	£0.30	2N2940	£0.17
AC180	£0.23	BC135	£0.17	BC212L	£0.10	BC559	£0.16	BF206	£0.30	2N2941	£0.17
AC180K	£0.32	BC136	£0.21	BC213	£0.10	BC559	£0.16	BF207	£0.30	2N2942	£0.17
AC181	£0.23	BC137	£0.21	BC251A	£0.18	BC559	£0.16	BF208	£0.30	2N2943	£0.17
AC181K	£0.32	BC139	£0.37	BC251A	£0.18	BC559	£0.16	BF209	£0.30	2N2944	£0.17
AC187	£0.21	BC140	£0.35	BC301	£0.32	BC559	£0.16	BF210	£0.30	2N2945	£0.17
AC187K	£0.32	BC141	£0.32	BC302	£0.32	BC559	£0.16	BF211	£0.30	2N2946	£0.17
AC188	£0.21	BC142	£0.25	BC303	£0.32	BC559	£0.16	BF212	£0.30	2N2947	£0.17
AC188K	£0.32	BC143	£0.25	BC304	£0.32	BC559	£0.16	BF213	£0.30	2N2948	£0.17
AD140	£0.69	BC147	£0.08	BC327	£0.18	BC559	£0.16	BF214	£0.30	2N2949	£0.17
AD143	£0.69	BC148	£0.08	BC328	£0.17	BC559	£0.16	BF215	£0.30	2N2950	£0.17
AD149	£0.69	BC149	£0.08	BC337	£0.17	BC559	£0.16	BF216	£0.30	2N2951	£0.17
AD181	£0.69	BC150	£0.23	BC338	£0.17	BC559	£0.16	BF217	£0.30	2N2952	£0.17
AD189	£0.40	BC150	£0.23	BC440	£0.35	BC559	£0.16	BF218	£0.30	2N2953	£0.17

### 74 SERIES TTL IC's

7400	£0.14	7422	£0.18	7448	£0.84	7489	£1.96	74123	£0.46	74175	£0.71
7401	£0.13	7423	£0.24	7450	£0.90	7490	£2.30	74124	£0.46	74176	£0.71
7402	£0.13	7425	£1.21	7451	£0.81	7491	£0.74	74141	£0.83	74177	£0.67
7403	£0.13	7426	£0.28	7453	£0.13	7492	£0.40	74145	£0.83	74180	£1.73
7404	£0.13	7427	£0.28	7454	£0.13	7493	£0.35	74150	£0.78	74181	£0.87
7405	£0.13	7428	£0.30	7456	£0.13	7494	£0.86	74151	£0.85	74182	£0.87
7406	£0.25	7430	£0.16	7470	£0.29	7495	£0.55	74152	£0.55	74184	£0.81
7407	£0.32	7432	£0.25	7472	£0.29	7496	£0.58	74154	£0.56	74185	£0.78
7408	£0.18	7433	£0.35	7473	£0.29	74100	£0.98	74155	£0.55	74191	£0.71
7409	£0.18	7437	£0.24	7474	£0.29	74101	£0.48	74156	£0.58	74192	£0.69
7410	£0.13	7438	£0.24	7475	£0.33	74104	£0.45	74157	£0.58	74193	£0.67
7411	£0.20	7440	£0.14	7476	£0.29	74105	£0.44	74160	£0.67	74174	£0.71
7412	£0.17	7441	£0.58	7480	£0.61	74107	£0.45	74161	£0.71	74195	£0.69
7413	£0.28	7442	£0.46	7481	£0.99	74110	£0.41	74162	£0.71	74196	£1.21
7414	£0.58	7443	£0.81	7482	£0.78	74111	£0.67	74163	£0.71	74197	£1.21
7416	£0.28	7444	£0.81	7483	£0.67	74118	£0.92	74164	£0.78	74198	£2.13
7417	£0.28	7445	£0.75	7484	£1.01	74119	£1.36	74165	£0.78	74199	£2.13
7420	£0.13	7446	£0.89	7485	£0.78	74121	£0.28	74166	£0.90	74200	£1.38
7421	£0.23	7447	£0.55	7486	£0.25	74122	£0.45	74174	£0.78	74201	£1.38

### CMOS IC's

CD4001	£0.16	CD4012	£0.22	CD4021	£0.94	CD4030	£0.88	CD4045	£1.81	CD4070	£0.20
CD4001	£0.23	CD4013	£0.48	CD4022	£0.94	CD4031	£2.30	CD4046	£1.81	CD4071	£0.20
CD4002	£0.16	CD4015	£0.94	CD4023	£0.22	CD4032	£0.37	CD4047	£1.00	CD4072	£0.20
CD4006	£1.08	CD4018	£0.49	CD4024	£0.75	CD4037	£1.00	CD4048	£0.85	CD4073	£0.20
CD4007	£0.20	CD4017	£0.94	CD4025	£0.22	CD4040	£1.01	CD4050	£0.85	CD4081	£0.20
CD4008	£1.08	CD4018	£0.98	CD4026	£1.38	CD4041	£0.87	CD4051	£1.27	CD4082	£0.20
CD4009	£0.82	CD4019	£0.48	CD4027	£0.88	CD4042	£0.83	CD4052	£1.18	CD4083	£0.20
CD4010	£0.85	CD4020	£1.04	CD4028	£0.78	CD4043	£1.01	CD4053	£1.85	CD4084	£0.20
CD4011	£0.85	CD4021	£1.04	CD4029	£0.98	CD4044	£0.94	CD4059	£0.20	CD4085	£0.20


### LINEAR IC's

CA3011	£1.12	CA3090	£4.14	LM3900	£0.67	NE567	£1.96	741P	£0.23	TBA810S	£0.85
CA3014	£1.85	CA3123	£2.19	MCI303L	£0.98	UA702C	£0.63	UA747C	£0.69	TBA810	£1.13
CA3018	£0.76	CA3130	£1.07	MCI304	£2.19	UA702	£0.53	72702	£0.67	TBA820	£0.81
CA3020	£1.96	CA3140	£0.81	MCI310	£1.09	UA703	£0.29	UA748	£0.40	TBA8200	£2.88
CA3028	£0.92			MCI312	£2.19	UA709	£0.29	72748	£0.40	TC4207S	£2.30
CA3035	£1.61	LM301	£0.33	MCI350	£1.38	72709	£0.83	748P	£0.40	TBA800	£0.92
CA3036	£1.1										

# STEVENSON

## Electronic Components

### SPRING SPECIALS

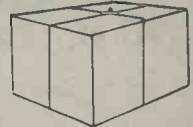

- Set of 4 AA (HP7) Rechargeable Cells . . . 500p 450p  
 PP3 Rechargeable cell . . . 450p 410p  
 Pack of 10 miniature slide switches . . . 150p 120p  
 Pack of 10 push to make switches . . . 150p 120p  
 Pack of 10 push to break switches . . . 200p 150p  
 Murata Ultrasonic Transducers, per pair . . . 350p 300p  
 Resistor Development packs.  
 10 off, each value from 4.7 ohm to 1M 1/4w 570p 500p  
 1/2w 750p 650p  
 Polyester Development packs.  
 5 off, each value from 0.01 to 3u2 . . . 620p 520p  
 Preset Potentiometer pack  
 5 off, each value 100 ohm to 1M, 65 presets 395p 305p  
 Ceramic Development pack  
 10 off, each value 22pF to 0.1uF, 310 caps. 595p 525p  
 LED pack, 10 off,  
 each type 0.2 Red, green, yellow . . . 350p 300p  
 Pack of 10 CA3080 Transconductance amps. 700p 620p  
 Pack of 10 LM301AN Op. amp. . . . 260p 230p  
 Pack of 10 LM380N 2W Audio Amp . . . 750p 620p  
 LM380 + LM381 and data . . . 235p 180p  
 Pack of 3 LM3909 LED flasher . . . 185p 150p  
 Pack of 10 TL081 Jfet Op. amp. . . . 450p 320p  
 MM57160 Stac. Timer + data . . . 690p 550p  
 SN76477 Sound generator + data . . . 240p 200p  
 Pack of 2 ZN414 AM chips . . . 160p 130p  
 SS-2 Breadboard . . . 1085p 990p  
 Expo Reliant Drill . . . 655p 570p  
 Expo Titan Drill . . . 1030p 920p  
 Drill stand for above . . . 1200p 1100p  
 Pack of 8 2708 Eprom . . . 4720p 4500p  
 Pack of 8 2114 Ram LP 300ns . . . 3425p 3000p  
 Pack of 8 4116 . . . 4560p 4300p

### CMOS

4001	20p	4020	100p	4060	120p
4002	20p	4022	100p	4066	50p
4007	20p	4023	20p	4068	20p
4009	40p	4024	50p	4069	20p
4011	20p	4025	20p	4070	20p
4012	20p	4027	45p	4071	20p
4013	35p	4028	85p	4072	20p
4015	80p	4029	85p	4081	20p
4016	30p	4040	110p	4093	50p
4017	65p	4041	85p	4510	80p
4018	90p	4042	85p	4511	90p
		4043	95p	4518	80p
		4046	110p	4520	80p
		4049	45p	4527	90p
		4050	45p	4528	90p

### MICRO

CPU'S	MEMORIES		
6800	21L02	85p	2516 2185p
8080A390p	2112	175p	2716 2185p
Z80	2114	390p	AYS-1013
	1116	570p	360p
	2708	590p	

### TTL

7400	10p	7473	20p	74145	55p
7402	10p	7474	22p	74148	90p
7404	12p	7475	25p	74150	55p
7408	12p	7476	20p	74154	65p
7410	10p	7486	20p	74157	40p
7412	12p	7488	20p	74158	55p
7414	10p	7490	25p	74164	55p
7416	10p	7492	30p	74165	55p
7418	12p	7493	25p	74174	55p
7420	12p	7494	45p	74177	50p
7422	12p	7495	45p	74190	50p
7424	12p	74121	25p	74191	50p
7426	12p	74123	38p	74192	50p
7428	12p	74125	35p	74192	50p
7430	12p	74126	35p	74193	50p
7432	18p	74132	45p	74196	50p
7434	18p	74133	45p	74197	50p

FULL DETAILS IN CATALOGUE!

### OPTO

LED's	0.125in.	0.2in	each	100+
Red	TIL209	TIL220	9p	7.5p
Green	TIL211	TIL221	13p	12p
Yellow	TIL213	TIL223	13p	12p
Clips	3p	3p		

### DISPLAYS

DL704	0.3 in CC	130p	120p
DL707	0.3 in CA	130p	120p
FND500	0.5 in CC	100p	80p

### SKTS

Low profile by Texas

8pin	8p	18pin	14p	24pin	18p
14pin	10p	20pin	16p	28pin	22p
16pin	11p	22pin	17p	40pin	32p

3 lead T018 or T05 socket, 10p each  
 Soldercon pins: 100:50p 1000:370p

### PCBS

Size in.	0.1in.	0.15in.	Vero
2.5 x 1	14p	-	Cutter 80p.
2.5 x 3.75	45p	45p	
2.5 x 5	54p	54p	Pin insertion tool 108p
3.75 x 5	64p	64p	
3.75 x 17	205p	185p	

Single sided pins per 100 40p 40p  
 Top quality fibre glass copper board. Single sided. Size 203 x 95mm. 60p each.  
 'Dalo' pens. 75p each  
 Five mixed sheets of A1fac. 145p per pack

### RESISTORS

Carbon film resistors. High stability, low noise 5%.

E12 series. 4.7 ohms to 10M. Any mix:

0.25W	each	100+	1000+
0.5W	1p	0.9p	0.8p
	1.5p	1.2p	1p

Special development packs consisting of 10 of each value from 4.7 ohms to 1 Meg-ohm (650 res) 0.5W E7.50. 0.25W E5.70.

### METAL FILM RESISTORS

Very high stability, low noise rated at 1/4w 1%. Available from 51ohms to 330k in E24 series. Any mix:

0.25W	each	100+	1000+
	4p	3.5	3.2

### POTENTIOMETERS

Preset vertical or horizontal 100ohms - 1M

Rotary 5K-2M2 Log or Lin single	28p
Rotary 5K-2M2 Log or Lin double	80p
Slide 60mm tr-zel 5K-500K Log or Lin, single	60p

Suitable knobs for above with coloured caps in red, blue, green, grey, yellow and black. Rotary controls 14p each. Slide type 12p each.

### LINEAR

THIS IS ONLY A SELECTION!

709	35p	LM308	60p	NE531	98p
741	18p	LM324	45p	NE585	23p
747	45p	LM339	45p	NE586	60p
748	30p	LM348	90p	NE587	100p
7106	850p	LM377	170p	RC4136	100p
CA3046	55p	LM378	230p	SN76477	230p
CA3080	70p	LM380	75p	TBA800	70p
LF356	80p	LM381	150p	TBA810S	100p
LM301AN	26p	LM382	120p	TBA1022	620p
		LM3900	50p	TL081	45p
		LM1458	35p	TL084	125p
		LM3909	65p	ZN414	80p
		LM3911	100p	ZN425E	390p
		MM57160	590p	ZN1034E	200p

### TRANSISTORS

AC127	17p	BC548	10p	ZTX107	14p
AC128	16p	BCY71	14p	ZTX108	14p
AC176	18p	BD131	35p	ZTX300	16p
AD161	38p	BD132	35p	ZTX500	16p
AD162	38p	BD139	35p	2N3054	50p
BC107	8p	BD140	35p	2N3055	50p
BC108	8p	BFY50	15p	2N3442	135p
BC108C	10p	BFY51	15p	2N3702	8p
BC109	8p	BFY52	15p	2N3704	8p
BC109C	10p	MJ2955	98p	2N3706	9p
BC147	7p	MPSA06	20p	2N3819	15p
BC148	7p	MPSA66	20p	2N3905	8p
BC177	14p	TIP29C	60p	2N3906	8p
BC178	14p	TIP30C	70p	2N5459	32p
BC182	10p	TIP31C	65p	2N5777	50p
BC182L	10p				
BC184	10p				
BC184L	10p				
BC212	10p				
BC212L	10p				
BC214L	10p				

### DIODES

1N914	3p	1N4006	6p
1N4148	2p	1N5401	13p
1N4002	4p	BZY88ser.	8p

ITT product  
 1N4148 - £1.40/100.

### CAPACITORS

#### POLYSTYRENE

High quality foil type. 63V working, 5% tol.

22pf to 1000pf	6p each
1500pf to 0.01uF	8p each

#### TANTALUM BEAD

0.1, 0.15, 0.22, 0.33, 0.47, 0.68, 1 & 2.2uF @ 35V . . . . . 8p  
 4.7, 6.8, 10uF @ 25V . . . . . 13p  
 22 @ 16V, 47 @ 6V, 100 @ 3V . . . . . 16p

#### MYLAR FILM

0.001, 0.01, 0.022, 0.033, 0.047, 0.068, 0.1 . . . . . 3p  
 0.068, 0.1 . . . . . 4p

#### POLYESTER

Mullard C280 series  
 0.01, 0.015, 0.022, 0.033, 0.047, 0.068, 0.1. 5p  
 0.15, 0.22 . . . . . 7p  
 0.33, 0.47 . . . . . 10p  
 0.68 . . . . . 14p  
 1.0uF . . . . . 17p

#### CERAMIC

Plate type 50V. Available in E12 series from 22pF to 1000pF and E6 series from 1500pF to 0.047uF . . . . . 2p

### MINIATURE TRIMMERS

Miniature film type, in 1.4pF - 5pF, 2pF - 22pF, 2pF - 22pF, 2pF - 10pF, 5.5pF - 65pF. 18p each

#### RADIAL LEAD ELECTROLYTIC

63V	0.47	1.0	2.2	4.7	10	5p	
				22	33	47	7p
							13p
							20p
25V	10	22	33	47			5p
							8p
							10p
							15p
							23p

### CONNECTORS

#### JACK PLUGS AND SOCKETS

2.5mm	9p	13p	7p
3.5mm	9p	14p	8p
Standard	16p	30p	15p
Stereo	23p	36p	18p

#### DIN PLUGS AND SOCKETS

2pin	7p	7p	7p
3pin	11p	9p	14p
5pin 180°	11p	10p	14p
5pin 240°	13p	10p	16p

#### 1mm PLUGS AND SOCKETS

Suitable for low voltage circuits. Red & black. Plugs: 6p each Sockets: 7p each.

#### 4mm PLUGS AND SOCKETS

Available in blue, black, green, brown, red, white and yellow. Plugs: 11p each Sockets: 12p each

#### PHONO PLUGS AND SOCKETS

Insulated plug in red or black	9p
Screened plug	13p
Single socket	7p
Double socket	10p

### SWITCHES

#### TOGGLE

Subminiature toggle. Rated at 2A. SPST 52p. SPDT 62p. DPDT 69p.

Standard type. Rated at 1.5A. SPST 34p. DPDT 48p.

#### SLIDE

Miniature	DPDT	15p each.
Standard	DPDT	16p each.

#### ROTARY

Available in 4 pole 3 way, 3 pole 4 way, 2 pole 6 way, 1 pole 12 way

Key operated switch	330p each
Miniature push to make	15p each
Miniature push to break	20p each

Rockers rated at 10A. SPST 32p each SPDT 42p each.

We now offer one of the widest ranges of components at the most competitive prices in the U.K. See catalogue for full details. We welcome callers at our shop in College Rd, Bromley, from Mon-Sat, 9am-6pm (8pm on Weds and Fridays). Special offers always available. We also provide an express telephone order service. Orders received before 5pm are shipped same day. Contact our sales office now with your requirements. TEL: 01-464 2951/5770.

Quantity discounts on any mix TTL, CMOS, 74LS and Linear circuits: 100+ 10%, 1000+ 15%. Prices VAT inclusive. Please add 50p for P & P, no charge for orders over £15. Official orders welcome. All prices valid to April 1980.

BARCLAYCARD & ACCESS WELCOME

Mail orders to: STEVENSON (Dept RE)

# 76 College Road, Bromley, Kent BR1 1DE.

Another projects book in the "110" series\*

## 110 IC timer projects for the home constructor

Jules H. Gilder

- \* Covers in detail the basic operation of the 555 timer IC that will enable you to design your own circuits using this device
- \* Divided into three sections describing the basic modes of operation as a monostable device, astable device and logic element
- \* Descriptions of applications include timer-based instruments, automotive applications, alarm and control circuits, and power supply and converter applications

1980

126 pages


£3.95

**Newnes Technical Books**  
Borough Green, Sevenoaks, Kent TN15 8PH

*\*If you are not familiar with previous books in this series for the home constructor, write to the publishers for a free colour brochure of all their hobbyist books*

## FASTER THAN A SCOPE— SAFER THAN A VOLTMETER

LOGIC MONITOR  
LM-1

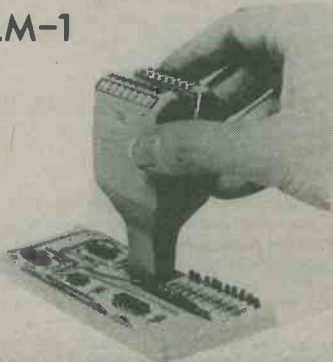

**ONLY £28.70**

plus 15% VAT, plus post and packing  
Total £34.44 including box and  
instruction manual.

CONTINENTAL SPECIALTIES CORPORATION  
**CSC**

C.S.C. (UK) Limited,  
Dept. 16S2 Unit 1, Shire Hill Industrial Estate,  
Saffron Walden, Essex CB11 3AQ  
Telephone: Saffron Walden (0799) 21682  
Telex: 817477

**Instant - simultaneous  
monitoring of the logic state  
of all IC nodes**

Just clip it over your IC.

LM-1 Instantly and accurately shows both static  
and dynamic logic states on a bright 16 LED  
display.

LM-1 finds its own power.

LM-1 cuts out guesswork, saves time, and eliminates  
the risk of short circuits.

LM-1 is suitable for all dual-in-line logic ICs.

LED on = logic state 1 (high), LED off = logic state  
0 (low), and each LED is clearly numbered 1 to 16  
in the conventional IC pattern.

**CSC**  
CONTINENTAL SPECIALTIES CORPORATION, DEPT. 16S2  
Unit 1, Shire Hill Industrial Estate, Saffron Walden, Essex.

Name .....

Address .....

QUANTITY  
REQUIRED

FREE catalogue

Tick box

I enclose cheque/PO for

LM1. £34.44

inc. p & p and VAT

£ .....

Phone your order with Access, Barclaycard or American Express

Card No. .... Expiry date. ....

### MOTORS

1.5-6VDC Model Motors 22p. Sub. Min. 'Big Inch' 115VAC 3 rpm Motors 32p. 12VDC 5 Pole Model Motors 37p. 8 track 12V Replacement Motors 55p. Cassette Motors 5-8VDC ex. equip. 70p. Geared Mains Motors (240V) 2.5 rpm 75p. 115VAC 4 rpm Geared Motors 95p.

### SEMICONDUCTORS

LM340 80p. BY103 10p. 2N5062 100V 800mA SCR 18p. BX504 Opto Isolator 25p. CA3130 95p. TBA800 50p. 741 22p. 741S 35p. 723 35p. NE555 24p. 2N3773 £1.70. AD161/2 70p. ZN414 75p. BD238 28p. BD438 28p. IN4005 10 for 35p. TIL305 alpha numeric displays £2.50. TIL209 Red Leds 8p each. 0.5" 7 segment Led display. Comm. Cathode, green, full spec. 85p each.


### PROJECT BOXES

Sturdy ABS black plastic boxes with brass inserts and lid. 75 x 56 x 35mm 65p. 95 x 71 x 35mm 75p. 115 x 95 x 37mm 85p.

### MOTOROLA PIEZO CERAMIC TWEETERS



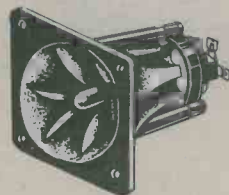2.5" Direct Radiating Tweeter, maximum rating 25 volts R.M.S. 100 watts across 8 ohms. Freq. range 3.8kHz-28kHz, £4.95.



3.5" Super Horn (flush mounting), maximum rating 25 volts R.M.S. 100 watts across 8 ohms. Freq. range 3.8-2.8kHz, £5.25.

### MORSE KEYS

Beginners practice key £1.05. All metal fully adjustable type, £2.60.

### MINIATURE LEVEL METERS

1 Centre Zero 17 x 17mm 75p. 2 (scaled 0-10) 28 x 25mm 75p. 3 Grundig 40 x 27mm £1.25.

JVC NIVICO STEREO CASSETTE MECHANISM. Music centre type. Rev. counter, remote operation £13.50 and £1.00 p&p.

### JUMPER TEST LEAD SETS

10 pairs of leads with various coloured croc clips each end (20 clips) 90p per set.

### TRANSFORMERS

All 240VAC Primary (postage per transformer is shown after price). MINIATURE RANGE: 6-0-6V 100mA, 9-0-9V 75mA and 12-0-12V 50mA all 79p each (15p). 280mA £1.20 (20p). 6V 500mA £1.20 (15p). 12V 2 amp £2.75 (45p). 15-0-15V 3 amp Transformer at £2.85 (54p). 30-0-30V 1 amp £2.85 (54p). 20-0-20V 2 amp £3.65 (54p). 0-12-15-20-24-30V 2 amp £4.75 (54p). 20V 2.5 amp £2.45 (54p).

### TRIAC/XENON PULSE TRANSFORMERS

1:1 (gpo style) 30p. 1:1 plus 1 sub. min. pcb mounting type 60p each.

### MICROPHONES

Min. tie pin. Omni, uses deaf aid battery (supplied), £4.95. ECM105 low cost condenser, Omni, 600 ohms, on/off switch, standard jack plug, £2.95. EM507 Condenser, uni, 600 ohms, 30-18kHz., highly polished metal body £7.92. DYNAMIC stick microphone dual Imp., 600 ohms or 20K, 70-kHz., attractive black metal body £7.75. EM506 dual impedance condenser microphone 600 ohms or 50K, heavy chromes copper body, £12.95. CASSETTE replacement microphone with 2.5/3.5 plugs £1.35. INSERT Crystal replacement 35X10mm 40p. GRUNDIG electric inserts with FET preamp, 3-6VDC operation £1.00.


### LIGHT DIMMER

240VAC 800 watts max. wall mounting, has built in photo cell for automatic switch on when dark £4.50

### RIBBON CABLE

8 way single strand miniature 22p per metre.

### SPECIAL OFFER TAPE HEAD DEMAGNETIZER

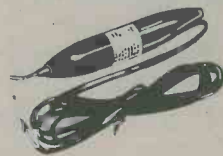

240VAC with curved probe suitable for reel to reel or cassette machines, £1.95.

STEREO FM/GRAM TUNER. AMPLIFIER CHASSIS, VHF and AM. Bass, treble and volume controls, Gram. 8-track inputs, headphone output jack, 3 watts per channel with power supply. £14.95 and £1.20 p&p (CCT supplied).

### MULTIMETER BARGAINS



Pocket Multimeter, 1,000 opv sensitivity. Ranges IKV AC/DC Volts, 150ma DC current, resistance 0-2.5K, 0-100K, £4.50.



20,000 opv., 1,000 volts AC/DC; DC current to 500ma, 5 ranges, resistance 4 ranges to 6 meg. Mirror scale, carrying handle, £9.75.

### MURATA MA401

40kHz Transducers. Rec/Sender £3.50 pair.

### TELEPHONE PICK UP COIL

Sucker type with lead and 3.5mm plug 82p.

### RELAYS

Plastic Encap. Reed Relay, 0.1 matrix. 1kΩ coil, 9-12VDC normally open, 35p. Miniature encapsulated reed relay 0.1 matrix mounting, single pole make, operates on 12VDC 50p each. Continental series, sealed plastic case relays, 24VDC 3pole change over 5 amp contacts, new 65p. Min. sealed relay, P.C. mounting, 6-9vdc operation changeover 3 amp contacts, new 85p. Metal Cased Reed Relay, 50 x 45 x 17mm, has 4 heavy duty make reed inserts, operates on 12VDC 35p each. Magnets 1/2" long 1/4" thick with fixing hole, 10 for 40p.

Dalo 33PC Etch Resist printed circuit maker pen, with spare tip, 79p.

### TERMS:

Cash with Order (Official Orders welcomed from colleges etc). 30p postage please unless otherwise shown. VAT inclusive.

S.a.b. for illustrated lists.

### AEROSOL SERVICE AIDS, SERVISOL

Switch Cleaner 226gm 80p. Freezer 226gm 70p. Silicone Grease 226gm 70p. Foam Cleanser 370gm 80p. Plastic Seal 145gm 80p. Excel Polish 240gm 47p. Aero Klene 170gm 55p. Aero Duster 200gm 70p.

### 2 METRE ANTENNA



Rubber duck type BNC termination, £3.50.

### CHIMPING TOOL

Combination type for crimping red blue and yellow terminations also incorporates a wire stripper (6 gauges) and wire cutter, with insulated handles only £2.30.

### POWER SUPPLIES

SWITCHED TYPE, plugs into 13 amp socket, has 3-4.5-6-7.5 and 9 volt DC out at either 100 or 400mA, switchable £3.45. HC244R STABILISED SUPPLY, 3-6-7.5-9 volts DC out at 400mA max., with on/off switch, polarity reversing switch and voltage selector switch, fully regulated to supply exact voltage from no load to max. current £4.95.

### AMPHENOL CONNECTORS

(PL259) PLUGS 47p. Chassis sockets 42p. Elbows PL259/SO239 90p. Double in line male connector (2XPL259) 65p. Plug reducers 13p. PL259 Dummy load, 52 ohms 1 watt with indicator bulb 95p.

### BUZZERS

MINIATURE SOLID STATE BUZZERS, 33 x 17 x 15mm white plastic case, output at three feet 70db (approx), low consumption only 15mA, voltage operating 4-15VDC, 75p each. LOUD 12VDC BUZZER, Cream plastic case, 50mm diam. x 30mm high 63p. GPO OPEN TYPE BUZZER, adjustable works 6-12VDC 27p. 12VDC siren, all metal rotary type, high pitched wail, £7.50.

### TOOLS

SOLDER SUCKER, plunger type, high suction, teflon nozzle, £4.99 (spare nozzles 69p each).

Good Quality snub nosed pliers, insulated handles, 5" £1.45.

Antex Model C 15 watt soldering irons, 240VAC £3.95

Antex Model CX 17 watt soldering irons, 240VAC £3.95.

Antex Model X25 25 watt soldering irons, 240VAC £3.95.

Antex ST3 iron stands, suits all above models £1.65.

Antex heat shunts 12p each.

Servisol Solder Mop 50p each.

Neon Tester Screwdrivers 8" long 59p each.

Miyama IC test clips 16 pin £1.95.

### SWITCHES

Sub. miniature toggles: SPST (8 x 5 x 7mm) 42p. DPDT (8 x 7 x 7mm) 55p. DPDT centre off 12 x 11 x 9mm 77p. PUSH SWITCHES, 16 x 6mm, red top, push to make 14p each, push to break version (black top) 16p each.

G.P.O. Telephone handsets £1.95. Electrolytic Caps, can type, 2,200mfd and 2,200mfd 50VDC 35p each.

### RES. SUB. BOX



Resistance Substitution Box. Swivelling disc provides close tolerance resistors of 36 values from 5 ohms to 1 meg. £3.95.



Signal Generator. Ranges 250Hz-100MHz in 6 Bands, 100MHz-300MHz (harmonics) internal modulator at 100Hz. R.F. output Max. 0.1vRMS. All transistorised unit with calibrating device. 220-240VAC operation, £48.95.

### TAPE HEADS

Mono cassette £1.75. Stereo cassette £3.90. Standard 8 track stereo £1.95. BSR MN1330 1/2 track 50p. BSR SRP90 1/2 track £1.95. TD10 tape head assembly — 2 heads both 1/2 track R/P with built in erase, mounted on bracket £1.20.

# PROGRESSIVE RADIO

31 CHEAPSIDE, LIVERPOOL 2.

ALL ORDERS DESPATCHED BY RETURN POST



# Conquer the chip.

Be it career, hobby or interest, like it or not the Silicon Chip will revolutionise every human activity over the next ten years.

Knowledge of its operation and its use is vital. Knowledge you can attain, through us, in simple, easy to understand stages.

Learn the technology of the future today in your own home.

## ELECTRONICS



Build your own oscilloscope

Learn to draw and understand circuits.

Carry out over 40 experiments.

## DIGITAL TECHNIQUES

From watches to sophisticated instrumentation, Digital Electronics adds scope to hobby or career.



## COMPUTER TECHNOLOGY


Learn to operate and programme your own home computer.


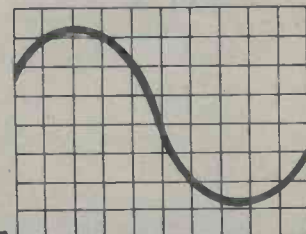
# FREE BROCHURES



No previous knowledge is necessary.  
— Just clip the coupon for a brochure



## TUTORCOURSE ELECTRONICS

Please rush me details of your ELECTRONICS COURSE

Name \_\_\_\_\_

Address \_\_\_\_\_

\_\_\_\_\_

RER/4

Block Caps. Please

Post now, without obligation to:

**British National Radio & Electronics School.**

P.O. Box 156, Jersey, Channel Isles.

# TRADE COMPONENTS

PAY A VISIT — THOUSANDS MORE ITEMS BELOW WHOLESALE PRICE. CALLERS PAY LESS ON MANY ITEMS AS PRICES INCLUDE POSTAGE. PRICES INCLUDE VAT AND ADDITIONAL DISCOUNT IN LIEU OF GUARANTEE. GOODS SENT AT CUSTOMERS RISKS UNLESS SUFFICIENT ADDED FOR REGISTRATION OR COMPENSATION FEE POST. CORRECT AT 6/3/80.

<b>CARTERS MINIMITE SIREN</b> 12/24V £6 for alarms etc.		
<b>VALVE BASES</b>		
Printed circuit B/G .....	7p	
Chassis B7-B7G .....	11p	
Shrouded Chassis B7G-B8A .....	13p	
B12A tube. Chassis B9A .....	13p	
Speaker 6" x 4" 5 ohm ideal for car radio	£1.00	
4 3/4" diam. 30 Ω	£1.75	
4" diam. 80 Ω	£1.00	
2 1/2" diam. 8 Ω	75p or 32 Ω	£1.07
<b>TAG STRIP</b>	5 x 50pF or 1000 +	
9-lay 4 1/2p	Single 2p	
	300pF trimmers	35p

Douglas 350VA Auto/transformer	£7.20
Car type panel lock and key	65p
Transformer 9V 4A	£3.30
<b>Aluminium Knobs</b> for 1/4" shaft. Approx. 5/8" x 5/8" with indicator Pack of 5	95p

JAP 4 gang min. sealed tuning condensers	40p
<b>ELECTROLYTICS</b> — Hundreds more in catalogue Value/Voltage	
Tant Bead .22, .47/35v 6p. .1, 1/35v, 47/6.3v	8p.
.22/20v, 3.3/16v, 4.7/35v, 10/25v, 22/16v	9p.
4.7/16v. 10/3v.	10p. 3.3/35v. 12p.
<b>Wire End</b>	
63v. 2.2, 3 1/2p. 4.7, 4p. 10, 33, 5p. 2.5 3p. 1.5, 22	47 6p. 68, 100, 220 8p. 150 7 1/2p. 330 9p. 470
17 1/2p. 1000 29p. 25v 6, 6.4, 10, 12, 16, 22, 25,	30, 33, 40, 47, 50, 64 4p. 100, 150, 160, 330
6p. 220 7p. 250, 300, 470 8p. 1000 11 1/2p.	22/16. 3.3/50, 10/50 4p. 100/10, 47/16 5p.
100/16 100/35, 220/16 6p. 470/6.3, 10/350	470/16 8p. 1000/16 10p. 1500/6.3 7 1/2p.
2200/10 20p. 4700/10 30p. 15/160 7p.	6800/16 46p. CANS 250/300 45p. 300/450
90p. 100/275 14p. 2000/100 82p. 1000/100	70p. 8+8/450 9p. 10,000/16 36p. 2000/50 36p.
2000+2000/50 40p. Full range in catalogue.	

**BOXES** — Grey polystyrene 61 x 112 x 31mm, top secured by 4 self tapping screws 67p. Clear perspex with sliding lid, 46 x 39 x 24mm 12p

**ABS**, ribbed inside 5mm centres for P.C.B., brass corner inserts, screw down lid, 50 x 100 x 25mm orange 69p; 80 x 150 x 50mm black £1.09; 110 x 190 x 60mm black £1.62.

**DIECAST ALI** superior heavy gauge with sealing gasket, approx 6 1/2" x 2 3/8" x 1 1/8" £1.60; 3 1/2" x 2 3/8" x 1 1/8" £1.10

**VARIABLE CAMM PROGRAMMER** 10, 12 or 15 pole 2 way, 50VAC motor — series with 1mfd, or 3k 10w or 15W pygmy bulb for mains operation. Ex equipment £3.10.

RS 100-0-100 micro amp null indicator	
Approx. 2" x 3/4" x 3/4"	£1.85

SWITCHES		
Pole	Way	Type
1	2	Flush Wall Wh. Rocker
6	2	Slide
2	1	Rotary Mains
2	Alternating	Micro with roller
4	2	Centre off 15A 250V A.C. Toggle
2	1	Toggle
1	2	Sub-Min Toggle
2	Alternating	2A Mains Push (1/4" hole)
1	3	Slide

RESISTORS	
1/4-1/2 watt 1p	
1 watt	1 1/2p
1 or 2%	1 1/2p
Up to 15W w/wound	10p, 10 same value 75p

**S.P.S.T.** 10 amp 240v. white rocker switch with neon. 1" square flush panel fitting 39p

1 pole 2-way 10 amp oblong clip in mains rocker appliance switch 36p

Standard thumb-wheel switch 0-9 in 1248N or B.C.D. or Comp. 1242 also 2p co 85p

Standard Lever Key switch D.P.D.T. locking plus D.P.D.T. and S.P.S.T. Heavy Duty non latching 73p

1 pole 2-way Micro; roller, lever or hair trigger 19p

button 15p

Push to make 15p to break 17p

4-bank of 2PCO independent 40p

5-bank of 2x2PCO, 4PCO, 6PCO, interlock plus 2PCO independent 48p

6-bank of 4x4PCO+6PCO+2PCO interlocking 58p

**COMPUTER & AUDIO BOARDS/ASSEMBLIES**

VARYING CONTENTS INCLUDE ZENER, GOLD BOND, SILICON, GERMANIUM, LOW AND HIGH POWER TRANSISTORS AND DIODES, HI STAB RESISTORS, CAPACITORS, ELECTROLYTICS, TRIMPOTS, POT CORES, CHOKES, INTEGRATED CIRCUITS, ETC.

3lb for £2.30 7lb for £4.30

RELAYS	
RS/Alma reed relay, 1K 12v or 3k Ω 18-30v d.c. coil, normally open	36p
12v d.p.c.o. heavy duty octal	£1
600 Ω 4 p/co mln sealed	75p. Base 10p.
D.I.L. 3.7-12V S.P.	£1.00

POTS	
Wirewound 38p. Log or Lin rotary 22p, or slide 30p. With switch 40p, Dual 45p	
Dual switch 55p 1.5m Edgetype 10 for 40p.	

Skeleton Presets	
Slider, horizontal or vertical standard 7p or submin 5p	

THERMISTORS and V.D.R.'s	
CZ12/2/6/11/14, KR22, KT150, VA1005/6/8/10/10/1033/4/7/8/9/1040/1053/5 / 1066/7/1074/6/7 / 1082/6/1091/6/7/8 / 1100/3/8 8602. Rod with spot blue/fawn/green.	
E299DDP120/218/224/338 / 340 / 350 / 352 / YF020 · E220ZZ/02	
KR1000 · KR150 · E23 glass bead · YG150-S534 bead · KB13 E299 DHP230, R53 Glass bead	
All 7p each	

1k horizontal preset with knob 10 for 40p	3" Tape Spools	5p
	1" Terry Clips	5p
	12 Volt Solenoid	40p
ENM Ltd. cased 7-digit counter 2 1/4 x 1 1/2 x 1 1/2 approx. 12V d.c. (48 a.c.) or mains		£1.10
Auto charger for 12V Nicads, ex-new equipment		£3.95

Miniature 0 to 5mA d.c. meter approx 7/8" diameter ..... £1.25

RS Yellow Wander Plug Box of 12 ..... 40p

18 SWG multicore solder ..... 3 1/2p foot

**SAPPHIRE STYLII.** 10 different; dual and single point, current and hard to get types. My mix £1

INDICATORS	
Bulgin D676 red, takes M.E.S. bulb	38p
12 volt, or Mains neon, red pushfit	23p
R.S. Scale Print, pressure transfer sheet	12p

<b>CAPACITORS:</b> up to 500v; Ceramic up to 4,700 pF 2p to .01 5p, to .1 5p, to .68 8p. Silver-mica up to 5000PF 5p, to .01 21p. Poly, etc. up to 999pF 3p, to .1 2p, to .27 5p, to .39 6p, to .56 9p, to .99 11p: 047/630V 11p .1, .22/900v 15p. 3/600v 4p. .97/160v 7 1/2p. 1mFd up to 250v 10p. 2.2mFd up to 100v 14p. 4/16v 25p. 4.7/63 11p, 10/100 35p. 6.8/63, 25/50 19p. 8/20v 40p. CAN 1/350 12p. 6/450 vac £1.88. 3/660 vac £1.75. 5/150 70p.
<b>Pulse Tube:</b> 8-12kV, 10, 47, 56, 82, 100, 120, 320pF 2p each. Hundreds of others in Catalogue

CONNECTOR STRIP	
Belling Lee L1469, 4 way polythene.	9p each
1 1/2 glass fuses 250 m/a or 3 amp (box of 12)	20p
Bulgin 5mm Jack plug and switched socket (pair)	40p

TV MAINS DROPPERS	
5 assorted multiple units for	45p
Reed Switch 28mm body length	5p
PP9 Battery Leads	8p
Transformers. Douglas 10-0-10V at 15A, 10A, or 7.5A. All £7.20 each.	

100pF air-spaced tuning capacitor	95p
5 1/4" x 2 1/4" Speaker, ex-equipment 3 ohm	65p
2 Amp Suppression Choke	10p
3 x 2 1/2 x 1 1/8"	5 for 35p
4 1/2 x 1 1/2 x 1 1/8"	10 for 15p
Nylon clip on MES bulb holder	4p
VALVE RETAINER CLIP, adjustable	5 for 15p
1 1/4" In-Lead Fuseholder	11p
Sub-miniature Transistor Transformer.	35p
Valve type output transformer	90p
<b>POT CORES with adjuster</b>	
LA2508 LA2519	43p per pair
<b>16 Watt Power Amp. Module</b>	
35v 1A power required, giving 16 watt RMS into 8 Ω	£3.70
<b>REGULATED TAPE MOTOR</b>	
Grundig 6V approx. 3" x 1 1/2", inc. shock absorbing carrier or Jap 9V, 1 1/2" diam.	£1.05
20mm fuse holder — chassis, 4p, panel 17p.	
Fane 8 ohm 3" sq. heavy duty communications speaker 1.60.	
RS neg. volt regulator 103, 306-099 (equiv. MPC900): 10A, 100 watt 4-30 volt. Adjustable short circuit protection.	Sacrifice at 75p

Digital count unit. Counts in steps of 1, 2, 5 or 10 with total limit switch (2 x D.I.L. BCD), reed relay remote out., ut. Mains power supply, relay and delay unit. UNUSED. £5.60

Displays on 2 Minitron. 7 segments sold separately.

**RELAY 6 amp changeover. Mains coil 1 1/8" x 1 1/2" £1.10**

200uA F.S.D. lever Meter 1 1/8" x 1 1/2" £2.27

50 Mixed Full-Spec. Marked 14-pin D.I.L. digital I.C.'s £2.00 ITC, Fairchild, Motorola

"Makeaswitch" 1p 10-way wafer 5p. Mixed pole/way 25 for £1. Wood cased 8-12V buzzer £2.60

DEAC rechargeable NICAD 450K. Capacity 6V 450 m.a.h. at 10 hour rate. Ex-new equipment £3.75

2000 DK, 6V 2A at 10 hour rate. New £9.75

2.5A r.f. thermo-couple and meter 2 1/4" square £3.86

Crouzet 30-minute timer-programmer, multi-variable contacts £7.80

ACOS DUST JOCKEY Automatic record cleaner £1.30

AUDIO LEADS  
3 pin din to open end. 1 yd. twin screened. 45p  
5 pin din. 180° to 2 ohm. .... 70p  
3 pole jack plug to tag ends 4ft. .... 45p

## BRIAN J. REED

ESTABLISHED 23 YEARS

161 ST. JOHNS HILL, BATTERSEA, LONDON SW11 1TQ  
Open 11 a.m. till 7 p.m. Tuesday to Saturday. VAT receipts on request.  
Terms: Payment with order. Telephone: 01-223 5016



# MIDLAND TRADING CO.

## GENTS MEMORY CALENDAR ALARM CHRONOGRAPH



Latest technology. Constant display of hours, minutes, sec's, weekday and snooze alarm indication. A further two optional display modes are available, one being the calendar and month, which can be increased or decreased to give the appropriate month of the year. A 1/100th sec. chronograph with split and lap mode facilities with a 12 hour capacity. A 24 hour alarm with a 10 minute snooze function is also standard to this watch. A further feature is the back light and fully adjustable stainless steel strap.

£19.95

## GENTS MULTI-MELODY CHIME ALARM CHRONOGRAPH

Latest technology. Constant display of hours, minutes, sec's, weekday, date and month, with mode and chime indication display. A musical alarm is built in and can be set to anytime within 24 hours, once activated playing the tune "Oh Suzzana". Two further alarm systems are built in (i) 24 hour alarm, (ii) countdown alarm, the watch can be set to chime on every full hour. A 1/100th sec. chronograph with split and lap mode facility is standard, the watch function may also be switched off. An excellent feature is the mineral glass face. This watch also has a battery hatch, backlight and infinite adjustable stainless steel strap.



£19.95

## GENTS CHRONOGRAPH

Probably the best looking chrono on the market. Constant display of hours, minutes, sec's, with am/pm indication, also month, date and weekday indication. 1/100th and 1/10th with split and lap mode facilities, backlight and close woven fully adjustable stainless steel strap.


SPECIAL £8.95



## GENTS FRONT BUTTON ALARM

Latest style! Constant display of hours, minutes, sec's, am/pm, weekday and alarm indication. A further two optional display modes are available. The watch comprises of 7 digits, 12 functions and is programmed to the year 2009. The alarm can be set to anytime within 24 hours and operates for 30 seconds. A backlight and a closely woven adjustable stainless steel strap highlight this extremely sleek looking watch — only 8mm thick.


£13.25

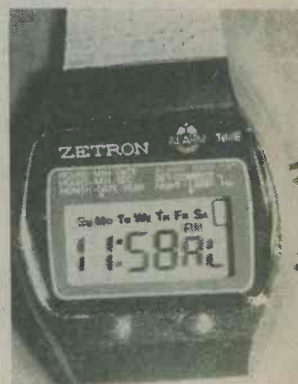

## "LADIES SUGAR COATED"

Another superb ladies watch with that extremely popular sugar frosted finish, (gold or silver finish). Links can easily be removed from the strap, and the clasp has a spring mechanism built in to give a comfortable fitting. Constant display of hours and minutes, with month, date and seconds mode. Auto calendar and backlight.

£10.50

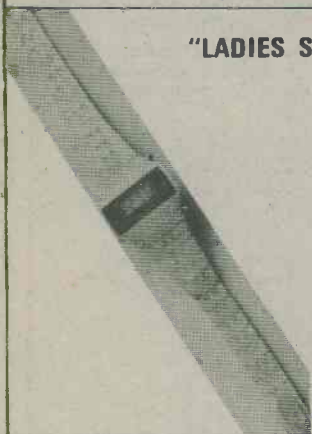

## LADIES COCKTAIL

"Elegance and Style", for the lady with a discerning taste, in gold or silver finish with matching adjustable bracelet. Constant display of hours and minutes with month date and seconds. Auto calendar and backlight.

VERY SPECIAL PRICE  
£10.50



## "ZETRON" WHERE RELIABILITY STYLE AND ELEGANCE REALLY COUNT "ZETRON"

BEFORE BUYING A DIGITAL WATCH, CONSIDER THE FOLLOWING WE OFFER:

- (i) 48 hour, display guarantee;
- (ii) Full instructions and 12 month guarantee;
- (iii) 10 day money back guarantee if not completely satisfied;
- (iv) Felt presentation case with each watch.

Phone or write for full comprehensive catalogue on the complete range of watches we carry. Huge discounts available for bulk buyers. Trade lists on application. P&P per item 75p. Cheques or P.O.'s should be made payable to Midland Trading Co; and sent to Dept.(R.E.C.), 58 Windmill Ave, Kettering, Northants NN16 8PA, — Tel: KETTERING 522024.

# GREENWELD

443G Millbrook Road Southampton SO1 0HX

All prices include VAT at 15% — Just add 40p post

## BUY A COMPLETE RANGE OF COMPONENTS AND THESE PACKS WILL HELP YOU

\*SAVE ON TIME — No delays in waiting for parts to come or shops to open!

\*SAVE ON MONEY — Bulk buying means lowest prices — just compare with others!

\*HAVE THE RIGHT PART — No guesswork or substitution necessary!

All packs contain Full Spec. Brand New, Marked Devices — Sent by return of post. V.A.T. Inclusive Prices.

K001 50V ceramic plate capacitors, 5%, 10 of each value 22pF to 1000pF. Total 210. £3.69.  
K002 Extended range. 22pF to 0.1uF. 330 values £5.53  
K003 Polyester capacitors, 10 each of these values: 0.01, 0.015, 0.022, 0.033, 0.047, 0.068, 0.1, 0.15, 0.22, 0.33, 0.47uF. 110 altogether for £5.07  
K004 Mylar capacitors, min. 100V type 10 each all values from 1000pF to 10,000pF. Total 130 for £4.05  
K005 Polystyrene capacitors, 10 each value from 10pF to 10,000pF. E12 series 5% 160V. Total 370 for £12.67  
K006 Tantalum bead capacitors, 10 each of the following: 0.1, 0.15, 0.22, 0.33, 0.47, 0.68, 1, 2.2, 3.3, 4.7, 6.8, all 35V; 10/25, 15/16, 22/16, 33/10, 47/6, 100/3. Total 170 for £14.56  
K007 Electrolytic capacitors 25V working, small physical size, 10 each of these popular values: 1, 2.2, 4.7, 10, 22, 47, 100uF. Total 70 for £3.59  
K008 Extended range, as above, also including 220, 470 and 1000uF. Total 100 for £8.05  
K021 Miniature carbon film 5% resistors, CR25 or similar, 10 of each value from 10R to 1M, E12 series. Total 610 resistors. £6.15  
K022 Extended range, total 850 resistors from 1R to 10M £8.50  
K041 Zener diodes, 400mW 5% BZY88 etc. 10 of each value from 2.7V to 36V, E24 series. Total 280 for £16.37  
K042 As above but 5 of each value £9.31

### £1 BARGAIN PACKS

K101- 16 BC239B N.P.N. Low Noise £1.00  
K102- 15 BC349B N.P.N. Low Noise £1.00  
K103- 10 BC546B N.P.N. 80 Volt £1.00  
K104- 18 BC182B N.P.N. 60 Volt £1.00  
K105- 50 IN4148 Silicon Diode £1.00  
K106- 18 BC184L N.P.N. Low Noise £1.00  
K107- 18 BC213L P.N.P. General Purpose £1.00  
K108- 8 2N5060 30N .8A SCR £1.00  
K109- 15 BC114 N.P.N. Low Noise £1.00  
K114- 15 XK6116 (BF241) N.P.N.-200 MHz £1.00  
K115- 18 SP1218 (2N3702) P.N.P. Gen. Purpose £1.00  
K117- 10 BF450 P.N.P. T.V. IF Amp. £1.00  
K118- 18 ME4101 N.P.N. 60V Low Noise £1.00  
K124- 50 .02uF Disc C-Funics £1.00  
K121- 200 1k 5% 1/4W. CF Resistors £1.00

### VU METERS

Voo2 Twin type, 2 meters 40x40mm and driver board, supplied with circuit and connexion data. £3.50  
Voo3 New type, just in. Twin type moulded in one piece, 80x40mm (No driver board but suitable circuit supplied) £2.50

### INVERTER

Prepare for the Power Cuts! Ready built inverter, 24V DC 290x55x37mm in, will power 6x8W fluorescent tubes. Circuit supplied. Only £2.90

## THE NEW 1980 GREENWELD CATALOGUE

### FEATURES INCLUDE:

- 60p Discount Vouchers
- Quantity prices for bulk buyers
- Bargain List Supplement
- Reply Paid Envelope
- Priority Order Form
- VAT inclusive prices

PRICE 40p + 20p POST

### VERO OFFCUTS

Packs of 100 sq ins of good size pieces about 4 x 3" in the following types:

K541 0.1" copper clad .....£1.60  
K544 0.1" plain .....£1.60

Also pieces 2½x1" — 10/£1.20 100/£9  
17x3½"x0.1" sheets — 10/£16.50

Large range of Standard Veroboard and boxes/cases in stock. Details in catalogue, 45p

**SCOOP!** Verobox type 2522, unused but has 3 ½" holes in one end and 1 ½" hole the other, so instead of £3.96, we are selling these at £1.85

### COMPONENT TRAY

Attractive yellow tray 285 x 165 x 42 mm with clear hinged lid and moveable compartments. Up to 15 can be made from dividers supplied. As an added bonus, a selection of new surplus components are included, all for the special low price of £3.95.

### SCR PANEL & REED-PANEL

Z525 contains 11 800mA 60V 2N5061 SCR's, 11 6V8 zeners, 11 1N4004 diodes + R's, C's etc. **Only £1.00.**  
Z527 2 x 6V reed relays, 6 x 2S030 or 2S230 6 x 400V recls, + R's. **Only 50p.**

### BUZZERS, MOTORS & RELAYS

Z401 Powerful 6V DC buzzer all metal construction. 50mm dia x 20mm **70p**  
Z402 Miniature type 6, 9 or 12V buzzer, only 22 x 15 x 16mm. Very neat **53p**

Z450 Miniature 6V DC motor, high quality type 32mm dia x 25mm high, with 12mm spindle. **Only £1**  
W890 DIL reed relay — SPCO 2.4V — 10V 200R coil. **Only £2.20**  
W892 Heavy duty 12V relay, ideal for car use — single 15A make contact. Coil 25R **85p**

### CLOCK CASE BARGAIN

Z472 Oval format, overall size 130x68x87mm deep, with built in stand. Rear panel drilled to accept 4 switches and alarm **60p**

### 74 SERIES PACK

Selection of boards containing many different 74 series IC's 20 for £1; 50 for £2.20; 100 for £4.

### PC ETCHING KIT MK III

Now contains 200 sq. ins. copper clad board, 1lb Ferric Chloride, DALO etch-resist pen, abrasive cleaner, two miniature drill bits, etching dish and instructions. **£4.85**

### 1A 400V RECTIFIERS

Plastic, like 1N4004, type 388F these diodes have preformed leads for horizontal mntg. (15mm FC). Supersaver price — 100 for £2.30; 500/£10 1000/£18.

### POWER DARLINGTON PAIR

Plastic power (TOP66 case) transistors type BD695A/BD696A. Just look at the spec! 70W 8A 45V — Hfs 750 at 4A! Special low price — £1.20 per pair.

### 1,000 RESISTORS £2.50!!

New stock just arrived — Carbon Film 2% and 5%, ¼W and ½W, all brand new, but have pre-formed leads, ideal for PC mntg. Enormous range of popular mixed values for just £2.50/1,000, £11/5,000 £50/25,000.

# ELECTROVALUE CATALOGUE 10

## Had yours yet?

Our computer has already selected thousands of our customers to whom our new catalogue has automatically been sent. If you would like a copy too, simply send us your name and address. It's

# FREE

(You don't even have to pay return postage)

## IT'S A GOOD DEAL BETTER FROM ELECTROVALUE

### ● We give discounts

on C.W.O. orders, except for a few items market Net or N in our price lists.

5% on orders, list value £10 or more

10% on orders list value £25 or more.

Not applicable on Access or Barclaycard purchase orders.

### ● We pay postage

In U.K. on orders list value £5 or over. If under, add 30p handling charge.

### ● We stabilise prices.

by keeping to our printed price lists which appear but three or four times a year.

### ● We guarantee

all products brand new, clean and maker's spec. No seconds, no surplus.

● Appointed distributors for SIEMENS, VERO, ISKRA, NASCOM and many others.

### OUR NEW CATALOGUE No 10

Over 120 pages. Thousands of items. Improved classification for easier selection. Valuable working information. Illustrations. Separate quick-ref price list.

# ELECTROVALUE LTD


### HEAD OFFICE (Mail Orders)

28(A) St. Judes Road, Englefield Green, Egham, Surrey TW20 0HB. Phone: 33603 (London prefix 87. STD 0784) Telex 264475.

### NORTHERN BRANCH (Personal Shoppers Only)

680 Burnage Lane, Burnage, Manchester M19 1NA. Phone: (061) 432 4945.

# LATEST BOUND VOLUME No. 32

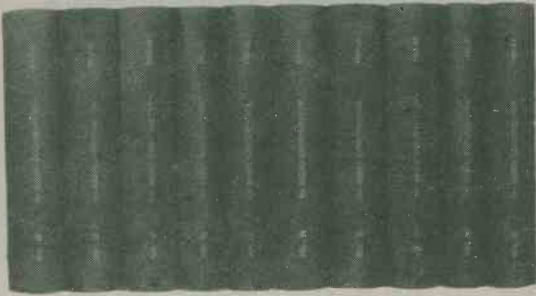

## of "Radio & Electronics Constructor"

Comprising  
776 pages  
inc. index

SEPTEMBER 1978  
to AUGUST 1979


PRICE £5.50 P&P £1.30

BOUND VOLUME No. 27 (August 1973 to July 1974)	PRICE £3.00 p&p £1.30
BOUND VOLUME No. 28 (August 1974 to July 1975)	PRICE £3.20 p&p £1.30
BOUND VOLUME No. 29 (August 1975 to July 1976)	PRICE £3.50 p&p £1.30
BOUND VOLUME No. 30 (August 1976 to July 1977)	PRICE £3.70 p&p £1.30
BOUND VOLUME No. 31 (August 1977 to August 1978)	PRICE £5.20 p&p £1.30

We regret all other volumes are now completely sold out.

Available only from:

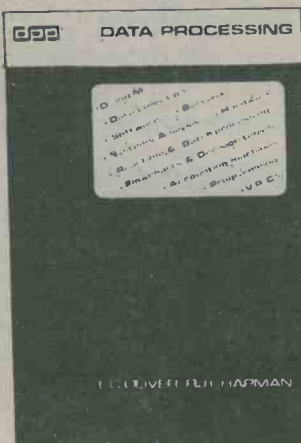**DATA PUBLICATIONS LTD., 57 MAIDA VALE, LONDON W9 1SN**



## UNDERSTAND DATA PROCESSING NEW FOURTH EDITION

DATA PROCESSING, by Oliver & Chapman, is now in  
its Fourth Edition

200 pages 9 $\frac{3}{4}$ " x 6 $\frac{3}{4}$ " **PRICE £2.75**

*P.&P. 48p*


**PUBLISHED BY D. P. PUBLICATIONS**

The primary aim of this outstanding manual is to provide a simplified approach to the understanding of data processing — (previous knowledge of the subject is not necessary).

The 40 chapters and appendices cover the following topics: Introduction to Data Processing; Organisation and Methods; Conventional Methods; Introduction to EDP and Computers; Hardware; Computer Files; Data Collection and Control; Programming and Software; Flowcharts and Decision Tables; Systems Analysis; Applications; Management of EDP, etc.

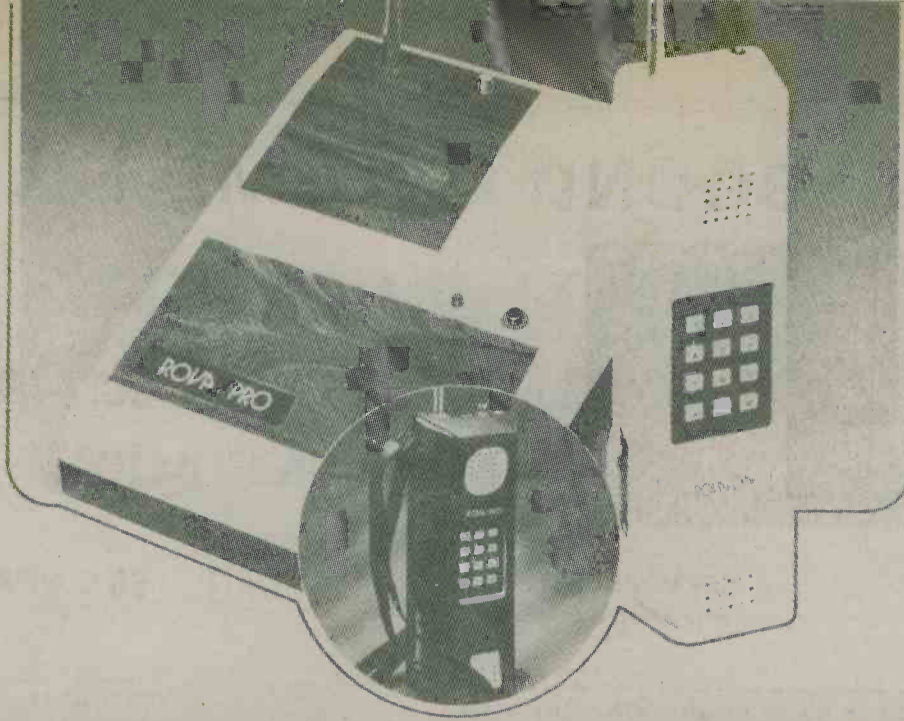**A Manual for Business and Accountancy Students**

Available from: **DATA PUBLICATIONS LTD.,  
57 MAIDA VALE, LONDON W9 1SN.**



## DIAL FREE ON A CORDLESS MOBILE EXTENSION TELEPHONE

The Parliament of The British Isles, Rovafone and a new telephone breakthrough open the door to new consumer savings.

Britain's phone system is the world's greatest. No country can compare. But what has made our phone system even greater is the recent parliamentary decision to allow consumers to plug in their own phones — phones they can buy themselves.

We will soon be able to choose which phone we want to plug in. And that creates competition, and competition usually results in lower prices, innovative products and better service.

We do now have lower prices and a very exciting new product which we have selected as the best example of the new telephone ownership decision. The big break for you is neither of these things, but something far more reaching, but more of that later.

### THE NEW PHONE

It's called the Rovafone Mobile Telephone System. And its manufacturer is a supplier of phones to other large telephone companies.

Rovafone is the Greatest innovative product of its kind in the World and of this century. . . . It's a Breakthrough in Communications for both industry and the private person.

### Why?

This solid state, microchip telephone has no cumbersome leads to cart about, is completely portable. Enables you to dial and answer calls at will up to a radius of what is an incredible 3 to 5 miles inside or outside doors . . . up to now impossible . . . from your main telephone. Whether in the garden, farm, warehouse, office, basement, at the pub or when ever you're not near your phone.

### What other features?

Takes up to 16 digit telephone numbers, has last number redial, push buttons, pager and intercom, security coded, rechargeable cells, charger, carrying case, belt clip and only weighs 28 ounces.

### THE 'DIAL FREE' KEYBOARD

The push buttons save time and money and temper. Simply key in the number as fast as you like. It goes straight into memory and is automatically dialed for you. Number engaged! Simply press Redial button and number will be recalled again automatically. Number remains in memory until updated with new number.

Push-button dialling, works

anywhere in the world, you are not charged by the telephone company for this extra service. Assuming that you have rotary dial service at present, you are actually able to Push-Button Dial for FREE!

**Base Station** only item to connect. Simply attach two wires to your telephone line, and you don't have to disconnect present phone (still operational). You're on the Air within seconds ready to go. And since Rovafone operates like a phone it's very easy to use.

**Intercom and Pager.** Touch one button on the base station (base station also very compact) and Rovafone beeps and you can talk direct to any telephone on the same line as the base station. This saves you time as you are easy to locate and can take necessary action straightaway, instead of having to run backwards and forwards getting in a tiz.

**Security Access Coded.** No other mobile phone can access your telephone line unless required as Rovafone has a digital code to prevent this happening. Means complete private two way conversations.

**Rechargeable Cells.** Saves You Money. Holds a single charge for 40 hours due to a unique energy saving circuit. The charger supplied takes a mere 3-5 hours to fully charge cells and be fully operational.

**Light Weight.** Only 28 ounces and is easily hand carried, clipped to belt or just simply slung over shoulder using the black grained carrying case supplied.

**Low Price.** The Rovafone is only £364.95 complete. It will pay for itself quickly, not only in conveniences, but with savings up to £20 a month rental charges from telephone company. (Amount charged rental for Rovafone).

When you determine the true cost of telephone ownership, you compare costs over 5 years. Even a £15 charge monthly equals a staggering £900 or over twice the cost of Rovafone.

Also other mobiles with only 300 feet range, and without half the facilities of Rovafone now cost in the shops £320. Rovafone Mobile Telephone Systems are the very best and longest range units available in the

world.

We make it an attractive proposition due to our policy of fair prices and fair play. We want to make it easy for you to own a Rovafone without being cost prohibitive which is usual on launch of new technology oriented products today.

### A PERSONAL TEST

All you do is order Rovafone. They'll be in the shops next year. Or avoid the wait and order one now, directly from us.

We were the first major distributor of Rovafone Mobile systems in the UK and have delivered thousands to homes throughout the country.

Put one in now you'll really appreciate the efficiency, time saved, convenience and other savings.

If service is ever required, we have a prompt service by mail offering free replacement of system up to one year.

In our experience the only item which goes wrong are the rechargeable cells and they are easy to replace, and available.

Rovafone Mobile Telephone Systems are made to very exacting standards of reliability and workmanship. Only the very best components and chips are used in its construction. And every Rovafone goes through very tough operational tests so that it won't let you down. Every system is built to last a long time.

### TRY ONE TODAY

We urge you to at least give Rovafone a try. A complete personal test right in your own home, under everyday conditions. Order one today from Goregrange Communicators Ltd under our 30 day trial period.

Plug it in. See how nice it looks, see how easy it is to dial numbers by pressing buttons and how little space it takes up and how convenient and efficient it is.

### YOUR SILENT PARTNER

Think how much hassle Rovafone saves you by being constantly on call ever alert and forever keeping you in constant contact with the outside world at a second's notice. Find out how much better you sound at the other end. See what a great talking point it will make with your friends, colleagues and associates.

### NOW FOR THE ALL IMPORTANT BREAK MENTIONED EARLIER . . .

We Now Take A Big Risk!!! That's right! But we're so confident about Rovafone measuring up to what

you've been told, and that you'll be 100% pleased with it that we are prepared to take the risk — so this is what we propose . . .

You send us a cheque for £364.95 and for thirty days from the date you receive the complete Rovafone System, you can check it all out thoroughly in everyway at no risk whatever. And remember the 30 days only start from when you receive the system. Not before.

If you're not totally convinced after this 30-day period (which will give you a chance to put Rovafone completely through its paces) simply return the complete system to us and we'll in return refund your £364.95 in full, plus a cheque of our own to cover your postage costs incurred on returning the system to us.

You have nothing to lose except a few minutes of time and a 10p stamp cost.

To order your Rovafone Mobile Telephone System send your cheque for £364.95.

We'll send you the Rovafone, Base Station, Rechargeable cells, Charger, attractive Black grained carrying case, Belt Clip, Full instructions and One full year's guarantee covering the whole system.


Why not act ahead of the crowd and order an exciting space age way to catch those calls immediately. Order your Rovafone System at no obligation today. Please note normal range of Rovafone is one mile. For 3 to 5 miles range, special booster and compact external aerial required at £95 extra inclusive. (Ranges quoted are under optimum transmitting conditions). Remember a missed call means lost business!

Order within 7 days and receive a 'Free Gift' worth an incredible £20 and it's yours to keep whether you keep Rovafone or not.

(Ad 15% VAT to price).

To GOREGRANGE COMMUNICATORS LTD (REC)  
5 Station Parade  
Woodthorpe Road  
Ashford, Middlesex  
Phone Number 09328-60453

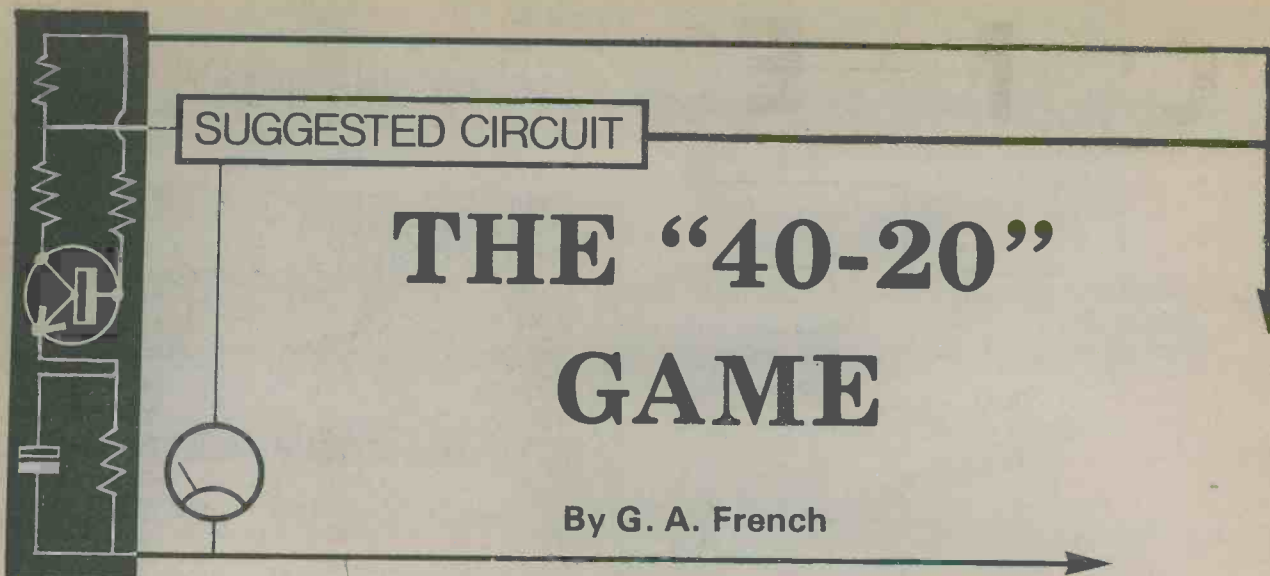100% Leasing available for Limited companies. Please phone Hamilton Leasing on FREEPHONE 3123 (Dial 100 and ask operator — call is free)



# THE "40-20" GAME

By G. A. French

A very useful CMOS integrated circuit which does not appear to have had its fair share of attention in the amateur electronic press is the CD4020. This device is a 14-stage binary counter-divider and it offers 14 divide-by-two stages, coupled internally so that one stage output feeds the following stage input. In consequence, it has the ability of dividing by 2 to the power of 14, or by 16,384.

## PIN FUNCTIONS

The pin functions of the CD4020 are illustrated in Fig. 1. Pins 16 and 8 are the usual VDD and VSS supply pins, and pin 11 is the reset pin. When taken to the positive rail, this pulls all outputs to zero regardless of whether an input is being fed to the i.c. or not. Input pulses are applied to pin 10, and divided outputs are available at all the remaining pins.

In the diagram the pin numbers are shown inside the i.c. rectangle. Each figure outside the rectangle in brackets indicates the power of 2 by which division has been made at the pin concerned and the following figure gives the resultant number in decimal. Pin 9 gives a divide-by-two function, and there are no outputs for 2 to the powers of 2 and 3. The next pin, pin 7, gives an output divided by 2 to the power of 4, or 16, and this is followed by pins which correspond to powers of 2 up to the power of 14.

To gain an idea of the manner in which the CD4020 functions, a simple test circuit can be made up in

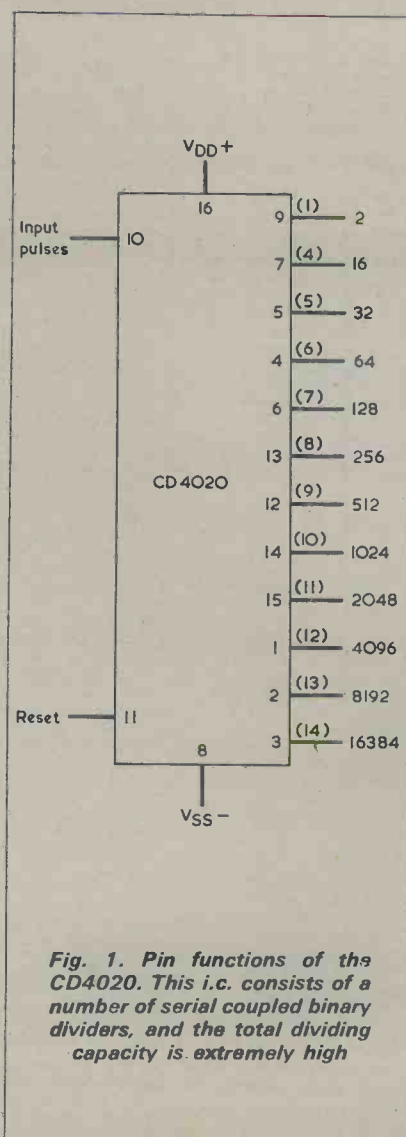


Fig. 1. Pin functions of the CD4020. This i.c. consists of a number of serial coupled binary dividers, and the total dividing capacity is extremely high

the manner shown in Fig. 2. The input pulses may be obtained from an oscillator of the type to be described later in this article, and outputs are taken from four pins giving divided outputs starting at 2 to the power of 4 and ending at 2 to the power of 7. Each l.e.d. lights up when the output to which it connects goes high.

The waveforms of the outputs are shown in Fig. 3. As is shown in this diagram, the output at pin 5 goes into transition from one state to the other with every negative-going pulse edge at pin 7. Similarly, transitions at pin 4 occur on negative-going pulse edges at pin 5, and transitions at pin 6 on negative-going pulse edges at pin 5. The same relationships between outputs would be given if we were to examine the succeeding divided outputs.

An interesting effect is that the four l.e.d.'s of Fig. 2 will count twice the number of pulses at pin 7 in binary, assuming that a lit l.e.d. corresponds to 1 and an extinguished l.e.d. to 0. At the start of the period designated "8 pulses" (or immediately after taking the i.c. out of reset) all the outputs are low, giving a binary count of 0000. The first pulse at pin 7 gives binary 0001, and when it ends the next binary count is 0010. This proceeds until the middle of the period, where 0111 gives way to 1000, and the l.e.d.'s then go through 1001, 1010, 1011, etc., until they reach 1111. After that all the l.e.d.'s extinguish, to start again at 0000.

There are a number of useful



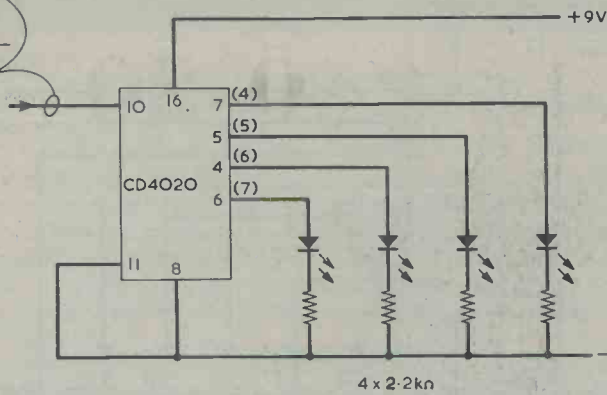
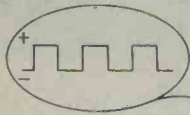


Fig. 2. A test circuit for examining the relationship between four successive outputs of the CD4020

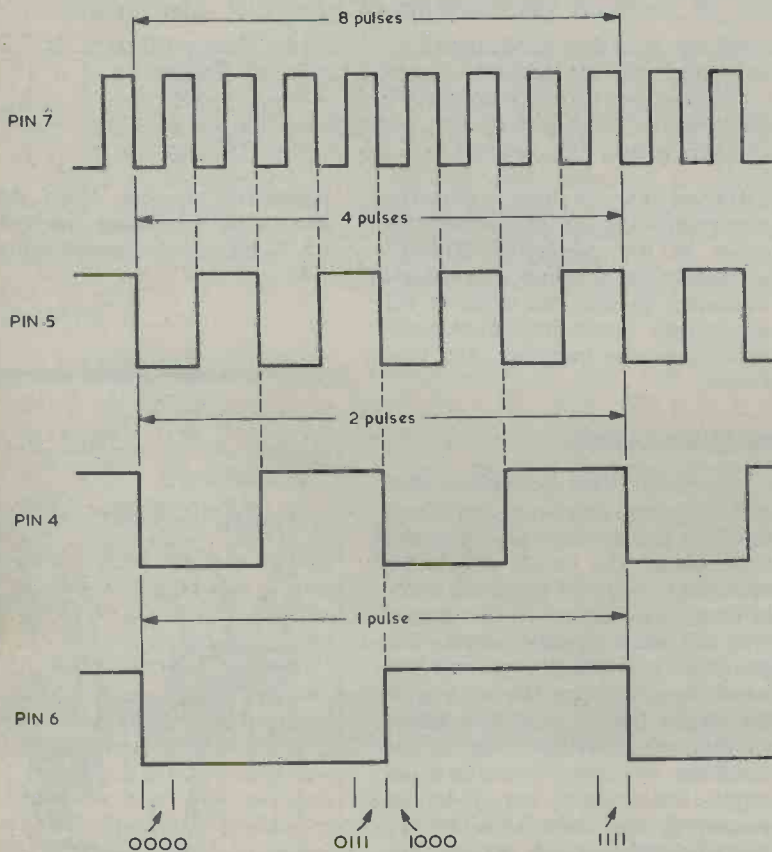


Fig. 3. The output waveforms given by the test circuit of Fig. 2. Each of the three lower waveforms goes through its transitions on the negative-going pulse edges of the preceding waveform. The waveforms also present a binary count

possibilities for which the CD4020 may be used, one of the most obvious ones being in a long-term timer. In this application, an oscillator would feed into pin 10 of the device, and the timed circuit would be activated by an output from, say, pin 3. In the present article, the CD4020 is employed in a simple electronic game in which eight successive outputs of the CD4020 are coupled to eight l.e.d.'s.


### GAME CIRCUIT

The circuit of the game is illustrated in Fig. 4, and in this an oscillator feeds the pin 10 input of the CD4020. The oscillator can be started by momentarily pressing S1, and it can be stopped by similarly pressing S2. The eight l.e.d.'s flash on and off following the pattern illustrated in Fig. 3, and the purpose of the game is to stop the oscillator at an instant when all eight l.e.d.'s are alight. A tantalising feature of the game is that all l.e.d.'s are alight only when the circuit has counted up to binary 11111111, after which all the l.e.d.'s extinguish. This binary number is equal to decimal 255, which means that, taking in the all-zeros state, there are 256 l.e.d. states of which only one is the required state.

The oscillator is given by two gates of a CD4011, the feedback loop comprising C1, R3 and R2. The oscillator is enabled when its pin 1 is high and is inhibited when this pin is low. The two lower gates of the CD4011 form a latch, giving an output at pin 11 which is taken to pin 1 of the oscillator gates. If the latch output is high, pressing S2 will immediately cause it to go low and to stay low, thereby stopping the oscillator. Pressing S1 takes the latch output high once more and allows the oscillator to start again. If both S1 and S2 are pressed at the same time, current from the 9 volt supply is limited by R1 to less than 1mA, and the "Stop" function predominates. The oscillator output passes to pin 10 of the CD4020.

A reset function is available by pressing S3, which then takes pin 11 high and sets all outputs to zero. When S3 is open, pin 11 is taken low by way of R5. The reset feature is not entirely necessary for the game application, although it allows new players to gain an idea of the manner in which the l.e.d.'s light up in turn starting from the condition in which they are all extinguished.

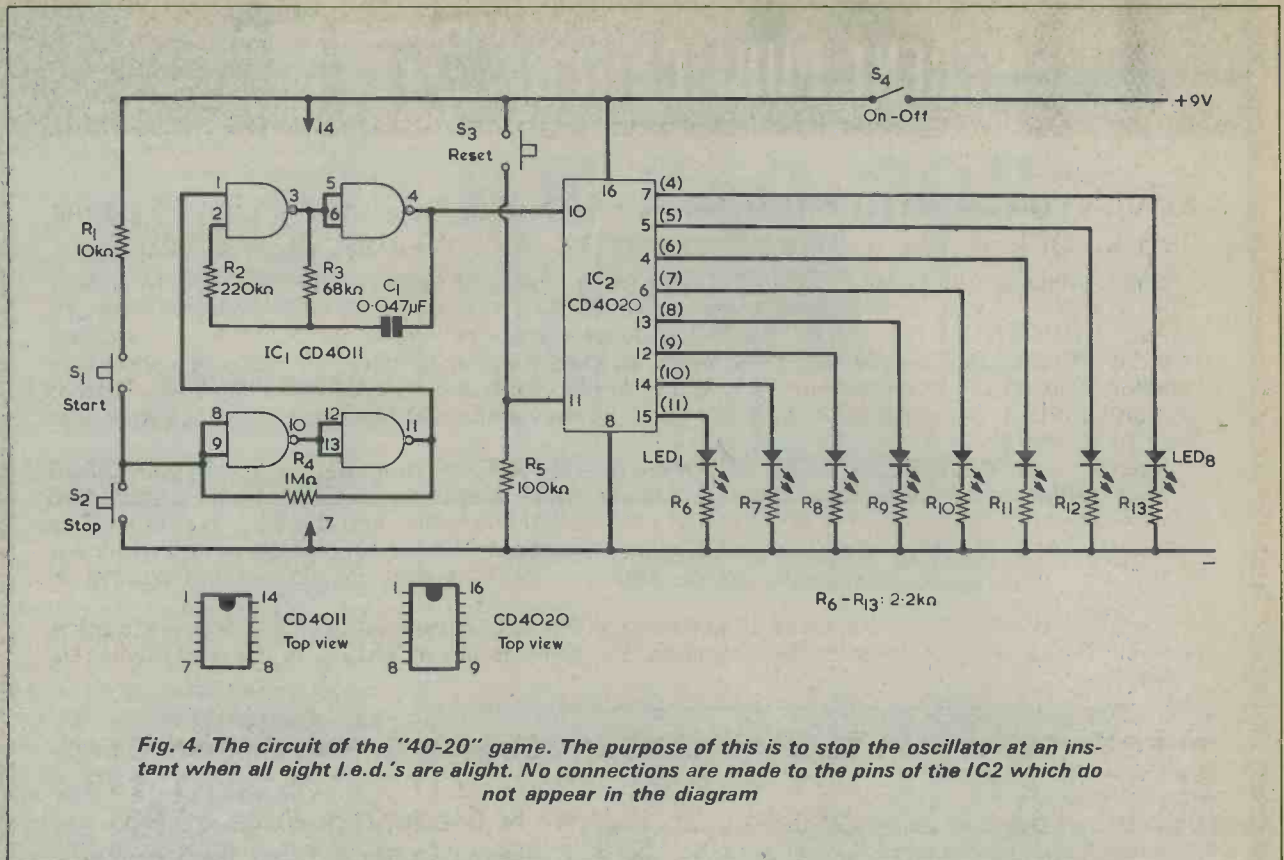The eight outputs from the CD4020 couple to the eight l.e.d.'s as shown. Each l.e.d. has a series



current limiting resistor in order that dissipation inside the i.c. can be kept to a low level. It is found that about 2 volts is dropped inside the i.c. for each l.e.d. that is lit. The l.e.d. current is about 2mA each, giving a total dissipation in the i.c. of around 32mW when all the l.e.d.'s are alight. Current consumption from the 9 volt supply is approximately 15mA when all the l.e.d.'s are lit, and is too low to be measured with a standard testmeter when they are extinguished. Average current is therefore about 7.5mA.

The oscillator frequency is such that LED1 goes through a 20 second cycle, consisting of 10 seconds alight and 10 seconds extinguished. This means that the cycle for LED8 is 20 seconds divided by 128, or 0.16 second. This is shorter than the normal human reaction time of around 0.25 second, with the result that a small element of luck is required to succeed in having all the l.e.d.'s alight. Nevertheless, this can be achieved by judicious operation of the "Stop" and "Start" buttons. If it is found that the cycle for LED1 is significantly longer or shorter than 20 seconds, this will be due to

differences in the transfer characteristics of the oscillator gates in the particular CD4011 employed for IC1, and it is merely necessary to alter the value of R3 accordingly. Increasing its value will slow down the oscillator, and vice versa.

### PRESENTATION

The circuit may be housed in a plastic case having the four switches and the eight l.e.d.'s on the front panel. The l.e.d.'s should be mounted in a line, in the same order in which they appear in the circuit. This will allow persons playing the game to understand the order in which they light up. The lighting of the l.e.d.'s has an appealing effect as they gradually build up to the condition in which they are all alight. Best results are given by employing the more sensitive, or "ultra-bright", l.e.d.'s which are nowadays available from many suppliers. All the resistors in the circuit are 1/4 watt 5% components, and C1 can be a polyester capacitor.

The circuit can also be used to count in binary from zero to 255, and this can be an instructive application. For counting it will be

necessary to slow down the oscillator by increasing the value of C1. Suggested increased values are 0.47 µ F or 1 µ F.



## RECENT PUBLICATIONS



**ADVENTURES WITH MICROELECTRONICS.** By Tom Duncan. 64 pages, 245 x 190mm. ( $9\frac{3}{4}$  x  $7\frac{1}{2}$ in.) Published by John Murray. Price £3.25.

The availability these days of circuit boards having holes with spring contacts in an 0.1in. matrix make possible the assembly of quite advanced electronic circuits, without even having to think of a soldering iron. The 12 projects in this well produced hard-cover book are built on such a circuit board and include a 2-octave electronic organ, a medium and long wave radio driving a speaker, a reaction timer, a traffic light simulator, a light operated alarm and a warbling/wailing siren. There is also an introductory section which describes each of the component types to be used together with their functions.

The term "microelectronics" in the title refers to fairly complex integrated circuits. Seven CMOS i.c.'s are employed, ranging from the 4011 to the 4047 monostable/astable multivibrator. Also used are three bipolar i.c.'s, the ZN414 and LM380 (for the radio) and the 556 dual timer. The reaction timer employs a 7-segment i.e.d. display for readout. The projects are presented with clear circuit and physical layout diagrams and many of them have suggestions for experimental modifications.

The book will be of especial value to anyone wishing to gain experience in practical electronics. As well as the absence of soldering problems, the projects are all battery driven and involve no shock risk.

**ELECTRONICS FOR TECHNICIANS LEVEL 2.** By B. F. R. Gillman, C.Eng., M.I.E.R.E. and B. A. Hudgell, B.Sc., C.Eng., M.I.E.E. 175 pages, 215 x 135mm. ( $8\frac{1}{2}$  x  $5\frac{1}{4}$ in.) Published by Hodder & Stoughton. Price £2.95.

B. F. R. Gillman is a Lecturer in Electronics, and B. A. Hudgell is a Senior Lecturer in Electronics, both at Southgate Technical College. The book is intended to benefit anyone studying electronics, telecommunications or electrical engineering, and has a depth of treatment aimed at Level II of the Technical Education Council Programmes. However, some of the subjects dealt with are expanded beyond this level to give a more complete and useful treatment.

Subjects covered are semiconductor materials, the p-n junction, simple power supply circuits, bipolar transistors, the transistor as amplifier, LC oscillators, waveform generators, thermionic valves, the cathode ray tube, and logic gates and circuits. Questions are set at the end of each chapter, with answers at the back of the book.

The volume is a good reliable text-book on the topics discussed, its major attraction being for the student.

**ELEMENTS OF ELECTRONICS 2. ALTERNATING CURRENT THEORY.** By F. A. Wilson, C.G.I.A., C.Eng., F.I.E.E., F.I.E.R.E., M.B.I.M. 223 pages, 180 x 105mm. ( $7$  x  $4\frac{1}{4}$ in.) Published by Bernard Babani (publishing) Ltd. Price £2.25. **ELEMENTS OF ELECTRONICS 3. SEMICONDUCTOR TECHNOLOGY.** By F. A. Wilson. 214 pages. Published by Bernard Babani (publishing) Ltd. Price £2.25.

These two titles appear in the Bernard Babani "Elements of Electronics" series, in which successive books advance from their predecessors without covering the same ground again. Each book can be considered as an entity in its own right, but if the books are read in the series starting with the first they unwind the whole story of electronic technology without repetition. "Elements of Electronics 1", it may be mentioned, dealt with simple electronic circuits and components.

"Elements of Electronics 2" deals extensively with alternating current theory, taking the reader to complex numbers and  $j$  notation. Also covered are time constants, reactance, impedance, resonance and transformers. Appendices at the end of the book deal with the trigonometry, mathematics and geometry required for a full study of alternating current behaviour.

In "Elements of Electronics 3" F. A. Wilson commences with semiconductor physics, then proceeds to semiconductor characteristics, basic semiconductor systems and analogue and digital integrated circuit technology. Again, there are appendices at the end of the volume, and these include notes on binary arithmetic and the determination of curve slope by graphical methods and by calculus.

Although these books are small enough to fit in the pocket they contain a mass of information, and at a modest price. Further books in the series will be appearing in the future.

## ROYAL OPENING OF MICROELECTRONICS CENTRE

His Royal Highness The Prince of Wales visited Ferranti early in the winter to open the Ferranti Electronics Limited — Microelectronics Centre at Hollinwood near Oldham.

The Centre, the most modern of its type in Europe, was built to meet the Company's expanding world-wide sales of complex LSI (Large Scale Integrated) circuits.

Ferranti Electronics Limited is the major British manufacturer of integrated circuits from simple logic devices to Europe's first, and one of the world's most sophisticated 16 bit microprocessor, the F-100L.

The Company pioneered, and is world leader in ULA (Uncommitted Logic Array) technology, a technique for producing custom designed LSI circuits quickly and economically. Ferranti ULA is one of the most powerful integrated circuit concepts to be developed. It is in high volume production and extensively used in automobile



On his arrival at Ferranti Electronics Limited. His Royal Highness The Prince of Wales drove the latest Jaguar XJ12 which is fitted with the world's first digital electronic fuel injection system.

electronics, telecommunications, cameras, computers, microprocessor systems, video games, toys, communications equipment, domestic appliances and preci-

sion instrument and test equipment.

The Royal opening was attended by guests from leading West European users and government departments.

## BROADCASTING HISTORY MADE



The BBC used digital audio recorders when they recorded the traditional Carol Concert at King's College Cambridge last Christmas Eve.

Duncan McEwan, the BBC's Chief Engineer, Radio Services (right) and engineer Ian Jolly (left) with the recording equipment.

The famous Festival of Nine Lessons and Carols from King's College Chapel, Cambridge made history not once, but twice, last Christmas.

The live broadcast on Christmas Eve, on Radio 4 was transmitted via satellite, in stereo, to 100 coast to coast National Public Radio stations in the United States.

BBC Radio always broadcasts the Festival of Nine Lessons and Carols live on Christmas Eve and a recording of it on Christmas Day on Radio 3.

The stereo recording on Radio 3 on Christmas Day was the first BBC digital recording ever transmitted. By bringing back the recording made on site to London by road, any distortion over the normal analogue circuit between Cambridge and London (used for the live broadcast) was avoided.

Duncan McEwan, the BBC's Chief Engineer Radio Broadcasting, says, "BBC Radio always likes to be in the vanguard of engineering development. We intend to experiment with digital recording on several productions in the coming year. It will give us useful experience so that we will know how to assess the purpose-built digital audio recorders, stereo and multitrack, that will be appearing in the next few years."

"Digital recording offers advantages that could have quite an impact on the technical quality of productions. It allows us to exploit a wider dynamic range much more easily than is possible with analogue equipment. There is a complete absence of wow and flutter and a much lower level of non-linear distortion."

# COMMENT

## FIFTY YEARS ON

### TV Exhibition

The exhibits, outlining television's development since the opening of the 405-line service in 1936, will be punctuated by a series of period room-settings, in each of which it is hoped to show a montage of contemporary programmes on restored receivers of appropriate vintage; these will include a pre-war set with a five-inch tube, and a 'projection' set of the early 1950s. A display of videotape recorders will illustrate the dramatic fall in their size and price since they were first introduced, and there will be a working specimen of a type of British telecine machine that has been used with conspicuous success through three decades.

In March 1930, Baird's much-heralded 'Televisor' was finally on sale, and the experimental 30-line transmissions from the BBC's Brookmans Park station were for the first time accompanied by sound. Television broadcasting, in fact, had arrived, and the fiftieth anniversary of this milestone is being marked by a special exhibition at the Science Museum, opening at the end of March for six months.

The title of the exhibition is "The Great Optical Illusion", and one of its aims is to reawaken the sense of wonder that is properly due to television but that our familiarity with it has inevitably dulled. An introductory exhibit will show what is involved in making a moving picture out of a single spot of light, and the 'illusion' theme will be maintained with other demonstrations: "Chromakey", an electronic overlay technique, will make visitors appear to be performing a feat of aerial daring while actually just off the floor, while 'Front Axial Projection' will insert them optically into a projected scene.


In our last issue we published a short article entitled 'Good Connections', a very practical article for those inexperienced in constructional work.

In this issue, also concerned with soldering, we include a review of a very interesting film — 'The Right Connection'. The film shows the use of tin-lead solder in the manufacture of printed circuit boards etc.

The film, which should be attractive to members of radio clubs etc., is available on free loan from the International Tin Research Institute of Fraser Road, Perivale, Greenford, Middlesex UB6 7AQ.

The "Presenter" of the film is Michael Rodd of the BBC's TV programme 'Tomorrow's World'.

## SMALL IS BEAUTIFUL

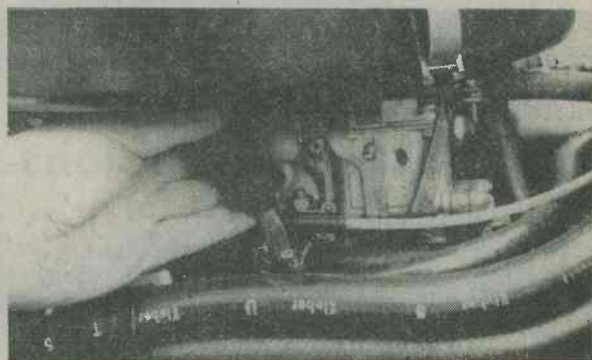


In the confined space of a car engine the Screwmaster's ratchet is invaluable.

Generations of skinned knuckles are a testimony to the fortune to be made by the company which produces a reliable, one-handed ratchet screwdriver small enough to get into awkward corners.

J. Stead & Co. Ltd., of Greenland Road, Sheffield believe they have done it with the Steadfast Screwmaster.

The secret of the Screwmaster is the ratchet mechanism, a miniaturised adaptation of a well-established clutch principle, encapsulated in an immensely strong cellulose acetate handle. The ratchet system utilises roller bearings, which are allowed to freewheel or jam between flat surfaces on the blade and the outer casing. This provides drive and freewheel, full lock and unscrew and freewheel positions.

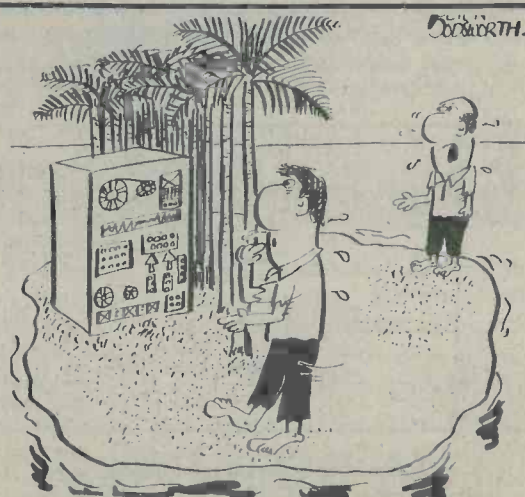As long as the blade has the resistance of a screw slot to hold it, the three positions — marked 'Forward', 'Neutral' and 'Reverse' on a rotating sleeve where handle meets shaft — can be selected at the touch of a finger of the hand grasping the handle. Price is £2.25.



"Anything over there, George?"

# MICRO CURRENT ICM7555 CIRCUITS

By A. P. Roberts

## Two applications for the "CMOS 555".

There can be few readers of this magazine who are not familiar with the popular 555 timer integrated circuit, and it is probable that a substantial proportion have had first hand practical experience with this device. For the amateur user it is certainly one of the most useful and versatile integrated circuits currently available.

However, this device has a few minor drawbacks which make it less than ideal in certain applications. This has led to improved versions of the 555 being produced, including in particular the "CMOS 555", or ICM7555, which forms the basis of this article.

### IMPROVEMENTS

One of the more obvious disadvantages of the standard 555 is its relatively high current consumption of about 8mA at 9 volts. Although not excessive, this is considerably higher than that of other modern integrated devices. By using CMOS circuitry the ICM7555 achieves the low level of current consumption that has helped to make CMOS i.c.'s so popular. The actual figure for the ICM7555 is of the order of 80 $\mu$ A; in other words, only about one-hundredth of that required by the standard 555.

Another advantage of the ICM7555 is that it does not, like the 555, produce a negative voltage spike on the positive supply rail as the output switches to the high state. This spike is produced by a sudden surge in the current consumption of the i.c. which can peak to as high as a few hundred milliamps for some 0.1 microsecond. In many applications, of course, this is of little or no conse-

quence, but it can cause spurious operation if the circuit includes t.t.l. devices or any other circuitry which is sensitive to noise on the supply lines. The normal solution is to connect a large value bypass capacitor across the supply lines close to the 555. Such a capacitor is totally unnecessary when using the ICM7555.

Other advantages of the ICM7555 are a wide operating supply voltage range of 2 to 18 volts, and low reset trigger and threshold currents of typically around 20 picoamps. The device will work perfectly well with timing resistances of 100 megohms or more.

One minor drawback of the ICM7555 is that it has a maximum output sink current of 100mA with a supply potential of 18 volts, as compared with a figure of 200mA for the standard 555. The maximum operating frequency in the astable mode is at least 500kHz.

### FLASHING PILOT LIGHT

The circuit of Fig. 1 shows a simple application in which the ICM7555 works well, and where the ordinary 555 would be totally unsuitable. The circuit is for a flashing indicator light which shows that the battery operated equipment in which it is installed is turned on, and it draws an extremely small current from the supply rails.

In Fig. 1 the ICM7555 is employed in the astable mode to briefly switch on an l.e.d. indicator at intervals of approximately 1 second. This type of pilot light has two advantages over a straightforward l.e.d. indicator permanently connected across the supply rails. First, it requires a much lower supply current because the l.e.d. is switched off for most of the time, whereupon the average current consumption can be made very small. Second, a flashing indicator is subjectively more noticeable than a non-flashing one, particularly under conditions of bright ambient light.

The circuit employs a standard 555 astable multivibrator arrangement. At one part of the cycle, capacitor C2 charges through R1 and R2 until the voltage across its plates reaches two-thirds of the supply voltage. During this part of the cycle, the output at pin 3 is high and the l.e.d. is extinguished. When the voltage across C2 is at two-thirds of supply voltage, a voltage detector coupled to pin 6 triggers the circuit to its alternative state, in which the output at pin 3 goes low, thereby turning on the l.e.d., and a low impedance is given between pin 7 and the negative rail. C2 then discharges through R2 and the internal circuitry of the i.c. until the voltage across it falls to one-third of supply voltage.

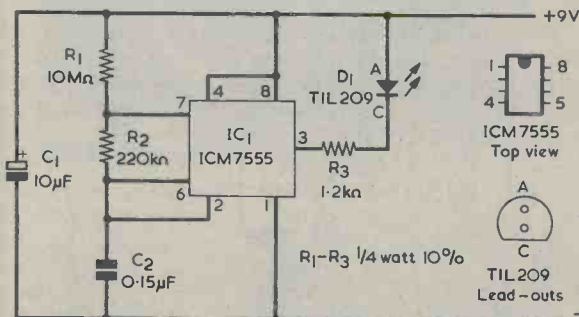


Fig. 1. A flashing light pilot indicator incorporating the ICM7555. This draws an average current from the 9 volt supply rails of only about 0.21mA

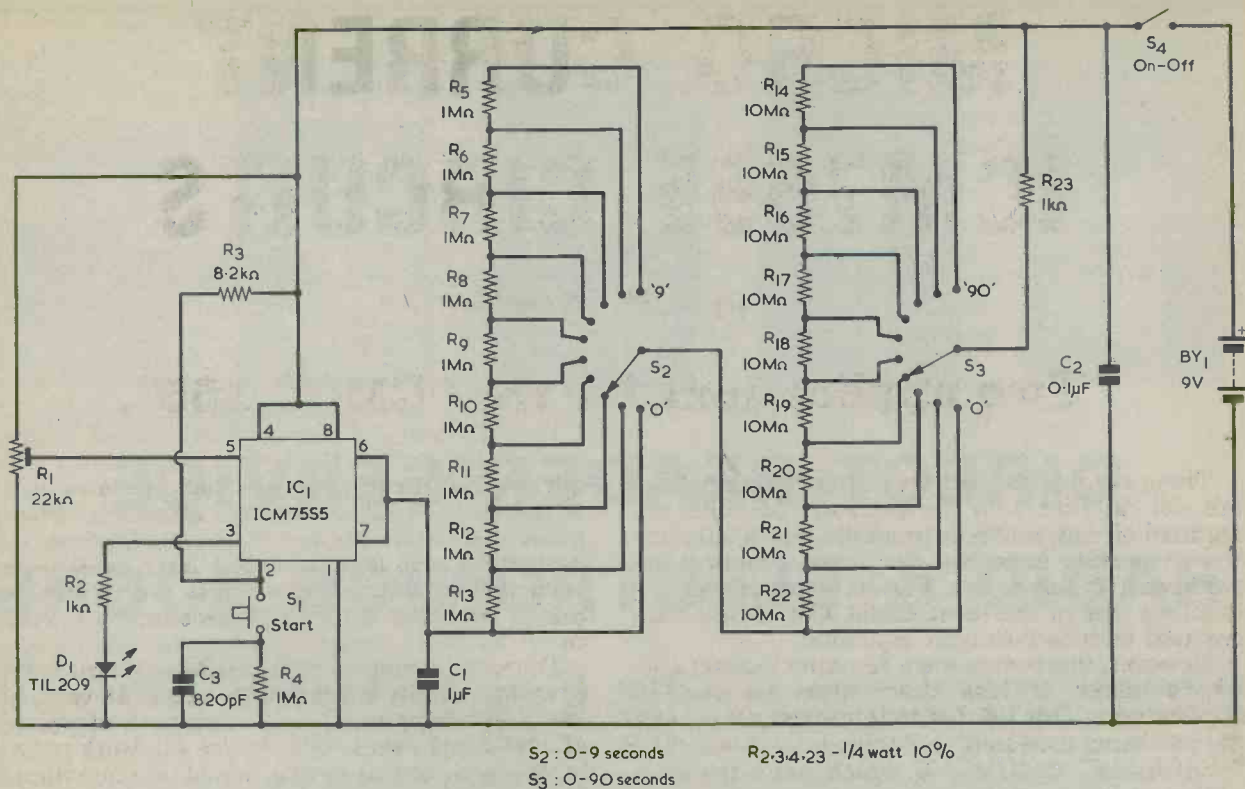


Fig. 2. A photographic timer offering a range of 1 to 99 seconds in 1 second steps. As is explained in the text, R5 to R22 should be close tolerance resistors

This voltage triggers a second voltage detector coupled to pin 2, and the i.c. reverts to the previous state, in which C2 once more charges via R1 and R2.

Because C2 charges through both R1 and R2, but discharges through R2 only, the length of the discharge period (when the l.e.d. is alight) is shorter than the charge period (when the l.e.d. is extinguished). In the circuit of Fig. 1 the discharge period is purposely made considerably shorter than the charge period, since R1 is given a value which is much higher than that of R2. In fact, the ratio of the discharge to the charge period is about 1 to 46. Thus, the brief pulsing on of the l.e.d. indicator is obtained.

The current consumption when the l.e.d. is switched off is only about  $80\mu\text{A}$ , and it rises to approximately 6mA when the l.e.d. is turned on. This gives an average current consumption of only about  $210\mu\text{A}$ , or 0.21mA. If a standard 555 were used in the circuit, this on its own would draw a standing current of around 8mA, which is more than the current consumption of the l.e.d. when it is turned on!

The operating frequency of the circuit in Hertz, is equal to  $1.46$  divided by  $CR$ , where C is the value of C2 in microfarads and R is equal to R1 plus 2 times R2 in megohms. This calculates at about 0.93 Hz, which is close enough to the required nominal figure of 1Hz.

### SIMPLE TIMER




When used in the monostable mode the ICM7555, like the standard 555, produces an output pulse length of approximately  $1.1CR$ . However, whereas the 555 can have a maximum timing resistance of about 10 or  $20M\Omega$ , the ICM7555 will

operate with a timing resistance of about  $100M\Omega$  or more. The ICM7555 also applies a very much smaller stray capacitance across the timing capacitor, and predictable timing results are feasible with a timing capacitance as low as 1pF. A performance of this nature would be impossible with the 555, which has a stray capacitance in the order of 50pF.

It is the ability to use a high value of timing resistance which is probably of more interest to the amateur user. Where, with a standard 555 it would be necessary to employ an electrolytic timing capacitor, with its relatively high leakage current and wide tolerance on value, with the ICM7555 it is possible to employ a non-electrolytic capacitor. An example of a timer circuit incorporating a non-electrolytic  $1\mu\text{F}$  timing capacitor is given in Fig. 2. This is primarily intended for use as an enlarger timer, but it can also be employed when making long time exposures with the camera shutter set to "B".

The timing period is initiated by pressing push-button S1. This causes the l.e.d. D1 to turn on. After a time, which is selected by switches S2 and S3, the l.e.d. turns off again to indicate that the timing period is over.

The circuit is based on a fairly straightforward 555 type of monostable. After switch-on, timing capacitor C1 is held discharged via pin 7 and the internal circuitry of the ICM7555, and the i.c. output at pin 3 is low. The trigger input at pin 2 is taken high by R3, and the circuit will start a timing period if pin 2 is taken below one-third of the supply voltage. This is done when S1 is pressed, because C3 momentarily takes pin 2 to the negative rail potential. When S1 is released, C3 is quickly discharged by R4, so that it is ready to initiate another timing period later.

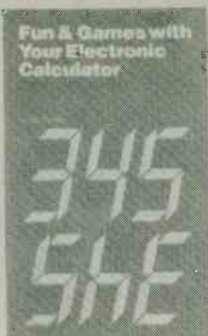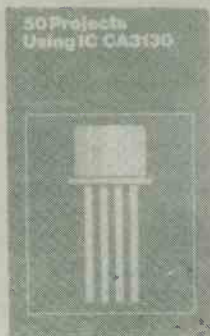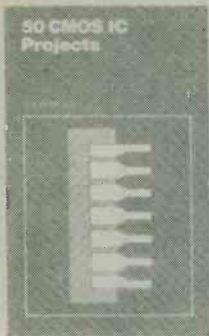

# DIRECT READER SERVICE

## RADIO & ELECTRONICS BOOKS

17. Solid State Power Supply Handbook	£1.25	38. How to Make Walkie-Talkies	£1.25
18. 50 Projects Using IC CA3130	£1.25	39. IC 555 Projects	£1.75
19. 50 CMOS IC Projects	£1.25	40. Projects in Opto-Electronics	£1.25
20. A Practical Introduction to Digital IC's	95p	41. Radio Circuits Using IC's	£1.35
22. Beginners Guide to Building Electronic Projects	£1.25	42. Mobile Discotheque Handbook	£1.35
23. Essential Theory for the Electronics Hobbyist	£1.25	43. Electronic Projects for Beginners	£1.35
25. 79 Electronic Novelty Circuits	£1.00	44. Popular Electronic Projects	£1.45
26. 52 Projects Using IC741	95p	45. IC LM3900 Projects	£1.35
28. Two Transistor Electronic Projects	85p	46. Electronic Music and Creative Tape Recording	£1.25
29. How to Build Your Own Metal and Treasure Locators	£1.00	47. Practical Electronic Calculations and Formulae	£2.25
30. Electronic Calculator Users Handbook	95p	48. Radio Stations Guide	£1.45
31. Practical Repair and Renovation of Colour TVs	£1.25	49. Electronic Security Devices	£1.45
32. Handbook of IC Audio Pre-amplifier and Power Amplifier Construction	£1.25	50. How to Build Your Own Solid State Oscilloscope	£1.50
33. 50 Circuits Using Germanium, Silicon and Zener Diodes	75p	51. 50 Circuits Using 7400 Series IC's	£1.45
34. 50 Projects Using Relays, SCR's and TRIACS	£1.25	52. Second Book of CMOS IC Projects	£1.50
35. Fun and Games with your Electronic Calculator	75p	53. Practical Construction of Pre-Amps, Tone Controls, Fitters & Attenuators	£1.45
36. 50 (FET) Field Effect Transistor Projects	£1.25	54. Beginners Guide to Digital Techniques	95p
37. 50 Simple L.E.D. Circuits	75p	55. 28 Tested Transistor Projects	£1.25
		56. Digital IC Equivalents and Pin Connections	£2.50
		57. Linear IC Equivalents and Pin Connections	£2.75

**POSTAGE: 20p PER BOOK. IF MORE THAN 3 BOOKS ORDERED: 10p PER BOOK**

To: Data Publications Ltd., 57 Maida Vale, London W9 1SN

Please send me within 21 days .....copy/copies

Book Nos: .....

.....

.....

I enclose Postal Order/Cheque for £.....

Name .....

Address .....

.....

(Block Letters Please)

*(We regret this offer is only available to readers in the U.K.)*



At the start of the timing period the i.c. output at pin 3 goes high and the l.e.d. lights up. Also, pin 7 goes open, and C1 is able to charge via whatever resistance is switched into circuit by S2 and S3. When the voltage across C1 reaches threshold level (normally two-thirds of supply voltage) the timing period ends. Pin 3 of the i.c. goes low and C1 is discharged via pin 7.

If, in the timing resistor chain, only R13 were switched into circuit (and ignoring R23 for the moment) the timing resistance would be  $1M\Omega$  and the calculated length of the timing period 1.1 second. However, this can be altered to exactly 1 second by adjusting R1, which controls the threshold voltage inside the i.c. and can make it other than two-thirds of supply voltage. With R1 correctly set up, S2 provides timing increments of 1 second up to 9 seconds, because each of the resistors R13 to R5 has a value of  $1M\Omega$ . Further resistors can be inserted by S3, and as the resistors R22 to R14 are each  $10m\Omega$ , S3 offers a timing range from zero to 90 seconds. Operating both switches provides timing ranges from 1 to 99 seconds in 1 second steps. Resistor R23 is included simply to prevent excessive current flow if both S2 and S3 should happen to be set to the "0" positions.

The timing resistors R5 to R22 should have tolerances of 5% or better, and 5% components in carbon film  $\frac{1}{2}$  watt are readily available. It is also possible to obtain  $1M\Omega$  resistors in  $\frac{1}{2}$  watt 2% and even 1%. Capacitor C1 does not need to be a close tolerance component because variations from its nominal value can be taken up by the adjustment

of R1. It should be a good quality plastic foil type. Whereas the electrolytic timing capacitors which would be required in a 555 circuit have insulation resistances in the order of megohms, a plastic film capacitor can have an insulation resistance of several gigaohms, i.e. several thousand megohms! Whilst in the subject of insulation resistance it is important that the insulation resistance of S2 and S3 should be of a high order.

After the circuit has been assembled, R1 can be adjusted to give a timing period of 10 seconds when this time is selected by S2 and S3. Then, when a reasonable accuracy has been achieved, the unit can be set to the full 99 second timing period, and final fine adjustments made. R1 should be the larger 0.25 watt type of skeleton potentiometer rather than the sub-miniature 0.1 watt type.

#### FINAL POINTS

It should perhaps be pointed out that in order to take advantage of the low current consumption of the ICM7555 it is advisable to use high value timing resistors, otherwise, the current flowing into the timing network will add significantly to the current consumption of the whole circuit. Indeed, if a timing resistance of only a few kilohms were used, the current consumption of the timing network would be many times that of the ICM7555 itself!

Although the ICM7555 is a CMOS device it requires no special handling precautions, as it is fully protected by internal circuitry. ■

---

# TRADE NOTE

## MAGNETISER/DEMAGNETISER FOR THE WORKBENCH



Have you ever wished that you possessed a magnetised screwdriver?


The answer could lie in an ingenious magnetiser/demagnetiser designed specifically for the engineering bench. The unit is compact, inexpensive and instantaneous in operation. At the touch of a button you can produce a bar magnet up to 9 mm diameter and any length. Press again to demagnetise tools before working on clocks, instruments or tape decks. You can remove ferrous

particles from oil or instantly magnetise a blade to recover that tiny part you just dropped and just as quickly demagnetise it before it becomes a nuisance on the bench.

The unit, which measures only 135 x 80 x 65 mm, operates on 240 volts, is housed in a steel case and is designed to last a life-time.

At £9.95 (incl. postage and V.A.T.) this piece of equipment is available from Magnadyne Products, 6 Lulworth Road, Welling, Kent, DA16 3LQ.

By  
J. K. Owen

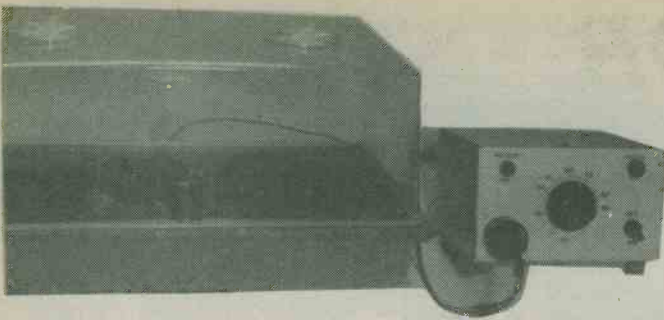

## Electronic control of soil temperature

The usual type of inexpensive seed propagator, comprising a plastic tray with a clear dome, offers some considerable advantage over the even more basic wooden seed box. Even so, it can still be inadequate when it comes to dealing with the more exotic seeds, some of which require a constant temperature of up to 80°F for germination. Even the tomato seed requires 60°F.

To maintain a room, even with central heating, at the higher germination temperature both night and day would be prohibitively expensive (not to mention uncomfortable!) whereas "central heating" of the propagator on its own would be much less costly. A propagator measuring around 15 by 9 in. could be maintained at a relatively constant high temperature for a power requirement of the order of 5 watts only.

This figure does not mean that a 5 watt propagator heater would be left running continuously. To maintain a constant temperature, a much more powerful heater would be required, this

being automatically switched on and off by a temperature sensing circuit. The average power would then be around the 5 watt figure.

### TEMPERATURE CONTROLLER

A temperature controller circuit is given in Fig. 1, and this is capable of offering an adequate range of temperatures, from below 50°F to above 90°F. It also incorporates a timing component which provides a small degree of hysteresis so that there is a differential between the "switch-on" and "switch-off" temperatures.

The thermistor, TH1, is the temperature sensing probe, and is buried in the soil or potting compost in which the seeds are to be germinated. Its resistance decreases as its temperature rises.

The base of TR1 is held at about 3 volts, or half the supply voltage, by the equal value resistors, R3 and R4. If the thermistor is cold, and therefore has a high resistance, the components R1, R13 and

### COMPONENTS

#### Resistors

(All fixed values  $\frac{1}{2}$  watt 5% unless otherwise stated)

- R1 470  $\Omega$
- R2 10k  $\Omega$
- R3 10k  $\Omega$
- R4 10k  $\Omega$
- R5 220k  $\Omega$
- R6 1.2k  $\Omega$
- R7 4.7k  $\Omega$
- R8 270  $\Omega$
- R9 120  $\Omega$
- R10 75  $\Omega$
- R11 10  $\Omega$  2 watts
- R12 10  $\Omega$  2 watts
- R13 5.6k  $\Omega$
- VR1 2k  $\Omega$  potentiometer, wire-wound

#### Capacitors

- C1 0.1  $\mu$ F disc ceramic
- C2 220  $\mu$ F electrolytic, 16V. Wkg

#### Transformer

- T1 Mains transformer type CT4, secondary 0-9-17V at 4A (see text)

#### Semiconductors

- TR1 BC108
- TR2 BCY70
- TR3 BC108
- TR11 NAS 0351X
- TH1 G23 (see text)
- D1 1N4001
- ZD1 BZY88C6V2

#### Lamps

- PL1 6.5V 0.3A, m.e.s.
- PL2 6.5V 0.3A, m.e.s.

#### Switch

- S1 d.p.s.t., toggle

#### Miscellaneous

- 2 m.e.s. lampholders, panel mounting with bezels
- Octal plug
- Octal socket
- Control knob
- Resistance wire (see text)
- Heat resistance sleeving (see text)
- Materials for case
- Materials for printed board
- Materials for thermistor probe
- Terminal block, 4-way 5A
- Wire, bolts, nuts, etc.

# PROPAGATOR HEATER



## Heating element switching at pre-selected temperature with very close control

VR1 cause the emitter of TR1 to be positive of the level at which base current flows. TR1 is therefore cut off and there is no voltage drop across its collector resistor R2. In consequence, TR2 is also turned off, and its lack of collector current results in TR3 being cut off as well. Gate current therefore flows via R8 and R9 to the triac, turning this on and completing the circuit between the 9 volt secondary of the mains transformer and the heating element.

The soil, and hence the thermistor probe, commences to warm up, causing the probe resistance and the voltage at TR1 emitter to fall. At a pre-determined temperature, which is governed by the setting of VR1, the emitter of TR1 becomes negative of its base by about 0.6 volt, whereupon TR1 commences to draw collector current through R2. The voltage across R2 turns on TR2 and this causes TR3 to become conductive also. TR3 collector takes up a potential which is only slightly positive of its emitter, and the gate current to the triac is cut off. The triac is turned off and no power

is applied to the heating element.

When, subsequently, the thermistor cools, its rising resistance causes the emitter of TR1 to go positive until TR1 cuts off again. The reverse process then takes place, with all three transistors becoming turned off and the triac turned on once more.

It is desirable to have a degree of hysteresis in the circuit so that there is a "snap-on" and "snap-off" action in the electronic switch. This is provided by the capacitor C1. When, with rising thermistor temperature, TR1 commences to pass collector current, its collector goes negative. Before TR2 commences to conduct, this negative excursion takes TR1 base negative via C1, thereby delaying the instant at which it draws sufficient collector current to make TR2 conductive. As soon as TR2 starts to draw collector current there is a regenerative action, again delayed by C1, in which increased base current passes to TR1 via R5. The delaying effect is also given in the reverse condi-

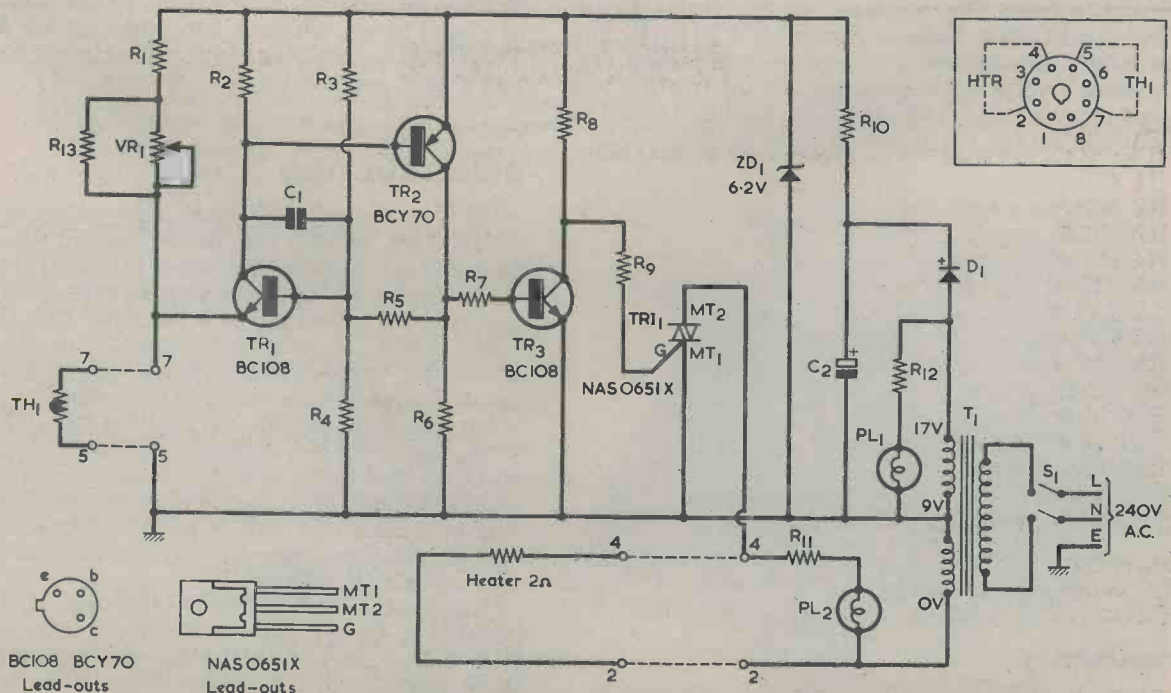


Fig. 1. The circuit of the propagator temperature controller. Connections to the thermistor probe and the heating element are made by way of an octal plug and socket




*The temperature control unit. The large central knob sets up the temperature to which the propagator is taken*

tion, when the thermistor cools and TR1 starts to turn off.

The value specified for R5 controls the hysteresis level and, at 220k $\Omega$ , it is found that there is a differential of about plus or minus 1°F. This is an acceptable figure for a seed propagator and ensures that extremes of temperature in either direction are not produced before switching takes place.

Two pilot lights are provided in the circuit, PL1 indicating that the mains supply is switched on and PL2 indicating when power is being applied to the heating element. Both lamps have a small resistor in series to limit the voltage which appears across them. The thermistor and the heating element connect to the remainder of the circuit by way of an octal plug which fits into an octal valveholder. T1 is a "charger transformer" type CT4 having a secondary offering 0-9-17 volts at 4 amps. This is available from Electrovalue, 28 St. Judes Road, Englefield Green, Egham, Surrey, TW20 0HB. The secondary is connected as shown in the diagram, allowing 9 volts to be available for the heating element circuit and 8 volts (17 volts minus 9 volts) to be available for the power supply rectifier, D1.

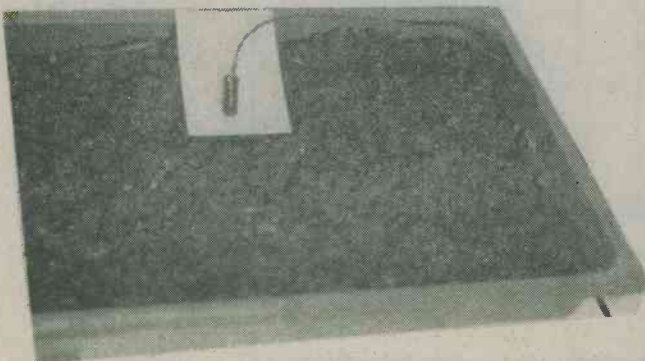

*The thermistor probe, ready for insertion in the soil*

## THERMISTOR PROBE

The thermistor is a glass bead component with a diameter of 3mm. It is a type G23 and can be obtained from Maplin Electronic Supplies. In the prototype it was encapsulated, using Araldite, in a Paxolin (s.r.b.p.) tube about 1in. long and having an inside diameter of 5mm. If a Paxolin tube is not available, a suitable tube can be made up in the following manner. Wind a short length of polythene film around the shank of a  $\frac{3}{8}$ in. drill. Then wind around the polythene a 4in. length of paper 1in. wide, smearing the paper liberally with a clear adhesive such as "UHU" as it is wound on. The polythene will prevent the adhesive sticking to the drill and, when the adhesive has set, the polythene can be readily removed from the resulting tube. ("UHU", in common with practically all adhesives, will not stick to polythene.)

The heating element consists of a suitable length of resistance wire, such as Eureka, and it requires a resistance of 2 $\Omega$ . This can be provided by a 27in. length of 26s.w.g. Eureka wire, which has a nominal resistance of 2.73 $\Omega$  per yard. (An alternative wire is the 26 gauge resistance wire listed by Home Radio, with a resistance of 2.6 $\Omega$  per yard. The required 2 $\Omega$  would be given by 27.7ins. of this wire.— Editor.) The wire should preferably be covered with heat resistant sleeving, available from Maplin Electronic Supplies, to prevent corrosion. The heating element wire should be laid out symmetrically on the base of the propagator, covering the whole area as evenly as possible, and then secured to the base by adhesive. A 4-way 5-amp terminal block can be screwed to the base of the propagator, and this will enable connections to be made to the element and the thermistor probe.

When the heating element is turned on, about 2 volts is dropped in the triac. The power dissipated in the element therefore calculated as 24.5 watts.

The triac employed by the author was an NAS 0351X. If an alternative is used it should be a sensitive type capable of turning on at the gate current of about 15mA which is available via R8 and R9. The C206D, listed by Maplin Electronic Supplies, has a gate turn-on current of 5mA.

## CONSTRUCTION

The prototype unit was housed in a home-constructed metal case measuring 6in. by 4in. by 5½in. deep. The only important criterion of the case is that it should house the components comfortably and without crowding. It is essential that the case, when metal, is reliably connected to the mains earth and that all precautions against accidental shock due to mains voltages are observed.

On the front panel, VR1 is mounted centrally, with a scale behind its knob. PL1 is at upper right and PL2 is at upper left. The mains on-off switch is at lower right with the octal socket at lower left. Any other suitable type of plug and socket offering four connections may be employed instead of the octal plug and socket.

A printed circuit board to take most of the components is shown full size in Fig. 2. R11, R12 and R13 do not appear on the board. The first two of these resistors are mounted close to the lamps to which they connect, a small tagstrip supporting the lead which does not connect to the lampholder. R13 is mounted on the tags of VR1. The triac is

The inside of the control unit case. The large circular component on the printed circuit board is the electrolytic capacitor, C2



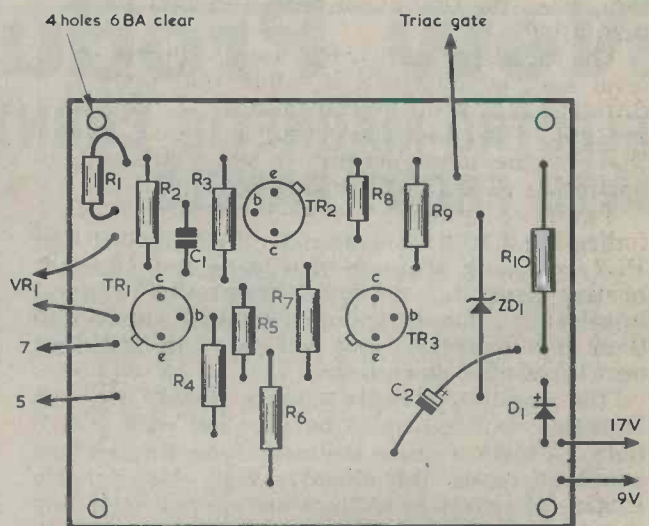
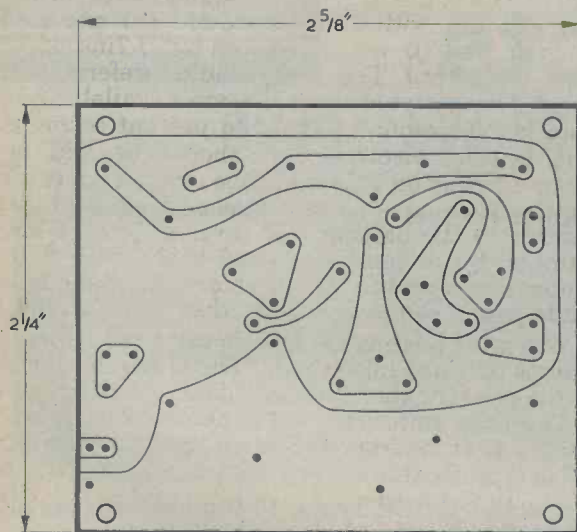
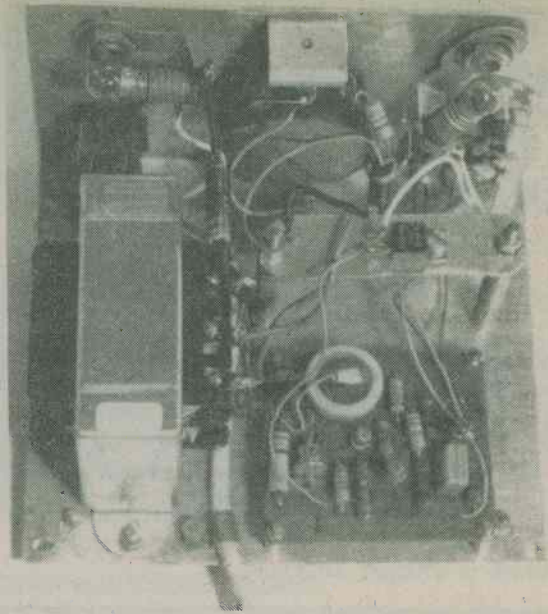


Fig. 2. Many of the components are assembled on a printed circuit board, which is reproduced here full size. The board is spaced off from the bottom of the case by metal spacing washers, which also provide the chassis connection to the board.

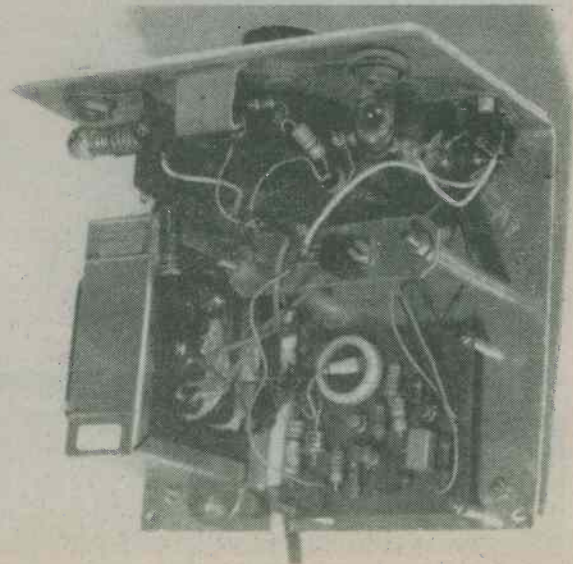Another view of the case interior. The triac is bolted to a rectangular piece of aluminium mounted on spacing pillars just in front of the printed board



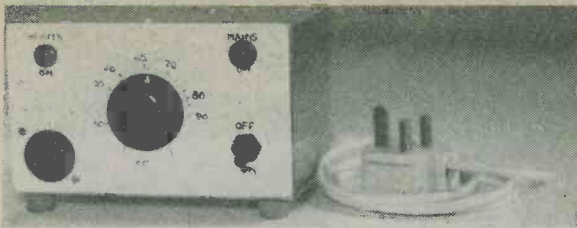

The control unit obtains its power from the mains, and is fitted with a 3-way mains lead and plug

mounted on a separate piece of 18 s.w.g. aluminium about 3in. by  $\frac{3}{4}$ in., which also serves as a heatsink. This aluminium item is supported at both ends by bolts passing through spacing pillars about  $1\frac{1}{2}$ in. long. All the wiring external to the printed board should be carried out to agree with the circuit diagram. VR1 should be connected such that the resistance it inserts into circuit decreases as its spindle is rotated clockwise.

## CALIBRATION

Calibration of the controller is straightforward, requiring nothing more than a supply of hot water and a suitable thermometer. Suspend the tip of the probe in a glass of water together with the thermometer. Start off with the water at 50°F and advance the potentiometer VR1 until the heating element switches on, as indicated by PL2. Mark a scale fitted to VR1 at this point, and add hot water to the glass until the thermometer reads 55°F. Again adjust the potentiometer until the lamp lights and mark the scale accordingly. Proceed in this manner until the whole range has been calibrated.

Finally, it may be mentioned that the use of a shunt 5.6kΩ resistor across VR1 is partly due to the fact that the value required in the potentiometer is 1.5kΩ, whilst 2kΩ potentiometers are more readily available. A further reason is that the parallel combination of fixed resistor and potentiometer results in an opening out of the calibration scale at the most useful part, around 50° to 75°. ■

# New Products




## ELECTRO-MAGNETIC COUNTERS WILL PLUG INTO FRONT PANELS

The new EMO10 range of miniature low cost electromagnetic counters from Impectron Limited, is designed for a wide variety of control applications. The 6-digit units measure just 88 x 50 x 26 mm (LxWxH) and will plug into standard panel-mounted receptacles.

The counters have six 4.5 mm display digits as standard, but may also be supplied with 4 or 5 digits. A further option is a magnifying window lens which increases the effective digit size. A wide variety of operating voltages are offered, including 6, 12, 24, 48, 60, 110, 150 and 220V DC, as well as 12, 48, 60 and 150V AC.

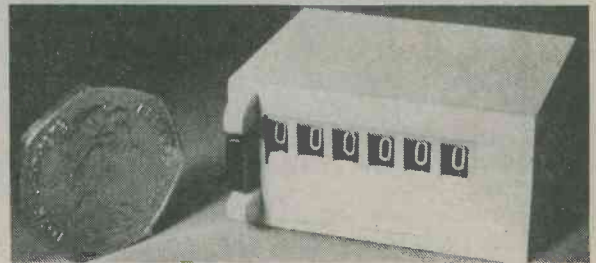
The mechanism operates on electrical pulses, which activate a pawl and ratchet system. The display indexes one count for each complete pulse, and rated life expectancy is in excess of 100 million counts. Maximum counting rates are 50 impulses



per second for DC types, 10 impulses per second for AC versions.

Although they are inexpensive, the counters are constructed to very high standards. Main body parts are moulded from resilient ABS while all exterior metal parts are zinc passivated. Operating temperature range is 20°C to 80°C, and coil insulation is greater than 100 Megohm at 500V DC.

## TWO NEW SOCKET TESTERS

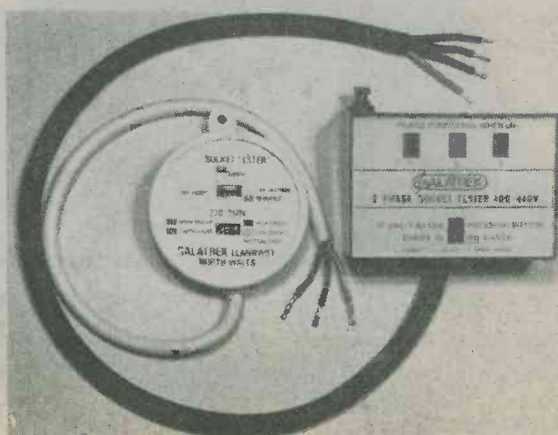

After the successful introduction of their 13 Amp Socket Tester in 1978 GALATREK ENGINEERING announce the arrival of two new models.

(1) A 6 function socket tester FOR ANY TYPE OF SOCKET (fit your own plug). By means of neons and indications on the front of the tester it shows immediately if:

(a) Socket is A1 OK; (b) DANGER reverse polarity; (c) DANGER no earth; (d) DANGER live fault; (e) DANGER neutral fault; (f) DANGER live earth reversed.

PRICE £4.50 VAT and post paid.

(2) 3 Phase tester which instantly indicates if phases are functional and whether there is an earth.


PRICE £8.95 VAT and post paid.

Designed and manufactured by: Galatrek Engineering, Scotland Street, Llanrwst, Gwynedd.


RADIO AND ELECTRONICS CONSTRUCTOR

**IN OUR NEXT ISSUE**

**LABORATORY POWER SUPPLY**

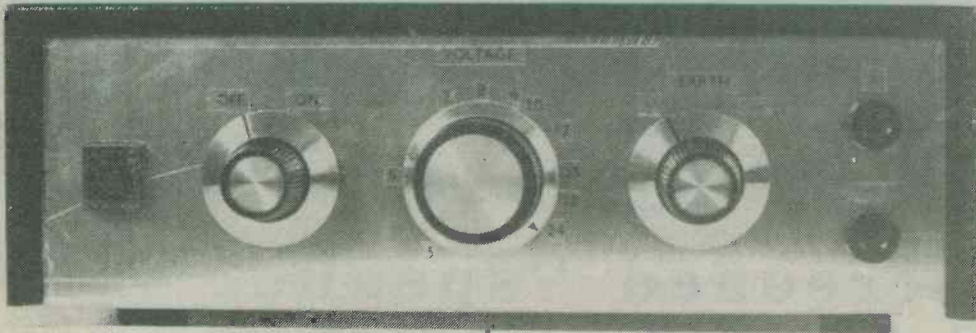

*THE  
"DIODYNE"  
RECEIVER*

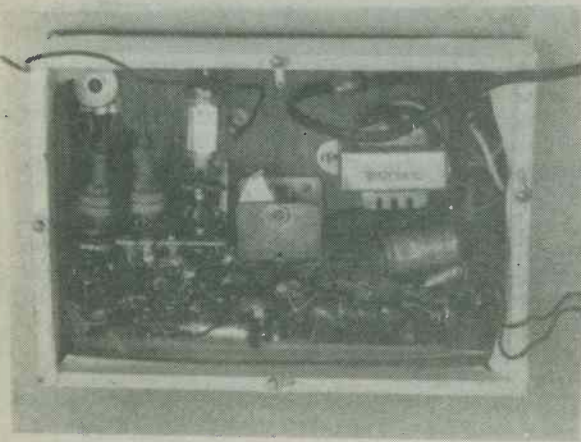

**DUAL  
POLARITY  
VOLTMETER**



**PLUS MANY OTHER ARTICLES**

# AMPLIFYING INTERCOM

By R. A. Penfold

- Inexpensive 2-way design
- Useful
- Unscreened "speaker cable" gives interconnection
- Call fac

A simple intercom system of the type to be described should be a very useful addition in virtually any household. The system has been tested with an interconnecting lead between the two stations which is 16 metres (52 ft.) in length, and it should be able to work over a greater distance than this if necessary. Only an unscreened 2-way cable is needed to connect the two stations. These are battery powered and, with normal use, battery life should extend over a considerable period.

## INTERCOM SWITCHING

The standard basic switching circuit for an amplifying intercom is shown in Fig. 1. In the "Receive" mode, the main unit amplifier output is coupled to a local loudspeaker and its input is connected to a second, remote, loudspeaker at the slave unit. This second loudspeaker functions as a moving-coil microphone, whereupon the sound it picks up is amplified and reproduced over the main unit loudspeaker. A loudspeaker does not function particularly well, in terms of audio quality, when

used as a microphone, but its performance is perfectly adequate for the transmission of intelligible speech. Since it presents a low impedance output to the connecting cable its signal output voltage is low, being typically well below one millivolt. In consequence the amplifier has to have quite a high voltage gain in order to give adequate volume at the reproducing loudspeaker. An advantage given by working at low impedance is that a long connecting cable can be used without incurring losses due to self-capacitance in the cable. Also, stray pick-up of mains hum, radio signals and other forms of interference is greatly reduced when compared with high impedance operation.

When the function switch in the main unit is set to the "Send" position, the local loudspeaker is connected to the amplifier input and the amplifier output is coupled by the connecting cable to the slave loudspeaker. The functions of the two loudspeakers are now reversed: the loudspeaker at the main unit is employed as a microphone and the amplified sound signal is reproduced over the slave loudspeaker.


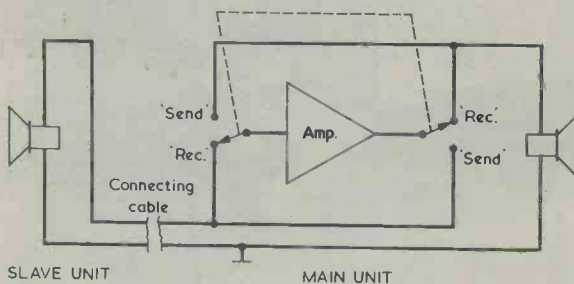


Fig. 1. A basic amplifying intercom system. According to the position of the "Send-Receive" switch in the main unit one or other of the loudspeakers functions as a microphone. The system has the disadvantage that the slave unit cannot call up the main unit when the amplifier is switched off

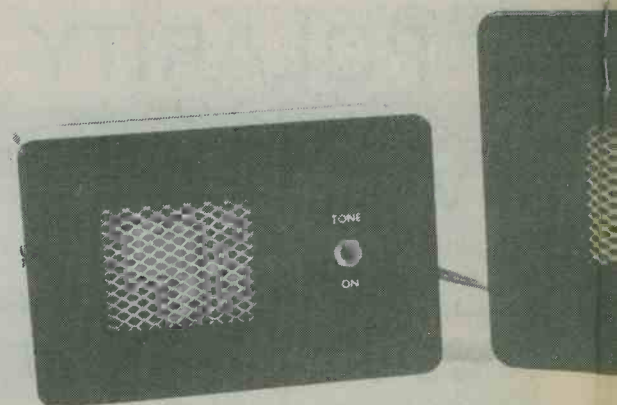

A picture taken just to show the neat microphone practice they have to be separated from



# INTERCOM



The main unit. At the right of the front panel S1 is at the top, S2 is in the middle and S3 is at the bottom

addition to any household

quality from slave station

An obvious shortcoming of this system is that a call facility is available in one direction only. It is possible for a person at the main unit to call up the slave unit by simply setting the function switch to "Send" and speaking into the main loudspeaker. However, it is not possible for the slave unit to attract the attention of someone at the main unit. Additional circuitry must be incorporated in the design to give the slave unit a calling up facility.

The method employed in the present system is illustrated in Fig. 2. The slave station is equipped with a battery supply, a very simple and inexpensive audio oscillator and a d.p.d.t. "Call" switch. This switch is spring biased so that it normally switches off the supply to the oscillator and connects the slave loudspeaker to the connecting cable. When it is put in the "Call" position, power is applied to the audio oscillator and the oscillator output is coupled to the connecting cable, thereby causing an audio tone to be reproduced by the main station loudspeaker. The slave unit switch is biased away from the "Call" position so that the slave unit loudspeaker is normally in circuit all the time,

ready to receive a call from the main unit. The bias ensures that the switch cannot be accidentally left at or knocked into the "Call" setting.

The call facility requires a second biased switch at the main unit, this being normally in the "Standby" position, where it ensures that the main unit loudspeaker is connected to the connecting cable ready to receive a call from the slave unit. When it is required to use the intercom for 2-way conversation, this switch is held in the "Operational" position and it connects the main unit loudspeaker to the same send-receive switching circuit that was shown in Fig. 1. Reference to Fig. 2 will show that, when the slave unit calls up, the output of the audio

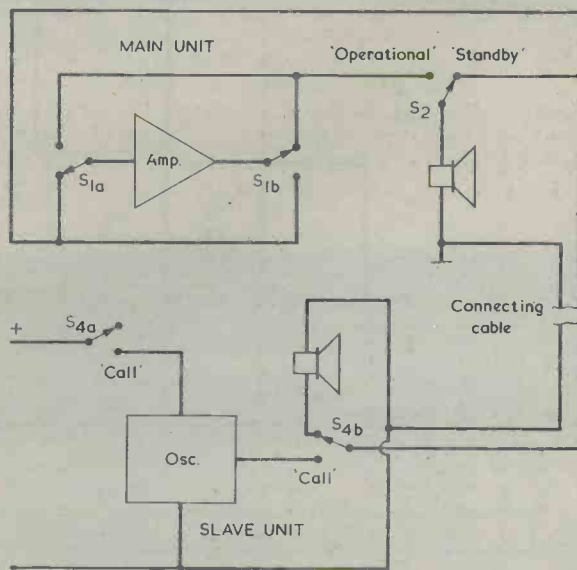


Fig. 2. A more complex version which permits calling up from the slave unit. The switches are given the same number references that they have in the full circuits



matching appearance of the two stations. In each other to prevent acoustic feedback

oscillator is fed to the input or output of the amplifier according to the position of the send-receive switch. This does not cause any damage to the amplifier nor does it result in any significant amount of the audio tone signal being diverted from the loudspeaker. There are similarly no ill effects if the slave unit switch is inadvertently set to "Call" whilst the main unit switches are at "Operational" and "Receive", in which instance the main unit loudspeaker is not connected across

the connecting cable. Although it is capable of giving an acceptably loud call signal from the main unit loudspeaker, the audio output power from the slave unit oscillator is relatively low.

Not shown in Fig. 2 is an on-off switch for the main unit amplifier. This is turned off at the main unit when the intercom system is not in use, and is turned on when the main unit wishes to call the slave unit or when a call has been received at the main unit from the slave unit.

## COMPONENTS

### Resistors

(All  $\frac{1}{4}$  watt 5% unless otherwise stated)

R1 2.2M $\Omega$ 10%	R7 2.7M $\Omega$ 10%
R2 4.7k $\Omega$	R8 180 $\Omega$
R3 10k $\Omega$	R9 4.7k $\Omega$
R4 10k $\Omega$	R10 39k $\Omega$
R5 680 $\Omega$	R11 33 $\Omega$
R6 47k $\Omega$	

### Capacitors

C1 330 $\mu$ F electrolytic, 10 V. Wkg.
C2 0.33 $\mu$ F type C280
C3 2.2 $\mu$ F electrolytic, 63 V. Wkg.
C4 0.1 $\mu$ F type C280
C5 100 $\mu$ F electrolytic, 10 V. Wkg.
C6 100 $\mu$ F electrolytic, 10 V. Wkg.
C7 22pF ceramic plate
C8 100 $\mu$ F electrolytic, 10 V. Wkg.
C9 0.1 $\mu$ F type C280
C10 10 $\mu$ F electrolytic, 10 V. Wkg.
C11 0.22 $\mu$ F type C280

### Semiconductors

TR1 BC109	IC1 CA3130T
TR2 BC109	IC2 555

### Switches

- S1 d.p.d.t. miniature toggle.
- S2 s.p.d.t. miniature toggle, biased one way
- S3 s.p.s.t. miniature toggle
- S4 d.p.d.t. miniature toggle, biased one way

### Loudspeakers

LS1, LS2 miniature moving coil, 50  $\Omega$  to 80  $\Omega$  impedance

### Batteries

- BY1 9 volt battery type PP6
- BY2 9-volt battery type PP3

### Miscellaneous

- 2 plastic cases (see text)
- Veroboard, 0.1in. matrix
- Connecting cable, 2-way "figure of 8" type, length as required
- 2 battery connectors
- 2-way terminal block (see text)
- Speaker fabric
- Wire, nuts, bolts, etc.


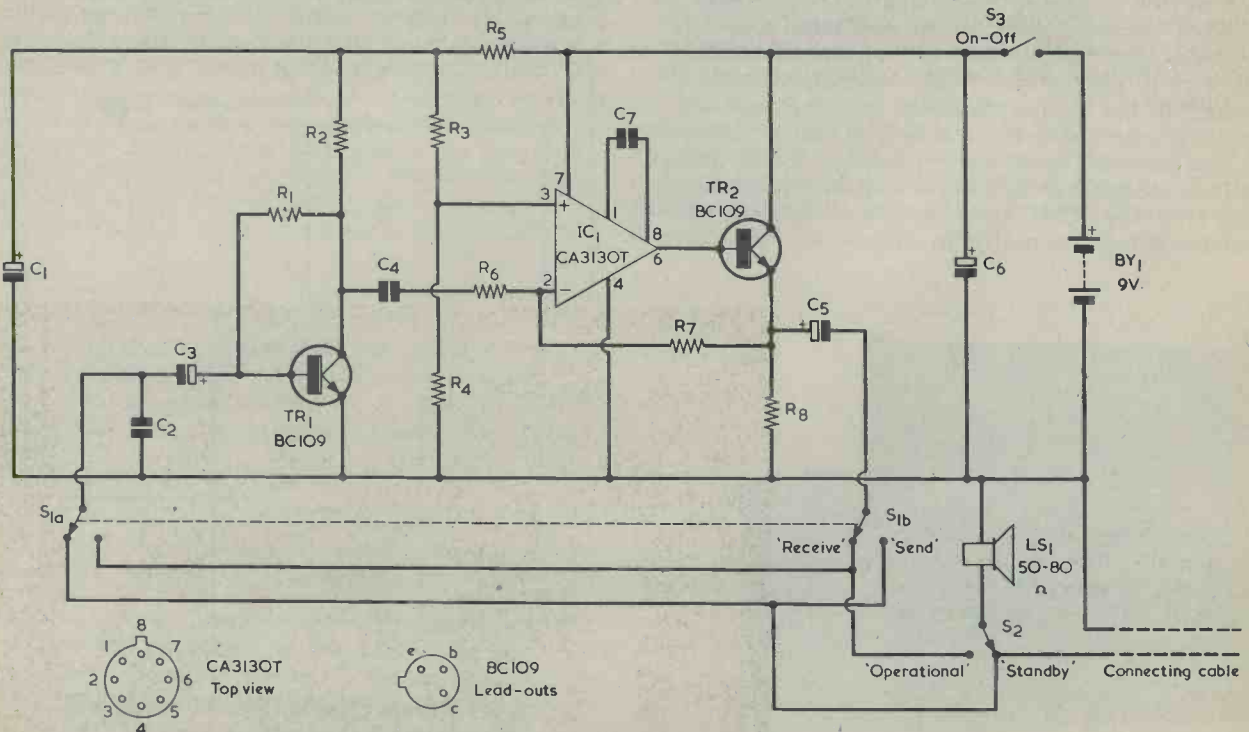


Fig. 3. Full circuit diagram for the master unit in the intercom system

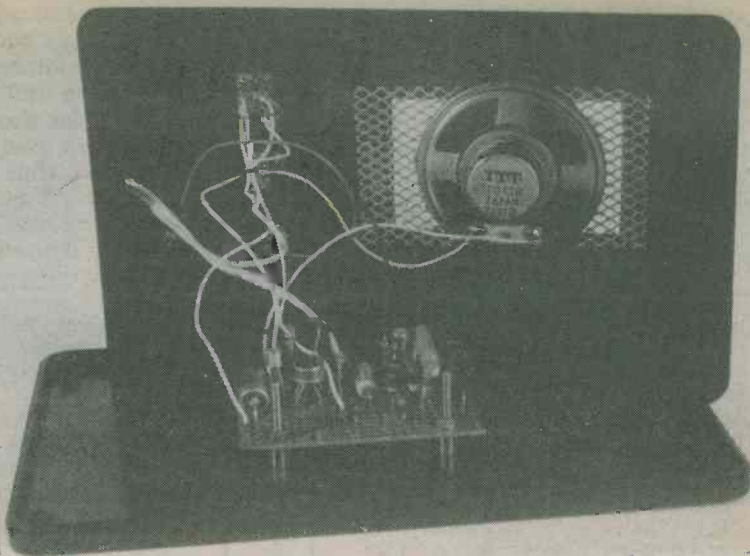The Veroboard component module for the main unit is bolted to the rear panel of the case



### MAIN UNIT CIRCUIT


The circuit for the main station is shown in Fig. 3. Only a low power output is required in this application, and the unit is unlikely to be used for long periods since equipment of this type is normally employed only to pass short messages. In consequence a very simple Class A amplifier is used instead of a more complex Class B circuit.

At the input, C2 is an r.f. filter capacitor, and its high value ensures that no r.f. break-through occurs. It causes no significant a.f. treble attenuation because of the low impedance of the slave unit loudspeaker when used as a microphone. TR1 is connected in a conventional high gain common emitter pre-amplifier stage, and it provides slightly more than half the overall voltage gain of the amplifier.

The output stage employs operational amplifier IC1, connected in the inverting mode, and the buffer emitter follower TR2 to give a suitably low output impedance. R7 and R6 provide a negative feedback loop which sets the voltage gain of the output stage at approximately 57 times. The CA3130T employed for IC1 does not have an internal compensation capacitor, and this function is provided by the discrete component, C7.

Despite the use of Class A output, good supply decoupling is required due to the high amplifier gain, and this is provided by C1, R5 and C6. Apart from on-off switch S3, the switching circuit is the same as that of Fig. 2, which has already been explained. The current consumption of the amplifier is approximately 25mA, which gives many hours of operation from the PP6 size 9 volt battery employed.

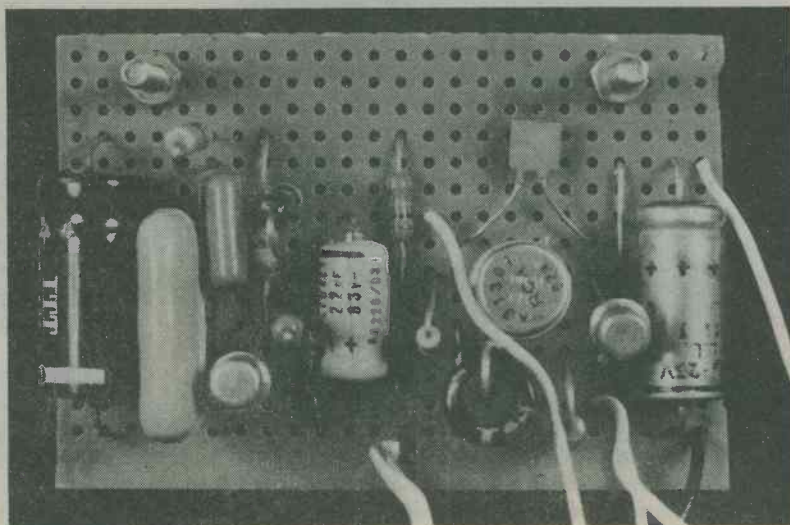The main unit component module. This is secured in place by two 6BA bolts and nuts with spacing washers



The slave station. The only control which this has is the "Call" switch, S4



## SLAVE STATION UNIT

The circuit of the slave station appears in Fig. 4. The audio oscillator uses the popular 555 timer i.c. in the astable mode. Timing components R9, R10 and C9 give an operating frequency of about 175Hz, and the frequency can be altered if desired by changing the value of C9. The frequency of oscillation is inversely proportional to the value of this component.

A low impedance rectangular waveform is available at pin 3 of the 555, and this is coupled to "Call" switch S4 by means of d.c. blocking capacitor C10 and an r.f. filter which is comprised of R11 and C11. This filter is needed to attenuate high frequency harmonics present in the 555 output, as these could be radiated by the connecting cable and possibly cause radio interference.

The current consumption of the oscillator is about 30mA. This can be supplied economically by a PP3 size 9 volt battery, as the call oscillator will only be used intermittently for brief periods.

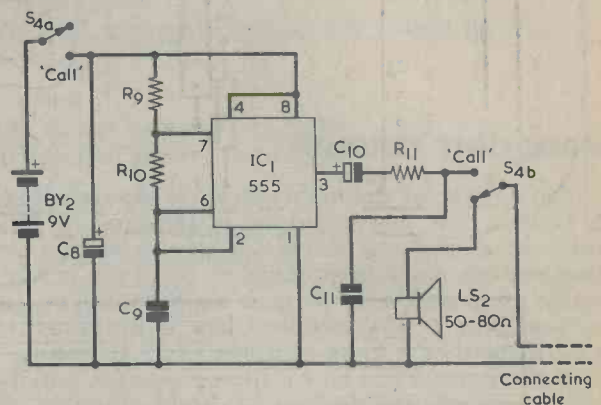



Fig. 4. The slave unit circuit. When S4 is set to "Call" an audio tone is sent to the main unit

## CONSTRUCTION


The prototype main unit is housed in a Verocase type 75-2861D which measures approximately 180 by 110 by 55mm., and the slave unit in a Verocase type 75-2860J having approximate dimensions of 120 by 80 by 35mm. These cases are available from Maplin Electronic Supplies under catalogue numbers LH51F and LH50E respectively. (The Verocases are not listed in the Maplin catalogue current at the time of writing, and are shown in the catalogue supplement for May 1979.)

A speaker aperture must be made in the front panel of each case and its size and shape can be judged from the photographs. The apertures can be cut out by means of a fretsaw or a coping saw. A piece of speaker "fret" or fabric is glued in place behind each aperture. Few miniature speakers have any integral mounting arrangements, and need to be glued in position. A good quality adhesive such as Bostik No. 1 or an epoxy resin should be used, and only a small amount should be applied to the front rim of each speaker, which is then glued behind the "fret" or fabric. Take care not to get any adhesive onto the speaker diaphragms, as this could impair performance.

RADIO AND ELECTRONICS CONSTRUCTOR

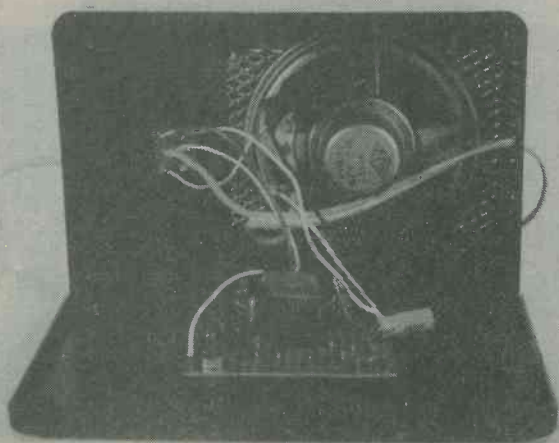

Inside the case of the slave station. The Veroboard component panel is mounted to the rear of the case in the same way as occurs in the main unit housing

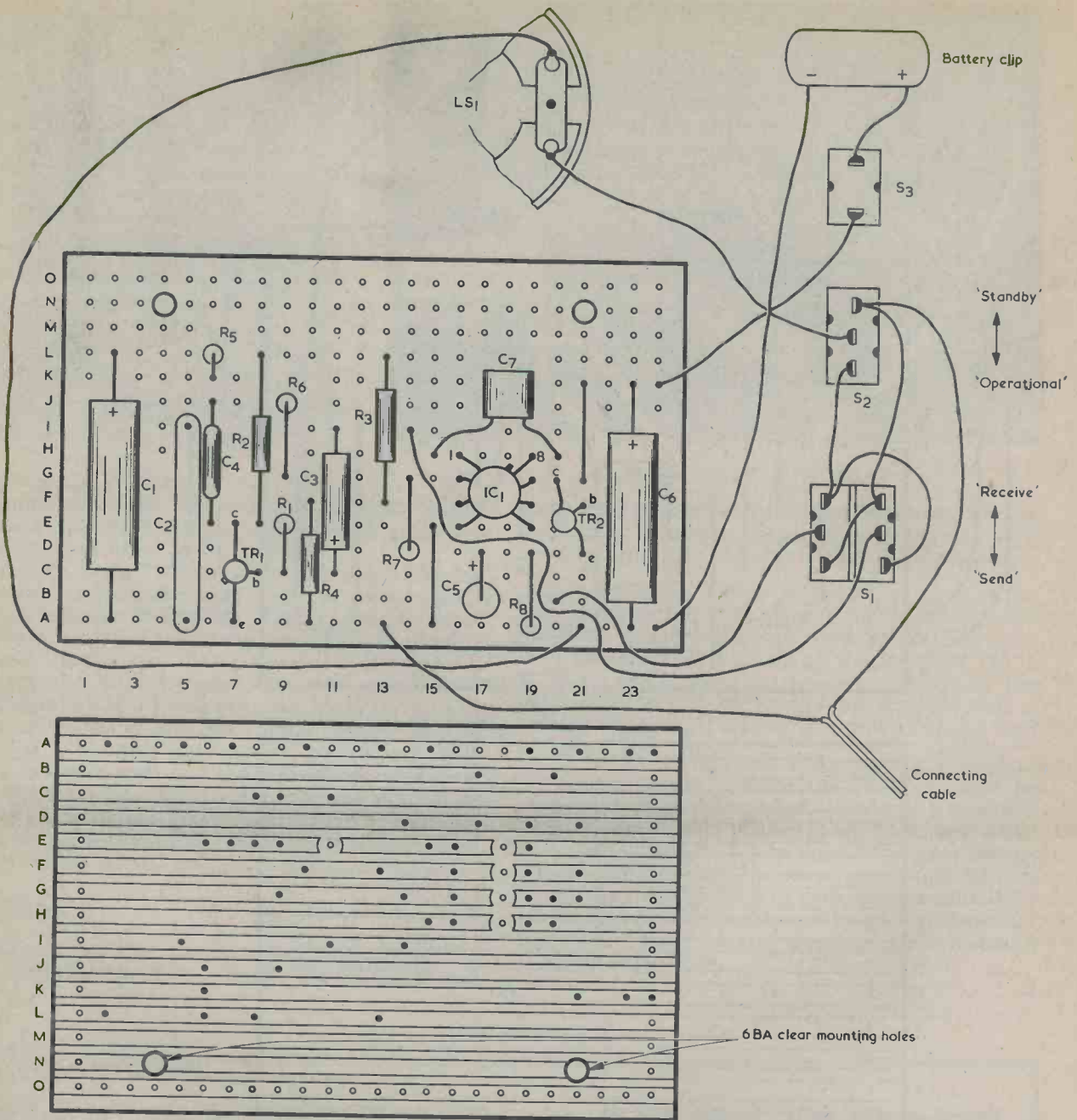

**Fig. 5. Details of the wiring at the main unit. Nearly all the components are assembled on a Veroboard panel. The arrows and legends alongside S2 and S1 indicate the contacts which close for the functions indicated**

Most of the main unit circuitry is wired up in an 0.1in. matrix Veroboard having 15 copper strips by 24 holes. This is illustrated in Fig. 5, which also shows the wiring external to the board. When the veroboard panel has been cut out the 5 breaks in the copper strips are made, after which the two mounting holes are drilled out. The components are

then soldered into position. IC1 has a MOS input stage, and the normal handling precautions should be taken. It should be the last component to be soldered to the board and it should be kept in its protective packaging until this time. It should then be handled as little as possible and soldered into circuit with an iron having an earthed bit.


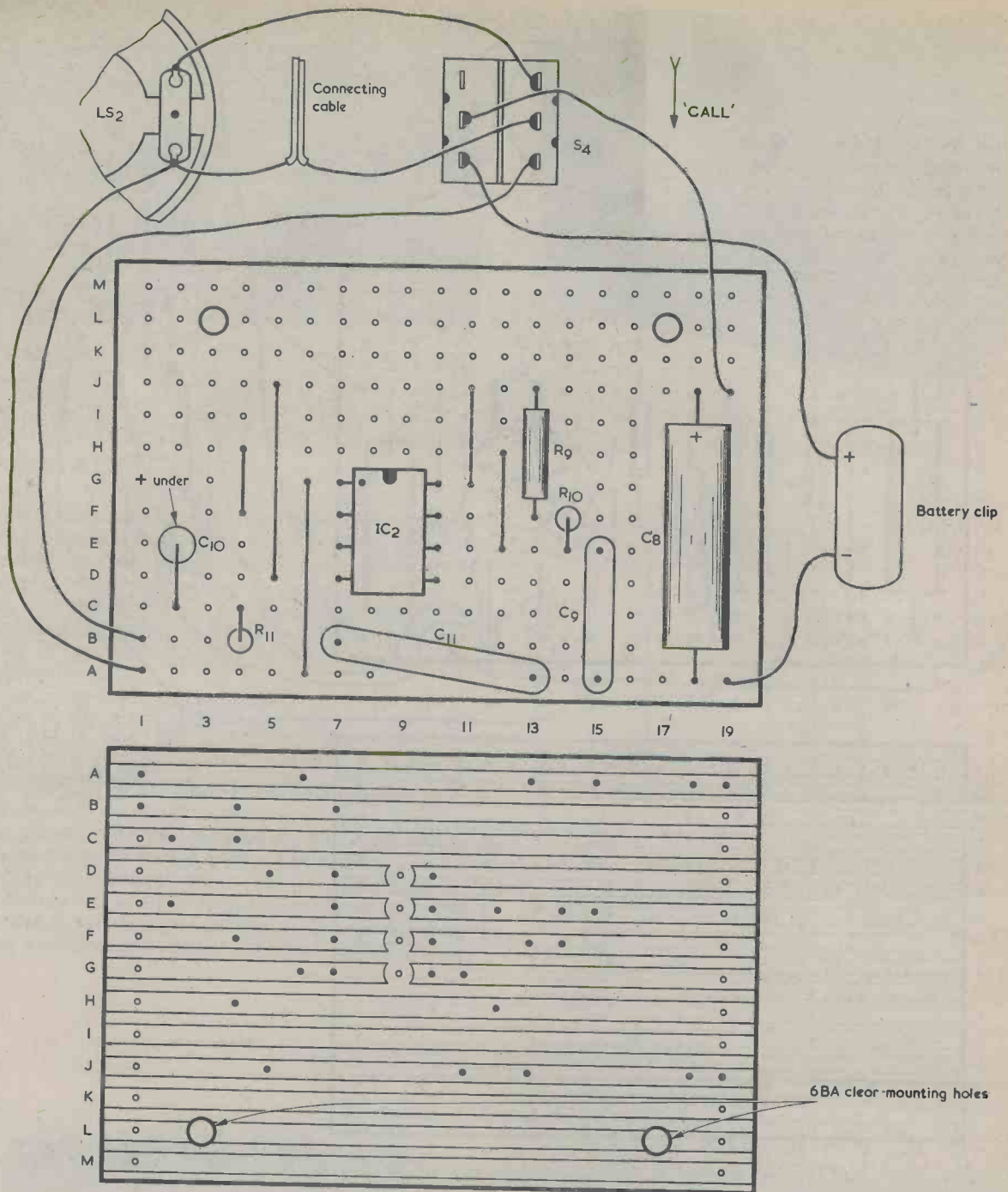


Fig. 6. Wiring details for the slave unit. Again, a Veroboard panel provides a convenient means of wiring up the components. C10 should be positioned in the manner shown in the photograph of the board assembly

When the component panel has been completed it may be wired up to the remaining components external to the board. Remember that S2 is biased to the "Standby" position. The Veroboard is then mounted on the rear panel of the case by means of two 6BA bolts and nuts, with spacing washers to keep the board underside clear of the rear panel. Ensure that the Veroboard components will not touch the loudspeaker when the rear panel is fitted to the case.

The main circuitry of the slave station is assembled on another Veroboard panel of 0.1in. matrix, this having 13 copper strips by 19 holes. It is prepared, wired up and mounted in the same general manner as the other Veroboard panel. Remember that S4 is biased away from the "Call" position. In this instance it is even more important to ensure that the components do not foul the speaker, as the slave unit case is shallower than the master unit case. In consequence, the board should

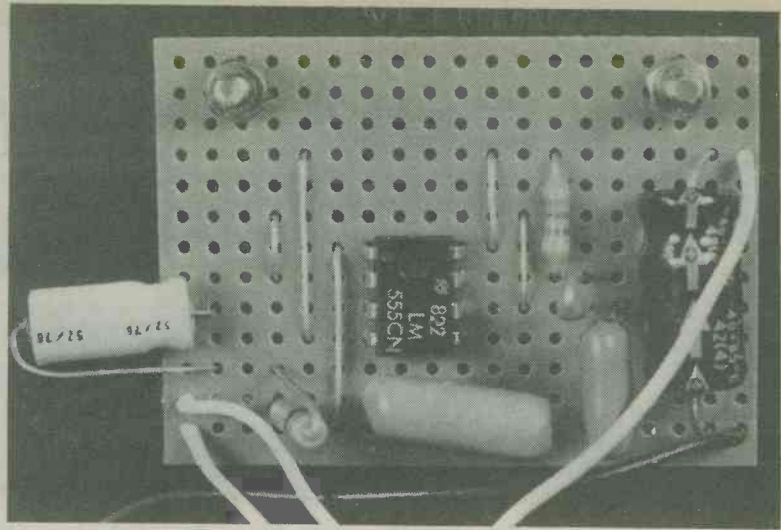Due to the shallowness of the slave unit case, care has to be taken to prevent the Veroboard components fouling the loudspeaker. It is for this reason that C10 leads have been bent so that the capacitor projects sideways from the board



be mounted on the rear panel in a position which ensures that there is adequate clearance when the rear panel is fitted to the case.

In both units there is adequate space for the battery required, and these may be secured with simple clamps, if desired. The connecting cable between the units passes through a hole in the side of each case. Since this may raise difficulties in routing the wire between the two units, it is desirable to add a 2-way terminal block on the outside of the slave unit rear. This can be used to provide a junction between the connecting cable from the main unit and the connecting cable from the slave station, thereby allowing the connecting cable to be routed and cut to the desired length. The use of the terminal block also enables a final check to be carried out more easily.

## TESTING

When completed, the system is ready for testing and installation. The stations should be spaced

away from each other by at least 5 metres (16ft.) as there may otherwise be acoustic feedback, with howling from one or other of the loudspeakers.

In some cases it may be beneficial to alter the gain of the amplifier to allow for loudspeakers with lower or greater efficiency than usual. The gain may be increased by raising the value of R7 to 4.7M  $\Omega$ , and it may be reduced by lowering the value of R7 to 1.5M  $\Omega$ . Ensure that the alteration is carried out using a soldering iron with an earthed bit to prevent damage to IC1.

This connecting cable to the slave unit may be connected either way round. However, it is worth checking the "Call" facility to the main unit when S1 is set to "Receive" with the cable connected one way round and then the other way round. If it is found that one method of connection results in a louder call tone from the master unit loudspeaker then that is the method of connection which should be finally adopted.

# ELECTRONIC CATALOGUE

Featuring 48 large pages plus an index, the 1980 Greenweld component and equipment catalogue has now become available. Many new lines have been introduced and a welcome fact is that a high proportion of prices have actually been reduced. A large number of items are priced with discounts for quantity.

The catalogue embraces a very wide range of components having particular interest to home constructors as well as to retail outlets, and includes a reference to Greenweld's associate company, Technical Circuits 79, who are specialists in printed circuits and can process a design from layout to the completed board. New items introduced

include a regulated power supply, an audible warning device and a 40 watt amplifier module, these all being exclusive Greenweld designs. There is also a comprehensive range of linear i.c.'s CMOS devices, voltage regulators and transistors. An unusual inclusion consists of storage trays and drawers.

Included with every catalogue is a first class reply-paid envelope, an order form and the latest Bargain List. The catalogue costs 40p plus 20p postage, which may be recouped from five 12p discount vouchers inside the back cover, and the full address of Greenweld is Greenweld, 443 Millbrook Road, Southampton, S01 0HX.



series  
No. 9

*really explains*  
*microprocessors*

By Ian Sinclair

# THE STATUS REGISTER

The status register of the CPU is unlike any of the other registers we have considered so far. All the other registers store one or two bytes of bits, and each byte represents a binary number, which may be an address, a data number or a code number representing a letter or other symbol. In the status register, though, each bit is a separate signal, and the complete set of bits doesn't represent anything in particular. In an 8-bit status register, the 8 bits don't really behave like a byte of data, to be added to or subtracted from other bytes, but we may very well wish to AND, OR or XOR the bits in the status register with the bits contained in a byte that is in the accumulator.

Before we start on the uses of the status register, let's go over what each bit does. Different types of CPU use their status registers in different ways, but there are nearly always four bits labelled zero (z), carry (c), overflow (o) and sign (s).

## CARRY BIT


Now we've met the carry bit already — it's changed (or set) from zero to 1 when two 8-bit binary numbers are added and there is a carry out of the highest order (8th) bit. The carry, in other words, acts as a temporary ninth bit in such an addition. If the numbers that are being added are two bytes long, the carry must be added in to the next two bytes and the carry flag reset to zero for the next time.

The overflow status bit (or flag) is not too easy to explain until we have discussed signed binary arithmetic. For the moment, take it that a carry out of the 7th bit (Fig. 2) cannot always be loaded into the 8th bit without causing an error, because the 8th bit is being used to represent the sign (+ or -) of the number. When this happens, the carry

out of the 7th bit is loaded into the OV (for "overflow") bit of the status register — in microprocessor jargon, the overflow bit is set.

The zero flag is straightforward — this bit is set to logic 1 if an operation in the accumulator causes a zero result. If an addition or subtraction leaves zero in the accumulator, then the status flag is set to 1. If a number is left in the accumulator, the zero status flag is left at 0. We make use of this for programming jumps, which may take place when the accumulator is at zero (flag at 1) or when the accumulator is not at zero (flag at 0). The other flag which is always provided is the sign(s) flag which is set to 1 when the byte in the accumulator has a logic 1 in the highest place (more on sign in Part 10).

Now these are the normal status flag bits which will be found on any microprocessor, but they are just four bits out of a possible eight. How the other four bits of the status register are used depends very much on what the designer of the CPU had in mind and so we can expect considerable differences between different microprocessor chips. The INS8060 (SC/MP), for example, has three flag bits

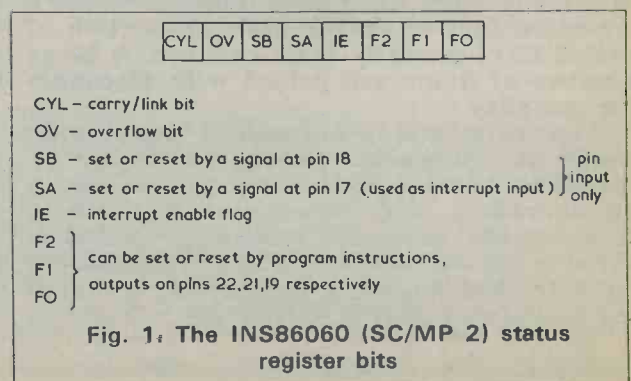



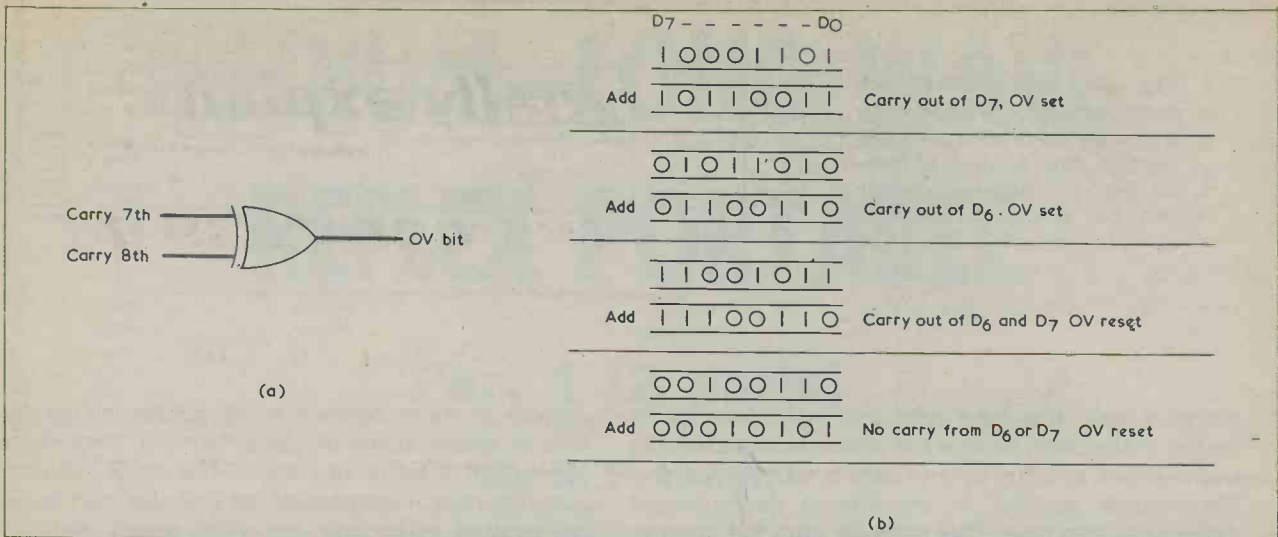


Fig. 2. The overflow bit. (a) The internal logic circuit. (b) Example showing when the overflow bit is set (1) or reset (0)

which can be set (to 1) or reset (to 0) by an instruction in the program, and which will cause the same voltages to appear at pins on the chip. This allows external devices to be operated under program control without the complication of input/output ports and is a popular method of using the SC/MP to generate square waves by alternately setting and resetting one of these status flags.

The 8080 has no overflow flag (because an overflow signal can be obtained on other ways), but has a parity flag and an auxiliary carry flag. The parity flag is set to 1 when an operation leaves the accumulator with an even number of 1's — as described earlier in Part 7, this allows the CPU to detect a byte which has an error. The auxiliary carry flag is used for BCD addition and subtraction, this flag is also used on the Motorola M6800 and the Mostek 6502.

### FLIP-FLOPS

The status register is not, however, just a set of flip-flops put in to record what happens in the accumulator. When a carry flag is set, for example, a bit exists which has to be added in to the next byte, if the number is a two-byte number. Practically every instruction that the microprocessor program uses will have an effect on one of the flag bits of the status register and these effects have been carefully thought out by the designers. A microprocessor instruction set, such as we shall examine in Part 11, will show which status flags are set by what instructions. A few of these flags may be used only occasionally — for example, if the microprocessor is used only for machine control the parity flag may never be used, since parity is used only to check if a coded letter or character is correct — it does not apply to numbers.

The use that is made of status flags, other than the obvious use of the carry flag in arithmetic, is in deciding when a program will branch. Now branching is an idea which will, once again, be familiar to readers who have followed the "Tune-in

to Programs" series which started in the January, 1979, issue of *Radio & Electronics Constructor* for new readers a quick summary is as follows. Very often in a program we want to go one or two ways depending on the value of a quantity in the accumulator. We might, for example, use a program to load seven bytes of data in from one part of memory and transfer them to another part. How can we instruct the micro-processor when to stop? The usual method is to load the number 7 (in binary) into a memory, unload a byte, reload it, take out the number 7 from the memory and decrement it, making 6. Now at this point, we instruct the microprocessor to compare the number in the accumulator with zero. If the number is more than zero (and 6 certainly is) then the number 6 is returned to


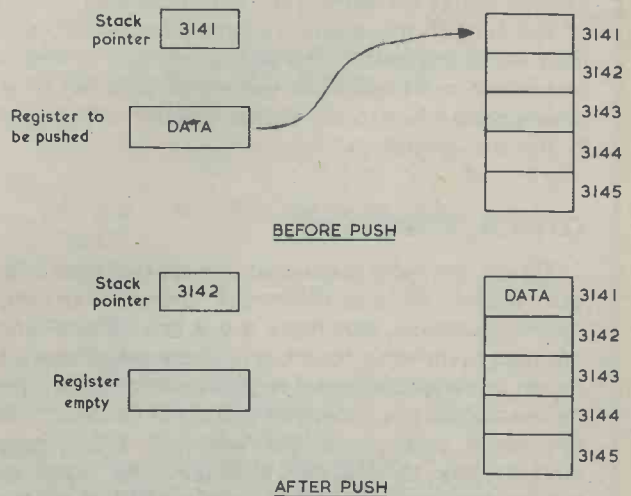


Fig. 3. Using the stack pointer. The stack pointer contains the address of the first vacant memory in the stack. After a push operation, the stack pointer is incremented so that the next push will be to the next vacant position. The counter is automatically decremented before the pop operation

**Fig. 4. Direct Memory Access (DMA).** A DMA control chip generates address signals and control pulses, so that the microprocessor can be isolated and data written directly into the memory

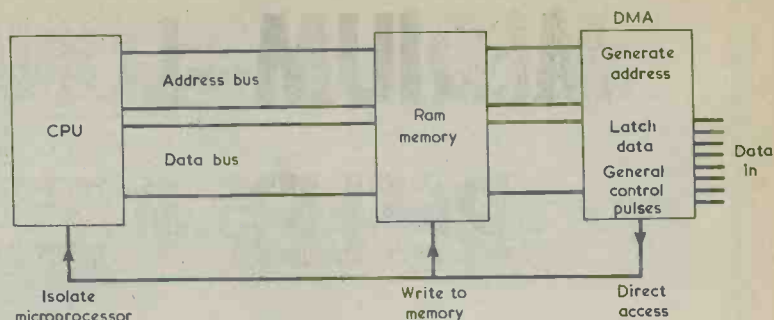

memory and the next program instruction is to return to the start, so that the action is repeated. On the next run, another byte of data is transferred, and the counter number in memory is decremented again to 5 this time. This goes on until the counter number at the last run is decremented to zero. When the compare-to-zero step is made, the program now skips or branches — the next step is not a return to the start, but a different part of program.

## BRANCH INSTRUCTIONS

Branching is extremely useful, and there are very few useful programs which do not include branching of some type — just to give one example, we can test the byte in the accumulator to see if it is equal to, less than, or more than a byte in memory.

Using four status flags makes eight possible branch instructions possible. The zero flag is, as the above example suggests, the one most used for branching, and the branch instruction can be to branch if the zero flag is set (accumulator 0) or not set (accumulator contains a number which is not zero). Similarly, instructions can be given for the overflow or sign flags. A set of instructions will also include codes for setting (to 1) or resetting (to 0) all of the bits in the status register. Some CPUs can load any number into the status register, or test the bits which are present in the status register, by exchanging the bits in the status register with the bits in the accumulator.

## OTHER REGISTERS

So far, we have discussed various registers which are found in one form or another in most microprocessors, but there are a few others which are also commonly found, and some which are a bit more unusual. Another register which very commonly appears is known as the stack counter; it has the same relation to the stack as the program counter has to ordinary memory. The stack was briefly described in Part 8 — it's a bit of memory which is the only piece of memory included inside the CPU (in several examples of CPU types) and it's being used to store the contents of registers while an interrupt is being served. The stack is used to store the data bytes, and the stack pointer is a register which is used to address the correct place in the stack memory. When bytes are being written into the stack memory (a push operation) the stack

pointer stores an address which guides the first byte into an empty piece of stack memory. Immediately after such a write operation, the stack pointer is automatically incremented, so that the next byte to be pushed goes into the next empty chunk of memory. The process works the other way round when data is being popped out of the stack again. This time, though, the stack pointer has to be decremented (1 subtracted) before reading, because the last push operation will have left the stack pointer aimed at the next spare bit of memory. If we popped this we would find nothing, — even worse we might find some random value left over from a previous operation. By arranging that the stack pointer is decremented before the pop operation, the CPU designer has ensured that the first byte taken back out of the stack is the same as the last byte stored there.

Not all CPUs have a stack memory built in, notably the INS8060 (SC/MP). When a stack is needed, a piece of RAM is used, addressed by one of the pointer registers (P2).

Most CPUs permit data to be moved from one register to another without passing through the accumulator. This type of operation has the advantage of being carried out very much more rapidly than a fetch-from-memory, because all the signals are inside the CPU chip. A few CPUs have a second accumulator register, some have three or more, so that several operations can be carried out without having to shift bytes around. In general, the way a CPU is designed very much affects the way in which it can be used, and it takes quite a long time to adapt completely from one to another. Learning to handle a new CPU is one thing — learning all its tricks and how to program it most economically is quite another!

Another point, not strictly belonging here but needing a mention, is direct memory access. Some CPUs can be switched so that they lose control of both address and data lines — this requires the CPU to be fitted with tri-state buffers, so that all the address and data outputs go to a high impedance. When this happens, bytes can be stored directly into memory without having passed through the accumulator, making it possible to store data whenever it comes along rather than when the program requests data. Direct memory access needs a separate i.c. which has an address register, and this separate i.c. must be under the control of the CPU.

*(To be continued)*

# MEDIUM-LONG WAVE REFLEX PORTABLE

## Part 1 (2 parts)

By R. F. Haigh

When embarking on the construction of a portable radio, the basic choice lies between a simple t.r.f. and a more complex superhet design. Although a high level of performance can be given by the superhet, complexity and cost are drawbacks, and small portables can be purchased for less than the cost of the components needed to construct a receiver of this kind. It must be admitted, however, that spurious responses and poor audio quality often mar the performance of inexpensive manufactured radios.

Bearing this in mind the author carried out experiments involving a number of t.r.f. circuits, and

it soon became apparent that a satisfactory level of sensitivity and selectivity can be obtained if manually controlled reaction is incorporated. The circuit finally adopted is based on a design due to G. W. Short which was published in this magazine some years ago. Incorporating currently available high gain transistors and modified by the addition of a reaction system, the sensitivity and selectivity of the receiver which forms the subject of this article approach those of a superhet. Using a suitable audio amplifier and a speaker of reasonable size, the overall performance will be found superior to that offered by most cheap imported radios.

### COMPONENTS

#### Resistors

(All fixed  $\frac{1}{4}$  watt 5%)

- R1 4.7k  $\Omega$
- R2 4.7k  $\Omega$
- R3 680  $\Omega$
- R4 100  $\Omega$
- R5 10k  $\Omega$
- R6 56  $\Omega$
- R7 1  $\Omega$
- VR1 100k  $\Omega$  potentiometer, linear
- VR2 4.7k  $\Omega$  potentiometer, log

#### Capacitors

- C1 4,700pF polystyrene
- C2 1,000pF polystyrene
- C3 10  $\mu$ F electrolytic, 10V. Wkg.
- C4 0.01 $\mu$ F polyester or ceramic
- C5 220 $\mu$ F electrolytic, 10V. Wkg.
- C6 470 $\mu$ F electrolytic, 10V. Wkg.
- C7 10 $\mu$ F electrolytic, 10V. Wkg.
- C8 1,000pF ceramic
- C9 470 $\mu$ F electrolytic, 10V. Wkg.
- C10 0.1 $\mu$ F polyester
- C11 220 $\mu$ F electrolytic, 10V. Wkg.
- C12 1,000pF ceramic
- C13 1,000 $\mu$ F electrolytic, 10V. Wkg.
- C14 0.1 $\mu$ F polyester
- C15 6,800pF ceramic or polystyrene
- VC1 500pF variable (see text)

#### Inductors

- L1 — L4 see text
- L5 2.5mH r.f. choke type CH1 (Repanco)

#### Semiconductors

- TR1 BC169C
- TR2 BC169C
- D1 OA47 (see text)
- IC1 TBA810AS

#### Switch

- S1 4-pole 3-way miniature rotary

#### Speaker


- LS1 3  $\Omega$ , 4  $\Omega$  or 8  $\Omega$ , 6in. round (see text)

#### Battery

- 9-volt battery type PP6 or PP9 (see text)
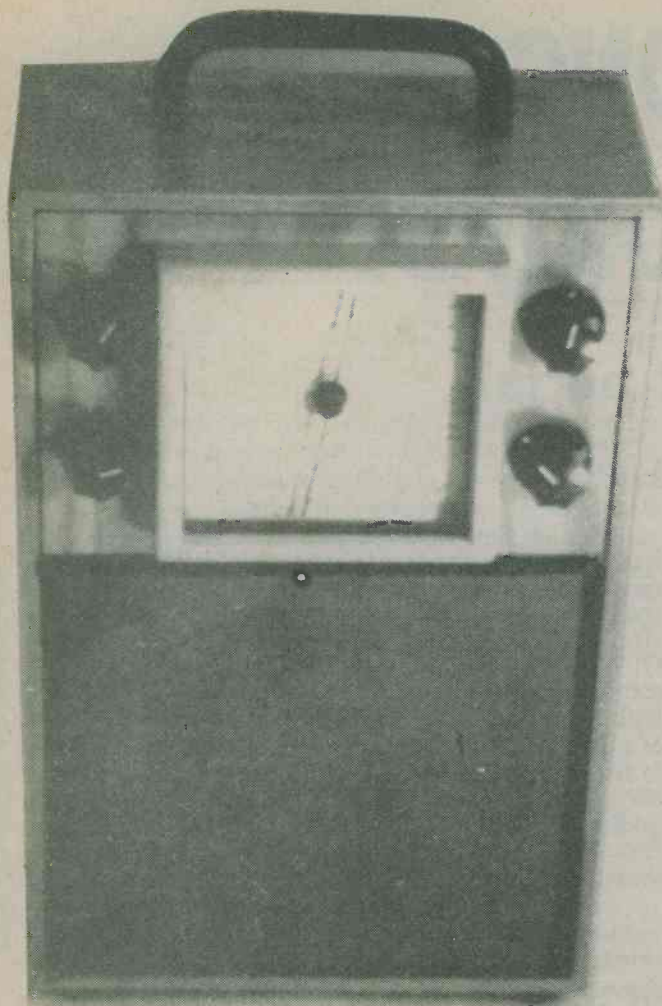
#### Miscellaneous

- 2 ferrite rods, 6in. x  $\frac{3}{8}$ in. diameter
- 26 s.w.g. enamelled wire
- 38 s.w.g. enamelled wire
- 2 28-way tagstrips,  $\frac{1}{4}$ in. pitch
- Drive drum, spindle and cord
- 4 knobs
- Battery connector
- 24 s.w.g. aluminium sheet (see text)
- Speaker fabric
- Materials for front panel, brackets, etc.
- Nuts, bolts, wire, etc.



The completed receiver housed in a simple cabinet

## CIRCUIT DESIGN

The complete circuit of the receiver is given in Fig. 1, and in this switch S1 is shown set to the medium wave position. Separate ferrite rod aerials are used for the two wavebands. This avoids absorption effects which are given when the coils are wound on the same rod; the long wave winding resonates with its own self-capacitance when switched out of circuit at a frequency in the medium wave band and it causes a "dead spot" at that frequency. L1 and L2 are windings in the medium wave ferrite rod aerial, whilst L3 and L4 are the long wave windings. L1 and L3 are tuned by VC1, and L2 and L4 couple the tuned circuits to the base of TR1 and also act as reaction windings.

TR1 and TR2 are connected in a reflex circuit and both transistors amplify at radio and at audio frequencies. TR1 acts in the common emitter mode at radio and audio frequencies. TR2 works as an emitter follower at radio frequencies, its collector being bypassed for r.f. by C4. Its r.f. voltage gain is therefore slightly less than unity, but it performs the desirable function of matching the relatively high impedance at TR1 collector to the low impedance of the diode detector circuit.

The germanium diode, D1, demodulates the signals developed across the r.f. choke, L5, and the resulting audio frequency signal is fed back via the aerial coupling windings to the base of TR1, which then amplifies these. This amplified signal is passed to the base of TR2 which, at a.f., functions as a common emitter amplifier. Thus, after two stages of a.f. amplification the audio signal appears across R2, the collector load of TR2, and it is then fed, via C7, R5 and volume control VR2 to the integrated circuit audio power amplifier, IC1.

## REACTION

A proportion of the r.f. signal is present in the output from D1, and the values of C1 and C2 have been chosen to ensure that the correct proportion of this is fed back to the tuned circuit via the base windings L2 or L4. Reaction is adjusted by VR1, which determines the collector voltage of TR1 and thereby controls its gain. In practice, the reaction control will be found to be extremely smooth and free from backlash. Weak signals which would otherwise be inaudible can be brought up to good loudspeaker volume, and selectivity is very much enhanced.

For regeneration to take place, the feedback has to be in phase with the signals picked up by each ferrite rod aerial and the base windings must be connected as shown in Fig. 1 to ensure this. In the diagram the letter "S" indicates the start of a winding and the letter "F" its finish. It will be noted that the long wave base winding is not connected in the same sense as the medium wave base winding. This is an unusual feature of the design, and clearly the circuit action is such that the phase of the feedback changes with signal frequency. This may be partly explained by the fact that the tuned windings are not physically connected into the reaction loop, whereupon the actual coupling of these windings into the loop is more complex than a first sight of the apparently simple reaction circuit might indicate.

## COMPONENTS

The components are readily available and few of them are in any way critical.

The 500pF air spaced variable capacitor VC1 should be a single-ganged component such as that available from Home Radio. Alternatively, it can be one half of a salvaged 2-gang capacitor, or the two gangs of a lower value capacitor can be connected together to give the required capacitance range. However, the capacitor employed should not have too great a depth or it may not fit into the layout. If the loss of the extreme low frequency end of the medium wave band can be accepted, a 365pF variable capacitor can be used. The 500pF component gives continuous coverage over the two bands from 1,800kHz (167 metres) to below 150kHz (2,000 metres).

The tuning capacitor is adjusted by way of a standard cord drive, and a suitable drive drum and spindle are available from Home Radio. A drive drum and spindle may also be obtained from an old discarded radio. Precise details here are not particularly important and are left to the constructor.

The r.f. choke, L5, is a 2.5mH Repanco component type CH1. In some reflex circuits it would need to be oriented for best results, but its orientation is not critical with the layout to be described. A

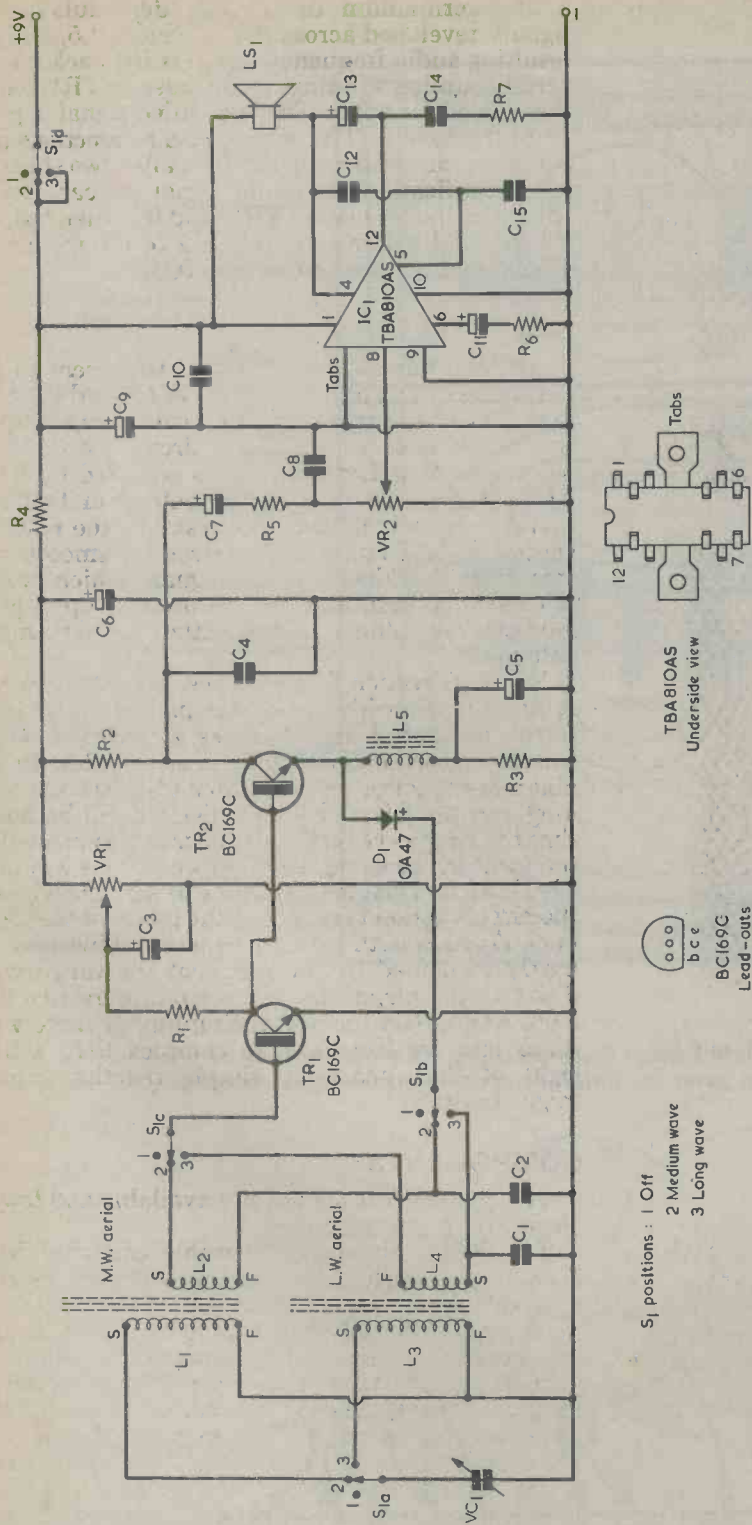


Fig. 1. The circuit diagram for the reflex medium and long wave receiver. The letters "S" and "F" alongside the ferrite aerial windings indicate "Start" and "Finish". The inset giving the i.c. pinout shows an underside view instead of the usual top view

number of high gain n.p.n. silicon transistors, including the 2N2926G and the BC108C, work reasonably well in the circuit, but the specified BC169C affords the greatest sensitivity. It is important that the high gain group "C" device should be used. It is found that almost any germanium signal detector diode, as well as the specified OA47, will prove suitable for D1. This diode must be connected with correct polarity or the set will not function at all.

A number of tagstrips are required, and these

can be cut from two 28-way tagstrips having tags at a pitch of  $\frac{1}{4}$  in. These tagstrips are available from Electrovalue.

The integrated circuit employed for IC1 can be obtained from Ambit International. It is capable of around 1 watt output when powered by a fresh 9 volt battery, and its no-signal current consumption is low, being less than 10mA. It will work into a 3  $\Omega$  load, and salvaged speakers of this impedance are often to hand. It will also function satisfactorily with 4  $\Omega$  or 8  $\Omega$  speakers.



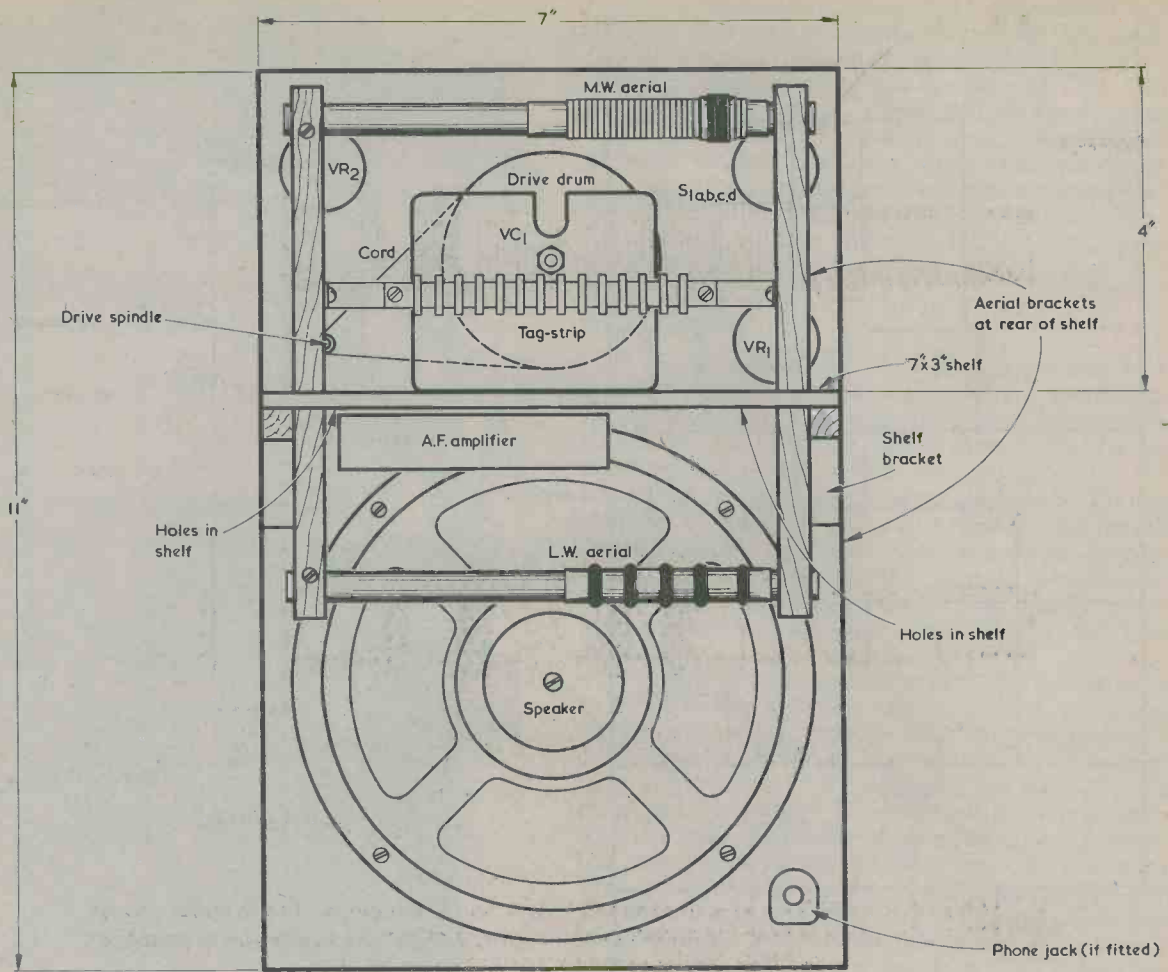



Fig. 2(a) General layout of parts behind the front panel. Dimensions may be slightly amended, if necessary, to cater for different speakers or variable capacitors.

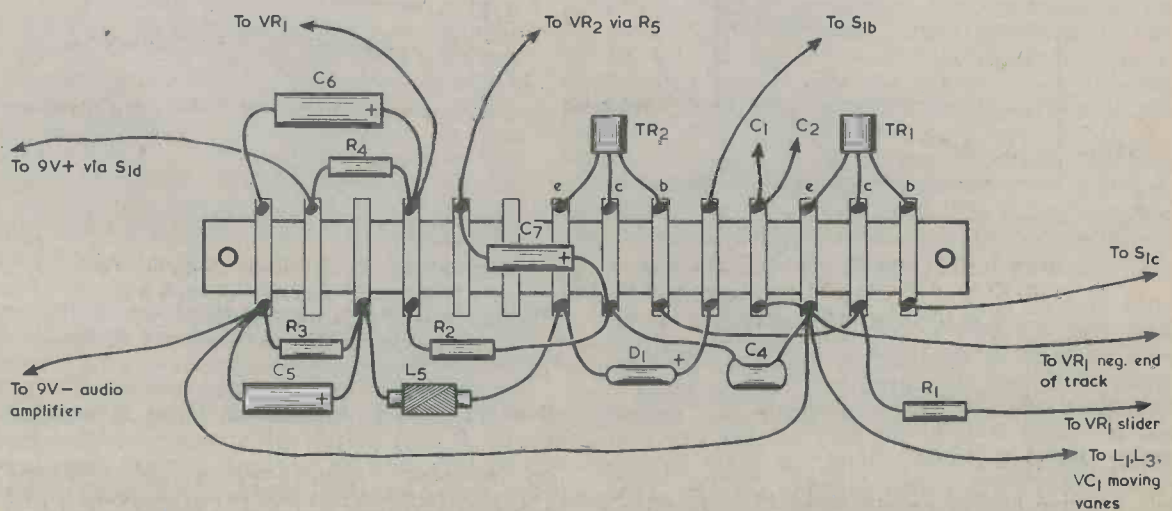

(c) Wiring up the 14-way tagstrip

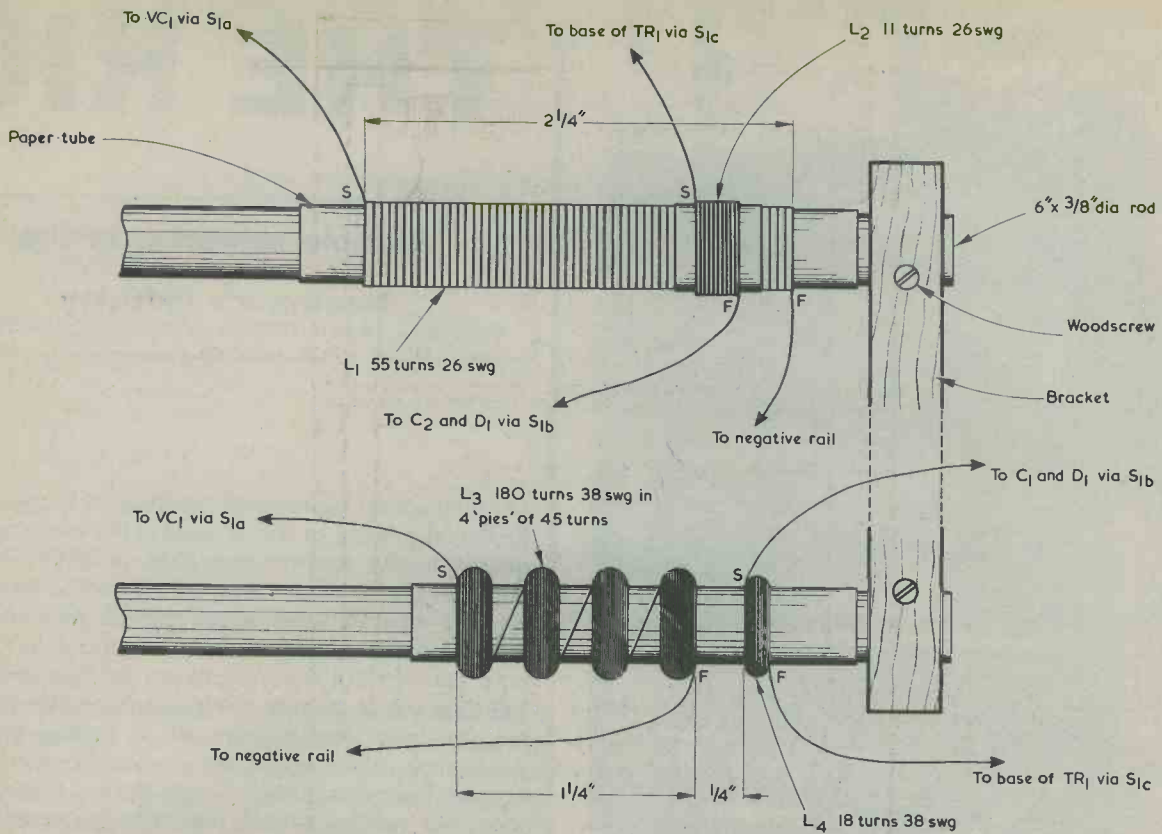

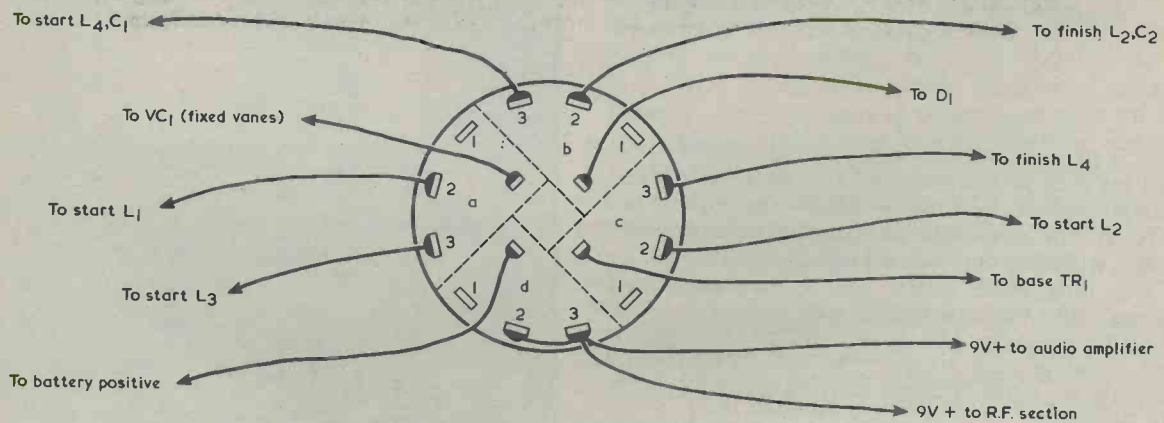(b) Details of the medium and long wave ferrite aerial windings. The woodscrew in each aerial mounting bracket is driven in sufficiently to hold the ferrite rod in position without applying excessive pressure on it




(d) Connections to the wachange switch. Before wiring to the switch check the positions of inside and outside tags with a continuity tester. Some switches may have relative tag positioning which is different from that shown here
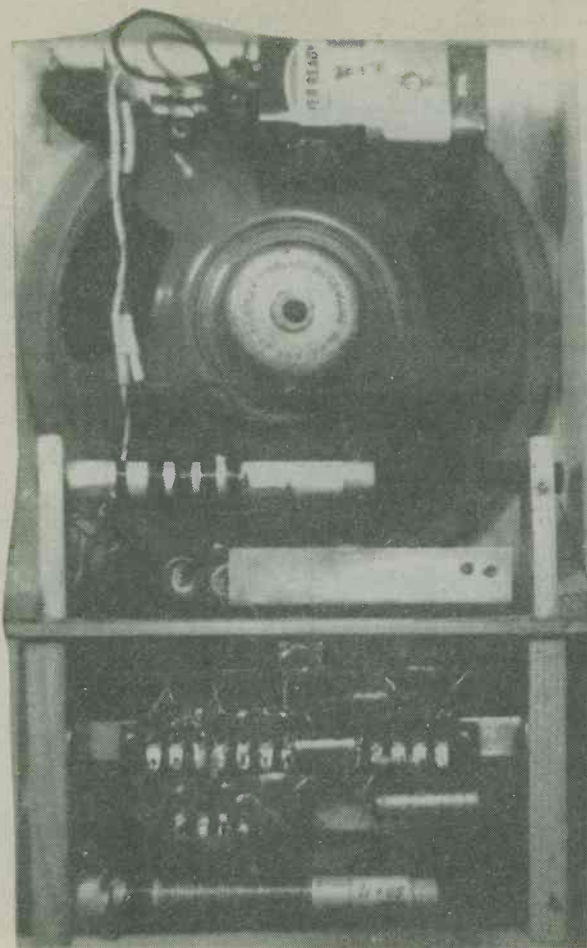
## AERIAL COILS

The general layout of the receiver is shown in Fig. 2(a), whilst Fig. 2(b) gives details of the ferrite rod aerial coils. Both rods are 6 in. by  $\frac{3}{8}$  in. diameter and paper tubes support the coils. These are form-

ed from stout writing paper wound round the rods and glued with balsa cement or a similar quick setting adhesive. The medium wave tuned winding, L1, consists of 55 turns of 26 s.w.g. enamelled wire spaced out over a length of  $2\frac{1}{4}$  in. A layer of sticky



Looking down on the rear of the receiver. The battery is on the loudspeaker side opposite to the r.f. section and audio amplifier

tape is placed over the negative rail end of the coil, and on this is close-wound the base winding, L2, which consists of 11 turns of the same wire. It is important that the base winding be wound over the tuned winding and not alongside it.

The long wave tuned coil, L3, consists of 180 turns of 38 s.w.g. enamelled wire wound in 4 "pies" of 45 turns each. The base winding is alongside it and consists of a single "pie" of 18 turns of the same wire. Approximate dimensions are given in the diagram.

As with Fig. 1, the letters "S" and "F" indicate the start and finish of each winding respectively. All turns must be wound in the same direction, and the windings may be smeared with balsa or polystyrene cement to hold them in position if required.

#### Editor's Note

The constructional details will be given in next month's concluding article.

To be concluded

# THE RIGHT

## Reliable soldering in the electronics industry

Tin-lead solder represents the second largest outlet for tin, and much of this is used in the electronics industry. In this fast-moving field, reliability is more important even than cost when components may have to operate unattended over a service life of many years. The preferred aim therefore, is to make sure that the soldered joints are as near perfect as possible when leaving the production line and this requires the development of a closely specified production plan which takes into account at all stages, from specification and design to manufacture and quality control, the need for good joints.

This is the theme of a film issued by the *International Tin Research Institute* which is intended as a guide towards achieving reliable soldering. It is essentially a training film and in order to present a more personalised approach, the services of Michael Rodd (best known for his work on BBC's TV Programme *Tomorrow's World*) was engaged as "presenter".



Michael Rodd in a public telephone box at Beaconsfield, for the film's opening sequence



# T CONNECTION...

Filming soldering operations at Standard Telephones and Cables, New Southgate.



The film opens with the presenter making a telephone call and he steps out of the telephone booth into the interior of a telephone exchange. He explains how modern communications systems employ many thousands of soldered joints, and reliability depends on the integrity of these joints. The viewer is then guided through the stages of printed circuit board production, which for simplicity are divided into four distinct steps "Specification, Evaluation, Control and Assessment" best

remembered by the acronym "SECA". "Specification" includes type of circuit board, location and disposition of conductive tracks and through holes, and finishes to protect the copper tracks. "Evaluation" of incoming materials, laminates and circuit boards, terminations and components is dealt with next, in a number of scenes showing typical operations in a quality control laboratory. Newer methods of testing for solderability, such as the surface tension balance and the globule tester are included in this sequence.

The next production stage is "Control", of the soldering process and the presenter takes the viewer to a typical Industrial assembly line, where boards are assembled, by hand forming and by automatic insertion, and then soldered. Factors influencing mass soldering operations such as wave soldering are illustrated and the need for control of solder bath composition and temperature and flux composition is stressed. Hot dipping is shown as an example of mechanical soldering and characteristics of the soldering iron for manual soldering are considered.

The final stage is "Assessment" and inspection personnel are seen subjecting completed boards to visual scrutiny. Photographic guides, which illustrate good and defective wetting and joints. Typical defects, such as bridging are presented in close-up, and re-working of faulty joints by hand soldering is also illustrated. The film ends with a recapitulation of the four basic SECA principles.

#### Editor's Note

The Right Connection, a 16 mm colour film with optical sound, produced for the Institute by Chess Valley Films Ltd., Little Chalfont, Bucks.

This film will be available soon on free loan from the Institute by arrangement. An accompanying booklet is currently being prepared.



Michael Rodd being filmed in the I.T.R.I. laboratories

# SHORT WAVE NEWS



## FOR DX LISTENERS

By Frank A. Baldwin

Times = GMT

Frequencies = kHz

### ● ITALY

Rome on **11800** at 1455, female announcer with station identification in French, guitar music then into a programme of local pops.

Rome on **11905** at 1854, young lady (YL) with the programme in Italian directed to Canada, Central America and the West Indies, scheduled from 1830 to 1905.

### ● SPAIN

Madrid on **11920** at 1900, male announcer (OM = Old Man) with the programme in Spanish intended for Europe, the Middle East and Africa, scheduled from 1800 to 2035.

### ● CANADA

Sackville on **11905** at 1905, OM with the world news in the English programme directed to Europe, scheduled from 1900 to 1930.

### ● ROUMANIA

Bucharest on **11940** at 1850, YL with a programme in French. Intended for European consumption, this programme is scheduled from 1830 to 1900.

### ● BULGARIA

Sofia on **11720** at 1930, OM with station identification and programme details followed by YL with a newscast in the English programme for the U.K. and Eire, scheduled from 1930 to 2000.

### ● KUWAIT

Kuwait on **11665** at 1933, YL with a newscast in the English programme, scheduled on this channel from 1800 through to 2100.

### ● MONTE CARLO

Trans-World Radio (TWR) Monte Carlo on **11725** at 1300, OM with station identification in English after the interval signal. A programme in Russian followed — "Govorit Monte Carlo" (Here is Monte Carlo).

### ● AUSTRALIA

Melbourne on **11870** at 1503, OM with a newscast in English. The schedule on this channel is from 1500 to 1730.

### ● MADAGASCAR

Radio Nederlands Relay on **11730** at 1920, OM with station identification at the end of the English programme for Africa, scheduled from 1830 to 1920.

### ● ANTIGUA

Deutsche Welle Relay on **11785** at 2130, OM with station identification at the commencement of the Portuguese programme for Brazil and Latin America, scheduled from 2130 to 2300.

### ● BRAZIL

Radio Tupi, Sao Paulo, on **11765** at 2127, OM with a talk in Portuguese during a sporting event. The power is 10kW and the schedule is unknown.

Radio Nacional, Brasilia, on **11780** at 2110, OM with an excited commentary on futebol (football = soccer). The power is 250kW and the schedule is from 1900 to 2400.

Radio Bandeirantes, Sao Paulo, on **11925** at 2123, OM with a commentary on a local sporting event. The power is 10kW and the schedule is from 2100 to 0305.

Radio Pernambuco, Pernambuco, on a measured **11867** at 2225, OM announcer with recorded local pops. The power is 1kW and the schedule is from 0800 to 0430.

### ● NORTH KOREA

Pyongyang on **11350** at 2205, YL with a talk in the Korean Domestic Service, scheduled on this channel and in parallel on **6600** from 2000 to 0300, 0400 to 0900 and from 1500 to 1800.

That completes a brief survey of the 11MHz band. Most of the stations listed are quite easy to log and should not present any great difficulty to most readers of these columns. The more difficult loggings follow:

### ● CHINA — REGIONALS

CPBS (Chinese People's Broadcasting Station) Peking on **3220** at 2150, OM with a talk in Chinese in the Domestic Service 1 programme, scheduled from 2000 to 2200 and from 1343 to 1735.

PLA Fuzhou, Fujian, on **4840** at 2210, YL in Chinese to Taiwan. The schedule is from 2000 to 0610 and from 0830 to 1900.

PLA Fuzhou on **4045** at 1513, OM in Chinese to Taiwan. The schedule is from 1000 to 0530.

YPBS Kunming, Yunnan, on **4760** at 1518, YL and OM with duet in a Chinese opera. The schedule is from 2150 to 0600 and from 0920 to 1600.

CPBS Changsha, Hunan, on **4990** at 1531, YL and OM in Chinese, Chinese orchestral music, heard under Yerevan on the same channel. The Changsha schedule is from 2105 to 1600.

CPBS Guiyang, Guizhou, on **3260** at 1531, YL with Chinese opera programme. The schedule is from 2130 to 0020, from 0150 to 0620 and from 0850 to 1605.

PLA Fuzhou, Fujian, on **2430** at 2225, YL songs in Chinese in the Network 2 programme. The schedule is from 1525 to 2100 but obviously extended on this occasion.

PLA Fuzhou, Fujian, on **2490** at 2215, OM and YL in Chinese in the Network 1 programme, scheduled from 1530 to 2230 on this channel.

PLA Fuzhou, Fujian, on 3400 at 1520, Chinese orchestral music, OM announcer in the Network 2 programme, scheduled here from 1330 to 2100.

Urumqi, Xinjiang, on 3990 at 1530, OM's with a rousing chorus in the Uigher programme scheduled from 2300 to 1730.

#### ● VIETNAM

Hanoi on a measured 4944 at 1527, OM in Vietnamese followed by a programme of local-type orchestral music in the Home Service 1, scheduled on this channel from 2130 to 1700.

#### ● INDONESIA

RRI (Radio Republik Indonesia) Palembang on 4855 at 2350, OM with songs in Indonesian. The schedule is from 2230 to 0115 (Sundays to 0700) and from 0900 to 1600. The power is 10kW.

RRI Palu on 3960 at 1522, OM and YL announcing in Indonesian followed by a programme of local-style music. The schedule is from 0900 to 1520 but closing time is variable. The power is 10kW.

RRI Bukittinggi, on a measured 3232 at 1529, OM announcements, YL with songs and local-type orchestral music.

#### ● NEPAL

Radio Nepal, Khumaltar, on 3425 at 1527, local-style music, YL with vocals. The schedule is from 0020 to 0350 (Sundays to 0450) and from 1150 to 1720. The power is 100kW.

#### ● MALAYSIA

Penang on 4895 at 1544, YL with a programme of songs together with local-type music. The schedule is from 2200 to 2300 and from 1000 to 1500, the power being 10kW.

Kuala Lumpur on 4845 at 1509, Indian-type songs and music in the programme, scheduled from 2130 to 0130 and from 0545 to 1530 to 1530 Monday to Friday, from 2130 to 0330 and from 0545 to 1530 on Saturdays; from 2130 to 1530 on Sundays. The power is 50kW.

#### ● NORTH KOREA

Pyongyang on a measured 3559 at 1538, YL with a talk in vernacular — presumably Korean. This station is listed on a nominal 3560 the schedule being from 0400 to 0050.

Pyongyang on 3015 at 2132, YL in Korean to South Korea, scheduled on this channel from 2000 to 0100, from 0300 to 0900 and from 1500 to 1950. The power is 120kW.

#### ● AFGHANISTAN

Kabul on 4775 at 1553, YL with a talk in English. The schedule is from 0030 to 0330 and from 1430 to 1630 with the Home Service 1; Foreign Service in Urdu from 1300 to 1400 and in English from 1400 to 1430 — but this has obviously been altered.

The power is 100kW.

#### ● THAILAND

Bangkok on 4830 at 1555, a programme of local music — lots of cymbals, drums and other percussion instruments — YL with songs. The schedule of this one is from 2200 through to 1600 and the power is 10kW. The frequency can at times vary to 4831.

#### ● INDIA

AIR (All India Radio) Kurseong on 3355 at 1533, YL with a newscast of local affairs in English — a relay of the Delhi news service in English. The

schedule of the Kurseong transmitter is from 1130 to 1700, the English newscast being timed at 1530. The power is 20kW.

AIR Delhi on 3365 at 1535, YL with the same programme as above but logged on a different occasion. The schedule is from 0025 to 0230 and from 1330 to 1740 with a programme for the Armed Forces from 1235 to 1315.

#### ● INDONESIA — 2

RRI Padang on a measured 4003 at 1518, a programme of what sounded like Indian-type music and songs, not a bit like an Indonesian broadcast. Oh well, I long ago ceased to be surprised at what one can hear on the short waves! The schedule of this one is from 2230 to 0045 and from 1000 to 1600. The power is 10kW.


RRI Jakarta on a measured 4774 at 1553, a programme of local music, YL with a ballad in Indonesian, newscast at 1600. According to the schedule, this one operates from a reported 1030 to 1505 on the occasion of special events only. I wonder what the festivities were about on this occasion! The power is 50kW and the signal was heterodyning with Kabul on 4775.


#### ● MOZAMBIQUE

Radio Mozambique, Maputo, on 4925 at 2140, OM with a song in vernacular together with a programme of local-style music. This is the B programme in Portuguese and vernaculars, scheduled from 0255 to 0600 and from 1600 to 2210. The power is 20kW but the frequency can vary up to 4926 on occasions.
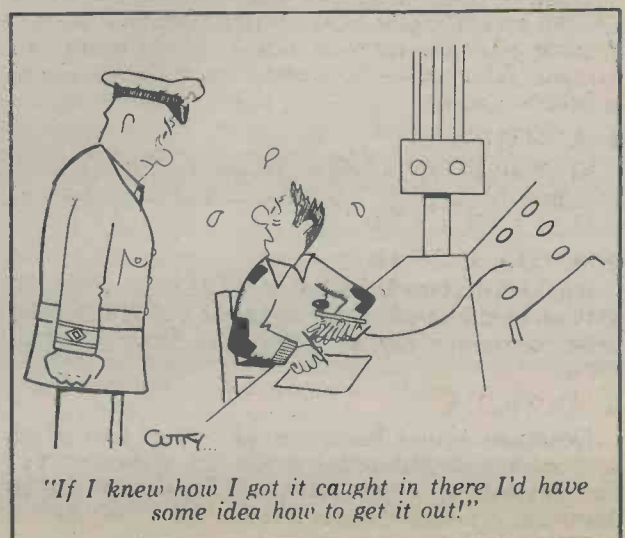
#### NOW HEAR THIS

Luang Prabang, Laos, on a measured 6997 at 2232, local-style music (similar to that often radiated by Radio Peking), YL with a plaintive song. The signal was wiped-out by commercial QRM at 2234. According to my information, this station should open at 2300, but obviously on this occasion it was varying from the norm. Or does it sign-on earlier? We shall now have to wait until the next Far East 'season' comes round — September through to March for best results.



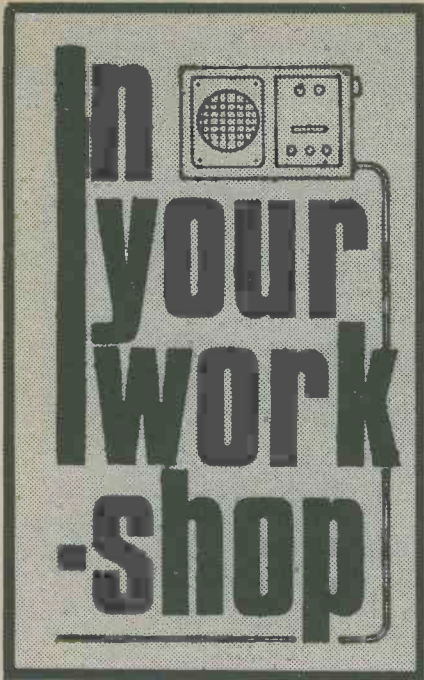

# MONOCHROME VIDEO FAULT

## A lack of vision

"Hallo," said Smity, looking at the "For Repair" rack, "I don't think we've had one of these in here before."

From his bench, Dick glanced over. A small monochrome television receiver in a neat white cabinet stood on the shelves.

"It's one of those Jap jobs," he remarked. "There seem to be plenty of that particular model in the TV shop windows these days."

"Humph," grunted Smity. "We haven't got any service gen on this particular make. Let's hope the fault is something fairly obvious."

He lifted the set from the rack and carried it over to his bench. As he did so, a small folded sheet of paper slipped unnoticed from one of the slots in the cabinet back grille and lay on the Workshop floor.

Smity placed the set on his bench, plugged in an aerial and connected it up to the mains. On the front of the receiver were four controls, these being a slow motion tuning control, two slide potentiometers for contrast and brightness, and a combined volume control and on-off switch. Smity found that the knob of the last control was free to rotate and so he experimentally pulled it out. There was a click and the sound channel of one of the local transmitters became immediately audible from the loudspeaker. He waited expectantly and, after a short while, the screen lit up. But it lit up with a completely blank white raster. There was no picture information in it whatsoever.

Smity adjusted the tuning control and was able to pick up the sound channels of the remaining two local stations. There was a hiss from the loudspeaker between transmissions, and each sound signal was reproduced clearly and at adequate volume level. The tuning adjustments caused no change whatsoever in the steady raster. Smity adjusted the contrast control, but this had no effect. He then adjusted the brightness control, to find that this merely increased and decreased the brightness of the raster.

### PIXIES

"Well," said Smity, turning off the set, "this one shouldn't be too difficult to sort out. It's almost certain that there's a fault between the video detector and the modulating electrode of the picture tube."

"You always sound so darned certain about these faults," exclaimed Dick in an exasperated tone. "What is more annoying is that you almost always turn out to be correct!"

"You don't have to be a magician to form a diagnosis with this set," stated Smity. "Just look at the situation. For starters, we're picking up the transmitted sound signals. This means that the video signal *must* be getting past the video detector because the 6MHz inter-carrier sound amplifier takes up its input after that detector. We're not getting any picture on the screen but we *are* getting this blank raster. So there must be e.h.t. getting to the tube final anode and the line and frame timebases are bound to be working. I admit that we can't tell whether they're working properly until we see a picture, but it's obvious that the first thing which has to be done is to find out what's stopping the picture getting to the tube."

He turned back to the set. "The only niggling thing," he went on, a note of irritation in his

voice, "is that finding the fault is liable to take quite a lot longer without service information than it would do if I had that information."

Dick's eyes travelled back to the music centre he had been repairing on his own bench. As he did so he spotted the folded paper on the floor. Switching off the music centre, he got down from his stool and picked up the paper. As he opened it out a grin appeared on his face and he walked over to Smity.

"How about this, then?" he chuckled.

Smity took the paper from his assistant and glanced over it.

"Well, I'm blown," he remarked, scratching his head, "this is the circuit for this TV! Where on earth did it come from?"

"It must have dropped out of the set as you carried it over. Don't forget that a lot of these imported receivers provide a small-size circuit diagram with the customer instructions. Perhaps the chap who sent in this set for repair thought he'd be doing us a favour if he included the circuit as well."

"He's certainly done that," said Smity, laying out the scaled-down diagram on his bench. "Let's see if this will help us to find the gremlins which are stopping the picture getting on to the screen."


Dick peered over the Serviceman's shoulder at the diminutive circuit diagram. A bemused expression slowly crept over his face.

"I don't know about gremlins," he said unhappily, "but from this distance there seem to be pixies in the circuit!"

"Pixies?"

"Yes, look," said Dick, pointing to the diagram. "There's a first pixie, a second pixie and a third pixie!"

"You steaming great nit," exploded Smity. The term isn't 'pixie', it's 'PIX IF'. There's a first 'PIX IF' transistor, a second 'PIX IF' transistor and a third 'PIX IF' transistor. They are the three transistors in the video

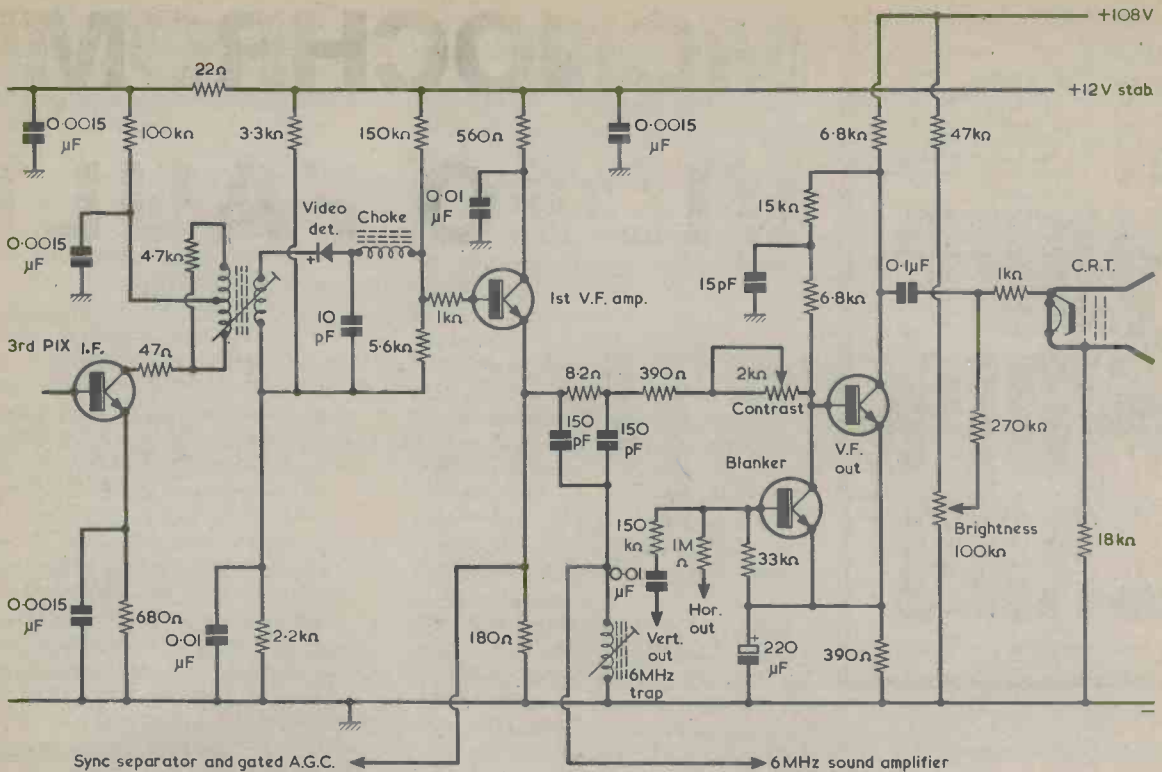

**Fig. 1.** The stages between the last video i.f. amplifier transistor and the cathode ray tube modulating electrode in the television receiver selected by Smyth. This circuit is employed in the Teleton monochrome receiver type TW-12BS Mk.II. The transistors are Japanese with 2SC type numbers

i.f. amplifier!"

Dick looked more closely at the diagram.

"Oh yes, I see now," he remarked brightly. "The last letter is 'F' and not 'E'. But what is this 'PIX' business, Smyth?"

"It's an old American abbreviation for 'pictures,'" explained Smyth. "Quite a few American TV service diagrams use the word 'PIX' instead of 'video'. Well now, let's have a look at the part of the circuit which most interests us. This starts at the video detector, which follows the third PIX IF transistor, and extends up to the tube modulating electrode. Which, in this set, is the tube cathode."

Smyth indicated the section of the overall circuit with his finger. (Fig. 1.)

"That third i.f. transistor," volunteered Dick, "seems to couple into an i.f. transformer which then feeds the video detector."

"That's right," agreed Smyth. "The anode of the detector diode couples into a 10pF parallel capacitor and the detected video signal then passes through an i.f. choke and a 1kΩ resistor to the base of the first video amplifier. This circuit uses the term 'VF' which, of

course, stands for 'video frequency'. The transistor is a standard emitter follower, which presents a reasonably high input impedance to the video detector circuit and which allows the detected video signal to be developed at a nice low impedance across the 180Ω emitter resistor. The signal across this resistor is then fed to the sync separator and gated a.g.c. stages, which are elsewhere in the receiver."

"The signal also goes to a 150pF capacitor," said Dick, "and an 8.2Ω resistor." (Fig.2.)


### TRAP CIRCUIT

"That's true," confirmed Smyth. "Those two components are part of the 6MHz trap, which also includes the second 150pF capacitor and the adjustable iron-dust core coil which connects between their junction and the negative rail. The two capacitors and the coil form a series tuned circuit. This offers a very low impedance at its resonant frequency, which in this case is 6MHz, and it prevents the 6MHz sound carrier from being passed on to the video output transistor. The 8.2Ω resistor will introduce a small amount of

resistance into the tuned circuit and make it a little less peaky."

"There's a line going from the top end of that coil," put in Dick, examining the circuit intently. "Where does that go to?"

"It goes to the 6 MHz intercarrier

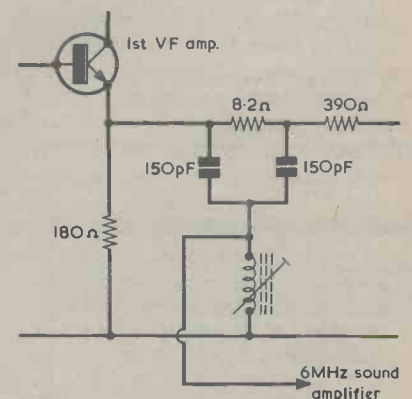

**Fig. 2.** The 8.2Ω resistor, the two 150pF capacitors and the variable inductance coil form a 6MHz trap. Not only does this prevent the sound carrier being passed on to the video output stage but it also picks out the 6MHz carrier for the intercarrier sound amplifier

## MORSE IMPROVEMENT

C90 Cassettes (A) 1-12 w.p.m. with simple exercises. Suitable for R.A.E. preparation. (B) 12-24 w.p.m. computer produced professional level operator material including international symbols.

Price each: complete with instruction and exercise booklets £4.75 including postage.

Morse Key and Buzzer Unit suitable for sending practice and DIY tape preparation.

Price £4.75 including postage  
Overseas Airmail £1.50 extra.

**MHEL ELECTRONICS (Dept. R)**  
12 Longshore Way, Milton,  
Portsmouth (UK), PO4 8LS

## THE MODERN BOOK CO.

Largest selection of English & American radio and technical books in the country

19-21 PRAED STREET  
LONDON W2 1NP  
Tel: 01-402 9176

## ELECTRONIC TUTOR KITS

Learn electronics the effective way by experiments. Each kit contains an illustrated handbook, which takes you step by step through the fundamentals of electronics, plus all the components of electronics, plus all the components needed. No soldering. Safe and instructive for even the young enthusiast. Kit 1, £5.85. Kit 2, £5.95. Kit 3, £6.15. SAE for leaflets on this and other RXG products.

**RXG ELECTRONICS LTD**  
15 Walnut Tree Crescent,  
Sawbridgeworth, Herts, CM21 9EB.

## PEATS for PARTS

### ELECTRONIC COMPONENTS

### RADIO & TELEVISION

For the convenience of Irish enthusiasts we supply:

Radio & Electronics  
Constructor Data Books  
Panel Signs  
Transfers

Also a postal service

**PEATS**  
the world of electronics  
25 Parnell Street, Dublin 1. Telephone 749972

sound amplifier," stated Smithy. "Although, as I've just said, the series tuned circuit which forms the 6MHz trap presents a low impedance at its resonant frequency, the 6MHz signal appears at its maximum amplitude across the coil on its own or across the capacitors on their own. These high amplitude signals are of opposite polarity and cancel each other out to give the overall trap low impedance, but at the same time the high amplitude signal across the coil on its own offers a high signal level at trap frequency for the intercarrier sound amplifier. Got it?"

"I've got it," confirmed Dick. "Let's get back to the video signal."

"Righty-ho," said Smithy. "Well, the video signal goes through a 390 Ω resistor and the contrast control and it then hits the base of the video output transistor. This is a very basic common emitter stage, and it has another 390 Ω resistor in

its emitter circuit which is bypassed by a 220 μF electrolytic. The collector couples to a 108 volt positive rail via a 6.8k Ω load resistor, and the amplified video signal is passed to the cathode of the picture tube by way of a 0.1 μF capacitor. You couldn't get things much simpler than that."

"Where does the 108 volt positive rail come from?"


"It's a rectified voltage taken from a tap on the line output transformer."

"Fair enough," commented Dick slowly. "As you say, it's a very simple circuit. Hang on a bit, though!"


"What's up?"

"There's another transistor connected up to the base and emitter of the video output transistor. Blimey, it's called a 'blanker'! What does that do?"

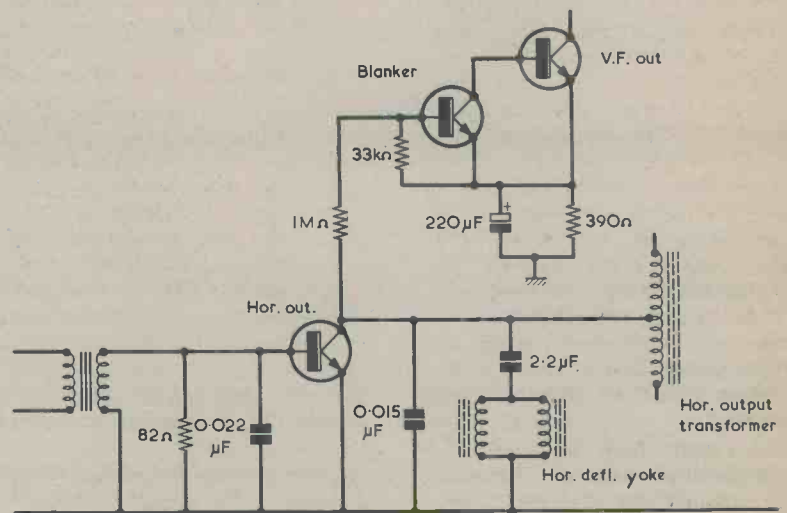"It provides line and frame flyback blanking," stated Smithy. "Incidentally, this set has got one of



(a)

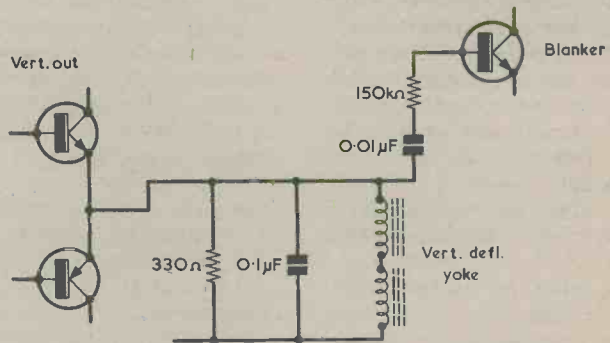

(b)

Fig. 3 (a). A very simple horizontal, or line, flyback blanking circuit. The horizontal output transistor collector goes highly positive during flyback and turns the blanker transistor hard on, thereby cutting off the video output transistor

(b). An equally simple blanking circuit is used for the frame, or vertical, flyback. The output point of the vertical timebase turns on the blanker transistor during the flyback period

the neatest blanking arrangements I've seen for many a long day. Let's have a look at the line blanking part first. In this circuit the word 'horizontal' is used to describe the line circuits, so let's have a quick look at the horizontal output stage. Here it is."

Smithy indicated the section of the television circuit diagram in which the horizontal output transistor appeared. (Fig.3(a).)

"Again," he went on, "everything is very nice and easy. The horizontal output transistor is turned hard on during the scan period of the line waveform, and it turns off during the flyback period. When it turns off, a high positive voltage appears on its collector and this voltage is passed, via a 1MΩ resistor, to the base of the blanker transistor. The transistor turns hard on, causing the voltage between the base and the emitter of the video output transistor to be only about 0.1 volt, whereupon the video output transistor is cut off. And that's all there is to it — a 1MΩ resistor from the horizontal output transistor and a single blanker transistor. Beautiful, isn't it?"

But Dick did not seem to share Smithy's admiration for the simplicity of the circuit.

"I suppose," said Dick slowly, "that the video output transistor will be a silicon type which normally needs about 0.6 volt between its base and emitter if it is to conduct."

"You suppose right," said Smithy. "All the transistors in the circuit are silicon types."


"What about the frame flyback blanking?"

"The word here is 'vertical'," stated Smithy. "And the circuit is, again, delightfully simple. If you trace through the diagram you'll see that the base of the blanker transistor couples via a 150kΩ resistor and a 0.01μF capacitor to one side of the vertical deflection coils, or 'yoke' as they are called in this diagram. The point to which the capacitor connects goes highly positive during the vertical flyback, so you get vertical flyback blanking this time. The circuit is a bit more complicated than the horizontal blanking circuit because, instead of one resistor, it uses one resistor and one capacitor!" (Fig.3(b).)


## CONTRAST CIRCUIT

"Stap me," said Dick, catching Smithy's enthusiasm. "This circuit really is cut to the bone. There's only one other thing that puzzles me now."

"Dear, oh dear," sighed Smithy.

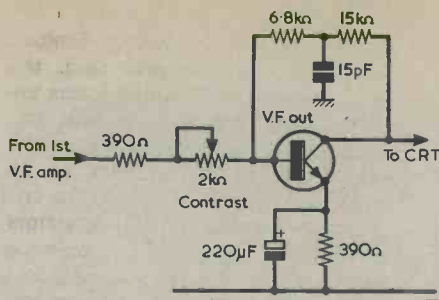


(a)

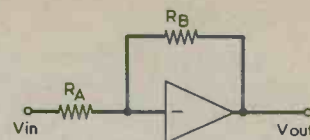


$$\frac{V_{out}}{V_{in}} = \frac{R_B}{R_A}$$

(b)

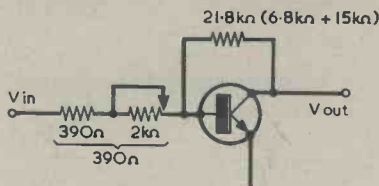

$$\frac{V_{out}}{V_{in}} = \frac{21.8k\Omega}{390\Omega} \approx 56$$

(c)

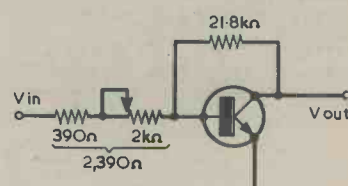

$$\frac{V_{out}}{V_{in}} = \frac{21.8k\Omega}{2,390\Omega} \approx 9$$

(d)

**Fig. 4 (a).** Basically, the contrast control varies the signal base current in the video output transistor by providing varying resistance between the signal input and the base. However, the feedback circuit from collector to base also affects the performance of the circuit

**(b)** Classic inverting amplifier circuit with series input resistance and resistive feedback

**(c).** Assuming infinite base input impedance the circuit of (a) can be reduced to the form shown here. The 21.8kΩ resistor is given by the 6.8kΩ and 15kΩ resistors in series

**(d).** Theoretical voltage gain when the contrast control inserts maximum resistance into circuit. In practice, the transistor input impedance will cause the gain figures to differ considerably from those shown here, but the effect illustrated will nevertheless have a significant influence on circuit performance

"When you start with your questions you never know when to stop."

"It's that contrast control circuit," said Dick. "All it seems to consist of is a 2kΩ pot in series with the input to the base of the video output transistor." (Fig.4(a).)

"That's virtually all that it is," replied Smithy, "although things are a little more sophisticated than that. At first sight, the contrast control merely varies the video signal voltage applied between the base and the emitter of the transistor. Speaking in very general terms, the input impedance at the transistor base will be of the order of several hundred ohms, with the result that, as the resistance inserted by the contrast control pot decreases, the signal voltage between the transistor base and emitter increases. But there's a secondary circuit which affects the issue to a small but significant extent."

"Secondary circuit? Where?"

"There's a negative feedback circuit from the video output transistor

collector back to the base and it's given by the 15kΩ and 6.8kΩ resistors in series. You'll see that there's a 15pF capacitor between the junction of these resistors and chassis. This capacitor reduces the level of negative feedback at the higher video frequencies so that a boost is given to these higher frequencies. High frequency boost arrangements are normal in video amplifiers, and they overcome high frequency losses due to stray capacitances to chassis. But there's another little matter here."

"What's that?"

"If you assume that the input impedance of the video output transistor is high you have a classic inverting amplifier circuit with feedback resistor and series input resistor. Like this."

Smithy took out a pen and scribbled out the circuit on his notepad. (Fig.4(b).)

"In that circuit," commented Dick, "the voltage gain is equal to the feedback resistance divided by the input series resistance, isn't it?"

"It is," confirmed Smithy. "Just for the fun of it, let's see what the gain of the video output transistor would be at different contrast settings under the assumption that there is a high input impedance at the transistor base. We can forget the 15pF capacitor for this exercise, as it will have little effect on the lower video frequencies, whereupon we can say that the feedback resistance is 21.8kΩ. When the contrast control inserts zero resistance the series input resistance will be 390Ω. So that the voltage gain will be 21.8kΩ divided by 390Ω."

Smithy scribbled the figures on his note-pad and carried out the calculation. (Fig.4(c).)

"That gives a voltage gain of about 56 times," he continued. "Now, when the contrast control inserts all its resistance into circuit the gain will be 21.8kΩ divided by 2,390Ω. Let's see what that is."

Smithy made a further calculation. (Fig.4(d).)

What's the result?"

"The voltage gain," replied Smithy, "is about 9 times. In practice the actual gain figures at the two contrast control settings will be considerably different from these calculated ones, because we have been ignoring the low input impedance of the transistor. Nevertheless, the effect of an inverting amplifier with feedback resistor is still present, and it will have a significant bearing on the actual performance of this video output stage and its contrast control."

Smithy turned and beamed silently at his assistant. Dick shifted uncertainly under Smithy's steady gaze.

"Well, that's great," he said uncomfortably.

"No more questions?"

"None that I can think of."

"Good, then we'll have a stab at fixing this set! Seeing that you're over here you might as well help me find the fault. With a bit of luck it shouldn't take too long. To start off, you could get the set back off so that we can get at the printed board."

## FAULT FINDING

Dick soon had the receiver ready for checking whilst Smithy studied the circuit diagram. The Serviceman then switched on the receiver, switched his testmeter to a high volts range and clipped its negative lead to the receiver chassis.

"Since we're getting a sound signal," he stated briskly, "I'm going

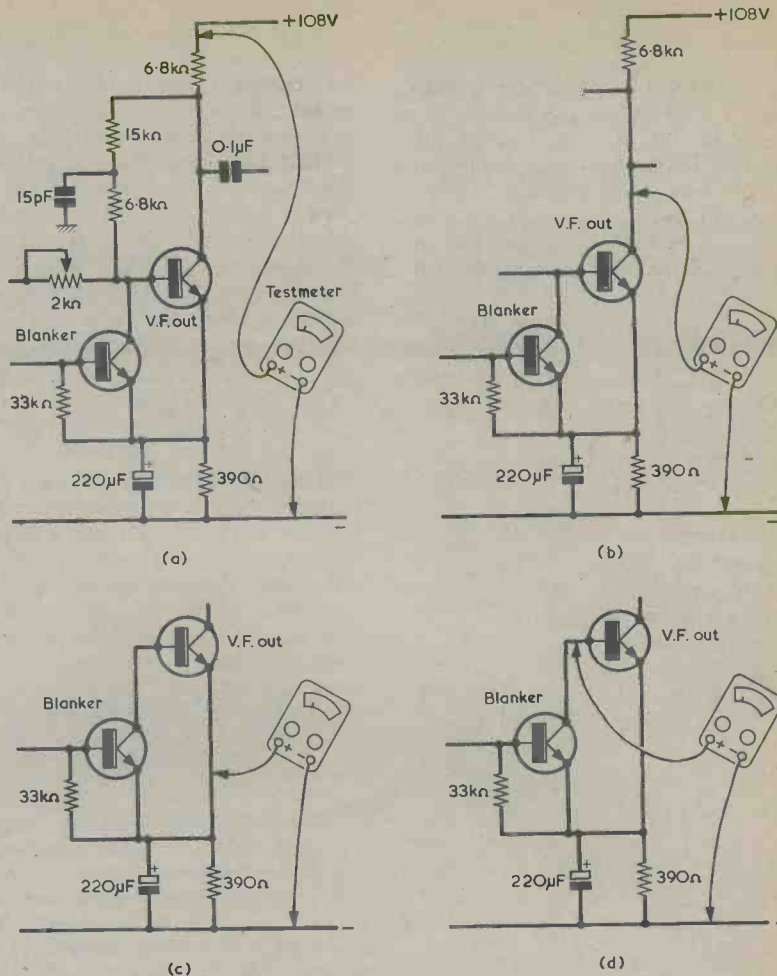


Fig. 5 (a) Smithy first confirmed that a correct supply voltage was available for the video output transistor (b). Next to be checked was the transistor collector voltage (c). He followed this by measuring the voltage at the emitter (d). The clincher! The voltage reading at the video output transistor base led him directly to the fault in the receiver

to make a guess that the first video transistor is all right, and I'll concentrate on the video output transistor. Voltage checks first. I'm going to put the positive test prod of the meter on the top end of the 6.8kΩ collector load resistor. You tell me what voltage I get."

Smithy examined the receiver printed board and then carefully placed the meter prod on the resistor lead-out. (Fig. 5(a).)

"You're getting a voltage," said Dick, "of about 110 volts."

"Good," said Smithy. "So there is a supply voltage for the output stage. Transistor collector next!"

Smithy moved his test prod. (Fig. 5(b).)

"The meter," called out Dick, frowning down at its scale, "says 85 volts."

"Humph," grunted Smithy. "That seems rather high. Let's try the transistor emitter."

He applied the prod to the video output transistor emitter. Dick selected a lower voltage range on the meter. (Fig. 5(c).)

"The meter is reading almost exactly 1.8 volts."

"And that," said Smithy, "seems to me to be a bit low. I'll try the base next."

He once more applied the test prod to the board. (Fig. 5(d).)

"1.8 volts again."

A gleam of elation appeared in Smithy's eyes.

"You're sure?"

"Of course I'm sure," responded Dick indignantly. "Blimey, I may not be so hot on theory but at least I *can* read a meter!"

To Dick's utter astonishment, Smithy burst into song.

"The rain in Spain," caroled Smithy exultantly, "falls mainly on the plain!"

Dick moved away uneasily.



"We've got it," sang Smithy happily, "I think we've got it!"

"Blow me, Smithy," asked the alarmed Dick, "have you fallen out of your tree, or something?"

"Don't worry," grinned Smithy. "I'm just exceptionally pleased at having located the fault in this set so very quickly."

"Well, I wish you'd give me a bit of warning before you do things like that. Stap me, you nearly gave me heart failure suddenly singing away like that! And what do you mean — we've got it?"

"We've got the fault," chortled Smithy happily. "The voltage reading on the transistor base should have been 0.6 volt higher than the reading on its emitter. But it wasn't. It was precisely the same. So, assuming that there are no shorts across the circuit print or anything silly like that, there are pretty well only two things that can be wrong. Either we've got a short-circuit between the base and emitter of the output transistor, or we've got a short-circuit across the emitter and collector of the blanker transistor. In either case the output transistor will not be able to amplify the video signal passed to its base. Also, it will be passing zero collector current."

"But the reading on its collector was lower than that of the 108 volt supply rail. There must have been some current in the collector load resistor."

"The collector voltage still wasn't as low as it would have been if the transistor had been passing collec-

tor current. With zero collector current, there is still a current path to the negative rail from the bottom of the 6.8k  $\Omega$  collector load resistor. The path is through the 15k  $\Omega$  resistor, the lower 6.8k  $\Omega$  resistor, the short-circuit which is causing the fault and the 390  $\Omega$  resistor at the bottom. It was that current which caused the bottom of the 6.8k  $\Omega$  load resistor to be below the potential of the 108 volt rail, and not any transistor collector current."

### FAULTY TRANSISTOR

It turned out that it was the blanker transistor which had become short-circuit. After a check through the Workshop copy of the invaluable *Tower's International Transistor Selector*, Smithy was soon able to find a suitable replacement for the Japanese transistor type employed in the receiver. When it had been connected into the receiver circuit, the set reproduced an excellent picture.

"Another one done," commented Smithy cheerfully as Dick replaced the back on the television receiver cabinet. "Nice 'one, too."

To Dick's relief, there were no further observations that day from the Serviceman concerning the proclivity of Spanish clouds to concentrate over level terrain. Indeed, Smithy's refrain about the rain did not entertain but caused strain and pain, went against the grain and did nothing to retain, sustain or maintain the normally sane and mundane atmosphere of their domain.

And you can say that again. ■

## GAREX

V.H.F. Receivers SR-9 for 2-metres F.M., fully tunable 144-146MHz, 2-speed slow-motion dial, also 11 xtal controlled channels. Compact, sensitive, ideal for fixed or mobile listening. Built-in L.S., 12v D.C. operation £47.15 inc. VAT. Crystals, if required: £2.60 each. All popular 2m. channels in stock. Marine band version (156 162MHz) £47.15 (xtals £2.90). Mains psu for above £11.95. Pocket VHF Receiver 12 channel xtal controlled complete with nicad and charger. 4MHz bandwidth in range 140-175MHz £57.95. Amateur and Marine xtals in stock, prices as SR-9.

Amplifier module new, fully assembled 6W IC unit, 12v D.C. Low impedance (4-8  $\Omega$ ) input and output for extn. speaker amplification, with circuit £2.75.

Neons min wire end 70p/10; £4.50/100 Slide switches min DPDT 20p ea; 5+ : 16p Resistor Kits E12 series, 22  $\Omega$  to 1M  $\Omega$  - 57 values, 5% carbon film,  $\frac{1}{2}$ W or  $\frac{1}{4}$ W Starter pack, 5 each, value (285) £3.10

Mixed pack, 5 each  $\frac{1}{2}$ W +  $\frac{1}{4}$ W (570) £5.55 Standard pack, 10 each (570) £5.55 Giant pack, 25 each (1,425) £13.60

BNC Cable mtg socket 50  $\Omega$  25p; 5+ : 20p; PL259 UHF Plug & Reducer 75p; 5+ : 67p; SO239 UHF Socket panel mtd. 60p; 5+ : 50p; Nicad rechargeables physically equiv. to zinc-carbon types: AAA (U16) £1.80; AA(U7) £1.30; C(U11) £3.35; PP3 £5.55. Any 5+ : less 10%. Any 10+ less 2.)

We stock V.H.F. & U.H.F. mobile aerials, s.a.e. details.

Access — Barclaycard

PRICES INCLUDE UK POST, PACKING & VAT  
Mail order only

Sole Address:

GAREX ELECTRONICS  
7 NORVIC ROAD, MARSWORTH,  
TRING, HERTS HP23 4LS  
Cheddington (STD 0296) 668684


## COMPUTER BASIC COURSE

Now launched by Cambridge Learning Enterprises is a new self-teaching course under the general title: "Computer Programming in BASIC". Written by Ian Williamson, Rodney Dale and Time Eiloart, the course is presented in four A4 books having the titles "Basic Basics", "Introducing Basic", "Applying Basic" and "Advanced Basic".

The course text is programmed so that the reader is able to test his knowledge and understanding as he proceeds, and a very important feature is that it can be mastered without access to a computer. Dealt with are BASIC and Advanced BASIC up to elementary file handling, and the course includes the five key aspects of programming, these being problem definition, flow, charts, program writing, debugging and the presentation of clear documentation.

There are 60 straightforward lessons, with in-built questions which check progress as the subject unfolds. A light background is provided by inclusion of cartoons by Mike Berry. The course is available from Cambridge Learning Enterprises, Rivermill Lodge, St. Ives, Huntingdon, Cambs., PE17 4EP, at a cost of £7.50, with discounts for bulk orders.

## MORSE MADE EASY

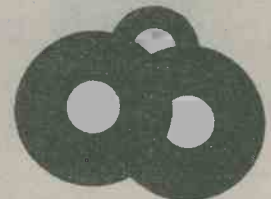

### BY THE G3HSC RHYTHM METHOD!

These courses which have been sold for over 25 years, have been proved many times to be the fastest method of learning Morse. You start right away by learning the sounds of the various letters, numbers, etc., as you will in fact use them. Not a series of dots and dashes which later you will have to transkate into letters and words.

Using scientifically prepared 3 speed records you automatically learn to recognise the code, RHYTHM without translating. You can't help it. It's as easy as learning a tune 18 WPM in 4 weeks guaranteed.

The Complete Course consists of three records as well as instruction books. For Complete Course send £5.50 (overseas mail £3.50 extra).

### THE G3HSC MORSE CENTRE


S. Bennett, (Box 8), 45 Green Lane,  
Purley, Surrey.

Name .....

Address .....

# TV
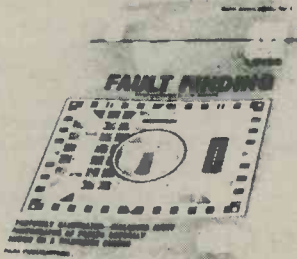
## FAULT FINDING MANUAL for 405/625 LINES



**£1.20**

P. & P. 27p

## REVISED & ENLARGED

EDITED BY J. R. DAVIES

132 pages

Over 100 illustrations, including 60 photographs of a television screen after the appropriate faults have been deliberately introduced.

Comprehensive Fault Finding Guide cross-referenced to methods of fault rectification described at greater length in the text.

# UNDERSTANDING TELEVISION



by

J. R. DAVIES

Over 500 pages  
300 diagrams

**£3.95**

P. & P. £1.00

UNDERSTANDING TELEVISION deals with:

- Principles of 405 line reception
- Principles of 625 line reception
- Nature of the television signal
- Receiver tuner units
- A.F. and video amplifiers
- Deflector coil assemblies
- Automatic gain and contrast control
- Receiver aerials
- The cathode ray tube
- Receiver i.f. amplifiers
- Vertical and horizontal timebases
- Synchronising
- Power supply circuits
- Colour television
- **COLOUR TELEVISION – 80 page comprehensive introduction to the subject**

The reader is required to have only a basic knowledge of elementary radio principles. The treatment is non-mathematical throughout, and there is no necessity for any previous experience in television whatsoever. At the same time UNDERSTANDING TELEVISION is of equal value to the established engineer because of the very extensive range it covers and the factual information it provides.

To Data Publications Ltd., 57 Maida Vale, London, W9 1SN

Please supply the 4th revised edition of TV FAULT FINDING, Data Book No. 5.....

Please supply UNDERSTANDING TELEVISION, Data Book No. 17.....

I enclose cheque/crossed postal order for.....(Tick which book is required)

NAME.....

ADDRESS.....

(BLOCK LETTERS PLEASE)

# SMALL ADVERTISEMENTS

Rate: 12p per word. Minimum charge £2.00

Box No. 30p extra

Advertisements must be prepaid and all copy must be received by the 4th of the month for insertion in the following month's issue. The Publishers cannot be held liable in any way for printing errors or omissions, nor can they accept responsibility for the *bona fides* of Advertisers. Where advertisements offer any equipment of a transmitting nature, readers are reminded that a licence is normally required. (Replies to Box Numbers should be addressed to: Box No. —, *Radio and Electronics Constructor*, 57 Maida Vale, London, W9 1SN.

**METAL DETECTORS** £6.90. 100 Mixed components £2.50. Lists 15p. Sole Electronics (REC), 37 Stanley Street, Ormskirk, Lancs., L39 2DH.

**FOR SALE:** Heathkit SB 401 Tx, 80-10 metres SSB/CW, 200 watts p.e.p. £100. Shure 444 microphone £15. BC 221 Frequency Meter with power supply and book £25. Sinclair PDM 35 Digital Multimeter in case with leads £30. CR100 with modifications £20. 500V Megger with leather case £5. All are o.n.o. Ed. Hartley, "Byways", Chapel Road, Mutford, Beccles, Suffolk, NR34 7UU.

**NEW QUALITY AMPLIFIERS!** From £12-£45. 60W stereo output. AX60: Vinyl case, fascia, all sockets, controls, switching, L.E.D. display. I.C. Preamp. F.E.T. Drivers. Stabilised power supply. Screened transformer, 240V a.c. £35. inc. Klifco Electronics, 1 Regent Road, Ilkley, West Yorkshire. S.A.E. for leaflet.

**FOR SALE:** "Challenge of the Stars" by Patrick Moore and David A. Hardy £2.00. "Destroyers" by Antony Preston £4.00. Box No. G376.

**FREE!** 12" x 6" Veroboard, with first 50 orders for our compilation pack of components. Hundreds of common and exotic use devices plus pcb's, thermistors, etc. This is really an offer not to be missed. Send P.O. or cheque for £8.20 immediately to: R. E. Norman, Portbuild Limited, 57 Amberwood Rise, New Malden, Surrey. Or send s.a.e. for list.

**ANY REQUESTED SERVICE SHEET** £1 (Plus large s.a.e.). Full repair data any named TV £5.50 (with circuits, layouts, £7). Large s.a.e. brings newsletter, bargains, etc. Ausrec, 76 Church Street, Larkhall, Lanarkshire, ML9 1HE.

**COLLECTORS' ITEMS.** Nearly 50 copies of Radio Society of Great Britain's *Bulletins* covering period 1945 to 1949. In reasonable condition. Offers to: Box No. G377.

**INTERESTED IN RTTY?** You should find the "RTTY Journal" of interest. Published in California, U.S.A., it gives a wide outlook on the current RTTY scene; RTTY-DX; DXCC Honour Roll; VHF RTTY news; and up to date technical articles are included. Specimen copies 35p from: The Subscription Manager, RTTY Journal, 21 Romany Road, Oulton Broad, Lowestoft, Suffolk, NR32 3PJ.

**OSCILLOSCOPE FOR £12.** Easy build converter plugs into TV aerial socket and converts to large screen oscilloscope. Components cost approx £12. Circuit and plans £3. Kerr, 27 Coles Road, Milton, Cambridge, CB4 4BL.

**200 MIXED COMPONENTS** £3.50. Money refunded if not satisfied. Send S.A.E. for list of our other bargain packs. Servio Radio, Dept. RE1, 156-158 Merton Road, Wimbledon, London SW19 1EG.

(Continued on page 509)



# Wilmslow Audio

*THE firm for speakers!*

**SEND 30p FOR THE WORLDS BEST CATALOGUE OF SPEAKERS, DRIVE UNITS KITS, CROSSOVERS ETC. AND DISCOUNT PRICE LIST**


AUDAX • AUDIOMASTER • BAKER • BOWERS & WILKINS • CASTLE • CELESTION • CHARTWELL • COLES • DALESFORD • DECCA • EMI • EAGLE • ELAC • FANE • GAUSS • GOODMAN'S • I.M.F. • ISOPON • JR • JORDAN WATTS • KEF • LEAK • LOWTHER • MCKENZIE • MONITOR AUDIO • PEERLESS • RADFORD • RAM • RICHARD ALLAN • SEAS • STAG • TANNAY • VIDEOTONE • WHARFEDALE • YAMAHA • SHACKMAN • TANGENT

## WILMSLOW AUDIO DEPT REC

SWAN WORKS, BANK SQUARE, WILMSLOW CHESHIRE SK9 1HF

Discount HiFi Etc. at 5 Swan Street

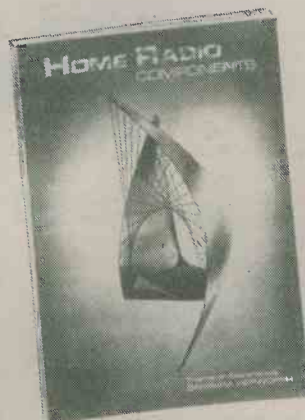Tel: 0625-529599 for Speakers, 0625-526213 for HiFi



**SOME THINGS YOU CAN DO WITHOUT ...**

**but the HOME RADIO CATALOGUE is Top Priority for every constructor**

- About 2,500 items clearly listed and indexed.
- Profusely illustrated throughout.
- 128 A-4 size pages, bound in full-colour cover.
- Bargain list of unrepeatable offers included free.
- Catalogue contains details of simple Credit Scheme.

HOME RADIO (Components) LTD.  
Dept. RC., P.O. Box 92, 215 London Road, Mitcham, Surrey  
Phone: 01-648 8422

Please write your Name and Address in block capitals

NAME .....

ADDRESS .....



HOME RADIO (Components) LTD., Dept. RC  
P.O. Box 92, 215 London Road, Mitcham, Surrey  
Regd. No. 912966, London

**POST THIS COUPON**  
with cheque or P.O. for £1.30

**UNDERSTANDING MICROPROCESSORS** Texas Ins. £4.25

For the newcomer to Microprocessors. An in-depth look at the magic of the solid-state chips that are affecting our lives. Written in everyday language. Ideal for self-paced individualised learning.

- ELECTRONIC PROJECTS IN THE HOME**  
by O. Bishop Price £2.50
- ELECTRONIC PROJECTS IN AUDIO**  
by R. A. Penfold Price £2.50
- OP-AMPS THEIR PRINCIPLES & APPL.**  
by J. B. Dance Price £2.50
- PRINTED CIRCUIT ASSEMBLY**  
by M. J. Hughes Price £2.10
- ELECTRONIC SECURITY DEVICES**  
by R. A. Penfold Price £1.65
- UNDERSTANDING DIGITAL ELECTRONICS**  
by Texas Inst. Price £4.00
- UNDERSTANDING MICRO-PROCESSORS**  
by Motorola Price £4.30
- THE FIRST BK OF MICROCOMPUTERS**  
by R. Moody Price £3.35
- HOW TO BUILD YOUR OWN SOLID STATE OSCILLOSCOPE**  
by F. G. Rayer Price £1.70
- THE OSCILLOSCOPE IN USE**  
by I. R. Sinclair Price £2.85

- THEORY & PRACTICE OF MODEL RADIO CONTROL**  
by P. Newell Price £4.50
- REPAIRING POCKET TRANSISTOR RADIOS**  
by I. R. Sinclair Price £2.55
- MAKING & REPAIRING TRANSISTOR RADIOS**  
by W. Oliver Price £2.30
- WORLD RADIO TV HANDBOOK**  
by J. M. Frost Price £9.25
- PROJECTS IN RADIO & ELECTRONICS**  
by I. R. Sinclair Price £2.50
- ELECTRONIC PROJECTS IN THE HOME**  
by O. Bishop Price £2.50
- SIMPLE CIRCUIT BUILDING**  
by P. C. Graham Price £2.20
- 110 SEMICONDUCTOR PROJECTS FOR THE HOME CONSTRUCTOR**  
by R. M. Marston Price £3.20
- HAM RADIO**  
by K. Ulyett Price £5.00

- UNDERSTANDING SOLID-STATE ELECTRONICS**  
by Texas Inst. Price £1.80
- A SIMPLE GUIDE TO HOME COMPUTERS**  
by S. Ditlea Price £4.00
- HOW TO BUILD A COMPUTER-CONTROLLED ROBOT**  
by T. Loofbourrow Price £5.30
- THE CATHODE-RAY OSCILLOSCOPE & ITS USE**  
by G. N. Patchett Price £4.00
- HOW TO GET THE BEST OUT OF YOUR TAPE RECORDER**  
by P. J. Guy Price £1.90
- A GUIDE TO AMATEUR RADIO**  
by P. Hawker Price £1.70
- RADIO CONSTRUCTION FOR AMATEURS**  
by R. H. Warring Price £2.80
- MAKING TRANSISTOR RADIOS A BEGINNER'S GUIDE**  
by R. H. Warring Price £2.90.


We have the Finest Selection of English and American Radio Books in the Country ☆ PRICES INCLUDE POSTAGE ☆

**19-21 PRAED STREET (Dept RC) LONDON W2 1NP**

Telephone: 01-402 9176

# SELF BINDER

for "Radio & Electronics Constructor"

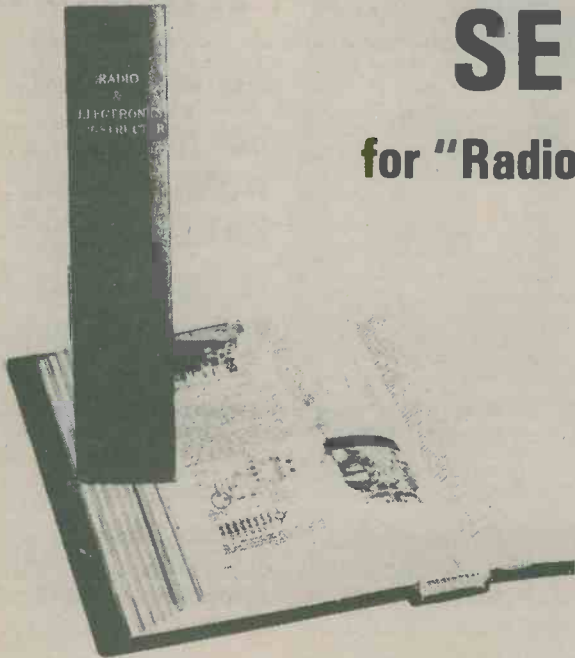

The "CORDEX" Patent Self-Binding Case will keep your issues in mint condition. Copies can be inserted or removed with the greatest of ease. Rich maroon finish, gold lettering on spine.

Specially constructed Binding Cords are made from Super Linen of great strength, very hard twisted and twice doubled. They are attached to strong RUSTLESS Springs under tension, and the method adopted ensures PERMANENT RESILIENCE of the Cords. Any slack that may develop is immediately compensated for and the Cords will always remain taut and strong. It is impossible to overstretch the springs, as a safety check device is fitted to each.

**PRICE £2.25**

including V.A.T. P.&P. 50p

Available only from:—

**Data Publications Ltd.**

**57 Maida Vale, London W9 1SN**

## SMALL ADVERTISEMENTS

(Continued from page 507)

**FOR SALE:** Arac 102 receiver 28-30MHz and 144-146MHz. AM-FM-CW-SSB. 12V d.c. Excellent condition. £85.00 o.n.o. G2UK. 21 Romany Road, Oulton Broad, Lowestoft, Suffolk.

**CATHODE RAY TUBES.** Surplus types, 09J, CV2750. 946A, CV1596, CV1391 £5 each. VCR138 £6 each. Large data display Brimar, V4167/LG/L4 £15. Tektronix T5021-P2 £15. CD1016 dual beam 5MHz scopes £90. AP1506 power supplies 200-500V, 6.3V at 10A, excellent condition £30. Solartron CD711S scope, requires e.h.t. xFr w/manual £20. 12AP7A Radar tube £10. Transformers 2 x 6.3V at 20A £8 each. Airmec crystal osc.213 £5. Loads of other surplus equipment! Box No. G387.

**THE RADIO AMATEUR INVALID & BEDFAST CLUB** is a well established Society providing facilities for the physically handicapped to enjoy the hobby of Amateur Radio. Please become a supporter of this worthy cause. Details from the Hon. Secretary, Mrs. F. E. Woolley, 9 Rannoch Court, Adelaide Road, Surbiton, Surrey, KT6 4TE.

**INGENIOUS GAMES** to distract and tantalise — and to construct. Three original designs by me in kit form, pocket sized with a top quality finish to grace your coffee table and deceive your friends. From £4.25 to £5.25. Send s.a.e. for details of all three to: H. S. Houston, 12 Harlech Avenue, Leeds 11, Yorkshire.

**FOR SALE:** Wide angle 9.5mm cine equipment: camera, projector, screen, etc. Also several other 9.5mm cine cameras. S.A.E. for details. Box No. G388.

**CUSTOM ENGRAVED FASCIAS** for your projects in brushed aluminium, bronze, brass and a wide range of colours. Send your requirements. We do the rest. Male, 159 Victoria Road, Swindon, Wilts., SN1 3DA.

**INTERESTED IN OSCAR?** Then join AMSAT-UK. Newsletters, OSCAR NEWS Journal, prediction charts, etc. Details of membership from: Ron Broadbent, G3AAJ, 94 Herongate Road, Wanstead Park, London, E12 5EQ.

**ENTIRE SHACK CLEARANCE:** Resistors, condensers, transistors, printed panels, variacs, transformers, valves etc. For details please telephone Surfleet (077-585) 517. Evenings only.


**FOR SALE:** Sinclair MK14 mini-microprocessor with power supply. £45.00 o.n.o. Box G389.

**POSTAL ADVERTISING?** This is the Holborn Service. Mailing lists, addressing, enclosing, wrapping, facsimile letters, automatic typing, copy service, campaign planning, design and artwork, printing and stationery. Please ask for price list. — The Holborn Direct Mail Company. Capacity House, 2-6 Rothsay Street, Tower Bridge Road, London, S.E.1. Telephone: 01-407 6444.

**WANTED:** Service manual, circuit of Hallicrafters SX28 receiver. Buy, borrow or copy. All expenses refunded. Maddocks, 70 Kings Road, Southsea, Hants. Telephone: Portsmouth 29129.

**JOIN THE INTERNATIONAL S.W. LEAGUE.** Free services to members including Q.S.L. Bureau, Amateur and Broadcast Translation, Technical and Identification Dept. — both Broadcast and Fixed Stations, DX Certificates, contests and activities for the SWL and transmitting members. Monthly magazine, *Monitor*, containing articles of general interest to Broadcast and Amateur SWLs, Transmitter Section and League affairs, etc. League supplies such as badges, headed notepaper and envelopes. QSL cards, etc., are available at reasonable cost. Send for League particulars. Membership including monthly magazines, etc., £6.00 per annum. (U.K. and British Commonwealth), overseas \$12.00. Secretary ISWL, 1 Grove Road, Lydney, Glos., GL15 5JE.

(Continued on page 511)

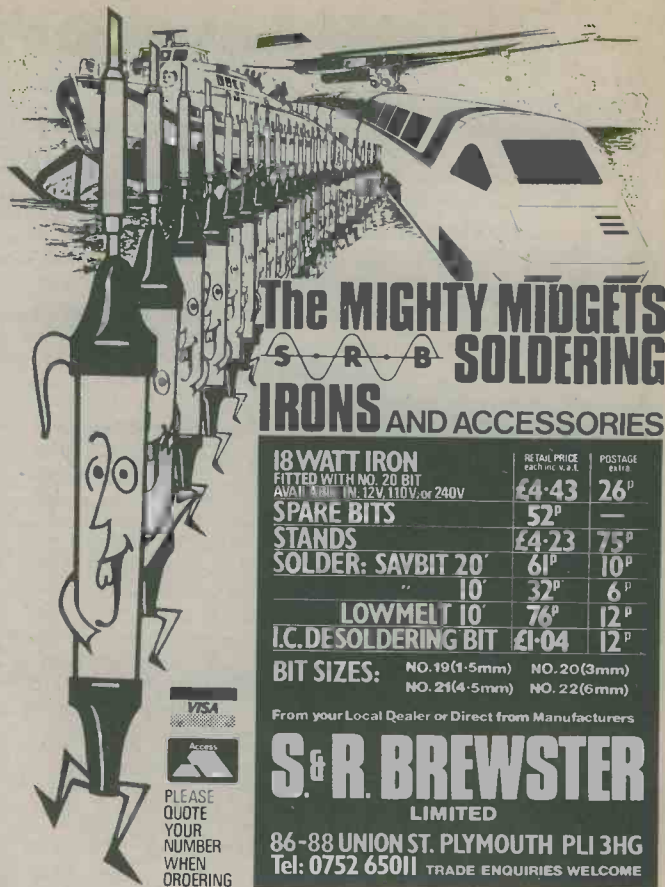

**The MIGHTY MIDGETS SOLDERING IRONS AND ACCESSORIES**

	RETAIL PRICE each inc. V.A.T.	POSTAGE extra
<b>18 WATT IRON</b> FITTED WITH NO. 20 BIT AVAILABLE IN: 12V, 110V, or 240V	<b>£4.43</b>	<b>26<sup>p</sup></b>
<b>SPARE BITS</b>	<b>52<sup>p</sup></b>	—
<b>STANDS</b>	<b>£4.23</b>	<b>75<sup>p</sup></b>
<b>SOLDER: SAYBIT 20'</b>	<b>61<sup>p</sup></b>	<b>10<sup>p</sup></b>
" 10'	<b>32<sup>p</sup></b>	<b>6<sup>p</sup></b>
" LOWMELT 10'	<b>76<sup>p</sup></b>	<b>12<sup>p</sup></b>
<b>I.C. DESOLDERING BIT</b>	<b>£1.04</b>	<b>12<sup>p</sup></b>

**BIT SIZES:** NO. 19(1.5mm) NO. 20(3mm)  
NO. 21(4.5mm) NO. 22(6mm)

From your Local Dealer or Direct from Manufacturers

**S & R. BREWSTER LIMITED**

86-88 UNION ST. PLYMOUTH PL1 3HG  
Tel: 0752 65011 TRADE ENQUIRIES WELCOME

VISA  
Access  
PLEASE QUOTE YOUR NUMBER WHEN ORDERING

## A CAREER IN RADIO

Start training **today** and make sure you are qualified to take advantage of the many opportunities open to the trained person. ICS can further your technical knowledge and provide the specialist training so essential to success.

ICS, the world's most experienced home study college, has helped thousands of ambitious men to move up into higher paid jobs — they can do the same for **you**.

Fill in the coupon below and find out how!

There is a wide range of courses to choose from, including:

**CITY & GUILDS CERTIFICATES**  
Telecommunications Technicians'  
Radio TV Electronics Technicians'  
Electrical Installations Technicians'  
Electrical Installation Work  
Radio Amateurs'  
MPT Radio Communications Cert  
**EXAMINATION STUDENTS —  
GUARANTEED COACHING  
UNTIL SUCCESSFUL**

**TECHNICAL TRAINING**  
ICS offer a wide choice of non-exam courses designed to equip you for a better job in your particular branch of electronics, including:  
Electronic Engineering & Maintenance  
Computer Engineering/Programming  
Radio, TV & Audio Engineering & Servicing  
Electrical Engineering Installations & Contracting

### COLOUR TV SERVICING

Technicians trained in TV Servicing are in constant demand. Learn all the techniques you need to service Colour and Mono TV sets through new home study course approved by leading manufacturer.

POST THIS COUPON OR TELEPHONE FOR FREE PROSPECTUS

I am interested in .....

Name ..... Age .....

Address .....

Occupation .....

**ICS** Accredited  
by CACC  
Member of  
ABCC

To  
International Correspondence Schools  
Dept T278, Intertext House, LONDON  
SW8 4UJ or phone 01-822 9911 (anytime)

# SMALL ADVERTISEMENTS

Use this form for your small advertisement

To: The Advertisement Manager, Data Publications Ltd., 57 Maida Vale, London W9 1SN

Please insert the following advertisement in the .....issue of RADIO & ELECTRONICS CONSTRUCTOR

→			

15 words at 12p  
= £1.80

ALL WORDING  
IN  
BLOCK LETTERS  
PLEASE


I enclose remittance .....being payment at 12p a word. MINIMUM £2.00.  
Box Number, if required, 30p extra.

NAME .....  
ADDRESS .....

Copy to be received four weeks prior to publication.  
Published on the 3rd of every month, forward dated.
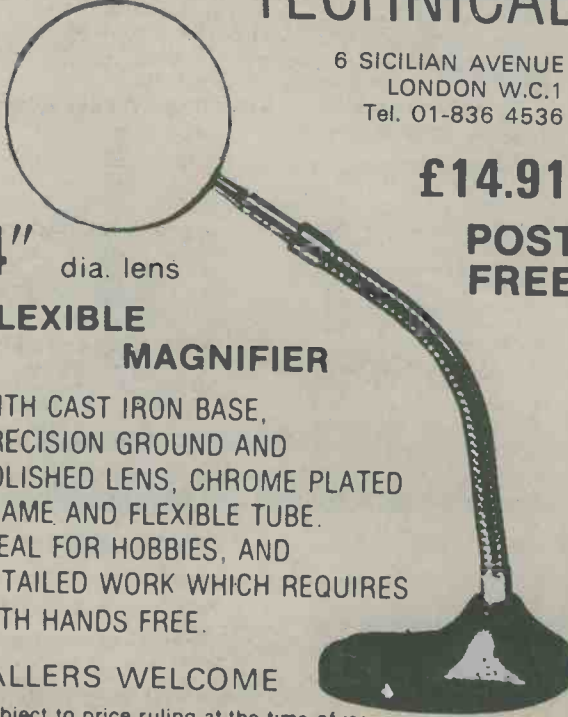
## REVOR OPTICAL & TECHNICAL

6 SICILIAN AVENUE  
LONDON W.C.1  
Tel. 01-836 4536



**4" dia. lens**

**£14.91**

**POST FREE**

**FLEXIBLE  
MAGNIFIER**

WITH CAST IRON BASE,  
PRECISION GROUND AND  
POLISHED LENS, CHROME PLATED  
FRAME AND FLEXIBLE TUBE.  
IDEAL FOR HOBBIES, AND  
DETAILED WORK WHICH REQUIRES  
BOTH HANDS FREE.

CALLERS WELCOME  
(Subject to price ruling at the time of issue)

## LEARN ELECTRONICS WITHOUT SOLDER

Build electronic circuits without solder on a Roden S-Dec. This has built-in contacts and holes into which you plug your components. Suitable for all ages. Can be used time after time. Ideal gift for students or experimenters. Full instructions and 2 circuit diagrams with each S-Dec.



**£3.85**  
plus 40p  
p.&p. each

Send cheque or P.O. to:-  
Roden Products, Dep R & EC  
High March, Daventry, Northants, NN11 4QE.

## BUILD YOUR OWN P.A., GROUP & DISCO SPEAKERS by R. F. C. Stephens

Save money with this practical guide. Plans for 17 different designs. Line source, I.B., Horn and Reflex types, for 8"-18" drive units. £3.95 post free (\$8 overseas).

## THE INFRA-BASS LOUDSPEAKER by G. Holliman

(full constructional details for versions using 15", 12" and 10" drive units.) £2.95 post free (\$6 overseas).

## THE DALESFORD SPEAKER BOOK by R. F. C. Stephens

This book is a must for the keen home constructor. Latest technology DIY designs. Plans for I.B., and Reflex designs for 10-100 watts. Also unusual centre-bass system. £2.20 post free (\$5 overseas).

VAN KAREN PUBLISHING  
5 Swan Street, Wilmslow, Cheshire

## SMALL ADVERTISEMENTS

(Continued from page 509)

**WANTED: FAX** equipment, manuals, service sheets, etc. G2UK, 21 Romany Road, Oulton Broad, Lowestoft, Suffolk. NR32 3PJ.

**BOOKS TO CLEAR.** "Solid State Design for the Radio Amateur", ARRL. £3.50. "The Radio Amateur's Handbook" by Frederick Collins, £3.00. "Computers for the Amateur Constructor" by R. H. Warring, 50p. "Amateur Radio Antennas" by Harry Hooton, £1.00. "Ham Antenna Construction Projects" by J. A. Stanley, 75p. "Ham, RTTY" by W2NSD, 50p. "The New RTTY Handbook" by Byron Kretzman, £1.00. "RTTY from A to Z" by Durward J. Tucker, £1.00. "All about Cubical Quad Antennas" by W6SAI, £1.00. "Guide to Astronomy" by James Muirden, 40p. "Astronomy" by David Evans, £1.25. "Atomic Radiation & Life", Pelican Books, 40p. Box No. G390.

**CONSTRUCT METAL DETECTORS:** 1. £120 pulse discriminator (£12 construction cost). 2. £60 model (£6 con/cost). 3. £30 BFO (£3 con/cost). For all three together, written guaranteed d.i.y. plans, send £2. (Dept. RC), J. Lucas, 2 College Road, Grays, Essex. (Established 1973).

**FOR SALE:** 50 2W zeners £1.00. Switch cleaner £1.00. 1N4007 diodes 7p. Reed relay inserts 25p. Miniature relays 25p. L.E.D.'s 10p. Fuseholders 10p. Electronic shooting game £5.00. Electronic blackjack game £6.00. Radio control car £7.50. Voice controlled ladybird toy £15.00. J. Fulton, Derrynaseer, Dromore, Co. Tyrone, N. Ireland.

## PERSONAL

**JANE SCOTT FOR GENUINE FRIENDS.** Introductions to opposite sex with sincerity and thoughtfulness. Details free. Stamp to: Jane Scott, 3/Con North St. Quadrant, Brighton, Sussex, BN1 3GJ.

**BROADLANDS RESIDENTIAL CLUB** for elderly people. Are you recently retired and looking for a home? We have a delightful top floor room overlooking Oulton Broad, facing south. Write to: The Warden, Broadlands Residential Club, Borrow Road, Oulton Broad, Lowestoft, Suffolk.

**IF YOU HAVE ENJOYED A HOLIDAY** on the Norfolk Broads, why not help to preserve these beautiful waterways. Join the Broads Society and play your part in determining Broadlands future. Further details from: — The Hon. Membership Secretary, The Broads Society, "Icknield," Hilly Plantation, Thorpe St. Andrew, Norwich, NR8 8SS.

**SPONSORS** required for exciting scientific project. Norwich Astronomical Society are building a 30" telescope to be housed in a 20" dome of novel design. All labour being given by volunteers. Already supported by Industry and Commerce in Norfolk. Recreational. Educational. You can be involved. Write to: NAS Secretary, 195 White Woman Lane, Old Catton, Norwich, Norfolk.

## NEW ELECTRONIC BOOKS

Build Your Own Transistor Radio.....	£2.25
TV Trouble Diagnosis Made Easy.....	£2.75
Electronic Musical Projects.....	£2.30
Electronic Gadgets for You.....	£2.25
Transistor Circuits & Servicing.....	£2.25
555 Timer & Its Applications.....	£2.40
Electronic Hobby Circuits.....	£2.25
Simple Crystal Diode Circuits.....	£2.25
Fascinating I.C. Projects.....	£2.30
Transistor Receivers Self-Constructor.....	£3.10
Build Your Own Digital Clock.....	£2.75
Cassette Recorders; How They Work; Care & Repair.....	£5.95
Build a 2-Band Silicon Transistor Radio.....	£2.30
Pictorial Guide to Colour TV Circuit Problems.....	£5.95

Books postpaid from:

**FINBARR'S LTD.,**

15 Boscombe Road, Folkestone.

MAIL ORDER ONLY

## T&J ELECTRONIC COMPONENTS

*Quality Components —  
Express Service*

**COMPONENT PROBLEMS?** Do you have problems in obtaining a certain component or part? If so let us know, we may be able to help. New lines are continually arriving and are not always therefore included in our latest lists.

**Cables:** Mains cable 3 core rated at 3A 15p, medium weight single core microphone 10p, twin figure of "8" lighting flex 6p. All prices per metre.

**Electrolytic capacitors:** All rated at 63V; 0.47, 1.0, 2.2, 4.7, 10 9p, 22, 33, 47 11p, 100 20p, 220 24p, 470uF 40p.

**Aerials:** Eight section telescopic, length extended 1200mm 145p. Indoor F.M. aerial, constructed from 300 ohm ribbon to form a folded dipole. With six foot down lead 65p.

**Aluminium boxes:** Complete with lid; 3" x 2" x 1" 50p, 4" x 2 1/4" x 1 1/2" 71p, 4" x 4" x 1 1/2" 71p. Many others in stock.

**Fuse holders:** Panel mounting for 1 1/2" fuses 24p, for 20mm 17p, In line car 10p. Fuses; 250mA, 500mA, 1, 2, 5A 1 1/2" 6p, 20mm 5p.

**P.C.B. KIT:** Comprehensive kit includes the following; etching dish, ferric chloride, Dalo etch resist pen, drill, 100 sq ins of copper clad board, set of p.c.b. transfers, instructions. £5.25 + 65p p&p. All parts available separately.

**Insulating tape:** 3/4" wide x approx 15 feet long 12p per roll. Colours; Black, Brown, Blue, White, Yellow, Red and Green.

**Insulating kits** (semiconductors): T03, T066, T0220 5p each.

All previously advertised items are still available. We also stock hardware, semiconductors, plugs and sockets. In fact too much to list here. Please send 30p in stamps for our full lists.

Mail order only. All prices include VAT. Please add 30p for postage. Same day service on all orders. SAE with enquires please.

98 Burrow Road, Chigwell, Essex IG7 4HB.

## MARCO TRADING

To obtain a free copy of our 35 page list simply send a 20p postage stamp or a large SAE. This advertisement shows only a part of our range. (Our new list includes Tants, Electrolytics, Disc ceramics, etc.)

### 400m/w ZENER DIODES Low Price

3V6 3V9 4V3 4V7 5V1 5V6 6V2 6V8 7V5 8V2 9V1 10V 11V 12V 13V 13V5 15V 16V 18V 20V 22V 24V 27V 30V 33V.

Price: 8p each 100 any mix £6.00

### RESISTORS

1/4W @ 40°C. 1/4W @ 70°C 5% tol., 2.2 3p.  
to 2MΩ. E24 2p each.  
Resistor Pack — 10 each value  
(730 resistors) £6.00.

### 1 watt

### ZENER DIODES

3V3 to 200V Full range  
Price 15p each 100 any mix £12.60

8 DIL 10p	22 DIL 23p
14 DIL 13p	24 DIL 24p
16 DIL 15p	28 DIL 28p
18 DIL 18p	40 DIL 40p
20 DIL 22p	

### VEROBOARD (Copper Clad)

Size Inch	0.1"	0.15
2.5 x 1	20p	N/A
2.5 x 5	55p	56p
2.5 x 3.75	46p	50p

Vero Wiring Pen Including spool of wire) £2.84

### CONNECTING CABLE

Black Blue Green Gray Orange Pink, Red White Violet Yellow, Brown.  
Singles 5p per metre  
7/0.2mm 5p per metre  
16/0.2mm 8p per metre

### SPECIAL OFFERS

Power Amplifier Sanyo STK015 Brand New Full Spec etc. 10 Watts into B12. Free spec sheet with every order. Our price: £2.50 each.  
Radio Spares Edge Meter Type MR100 (259-562). All new and boxed. RS price over £4.00 each. Our price: £2.50 each.

Send your orders to:

**DEPT. DP12, MARCO TRADING, THE OLD SCHOOL, EDSTASTON, Nr. WEM, SHROPSHIRE SY4 5RJ**

**Tel: Whixall (094872) 464/465**

Please add 25p postage and packing to each order and add 15% VAT to your total order. Export add NO VAT but add postage Air/Sea at cost

### SUB. MIN. TOGGLE SWITCHES

SPST —	70p
SPDT —	78p
DPDT —	82p
DPDT —	90p
(C-OFF)	

### BRIDGE RECTIFIERS

50V	32p	400V	60p
400V	43p	60Amp 50V	70p
800V	58p	200V	78p
20Amp 50V	36p	400V	85p
100V	42p		

### 0.1W SUB. MINIATURE PRE-SETS

100Ω to 1MΩ Vertical or Horizontal  
Price: 6p each. 100 any mix £4.60

### LINEAR IC's

CA3018	.. 87p	AY11313	£6.60
CA3035	£2.30	AY51224A	£2.50
CA3046	.. 70p	AY51230	£4.40
CA3048	£2.18	AY58100	£6.60
AY10212	£6.60		

Full range of Panel Meters available  
£6.25 each

# RADIO & ELECTRONICS CONSTRUCTOR

## Single Copies

Price **55p** each, p&p **18p**

Issue(s) required .....

## Annual Subscription

Price **£8.50** inland, **£9.50** overseas (including Eire)

post free, commence with ..... issue

## Bound Volumes:

Vol. 27. August	1973 to July	1974	Price <b>£3.00</b> , post & pkg <b>£1.30</b>
Vol. 28. August	1974 to July	1975	Price <b>£3.20</b> , post & pkg <b>£1.30</b>
Vol. 29. August	1975 to July	1976	Price <b>£3.50</b> , post & pkg <b>£1.30</b>
Vol. 30. August	1976 to July	1977	Price <b>£3.70</b> , post & pkg <b>£1.30</b>
Vol. 31. August	1977 to August	1978	Price <b>£5.20</b> , post & pkg <b>£1.30</b>
Vol. 32. September	1978 to August	1979	Price <b>£5.50</b> , post & pkg <b>£1.30</b>

## CORDEX SELF-BINDERS

With title, 'RADIO & ELECTRONICS CONSTRUCTOR' on spine, maroon only

Price **£2.25**, post & pkg **50p**

With no title on spine, maroon

Price **£2.25**, post & pkg **50p**

With no title on spine, green

Price **£2.25**, post & pkg **50p**

Prices include V.A.T.

## DATA BOOK SERIES

DB5 TV Fault Finding, 132 pages Price **£1.20**, P. & P. **27p**

DB6 Radio Amateur Operator's Handbook,  
New edition in course of preparation

DB17 Understanding Television, 504 pages Price **£3.95**, P. & P. **£1.00**

DB19 Simple Short Wave Receivers  
140 pages Price **80p**, P. & P. **27p**

## STRIP-FIX PLASTIC PANEL SIGNS

Set 3: Wording — White — 6 sheets Price **£1.50**, P. & P. **11p**

Set 4: Wording — Black — 6 sheets Price **£1.50**, P. & P. **11p**

Set 5: Dials — 6 sheets Price **£1.50**, P. & P. **11p**

Prices include V.A.T.

I enclose Postal Order/Cheque for ..... in payment for .....

NAME .....

ADDRESS .....

(BLOCK LETTERS PLEASE)

*Postal Orders should be crossed and made payable to Data Publications Ltd.*

*Overseas customers please pay by International Money Order.*

*All publications are obtainable through your local bookseller*

**Data Publications Ltd., 57 Maida Vale, London W9 1SN**

**PLEASE MENTION THIS MAGAZINE WHEN WRITING TO ADVERTISERS**