

HEAR PILOT-TO-TOWER TALK WHILE IN FLIGHT

14278

# Popular Electronics

WORLD'S LARGEST-SELLING ELECTRONICS MAGAZINE

MAY 1977/\$1.25

## FOR HI-FI BUFFS

- HOW TO MATCH STEREO COMPONENTS BY \$\$\$
- HIRSCH-HOUCK LABS EXAMINES:  
SENNHEISER'S WIRELESS STEREO HEADPHONES  
TEAC'S PORTABLE STEREO CASSETTE DECK

## FOR COMMUNICATION HOBBYISTS


- MORSE CODE ALPHANUMERIC READOUT ON TV
- TESTING KENWOOD'S DIGITAL HAM TRANSCEIVER

## HANDS-ON REPORT FOR EXPERIMENTERS

- THE NEW "NO CAMERA" PC BOARD KITS
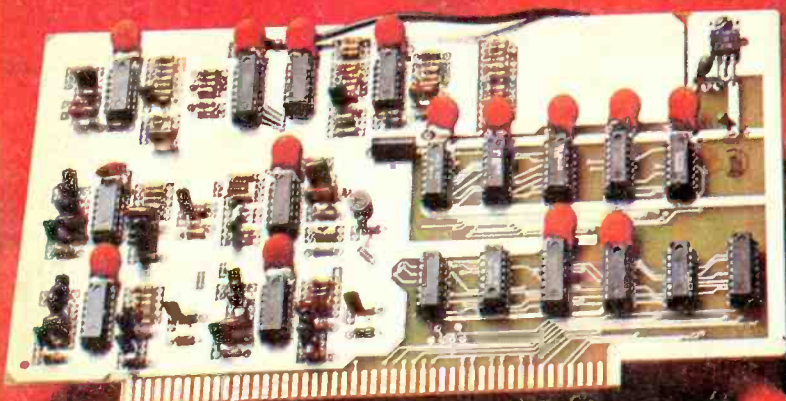
# VOICE COMMUNICATIONS WITH COMPUTERS!

...speech recognition device substitutes for keyboard



MAJOR

PROJECT

BREAKTHROUGH

303196 DRK 6450M090 141D NOV79  
L DARKNELL JR 05  
6450 WARTLEWOOD DR  
SAN JOSE CA 95129



Popular Electronics

The 40-channel Cobra 29XLR. From the sleek brushed chrome face to the matte black housing, it's a beauty. But its beauty is more than skin deep. Because inside, this CB has the guts to pack a powerful punch.

The illuminated 3-in-1 meter tells you exactly how much power you're pushing out. And pulling in. It also measures the system's efficiency with an SWR check. In short, this Cobra's meter lets you keep an eye on your ears.

The Digital Channel Selector shows you the channel you're on in large LED numerals that can be read clearly in any light. There's also switchable noise blanking to reject short-pulse noise other systems can't block. The built-in power of DynaMike Plus. Automatic noise limiting

and Delta Tuning for clearer reception.

And the added protection of Cobra's nationwide network of Authorized Service Centers with factory-trained technicians to help you with installation, service and advice.

The Cobra 29XLR. It has 40 channels. And it has what it takes to improve communications by punching through loud and clear on every one of them. That's the beauty of it.



**Punches through loud and clear.**

Cobra Communications Products  
**DYNASCAN CORPORATION**

6460 W. Cortland St., Chicago, Illinois 60635

Write for color brochure

EXPORTERS: Empire • Plainview, N.Y. • CANADA: Atlas Electronics • Toronto

CIRCLE NO. 15 ON FREE INFORMATION CARD

# PUNCH AND BEAUTY





Whether you're a  
seasoned practitioner  
or a striving beginner...

Here are the  
fundamentals.

Software Design  
for Microprocessors.  
378 pages  
only \$12.95.\*

Basic Electricity and DC  
Circuits. 1,016 pages  
only \$19.95.\*

Both of these new books get down to basics—present clear, readable discussions. Loaded with examples, references, graphs, tables. Also, data sheets, bibliography and appendices. You're *encouraged* to learn—and apply your knowledge to practical situations.

**Software Design for Microprocessors.** Helps you understand the hardware/software relationship of microprocessors. A convenient, stand-alone text, suitable for both first-time users of microprocessors and the technically advanced.

Beginning chapters deal with basic terms, basic machine architecture, instructions and addressing. Successive chapters treat the process of generating software, defining required support and documentation, and designing a simple machine to program a problem. Sample problems at the conclusion allow you to apply your new knowledge.

**Basic Electricity and DC Circuits.**

A self-teaching course designed to enable you to predict and control the behavior of most basic and complex DC circuits. Each lesson begins with a listing of objectives—what new skills and knowledge you should have upon successful completion. The text within each chapter is arranged so that you progress at your own pace, with answers to commonly asked questions presented at key points.

Examples show you how to use the principles of basic DC electricity as

they are taught. You'll analyze basic DC circuit schematics and find yourself experimenting with your own designs. Plus, a quiz included at the end of each lesson allows you to gauge your progress.

If you're a hobbyist, student, or simply interested in broadening your knowledge of electronics, these books are *must* additions to your library. Use the coupon below to order your copies today.



<b>Texas Instruments Learning Center.</b> Mail checks and money orders to: P.O. Box 3640, M/S 84, Dallas, Texas 75285. Postage paid. Add state and local taxes where applicable.		PE-2	
Mail company purchase orders to: P.O. Box 5012, M/S 84, Dallas, Texas 75222. Postage and taxes will be added to your invoice.		I enclose <input type="checkbox"/> check <input type="checkbox"/> money order for \$ _____	
Please send me _____ copies of (LCB 1891) Software Design for Microprocessors at \$12.95* per copy. _____ copies of Basic Electricity and DC Circuits at \$19.95* per copy.		Name _____	
		Address _____	
		City _____ State _____ Zip _____	
*All states except: AK, DE, HI, MT, NH, OR.			

\*Suggested retail price; subject to change without notice.

© 1976 Texas Instruments Incorporated

**TEXAS INSTRUMENTS**  
INCORPORATED

91011

# THE CATS TO CATCH.

"Roar Power" puts these new 40-channel CB's from Pearce-Simpson out in front. The Lion 40™ and Tiger 40™. Built with all the power and prestige you'll ever need in the CB jungle. As well as some advanced Pearce-Simpson features that command real attention. Like HetroLock™, for zeroing in on the right frequency. Receiv-O-Slide™ tuning for the best reception and superior adjustment of signals (even from "off-freq." sets). And the Lion's bold new LED digital read-out.

Both sets are backed by Pearce-Simpson's over quarter-century of experience in personal two-way communications. And both are available right now. So stop by your Pearce-Simpson dealer today. He'll be glad to help you make the big cats roar.

*For further information, write Pearce-Simpson, 4701 N.W. 77th Ave., Miami, FL 33166. In Canada, Scotcomm Radio, Inc., 4643 Levesque Blvd., Chomedey, Laval, Quebec.*



**PEARCE-SIMPSON**  
DIVISION OF GLADDING CORPORATION  
THE CB RADIO • MARINE RADIO • ANTENNA PEOPLE.

CIRCLE NO. 47 ON FREE INFORMATION CARD

POPULAR ELECTRONICS

# Popular Electronics®

WORLD'S LARGEST-SELLING ELECTRONICS MAGAZINE

## FEATURE ARTICLES

**NEW "NO-CAMERA" PRINTED CIRCUIT BOARD METHODS** ..... A. A. Mangieri 55  
*How to make etching and drilling guides directly from printed matter.*

**HOW TO MATCH HI-FI COMPONENTS** ..... 66  
*Price tags serve as a good guide to apportioning your money.*

**MAY-AUGUST ENGLISH-LANGUAGE SW BROADCASTS** ..... Richard E. Wood 101

## CONSTRUCTION ARTICLES

**INTRODUCING SPEECHLAB—THE FIRST HOBBYIST VOCAL INTERFACE FOR A COMPUTER** .....  
 Horace Enea and John Reykjalin 43  
*Now your computer can respond to vocal commands.*

**BUILD A LEGAL IN-FLIGHT AIRLINE RECEIVER** ..... Cass R. Lewart 61  
*Hear pilot-to-control conversations with low-cost Varactor-diode crystal set.*

**MORSE CODE AUTOMATIC READOUT ON A TV SCREEN** ..... George R. Steber 64  
*Interface the Morse-A-Letter to a "TV Typewriter."*

## COLUMNS

**STEREO SCENE** ..... Ralph Hodges 18  
*The Decontamination Squad.*

**SOLID STATE** ..... Lou Garner 76  
*VMOS—MOSFET's With Muscle.*

**EXPERIMENTER'S CORNER** ..... Forrest M. Mims 86  
*Using LED's as Light Detectors.*

**HOBBY SCENE** ..... John J. McVeigh 88

**COMPUTER BITS** ..... Hal Chamberlin 96  
*Debugging Aids.*

**CB SCENE** ..... Ray Newhall 98  
*Uncle Charlie Is Snowed-In.*

**DX LISTENING** ..... Glenn Hauser 100

## JULIAN HIRSCH AUDIO REPORTS

**HOW HEADPHONES ARE TESTED** ..... 26

**SENNHEISER MODEL HDI 434 INFRARED HEADPHONES** ..... 32

**TEAC MODEL PC-10 CASSETTE RECORDER** ..... 36

## ELECTRONIC PRODUCT TEST REPORTS

**KENWOOD MODEL TS-820 TRANSCEIVER** ..... 90

**MURA MODEL PRX-100 "PRM" CB MICROPHONE** ..... 93

**B&K PRECISION MODEL 1471B OSCILLOSCOPE** ..... 94

## DEPARTMENTS

**EDITORIAL** ..... Art Salsberg 4  
*The CB Crossover Point.*

**LETTERS** ..... 6

**NEW PRODUCTS** ..... 12

**NEW LITERATURE** ..... 17

**NEWS HIGHLIGHTS** ..... 40

POPULAR ELECTRONICS, May 1977, Volume 11, Number 5, Published monthly at One Park Avenue, New York, NY 10016. One year subscription rate for U.S., \$9.98; U.S. Possessions and Canada, \$12.98; all other countries, \$14.98 (cash orders only, payable in U.S. currency). Second Class postage paid at New York, NY and at additional mailing offices. Authorized as second class mail by the Post Office Department, Ottawa, Canada, and for payment of postage in cash.

POPULAR ELECTRONICS including ELECTRONICS WORLD, Trade Mark Registered. Indexed in the Reader's Guide to Periodical Literature.

COPYRIGHT © 1977 BY ZIFF-DAVIS PUBLISHING COMPANY. ALL RIGHTS RESERVED.

Ziff-Davis also publishes Boating, Car and Driver, Cycle, Flying, Modern Bride, Popular Photography, Skiing and Stereo Review.

Material in this publication may not be reproduced in any form without permission. Requests for permission should be directed to Jerry Schneider, Rights and Permissions, Ziff-Davis Publishing Co., One Park Ave., New York, NY 10016.

Editorial correspondence: POPULAR ELECTRONICS, 1 Park Ave., New York, NY 10016. Editorial contributions must be accompanied by return postage and will be handled with reasonable care; however, publisher assumes no responsibility for return or safety of manuscripts, art work, or models.

Forms 3579 and all subscription correspondence: POPULAR ELECTRONICS, Circulation Dept., P.O. Box 2774, Boulder, CO 80302. Please allow at least eight weeks for change of address. Include your old address, enclosing, if possible, an address label from a recent issue.

**EDGAR W. HOPPER**  
*Publisher*

**ARTHUR P. SALSBERG**  
*Editorial Director*

**LESLIE SOLOMON**  
*Technical Editor*

**JOHN R. RIGGS**  
*Managing Editor*

**IVAN BERGER**  
*Senior Editor*

**ALEXANDER W. BURAWA**  
*Features Editor*

**EDWARD I. BUXBAUM**  
*Art Director*

**JOHN McVEIGH**  
*Associate Editor*

**ANDRE DUZANT**  
*Technical Illustrator*

**PATRICIA GIRRIER-BROWN**  
*Production Editor*

*Contributing Editors*  
HAL CHAMBERLIN, LOU GARNER  
GLENN HAUSER, JULIAN HIRSCH  
RALPH HODGES, FORREST MIMS  
RAY NEWHALL, WILFRED SCHERER

**JOSEPH E. HALLORAN**  
*Advertising Director*

**JOHN J. CORTON**  
*Advertising Sales*

**LINDA BLUM**  
*Advertising Service Manager*

**PEGI MCNEANEY**  
*Executive Assistant*

**STANLEY NEUFELD**  
*Associate Publisher*

ZIFF-DAVIS PUBLISHING COMPANY  
Popular Electronics  
Editorial and Executive Offices  
One Park Avenue New York, New York 10016  
212-725-3500  
Hershel B. Sarbin, President  
Furman Hebb, Executive Vice President  
John R. Emery, Sr. Vice President, Finance and Treasurer  
Phillip T. Heffernan, Sr. Vice President  
Edward D. Muhlfield, Sr. Vice President, Sports Division  
Philip Sine, Sr. Vice President  
Frank Pomerantz, Vice President, Creative Services  
Arthur W. Butzow, Vice President, Production  
Lawrence Sporn, Vice President, Circulation  
George Morrissey, Vice President  
Sydney H. Rogers, Vice President  
Sidney Holtz, Vice President  
Albert S. Traina, Vice President  
Philip Korsant, Vice President  
Paul H. Chook, Vice President  
Edgar W. Hopper, Vice President  
Charles B. Seton, Secretary  
  
William Ziff, Chairman  
W. Bradford Briggs, Vice Chairman

Midwestern Office  
The Pattis Group, 4761 West Touhy Ave.,  
Lincolnwood, Illinois 60644, 312 679-1100  
Thomas Hockney, Michael Neril, Gerald E. Wolfe  
Western Office  
9025 Wilshire Boulevard, Beverly Hills, CA 90211  
213 273-8050; BRadshaw 2-1161  
Western Advertising Manager: Bud Dean

Japan: James Yagi  
Oji Palace Aoyama: 6-25, Minami Aoyama  
6 Chome, Minato-Ku, Tokyo 407-1930/6821,  
582-2851



Member Audit Bureau  
of Circulations



The publisher has no knowledge of any proprietary rights which will be violated by the making or using of any items disclosed in this issue.



## Editorial

### THE CB CROSSOVER POINT

I felt the pulse of the CB industry this past February at the second annual Personal Communications 2-Way Radio Show, where some 380 manufacturers exhibited their newest CB transceivers, antennas and accessories. It was strong, though beating a little slower than in the recent past. Clearly, the crossover sales point from 23-channel CB transceivers to 40-channel units had not yet been reached in February, although indications are that it will have happened by the time you read this.

A transition period is, of course, a natural state of events, especially when the old and the new are running side by side, with the former sold at spectacular discounts. What we were watching at the PC-77 trade show was "tomorrow," while "today" was having its last hurrah in the marketplace. Making my way through the exhibit hall, I became aware of a few 40-channel misconceptions shared by some dealers and distributors—and perhaps passed on to their customers. Two of them were: 40-channel CB transceivers only produce two watts of r-f output power and they exhibit inferior modulation. Both are fallacious, of course!

Now, really, there is simply no reason why, given good design, expanding a band of frequencies a paltry 150 kHz should influence r-f power output or modulation capability. Sure, a warmed-over 23-channel design that exhibited poor automatic modulation limiting to begin with won't be able to hack it, though passing FCC type-acceptance tests. (These are actually being performed now. The "good old days" of passing tests by submitting paper results to the FCC are over, thankfully). However, we've tested enough new 40-channel rigs to verify that they can provide as much r-f carrier output power and modulation throughout the new, expanded band as the 23's. Moreover, the new rigs are decidedly less prone to overmodulate owing to improved modulation limiters. This means fewer cases of voice distortion and, more important, less splatter to interfere with adjacent channel communication.

Interestingly, the foregoing points were emphasized by a major CB radio manufacturer at a Show press meeting. Furthermore, a spokesman analyzed the signal strength required at the receiver for a standard 10-dB signal-to-noise ratio in a typical urban environment to illuminate another advantage for 40-channel rigs. Assuming a typical receiver sensitivity of 0.5 microvolts for 10-dB (S + N)/N, about 14.5 microvolts of *additional* signal strength is required for the current 23 channels to make the standard due to interference from on-channel users; 15 microvolts more at the receiver is needed to combat adjacent-channel interference, for a total of 30 microvolts. In contrast, the upper new channels require only a total of 1.5 microvolts to receive an intelligible communication, the manufacturer estimated.

As a consequence of the above, the communication range with the upper new channels is estimated to be four times that of the lower 23 channels (30 microvolts/1.5 microvolts = 20 times = 26 dB). Typical area coverage on the new channels (actually, 80% of the upper new ones, since some are still within splatter distance of the original 23) would, therefore, be enlarged about 16 times.

For CB'ers trying to get through during rush-hour traffic, the upper 17's on a 40-channel AM rig might be considered to simulate the effectiveness of single sideband on one of the less popular lower 23 channels. So, though 23-channel transceivers are tremendous bargains (and hard to resist), right now, 40 channels is the way to go to fully appreciate the utility of the citizens band.

*Art Salsberg*

**One Call.  
Your Mallory distributor's  
got them all.**


Take the search and wait out of your electronic parts finding.

Go straight to your Mallory distributor, by phone or in person.

Get to know the convenience and economy of simplified single-source buying. To

deliver exactly what you want in parts, quality, and quantity. Immediately from stock on hand, or in most cases within 24 hours from the factory.

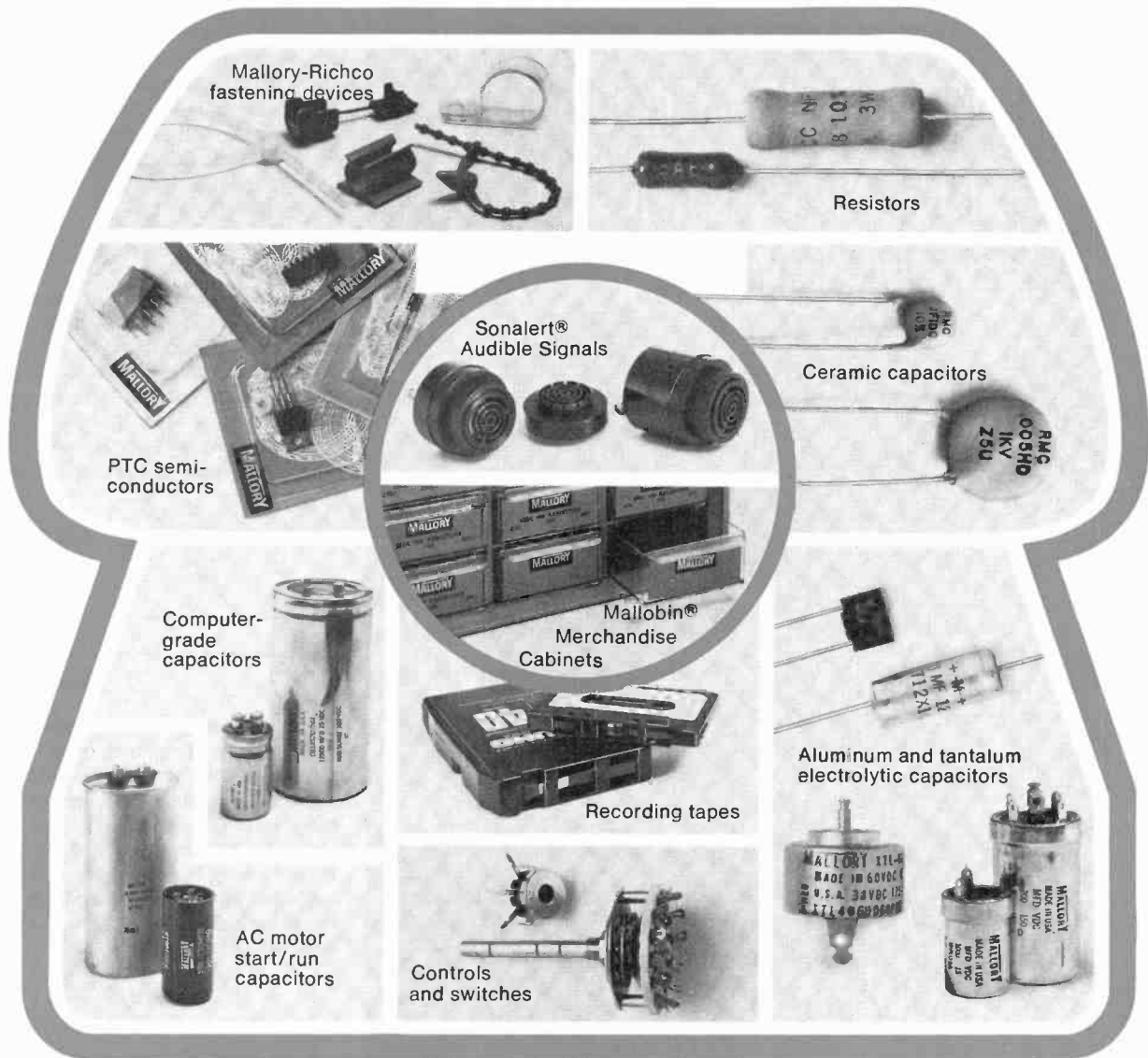Your Mallory distributor goes all out for his Number 1 VIP . . . you. Get in touch with him soon. Mallory Distributor Products Company, a division of P. R. Mallory & Co. Inc., Box 1284, Indianapolis, Indiana 46206. (317) 856-3731.



# MALLORY

Capacitors • Controls • Fastening Devices • Resistors • Security Products • Semiconductors • Solderless Terminals • Switches



# Letters

## ABOUT PC ARTWORK

I recently tried, for the first time, GC Electronics' new Lift-It direct-art pc kit and have a few questions I hope you will answer. First, if I

attempted to use the Lift-It master to directly expose positive-resist-treated pc blanks, would it work? I fear that the black ink will not have the density required to block out light. Secondly, if the Lift-It artwork would work, what are chances for POPULAR ELECTRONICS to print the pc etching and drilling guides as negative artwork so that one-timers like me could use commonly available negative resist without having to reverse the exposure mask? —Warren D. White, Berkeley, CA.

We have used the Lift-It artwork directly to expose photosensitized pc blanks with a high degree of success. During our experience, we have not had one instance where the ink was not dense enough to exclude light. (For detailed information about the Lift-It kit and

another direct-art kit from Datak, see the feature article in this issue.)

As for printing our pc etching and drilling guides as negative artwork, we have anticipated you. As you can see, beginning in this issue, our pc artwork is now printed in the negative format. We have taken this step because a recent survey revealed that almost all spray-on photoresist available to the hobbyist is the negative variety (although GC Electronics does sell a positive photo-resist). By printing our pc artwork in negative format, readers can save at least one step in the board fabrication process.


## CONSTANT VERSUS VARIABLE

I believe that the explanation of dual-slope analog-to-digital conversion on page 37 of the "Multimeters For Electronics" story (February 1977) is incorrect. The  $T_1$  to  $T_2$  time period is a constant—a specific number of oscillator pulses—not a variable as stated in the text. —David E. Purdy, Philadelphia, PA

You're correct. It's the  $T_2$  to  $T_3$  time that's the variable.
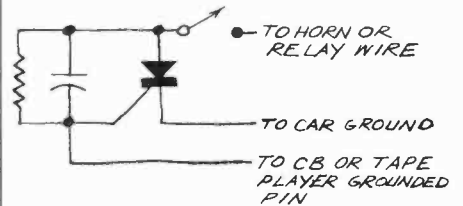
## SIMPLE TO SIMPLER

The SCR trigger circuit for possible use in protecting CB and other electronic equipment in automobiles shown in the January 1977 CB Scene can be further simplified when applied to CB transceivers. This is particularly true in the case where the rig has a three-prong plug for the 12-volt line and one of the prongs is not used. In my circuit (see below),



note the elimination of the relay. Wire #3 goes to the unused prong of the plug, while the unused contact in the mating female connector goes to ground. Removal of the power cable or physical removal of the CB rig or tape recorder from the vehicle will trigger the vehicle's horn. From actual experience, I can attest that the circuit has paid for itself in value of equipment protected. —Robert B. McKinley, Jr., Tinton Falls, NJ.

## AMPLIFIER DIAGRAMS SWITCHED

In my article "Classes of Audio Amplifiers" (March 1977), the diagrams for Figs. 5 and 6 have been interchanged. The captions are correct. —Len Feldman.

## SILENCER PC BOARDS AVAILABLE

Although no source was given for pc boards in my article "Build a Silencer" (March 1977, p 57), they are available from me at the following address: Ronald Miles, Rte. 1, Box 190, Rustburg, VA 24588. Price is \$4.60 per board. Virginia residents, add 4% sales tax.

# About damping, bi-amping and the Crown DC-300A

Because of inertia, speaker transducers over-react to amplifier signals. This can be minimized by speaker design, but it can't be eliminated entirely. In the process, the transducers feed spurious signals back into the signal processing units.

A good amplifier is designed to control excessive transducer excursions by reducing — and absorbing — the unwanted signals generated by such excursions. It's part of a process audio engineers call damping. The Crown DC-300A power amplifier, in addition to its other well-known specifications, has a damping factor of 700, which means it should easily control speaker excursions. (A rating of 400 is considered good.)

But in a standard hi-fi stereo system, the DC-300A can't do all the damping it was designed for. The sound is a little muddier than it should be.

Why? Because the speaker crossovers — with their own impedance — get in the way. The amp is not directly

hooked up to the transducers.

Solution? Move the crossovers back between amp and pre-amp. Add another DC-300A and bi-amp the speakers.


The DC-300A now damps excessive transducer excursions efficiently. Which can mean crisper, cleaner sound.

Each transducer now has 155 watts of power available to drive it, and is limited only by its own characteristics. Which can mean more sound pressure.

There can also be less distortion, since harmonics of low-frequency distortion cannot feed to high-frequency transducers through the crossover.

Are you interested in how to use all the power and performance of a Crown DC-300A amplifier? Write. We'll send you information about the Crown VFX-2A, a two-channel variable-frequency crossover that makes bi-amping easy. Plus reprints of some articles that may help you decide if bi-amping is for you.

# Crown VFX-2A

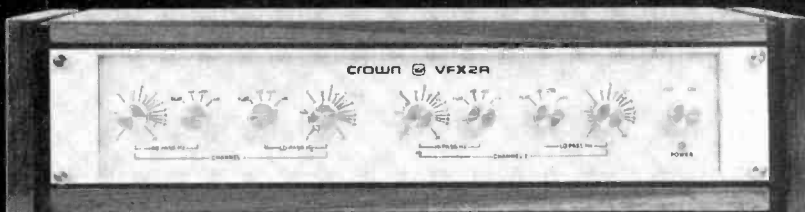

**CROWN**  
Box 1000, Elkhart IN 46514



101-416 p.—Electronic Circuit Design Handbook-4th Edition (\$17.95)

**ELECTRONIC CIRCUIT DESIGN HANDBOOK**  
By the Editors of ESD: Design

**Practical CB Radio Troubleshooting & Repair**  
By David F. Norman

754-234 p.—Practical CB Radio Troubleshooting and Repair (\$8.95)

**OPTOELECTRONICS GUIDEDBOOK—**  
with tested projects  
By R. W. Fox

**THE COMPLETE AUTO ELECTRIC HANDBOOK—**  
A Practical Guide to Diagnosis & Repair

741/749-466 p.—TWO BOOKS—The Complete Auto Electric Handbook & Auto Electronics Simplified (\$17.90)

836-196 p.—Optoelectronics Guidebook—With Tested Projects (\$8.95)

**AUTO ELECTRONICS SIMPLIFIED—**  
Diagnosis & Repair

**Electronic Music Circuit Guidebook**  
by Bruce Ward

**Master Handbook of 1001 Practical Electronic Circuits**  
Edited by Kenneth Webster Sessions

800-602 p.—Master Handbook of 1001 Practical Electronic Circuits (\$12.95)

785-254 p.—Microprocessor Microprogramming Handbook (\$9.95)

**Microprocessor Microprogramming Handbook**  
by Bruce Ward

**BUILD YOUR OWN WORKING ROBOT**  
BY DAVID L. HEISERMAN  
Step-by-step instructions on how to build a robot with great brain characteristics. Also includes construction details.

841-238 p.—Build Your Own Working Robot (\$8.95)

**Practical Solid-State DC Power Supplies**

891-196 p.—Practical Solid-State DC Power Supplies (\$9.95)

**How to Repair Home Laundry Appliances**

855/885-574 p.—TWO BOOKS—How to Repair Home Laundry Appliances & How to Repair Home Kitchen Appliances (\$17.90)

628/637-392 p.—TWO BOOKS—Basic Electricity and Beginning Electronics & Fun With Electronics (\$15.90)

**Beginner's Guide to TV REPAIR**

132/627/672-363 p.—THREE BOOKS—How to Test Almost Everything Electronic & Basic Electronic Test Procedures & Understanding and Using the VOM and EVM (\$24.85)

**MASTER TRANSISTOR/IC SUBSTITUTION HANDBOOK**

970-518 p.—Master Transistor/IC Substitution Handbook (\$11.95)

**2ND CLASS FCC ENCYCLOPEDIA**  
—Complete Study Guide to the Commercial Radiotelephone Exam  
Topics: 1, 2, 3, 4, 9

652-602 p.—2nd Class FCC Encyclopedia: Complete Study Guide to the Commercial Radiotelephone Exam (\$10.95)

**How to Repair Home Kitchen Appliances**

**FUN WITH ELECTRONICS**  
By Kenneth Webster Sessions

**INSTALLING TV & FM ANTENNAS**  
Leo G. Sands

563/636-344 p.—TWO BOOKS—Beginner's Guide to TV Repair & Installing TV and FM Antennas (\$15.90)

**BASIC ELECTRONIC TEST PROCEDURES**

**Radio Astronomy for the Amateur**  
by Dava Heiserman

714-252 p.—Radio Astronomy for the Amateur (\$8.95)

An Extraordinary Offer to introduce you to the benefits of Membership in  
**ELECTRONICS BOOK CLUB**  
take any **3** of these unique electronics books (value to \$62.70) for only **99¢** each  
with a Trial Membership in the Book Club that guarantees to save you 25% to 75% on a wide selection of electronics books

May we send you your choice of these 3 practical, time-and-money-saving books as part of an unusual offer of a Trial Membership in Electronics Book Club?

Here are quality hardbound volumes, each especially designed to help you increase your know-how, earning power, and enjoyment of electronics. Whatever your interest in electronics, you'll find Electronics Book Club offers practical, quality books that you can put to immediate use and benefit.

This extraordinary offer is intended to prove to you, through your own experience, that these very real advantages can be yours...that it is possible to keep up with the literature published in your areas of interest, and to save substantially while so doing. As part of your Trial Membership, you need purchase as few as four books during the coming 12 months. You would probably buy at least this many anyway...without the substantial savings offered through Club Membership.

To start your Membership on these attractive terms, simply fill out and mail the coupon today. You will receive the 3 books of your choice for 10-day inspection. **YOU NEED SEND NO MONEY!** If you are not delighted, return the books within 10 days and your Trial Membership will be cancelled without cost or obligation.

ELECTRONICS BOOK CLUB, P.O. Box 10, Blue Ridge Summit, Pa. 17214

**Facts About Club Membership**

- The 3 introductory books of your choice carry publishers' retail prices of up to \$62.70. They are yours for only 99¢ each (plus postage/handling) with your Trial Membership.
- You will receive the Club News, describing the current Selection, Alternates and other offerings, every 4 weeks (13 times a year)
- If you want the Selection, do nothing; it will be sent to you automatically. If you do not wish to receive the Selection, or if you want to order one of the many Alternates offered, you simply give instructions on the reply form (and in the envelope) provided, and return it to us by the date specified. This date allows you at least 10 days in which to return the form. If, because of late mail delivery, you do not have 10 days to make a decision and so receive an unwanted Selection, you may return it at Club expense.
- Personal service for your account—no computers used!
- To complete your Trial Membership, you need buy only four additional monthly selections or alternates during the next 12 months. You may cancel your Membership any time after you purchase these four books.
- All books—including the Introductory Offer—are fully returnable after 10 days if you're not completely satisfied.
- All books are offered at low Member prices, plus a small postage and handling charge.
- **Continuing Bonus:** If you continue after this Trial Membership, you will earn a Dividend Certificate for every book you purchase. Three Certificates, plus payment of the nominal sum of \$1.95, will entitle you to a valuable Book Dividend of your choice which you may choose from a list provided Members.

**ELECTRONICS BOOK CLUB**

P.O. Box 10  
Blue Ridge Summit, Pa. 17214

Please open my Trial Membership in ELECTRONICS BOOK CLUB and send me the 3 books circled below. I understand the cost of the books I have selected is only 99¢ each, plus a small shipping charge. If not delighted, I may return the books within 10 days and owe nothing, and have my Trial Membership cancelled. I agree to purchase at least four additional books during the next 12 months, after which I may cancel my membership at any time.

101	132/627/672	563/636	628/637
754	785	800 836	841 855/885 891 970

Name \_\_\_\_\_ Phone \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_

State \_\_\_\_\_ Zip \_\_\_\_\_

(This offer valid for new Members only. Foreign and Canada add 10% PE-57)

# Where do the pros get their training?



**Almost half of the successful TV servicemen have home study training and with them, it's NRI 2 to 1.** It's a fact! Among men actually making their living repairing TV and audio equipment, more have taken training from NRI than any other home study school. More than twice as many!

A national survey\*, performed by an independent research organization, showed that the pros named NRI most often as a recommended school and as the first choice by far among those who had taken home study courses from any school. Why? Perhaps NRI's 62-year record with over a million students . . . the solid training and value built into every NRI course . . . and the designed-for-learning equipment originated by NRI provide the answer. But send for your free NRI catalog and decide for yourself.



**25" Diagonal Color TV...  
And 4-channel  
Quadraphonic Stereo.**

As a part of NRI's Master Course in color TV/Audio servicing, you build a 25" diagonal solid state color TV with console cabinet. As you build it, you perform stage-by-stage experiments designed to give you actual bench experience. And you get a Quadraphonic system with 4 speakers. NRI's instruments are a cut above the average, including a transistorized volt ohm-meter, triggered sweep 5" oscilloscope, CMOS digital frequency counter and digital integrated circuit color TV pattern generator. They're top professional quality, designed to give you years of reliable service. You can pay hundreds of dollars more for a similar course and not get a nickel's worth extra in training and equipment.

**Widest Choice of  
Courses and Careers.**

NRI doesn't stop with just one course in TV/Audio servicing. You can pick from five different courses (including an advanced color course for practicing technicians) so you can fit your training to your needs and your budget. Or, you can go into Computer Technology, learning on a real, digital computer you build yourself. Communications with your own 400 channel digitally-synthesized VHF transceiver. Aircraft or Marine Electronics. CB, Mobile Radio, and more.

**Free Catalog...  
No Salesman Will Call.**

Send the postage-paid card for our free color catalog showing details on all NRI electronics courses. Lesson plans, equipment, and career opportunities are fully described. Check card for information on G.I. benefits. No obligation, no salesman will call. Mail today and see for yourself why the pros select NRI two to one!

If card is missing, write,


\*Summary of survey results upon request.

**Two Famous Educators...  
NRI and McGraw-Hill.**

NRI is a part of McGraw-Hill, world's largest publishers of educational material. Together, they give you the kind of training that's geared for success . . . practical know-how aimed at giving you a real shot at a better job or a business of your own. You learn at home at your convenience, with "bite-size" lessons that ease learning and speed comprehension. Kits designed to give you practical bench experience also become first-class professional instruments you'll use in your work.



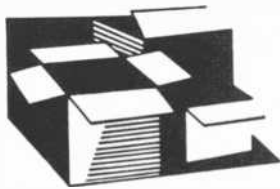**NRI SCHOOLS**  
McGraw-Hill Continuing Education Center  
3939 Wisconsin Avenue,  
Washington, D.C. 20016



# New Products

Additional information on new products covered in this section is available from the manufacturers. Either circle the item's code number on the Reader Service Card inside the back cover or write to the manufacturer at the address given.

## PRESIDENT 40-CHANNEL CB TRANSCEIVER

The "Zachary T" 40-channel CB AM base-station transceiver from President Electronics features a new automatic speech compression circuit and a PLL in the frequency synthesizing system. The compressor is designed to provide consistent high-level modulation, while the PLL circuit is said to provide




better on-frequency response than is possible with a conventional synthesizer. Selectivity is rated at -65 dB. Controls include volume, r-f and mike gain, anl (with manual override) and PA/CB switches. Also on the front panel is an S/r-f meter. Back-panel jacks provide for both ac and dc power input, antenna connection, and hookup of PA and external speakers. The earphone and mike jacks are up front. The transceiver also features a LED numeric channel display. \$249.95.

CIRCLE NO. 92 ON FREE INFORMATION CARD
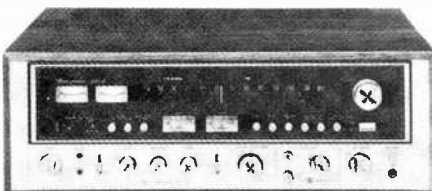
## SANSUI HIGH-POWER STEREO RECEIVER

Sansui's high-power Model 9090DB AM/stereo FM receiver is rated at 125 watts / channel (8 ohms) minimum rms at no more than 0.1% THD. The power amplifier is direct-coupled throughout, with fully complementary parallel push-pull OCL circuitry. Twin power meters provide convenient output power monitoring. Built in is a Dolby noise reduction system that can be used for both encoding and decoding for full flexibility. The tuner section features a PLL IC multiplex demodulator



12

that provides improved stereo separation on FM. FM sensitivity is rated at 9.8 dBf (1.7  $\mu$ V) and capture ratio and alternate-channel selectivity are rated at 1.5 and 85 dB, respectively. A front-panel microphone jack, with its own level control, permits mixing any selected source with the microphone signal for use in PA systems. \$750.

CIRCLE NO. 93 ON FREE INFORMATION CARD

## CIBCO CB PERFORMANCE MONITOR

A constant CB performance indicator that features light-emitting diodes for easy monitoring of SWR and transmitter output power is available from CiBco Division of Southwest Factories, Inc. The Model CPI II in-line monitor employs a green LED that indicates trans-



mission output of 3.5 watts or more. A red LED comes on when reflected power exceeds a 1.8:1 SWR. (The red LED doubles as a speech modulation indicator.) Indications are produced automatically by pressing the microphone switch. In case of trouble, the red LED flashes an immediate warning. Hence, shorting or theft of the antenna is immediately evident, preventing damage to the output transistors in a CB transmitter. The monitor comes with a PL259 connector for easy installation between transceiver and antenna. \$19.95. Address: CiBco Div., Southwest Factories, Inc., 3801 Willow Springs, Oklahoma City, OK 73112.

## MICRO-ACOUSTICS PHONO CARTRIDGE

The Model 282-e stereo phono cartridge from Micro-Acoustics has a unique design that is said to enable it to track warped records 25% better than competitive cartridges. It is also said to be immune to the effects of cable ca-



pacitance and not to be tonearm sensitive. The cartridge is fitted with a 0.002 x 0.007 mil elliptical diamond stylus. Frequency response is rated at 5 to 20,000 Hz  $\pm$ 2 dB, tracking force range at 0.75 to 1.5 grams, separation at nominally 25 dB at 1000 Hz (15 dB at 10,000 Hz), and output voltage at 3.5 mV/channel at 5 cm/s peak recorded velocity. Load requirements are not critical and can

be anywhere in the range from 10,000 to 100,000 ohms. Similarly, cable capacity is not critical at 100 to 1500 pF.

CIRCLE NO. 94 ON FREE INFORMATION CARD


## AMI MICROCOMPUTER KIT

American Microsystems, Inc., is offering its S6800  $\mu$ P in kit form for computer hobbyists. The top-of-the-line Model EVK 200 kit contains all necessary components for complete construction, including a preprogrammed ROM for system monitor and general software utilities. Only a power supply and suitable I/O devices are required for operation. Level-control circuitry, baud-rate generation (50 to 9600 baud), and adjustability are built into the basic board. The CPU is the AMI S6800 eight-bit chip, with an instruction execution of 2  $\mu$ s and memory access time of 575 ns. The system provides four available interrupt vectors and three types of DMA. A 1-MHz clock provides a 100- $\mu$ s and 1-ms timer. Also on-board are the I/O interfaces and an EPROM programmer (EPROM device included). \$495. (Also available fully assembled as Model EVK 300 for \$765.)

CIRCLE NO. 95 ON FREE INFORMATION CARD
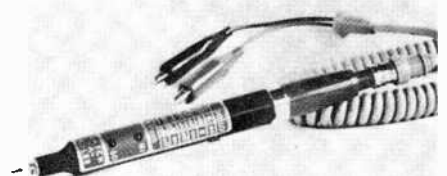
## AVR LOGIC PROBE

The Catch-A-Pulse logic probe from AVR is compatible with RTL, DTL, TTL, CMOS, MOS, and with microprocessors using 3.5-V to 15-V power supplies. Thresholds are automatically programmed for multi-logic-family operation. The memory circuit for single or



multi-pulse detection resets automatically. LED's indicate high and low levels, open-circuit logic, and pulses. Designed for carrying in a shirt pocket, the probe has a protective cap for the top, and a removable coiled cord. \$24.95.

CIRCLE NO. 96 ON FREE INFORMATION CARD

## KOSS ELECTROSTATIC STEREOPHONES

The Model ESP/10 electrostatic stereo headphones made by Koss plug into an electrostatic energizer unit that can be operated on as little as 25 watts of continuous power per channel. The energizer, which accommodates two sets of headphones, has semi-



POPULAR ELECTRONICS

# Old Fashion **VALUE**

## in the **U.S.A.** Tradition

Our 6800 computer system represents the best value available today, with no sacrifice in performance.

I would like to explain why this is true. The most basic reason is that the 6800 is a simpler, more elegant machine. The 6800 architecture is memory oriented rather than bus oriented as are the older 8008, 8080 and Z-80 type processors. This is an important difference. It results in a computer that is far easier to program on the more basic machine language and assembly language levels. It also results in a far simpler bus structure. The 6800 uses the SS-50 bus which has only half the connections needed in the old S-100 (IMSAI/MITS) bus system. If you don't think this makes a difference, take a look at the mother boards used in both systems—compare them. The SS-50 system has wide, low impedance 0.1 lines with good heavy, easily replaced Molex connectors. The S-100 bus, on the other hand, has a very fine hair-like lines that must be small enough to pass between pins on a 100 contact edge connector. I'll give you one guess which is the most reliable and noise free. As for cost—well any of

you who have purchased extra connectors for your S-100 machines know what kind of money this can run into. The 6800 is supplied with all mother board connectors. No extras, or options like memory, or connectors for the mother board are needed in our 6800 system.

The 6800 is not beautiful, but "Oh Boy" is it functional. That plain black box is strong and it has an anodized finish. This is the hardest, toughest finish you can put on aluminum. Most others use paint, or other less expensive finishes. The 6800 does not have a pretty front panel with lights and multicolor switches. This is because the lights and switches are not only expensive, and unnecessary, but also a great big pain to use. We don't crank up the 6800; we use an electric starter—a monitor ROM called Mikbug. He automatically does all the loading for you without any time wasting switch flopping. So in the 6800 system you don't buy something expensive (the console) that you will probably want to stop using as soon as you can get your hands on a PROM board and a good monitor.

That's another thing. Mikbug<sup>®</sup> is a standard Motorola part. It is used in many systems and supported by the Motorola software library in addition to our own extensive collection of programs. It is not an orphan like many monitor systems that are unique to the manufacturer using them and which can only run software provided by that manufacturer. Check the program articles in Byte, Interface and Kilobaud. You will find that almost all 6800 programs are written for systems using a Mikbug<sup>®</sup> monitor. Guess how useful these are if you have some off-brand monitor in your computer.

The 6800 will never win any beauty prizes. It is like the Model "T" and the DC-3 not pretty, but beautiful in function. It is simple, easy to use and maintain and does its job in the most reliable and economical way possible. What more could you want?

*Mikbug<sup>®</sup> is a registered trademark of Motorola Inc.*

**SWTPC 6800**  
Computer System  
with serial interface and 4,096 words of memory . . . . . \$395.00



Enclosed is \$395 for my SWTPC Computer Kit       Send Data

or BAC \_\_\_\_\_ # \_\_\_\_\_

or MC \_\_\_\_\_ Ex Date \_\_\_\_\_

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

CITY \_\_\_\_\_ STATE \_\_\_\_\_ ZIP \_\_\_\_\_

Southwest Technical Products Corp., Box 32040, San Antonio, Texas 78284

# VALUE & PERFORMANCE

EICO's 30 Years Experience  
Assures More Electronics Value  
For Your Money!

## TEST INSTRUMENTS



**NEW!**

### EICO 388 COLOR BAR GENERATOR

Pocket-size, battery operated with LED Indicator. MOS LSI IC provides 9 digitally controlled, stable patterns. Crystal controlled chroma and timing oscillators. Simply connects to TV's VHF antenna terminals.

Wired \$89.95

### EICO 390 FUNCTION/SWEEP GENERATOR

Outstanding features include: Sine, Square, Triangle Waveforms; .2 Hz to 200 KHz frequency range; Linear and Log Sweep; Calibrated attenuator, VCO for External Frequency Control; BNC Front Panel Output.

Wired \$169.95

## CB ACCESSORIES



**NEW!**

### EICO 700 CB FREQUENCY COUNTER

Compact in-line mobile frequency counter for the serious CB'er/Hobbyist. Operates automatically on transmit. 10 Hz to 30 MHz. \$99.95

### EICO LR-3 "LONG RANGER" INLINE PREAMP

Bring in those distant/weak signals. Boosts receiver sensitivity up to 20 db. Automatic transmit/receive switching. \$29.95

### EICO CM-2 "CHANNEL MONITOR" AUTO-SWITCH

Automatically silences car radio when CB call is received/transmitted. \$29.95

## EICOCRAFT® IC KITS

EC-5000  
SCA  
ADAPTOR KIT  
ONLY \$12.95



Convert your FM radio or receiver to pick up the official FCC-licensed background music service (SCA). IC decoder/adaptor permits hearing uninterrupted, commercial-free music broadcast by many FM stations (For personal, non-commercial use only).

### IC PROJECT KITS NOW AVAILABLE

EC-5100 ESP Tester \$10.95  
EC-5200 "Decision Maker" \$9.95  
EC-5400 Stereo Power Amplifier \$10.95  
EC-5500 Stereo Pre-Amp \$9.95  
EC-5600 Electronic Lock \$11.95  
EC-5700 Universal Power Amp \$8.95

## HOBBY/AUTOMOTIVE



**NEW!**

### BW-300 ALPHA BRAINWAVE MONITOR

Lowest cost, battery operated, professional Biofeedback System. IC Circuit design features an active filter and 5-microvolt sensitivity. Complete with stethoscopic earphone, electrode headband and instructions.


Kit \$34.95 Wired \$59.95

### 885 "TUNEMASTER" ENGINE ANALYZER

Automatic all-in-one test bench for all 6 or 12 volt ignitions—conventional or transistorized. Giant 6" meter with 6 color coded scales. Complete with tune-up and trouble-shooting manual.

Wired \$59.95

## BURGLAR/FIRE ALARMS

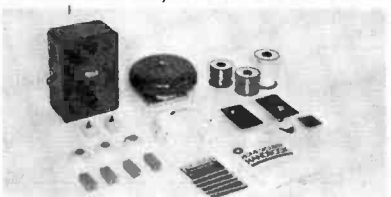

### SS-500 BURGLAR/FIRE ALARM SYSTEM

Professional Security System designed for easy do-it-yourself installation. Features EICO FC-100 Control Center with AC/DC automatic transfer to battery operation. Complete system includes Installation Handbook. Add additional sensors, bells, to suit your own needs. \$159.95

### SD-75 BATTERY OPERATED FIRE/SMOKE ALARM

Ionization-type detector gives earliest possible fire warning. Mounts directly to ceiling with 2 screws. "Beeps" when battery needs replacement. U.L. listed. \$39.95

## FREE EICO CATALOG

The more you know about electronics, the more you'll appreciate EICO. Every EICO product is designed to provide you with the most pleasure and quality performance for your money. The fact that more than 3 million EICO products are in use attests to their quality and performance.

"BUILD-IT-YOURSELF" and save up to 50% with our famous electronic kits.

For the latest EICO Catalog and name of nearest EICO Distributor, check reader service card or send 50¢ for fast first class mail service.

EICO-283 Malta Street, Brooklyn, N.Y. 11207

Leadership in creative electronics since 1945.



peak-indicating level meters and features an automatic overload device that protects against excessive audio input levels. The LED indicator glows when the protection circuit is activated and shuts off the energizer. Once the protection circuit is activated, it keeps the energizer shut off for 3 to 4 seconds after the excessive level drops to a safe value. \$300.

CIRCLE NO. 97 ON FREE INFORMATION CARD


## MAYCOM CB MOBILE ANTENNAS IN COLOR

Riotous Red, Lily White, Big Blue, Sand Tan, Cat Black, Down Brown, Grimly Gray, Machine Green, and Yellin' Yellow are the colors of a new line of CB "Colorwhip" mobile antennas from MayCom. The antennas and mounts can be purchased in matching or mixed colors to complement or coordinate with the vehicles on which they are installed. The patented fiberglass whips come in 4' and 6' (1.2 and 1.8 m) lengths with top-loaded, helically wound radiators, plastic sheaths, and chrome-plated brass ferrules. Prices are \$10.25 and \$11.25, respectively. No-drilling Model GW-7 trunk mounts are also available in color for \$13.45.

CIRCLE NO. 98 ON FREE INFORMATION CARD
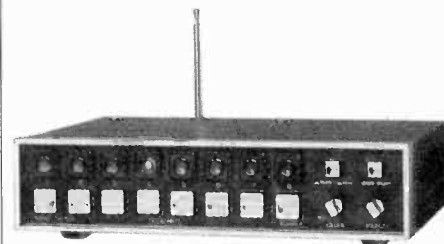
## HEATH HIGH-BAND SCANNING RECEIVER

The Model GR-1131 high-band scanner from the Heath Company monitors any combination of eight channels in the "emergency-services" public-safety band between 146 and 174 MHz, including those from the U.S.



Weather Service. The receiver scans each channel, stopping at any that is active, and resumes scanning after the transmission. A priority channel feature checks the channel in which the user is most interested every four seconds and automatically switches to it if there is activity there. Features include channel lockout buttons, lighted channel indicators, automatic/manual channel selection, and a four-pole crystal filter for good selectivity. For crowded areas, an optional eight-pole filter is available. Also featured are a built-in telescoping antenna and provision for an external antenna. Ac or 12-volt dc operation. \$89.95.

CIRCLE NO. 90 ON FREE INFORMATION CARD

## AMP HAND WIRE STRIPPER

AMP Special Industries Hand Wire Stripper employs front-feed stripping action to make short wires easy to strip. A built-in sensor

POPULAR ELECTRONICS

# THE TERMINAL YOU ASKED FOR

# CT-64

- \* 16 LINES – 64 or 32 CHARACTERS PER LINE
- \* SCROLLING ON EITHER OF TWO PAGES OF DISPLAY
- \* 128 CHARACTER ASCII SET – UPPER AND lower CASE LETTERS
- \* PRINTS CONTROL CHARACTERS IF DESIRED
- \* FULL 32 CHARACTER CONTROL DECODING
- \* FULL 8 BIT MEMORY
- \* 110/220 Volt 50-60 Hz POWER SUPPLY
- \* COMPLETELY INDEPENDENT DESIGN—Usable with any 8 bit ASCII computer or with modem for time share applications.
- \* MOLDED PLASTIC COVER – MATCHING MONITOR AVAILABLE

Now you can buy it. The terminal that has all the features that people have been asking us to include. The CT-64 has all the functions that you could want in a terminal and they may be operated by either switches, or through a software program.

All cursor movements, home-up and erase, erase to end of line, erase to end of frame, read on, read off, cursor on, cursor off, screen reversal, scroll, no scroll, solid cursor, blinking cursor, page selection and a beeper to warn you of end of page; all are provided for your use in the CT-64.

You may also switch from upper case only teletype style operation to upper-lower case typewriter style operation. You can reverse the field on individual words to highlight them, or you can reverse the whole screen.

CT-64 is complete with keyboard, power supply serial interface and case. A matching 9 inch monitor with coordinated covers is also available to make a complete system.

CT-64 Terminal Kit \$325.00

MM-1 Monitor (assembled) \$175.00



219 W. Rhapsody

San Antonio, Texas 78216

You are right, it's just what I have been asking for.

Enclose is \$325.00 for the CT-64

Send the MM-1 monitor too.

Send Data

or BAC \_\_\_\_\_ # \_\_\_\_\_

or MC \_\_\_\_\_ Ex Date \_\_\_\_\_

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

CITY \_\_\_\_\_

STATE \_\_\_\_\_

ZIP \_\_\_\_\_

Southwest Technical Products Corp.

219 W. Rhapsody, San Antonio, Texas 78216



measures the wire and adjusts the tool for optimum stripping action with minimum hand pressure. The tool is molded of lightweight plastic. Wire and cable up to #12 AWG solid or stranded can be cut and stripped by the tool. Paired wires can be stripped simultaneously. \$33. Address: AMP Special Industries, Valley Forge, PA 19482.

#### KEYBOARD VIDEO INTERFACE

The Merlin keyboard video interface, from MiniTerm Associates, provides ASCII characters (20 lines of 40 characters), high-resolution graphics, and optional monitor and editor functions. The two boards include a DMA controller that permits displaying any part of the computer memory. Also, since the display's starting address is software-controlled, the memory segment displayed can be changed with every screen refresh. Dense graphics will display 2k words of memory as 160H by 100V dots; sparse graphics displays



1k as 80H by 100V. Versions of Merlin for Altair, Imsai, Southwest 6800 and Digital Group computers are available at \$249.00 kit plus \$34.95 for an optional on-board 2k ROM for the monitor and editor functions.


CIRCLE NO. 99 ON FREE INFORMATION CARD

#### POLYTRON OP AMP DESIGNER TESTER

Designed to help both the beginner and experienced user to experiment with and test circuits containing one or two op amps, the "Dual Op Amp Designer Tester" from Polytron Devices doesn't require any soldering. Components other than op amps can be plugged in. Features include solderless tie points, two 10k potentiometers, four pairs of binding posts, four IC sockets. Model 202 with  $\pm 15\text{-V}$ , 100-mA dc regulated power supply is \$55; Model 201, using 9-V batteries, is \$33. Address: Polytron Devices, Inc., Box 398, Paterson, NJ 07524.
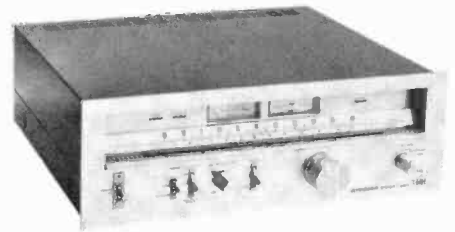
#### PIONEER AM/STEREO FM TUNER

Pioneer's Model TX-9500II AM/stereo FM tuner has an automatic pilot-signal canceller that minimizes 19-kHz leakage into the audio



section. Featuring both narrow- and wide-band operation, it also has a SAW (surface acoustic wave) filter that minimizes adjacent-channel interference. A switch permits using the amplifier/speaker system, minus oscilloscope, to detect multipath reflections as the FM antenna is adjusted. The alternate position of this switch generates a 440-Hz signal every 1.6 seconds (equivalent to 50% FM modulation) for checking the level on a tape deck before recording off the air. Specifications include: 8.8 dBf (1.5- $\mu\text{V}$ ) sensitivity in mono; 13.2 dBf (2.5  $\mu\text{V}$ ) in mono and 36.1 dBf (35  $\mu\text{V}$ ) in stereo 50-dB quieting sensitivity; 77 to 82 dB S/N at 65 dBf; 20 to 15,000 Hz  $+0.2/-0.5$  dB stereo frequency response; and 0.05% to 0.07% distortion in mono at 1000 Hz. \$400.

CIRCLE NO. 100 ON FREE INFORMATION CARD

# Aircommand 40-channel CB..



From the people who bring you Marantz—the world's finest stereo systems—comes the Aircommand CB-640—the finest in 40-channel CB. With Aircommand you get over 25 years experience in outstanding 2-way communications products.

**Full 6 Watts of audio power.** Provides plenty of punch so your speaker cuts through freeway noise.

**Dual-conversion superheterodyne receiver** with dual-cascaded ceramic filters. Together, both features provide the most complete rejection of unwanted signals, assuring you unsurpassed selectivity and sensitivity.

**4 big Watts of RF power.** Aircommand delivers the maximum power legally allowable to let you belt out the big sound.

**100% modulation capability.** Even when you talk softly into the mike, your message cuts through loud and clear, thanks to one of the most advanced mike preamp and compressor designs in CB today. With Aircommand, you don't have to spend an extra \$30 to \$40 on a "power mike." You can't buy better modulation than Aircommand.

**Specially tailored frequency response.**


**LED 40-channel selection display.** Easy-to-read, night or day.

**8-LED (light emitting diode) meter display.** Provides an easy-to-read display of SWR (standing wave ratio), modulation, and incoming or outgoing signal strength—instantly, accurately.

**Special emergency Channel 9 scan with exclusive Aircommand "beep" alert.** No matter what channel you're on, a special Aircommand CB-640 circuit continuously and silently monitors Emergency Channel 9. When someone starts transmitting on Channel 9, a unique "beep" alerts you, so you can tune yourself in and give assistance.

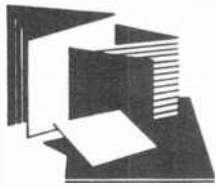**Public address capability.** The versatile Aircommand CB-640 public address package lets you (1.) Talk into the CB mike and out an exterior public address speaker. (2.) Attach a tape recorder to the auxiliary jack on the





# New Literature

## VOLTAGE-SURGE SUPPRESSOR CROSS-REFERENCE

A new cross-reference application note, AN504A, for voltage-surge suppressors to protect power semiconductors is available. Over 175 General Electric parts numbers are listed, along with the International Rectifier replacements that are exact mechanical duplicates, including the same power-handling capability. Address: Semiconductor Division, International Rectifier, 233 Kansas St., El Segundo, Calif. 90245.

## SEMICONDUCTOR TEST INSTRUMENTS

A 6-page brochure from B&K Precision describes the company's complete line of discrete semiconductor test instruments. Products featured include the Model 530 semiconductor tester with unity-gain frequency measurement up to 1500 MHz. Technical specifications provide data on in-circuit and out-of-

circuit tests, applied test currents, indicator, calibration and limiting in-circuit shunt values. Applications for each model are also discussed. Address: B&K Precision, 6460 W. Cortland Ave., Chicago, IL 60635.

## GUIDE TO SOLDERING ALUMINUM

A 6-page brochure from Multicore Solders provides information on soldering aluminum. Performance information including a table on the solderability of various wrought and cast aluminum alloys is presented with application and technical data, joint recommendations and soldering techniques. Technical specifications and performance of the company's Alu-Sol 45D are also discussed. Address: Multicore Solders, Westbury, NY 11590.

## CB ANTENNA CATALOG

A new catalog SP-4 from Antenna Incorporated describes its line of Citizens Band antennas and accessories. Specifications are provided for each base and mobile antenna with similar styles listed together for easy reference. Replacement parts and accessories are also included. The catalog, Form SP-4, is available from Antenna Incorporated distributors.

## VOLTAGE DROP MEASUREMENTS

"Forward Voltage Drop Measurements" is the title of Tech Tips 4-6 from Westinghouse. The 3-page article, written to assist in making accurate measurements on power diodes

and thyristors that can be used as a quality control check or matching criteria for operating devices in parallel, utilizes a simplified diagram of a test circuit and explains ways to avoid inaccurate measurements caused by pulse widths, duty cycles, peak currents, mounting and measurement techniques. Address: Semiconductor Division, Westinghouse Electric Corp., Youngwood, PA 15697.

## EXACT REPLACEMENT GUIDES

Thordarson Meissner, Inc. offers two new cross-reference replacement guides for CB radios and TV sets. "TV Replacement Parts Guide" Form TVPG 9 and "CB Replacement Parts Guide" Form CBRG 2 include 127 new exact electronic replacement products recently made available by the company. Guides are available from Thordarson distributors.

## WIRE-WRAPPING AND TOOL CATALOG

Catalog 36G is the new 58-page catalog from O.K. Machine and Tool Corp. which describes its line of Wire-Wrapping tools and machines. Additions to the line, including circuit boards, closures and instrument cases, are described; an illustrated section explains the technology of Wire-Wrapping. Address: O.K. Machine and Tool Corp., 3455 Conner St., Bronx, NY 10475.


# ...You never heard it so good!!!

CB-640 rear panel, and boom your tape out through the same external speaker. (3.) Mix your voice from the CB microphone with the program material on the tape recorder. Both voice and tape sound at the same time through the external speaker. (4.) Beam your received signal through the external speaker. Built-in standing wave ratio circuitry. Measures the efficiency of the antenna system for optimum performance. Other outstanding features include: Delta fine tuning control, digital synthesizer with phase-locked loop,

automatic noise limiting switch, noise blanking switch, squelch control, RF gain control.

Also available: Aircommand CB-140; Aircommand CB-340. All 3 units bring you state-of-art design, flawless craftsmanship and day-in, day-out reliability. Try them out now at your Superscope Aircommand dealer.

**Aircommand** by **SUPERSCOPE.**

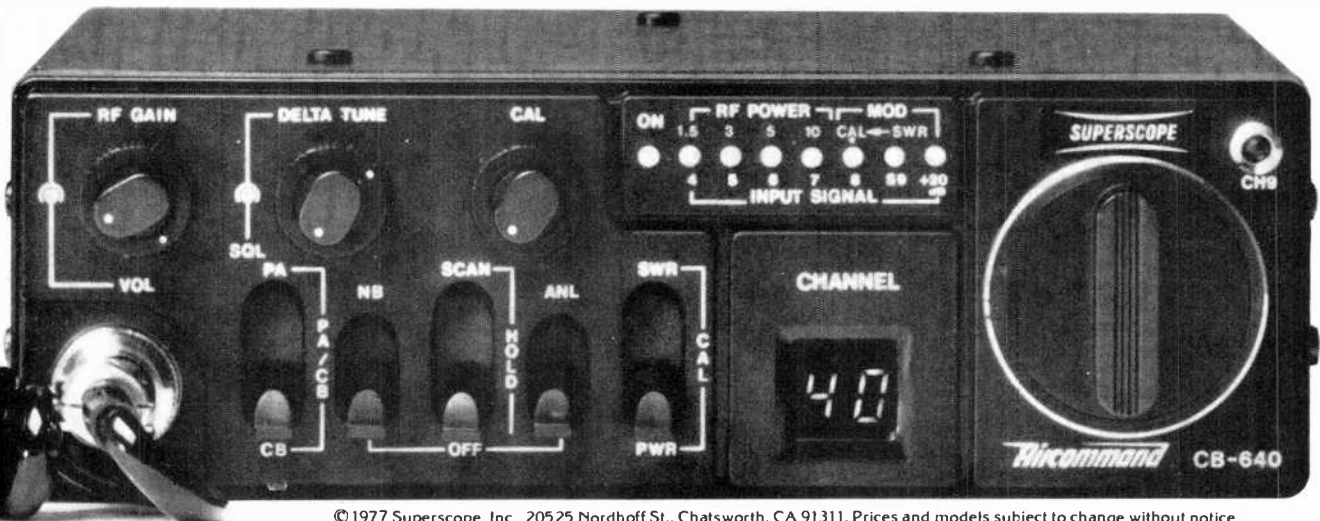

©1977 Superscope, Inc., 20525 Nordhoff St., Chatsworth, CA 91311. Prices and models subject to change without notice.



# Stereo Scene

By Ralph Hodges

## THE DECONTAMINATION SQUAD

**F**OR THE PAST few months (whenever I've remembered to), I've been asking people how they care for their phonograph records. Their replies have been highly individualistic. On the one hand we have the manic camp, systemized to the point where they feel vaguely uncomfortable listening to a record that has not been put through an elaborate cleaning ritual, whether they can hear any noise or not. (I number myself among this group.) At the other extreme are those joyous devil-may-cares who may blow on a disc several times (quite ineffectually, no doubt) as they carry it to the turntable, but otherwise hardly give the matter a thought.

In my circle, almost everyone who takes records seriously owns some sort of cleaning appliance for them. Velvet or plush-covered pads and specially designed brushes are common (choice of pad or brush seems to depend on intui-

tive "feel" for the cleaning process), as are Dust Bugs and similar devices. These may or may not be used religiously. I have seen some Dust Bugs so begrimed that their use would probably be a hazard rather than a help to the condition of any decent record, so the benign-neglect approach is not always inappropriate.


**Ask the Experts.** Why, after all these years, is record hygiene still a matter of guesswork rather than science? The question would be a fascinating one if its answer weren't so obvious. Ask the phono-cartridge manufacturers, whose interest in properly maintained records is readily apparent: "You know, we've always been meaning to look into that. We use the Whatchamacallit, or at least there's one at every testing station, and it seems to do okay. But then again, in the absence of a suitable control sam-

ple . . ." Ask the record companies: "All our records are clean and defect-free when they leave the plant, and with reasonable care . . ." In other words, no one—or at least no one who doesn't intend to manufacture a record-cleaning device of his own—has the time to undertake the research necessary. And no wonder, because when you think about it, such a research project turns out to be fairly formidable.

A few hardy types, including some of my eminent colleagues in the press, have made yeomanly attempts to settle the issue in the laboratory. Their tests have generally taken two forms. The first is to play the dirty record, count (somehow) the number and severity of the ticks and pops presumably caused by dirt, then clean the record with the device under test, and play it again to note the improvement, if any. The trouble here is that the very process of playing a record alters its noise content. According to theory, certain dust particles will become embedded in the vinylite material by the stylus pressure—embedded too firmly for removal by any practical cleaning device. Hence the cleaning device under test faces the handicap of working with a record that has already been damaged by being played when dirty. But then, if you go on to play the record several more times, the severity of the "tick" caused by the embedded particle may abate considerably, as repeated passages of the stylus smooth the blight on the groove wall. Play the record with a different stylus and the "tick" may disappear altogether, because the stylus rides lower or higher in the groove.

Testing approach number two involves the visual inspection of the dirty and cleaned record with a high-magnification device such as a scanning electron microscope. Here the problem is that on one hand, you can't be sure that what you do see will cause noise. (Certain particles will be nudged aside or missed by the stylus.) On the other hand, what you can't see may cause noise. (An invisible residue of the cleaning agent may gum the stylus and/or raise the base noise level.) Also, there is the considerable drawback of the time involved in examining the whole record—or even a significant portion of it—with high magnification. And time is critical, because with each passing moment the record acquires a little bit of *new* dust.

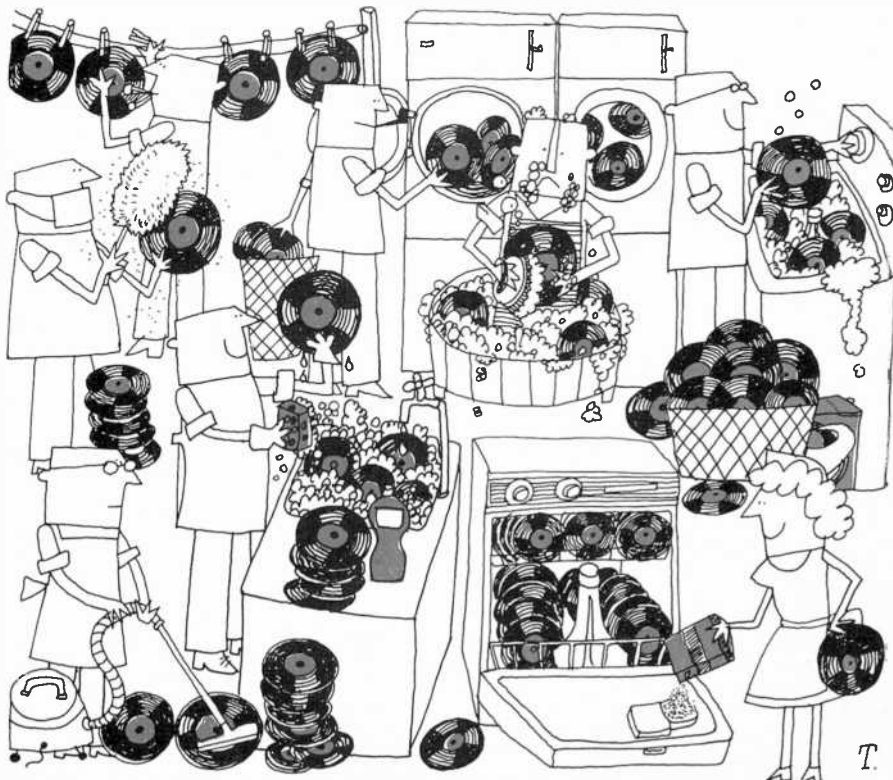Common to both tests are such quandaries as how do you manage to use the cleaning device consistently (most of



# MAGAZINES AT DISCOUNT!

## You SAVE up to 50%

Here's your chance for a real bargain bonanza on your favorite magazines. Select as many as five of these titles at the low introductory rates shown below—up to 50% off. Use attached card to order or write to: **MAGAZINES AT DISCOUNT**, A Division of Ziff-Davis Publishing Co., P.O. Box 2703, Boulder, Colorado 80322.



- APARTMENT LIFE (21)** You pay only \$7.97  
Reg. Rate: 24 Issues for \$14.97
- BOATING (01)** You pay only \$6.00  
Reg. Rate: 12 Issues for \$10.00
- CAR & DRIVER (02)** You pay only \$3.99  
Reg. Rate: 12 Issues for \$7.98
- CYCLE (03)** You pay only \$3.99  
Reg. Rate: 12 Issues for \$7.98
- FLYING (04)** You pay only \$7.99  
Reg. Rate: 12 Issues for \$12.00
- HANDY ANDY (57)** You pay only \$5.88  
Reg. Rate: 10 Issues for \$7.95
- PLAYBOY (34)** You pay only \$12.00  
Newsstand Rate: 12 Issues for \$19.00
- POPULAR ELECTRONICS (06)** You pay only \$6.99  
Reg. Rate: 12 Issues for \$9.98
- POPULAR PHOTOGRAPHY (07)** You pay only \$4.99  
Reg. Rate: 12 Issues for \$9.98
- POPULAR SCIENCE (35)** You pay only \$4.50  
Newsstand Rate: 12 Issues for \$9.00
- PSYCHOLOGY TODAY (08)** You pay only \$7.00  
Reg. Rate: 12 Issues for \$12.00
- SPORTS ILLUSTRATED (38)**  
You pay only \$9.75 for 25 Issues  
Newsstand Rate: 25 Issues for \$25.00  
Basic annual rate: 52 Issues for \$20.00
- STEREO REVIEW (11)** You pay only \$3.99  
Reg. Rate: 12 Issues for \$7.98
- TENNIS (39)** You pay only \$4.75  
Reg. Rate: 12 Issues for \$9.50
- TIME (40)** You pay only \$12.50  
Newsstand Rate: 25 Issues for \$25.00
- TV GUIDE (41)** You pay only \$8.35  
Lowest Available Sub. Rate for 32 Issues

them are hand operated), and how do you establish an adequate control sample of the record. It has been shown repeatedly that "identical" pressings of the same record are far from identical to the stylus and the record-playing environment. According to one theory, the vinylite material of a record takes on a molecular "set" when it is molded, so that the entire disc—or certain random sections of it—acquires a permanent static charge. If the charge distribution varies from pressing to pressing (as it logically should), you have no hope of getting identical pressings.

### **The Mechanism of Dirty Discs.**

The laboratory is revealing but not always authoritative about the record-cleaning question. The reported experiences of long-time record users are valuable but difficult to verify. At this point we need a working hypothesis of how records get dirty so that we can consider what *ought* to be done to get them clean again. Surprisingly, there is no universal consensus on the "mechanism" of dirty discs, but here is the theory to which I generally subscribe.

First, there are airborne particles. These settle on the record as they settle on everything, and remain there unless disturbed. Perhaps they are attracted and held in place by some "net" static charge molded into the record. Then there is grosser debris, from the jacket liner or the turntable mat. This is highly visible and hence disturbing, but most of it is too big to penetrate the record grooves and thus is probably harmless. However, its persistent presence suggests that smaller, invisible bits lie within the grooves themselves.

Next comes the record-playing process, which nicely parallels the workings of a Van de Graaff generator. The intimate contact of stylus and groove (much more intimate with the superior tracing and tracking of today's cartridges) builds up some surface voltages on the disc that are probably quite impressive. These are local charges, but they apparently cooperate with any net charges present in various ways. With your record cleaner you can drag a dust particle some inches away from its location on the record surface, only to have it break free and skip back to its precise point of origin.

When the record becomes surface-charged it acts on dust, certain colloids, and anything else available just as an electrophorous acts on a pith ball. The charges give rise to three noise-producing mechanisms. First, they hold dust

motes in place where they can be played by the stylus and pounded into the vinyl. No casual puff of breath or swipe of record cleaner will effectively dislodge them. Second, they create noises—sometimes quite alarming ones—in themselves, by freely discharging through the phono cartridge. Cartridges and arms differ in their susceptibility to this, but in a dark room you can often see sparks generated as a record is played, accompanied by loud "bam" sounds through the speakers. In milder cases the static discharges are virtually indistinguishable from noise created by dust contamination.

Third, the colloids attracted by the charges often build up to form a tar-like coating on the grooves that interferes with tracing and ultimately gums up phono styli. The irreplaceable Percy Wilson studied the atmosphere's content of such substances and their effects on discs. Ponder his results for a few minutes and you'll begin to sense the onset of black-lung disease.

**On to the Bizarre.** More recently, Bruce Maier of Discwasher has documented the effects of fingerprints (always to be avoided) on records, and also raised the subject of certain fungi that subsist on vinylite and that are actually encouraged by the use of some record-cleaning solutions. I was not at all impressed by Dr. Maier's ideas until, several years ago, I visited Singapore, one of the brisker hi-fi markets of today and, being a mere ninety miles from the equator, a miasma of heat and humidity. There, in the home of a prominent audiophile, I saw my first—heaven help us!—*green* record. According to my host, the algae-like growth forms within a few days. He takes his records to the washroom and uses soap and water to combat it. (I noted few other green records in Singapore, so perhaps he was doing something Dr. Maier wouldn't have approved of.)

**Getting wet.** Many record listeners (Singaporeans excepted) endorse a high-humidity environment as being ideal for the static problem. They place open jars of water beneath their turntables' closed dust covers, or spend a fortune on a large and quiet humidifier. I advise against this. My first reason (another will be discussed later on) is obvious: rust! Back when I could manage long vacations, I summered in a little cottage not twenty-five feet from a quiet seaside harbor. Hardly two years had passed before my tonearm (a cring-

ingly expensive model) began to show characteristic brown stain creeping out of its pivot housing. Most of the arm was aluminum, stainless steel, and/or chrome plated. Unfortunately, the pivot bearings weren't (and few are, for excellent reasons).

Some record-cleaning devices deliberately apply a moisture slick on the record surface and let the stylus plow through that. If there's anything wrong with these appliances (aside from the above) it's hard to detect. In the opinion of some, the stylus cantilever acts as a wick to draw fluid up toward the cartridge. I've never heard anyone complain about this, however. Perhaps what's most suspicious is that the "wet cleaners" tend to remove *all* noise, including that which is molded into the record as groove imperfections. This effect has been ascribed to surface tension, viscosity, and the fact that sound wavelengths are different in water than in air. Or perhaps it's simply a function of the fluid's lubrication. No one seems to know for sure, but a significant number of audiophiles—particularly those with overbright systems—seem to swear by wet playing.

**The Author's Approach.** I suspected you were interested in my own record-cleaning techniques, and I thought you'd never ask. With the record rotating on the turntable, I begin with an anti-static device such as the Discwasher "Zerostat" pistol, which produces clouds of positive and negative ions when the trigger is squeezed or released. This treatment is simply to release the debris particles being held by static charges, which then can be scooped up by a velvet or plush cleaning pad. (Some claim that such a pad won't scoop unless its bristles are slanted, but my experience suggests that a curvature in the contour of the cleaner accomplishes the same thing as a slanted pile.) A little moisture will help the dust particles adhere to the bristles, and I am indebted to a reader for pointing out that open-mouthed breathing on a record will lightly fog it with condensed pure water vapor. So I breathe on the record as I brush.

As the record plays I use a device similar to a Dust Bug, but with a difference. Some years ago, at the height of a very humid summer (remember the objections raised to humidity earlier), I came up against an unaccountable, steady "thththth" sound on a record I knew was intrinsically good and well cared for. What?! Could it be static, encouraged by the high humidity to dis-

# MIDLAND POWER

## IT'S WHAT YOU GET WHEN YOU RUN WITH NUMBER 1.

For 1977, Midland gives you the power to communicate. To reach out beyond your personal horizon.

In an entire new generation of Midland 40-channel CB radios, spearheaded by the remarkable Midland 838.



CIRCLE NO. 37 ON FREE INFORMATION CARD

The 838 features switchable automatic noise limiter, noise blander and audio filter. Plus an automatic channel advance and volume control right on the mike, and a big, bright L.E.D. digital channel indicator.

But the 838 is only one of Midland's '77 CB line, which includes eighteen very comfortably priced base-station, mobile and portable 40-channel models.

All backed by Midland's 15 years of CB experience, Midland's warranty and

convenient service centers, coast to coast.

No wonder we sold over 2 million Midland CB's last year, making us the world's number 1 CB brand.

Midland Power. It's what you want from a CB. It's what you get when you run with number 1.



### MIDLAND CB

A member of the Beneficial Corporation Family

Shop for these active-living products from Midland International: Medalion Car-Sound Products • Goodwin Sporting Goods • Benchmark Tools • Midland Television • Young World Toys

# THE STORM ALARM.

## IT WARNS YOU ABOUT STORMS THE WAY A SMOKE ALARM WARNS YOU ABOUT FIRES.



charge through the cartridge in a rather relaxed fashion? Within ten minutes I had acquired one of the record-tracking/cleaning devices that has conductive bristles intended to be grounded at the tonearm or preamp input. To my fascination, I found that the annoying sound disappeared within a few moments of my lowering the bristles to the record surface, and reappeared a few moments after I had raised them. Needless to say, I held onto this contraption, and it has been doing a fine job ever since. This is my idea of how to clean records; I welcome comments.

As long as this article has been, it has left out some pertinent points: the how and whys of stylus cleaning; the efficacy of the new friction-reducing record sprays; the "dust-bug" brushes that come attached to cartridges; the reason some records seem to be more static-prone than others; and the ways in which cartridge/tonearm choice and alignment can effect the annoyance factor of record noise (they can, apparently). I don't have firm responses to any of these (implied) questions, but I do have opinions, which will be forthcoming later on. In the meantime, let me give you several warnings:

(1) Don't rashly buy a record cleaner meant to be used while the record is playing if your turntable has limited torque, as many belt-drive units do. Dust-Bug-type devices are usually okay, but the ones that span an entire LP radius or which are driven off the turntable itself may make it impossible for your record player to get up to speed.

(2) Don't use the turntable's dust cover as a record cleaner. Laboratory tests have shown pretty conclusively that many dust covers provide an excellent path for acoustic feedback. Keep the cover removed or at least raised when you play a record. It is meant only to keep the turntable clean when it is *not* in use, and I don't know of any responsible turntable manufacturer who claims that it is otherwise.

(3) Experiment with anything meant to be applied to a record cautiously. All solvents and even distilled water are suspect with many, although they are beloved by some. When you feel you must evaluate a record-treating substance, dose one half (180 degrees) of a good record with the stuff and leave the other half untreated. At 33 1/3 rpm you should be able to detect the transition from the one side to the other (at 45 rpm things may happen too fast). And be prepared to buy a new record just in case your experiment doesn't work. ♦

It sounds an alarm. A built-in alarm that's set off any time—night or day—when severe weather threatens. The alarm is triggered by a signal from your local National Weather Service transmitter. After it sounds, a report on the danger and survival instructions come on.



When conditions are normal, the Storm Alarm picks up the weather station's continuous, up-to-the-minute forecasts.

Unlike ordinary weather radios, which the user must monitor, the Storm Alarm continually monitors itself. The alarm sounds full blast whether or not you have the volume turned up and are listening. You're warned even when sleeping. Crystal-controlled and switch-selectable.

Superior reception from as far out as 40-50 miles. Works on AC. Built-in back-up battery feature. 25" telescoping antenna. 2 1/4" speaker. Unit only 3" x 5" x 1 1/4".

With all these features, it's no wonder a leading electronics magazine called the Storm Alarm a "sensitive weather receiver and, for a relatively low price, an excellent disaster alarm."

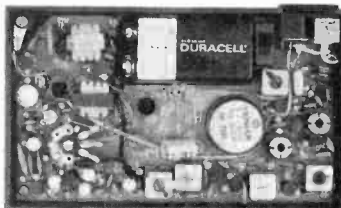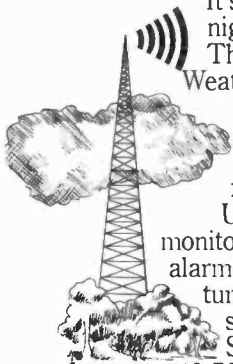Get the Storm Alarm. It's a foul and fair weather friend.



### STORM ALARM FROM WEATHERALERT

637 So. Dearborn, Chicago, IL 60605

Please send \_\_\_\_\_ (qty.) Storm Alarm units at \$37.50 each (includes shipping and handling). Enclosed is \$\_\_\_\_\_.

Check enclosed  BankAmericard  
 Master Charge  American Express

(Master Charge Bank No. \_\_\_\_\_)

Card No. \_\_\_\_\_

Expiration Date \_\_\_\_\_

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_

State \_\_\_\_\_ Zip \_\_\_\_\_

Signature \_\_\_\_\_

PE 5



© 1976 by WeatherAlert™, Chicago, Ill. 60605

Illinois residents add 5% sales tax. Alaska, Hawaii, Puerto Rico residents add \$2.50 per unit for special shipping and handling. Not available in Canada.

CIRCLE NO. 68 ON FREE INFORMATION CARD

# afs® / Kriket® CB speaker Sound and Safe!



**kamel™**  
Hump-mount speaker

**Speakers are our only business.  
They have to be better!**

Designed with security and superior sound in mind, the AFS® / KRIKET KAMEL KC-3085 hump-mount external speaker rests snugly on the transmission hump while driving. CB dials are readily visible.

CB transceiver mounts on speaker base forming single unit. No installation problems. For maximum security, unplug antenna and power leads, lift unit and place in trunk. No screws to unscrew. No hassle. No annoying rattles while driving. Solid!

"WORKING WALL" enclosure of cross laminated fiberboard deadens static and channel noise, eliminates voice distortion.

AFS makes having an expensive CB rig in your car or truck safe and worthwhile. Isn't it about time somebody did?

*Kriket Cares*

Available at CB dealers everywhere



**ACOUSTIC FIBER SOUND SYSTEMS, INC.**  
7999 KNUE ROAD, SUITE 116 INDIANAPOLIS, INDIANA 46250 (317) 842-0620

Canadian Distributor Muntz Canada Ltd. 1149 Pioneer Road Burlington Ontario, Canada (416) 639-5373

All AFS®/KRIKET® speakers are manufactured in the U.S.A. using American materials and craftsman.

Copyright 1976 Acoustic Fiber Sound Systems, Inc.



## Audio Reports

### HOW HEADPHONES ARE TESTED

**M**ANY PEOPLE are aware, at least in general terms, of some of the effects that room reflections and resonances have on the perceived frequency response of a loudspeaker. For example, the bass response varies widely as one moves about the room, usually being strongest at an opposite wall or corner or close to the woofer, and weakest in the center of the room. High frequencies, on the other hand, are progressively absorbed by room furnishings as one moves away from the speaker. High-frequency level can also change greatly at different angles between the listener and the speaker.

There are ways to circumvent these problems, and even put them to good use, when measuring loudspeaker performance. Most designers, though, choose to test a speaker in an anechoic chamber (a room whose interior surfaces absorb essentially all sound impinging on them, and reflect little or nothing to a microphone placed in the chamber). In this way, the characteristics of the speaker can be determined, free from interaction with its surroundings.

In the case of headphones, the audible results are closely related to the dimensions of the wearer's ear cavity, and the manner in which the earpieces fit the pinna or external ear. These are analogous to the relationship of the room to the loudspeaker. Although anechoic measurements might be possible with headphones, they would be of little practical value since the ear affects the frequency response through the entire audio range.

It is possible to measure headphone response directly on a human head by means of probe microphones inserted into the ear cavity. This is valuable for psychoacoustic and physiological studies, but clearly is of no use to someone wishing to evaluate a headphone. It would be convenient to have a "standard ear," on which any phone could be checked. Even if such an ear were not identical to any specific human ear, it would provide a test bed on which to make comparative headphone measurements.

There are standard artificial ears—several different types, in fact. Some have been shaped to correspond roughly to the external human ear, but others merely present a flat surface to the headphone's ear cushion, with a cavity drilled in the center to expose the end of a calibrated capacitor microphone that simulates the eardrum. This is the basic configuration of the ANSI standard headphone coupler, which we use in slightly modified form for our headphone tests.

The original purpose of the standard coupler was to measure headphone response in the speech frequency range (300 to 5000 Hz). It was recognized that resonances in the coupler cavity would produce severe response changes at higher frequencies. The standard coupler has a 6-cc cavity, simulating the volume of a typical ear. The shape of this cavity is subject to slight modification to suit the particular type of headphone being tested.

Experiments made by Koss Electronics indicated that a good correlation between measured frequency response and the subjective headphone response would be achieved with a slight modification of the shape of the coupler cavity (keeping its volume at the standard 6 cc). The Koss coupler, which we use for our tests, conforms to the 1949 ANSI standard, except for the details of the cavity shape. It is a flat plate coupler into which our test microphone fits snugly. When the headphones are mounted on the coupler stand, the normal tension of the headband provides sealing around the ear cushion of the measured earpiece, equivalent to what would exist with normal wearing.

Although the Koss coupler makes it possible to measure headphone frequency response through the full audible range, it has a few intrinsic high-frequency resonances that make measurements less reliable above 10,000 Hz. Our coupler has been calibrated by Koss, with the aid of a calibrated set of its ESP-9 electrostatic phones. This enables us to check the performance of the test set-up and also provides an absolute calibration of sound pressure level (SPL), since the output of the ESP-9 phones is known at a particular frequency and drive level.

To measure the frequency response of a headphone, it is placed on the coupler and driven from an amplifier whose input is derived from our General Radio frequency-response plotter. The microphone output goes directly to the graphic level recorder input, and the chart reads out directly in dB on the SPL scale (referred to 0.0002 dyne/cm<sup>2</sup>). The voltage across the phone is set to a value recommended by the manufacturer (usually in the range of 1 to 3 volts) and a swept response measurement is made using a fast chart speed (25 inches per minute) and moderate pen damping (pen speed, 3 inches per second) to smooth out small variations caused by the coupler.

Distortion is measured at 1000 Hz as a function of applied voltage. The microphone output goes direct-





**Some guys rely on their 2-way radios more than others.**

Fighting a fire takes tough men. And tough equipment. Equipment like the Motorola® 2-way radios carried by so many fire fighters.

Today you can own a 2-way radio with many of the engineering principles that go into Motorola professional radios.

You can own a Motorola CB.

Features like gain control, audio compression, and noise limiting are built in, fully automatic.

So a Motorola CB is exceptionally simple to operate. Yet offers outstanding talk/listen performance.

A top-fire 3½-inch professional-quality speaker produces an audio fidelity that must be heard to be fully appreciated.

A power mic that doesn't require batteries, that doesn't cost extra, is standard equipment.

When you've made 2-way radios as long as Motorola, the result is a radio with a difference you can hear.

Whether you're fighting a fire. Or fighting the traffic home.



## Motorola CB


From the voice of experience in 2-way radio.

To find the dealer nearest you, write: Customer Relations Manager, Motorola Inc., Automotive Products Division, 333 Northwest Ave., Northlake, Illinois 60164. Motorola is a registered trademark of Motorola Inc.

CIRCLE NO. 38 ON FREE INFORMATION CARD



# You gotta shop around.

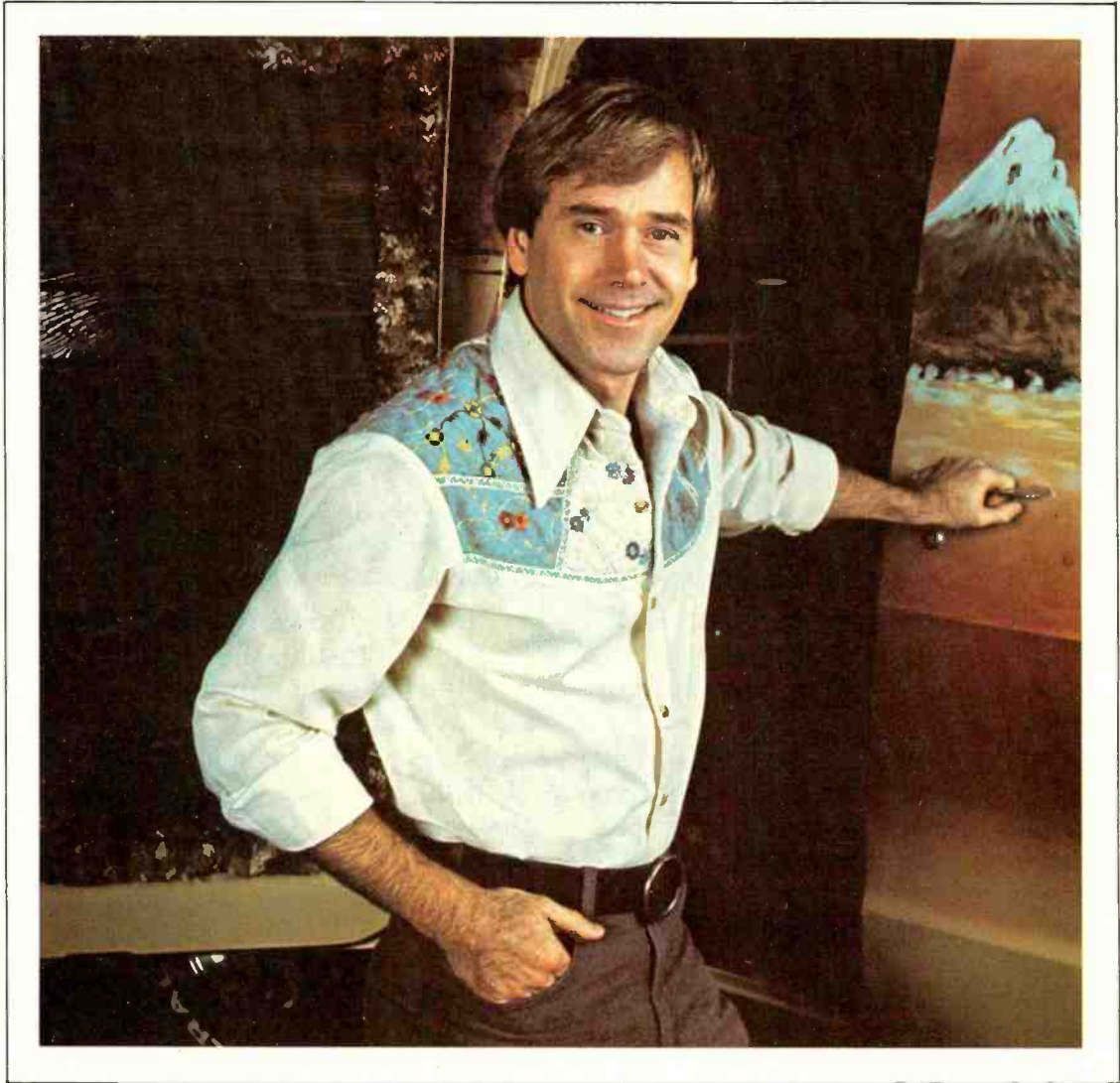

**When you do, you'll probably pick CIE.  
You can't afford to settle for  
less when it comes to something like  
electronics training that could  
affect your whole life.**

**W**hen you shop around for tires, you look for a bargain. After all, if it's the same brand, better price — why not save money?

Education's different. There's no such thing as "same brand." No two schools are alike. And, once you've made your choice, the training you get stays with you for the rest of your life.

So, shop around for your training. Not for the bargain. For the best. Thorough, professional training to help give you pride and confidence.

\* \* \*

If you talked to some of our graduates, chances are you'd find a lot of them shopped around for their training. They pretty much knew what was available. And they picked CIE as number one.

### Why you should shop around yourself.

We hope you'll shop around. Because, frankly, CIE isn't for everyone.

There are other options for the hobbyist. If you're the ambitious type — with serious career goals in electronics — take a close look at what we've planned for you at CIE.

### What you should look for first.

Part of what makes electronics so interesting is it's based on scientific discoveries — on ideas! So the first thing to look for is a program that starts with ideas and builds on them!

That's what happens with CIE's Auto-Programmed® Lessons. Each lesson takes one or two principles and helps you master them — before you start using them!

### How practical is the training?

This is the next big important question. After all, your career will be built on what you can do — and on how well you do it.

Here are ways some of CIE's troubleshooting programs help you get your "hands-on" training...

**With CIE's Experimental Electronics Laboratory...**




you learn and review the basics — perform dozens of experiments. Plus, you use a 3-in-1 precision Multimeter to learn testing, checking, analyzing!



**When you build your own 5 MHz Triggered-Sweep, Solid-State Oscilloscope** you take your first real professional step. You use it as a doctor uses an X-ray machine — to "read" waveform patterns... lock them in... study, understand and interpret them!

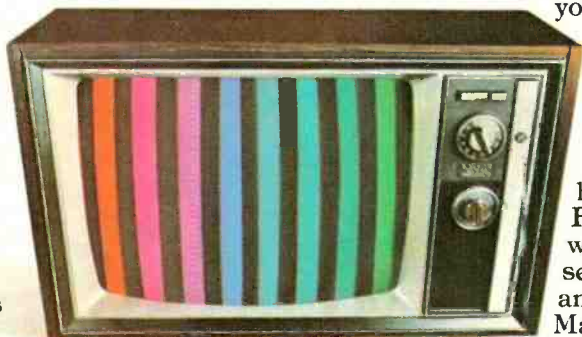**When you get your Zenith 19-inch Diagonal Solid-State Color TV** you



Pattern simulated.

apply your new skills to some real on-the-job-type troubleshooting! You learn to trace signal flow... locate malfunctions... restore perfect operating standards — just as with any sophisticated electronics equipment!



**When you work with a completely Solid-State Color Bar Generator** — actually a TV signal transmitter — you study up to ten different patterns on your TV screen... explore digital logic circuits... observe the action of a crystal-controlled oscillator!

Of course, CIE offers a more advanced training program, too. But the main point is

simply this:

All this training takes effort. But you'll enjoy it. And it's a real plus for a troubleshooting career!

### Do you prepare for your FCC License?

Avoid regrets later. Check this out before you enroll in any program.

For some troubleshooting jobs, you must have your FCC License. For others, employers often consider it a mark in your favor. Either way, it's government-certified proof of specific knowledge and skills!

More than half of CIE's courses prepare you for the government-administered FCC License exam. In continuing surveys, nearly 4 out of 5 CIE graduates who take the exam get their Licenses!

### Shop around... but send for CIE's free school catalog first!

Mail the card. If it's gone, cut out and mail the coupon. If you prefer to write, mention the name and date of this magazine. We'll send you a copy of CIE's FREE school catalog — plus a complete package of independent home study information! For your convenience, we'll try to have a representative contact you to answer your questions. Mail the card or coupon — or write: CIE, 1776 East 17th St., Cleveland, OH 44114.

## CIE Cleveland Institute of Electronics, Inc.

1776 East 17th Street, Cleveland, Ohio 44114  
Accredited Member National Home Study Council

**YES...** I'm shopping around for the **right** kind of career training in electronics troubleshooting — and CIE sounds well worth looking into. Please send me my FREE CIE school catalog — including details about troubleshooting courses — plus my FREE package of home study information! PE-34

Print Name \_\_\_\_\_

Address \_\_\_\_\_ Apt. \_\_\_\_\_

City \_\_\_\_\_

State \_\_\_\_\_ Zip \_\_\_\_\_

Age \_\_\_\_\_ Phone \_\_\_\_\_

(area code)

Check box for G.I. Bill information:

Veteran  Active Duty

**Mail today!**

ly to a Hewlett-Packard 3580A spectrum analyzer, on which all significant harmonic amplitudes can be measured. Impedance is measured by driving the phones through a fairly high resistance and plotting the voltage across them on the chart recorder. The resistance axis of the recorder chart is calibrated against a precision standard decade resistor, substituted for the headphones.

Interpreting the frequency-response curve of a headphone measured in this way is not as easy as we would like it to be. Sometimes the response is relatively flat over most of the audio range, and this is always associated with a phone which has a smooth, natural sound. Sometimes there will be one or more huge peaks (as great as 30 dB in amplitude) in the upper midrange. Such a phone always sounds harsh and unnaturally colored. The difficulty is in the intermediate cases, which comprise the majority of

phones. Their response curves often have rather sizable peaks or holes in the range of a few kilohertz. These cannot easily be separated into true headphone response and the coupler response. Many of these phones sound excellent, virtually indistinguishable from some which test much better, while others that are seemingly not too different sound mediocre.

Thus, as with speakers, the only way to buy a headphone is to listen for yourself. With headphones, you have the advantage that the listening room is not a part of the equation, so the phones will sound the same in your home as at the dealer's showroom. Since the physical "fit" of a headphone can be as important as its sound, a personal selection is highly desirable. Test reports can be a guide to those phones that are worthy of your consideration, but response curves should never take priority over the judgment of your own ears.



### SENNHEISER MODEL HDI 434 INFRARED HEADPHONES

*Cordless headphones provide unfettered personal listening.*



8"W × 3.15"D × 0.7"H (20.3 × 8 × 1.8 cm), and the headphones weigh 13.5 oz (420 g) including battery. Prices: \$209 for the Model HDI 434 phones and \$184 for the SI 434 infrared transmitter.

**General Description.** The earcups of the headphones house magnetic open-air drivers. The earcups are designed to provide little or no isolation from external sounds. The semirigid headband has a padded adjustable inner band that rests on the user's head.

On the rear of the right earcup are a pair of slide-type controls for separately adjusting the volume levels in the two earcups. A slide-type switch allows selection of normal stereo listening, channel-A mono through both earcups, or channel-B mono through both earcups. A separate switch controls power to the headphones from its own 9-volt battery. The left earcup has no controls; it houses the battery that powers the phones. A clear plastic on the front edge of the right earcup protects an infrared sensor that picks up the invisible beam radiated by the transmitter.

Across the front panel of the transmitter is a row of 12 light-emitting diodes (LED's) that generate the invisible infrared carrier beam. A separate LED, located at the far left of the panel, is used as the power-on indicator for the line-powered transmitter. The pushbutton power switch is located at the far right of the front panel.



With these innovative, cordless, stereo headphones, the listener can be free

at last from the tether that attached him to the headphone jack. In the past, most attempts at designing cordless hi-fi headphones failed to meet the high quality sound needs of the home listener. The various cordless approaches tried were plagued by poor sound quality, high noise levels, and inability to handle stereo program material. The new Model HDI 434 infrared stereo

phones from Sennheiser have solved most of the technical problems.

The Model HDI 434 is actually a headphone "system" that consists of rather large (but lightweight) phones and a separate infrared transmitting unit. No physical connection is needed between the phones and transmitter, nor are there antennas or other appendages on the phones themselves. The only link between the phones and the transmitter is an invisible infrared beam. The transmitter plugs into the headphone jack of any amplifier, tuner, or tape deck.

The infrared transmitter measures

You may have noticed that few turntable manufacturers call your attention to the critical role of the tonearm in record playback. Dual is an exception.

Whatever the shape, materials, or mechanics of a tonearm, the goal is always the same: to maintain the cartridge in the correct geometric relationship to the groove, and to permit the stylus to follow the contours of the groove walls freely and accurately. Whenever the stylus cannot follow the groove undulations, it will gouge its own way. And as we have frequently reminded you, there is no way to repair a damaged record. Every tonearm designer should consider

# Why we want you to know more about tonearms. And why others may not.


geometry, mass, balance, resonance, bearing friction, and the accuracy and stability of settings for stylus force and anti-skating. However, despite the simple fact that the shortest distance between two points is a straight line, some designers are more concerned with appearance. Hence, the curved tonearm, whose deviations between pivot and stylus simply add mass, reduce rigidity and increase the likelihood of resonance.

Dual engineers have always designed for optimum performance. The essential differences in approach and results are indicated below. You might keep all this in mind when you are considering your next turntable. Chances are you'll want it to be a Dual.




**United Audio Products, 120 So. Columbus Ave. Mt. Vernon, N.Y. 10553**  
Exclusive U.S. Distribution Agency for Dual

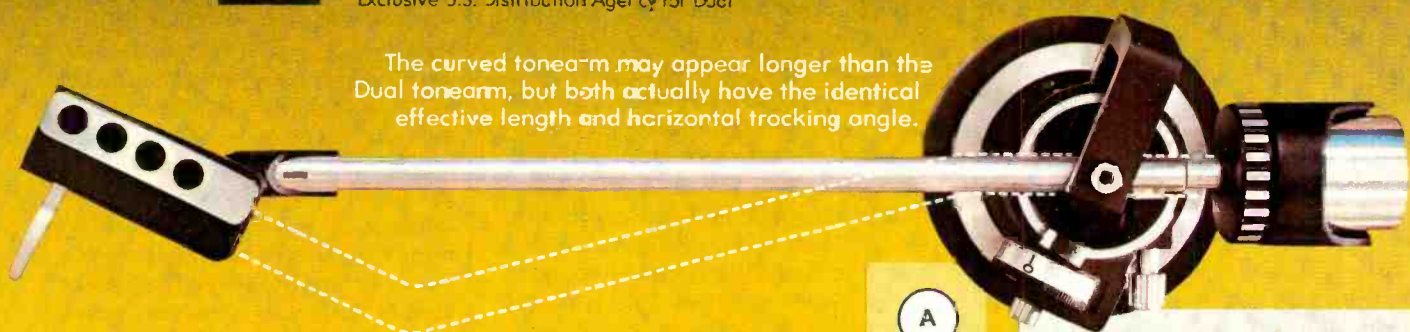The curved tonearm may appear longer than the Dual tonearm, but both actually have the identical effective length and horizontal tracking angle.



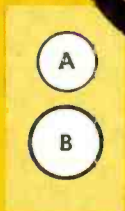Actual size of Dual tube (A) and typical curved tonearm (B). For the same effective length, straight Dual tonearm has lower mass and resonance, yet greater rigidity.



**Dual 1249.** Single-play/multi-play. Belt-drive. Fully automatic start and stop, plus continuous repeat. Made Selector parallels tonearm to record in single-play; 6% pitch control; illuminated strobe; cue control; viscous-damped in both directions; multi-calibrated anti-skating. Less than \$230.

**Dual-510.** Similar except semi-automatic. Lect-in groove sensor. Tonearm lifts automatically at end of play and motor shuts off. Less than \$200.

**Dual 502.** Semi-automatic. Less sensor strobe and pitch control. Less than \$160.




Gimbal-mounted Dual tonearms pivot horizontally and vertically on identical sets of pivot points and high-precision low-friction bearings. Bearing friction: vertical, <math>\leq 0.007</math> gram; horizontal, <math>\leq 0.015</math> gram.

Stylus force, applied by long coiled spring around vertical pivot, remains perpendicular to record even if turntable is not level.

Specifications (DIN B1; Rumble, >66dB; Wow and Flutter, <math>\leq \pm 0.05\%</math>

CIRCLE NO. 4 ON FREE INFORMATION CARD

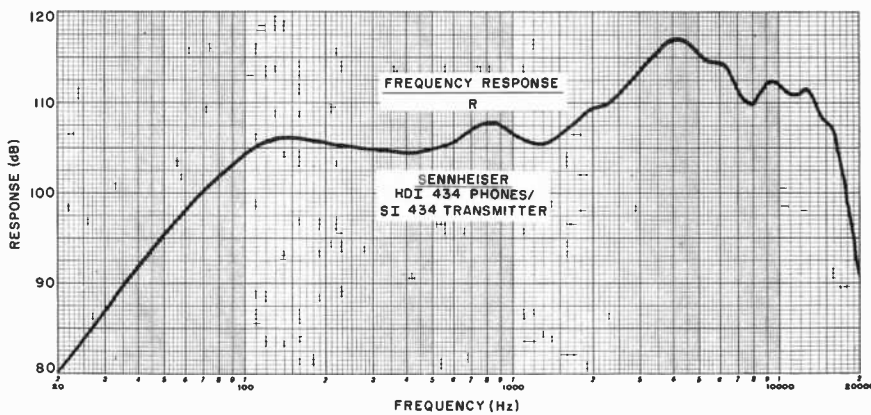

Overall frequency response of headphones and transmitter.

In operation, the transmitter is placed in a location where its beam will cover the preferred area of the listening room. Then, with the headphone worn in the usual manner, the stereo program is heard just as with conventional headphones. The big difference here is that the listening volume is set by the slide controls on the right earcup.

It is important to have a sufficient, but not excessive, modulation level driving the transmitter. This is accomplished by turning up the volume control of the audio component that drives the transmitter until the glowing LED on the latter suddenly begins to flash, and then backing off slightly until the flashing just ceases. Thereafter all volume level adjustments are made by operating the controls on the phones.

The stereo program is carried over the infrared beam on two subcarrier frequencies—95 KHz for the left channel and 250 kHz for the right channel. The specifications call for a 30-kHz deviation at 1-volt input to the transmitter and 50-kHz deviation at the 1.5-volt maximum allowable input. The headphones contain two FM discriminators that are tuned to the subcarrier frequencies and are capable of demodulating signals with deviations as great as 50 kHz.

The specifications for the phones call for a frequency response of 20 to 20,000 Hz (no tolerance given) with less than 1% THD at 1000 Hz (at an unspecified level) and a maximum output capability of 108 dB SPL. The S/N ratio is rated at approximately 60 dB, and estimated operating life of the standard 9-volt battery is 100 hours.

**Laboratory Measurements.** We tested the acoustic performance of the phones on a modified ANSI headphone coupler in the usual manner. The transmitter was placed a few feet from the

headset and driven directly from our General Radio response plotter. Having determined that a 1-volt drive level to the transmitter resulted in spurious "birdies" at frequencies beyond 12,000 Hz, we reduced the drive to 0.5 volt for the response measurement.

The midrange response was very flat, varying only  $\pm 1.5$  dB from 100 to 1700 Hz. The output rose at higher frequencies and was at or above the midrange level all the way up to our measurement limit of about 16,000 Hz. The low-frequency output, as is usually the case with open-air headphones, dropped off at a 12 dB/octave rate below 100 Hz. The midrange SPL was about 105 dB, or 111 dB at the recommended maximum operating level of 1 volt.

The overload indicator glowed at a 1.15-volt input with frequencies of 1000 Hz or lower. Overload occurred at smaller signal voltages at high frequencies, reducing to 0.43 volt at 10,000 Hz and 0.32 volt at 15,000 Hz. The distortion of the acoustic output of the headphone was less than 1% for drive levels up to about 1 volt at 1000 Hz. With the phone's volume controls set to maximum, the distortion increased abruptly above about 1.2 volts. This was apparently due in part to overdriving the headphone amplifiers, since reducing the setting of the volume controls by 10 dB resulted in a more gradual increase in distortion, to 2% at 1.8 volts and 3.4% at 3 volts. Distortion is not a problem when using the phones, since it became appreciable only when the SPL exceeded a very loud 110 dB.

The S/N was measured relative to the output at 1000 Hz with a drive level of 1.15 volts. Without weighting, the S/N was 40 dB, and with CCIR weighting it was 54 dB. The stereo channel separation reduced with increasing frequency, from 40 dB at 100 Hz to 21 dB at 3000

Hz. It remained in the 18-to-21-dB range from 3000 to 15,000 Hz. The electrical impedance of the transmitter input was 100,000 ohms up to about 1000 Hz. It decreased to between 13,000 and 25,000 ohms in the 10,000-to-20,000-Hz range.

**User Comment.** Considered only as stereo headphones, we would rate these on a par with other Sennheiser phones we have tested. They are excellent, producing a clean, wide-range, transparent sound that could not be distinguished from conventional phones.

The listening volume was most satisfactory, and we heard no background hiss or other noise that was not in the program material. In other words, the

**Editor's Note:** The listening experience with these infrared phones may differ according to the environment and the placement of the transmitter. For example, using the same new Sennheiser phones in a large (25 ft  $\times$  19 ft  $\times$  8 ft) wood-paneled listening room in the editor's home, a person standing in front of the transmitter or the headphone wearer did *not* change the sound quality received by the phones when the infrared transmitter was positioned near the corner of the room (a position also tried during Hirsch-Houck tests). Furthermore, in this position, headphone reception was not at all marred by noise when turning a head or even one's back so that the phone receiver's single sensor was facing away from the transmitter. Nor was there any change in sound when a cigarette lighter was flicked, a pipe lighted, or pipe smoke blown by the headphone user. Moreover, the signal-to-noise ratio did not even exhibit an apparent change when the user walked into a hallway off the listening room so that he was *behind* the transmitter. Turning one's head in this area, however, did cause a high level of noise to occur, as did standing under a strong spotlight.

It should be mentioned, as a footnote, that this listening room has angled ceilings emanating from four-foot-high paneled walls and rising to a flat plasterboard ceiling surface. In contrast, Hirsch-Houck's ceiling is constructed with acoustic panels. These differences evidently account for the contrary results in infrared reception. It's obvious that, in the editor's home, the environment enhanced reflections of the infrared beams. As a consequence, the performance of these infrared stereo phones was superb with no reservations whatsoever.

# Shakespeare's Double Trucker™ Antenna. Professional. Co-phased. And no strong two ways without it.

Ask a trucker about the best antenna team for your CB operations. He knows the Citizens Band. And he knows the performance of Shakespeare's Double Trucker Antenna. Because the men who ride for a living can't settle for anything small-time in their signal power.

Those two solid fiberglass whips stand firmly upright for maximum range and clarity. Perfectly co-phased through Shakespeare's exclusive Diplexer phasing harness. Pre-tested and pre-tuned for the 40 channel band. Delivering the kind of performance true Knights of the Road depend on.

*Shakespeare*

**The best antenna going.  
And coming.**

Shakespeare's Double Trucker Antenna, Style 464-1/ Installs quickly and easily on any horizontal bar up to 3/4". Comes complete with corrosion proof mirror mount, cable and all connectors. Under \$35.

S/N of the infrared system was at least as good as that of the FM and commercial phonograph records we used for program sources.

The transmitter evidently radiates a fan-shaped pattern into the room, which does not reflect from room boundaries to any significant extent (unlike ultrasonic remote-control devices, whose output can be "bounced" off a wall to reach around a corner). This means that the phones must be in a direct line of sight with the transmitter, although distance does not seem to be a problem. (We covered 30 feet or more without difficulty.) However, if someone walks between the listener and the transmitter, the sig-

nal drops markedly or disappears altogether, delivering a burst of noise like that of an unmuted FM tuner when the signal drops out. Interestingly, a crackling sound occurred when the listener flicked a flint-type lighter, followed by noise when the lighter's flame appeared.

If one turns away from the transmitter, or even to the side so that the left ear is closest to the transmitter, however, a loss of signal is likely to occur. We found this in some ways to be restrictive, although one quickly adjusts to the minor limitation. This occurs because the receiver sensor is on the front of the right earpiece. The answer, it would seem, would be to either place a sensor on

each earpiece or mount a single one at the top of the rigid headband to prevent shadowing of the receiver as the wearer moves or turns.

Aside from the above, we were highly impressed with the concept used by these phones, as well as its execution. The system does a remarkably fine job without excessive weight or bulk. True, they are among the most expensive headphones you can buy, but they also do things that no other phones can. One simply has to experience the wonderful feeling of not being tied down to a headphone's umbilical cord to appreciate it. And, the sound is truly superb.

CIRCLE NO. 101 ON FREE INFORMATION CARD

## TEAC MODEL PC-10 CASSETTE RECORDER

*Portable stereo recorder has performance characteristics of home component types.*



The Model PC-10 portable cassette recorder is part of Teac's new "Esoteric" line. It is one

of the new breed of true high-fidelity portable stereo recorders with all the features and performance quality expected of deluxe home cassette decks. It comes with a separate ac power supply for line operation and can be operated in the field from six D cells that fit within its case.

The recorder measures 11½" W × 9½" D × 3½" H (29.2 × 24.1 × 8.9 cm) and weighs 11 lb (5 kg). Nationally advertised value is approximately \$500.

**General Description.** The recorder features a direct-drive dc capstan motor that is servo-controlled through a phase-locked loop (PLL). This eliminates belts and flywheels; it starts up and brings the transport to final operating speed rapidly. (There is a separate dc motor for the tape hubs.) The PLL motor drive makes the recorder's operating speed relatively

independent of supply voltage and temperature, the latter specified over a range of 32° to 140° F (0° to 60° C).

The cassette well is on what would be the top of the recorder when it is placed on a shelf or table. When the recorder is carried over a shoulder via its built-on strap, the cassette well is on the side for convenient loading and unloading. A small lever opens the cassette cover, while a firmer push on the lever ejects the cassette. Located near the cassette well is a pushbutton-resettable index counter.

The control panel is dominated by two large VU meters, whose scales are labelled with the standard Dolby level mark at the +3 indexes. Between the meters is a PEAK LEVEL LED that flashes when momentary peaks reach +6 dB. The meters and PEAK LEVEL indicator function in playback as well as in the record mode.

The transport mechanism is controlled by two slide-type levers. The upper lever has STOP and PLAY positions, and next to it is the REC button that must

be pressed before going to PLAY if a recording is to be made. The second lever has three positions. The left position is for rewind, center position for off, and right position for fast forward tape motion. Neither lever can be moved unless the other lever is in its stop (center) position. A PAUSE button is located just below the REC button. A red indicator comes on for the record mode.

The REC level controls for the left and right channels are concentrically ganged together. The lowest quarter of their adjustment range is marked in white as a warning that input signal levels are excessive if the controls must be set so low. Otherwise, the rest of the scales are in red for the right channel and green for the left channel. A small button below the level controls can be pressed to momentarily illuminate the VU meters or pressed and twisted to lock on the illumination. A similar button connects the right-channel meter to give an indication of battery condition.

Separate BIAS and EQ (equalization) switches are provided for setting the operating conditions to suit most tape formulations. The bias levels roughly correspond to those used with low-noise ferric-oxide and CrO<sub>2</sub> (or the chrome equivalent) tapes. The EQ characteristics conform to the standard 120- and 70-μs curves for these tapes. (The instruction booklet that comes with the recorder lists a number of suitable tapes and recommended switch settings.) The DOLBY NR switch turns on and off the Dolby B noise-reduction system, and the LIMITER switch turns on and off a peak limiter that takes effect at levels over +3 dB.

The positions on the MIC ATT switch are labelled 0, 15, and 30 (dB). With this switch properly set, it is possible to record very high sound levels without



# There's more to Realistic<sup>®</sup> 40-channel CB than just 17 added channels...



## there's 17 years of know-how!

With so many new and unproven brands on the CB bandwagon, the reasons for buying Realistic are clearer than ever. Seventeen years' experience and sales of a million sets annually have shown us what it takes to be a leader:

Intelligent, reliable engineering. Easy-to-find sales and service — to the tune of 4800 Radio Shacks in the USA alone. And low prices that are possible only because Radio Shack is a do-it-yourself company, from factory to warehouse to sales counter.

Take a look at our new high-performance mobile transceiver, the TRC-467. Advanced phase-lock loop circuitry generates all 40 channels with an electronic precision far beyond the limits of the multi-crystal sets.

Three ceramic IF filters improve the selectivity for a whopping 80 dB of adjacent-channel rejection. An automatic noise limiter cuts pulse interference, and it's switchable for maximum clarity on stronger signals.

Illuminated signal strength/RF output meter and channel selector, LED modulation indicator — conveniences that make your CB easier and more fun to use. With dynamic plug-in microphone, adjustable mobile bracket, and power cables for any vehicle with 12 VDC positive or negative ground.

Come in today and see the TRC-467. Designed, manufactured and sold only by "the" CB experts — Radio Shack. Just 119.95\*.




These two credit cards honored at most Radio Shacks.  
\*Prices may vary at individual stores and dealers.


SOLD ONLY WHERE YOU SEE THIS SIGN:
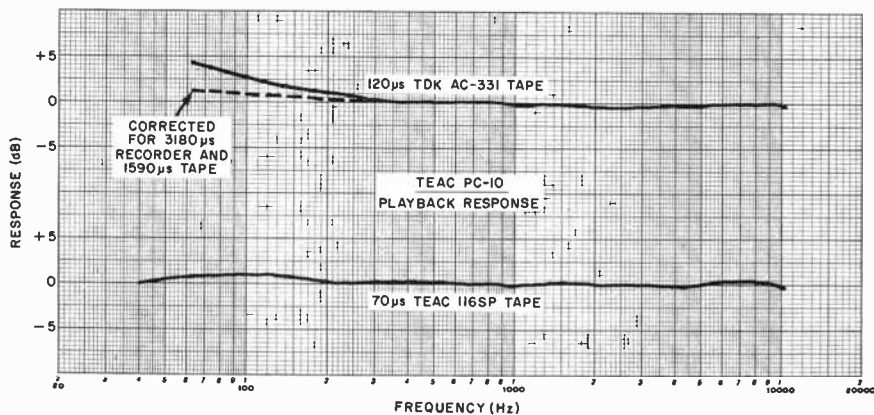
# Radio Shack<sup>®</sup>


A TANDY COMPANY • FORT WORTH, TEXAS 76107  
OVER 5000 LOCATIONS IN NINE COUNTRIES



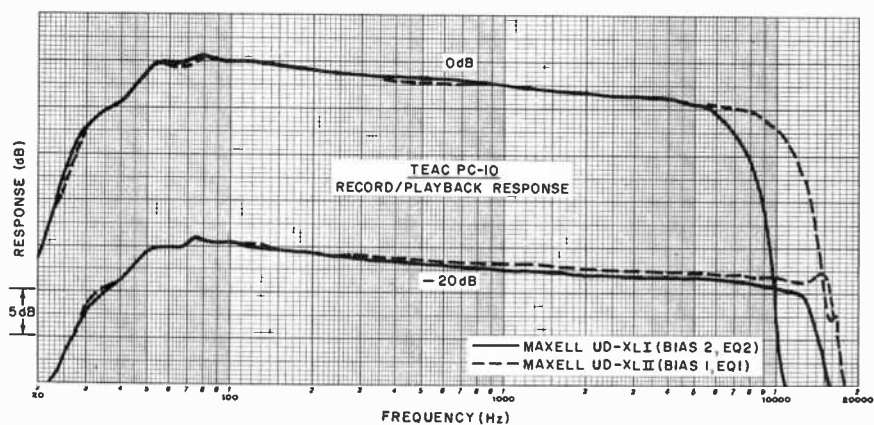Playback frequency response tests using two different types of tape.



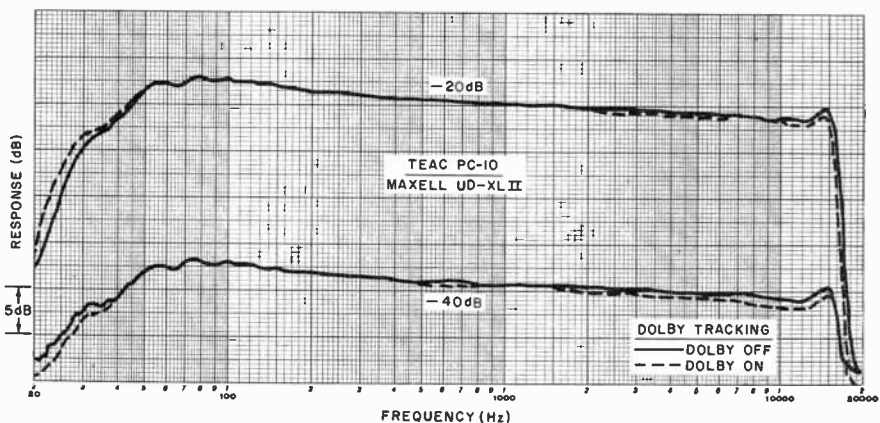Overall record/playback frequency responses at 0 dB and -20 dB.



Response curves showing Dolby tracking error at two levels.

overloading the microphone preamplifier stages.

Set into the right side of the recorder is a well that contains the various input and output connectors, a slide switch for selecting either the microphone or line inputs, playback output jacks, a headphone jack, and a small volume control for the built-in speaker. There is also a jack for connecting the external ac power supply to the recorder.

The published performance specifications of the recorder are similar to those for a better-quality line-operated cassette deck. The recorder can be oper-

ated continuously for approximately two hours with six fresh D cells installed.

**Laboratory Measurement.** We used TDK AC-331 tape with 120  $\mu$ s equalization and Teac 116SP tape with 70  $\mu$ s equalization during our playback frequency response tests. In both cases, the response was flat within  $\pm 0.5$  dB from 150 to 10,000 Hz, with a maximum departure from flatness of only 1 dB at the lower frequencies (which extended, respectively, to 63 and 40 Hz with the two tapes).

Several types of tapes were used to

measure the overall record/playback frequency response. The curves obtained with Maxell's ferric-oxide UD-XL I and cobalt-treated ferric-oxide UD-XL II (designed to be used with "chrome" bias and equalization) tapes were typical of the recorder's performance with other high-quality tapes. The frequency response was a nearly straight line that sloped downward with increasing frequency. The total variation was  $\pm 3$  dB from 35 to 12,500 Hz using UD-XL I tape and from 35 to 15,500 Hz with UD-XL II tape. The principal difference between the two tapes was not in their frequency responses but in their high-frequency saturation characteristics. When the measurement was made at 0 dB instead of the usual -20 dB, the UD-XL II tape delivered a much better high-frequency response.

The tracking error of the Dolby circuits between the recording and playback conditions (they are supposed to be exactly balanced at all levels and frequencies) was excellent. At levels of -20 and -40 dB, there was no more than 1 dB of change in response at any frequency when using the Dolby system.

A line input of 62 mV or a microphone input of 0.22 mV was needed for a 0-dB recording level. The latter increased to 1.6 and 8 mV when the MIC ATT switch was set to its 15- and 30-dB positions, respectively. The microphone overload levels were 82, 550, and 1550 mV in the three positions of the MIC ATT switch. The playback output from a 0-dB recording level varied somewhat with the tape used. The premium ferric-oxide tapes—Maxell UD-XL II and TDK SA—gave about a 0.7-to-0.8-volt output, which roughly corresponds to the rated 0.775-volt output. However, the UD-XL I tape yielded a higher output at 0.93 volt.

The playback distortion from a 0-dB recording at 1000 Hz was 0.63% with UD-XL I and 0.8% with UD-XL II tapes. The 3% THD level was reached with respective recording levels of +6.5 and +5 dB. The PEAK indicator flashed at +5 dB. The recording limiter had no effect at 0-dB or lower levels, but it made a worthwhile reduction in playback distortion when the recording levels were well off-scale on the meters. For example, at +7 dB, with UD-XL II tape, the distortion reduced from 5.3% to 2.1% with the limiter switched in. At +10 dB, the distortion was a still-tolerable 3.5%, but at 20 dB it reached an unacceptable 10%. It is clear that the presence of the limiter is not a justification for entirely ignoring recording levels.

We were pleased to note that the VU

meters were correctly named, at least with respect to their performance. Their ballistics matched the specifications for professional VU meters, with a 0.3-second, 1000-Hz tone burst occurring once per second to give exactly the same meter indication as a continuous tone of the same level.

With UD-XL I tape, the S/N referred to the 3% THD level was 56.5 dB unweighted, 60.5 dB with IEC A weighting, and 56.5 dB with CCIR/ARM weighting (the type preferred by Dolby Laboratories). With the Dolby system switched in, these figures improved to 61, 68, and 66.5 dB. With UD-XL II tape, the S/N was not quite as good, yielding readings of 55 dB unweighted, 59 dB IEC A weighted, and 56 dB CCIR weighted. The Dolby system improved these figures to 56.5, 65.5, and 66 dB. The noise level through the microphone inputs was 14.5 dB greater at full gain but much less with normal settings of the recording gain. Playing a 200-nanowebber/meter standard Dolby level tape provided meter readings within 0.5 dB of the Dolby calibration marks on the meters.

The measured wow was the 0.01% residual of our test equipment and tapes. Unweighted rms and flutter measured 0.145% in both the playback and combined record/playback tests. These figures cannot be compared to Teac's own rating, which was based on a weighted measurement. The transport operated smoothly and reliably and moved a C60 cassette from end to end in about 84 seconds. The crosstalk between stereo channels was -45 dB at 1000 Hz, measured with a TDK AC-352 test tape. All these tests were made using an ac power supply.

**User Comment.** The overall performance of this recorder is squarely in the class of the better component-type cassette decks used in home hi-fi systems. In fact, with respect to distortion and noise levels, almost perfect playback equalization, and virtually ideal Dolby tracking, this recorder was superior to all but a handful of the component cassette decks we have tested.


Used in a fixed home hi-fi system, the recorder's sound quality and handling convenience left little to be desired. Our only criticism of its operation concerns the eject lever. With the recorder slung over a shoulder, it is very easy to brush against the lever and inadvertently open the cassette door. Otherwise, this fine little recorder offers the best of portable and fixed operation, albeit at a price.

CIRCLE NO. 102 ON FREE INFORMATION CARD
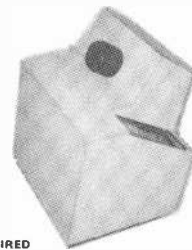
## BUILD THE LIFESCREEN® BIG SCREEN COLOR TELEVISION

THE CREATION OF BIG SCREEN TELEVISION OFFERS A NEW DIMENSION IN TELEVISION VIEWING

- Sporting Events Are An Experience As Exciting As Being There!
- Movies Are Seen The Way They Were Meant To Be Seen!
- Pong And Other Video Games Are More Exciting Than Ever!
- Can Be Used With Video Tape Playback Equipment!



NO ELECTRONIC SKILLS REQUIRED

The LIFESCREEN® TV was designed for the Do-It-Yourself enthusiast who wishes to have the enjoyment and excitement of a professional Big Screen TV but refuses to pay the \$1500 to \$4000 and higher prices that most major manufacturers charge for this luxury.

### HOW TO ORDER COMPONENTS


The LIFESCREEN® Lens and Front Surface mirror can be ordered from Extron.

The Kodak Ektalite Screen can be purchased from a local Kodak retailer for about \$100.

The Sharp 13" Model 13A21 Color TV can be purchased from a local Sharp retailer for about \$300.

Extron can supply you with the screen or the television for the prices quoted above.

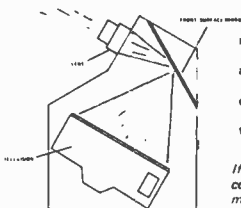If you now own a portable color TV that has a bright, color pure picture, IT MAY BE ACCEPTABLE with minor alterations. DETAILS WITH PLANS.



HOW THE LIFESCREEN® PROJECTION SYSTEM WORKS

START BY ORDERING YOUR PLANS TODAY!

Don't be discouraged because this is a kit! This system when built according to instructions is even better than the projection TV's on the market today.

Please Rush Me one complete set of LIFESCREEN® Plans @ \$9.00

Please also send me the items checked below.

LIFESCREEN® Lens @ \$150.00

LIFESCREEN® Front Surface Mirror @ \$20.00

All prices F. O. B. Factory

Name \_\_\_\_\_ Card Name \_\_\_\_\_

Address \_\_\_\_\_ Card Number \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_ Expiration Date \_\_\_\_\_

Enclosed

Charge to my credit card

**Extron LIFESCREEN® Projection System** 8831 Sunset Blvd.  
W. Hollywood, Calif 90069

**8831 Sunset Blvd.**  
W. Hollywood, Calif 90069

**8831 Sunset Blvd.**  
W. Hollywood, Calif 90069

CIRCLE NO. 25 ON FREE INFORMATION CARD

# BYTE

The Small Systems Journal

## Isn't it time you had your own personal computer?

Read BYTE, the leading national publication covering the fantastic new field of personal computer applications. Today, large scale integration has made it possible for the individual to enjoy the unique benefits of a general purpose computing system. Now, an entire micro industry markets microcomputer related items, products that range from computer system kits to peripherals, software and literature on the subject. But where should you go for all the details about your personal involvement in computer technology?

Read BYTE, the Small Systems Journal devoted exclusively to microcomputer systems. Every issue a monthly compendium of lively articles by professionals, computer scientists, and serious amateurs.

Fill in subscription coupon today, or phone your request directly — call 603/924-7217 and ask for subscription department. Read your first copy of BYTE, if it's everything you expected, honor our invoice. If it isn't, write 'CANCEL' across invoice and mail it back. You won't be billed and the first issue is yours.

Allow 4 to 6 weeks for processing.

**BYTE** 70 Main St., Peterborough, N.H. 03458 07A5

Please enter my subscription to BYTE...

\$12 One Year     \$22 Two Years     \$30 Three Years

Bill me     Check Enclosed

Bill BankAmericard     Bill Master Charge

Credit Card Number

Credit Card Expiration Date

Name (Please Print)

Address

City  State  Zip

CIRCLE NO. 12 ON FREE INFORMATION CARD

# news HIGHLIGHTS

## Auto Cigar Lighter Transmitter

It looks like the car's cigar lighter, since it's in the lighter slot. But the "Merc," developed by Mallard Manufacturing, Sterling, IL, is a one-ounce transmitter that, when pushed in just like a cigarette lighter, sends a coded signal that opens a garage door. The Merc (Mallard Electronic Radio Control) is said to work with any door opener on the market, and can be easily unplugged and moved to another car. Since it stays in the lighter slot, it isn't easily misplaced or, since it looks like the lighter, stolen. The Merc transmitter and companion receiver will sell for about \$65 together.

## Hearing-aid TV Captions

The Federal Communications Commission has given approval to an electronic system for producing captions on TV programs for hearing-impaired viewers whose TV receivers are equipped with the proper decoding accessory. While this gives the nod to manufacturers who wish to make the accessories, it does not require stations to supply the captions. PBS (Public Broadcasting Service) has been experimenting with the system for two years, but opposition has come from the commercial networks who want more time for testing. According to estimates presented to the FCC, the equipment to produce the captions will cost each station \$30,000 to \$50,000 and encoding the programs is expected to add another \$1000 to \$3400/hr to production costs.

## "Citizens Band" Movie

"Citizens Band," a feature movie about the phenomenon of CB radio and its effect on the lives of some of the people who use it, is being filmed on locations in Marysville and Yuba City in northern California. The Fields Company production for Paramount Pictures release is to be a contemporary comedy-drama about the personal adventures of an interrelated group of characters in Everytown, U.S.A. The movie depicts various uses of CB radio, including heroic rescue operations in highway and air emergencies. All the principal performers who use CB radios in the picture were given CB equipment and operating instructions long before the start of production so that they would become accomplished CB'ers and play their roles authentically.

## The "Leap Second" Year

To keep official time in step with the spinning earth, a leap second was inserted into the world's time at the end of 1976. By recommendation of the International Time Bureau in Paris, France, the leap second began on December 31, 1976, at precisely 23:59:60 Universal Coordinated Time. It ended at 00:00:00 on January 1, 1977, making the "leap second" part of 1976, not 1977. This additional second was inserted by all standard time organizations around the world, including WWV, WWVB, and WWVH in the U.S. The 1976 leap second

was the sixth since the practice began in 1972, and is required because, in comparison with atomic clocks, the earth is slowing down enough so that the extra second is needed to keep the clocks synchronized to the spin of the earth to within one second.

## WWV/WWVH Cutback

On February 1, 1977, the National Bureau of Standards discontinued broadcasts on the less-used frequencies of its two time and frequency radio stations. The affected frequencies are 20 and 25 MHz at WWV (Fort Collins, Colorado) and 20 MHz at WWVH (Kauai, Hawaii). Both stations will continue to broadcast on 2.5, 5, 10, and 15 MHz with no change in radiated power. Radio station WWVB will continue broadcasting on 60 kHz with no changes. Broadcast equipment previously used on the discontinued frequencies will be converted to serve as back-up systems for the remaining frequencies, and will be automatically turned on if the primary transmitters or antennas fail. The NBS also announced that this partial discontinuance of service will be reviewed periodically as changes occur in radio propagation conditions, sunspot activity, etc. If conditions warrant, a resumption of service on the higher frequencies will be considered.

## Video Equipment Bright Spot

Frost & Sullivan, a market research organization, has detected many long-term bright spots in consumer electronics, including video tape systems, video discs, video games, and video projection systems. Despite stiff competition from the Japanese and Taiwan manufacturers for the TV receiver market, Frost & Sullivan concludes that the U.S. can dominate the field of video entertainment systems because of its early start and sophisticated circuitry. The video game market, which checked in at \$26 million in 1976, is expected to climb to more than \$130 million by 1985. There are now more than 70 companies in the field. Video tape systems will be dominated by the Japanese, with a market peaking in 1980 before giving way to video disc systems . . . if the industry agrees to standardization of software and hardware, says Frost & Sullivan.

## Marine Guidelines for CB Monitors

The Coast Guard has established guidelines to assist volunteer CB-monitoring groups in relaying boating distress information. The guidelines are required to make sure a message gets through the various relay stations unchanged. The boatman can't reach the Coast Guard directly on CB because the Coast Guard doesn't monitor CB channels, a task left to REACT teams and other CB groups. The Coast Guard needs the following information: name and description of the boat, position, nature of the assistance required, number of persons aboard, radio frequencies available, name of the owner or operator and his home port and telephone number, and the name and phone number of the original contact for confirmation and callbacks.

# handic®



**FREE!**  
**FULL COLOR**  
**CATALOG OF**  
**handic**  
**EQUIPMENT**  
 Send today  
 for your free  
 copy.

## Now you can buy Europe's No.1 CB in the U.S.A.

The country that created superior steel, jet fighters, automobiles and cameras has also created the world's finest CB equipment.

handic, from Sweden, is the best selling, most popular CB in all Europe.

It is a true system. Base stations, mobiles, hand-holds and accessories interface with one another as a system should.

handic CBs have not only met but exceeded all FCC specifications at their time of introduction. Including the extraordinarily handsome new 40 channel line.

Ruggedly made for tough Swedish geography and extreme weather conditions, yet stunningly designed, handic has drawn rave reviews from CB publications in the U.S.



handic USA, Inc., 14560 N.W. 60th Ave., Miami Lakes, FL 33014

- A. handic 240 - in-dash 40 ch/5w Mobile CB/AM/FM Radio MPX (LED) - \$259.95
- B. handic 230 - under-dash 40 ch/5w Mobile CB (LED) - \$199.95
- C. handic 21 - 2 ch/1w Hand-held CB - \$59.95
- D. handic 32 - 3 ch/2w Hand-held CB - \$69.95
- E. handic 43C - 4 ch/3w Hand-held CB - \$69.95
- F. handic 65C - 6 ch/5w Hand-held CB - \$109.95
- G. UCB - Universal Cassette. Recharge/Power Holder for Hand-holds - \$19.95
- H. handic S-12 - Selective Call for Base & Mobile - \$79.95
- I. handic 305 - 3 ch/5w Mobile CB - \$79.95
- J. handic 4005 - 40 ch/5w Base CB w/Sub-receive (LED) - \$279.95
- K. handic 3605 - 40 ch/5w Base (LED) - \$249.95
- L. handic 007 - 8ch/hi-lo band Scanner w/FM Radio - \$239.95
- M. handic 006-H/L - 8ch/hi-lo band or UHF Scanner - \$149.95
- N. handic 004-U - 4ch/hi-lo band or UHF Pocket Scanner - \$139.95
- O. BK-305 - Power-pak for handic 305, 605, 006 - \$34.95
- P. handic 80 - Base Power Mike - \$49.95

Please send the free handic color catalog and name of my nearest dealer.


Name \_\_\_\_\_  
 Address \_\_\_\_\_  
 City \_\_\_\_\_  
 State \_\_\_\_\_  
 Zip \_\_\_\_\_

**handic**  
 USA Inc.



Telephone: (305) 558-1522 Telex: 519139  
 Kennedy Building, 14560 N.W. 60th Ave.  
 Miami Lakes Florida 33014 USA

# Meet The Digital Group

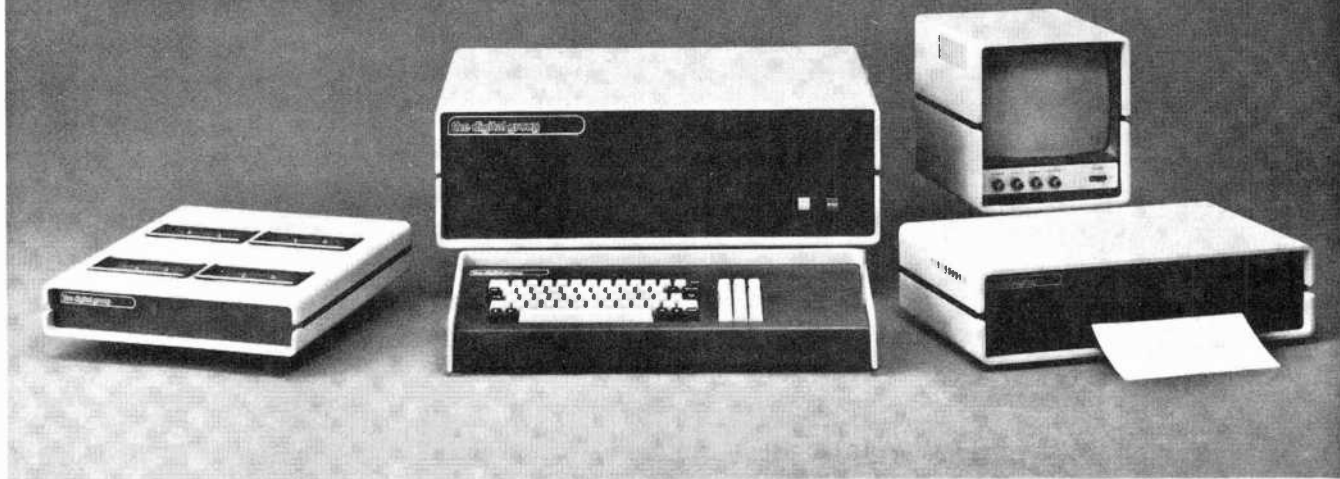

Clockwise from top: CPU, 9" Video Monitor, Impact Printer, Keyboard, Cassette Storage System with Four Drives.

If you are seriously considering the purchase of a microcomputer system for personal or business use...or just beginning to feel the first twinges of interest in a fascinating hobby...the Digital Group is a company you should get acquainted with.

For many months now, we've been feverishly (and rather quietly) at work on our unique, high-quality product—a microcomputer system designed from the inside out to be the most comprehensive, easy-to-use and adaptable system you'll find anywhere. And our reputation has been getting around *fast*. In fact, you may have already heard a little something about us from a friend. We've found our own best salesmen are our many satisfied customers.

There's a good reason. Simply, the Digital Group has a lot to offer: state-of-the-art designs, a totally complete systems philosophy, unexcelled quality, reasonable software, affordable prices and the promise that our products will not become rapidly obsolete, even in this fast-moving, high-technology field.

## The Advantages

Here are a few specific advantages of our product line:

- We offer interchangeable CPUs from different manufacturers (including the new "super chip"—the Z-80 from Zilog) which are interchangeable at the CPU card level. That way, your system won't become instantly obsolete with each new design breakthrough. The major portion of your investment in memory and I/O is protected.
- Digital Group systems are complete and fully featured, so there's no need to purchase bits and pieces from different manufacturers. We have everything you need, but almost any other equipment can be easily supported, too, thanks to the universal nature of our systems.
- Our systems are specifically designed to be easy to use. With our combination of TV, keyboard, and cassette recorder, you have a system that is quick, quiet, and inexpensive. To get going merely power on, load cassette and go!

the digital group

P.O. Box 6528  
Denver, Colorado 80206  
(303) 777-7133

OK, I'd like to get to know you guys better. Send me the whole package!

Name \_\_\_\_\_

Address \_\_\_\_\_

City/State/Zip \_\_\_\_\_

- Design shortcuts have been avoided—all CPUs run at full maximum rated speed.
- All system components are available with our beautiful new custom cabinets. And every new product will maintain the same unmistakable Digital Group image.

## The Features

Digital Group Systems—CPUs currently being delivered: Z-80 by Zilog, 8080A/9080A, 6800, 6500 by MOS Technology.

All are completely interchangeable at the CPU card level. Standard features with all systems:

- Video-based operating system
- Video/Cassette Interface Card  
512 character upper & lower case video interface (1024 optional)  
100 character/second digitally synthesized audio cassette interface
- CPU Card  
2K RAM, Direct Memory Access (DMA)  
Vectored Interrupts (up to 128)  
256 byte I702A bootstrap loader  
All buffering, CPU dependencies, and housekeeping circuitry
- Input/Output Card  
Four 8-bit parallel input ports  
Four 8-bit parallel output ports
- Motherboard

Prices for standard systems including the above features start at \$475 for Z-80, \$425 for 8080 or 6800, \$375 for 6500.


## More

Many options, peripherals, expansion capabilities and accessories are already available. They include rapid computer-controlled cassette drives for mass storage, printers, color graphics interfaces, memory, I/O, monitors, prom boards, multiple power supplies, prototyping cards and others. Software packages include BASICs, Assemblers, Disassemblers, Text Editors, games, ham radio applications, software training cassettes, system packages and more (even biorhythm).

## Sounds neat—now what?

Now that you know a little about who we are and what we're doing, we need to know more about you. In order for us to get more information to you, please take a few seconds and fill in our mailing list coupon. We think you'll be pleased with what you get back.

BY HORACE ENEA  
AND JOHN REYKJALIN

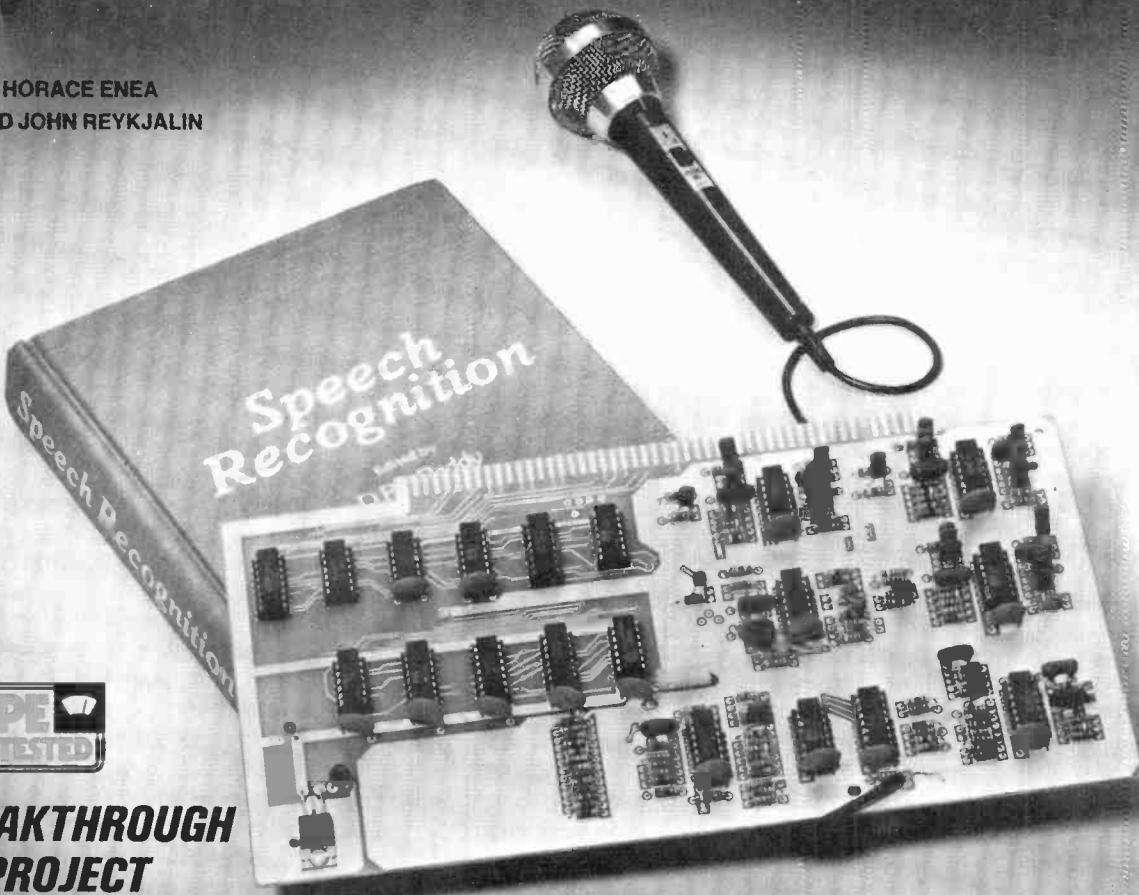

**BREAKTHROUGH  
PROJECT**

# INTRODUCING SPEECHLAB

THE FIRST HOBBYIST VOCAL INTERFACE FOR A COMPUTER!

***Now your computer can respond to vocal commands  
by the simple addition of a \$250 single-board unit.***

IMAGINE being able to *talk* to your computer and have it respond by way of a hard-copy device or by activating some external appliance! Computer hobbyists can now enjoy this facility by building "Speechlab," a new, low-cost (under \$250) computer peripheral. To use it, all one does is plug the single Speechlab pc board into an Altair-bus connector (used by many microcomputer manufacturers), enter a special program, and the computer does the rest.

It's a state-of-the-art approach at a moderate cost.


One section of the program allows the user to "train" the computer to accept a vocal input (via a microphone), analyze the spoken word, and create a digitized version that is stored in memory. The second part of the program allows the user to speak to the Speechlab and have the computer generate the output selected for that particular sound.

The vocabulary size of Speechlab is a

function of the speech recognition algorithm used and the amount of memory available. For the program used in this article, it is 64 bytes per spoken word.

The unique characteristics of Speechlab open many formerly closed doors. Since Speechlab will operate with any audio input (not necessarily a recognized language), a person who's vocally handicapped can operate almost any number of appliances (TV receiver, stereo system, solenoid-operated door,

Fig. 1. The mic input is amplified, filtered and applied to S1 along with raw audio, zero-crossing detection, and three reference voltages. Output of S1 is computer selected by switch S2 for digitizing.

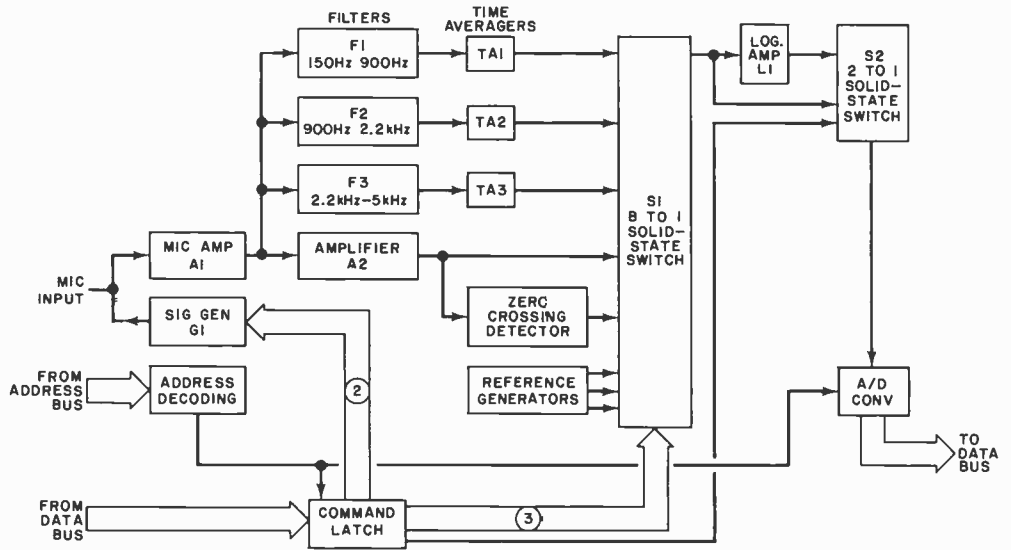

etc.) using a repeatable sound such as a grunt. One can use Speechlab, too, as a vocal processor to add spoken commands to many computer games (such as the "Star Trek" game), or enter the world of artificial intelligence and advanced programming.

**Circuit Operation.** The basic block diagram of Speechlab is shown in Fig. 1. The audio input is amplified by A1 and applied to three 80-db/decade rolloff band-pass filters F1, F2, and F3. These filters encompass the ranges of 150 to 900 Hz, 900 Hz to 2.2 kHz, and 2.2 kHz to 5 kHz, respectively. These ranges correspond to the frequency ranges of the first three resonances of the average human vocal tract.

Each filter is passed to a time averager (TA1, TA2, and TA3) to generate a voltage proportional to the level of the speech waveform within each band.

The amplified audio signal from A1 is further amplified by A2 to generate an unfiltered waveform that can swing  $\pm 2$  volts about a rest level of 2 volts. This signal is also applied to a zero-crossing detector that generates a voltage proportional to the number of times the speech waveform crosses the 2-volt rest level in a given period of time, thus generating a measure of the dominant frequency in the speech signal.

These five voltages—TA1, TA2, TA3, A2, and ZCD—are fed to solid-state switch S1 along with three reference voltages used for calibration and self test. A computer output command selects one of these five voltages to be passed through S1.

The selected output from S1 is passed to a second solid-state switch (S2), and to a logarithmic amplifier (L1) that emphasizes the low-level signal be-

fore being passed to S2. Switch S2 can select either the direct output from S1, or the output from L1, and pass this selected signal to a 6-bit A/D converter where the voltage is converted to a digital value. The output of the A/D converter is fed to the computer data bus.

All operations of the Speechlab are controlled through a single I/O port (address AF<sub>hex</sub>). As shown in Fig. 2, six bits are used: bit-5 disables the 8-to-1 multiplexer (S1), and is used when switching between bands; bit-4 controls signal generator G1 which is used either to drive the microphone so that it acts like a miniature loudspeaker for prompting during voice input, or to drive the filters and zero-crossing detector during calibration and test; bit-3 selects either linear or logarithmic scaling of the voltage applied to the A/D converter; while bit-2, bit-1, and bit-0 select one of the eight signals from S1 for A/D conversion.

The input data word contains the 6-bit A/D output in bits 0 through 5, bit-6 is unused and is always 0, while bit-7 is the A/D converter status with a 1 corresponding to busy, and 0 corresponding to finished.

Speechlab is physically configured to occupy one slot in the Altair bus, and the complete schematic is shown in Fig. 3 through Fig. 7.

**Construction.** The two foil patterns (Speechlab uses one double-sided pc board) are shown half-size in Fig. 8. (Blow up to full size on film only.) Component layout is shown in Fig. 9.

All the components are mounted on one side of the board, with all the soldering done on the noncomponent side. Sockets are recommended for all IC's since most of them are MOS-types that

may be damaged by improper handling.

Integrated circuits IC1, IC4, IC7, IC8, IC9, IC15, and IC16 should be selected so they are capable of delivering a 4-volt output when using a 5-volt supply. Dual flip-flop IC14 can be from any manufacturer but Fairchild, as their truth table is somewhat different from the conventional table.

Start construction by installing the voltage regulator (IC6), all the discrete components, and the IC sockets—do not install the IC's at this time. Check the board for correct parts installation, and to make sure that there are no solder bridges between adjacent foil traces. Mount the board in an Altair bus connector, and check for the presence of 5 volts at the output of the voltage regulator and at the appropriate socket pins. Remove the board from the computer.

Install IC2 through IC5, IC10 through IC14, and IC17 through IC22. Install the board back in the Altair bus connector, and turn on the computer. Load the test

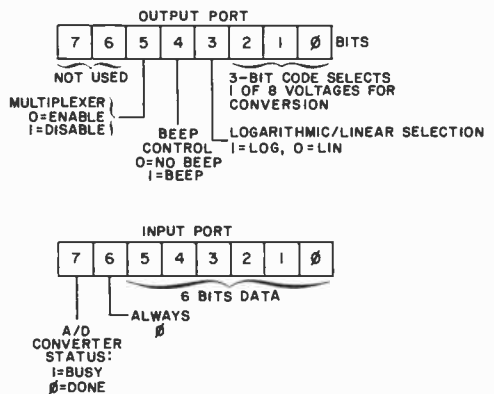


Fig. 2. Input and output port bit configuration.



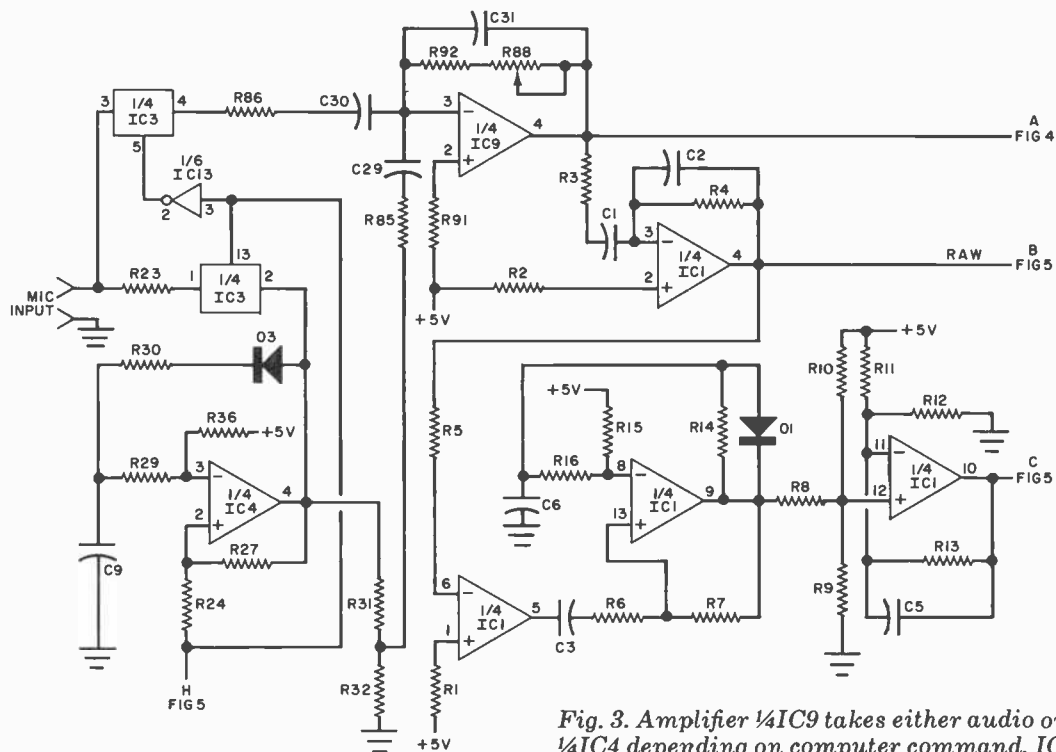


Fig. 3. Amplifier  $\frac{1}{4}$ IC9 takes either audio or tone from  $\frac{1}{4}$ IC4 depending on computer command. IC1 circuits are used as raw audio amplifier and zero-crossing detector.

### PARTS LIST

Unless otherwise noted, the following capacitors are 10% Mylar types, and all picofarad sizes are CM05 types.

- C1, C16, C21, C43, C47, C49, C52, C57—0.0047  $\mu$ F
- C2, C31—100 pF
- C3, C17, C20—270 pF
- C4, C7, C8, C10, C12, C19, C27, C32, C33, C34, C35, C36, C37, C44, C55, C61, C62—0.1  $\mu$ F, 25-V disc
- C5, C14, C18, C24, C54, C60—0.01  $\mu$ F
- C6, C42, C45, C53, C56—240 pF
- C9, C40, C48—0.022  $\mu$ F
- C11, C29—47 pF
- C13—15  $\mu$ F, 25 V tantalum
- C15, C22, C51, C59—0.0015  $\mu$ F
- C23—0.0022  $\mu$ F
- C25, C26, C28, C38—1  $\mu$ F
- C30, C39, C46—0.047  $\mu$ F
- C41—0.1  $\mu$ F
- C50, C58—0.001  $\mu$ F
- D1, D3 through D6—1N4148 or 1N914 diode
- D2—1N746 diode
- IC1, IC4, IC7, IC8, IC9, IC15, IC16—LM3900 quad amp
- IC2—4051 8-to-1 analog multiplex
- IC3—4016 quad analog switch
- IC5—LM311 comparator
- IC6—78M05 5-volt regulator
- IC10—4024 7-stage binary counter
- IC11, IC18—74C174 D flip-flop
- IC12—4050 hex buffer
- IC13, IC22—4049 hex buffer inverter
- IC14—4013 (see text) dual-D flip-flop
- IC17—74LS30 8-input NAND gate
- IC19—8097 three-state hex buffer
- IC20—8093 three-state quad buffer
- IC21—4001 NOR gate
- MIC—Mura DX-121 dynamic microphone (part of stereo set Mura DX-242)

L1—22- $\mu$ H choke

Unless otherwise noted, the following resistors are  $\frac{1}{4}$ -W, 5%

- R1—619,000 ohms, 1%
- R2—1 megohm, 1%
- R3—6810 ohms, 1%
- R4—332,000 ohms, 1%
- R5—200,000 ohms, 1%
- R6, R20, R21—30,000 ohms
- R7, R100—3 megohms
- R8, R9, R10, R12, R14, R16, R104—1 megohm
- R11—910,000 ohms
- R13—2.7 megohms
- R15, R48—10 megohms
- R17, R18—20,000 ohms
- R19, R22, R106—10,000 ohms
- R23—1000 ohms
- R24, R27—1.2 megohms
- R25, R34, R39—470,000 ohms
- R26, R38—750,000 ohms
- R28, R31—100,000 ohms
- R29—110,000 ohms
- R30—39,000 ohms
- R32—47,000 ohms
- R33, R41—68,100 ohms, 1%
- R35, R96, R102—75,000 ohms
- R36—3.9 megohms
- R37, R46—357,000 ohms, 1%
- R40, R50, R52, R54, R56, R58, R60, R61—10,000 ohms, 1%
- R42—12,100 ohms, 1%
- R43, R49—4750 ohms, 1%
- R44—4320 ohms, 1%
- R45, R47—681,000 ohms, 1%
- R51, R53, R55, R57, R59—4990 ohms, 1%
- R62—274,000 ohms, 1%
- R63—7500 ohms
- R64, R66, R72, R75—160,000 ohms
- R65, R71—12,000 ohms

- R67, R70—300,000 ohms
- R68—931,000 ohms, 1%
- R69—2 megohms
- R73—620,000 ohms
- R74, R76, R90, R92—62,000 ohms
- R77—15,000 ohms
- R78, R83, R84—147,000 ohms, 1%
- R79, R80, R87—51,100 ohms, 1%
- R81, R82, R89—174,000 ohms, 1%
- R85—330,000 ohms
- R86—680 ohms
- R88—100,000-ohm pc trimmer potentiometer
- R91—270,000 ohms
- R93—249,000 ohms, 1%
- R94—4300 ohms
- R95, R97, R103, R105—360,000 ohms
- R98, R101—820,000 ohms
- R99—845,000 ohms, 1%
- R107—158,000 ohms, 1%
- R108—4700 ohms
- R109, R111, R117, R119—82,000 ohms
- R110, R116—5100 ohms
- R112, R115—180,000 ohms
- R113—549,000 ohms, 1%
- R114—1.6 megohms
- R118—510,000 ohms
- R120—6800 ohms
- R121—2000 ohms
- Misc.—Sockets (one 8-pin, thirteen 14-pin, seven 16-pin), regulator mounting hardware, tie-wrap etc.

Note 1: The following is available from Heuristics Inc., 900 N. San Antonio Rd. (Suite C-1), Los Altos CA 94022 (Tele: 415-948-2542): complete kit of all parts including pc board, sockets, microphone, hardware manual, and 200-page lab manual, SpeechBasic, and assembly language programs at \$249. (California residents please add 6 $\frac{1}{2}$ % sales tax.)

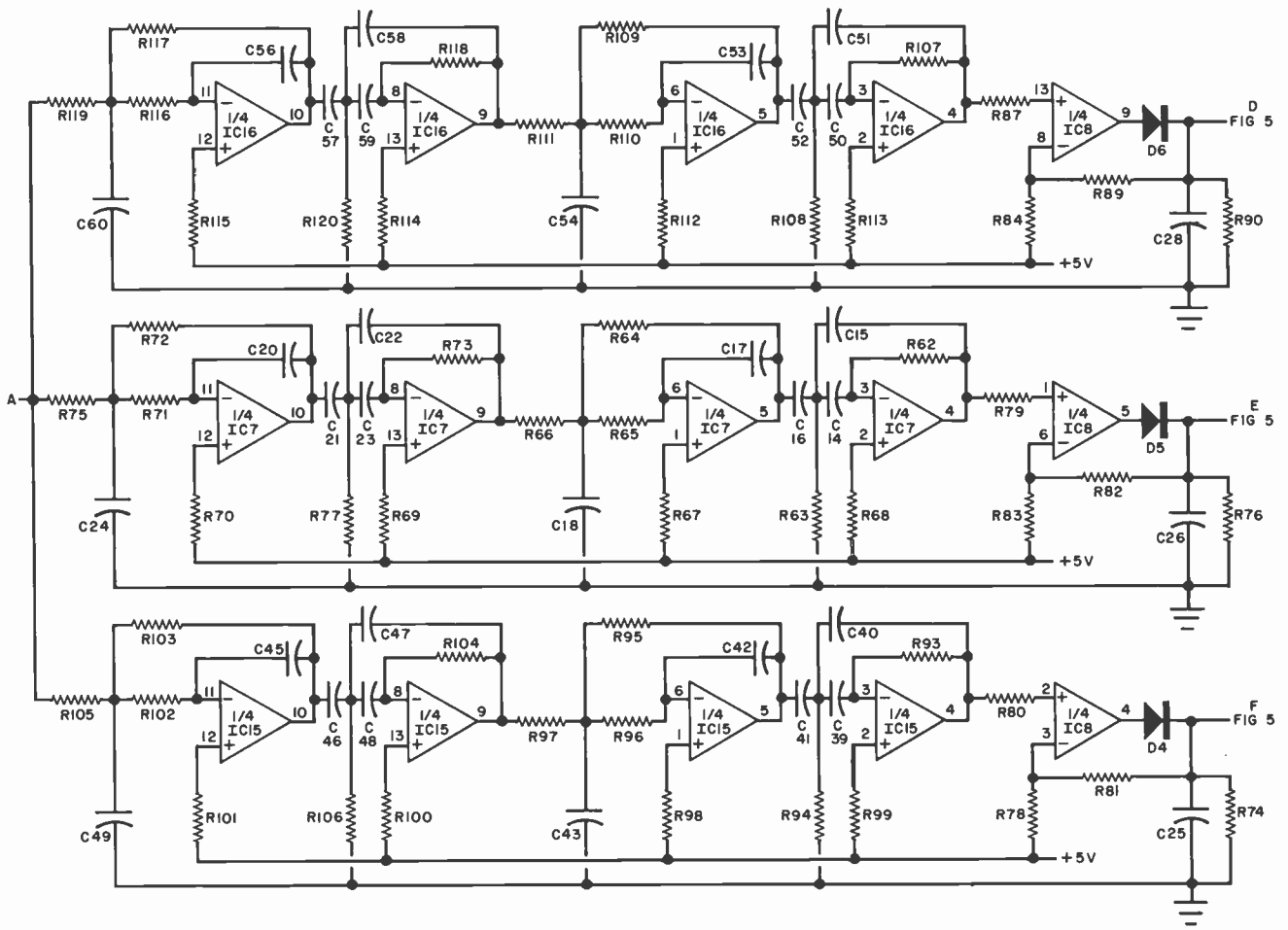


Fig. 4. Three bandpass filters and their associated time averagers. They encompass three ranges corresponding to frequency ranges of the first three resonances of an average human vocal tract.

program of Table I at 100 (hex). NOTE: all program data in this article is in hex.

You must jump to your monitor routine at address 0164-0165. Load address 195 with 05 and run the program. This will input the fixed reference voltage levels to the A/D converter and check the signal paths from switch S1 to the computer data bus.

After running this program, examine locations 200 through 20F, 300 through 30F, and 400 through 40F. Location 200 through 20F should contain  $12 \pm 4$ , 300 through 30F should contain  $24 \pm 4$ , and 400 through 40F should contain  $36 \pm 4$ .

Insert the remaining IC's in their sockets, load location 195 with 10, and run the test program (Table I). This test uses the signal generator (G1) to create an input for the filters, amplifiers, and zero-crossing detector, and thereby checks the remaining signal paths on the board and calibrates the microphone preamplifier. After running the program, examine locations 200 to 20F to see if it contains 16 to 18. If not, adjust potentiometer R88 and rerun the program until these outputs occur.

#### Calibration and Test Program.

The test program (Table I) is a general-purpose calibration, test, and diagnostic program for the Speechlab. It loads at location 100 and requires memory from 100 to 600 for program and data areas. Locations 163-165 should be loaded

with a jump to your monitor address so that the program will return control to your monitor after execution. If you do not have a monitor, place a halt at this location.

The program collects four 256-byte buffers of data from four of the eight pos-


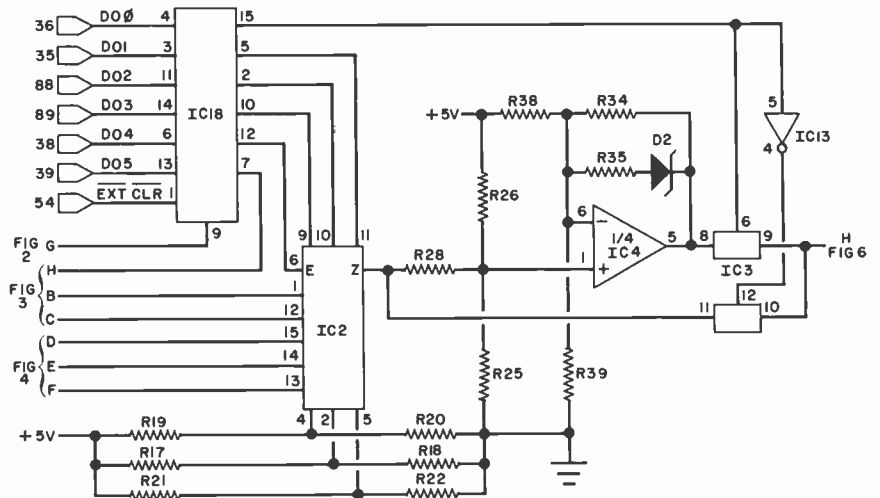


Fig. 5. Command latch (IC18) can activate tone generator and switch S1 (IC2). Op amp (1/4 IC4) is logarithmic amplifier.

Fig. 6. IC17 circuit selects board address and IC14 forms S2. IC10 and IC11 form 6-bit A/D converter. Digitized data is then passed to computer.

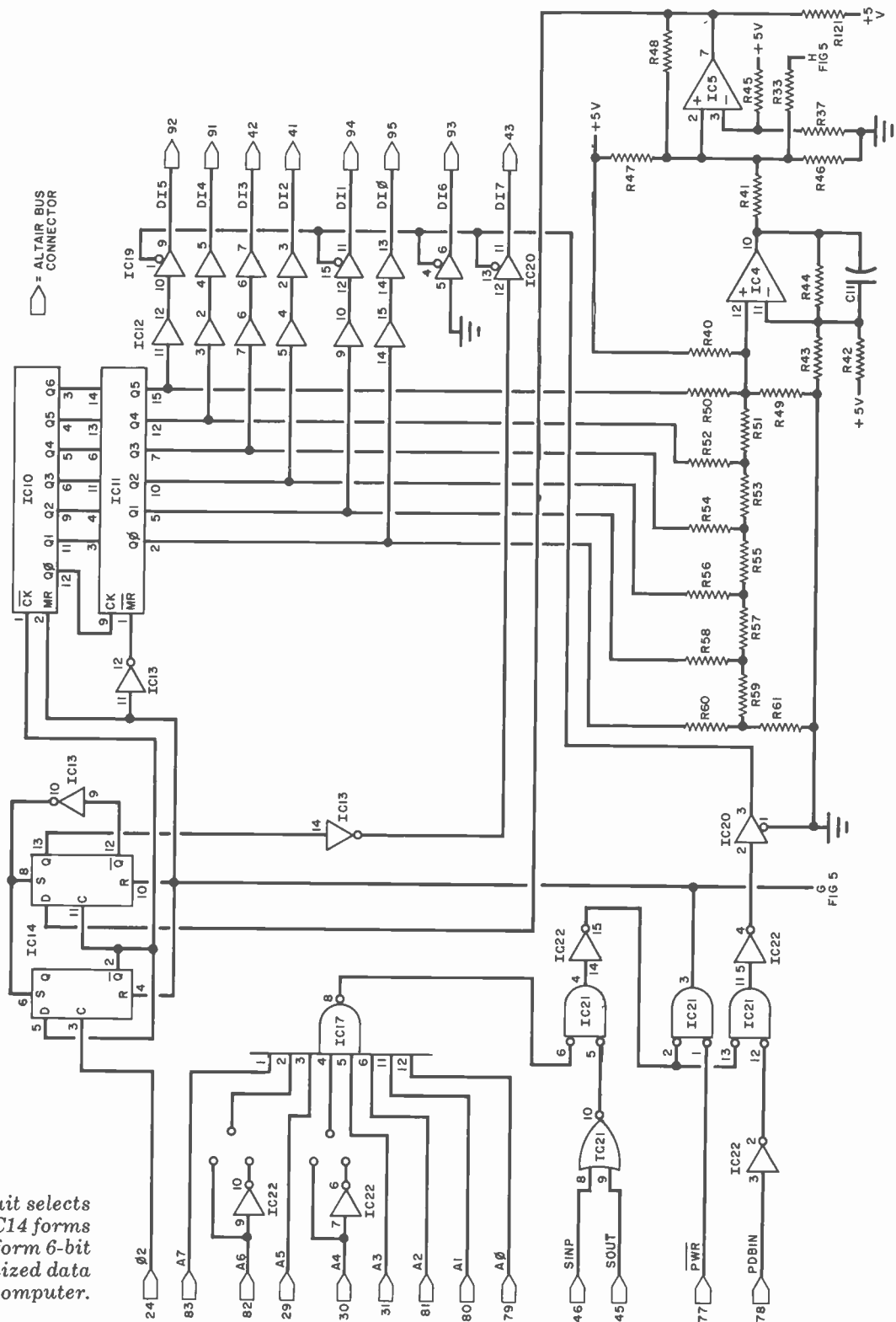

sible inputs to the A/D converter. The first of the four bands is specified by the Test Command word, which also specifies beeper on/off and linear or logarithmic scaling. The next three bands are 1, 2, and 3 greater than specified by the Test Command word. Each band is sampled every five milliseconds until 256 samples have been collected from

each of the four bands. Data from the first band is stored in 200 to 2FF, the second band from 300 to 3FF, the third from 400 to 4FF, and the fourth from 500 to 5FF.

For example, if the Test Command word is set to 00, after the test program is run, the four data areas will contain numbers representing the outputs of

band-0 (low frequency), band-1 (mid frequency), band-2 (high frequency), and band-3 (zero-crossing detector). Anything that was spoken into the microphone while the program was running, is filtered, converted into a binary number, and stored in the data areas.

If the Test Command word is set to 05, the first three data areas will contain

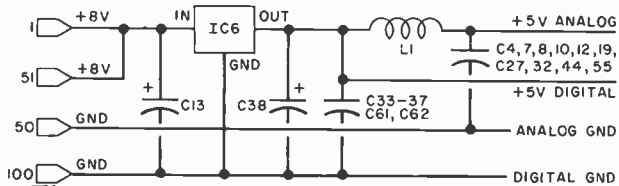


Fig. 7. Power supply circuit is conventional. Note bypass capacitors that are actually mounted between IC power supply pins and ground.

constant numbers corresponding to the three reference voltage levels to the A/D converter on band 5, 6, and 7. This is useful for checking the A/D converter operation and isolating problem areas to one side or the other of the 8-to-1 analog switch *S1*.

If the Test Command word is set to 10, signal generator *G1* is enabled which begins to "beep" the microphone and connects the signal-generator output into the microphone preamplifier *A1*. The four data areas contain data from bands 0, 1, 2, and 3 as when the Test Command word was 00, but the input signal comes from the signal generator rather than from the microphone. This allows calibration of the microphone preamplifier and isolates problems in one of the filter-averager chains.

Adding bit-3 to the command word will cause logarithmic rather than linear data scaling and will isolate problems to the log amplifier or either of the two analog switches comprising *S2*, the 2-to-1 analog switch.

Various combinations of bits in the Test Command word will allow quick calibration and fault isolation, and also provide a quick way to look at raw data from any input through the microphone.

**Software.** A simple technique for speech recognition of the digits zero through nine with a recognition rate of 90% or better, is shown in the flowchart of Fig. 10. An 8080 program for this algorithm is shown in Table II. The program starts at memory location 0100 and requires less than 4K bytes of storage including table space.

There are two modes of operation—training and performance. During training, speech examples of the digits are read into the microphone and the parameters of the speech input are extracted and placed in the tables. In the performance mode, an unknown utterance is presented and recognized.


To use the program, enter it into the computer starting at location 0100, and then run the program. The Teletype will respond with "T" (train) or "P" (perform). Type a "T" and the Teletype will respond with "NUMBER?" which can be between 0 and F. Type the digit you desire, and the microphone will emit a "beep" indicating that the speech window is open. When this beep occurs, vocalize the same digit you just typed in. The microphone will beep again to indicate that the speech window is now closed. The machine will then type T or

TABLE I

0100	ORG 100H
0100 =	START EQU 100H
0100 210002	LXI H,START+100H
0103 228001	SHLD TEMP1
0106 210003	LXI H,START+200H
0109 228F01	SHLD TEMP2
010C 210004	LXI H,START+300H
010F 229101	SHLD TEMP3
0112 210005	LXI H,START+400H
0115 229301	SHLD TEMP4
0118 3A9501	LDA COMAND
011B CD6601	CALL INPUT
011E 2A8D01	LHLD TEMP1
0121 77	MOV M,A
0122 2C	INR L
0123 228D01	SHLD TEMP1
0126 3A9501	LDA COMAND
0129 C601	ADI 1
012B CD6601	CALL INPUT
012E 2A8F01	LHLD TEMP2
0131 77	MOV M,A
0132 2C	INR L
0133 228F01	SHLD TEMP2
0136 3A9501	LDA COMAND
0139 C602	ADI 2
013B CD6601	CALL INPUT
013E 2A9101	LHLD TEMP3
0141 77	MOV M,A
0142 2C	INR L
0143 229101	SHLD TEMP3
0146 3A9501	LDA COMAND
0149 C603	ADI 3
014B CD6601	CALL INPUT
014E 2A9301	LHLD TEMP4
0151 77	MOV M,A
0152 2C	INR L
0153 229301	SHLD TEMP4
0156 CA5F01	JZ STOP
0159 CD7701	CALL DELAY
015C C31801	JMP GO
015F 3E00	MVI A,0
0161 D3AF	OUT OAFH
0163 C3XXXX	JMP SYSTEM
0166 F620	ORI 20H
0168 D3AF	OUT OAFH
016A E6DF	ANI 0DFH
016C D3AF	OUT OAFH
016E DBAF	JMP OAFH
0170 17	RAL
0171 DA6E01	JC LOOP
0174 DBAF	IN OAFH
0176 C9	RET
0177 C5	PUSH B
0178 3E05	MVI A,5
017A FE00	CFI 0
017C CA8B01	JZ RETDEL
017F 0669	MVI B,69H
0181 00	NOP
0182 00	NOP
0183 05	DCR B
0184 C28101	JNZ DEL1
0187 3B	DCR A
0188 C37A01	JMP DEL0
018B C1	RETDEL POP B
018C C9	RET
C000 =	SYSTEM EQU 0C000H
018D	TEMP1 DS 2
018F	TEMP2 DS 2
0191	TEMP3 DS 2
0193	TEMP4 DS 2
0195 YY	COMAND EQU B
0100 21 00 02 22 8D 01 21 00 03 22 8F 01 21 00 04 22	
0110 91 01 21 00 05 22 93 01 3A 95 01 CD 44 01 2A 8D	
0120 01 77 2C 22 8D 01 3A 95 01 C6 01 CD 44 01 2A 8F	
0130 01 77 2C 22 8F 01 3A 95 01 C6 02 CD 66 01 2A 91	
0140 01 77 2C 22 91 01 3A 95 01 C6 03 CD 66 01 2A 93	
0150 01 77 2C 22 93 01 CA 5F 01 CD 77 01 C3 18 01 3E	
0160 00 D3 AF C3 53 00 F6 20 D3 AF E6 DF D3 AF DB AF	
0170 17 DA 6E 01 DB AF C9 C5 3E 05 FE 00 CA BB 01 06	
0180 69 00 00 05 C2 81 01 3D C3 7A 01 C1 C9 9B F7 F0	
0190 FE 57 DC 49 E2 A6	
?	

## "HANDS ON" EXPERIENCE WITH A TALKING COMPUTER

BY LESLIE SOLOMON, Technical Editor

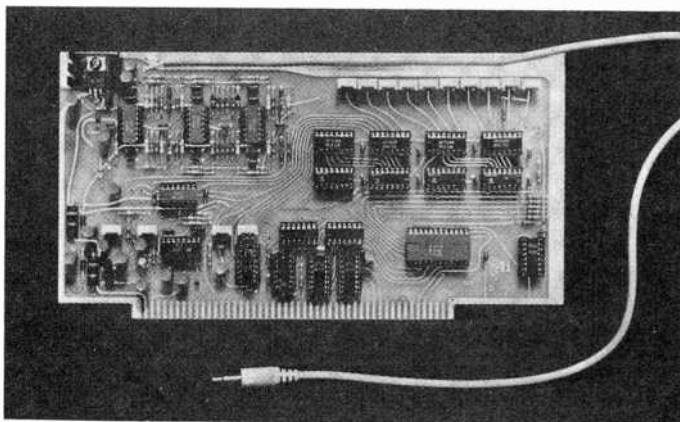

While testing the Speechlab, we borrowed an AI Cybernetic Systems (Box 4691, University Park, NM 88003) Model-1000 Speech Synthesizer (\$325, assembled) to see if our microcomputer could "talk" as well as "hear." The Model 1000 is designed to fit into one slot of an Altair bus and delivers its output via an audio cable that can be plugged into any audio amplifier system. The output level is 0.6 volt p-p; impedance is 1000 ohms; and frequency range is 150 to 4500 Hz.

This synthesizer is phoneme-oriented. Accordingly, you can program it to say anything, as opposed to speech synthesizers that have only several words fixed in ROM. Essentially, the Model 1000 is a hardwired analog of the human vocal tract and various portions of the circuit emulate the vocal cords, the lungs, and the variable-frequency resonant acoustic cavity of the mouth, tongue, lips and teeth.

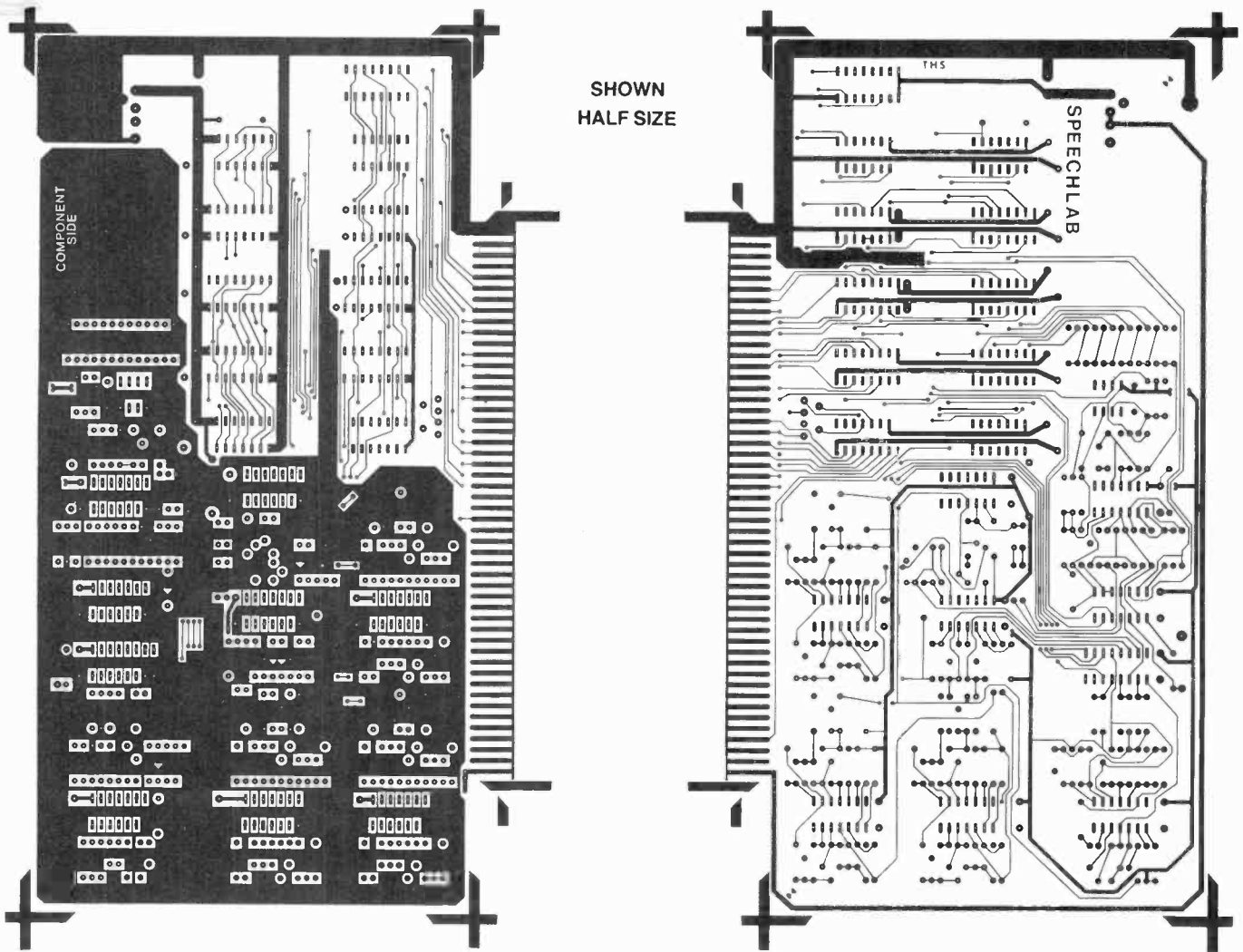


Fig. 8. Etching and drilling guides for pc board are shown half size. Guide at left is the component side. Component layout is in Fig. 9.

P again. You answer with a T, and the process is continued as long as you want. Do not exceed 16 entries with this sample program.

Once you have some vocalized digits in memory, run the program again. This time, when the Teletype asks T or P, answer with a P (for perform). Now, as you

speak the digits into the microphone, the Teletype will respond by typing that digit. When used in a quiet room, with the same vocalization, this algorithm can be

All the information necessary to perform the synthesis functions are located within a ROM that is accessed by the program. Words and sentences are formed by supplying a string of ASCII characters as would be done when outputting to any port, except that these strings also use some non-alphanumeric characters (i.e., the "+" is used to form "th" as in "thaw" or "earth"). Each ASCII character represents a particular phonetic sound or phoneme. If desired, you can create a program that produces simultaneous printout and "voiceout" of the same string.

The device requires very little software to implement: less than 50 bytes of assembly language or a handful of BASIC statements. The manual accompanying the synthesizer covers speech generation in detail, how it is created, and what is involved. It also illustrates how to "mechanize" speech, with several examples shown.

After working with the synthesizer for a couple of weeks, we

found that we have a lot to learn about how humans create speech. After many hours of studying, experimenting, and re-doing programs, we made the Model-1000 utter some recognizable sentences. It is not easy, our experience showed, even when one uses the wealth of instructions provided.

Working with a phoneme-oriented speech synthesizer is a little like learning to use a microprocessor. All the logic is there, but programming it properly is another story. Like working with a processor for the first time, one must crawl frustratingly before walking. Slowly, however, the ideas start to percolate. Our computer still talks with a rather heavy "robotic" accent, but we have hopes that someday it will "humanize."

To paraphrase Sam Johnson: "Sir, a computer talking is like a dog walking on its hind legs. It is not done well; but you are surprised to find it done at all." We have a long road ahead to the "HAL-9000," but the first step has been taken.

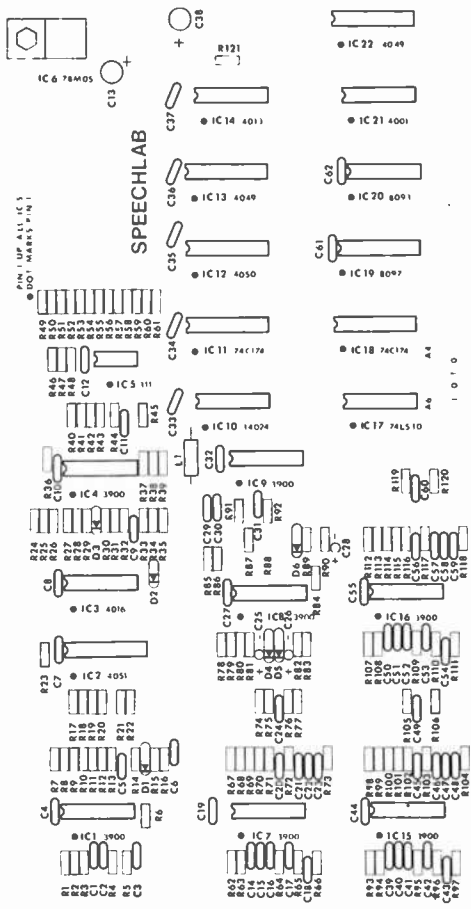


Fig. 9. Component layout for the Speechlab. See etching and drilling guide on previous page.

expected to have a recognition rate greater than 90%.

The program works as follows: the sampling subroutine is entered to obtain a sample of the amplitude every 10 milliseconds in each of the three frequency bands and to estimate the number of zero crossings during each time period. One hundred and fifty samples are collected, allowing up to 1.5 seconds of speech (between microphone "beeps"). A preset threshold is used to find the beginning and end of the word. The duration of the word can now be computed by a simple subtraction. Typically, this duration will be about 400-milliseconds for the digits. The duration time is divided by 16 to select 16 evenly spaced parameters from the three bands and zero-crossing information.

The 64 bytes obtained (16 parameters from each of the four bands) are compared with similar parameters which were collected during the training mode. A summation (running total) of the difference between the 64 parameters of the sample and the parameters of the training "templates" is computed. The totals represent a measure of the difference between the sample and each of the previously stored templates. The tem-

TABLE II

0100	31	00	10	CD	5B	03	21	35	9B	CD	3A	03	CD	8F	03	FE	
0110	54	C2	1A	01	CD	33	81	C3	00	01	FC	5B	C2	2B	01	CD	
0120	5B	03	CD	79	01	CD	81	03	C3	00	01	FC	5B	3F	CD	70	03
0130	C3	00	01	F5	C5	D5	E5	CD	5B	03	21	3D	8B	CD	3A	03	
0140	CD	DA	03	32	6E	04	3C	47	3A	6D	04	B8	DA	2B	01	CD	
0150	5B	03	CD	A3	02	CD	99	01	CD	07	94	3A	6E	04	4F	16	
0160	40	CD	F7	02	11	13	07	CD	A3	03	60	69	0E	40	11	C8	
0170	06	CD	9C	01	E1	D1	C1	F1	C9	C5	D5	E5	CD	A3	02	CD	
0180	99	01	CD	07	04	CD	3D	E2	F1	D1	C1	C9	F5	E8	7E	23	
0190	EB	77	23	0D	C2	8D	01	F1	C9	RE	00	21	6F	04	CD	F9	
01A0	03	FE	06	D2	B2	01	79	FE	96	C2	9E	01	21	44	8B	C3	
01B0	9D	02	79	3D	32	08	07	47	CD	F9	03	FE	06	DA	CC	01	
01C0	79	FE	96	C2	BB	01	21	4E	00	C3	9D	02	79	3D	3D	32	
01D0	09	07	90	3C	32	C7	06	FE	0A	DA	A6	01	0E	01	CD	F9	
01E0	03	FE	06	D2	ED	01	79	FE	0A	C2	DE	01	C9	3A	C7	06	
01F0	81	4F	3A	08	07	81	4F	FE	0A	01	21	FF	FF	22	13	00	
0200	3E	00	32	6E	04	3A	6D	94	3D	4F	06	09	C5	79	07	4F	
0210	21	15	00	09	46	23	4E	21	13	00	56	23	5E	CD	B2	03	
0220	DA	2B	02	C1	0D	FA	39	02	C3	8C	02	21	13	00	70	23	
0230	71	C1	79	32	6E	04	C3	24	02	3A	6E	04	C9	CD	64	02	
0240	06	00	48	16	40	3E	00	5F	21	13	07	CD	D5	03	CD	75	
0250	02	1C	7B	FE	3F	C2	48	02	04	3A	6D	04	B8	C2	42	02	
0260	CD	FA	01	C9	3A	6D	04	87	4F	3E	00	21	15	00	77	23	
0270	0D	C2	6E	02	C9	E5	D5	C5	F5	21	C8	06	16	00	19	96	
0280	F2	85	02	2F	3C	57	78	87	21	15	00	4F	06	00	09	23	
0290	7A	06	77	D2	98	02	29	34	F1	C1	D1	E1	C9	CD	3A	03	
02A0	C3	80	01	3E	FA	CD	E3	02	CD	4B	03	3E	64	CD	E3	02	
02B0	21	6F	04	1E	96	16	00	7A	FE	04	CA	C6	02	CD	D3	02	
02C0	77	23	14	C3	B7	02	3E	0A	CD	E3	02	1D	C2	B5	02	CD	
02D0	4B	03	C9	F6	20	D3	AF	E6	DF	D3	AF	DB	AF	17	DA	DB	
02E0	02	1F	C9	C5	FE	00	CA	F5	02	06	69	00	00	05	C2	EB	
02F0	02	3D	C3	E4	02	C1	C9	F5	D5	06	00	1E	09	79	1F	4F	
0300	1D	CA	0E	03	78	D2	09	03	82	1F	47	C3	FD	02	D1	F1	
0310	C9	F5	D5	1E	09	78	47	79	17	4F	1D	CA	2F	03	78	17	
0320	D2	27	03	92	C3	16	03	92	D2	16	03	82	C3	16	03	17	
0330	5F	3E	FE	A9	4F	7B	1F	D1	F1	C9	7E	FE	00	CA	47	03	
0340	CD	70	03	23	C3	3A	03	CD	5B	03	C9	F5	3E	10	D3	AF	
0350	3E	64	CD	E3	02	3E	00	D3	AF	F1	C9	F5	3E	0D	CD	70	
0360	03	3E	0A	CD	70	03	3E	00	CD	70	03	CD	70	03	F1	C9	
0370	F5	DB	00	07	D2	71	03	F1	D3	01	C9	00	00	00	00	00	
0380	00	E6	0F	C6	30	FE	3A	DA	70	03	C6	07	C3	70	03	DB	
0390	00	E6	40	CA	8F	03	DB	01	E6	7F	C3	70	03	00	00	00	
03A0	00	00	00	00	00	00	00	42	4B	C9	F5	79	93	4F	78	9A	47
03B0	F1	C9	32	0A	07	7B	8A	CA	BE	03	3A	8B	07	C9	79	BB	
03C0	3A	0A	07	C9	F5	C5	D5	CD	F7	02	89	85	6F	D2	D1	03	
03D0	24	D1	C1	F1	C9	C4	03	7E	C9	CD	8F	03	E6	7F	FE		
03E0	30	DA	2B	01	FE	3A	DA	06	03	FE	41	DA	2B	01	FE	47	
03F0	3F	DA	2B	01	D6	07	D6	30	C9	AF	C5	DA	2B	03	86	23	05
0400	C2	FD	03	C1	23	0C	C9	21	C8	06	22	0B	07	3A	C7	06	
0410	4F	16	0A	CD	F7	02	16	18	CD	11	03	26	00	69	22	11	
0420	07	21	00	00	22	0F	07	1E	10	D5	2A	00	07	44	4D	16	
0430	0A	CD	11	03	06	00	3A	80	07	5F	16	00	CD	A3	03	16	
0440	0A	CD	F7	02	21	6F	0A	89	54	5D	2A	00	07	E4	00	00	
0450	8C	01	22	BB	07	2A	0F	07	44	4D	2A	11	07	54	5D	CD	
0460	A3	03	60	69	22	0F	07	D1	1D	C2	29	04	C9	10	CD	EF	
0470	DA	9C	FE	02	C2	54	20	4F	52	20	50	3F	00	4E	55	4D	
0480	42	45	52	00	4E	4F	20	53	50	45	45	43	48	00	4F	55	
0490	54	20	4F	46	20	57	49	4E	44	4F	57	00	00	32	5C	00	


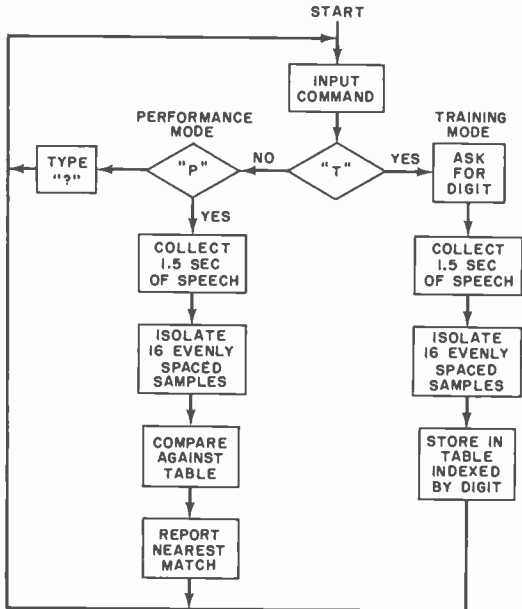


Fig. 10. Flow chart of a simple program that is used to "T" (train) and "P" (perform) a vocal operation. The program is shown in Table II.

plate with the smallest difference from the sample is then selected as the answer (output).

The above algorithm, while relatively simple, illustrates many of the basic concepts of speech recognition. A manual supplied with the Speechlab kit contains descriptions of other approaches to speech recognition, along with sample programs to demonstrate the techniques of speech recognition. ◇

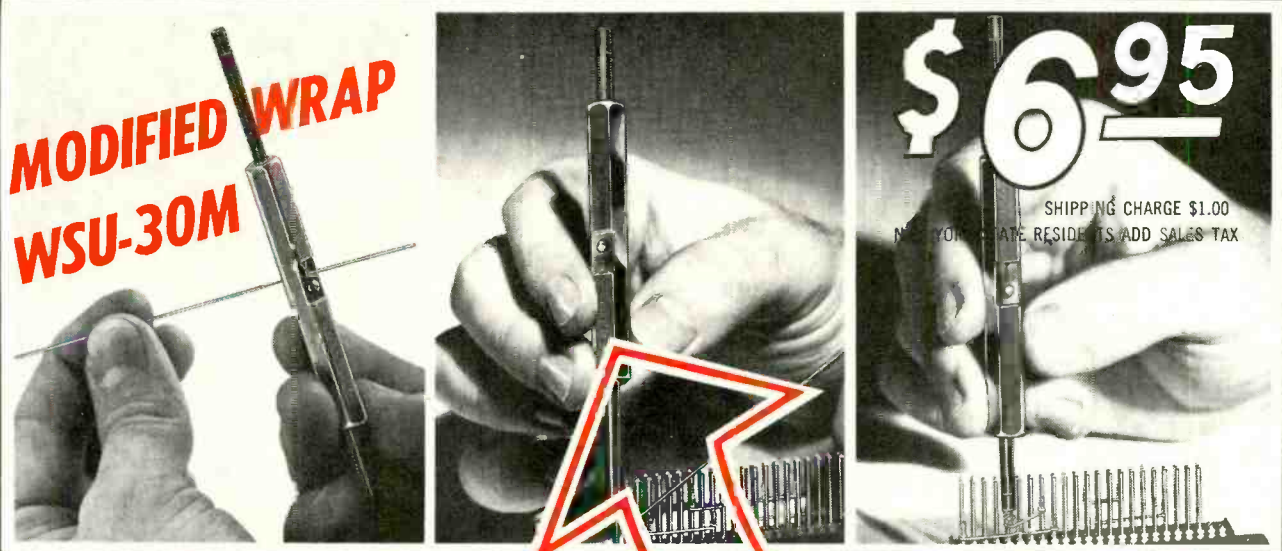**HOBBY-WRAP** WIRE-WRAPPING, STRIPPING, UNWRAPPING TOOL FOR AWG 30 (.025 SQUARE POST)



**MODIFIED WRAP**  
**WSU-30M**

**\$6<sup>95</sup>**

SHIPPING CHARGE \$1.00  
NEW YORK STATE RESIDENTS ADD SALES TAX

**STRIP**

**WRAP**

**UNWRAP**




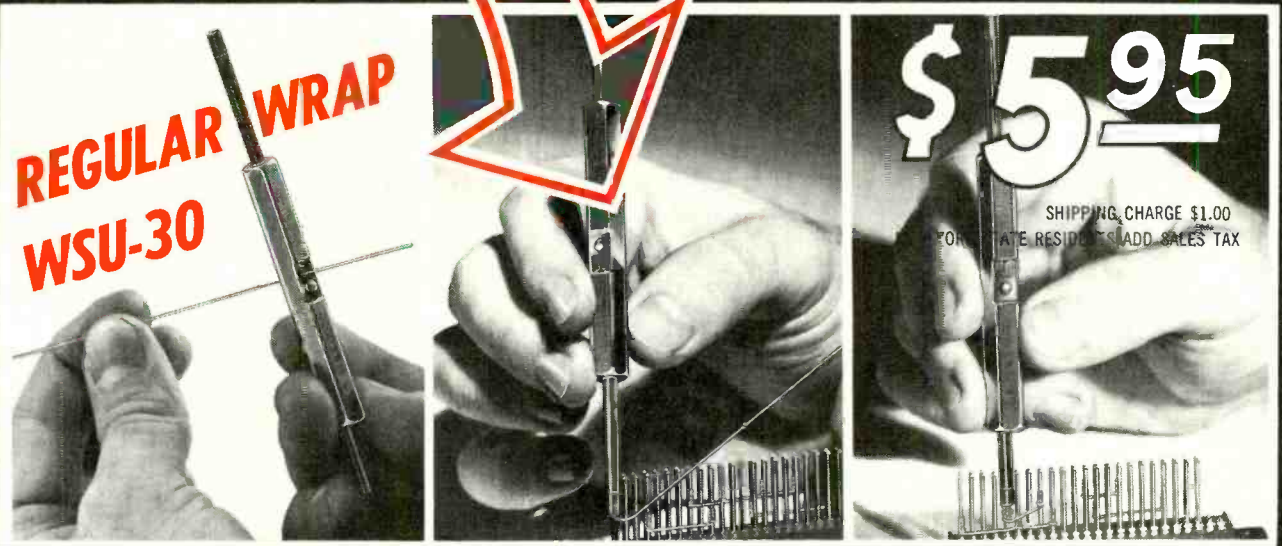**TYPES OF WRAP**

■ A "Regular" bit wraps the bare wire around the terminal. A "Modified" bit wraps a portion of insulation around the terminal in addition to the bare wire. This greatly increases the ability to withstand vibration.



**HOBBY-WRAP** WIRE-WRAPPING, STRIPPING, UNWRAPPING TOOL FOR AWG 30 (.025 SQUARE POST)



**REGULAR WRAP**  
**WSU-30**

**\$5<sup>95</sup>**

SHIPPING CHARGE \$1.00  
NEW YORK STATE RESIDENTS ADD SALES TAX

**STRIP**

**WRAP**

**UNWRAP**

**OK MACHINE & TOOL CORPORATION**

3455 CONNER STREET, ERDIX, NEW YORK, N.Y. 10478 U.S.A. - PHONE (212) 994-6600


TELEX: 125091 TELEX: 232395

**MOST  
\$600 RECEIVERS  
SOUND AS GOOD  
AS THIS ONE.**




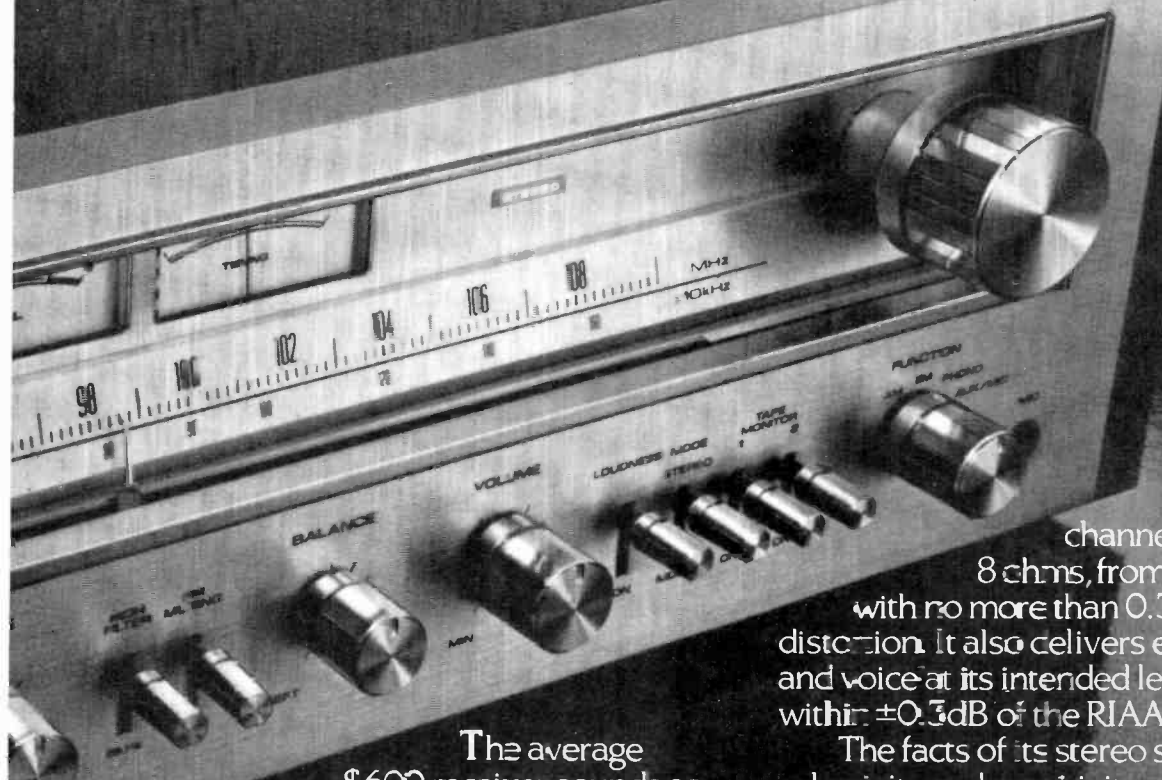
# UNFORTUNATELY FOR THEM, THIS ONE SELLS FOR UNDER \$300.\*



The average \$600 receiver sounds as good as the new Pioneer SX-650 until you start listening to prices.

If \$600 is your kind of price, an SX-650 should qualify as your kind of receiver. Not only will it give you the kind of features and sound quality you'd expect for that kind of money; it'll also leave you with roughly half your receiver budget unexpectedly unspent.

But suppose your idea of a receiver price is somewhere under \$300. The SX-650 will sound better to you than anything you thought you could afford. Because it has more power, a wider frequency range, less distortion, and far greater versatility than most other receivers in that category.

It's a fact that the SX-650 provides a continuous power output of 35 watts per

channel, min. RMS into 8 ohms, from 20 to 20,000 Hz, with no more than 0.3% total harmonic distortion. It also delivers each instrument and voice at its intended level, balanced within  $\pm 0.3$  dB of the RIAA curve.

The facts of its stereo separation, selectivity and sensitivity must really be experienced: sometimes only hearing is believing.

You'll also be impressed by what you don't hear from the SX-650. You won't hear the thousand miscellaneous acoustic devils that live in the limbo between FM stations on lesser receivers.

On your next visit to a high fidelity dealer, listen to a Pioneer SX-650 with any reasonably accurate speakers.


You'll find either its price or its performance amazing. Depending on which you hear first.

## PIONEER®

U.S. Pioneer Electronics Corp., 75 Oxford Drive, Moonachie, New Jersey 07074.  
The value shown in this ad is for informational purposes only. Actual resale prices will be set by the individual Pioneer dealer at his option.

CIRCLE NO. 65 ON FREE INFORMATION CARD

# POWER.

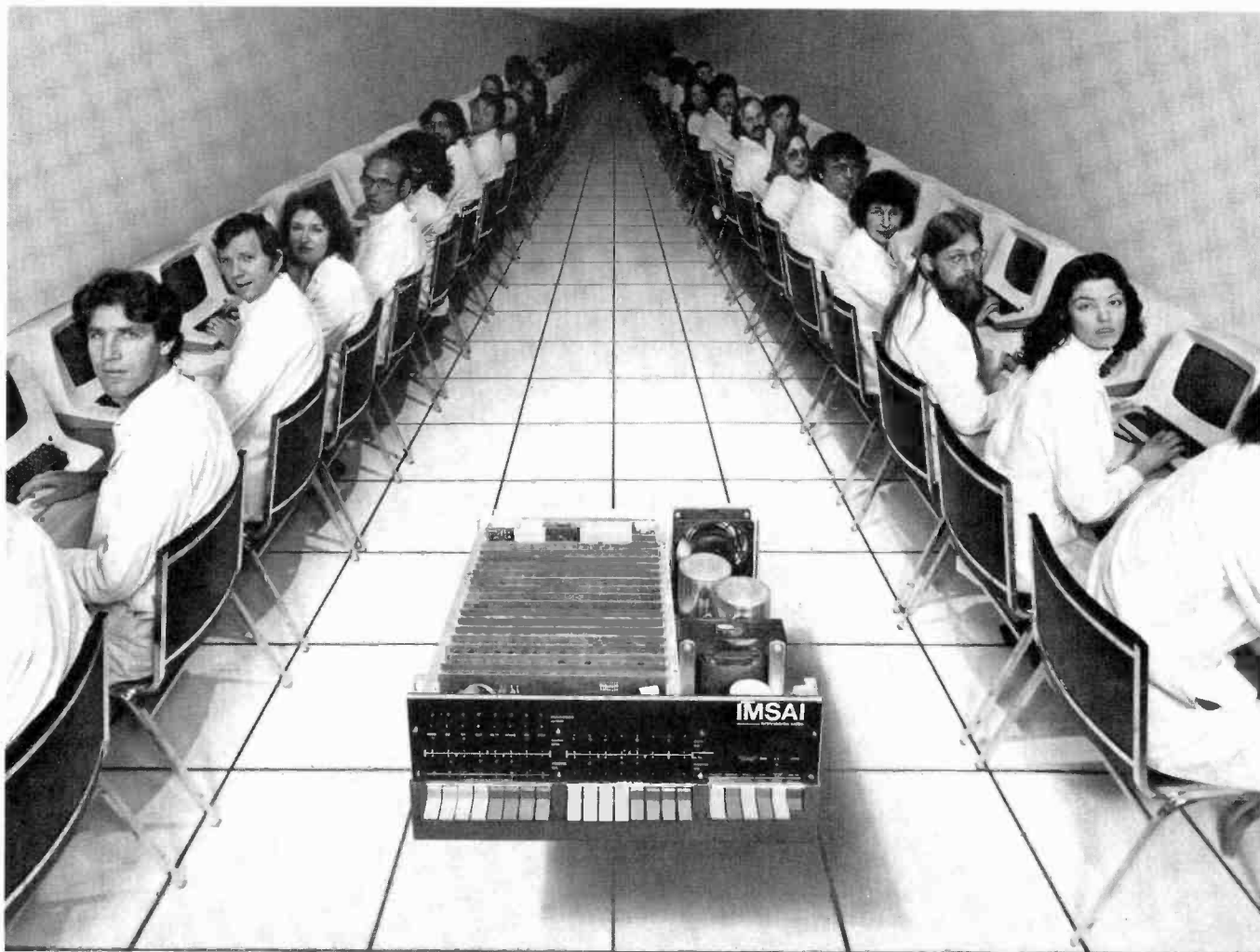

## IMSAI Introduces the Megabyte Micro.™

### The Megabyte Memory

Until today, the largest memory you could fit and address in a single microcomputer CPU was 65K.

Now, IMSAI presents an incredible memory system for micros 16 times more powerful than yesterday's best.

Imagine, a full megabyte of power from sixteen 65K RAM boards.

And, to control all this, the IMSAI Intelligent Memory Manager (IMM), the super control board.

You can write protect blocks throughout the full megabyte. Or, map in 16K blocks.

Plus, preset 16 mapping configurations with protect for high speed transfer or rapid change.

All interrupts are fully vectored, and there's an interrupt if an attempt is made to write into protected memory.

There's even a real "time of day" clock.

### 65K, 32K and 16K RAM Boards

Until today, the most memory you could plug into a single slot was 16K.

Now, IMSAI presents memory boards in astonishing multiples of sixteen: 65K, 32K and 16K low power, dynamic RAM Boards. They can be used in any S-100 bus computer individually or in combination to form conventional systems up to 65K bytes.

Every board is fast. With "hidden refresh" and *no* "wait state."

### The Complete Megabyte Microcomputer System

The IMSAI Megabyte Micro™ is only part of the story. The full system can include dual floppy disks, terminals, plotters, printers and tape cassettes.

IMSAI also offers the finest high level and peripheral software available. Paper tape and Tape Cassette I/O and super Disk Operating Systems. Plus, BASIC and Disk BASIC with more high level languages coming.

Until today, the microcomputer's potential was just something you talked about.

Now, you can put it to work. Powerfully.

#### GENTLEMEN:

I'm power hungry!

- |  |   |
|--|---|
| <input type="checkbox"/> Send 65K RAM Board Kit \$2599   | <input type="checkbox"/> Assembled \$3899 |
| <input type="checkbox"/> Send 32K RAM Board Kit \$749    | <input type="checkbox"/> Assembled \$1099 |
| <input type="checkbox"/> Send 16K RAM Board Kit \$449    | <input type="checkbox"/> Assembled \$679  |
| <input type="checkbox"/> Send IMM ROM Control Kit \$299  | <input type="checkbox"/> Assembled \$399  |
| <input type="checkbox"/> Send IMM EROM Control Kit \$499 | <input type="checkbox"/> Assembled \$699  |
| <input type="checkbox"/> Send full catalog \$1.00        |   |

Check/MO enclosed. Amt. \$ \_\_\_\_\_

Charge my:  BAC  M/C

# \_\_\_\_\_ Exp. Date: \_\_\_\_\_

Sig. \_\_\_\_\_

Send name of my nearest IMSAI dealer

Name \_\_\_\_\_

Company \_\_\_\_\_ Title \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_

State/Zip \_\_\_\_\_

# IMSAI®

IMSAI Manufacturing Corporation  
14860 Wicks Blvd.  
San Leandro, CA 94577  
(415) 483-2093 TWX 910-366-7287

POPULAR ELECTRONICS



# NEW NO-CAMERA PRINTED CIRCUIT BOARD METHODS

*How to use GC Calectro and Datak kits  
for making pc boards directly from printed matter.*

BY A. A. MANGIERI

**Y**OU CAN now copy pc etching and drilling guides directly from the printed page without using a camera or laying out an artwork master. Two pc kits that can accomplish this dream feat for the electronics hobbyist are now on the market. One of these kits is called "Lift-It" from GC Electronics; the other is Datak's No. ER-4 kit.

The two direct-copy pc kits use different approaches to achieve essentially the same end. The Lift-It technique actually lifts the printed pattern from the page with a paint-on transparent film that has an affinity for the printing ink. The ER-4 technique uses a no-camera photographic process to duplicate or reverse a printed image or a positive or negative transparency, depending on how the copy film is exposed. Either copy method will greatly speed up the artwork portion of a construction project in which a pc board is used.

**Kit Lineups.** The Calectro No. J4-828

Lift-It kit from GC contains seven chemicals in bottles and cans, three trays, and pc contact film. The chemical lineup includes the paint-on Lift-It film solution around which the kit is built, board-stripping solution, contact film developer, board developer, paint-on resist lacquer, aerosol resist sensitizer, and premixed ferric-chloride etching solution. Two of the trays supplied are aluminum and are meant for the developing processes, while the third tray is plastic and is for etching only.

The only additional items needed for making printed circuit boards with the Lift-It kit are a yellow "safe" light, any of several light sources for exposing the contact film and board, and copper-clad board blanks. All chemicals in the kit come premixed and ready to use.

Datak's No. ER-4 kit uses a unique direct-photocopy process, called Pos-Neg. The kit contains four chemicals, a printing frame with yellow filter, artwork aids (layout film, drafting tape, and di-

rect-etch dry-transfer pc patterns), photocopy film, and two copper-clad pc blanks. The two types of film developer, film fixer, and ferric-chloride etchant are supplied in powder form (to be mixed when needed), while the board developer and photoresist come ready to use.

The only additional materials needed with the ER-4 kit are a photoflood lamp, three glass or plastic trays, and bottles for the home-mix chemicals.

With both kits, you receive complete, detailed instructions on how to use them. In both cases, materials are supplied for making both positive and negative exposure masks for use with presensitized pc blanks (single-sheet original artwork can measure up to 5" by 5").

**Note:** The two methods are described separately on the following two pages. Methods of transferring from artwork to pc board are given on the final page of this article.

## THE "LIFT-IT" METHOD

If you are new to pc techniques and have little or no experience in working with photographic techniques, the GC Lift-It kit may prove to be more convenient to use. There are no photo methods used in making the first film artwork.

Since using the Lift-It method destroys the original published etching and drilling guide, it pays to photocopy both sides of the magazine page on which the artwork appears so that none of the published material is lost. Cut the page from the magazine, trim the artwork to leave about 1/4" (6.35 mm) excess on all sides, and tape the artwork flat on a sheet of waxed paper. Paint the Lift-It emulsion over the entire surface of the artwork and allow to dry for 15 minutes. Repeat painting on the Lift-It emulsion and allowing it to dry until six thin, even coatings have been built up. After applying the final coating, allow the emulsion to dry for at least two hours.

When final drying is complete, soak the artwork in warm, soapy water for an hour or more. Remove the artwork from the soaking bath and carefully remove the softened paper from the Lift-It film by rubbing with the tip of your finger. Be careful to avoid tearing, stretching, or deforming the film. If particles of paper

prove to be stubborn, return the artwork to the soaking bath for 15 minutes to a half hour. Finally, when all particles of paper have been removed from the film, allow the latter to completely air dry, after which you can apply a coat of the Lift-It emulsion to the ink side of the film. Make this coat as thin as possible.

You can greatly reduce the time to make the first artwork if, after applying the Lift-It emulsion, you dry it under a heat lamp or in a just-warm oven. Arrange the heating to dry the film in 3 to 5 minutes. (The wet emulsion is milky; as it dries, it becomes clear.) Using heat to speed up the drying, you can put the artwork in the soaking bath after 30 to 45 minutes of final drying. To reduce soaking time, tape the artwork, paper side up, to a clean glass plate and place both in the bath. After 10 minutes or so of soaking, cautiously rub the surface of the paper to break up any glaze. Repeatedly rub the paper gently until it begins to roll off in small bits at first and then in larger pieces. If the paper stubbornly adheres to the film, do *not* rub harder; allow additional soaking time and then proceed.

The prepared artwork can be used as is to expose presensitized pc blanks treated with positive photoresist, such as GC's No. 22-232 spray-on positive

resist (use only GC No. 22-225 resist developer when using this positive photoresist—not the No. J4-630 board developer supplied in the Lift-It kit).

**Positive to Negative.** Assuming you are using negative photoresist and have a Lift-It positive, the next step is to make a negative of the Lift-It artwork. To do this, you use the contact film supplied in the kit. The procedure is simple. Working under safe-light conditions, you cut the film to size, place it glossy side up in a contact frame (such as GC's No. 22-280 frame), place over the film the Lift-It positive with ink side down, close the frame, and expose it under cool-white fluorescent light. If you do not have a contact frame, two clean sheets of glass will do. Excellent results are obtained with a pair of 20-watt cool-white fluorescent lamps at a distance of 4" (10.2 cm). Exposure time will first have to be established by exposing segments of a thin strip of the film for 1/2, 1, 2, and 4 minutes.


Once you have established the correct exposure time and have exposed the film through the Lift-It positive, switch to safe-light conditions, remove the film from the contact frame, and place it, dull side up, on a clean sheet of glass. Flow onto the film a liberal quanti-

## THE "POS-NEG" METHOD

The Pos-Neg method used in the DataK ER-4 kit depends on accurate timing during the exposure of the sensitized film supplied in the kit. Using the Pos-Neg copy mode, you can directly copy the pc etching and drilling guide from the printed page. This results in a film positive that can be used directly to expose positive-resist-sensitized pc blanks.

To use the direct-copy Pos-Neg method, you begin by loading the contact frame (included in the kit) with the printed etching and drilling guide with the artwork facing up, followed by a narrow test strip of the sensitized film with its brown side up, and with the yellow filter on top. The whole is firmly sandwiched together between the contact frame and its top glass.

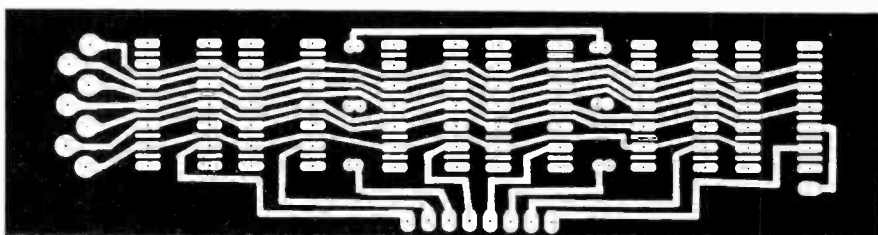
Next, you expose the test strip in blocks for 30 to 100 seconds at 10-second intervals. After developing and fixing the exposed film strip, you may find only one block satisfactory for your



Typical ER-4 mask.



Mask made using the "Lift-It" process.

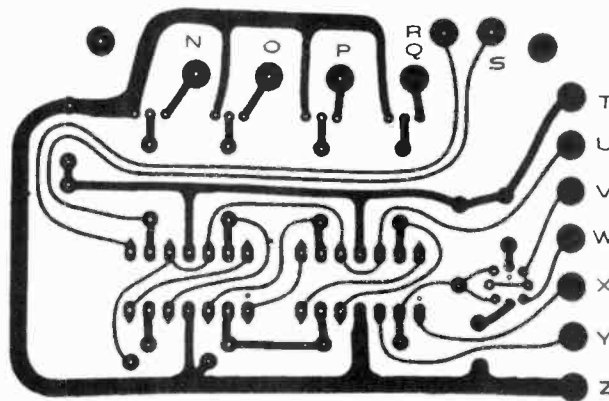

needs. The "good" block will have almost opaque blacks surrounded by a slight brownish haze in the "clear" areas. It is usually necessary at this point to run off another test strip, this time in 3-second steps that span the exposure time of the "good" test block, to determine the exact required exposure time within 3 seconds.

Since the Pos-Neg technique involves both direct and indirect lighting effects, it is quite critical. An accurate enlarger timer to control the on-time of the photo-flood light will prove helpful. If you do not have an enlarger timer, you can use a clock with a sweep second hand and manually control the lamp.

At all times, the presensitized film must be in intimate contact with the printed etching and drilling guide. Additionally, there can be no "print-through" in the artwork. If printing on the reverse side of the page from the etching and drilling guide is visible, back the artwork with matte black paper.

The simplest of the photo copying

procedures with the ER-4 kit is the duplication of a positive from positive or negative film transparency. Here, again, you must determine the proper exposure time. You load the contact frame with the grey side of the sensitized film up, transparency, and yellow filter on top, and expose in blocks for 20 to 90 seconds in 10-second intervals. After developing and fixing the exposed film, the correct exposure time will be that represented by the block with opaque black areas surrounded by water-clear areas.

**Positive to Negative.** Two separate exposures of the sensitized film are required to make a positive from a film negative or vice-versa. First, you must determine a "clearing" time. To do this, you load the contact frame with the film test strip with its grey side up and place the yellow filter on top. Then, you expose the strip in blocks for 20 to 90 seconds in 10-second intervals. After this, you develop the film in fresh developer at 68° F (20° C) for 2 minutes, place it in

ty of contact-film developer. Soak a wad of cotton with the developer and rub gently, in a circular motion, over the entire dull surface of the exposed film. After a minute or two, the areas of the film that were not exposed to the exposing light will begin to dissolve and come away from the film. Continue rubbing until all soft areas of emulsion have been removed. Be as gentle as possible with your rubbing because the emulsion left behind at this point will be soft. When all unwanted emulsion has been removed, rinse the film under gently running warm water and allow to dry completely.

What you should now have is a high-contrast film negative with opaque orange areas surrounding water-clear conductor areas. The details should be as sharp as they are in the Lift-It positive. Carefully examine the film negative for discontinuities and other flaws. You can repair discontinuities by cutting away the appropriate portions of the film with a razor blade or sharp X-acto knife. Pits and other flaws in the emulsion can be repaired with the paint-on resist lacquer in the kit.

Although exposure time is not critical, gross underexposure will result in complete removal of the emulsion. Conversely, gross overexposure might preclude any development at all.

the fixer for 5 minutes, wash it under gently running water, and allow it to dry. The test strip should go from fully opaque black to fully water clear, with one or two intermediate shades. If the first fully clear block was exposed for 60 seconds, the clearing time is 70 seconds, for example. Record the clearing time for future reference.

Now, to reverse your film transparency, you first expose the entire test strip through the yellow filter for the recorded clearing time. Then, remove the yellow filter and substitute it with the film transparency and expose again in blocks for 3 to 21 seconds at 3-second intervals. After developing, fixing, and washing the test strip, select the block that has opaque blacks with water-clear whites. You now know the exposure times for both clearing and copying.

The ER-4 Pos-Neg system sounds more complicated than it really is. Once you gain some experience with it, it will be no more difficult to use than were other "photo" methods used in the past.

## FROM ARTWORK TO BOARD

With very little practice, you can easily photosensitize copper-clad pc blanks. The blanks must be flat and free of ragged edges. The best way to deal with a ragged edge is to use a fine steel file to remove copper burrs and fine emery cloth to smooth the edges. Next, thoroughly scour the copper with a steel-wool soap pad until it has a burnished finish and sheds water. Rinse thoroughly and allow to air dry, either at ambient room temperature or in a just-warm oven. Do *not* wipe the blank dry with a towel. The blank is now ready to be sensitized with photoresist.

Go to safe lighting conditions and place the pc blank with its copper side up on a couple of thicknesses of newspaper, thoroughly shake the can of spray resist, and spray a thin, even coating of the resist over the entire copper surface. Dry the resist for an hour at room temperature or for 15 minutes in a just-warm oven. Then inspect your work under safe lighting. If the coating of resist lacquer appears to be too thin, apply a second thin, even coat and again allow to dry. Before taking on a big job, develop a "feel" for the spray technique, using a piece of scrap pc blank.

**Finishing Steps.** Under safe light, place the sensitized pc blank in the contact printing frame and place the exposure mask on top. Make absolutely certain that the proper side of the mask is in contact with the blank. You can now expose the blank with any of four light sources, detailed in the instructions supplied with the kits. A fluorescent lamp with two 20-watt cool-white tubes at a distance of 4" from the top of the contact frame is suitable. You will have to determine the proper exposure time by trial and error with sensitized scrap pc blank.

Once the blank has been exposed, go to safe lighting and immerse it in the appropriate pc board developing solution and agitate. Remove the blank from the solution promptly when the circuit pattern appears, usually in about a minute or less. At this point, the resist is no longer sensitive to light, and you can switch back to normal lighting. Flush the developed blank under gently running water and allow to air dry at room temperature for an hour or in a just-warm oven for about 20 minutes. At no time before the board is dry should you touch the resist pattern. The pattern will still be soft and easily damaged.

After drying is complete, carefully inspect the pattern for faults and use


paint-on resist lacquer or dry-transfer patterns to touch up any breaks. Then etch the blank in pc etching solution. You can speed up the etching time by preheating the etching solution by setting the bottle of solution in hot water until it becomes too hot to handle. Do *not* pour the etchant into a pot and heat it directly on a stove. Pour the etchant into a glass or plastic tray large enough to accommodate the pc blank. Place the blank, copper side down, in the hot etchant and agitate the bath by gently rocking it back and forth. Periodically check the progress of the etching after 20 minutes. When all unwanted areas of copper have been etched away, remove the pc board from the etchant and thoroughly rinse it under running water. Then remove the resist on the copper with pc board stripping solution.

The final step in making a professional-quality pc board at home is to trim the board to size and drill all component-lead and mounting holes. From initial artwork to ready-to-go etched and drilled board, the job should take between five and eight hours, depending on the size and complexity of the board. The boards you make with either of the two kits described here will be indistinguishable from boards made by a professional. ◇


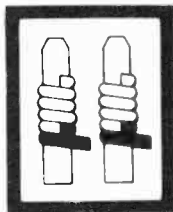
### WIRE WRAPPING TOOL

For AWG 30, .025" (0,63mm) sq. post, "MODIFIED" wrap, positive indexing, anti-overwrapping device



### OK MACHINE & TOOL CORPORATION

3455 Conner St., Bronx, N.Y. 10475 / (212) 994-6600 / Telex 125091

# NEW

HOBBY-WRAP  
Model BW-630



Battery  
**wire**  
wrapping  
tool

**\$34<sup>95</sup>**  
ONLY (batteries  
not included)  
COMPLETE WITH BIT  
AND SLEEVE

# If You're Still Playing Games It's Because You Haven't Seen Our Software Library

This Library is the most comprehensive work of its kind to date. There are other software books on the market but they are dedicated to computer games. The intention of this work is to allow the average individual the capability to easily perform useful and productive tasks with a computer. All of the programs contained within this Library have been thoroughly tested and executed on several systems. Included with each program is a description of the program, a list of potential users, instructions for execution and possible limitations that may arise when running it on various systems. Listed in the limitation section is the amount of memory that is required to store and execute the program.

Each program's source code is listed in full detail. These source code listings are not reduced in size but are shown full size for increased readability. Almost every program is self instructing and prompts the user with all required running data. Immediately following the source code listing for most of the programs is a sample executed run of the program.

This Library is destined to become one of the reference bibles for the small computer field, due to its versatility and uniqueness and the ease of operation of the programs it contains. These volumes are deductible as a business expense when purchased by a company. Send your remittance for prompt delivery, while supplies last. Volume discounts are available to qualified dealers.

The entire Library is 1000 pages long, chock full of program source code, instructions, conversions, memory requirements, examples and much more. ALL are written in compatible BASIC executable in 4K MITS, SPHERE, IMS, SWTPC, PDP, etc. BASIC compilers available for 8080 & 6800 under \$10 elsewhere.

This LIBRARY is a complete do it yourself kit. Knowledge of programming not required. EASY to read and USE. Written in compatible BASIC immediately executable in ANY computer with at least 4K, NO other peripherals needed.

<b>VOLUME ONE</b>	Pert Tree Rate Return 1 Return 2 Schedule 1	Pony Roulette Sky Diver Tank Teach Me
Part 1		
<b>BOOKKEEPING</b>	Part 2	<b>PICTURES</b>
Bond	<b>GAMES</b>	A. Newman
Building	Animals Four	J.F.K.
Compound	Astronaut	Linus
Cyclic	Bagel	Ms. Santa
Decision 1	Bio Cycle	Nixon
Decision 2	Cannons	Noel Noel
Depreciation	Checkers	Nude
Efficient	Craps	Peace
Flow	Dogfight	Policeman
Installment	Golf	Santa's Sleigh
Interest	Judy	Snoopy
Investments	Line Up	Virgin
Mortgage		
Optimize		
Order		



<b>VOLUME TWO</b>	Rand 2 Solve Sphere Trian Stars Track Triangle Variable Vector	Differences Dual Plot Exp-Distri Least Squares Paired Plot Plotpts Polynomial Fit Regression Stat 1 Stat 2 T-Distribution Unpaired Variance 1 Variance 2 XY
Part 3		
<b>MATH &amp; ENGINEERING</b>	Part 4	<b>APPENDIX A</b>
Beam	<b>PLOTTING &amp; STAT</b>	<b>BASIC</b>
Conv.	Binomial	<b>STATEMENT DEF</b>
Filter	Chi-Sq.	
Fit	Coeff	
Integration 1	Confidence 1	
Integration 2	Confidence 2	
Intensity	Correlations	
Lola	Curve	
Macro		
Max. Min.		
Navaid		
Optical		
Planet		
PSD		
Rand 1		



<b>VOLUME FOUR</b>
Bingo
Bonds
Bull
Enterprise
Football
Funds 1
Funds 2
Go-Moku
Jack
Life
Loans
Mazes
Poker
Popul
Profits
Qubic
Rates
Retire
Savings
SBA
Tic-Tac-Toe



VOLUME I & II — \$24.95 each  
VOLUME III — \$39.95 each  
VOLUME IV — \$9.95 each

Add \$1.50 per volume for postage and handling.

<b>VOLUME THREE</b>
Part 5
<b>ADVANCED BUSINESS</b>
Billing
Inventory
Payroll
Risk
Schedule 2
Shipping
Stocks
Switch



## SCIENTIFIC RESEARCH

1712-P FARMINGTON COURT  
CROFTON MD 21114

Phone Orders call (800) 638-9194

Information and Maryland Residents Call (301)-721-1148



# NEW 3½ Digit Multimeter from B&K-PRECISION



**B&K PRECISION** MODEL 283—\$170

...you'll want it for its features  
...but it's the price that will sell you!

- High intensity LED display is easily read from at least 6 feet in the brightest room.
- Measures AC and DC voltage, AC and DC current and resistance.
- 0.5% DC accuracy.
- 100% overrange (1000 scale reads to 1999).
- Automatic polarity.
- Automatic decimal point.
- Flashing overrange indication on display.
- Four voltage ranges to 1000V
- Four current ranges to 1000mA.
- Six resistance ranges to 10 meg.
- In-circuit resistance measurements at voltage levels below conduction threshold of semiconductors.
- Overload protection on all ranges.

Complete new circuitry makes the Model 283 the most dependable and versatile 3½ digit multimeter you can buy. The extra-bright display allows you to use it where other units would cause reading problems. The selectable "low ohms" function permits accurate measurement of semiconductor shunted resistors.

An optional, internal battery pack (BP-83, \$50.00) provides 8 hours of continuous use on one overnight charging and charges when the Model 283 is in use on 115/230VAC.

Thoughtful, convenience features like a side carrying handle, tilt stand and detachable line cord add to its usefulness.

Your B&K-PRECISION distributor has them in stock and will be glad to demonstrate its features to you. Call him, or write for additional information.

**B&K PRECISION**  
**DYNASCAN**  
**CORPORATION**

6460 West Cortland Avenue  
Chicago, Illinois 60635 • 312/889-9087  
In Canada: Atlas Electronics, Ontario





# Build a Legal In-Flight AIRLINE RECEIVER

*Hear pilot-to-control conversations while in-flight  
with low-cost Varactor-tuned crystal set.*

BY CASS R. LEWART

**U**NTIL NOW, "armchair pilots" wishing to listen to airplane-to-tower communications have had to confine their activities to ground-based monitoring. But the project described here—essentially a vhf crystal set with a small audio amplifier—will allow reception of such conversations when the user is on board an airliner. It will do so *without creating any hazard* to the plane's navigation system. The receiver is easily built, using readily available, inexpensive parts.

**About the Circuit.** Unlike super-heterodyne receivers, whose local oscil-

lators generate signals which can interfere with reception in the 108-to-118-MHz radio-navigation band, this project can be used with complete safety. The heart of the project is a 4-transistor audio amplifier with a built-in speaker, shown schematically in Fig. 1. Power switch *S1* is ganged with *R1*, the volume control. The amplifier draws current from a single 9-volt transistor battery, *B1*.

A few modifications transform this amplifier module into an airline receiver, shown schematically in Fig. 2. The receiver comprises a tuned r-f circuit (*L1*, *C1* and *D1*), a demodulator (*D2*) and the modular audio amplifier. The tuned cir-

cuit is unusual in one respect—it uses a voltage variable capacitor or Varactor as the variable capacitance. This diode, when reverse biased over a range of 0 to 9 volts, behaves like a variable capacitor of 5 to 15 pF. Because *C1* is in series with *D1*, the effect of the fixed capacitor is negligible. The combination of *L1*, a small hand-wound coil, and *D1* resonate to provide coverage from 118 through 135 MHz. (Construction details for *L1* are given on the next page.)

A short piece of insulated, stranded hookup wire serves as an antenna. The wire is terminated with a pin or banana plug (*P1*), and is connected to the rest of

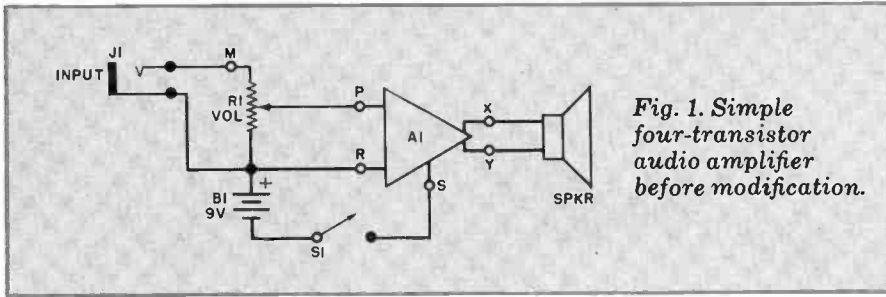


Fig. 1. Simple four-transistor audio amplifier before modification.

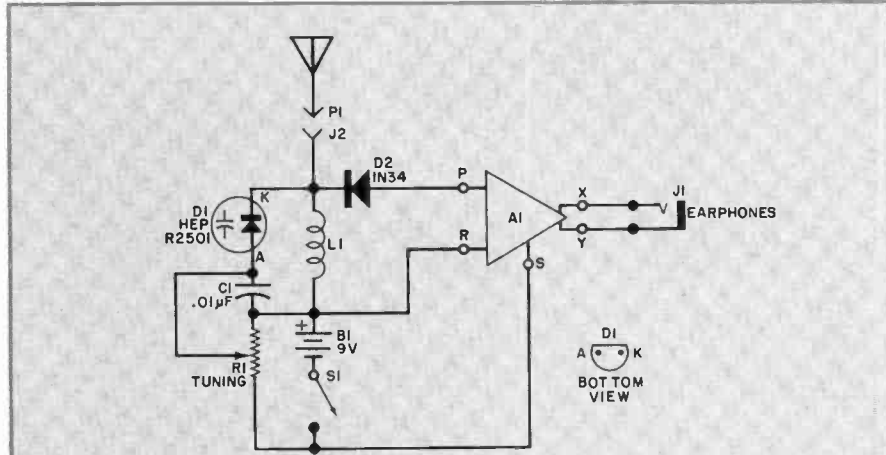


Fig. 2. Schematic of the amplifier with minor additional circuits needed to make airline receiver.

**PARTS LIST**

- |  |   |
|--|---|
| A1—Modular Amplifier (Radio Shack 277-1008 or equivalent)                            | J2—Pin or banana jack   |
| B1—9-volt transistor battery   | L1—Five turns of No. 24 enamelled copper wire on a 3/8-inch form, approx. 10 turns per inch |
| C1—0.01- $\mu$ F, 50-V disc ceramic capacitor  | P1—Pin or banana plug   |
| D1—5-15-pF voltage-variable capacitance diode (Motorola HEP R2501—do not substitute) | R1—Volume/tuning control (part of A1)   |
| D2—1N34 germanium diode  | S1—Spst switch (ganged with R1, part of A1)   |
| J1—Miniature phone jack (part of A1)   | Misc.— Dynamic earphone (8 ohms), hook-up wire, solder, etc.                                |

the circuit via J2, a pin or banana jack. Signals are thus applied to the tuned circuit, which is resonated by means of R1. This potentiometer, which served as the volume control in the unmodified amplifier, functions as a voltage divider to apply variable reverse bias across D1.

After the vhf signal has been boosted by the parallel LC circuit, it is demodulated by germanium diode D2 and applied to the audio amplifier. The output of the amplifier drives a dynamic earphone plugged into jack J1 (the former input to the amplifier).

**Construction** of the receiver is greatly simplified by modifying a ready-built audio module and adding a few additional components. In the author's prototype, a Radio Shack 277-1008 amplifier was used. However, other units can be used equally well. The additional components fit in place of the module's speaker.

Start by removing the three small Phillips screws which secure the amplifier pc board to the plastic enclosure. Then remove jack J1 and unsolder the leads running to it. Raise the pc board and unsolder the leads connected to the speaker. Remove the speaker by softening the glue holding it to the plastic enclosure. Use acetone or nail-polish remover and pry the speaker away with a sharp knife. Then attach what were the speaker leads (points X and Y) to J1. Polarity is not important.

Refer to Fig. 3A and 3B for the following steps. Open the pc foil running from the volume control (R1) to the amplifier input (point P) and to the input jack (point M) by scraping it off with a sharp blade. Connect the terminal previously running to point M to one side of switch S1 (point S), which is ganged with R1. Solder a wire to the wiper of R1 and connect the other end to one side of C1 and the anode of D1. Then solder a wire to the pc foil that formerly ran to the wiper of R1 (on the other side of the break in the foil), and attach the other end of the wire to the anode of D2.

Next, drill a hole about 1-9/16" (3.97 cm) from the top of the enclosure on the left side (as viewed from the rear) to accommodate J2, the antenna input jack. Mount the jack and secure the pc board to the enclosure with the three small Phillips screws. To form L1, wind five turns of No. 24 enamelled copper wire on a 3/8-inch (9.53-mm) form, spaced about 10 turns per inch. Scrape the insulation off the ends of L1 and position the coil in the speaker cutout of the pc board. Connect D1, D2, L1, and C1 as indicated in the schematic, using J2

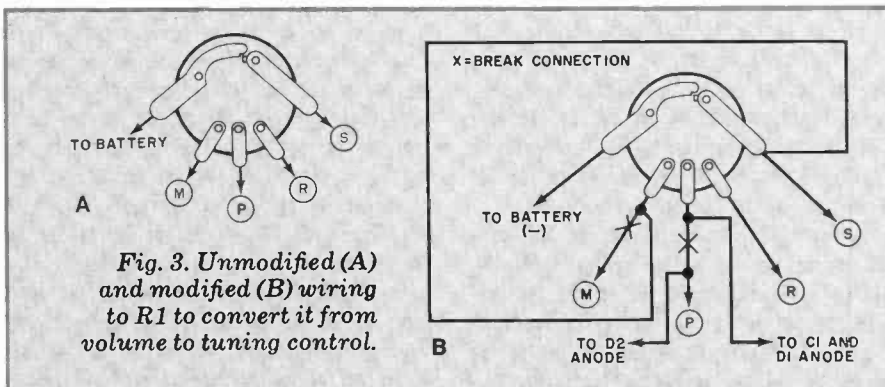


Fig. 3. Unmodified (A) and modified (B) wiring to R1 to convert it from volume to tuning control.

for mechanical support. Be sure to observe correct polarity for the diodes or you will damage them. Solder all remaining connections.

**Alignment.** The best way to align the receiver is to couple it to a signal generator producing an output at 125 MHz with internal 400-Hz modulation. Connect a small dynamic earphone to *J1* and set the tuning control (*R1*, the former volume control). Compress or expand the winding of *L1* for maximum audio output. If you can't get access to a signal generator with the required output, just go to your local airport. Connect a short (one foot or so) wire terminated with a suitable plug to *J2*, and listen to transmissions from the airport tower. Adjust *L1* for best reception with *R1* at center position.

**Operation.** The airline receiver is very simple to use. When you are taking a flight, try to get a seat near the window. Attach the antenna wire to the window with a small piece of masking tape, and plug the earphone into *J1*. This will allow you to monitor the pilot's conversations without causing a commotion.

You will not usually know the exact frequencies used by a particular airplane. Airport towers generally transmit and receive below 120 MHz. Other communications can be found anywhere between 120 and 135 MHz. Between take-off and the time when a plane reaches cruising altitude, its pilot will use several frequencies in succession, communicating with the tower, departure control, and possibly to the particular airline controller. Similarly, the pilot will use several frequencies during the descent.

Each conversation will be brief, lasting only a few seconds. Accordingly, an important characteristic of this receiver is its broad selectivity as compared to that of a superheterodyne receiver. The user can therefore leave the tuning control at its center position. The pilot's transmission will still be heard—even if the tuned circuit is not resonant exactly at the operating frequency. The receiver can be quickly returned for optimum reception if desired. Another possibility is to continuously tune the receiver back and forth, scanning the band until you can hear the pilot's voice.

When using the receiver, you may try to explain to the stewardess what you are doing in case other passengers think you are using a radio that might foul up airline communications. Your radio is similar to a tape recorder which would be permitted on board. ◇

**LEADER LAS-5500**  
**AUDIO SYSTEMS ANALYZER**  
**7 Instruments-In-One!**

**An extraordinary range of applications for every audio designer, engineer and technician who wants professional results**

<p><b>OSCILLOSCOPE</b></p> <ul style="list-style-type: none"> <li>● DC to 10MHz bandwidth; AC 2Hz-10MHz (-3dB)</li> <li>● 20mV/Div. vert. sens.</li> </ul>	<p><b>ATTENUATOR</b></p> <ul style="list-style-type: none"> <li>● 600Ω input/output impedance</li> <li>● 0.101dB attenuation range, ±2% accuracy</li> </ul>	<p><b>DRIFT METER</b></p> <ul style="list-style-type: none"> <li>● 3KHz ±0.1% test freq. source</li> <li>● 0.3Vrms signal output</li> </ul>	<p><b>WOW/FLUTTER METER</b></p> <ul style="list-style-type: none"> <li>● 3KHz ±10% and 3.15KHz ±10% range</li> </ul>
<p><b>AUDIO FREQUENCY OSCILLATOR</b></p> <ul style="list-style-type: none"> <li>● Frequency, 10Hz-1MHz, 5 ranges</li> <li>● &lt;0.5% distortion, 500Hz-20KHz and better.</li> </ul>	<p><b>AC MILLIVOLT METER</b></p> <ul style="list-style-type: none"> <li>● Reads as low as 30μV ranging to 100V, 12 steps</li> <li>● ±3% full scale accuracy</li> <li>● 5Hz-100KHz freq. resp</li> </ul>	<p><b>DUMMY LOAD</b></p> <ul style="list-style-type: none"> <li>● To 100W rated power.</li> <li>● 8Ω (L,R) impedance.</li> </ul>	<p>At \$1995, the LAS-5500 saves up to 50%... it's a smart investment!</p>

**LEADER Instruments Corp.**

151 Dupont Street, Plainview, N.Y. 11803 (516) 822-9300  
West Coast: 7733 Densmore Ave., Van Nuys, Calif. 91406 (213) 989-2760 In Canada: Omnitrax Ltd., Montreal, Quebec

CIRCLE NO. 34 ON FREE INFORMATION CARD

# FREE McIntosh CATALOG and FM DIRECTORY

Get all the newest and latest information on the new McIntosh Solid State equipment in the McIntosh catalog. In addition you will receive an FM station directory that covers all of North America.



## MX 113

FM/FM STEREO - AM TUNER AND PREAMPLIFIER


SEND TODAY!

McIntosh Laboratory, Inc.  
East Side Station P.O. Box 96  
Binghamton, N.Y. 13904  
Dept. PE

NAME \_\_\_\_\_  
ADDRESS \_\_\_\_\_  
CITY \_\_\_\_\_ STATE \_\_\_\_\_ ZIP \_\_\_\_\_

If you are in a hurry for your catalog please send the coupon to McIntosh.  
For non rush service send the Reader Service Card to the magazine.

CIRCLE NO. 35 ON FREE INFORMATION CARD

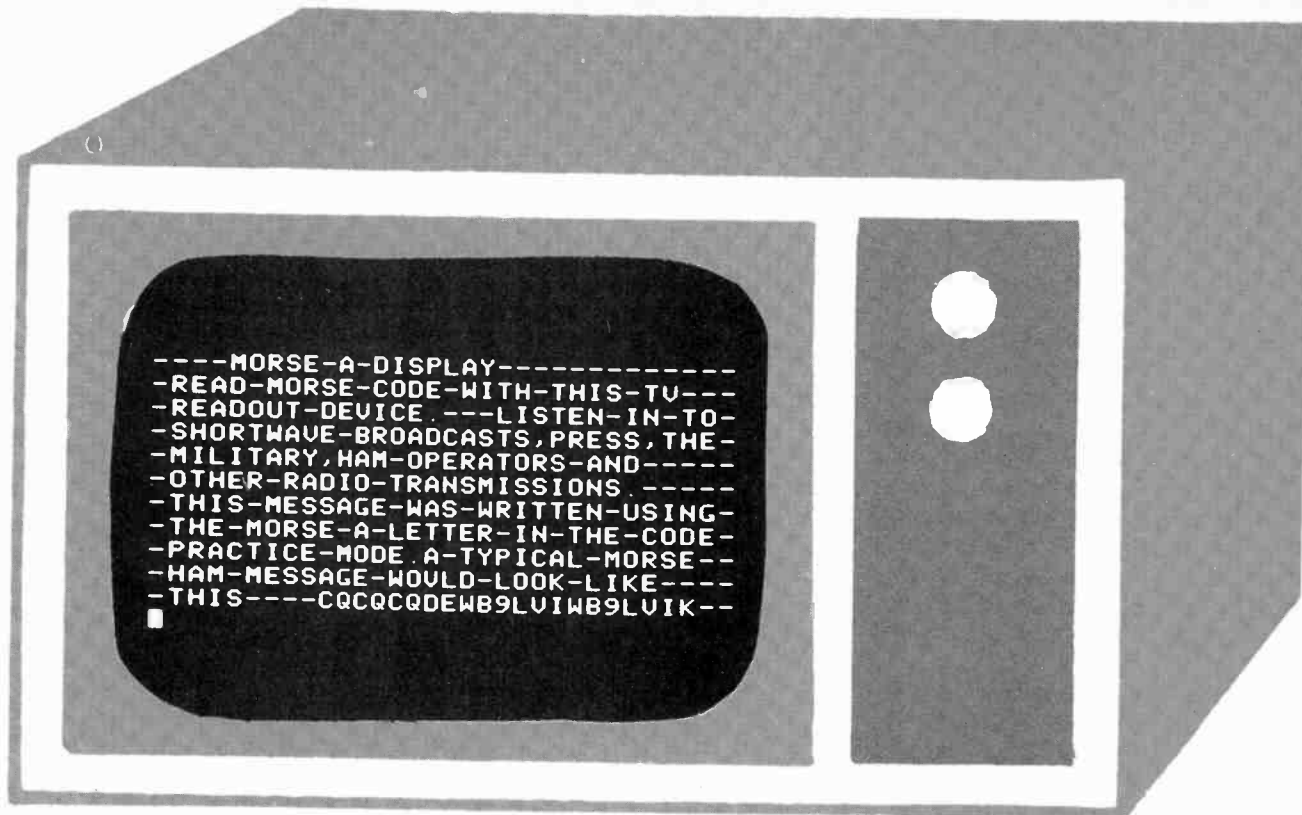

# MORSE CODE AUTOMATIC READOUT ON A TV SCREEN

*How to interface the Morse-a-Letter to a "TV Typewriter."*

BY GEORGE R. STEBER, WB9LVI

**A**LTHOUGH the Morse-A-Letter (January 1977) deciphers Morse code signals very effectively, its usefulness is somewhat limited by its single-character LED readout. At higher code speeds, the characters are displayed briefly, straining the operator's ability to copy down the entire text. However, it's easy to interface the Morse-A-Letter to a "TV typewriter." This combination, called "Morse-A-Display," will allow message display in page format—a boon to CW operators and SWL's interested in copying Morse.

Designed with this application in mind, the Morse-A-Letter contains all electronics necessary for converting dits and dahs to TTL-compatible ASCII-6 code. The required interface is simple and straightforward. All features of the original project are retained.

**ASCII.** Before examining the interface, let's review some basics of ASCII code. This will help us understand how the Morse-A-Letter/TV typewriter team op-

erates. ASCII is a standard 8-bit information code used with most computers and data terminals. It may be used in the parallel (all bits present simultaneously on separate lines) or serial (one bit at a time on a single line) mode. Most systems do not use the eighth bit of the code and it is, therefore, assumed to be a logic one at all times. Some systems, however, use the eighth bit for parity or error testing. The remaining seven bits provide a total of 128 possible charac-

ters. Of these, one group of 32 is reserved for the upper case alphabet and a few punctuation marks. Another group of 32 is used for numbers, spacing and additional punctuation symbols. Rarely used punctuation marks and a lower case alphabet are assigned a third group of 32. Finally, the last 32 combinations are assigned as machine or control commands. This group does not actually get printed but is provided to handle hardware operations such as line feed (LF) or carriage return (CR). If only upper case alphanumeric are needed, only the first two groups of 32 codes are required, and only six of the eight bits of the code are used. This diminutive ASCII code is called ASCII-6 and is essentially the code produced by the Morse-A-Letter. No control codes are produced by the Morse-A-Letter, however, so most "housekeeping" operations (line feed, carriage return, etc.) must be performed by the TV terminal. This does not present a real problem, since most TV terminals are programmed to handle

INTERCONNECTIONS	
Morse-A-Letter Connector	TV Terminal Connector
A13	Bit 7*
A21	Bit 6
A20	Bit 5
A19	Bit 4
A18	Bit 3
A17	Bit 2
A16	Bit 1
A14	Strobe
A1, A9	Ground

\* Optional, see text

these operations automatically in the absence of specific commands.

**Interfacing.** Almost any TV terminal capable of receiving TTL-level, 7-bit parallel ASCII code can be used with the Morse-A-Letter. Most terminals will work well with the ASCII-6 code without any changes or additions. However, some terminals require the presence of the seventh bit (B7—not to be confused with edge connector location B7) to produce a question mark (?), due to the method used to check control characters. If the seventh bit is required by your terminal, don't despair! It can easily be obtained because B7 is merely the complement of B6 for the 41 valid ASCII characters produced by the Morse-A-Letter. This modification requires a small amount of additional wiring on the Morse-A-Letter circuit board. Fortunately, no additional parts are needed since an unused inverter (actually one half of IC5, a 7413 dual NAND Schmitt Trigger) is already "on the board."

To generate bit 7, connect a wire from B6 of the ASCII output (edge connector location A21) to pin 13 of IC5. Also, connect a wire from pin 8 of IC5 to edge connector location A13. This becomes B7 of the ASCII code. Keep in mind that

many TV terminals will function adequately with just the ASCII-6 code, so this addition may be optional.

The TV terminal will normally require a "data ready" signal to tell it when an ASCII character is applied to its input connector. This signal is also sometimes referred to as a "keypressed strobe" or "new character" pulse. It is usually a positive going pulse that appears whenever the ASCII character is ready to be entered. The Morse-A-Letter provides this new character pulse in the form of a positive going pulse at edge connector location A14, which is generated every time a new Morse character is received.

A word of caution is in order. If your terminal does not utilize TTL levels at the ASCII input connector and/or requires a negative-going strobe pulse, an additional interface is needed.

As an example of an interface, the Table lists the wiring requirements for interfacing the Morse-A-Letter to the Southwest Technical Products CT-1024 Terminal, which has a TTL-compatible input and a positive strobe line. All that's required is connecting a suitable cable from the appropriate points on the Morse-A-Letter connector to the TV terminal connector. Note that no power supplies or additional electronics are

necessary. Most other TV terminals will interface in a similar manner.

**Operation.** There are no adjustments required for the Morse-A-Display other than the normal code speed adjustment. It will function in either the code practice or the reception mode. Once a signal is properly tuned in, the television display will read out the incoming characters directly on the television screen. Illegal Morse characters will be displayed as "@" Noisy signals may generate strings of "E"s or "T"s on the screen, but this is normal. Do not expect to view perfectly edited copy since word spaces are rarely sent in Morse code and the Morse-A-Display is not designed to decode them. This is not a serious handicap, however, and with a little practice you will be able to read complete messages from the screen. To copy high-speed Morse, it might be desirable to reduce the Morse-A-Letter's C9 from 6.8 microfarads to 2.0 microfarads in the original circuit. This reduces noise immunity slightly, but enables copy at code speeds up to 50 WPM or more.


Remember it is illegal to pass information garnered from ship-to-shore, military, or press transmissions to third parties. ◇

## SCORE 2 WAYS WITH MARK TEN B AND ...

You can add real zip to engine performance and eliminate the need for 3 out of 4 tune-ups with a Mark Ten B Capacitive Discharge Electronic Ignition. Over a million happy, satisfied users testify to the fact that the Mark Ten B really does:

- Eliminate 3 out of 4 tune-ups.
- Improve gasoline mileage—up to 20%.
- Give dramatic increases in acceleration and general performance.
- Extend spark plug life 3 to 10 times.
- Give instant all weather starts.

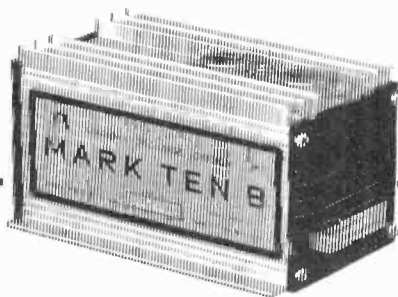
Put spark under the hood and score with *real* performance!


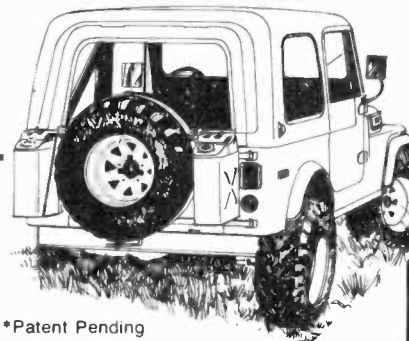
## DELTA'S MOUNTAIN MAN SADDLE BAG CAN AND ACCESSORY CARRIER\*

The only carrier with truly innovative engineering, Delta's Mountain Man Carrier installs *without drilling a single hole*. A completely unique concept, it forms the basic unit of the first modular system ever devised to carry a variety of accessories. Look at these great features:

- Versatility: use alone with one or two jerry cans, or use with other Mountain Man accessories. (Sorry, cans not included.)



\*Patent Pending

- Fits all externally mounted 14", 15" and 16.5" tires.
- Easy installation; all you need is a wrench.
- Made of rugged 11 gauge steel for strength and durability.

Winner of PV4 Magazine's 1976 Product Of The Year Award, it will score on your 4WD, van, pickup, or mini, and it's a steal at only \$39.95 F.O.B.


**DELTA PRODUCTS, INC.**  
One Delta Way, Dept. PE, Grand Junction,  
Colorado 81501 (303) 242-9000

Please send \_\_\_\_\_ Saddle Bag Carrier(s) @ \$39.95 F.O.B.  
 Check enclosed. Charge my  Master Charge  
 BankAmericard

Credit Card # \_\_\_\_\_  
Interbank No. \_\_\_\_\_ Exp. Date \_\_\_\_\_  
(Master Charge only) Mo. Year

- I have enclosed \$2.00 for my complete Mountain Man catalog (to be applied toward my first purchase).
- Please rush free brochure on Mark Ten CDI Systems.

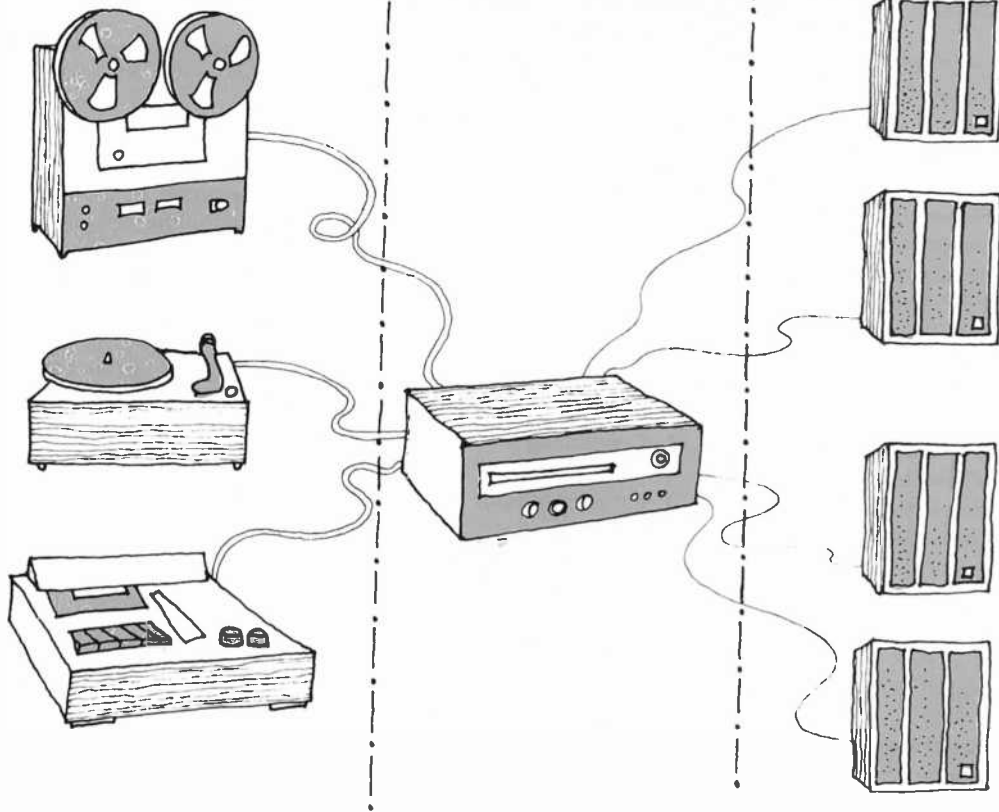Name \_\_\_\_\_  
Address \_\_\_\_\_  
City \_\_\_\_\_ State \_\_\_\_\_  
Phone \_\_\_\_\_ Zip \_\_\_\_\_



# HOW TO MATCH HI-FI COMPONENTS

Price tags serve as a good guide to apportioning dollars for each component.

**M**ATCHING hi-fi components of a stereo or four-channel system means that each component must operate compatibly with each other.

For example, your loudspeakers should be efficient enough to deliver satisfactory sound levels—especially in the low bass region—when driven by the amplifier or receiver of your choice. Yet, they should have sufficient power-handling capacity to avoid damage if driven by too much power.

In another sense, compatibility also means that one component should not have substantially better performance

than another component in the system. It would be foolish, for example, to have a \$300 single-play turntable, \$800 receiver, and two speaker systems at \$500 each and then add a \$19.95 phono cartridge. The latter's electrical/mechanical performance would be well below that of the other components in the system. As a result, one would not get the full performance capability inherent in the better components. Remember that the final reproduced audio will sound only as good as the weakest component link in the system.

One can often ignore electrical and

mechanical considerations at the onset of rounding up his choices, however, by viewing compatibility in terms of each component's price tag. Thanks to competition among manufacturers, the quality of each type of component varies almost directly in relation to its price (although exceptions can always be found to virtually any generalization).

Most newcomers to component hi-fi (and some experienced audiophiles, too) have little or no idea of how to apportion their dollars to the various components they plan to buy.

Many audio dealers try to simplify this

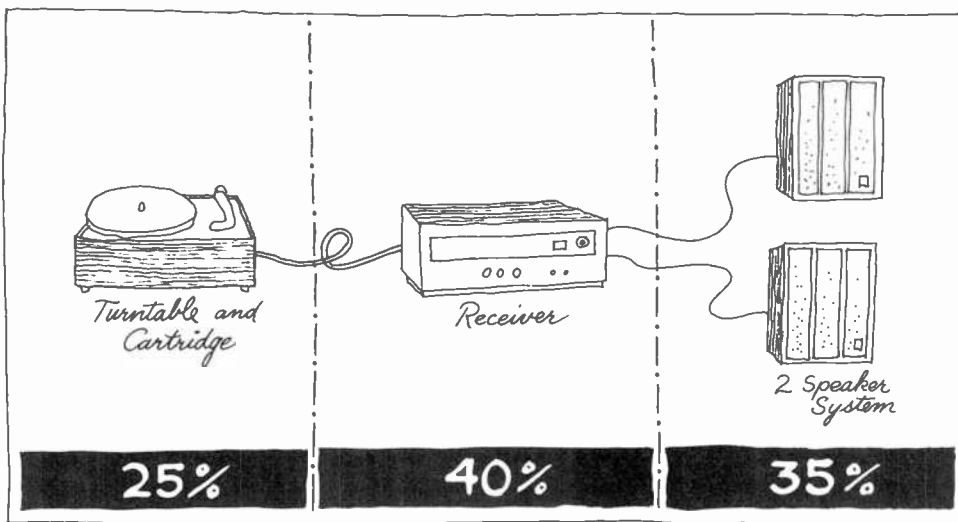


Fig. 1. Apportioning dollars to a stereo receiver/turntable/speaker system.

problem by "assembling" pre-selected components into a complete system. Such systems usually bear a single price tag and offer significant savings over the prices of the individual components added together. There are both advantages and disadvantages in choosing such a dealer-selected system. Certainly, if the dealer is knowledgeable and reputable, you are at least

assured that the components which have been put together in this way will work compatibly with each other—and the savings in making a single purchase from one source are often worthwhile. On the other hand, you may have different ideas about which components you think sound better with which other components. Consequently, your dream system may not be represented by any

of the pre-selected groupings offered by the dealer.

In addition, it is common practice for some dealers (but not all) to have loud-speaker systems "custom designed" by local manufacturers who are essentially cabinet makers rather than speaker system designers. Since such speakers are rarely advertised nationally, almost any "suggested retail price" can be assigned

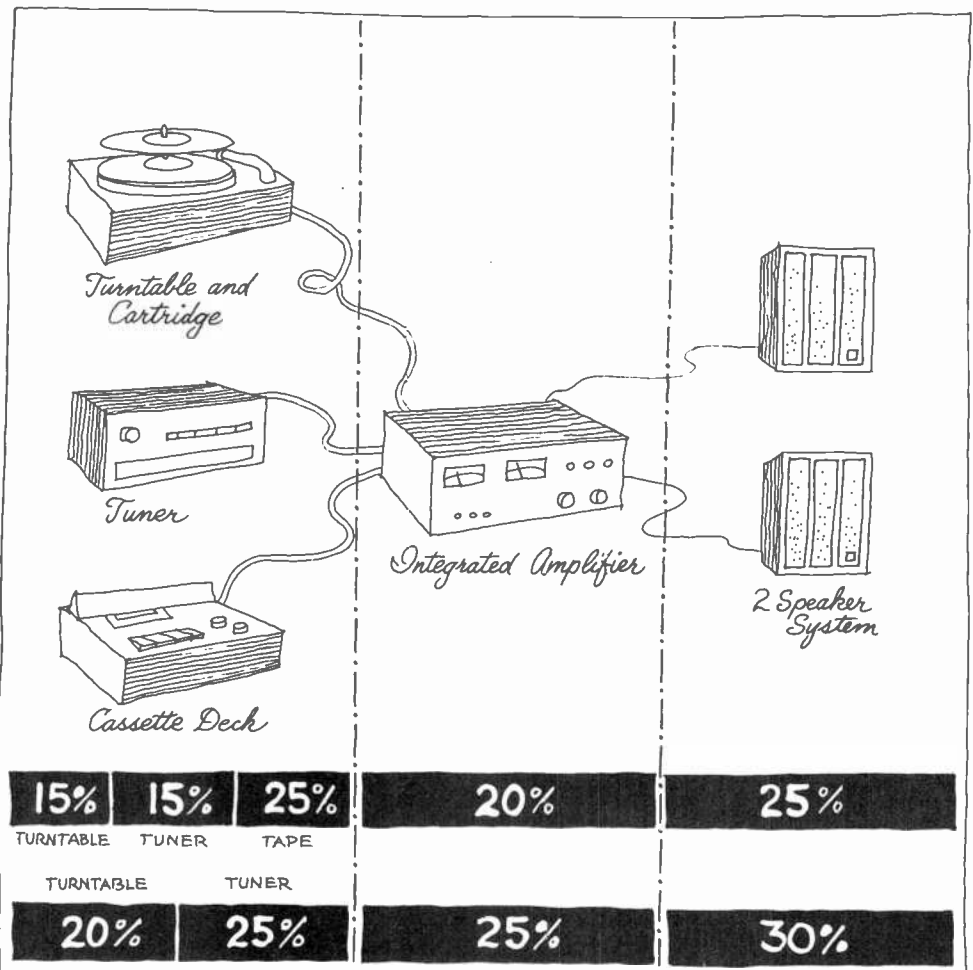


Fig. 2. Percentage of dollars to be spent on components for a system including tuner and cassette deck.

to them. In such instances, the "savings" shown in the final system price tag may actually be the result of reducing these speaker prices to more realistic levels. (This practice is not universal, of course.) What we are suggesting is that each component in such systems be analyzed and evaluated for its own mer-

fast rules; these are simply rough guidelines. In the system shown, any tape equipment would be considered extra and is not included in the initial percentage breakdown.

Suppose you decided to include a cassette deck as part of your initial hi-fi investment, and that you prefer to have

quality. In Fig. 3 we have represented a typical quadraphonic system centered around a 4-channel receiver. Again, percentages are shown below for each element of the system. If we assume that you are prepared to spend \$3000 for such a system (note that it includes both an open-reel tape deck and a stereo

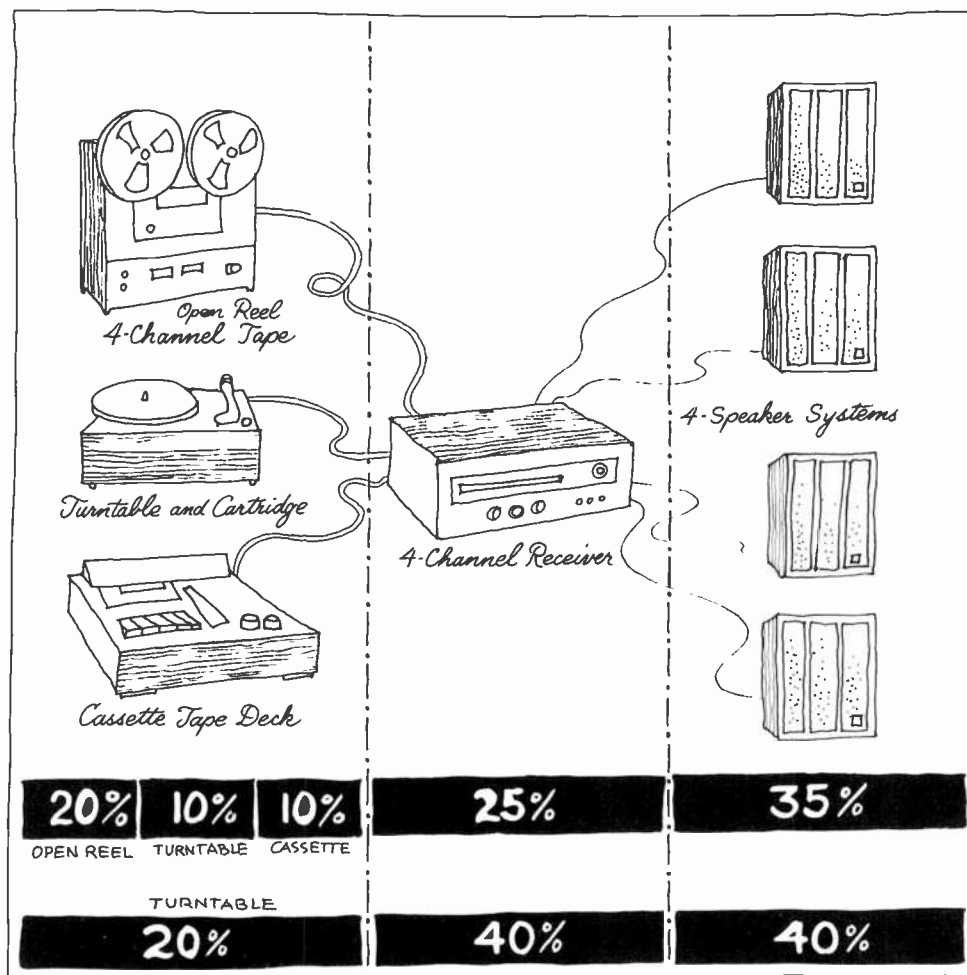


Fig. 3. How dollars should be apportioned for a four-channel system with open-reel and cassette decks.

its and performance—for that is the essence of shopping for components for your own high-fidelity system.

**Apportioning Hi-Fi Dollars.** By far the greatest number of high fidelity stereo component systems consist of an all-in-one receiver, a turntable system (either single-play or multiple-play) and a pair of loudspeaker systems. This basic layout is shown in Fig. 1. Below it is a typical cost breakdown in percentages of available dollars. As an example, if you have \$500 to spend on such a basic system, you might consider a turntable (including the phono cartridge, which is usually purchased separately) selling for approximately \$125, a \$200 receiver and two speakers for about \$87.50 each. There are, of course, no hard-and-


a separate tuner and an integrated amplifier (preamplifier-amplifier combination) instead of a receiver. Your system might then look something like that shown in Fig. 2, with the percentages spent for each component given below. Since such a system is necessarily more expensive than the simpler, 4-piece arrangement, let's start with a budget of \$1000. You might spend \$150 for a turntable and cartridge, \$150 or so for a separate FM/AM tuner, \$250 for a cassette deck with Dolby, \$200 for an integrated amplifier and perhaps \$125 for each of your two speaker systems. If the tape deck is eliminated for the moment, percentages could be reassigned as shown in the lower percentage table.

Quadraphonic systems necessarily cost more than stereo systems of equal

cassette unit) your dollars might be apportioned as follows: \$600 for the open-reel deck, \$300 for the cassette deck and a similar amount for the turntable/cartridge combination (you will need a cartridge designed to play CD-4 records this time), \$750 for the 4-channel receiver and \$262.50 for each of the four speakers in the system. If you were to omit the tape decks and had only \$2000 to spend, the lower percentage table in Fig. 3 suggests that you might spend \$800 on the 4-channel receiver, \$200 for each of the four speakers needed, and up to \$400 for the turntable/cartridge combination.

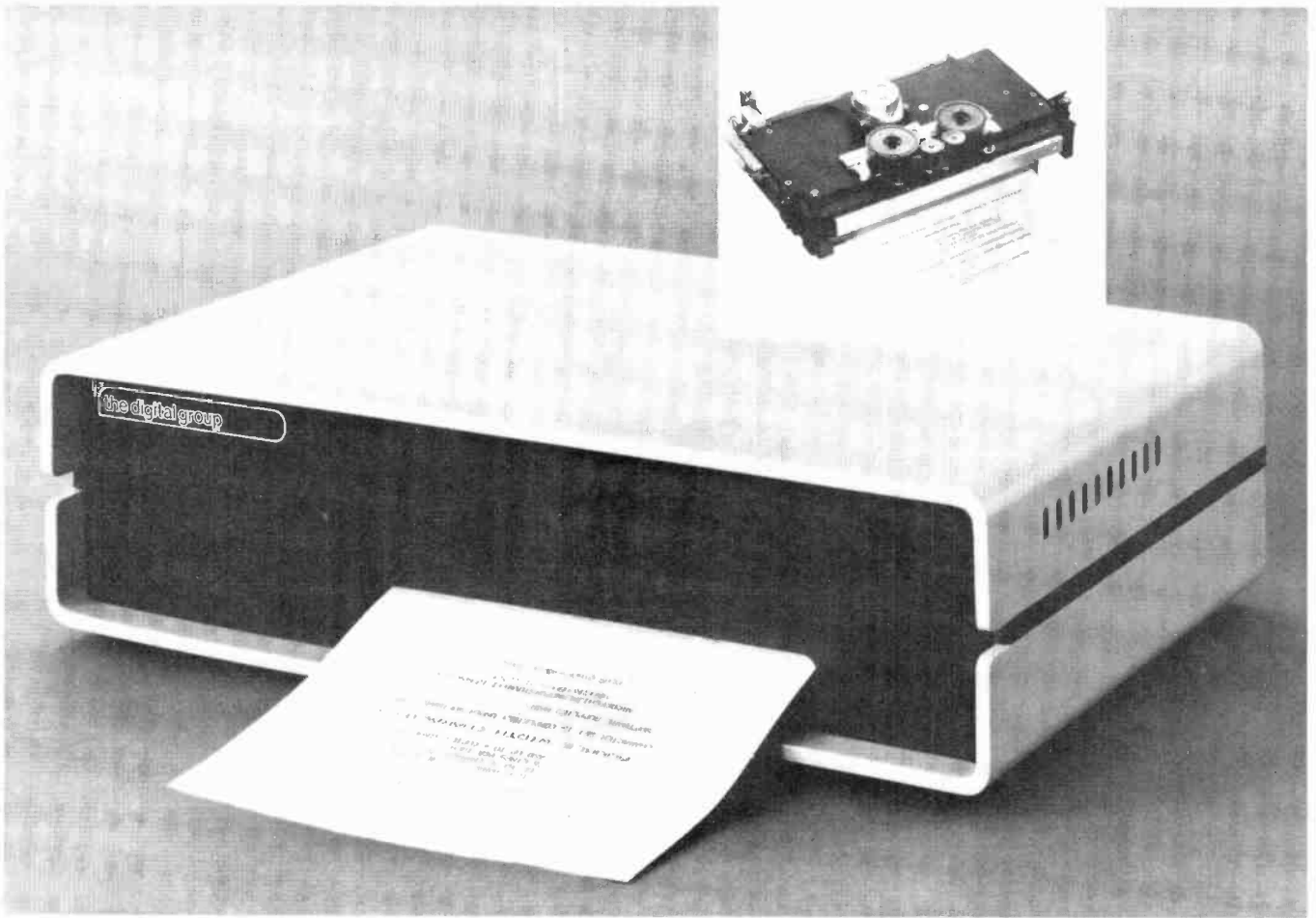**Specs To Expect.** Although specifications are certainly not the only criterion involved in making an intelligent





# Print Your Heart Out.

With help from the Digital Group, naturally.

Now, that small computer system you own or have been considering for personal or business use suddenly becomes a lot more usable—with the addition of a full-size impact printer from the Digital Group. A printer designed for small computers that need big output (like yours).

With the Digital Group printer, you can print your heart out...and it won't cost an arm and a leg. The Digital Group printer is available for less than \$500. That's right—\$500.

#### Just look at these specifications:

- Fast—120 characters per second
- 96 characters per line
- 12 characters per inch horizontal
- 6 lines per inch
- Makes up to 4 copies simultaneously
- Character set and pitch variable under software control—double width characters, etc.
- 5 x 7 character matrix
- Ribbon has built-in re-inkers for a life of 10,000,000 characters
- Paper can be either a standard 8½-inch roll, fanfold or cut page
- Interfaces to 8-bit parallel ports

There are lots of capabilities and outstanding features of the Digital Group printer...and (as always) the best news is our price. Kit prices start as low as \$495 for the printer and interface card. It simply can't be beat.

Find out all the facts about the Digital Group printer now. Just fill in the coupon below or give us a call for the details. We think you'll find a place for our printer in your system...and in your heart.

-----  
the digital group

P.O. Box 6528  
 Denver, Colorado 80206  
 (303) 777-7133

Quick. I want to print my heart out.  
 Send me all the details on your full-size impact printer.

Name \_\_\_\_\_

Address \_\_\_\_\_

City/State/Zip \_\_\_\_\_

Please print.

# Be the “New Professional” in electronics

**CREI trains you at home  
for one of the most important  
career levels in electronics—  
plus offers you special  
arrangements for engineering  
degrees**

Most people think there are only two levels of careers in electronics: the technician level and that of the degree engineer.

There is, however, a third and very important level. It is that of the engineering technician or *practical* engineer. The growing importance of this career level has created what might well be called the “New Professional” in electronics.

If you look at the various levels of employment in electronics, you will understand why this “New Professional” is so important.

The average technician is a person who has had vocational training in electronics. He understands the basic principles of electronics so he can troubleshoot, repair and maintain equipment. He usually works under close supervision in performing his duties.

The engineer has college training in electronics. He usually supervises technician personnel and is responsible for planning and developing of electronic equipment and systems. Frequently, however, engineers are more heavily trained in the scientific principles of electronics and less in their practical application.

The engineering technician, by contrast, is a specialist in the practical application of electronics. His training usually consists of a two-year college program in electronic engineering technology. In many organizations, the engineering technician handles several of the responsibilities of the degree engineer. He often has the title of engineer.

CREI programs are designed to give you at home the same level and depth of training you receive in a two-year college program in electronic engineering technology. CREI programs are, in fact, more extensive than you will find in many colleges. And CREI gives you the opportunity to specialize in your choice of the major fields of electronics.

## **Unique Design Lab**

CREI gives you both theory and practical experience in circuit design with its Electronic Design Laboratory Program. The professional equipment included in this program allows you to construct, test out and correct the circuits you design until you have an effective circuit.

This Lab Program helps you understand advanced electronics. It also gives you practical experience in many other important areas of electronics, as in pro-

# Career Training at Home

totype construction, breadboarding, test and measurement procedures, circuit operation and behavior, characteristics of electronic components and how to apply integrated circuits.

Only CREI offers the unique Lab Program. It is a complete college Lab and, we believe better than you will find in most colleges. The "Lab" is one of the factors that makes CREI training interesting and effective. And the professional equipment in this program becomes yours to keep and use throughout your professional career after you complete the training.

## Engineering Degree

CREI offers you special arrangements for earning credit for engineering degrees at certain colleges and universities as part of your home study training program. An important advantage in these arrangements is that you can continue your full time job while "going to college" with CREI. This also means you can apply your CREI training in your work and get practical experience to qualify for career advancement.

## Wide Program Choice

CREI gives you a choice of specialization in 14 areas of electronics. You can select exactly the area of electronics best for your career field. You can specialize in such areas as computer electronics, communications engineering, microwave, CATV, television (broadcast) engineering and many other areas of modern electronics.

## Free Book

In the brief space here, there isn't room to give you all of the facts about CREI college-level, home study programs in electronics. So we invite you to send for our free catalog (if you are qualified to take a CREI program). The catalog has over 80, fully illustrated pages describing your opportunities in advanced electronics and the details of CREI home study programs.

## Qualifications

You may be eligible to take a CREI college-level program in electronics if you are a high school graduate (or the true equivalent) and have previous training or experience in electronics. Program arrangements are available depending upon whether you have extensive or minimum experience in electronics.

MAY 1977

# Send for this FREE Book describing your opportunities and CREI college-level programs in electronics



Mail card or write describing qualifications to

**CREI** **CAPITOL  
RADIO  
ENGINEERING  
INSTITUTE**

**McGraw-Hill Continuing Education Center  
3939 Wisconsin Avenue Northwest  
Washington, D.C. 20016**

**Accredited Member National Home Study Council**

## GI Bill

*CREI programs  
are approved  
for training of  
veterans and  
servicemen under  
the G.I. Bill.*



to the first NAND gate, as shown, or the two inputs may be tied together for continuous operation.

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_  
Phone Number \_\_\_\_\_

CIRCLE NO. 29 ON FREE INFORMATION CARD

MAY 1977

77

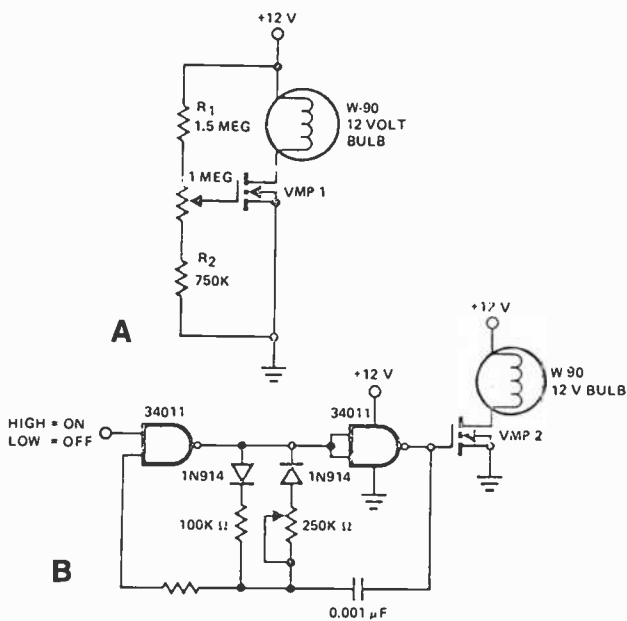


Fig. 3. VMOS light dimmer circuits: (A) Continuous (analog) control; (B) Pulse-width switched type.

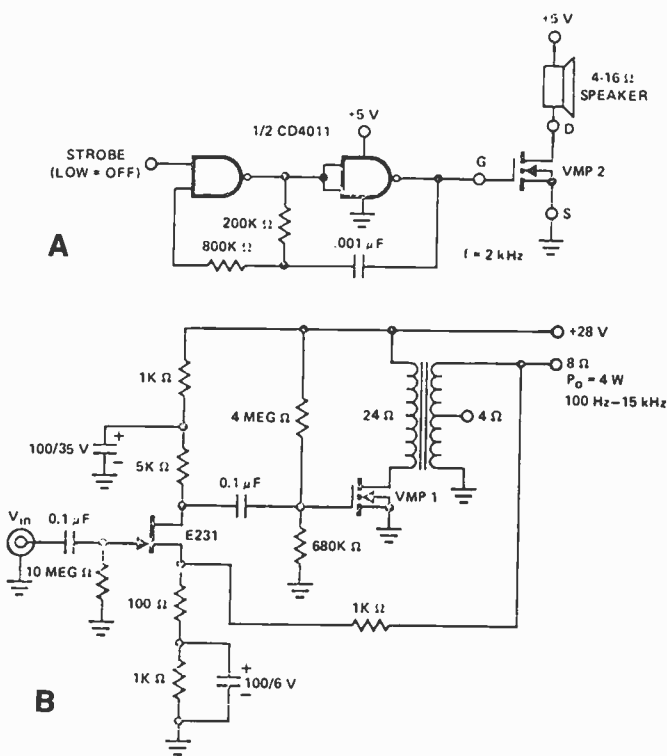


Fig. 4. VMOS audio circuits: (A) Alarm; (B) Class A amplifier.

Two of many possible audio circuit applications for VMOS transistors are illustrated in Fig. 4. The first, Fig. 4A, is a simple sound source which may be used in intrusion and fire alarms or similar projects. The design features a NAND gate oscillator similar to the one used in the second lamp dimmer circuit, with the VMOS transistor serving as a power driver for a PM loudspeaker.

The second, Fig. 4B, employs a single VMOS transistor as a Class A linear power amplifier in conjunction with a JFET preamp stage. Suitable for use in radio receivers, TV sets,

record players, intercoms, and low-power PA installations, the circuit can deliver 4 watts to a suitably matched loudspeaker load and has a reasonably flat frequency response from 100 Hz to 15 kHz. Overall distortion is kept to within 2% (at 3 W output) by 10 dB of inverse feedback provided by a 1-k resistor between the output and the preamp's source electrode. A 28-volt dc supply is required.

With their fast switching characteristics, VMOS transistors are suitable for many high-frequency projects. A typical linear vhf amplifier circuit is illustrated in Fig. 5. Designed for operation in the 144-to-146-MHz band, the design may be used in both transmitter and receiver applications. As a transmitter power amplifier, the stage has a minimum power gain of 12 dB and can deliver 5 W PEP at 146 MHz. If used as a receiver r-f preamp, the design can furnish 11 dB gain with a low noise factor of only 2.4 dB. All resistors are half-watt types and the coils are hand-wound, with  $T1$  consisting of 8 turns of #24

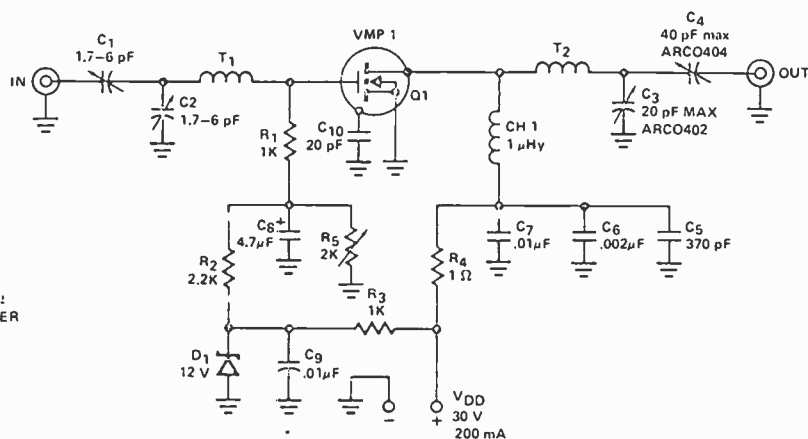


Fig. 5. Vhf linear amplifier using a VMOS transistor.

AWG, 1/8-in. diam., close-wound, and  $T2$  of 5 turns of #24 AWG, 1/8-in. diam., close-wound. In common with most vhf designs, careful layout and proper lead dress during assembly are essential for optimum circuit performance.

A further example of the VMOS transistor's versatility is found in the high-power audio amplifier circuit shown in Fig. 6. Of potential interest to audiophiles and more advanced experimenters, the design is suitable for use in high-quality stereo or quadraphonic systems. Capable of delivering 40 watts to an 8-ohm load, the amplifier has an essentially flat closed-loop frequency response (exclusive of the r-f input filter) from 1 Hz to 1 MHz and a slew rate of better than 100 V/μs. Its total harmonic distortion at 1 kHz, full rated output, is less than 0.05%. Featuring a Class AB quasi-complementary push-pull output stage using three paralleled VMOS transistors in each arm, the circuit is described in detail in Siliconix Design Aid DA76-1, *The MOSPOWER™ FET Audio Amplifier*. In addition to the schematic diagram and a suggested dc power supply circuit, the 4-page publication includes pc board and chassis layouts, response curves, signal waveforms, construction and adjustment hints, and a detailed parts list.



**Reader's Circuit.** Both early and contemporary design concepts are combined in the interesting AM broadcast band receiver circuit illustrated in Fig. 7. Submitted by William J. Wolf (3543 Dubarry Rd., Indianapolis, IN 46226), the circuit features a *reflex* front-end, an IC op amp audio amplifier and a Darlington power output stage. Old timers probably will re-


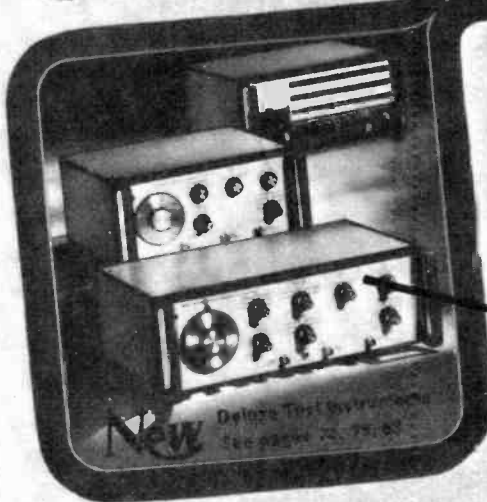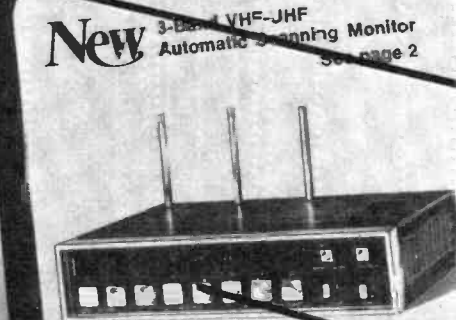
# Heathkit®

SPRING 1977

Heathkit products are known world-wide for quality, performance and VALUE. And no matter what your interest — there's a kit that's just right for you. Every Heathkit product comes with a thorough step-by-step assembly manual that leaves nothing to chance, and all our kits are backed by our famous "We won't let you fail" pledge. See all the exciting electronic products YOU CAN BUILD YOURSELF right here in this catalog.



HEATH  
MAIL ORDER CATALOG

"Heath" and "Heathkit" are registered trademarks of Heath

© 1977 Heath Company  
See index on page 3

Heath Company, Dept. 10-29  
Benton Harbor, Michigan 49022  
POPULAR ELECTRONICS

# FREE!

Some of the most exciting electronic kits ever to come along are described in this **NEW Heathkit Catalog**.

## NEW! AS-1348 deluxe Three-Way Speaker System

Our biggest and best speaker system is designed for use with the finest stereo components! Has a massive 15" woofer for bass response all the way down to 20 Hz; dual 4½" midrange speakers for twice the power handling at the important middle frequencies, and a three-tweeter array that maintains dispersion and stereo image throughout any listening area. The AS-1348 provides "live performance" sound levels at ALL audible frequencies.

## NEW! Electronic Circuits Learn-at-Home Course

The latest in our series of programmed learning courses — the Electronic Circuits Course provides an explanation of most common circuits and gives you the "hands-on" experience you need for circuit design and development. Covers amplifiers, power supplies, oscillators, pulse circuits, modulation and demodulation with emphasis on integrated circuits. Includes text material, audio records and 110 electronic parts for 18 different experiments with the optional electronic trainer.

## NEW! GR-1132 3-Band VHF/UHF Automatic Scanning Monitor

Listen to ALL the action — automatically! Covers any combination of 8 crystal-controlled channels in the 30-50 and 146-174 MHz VHF bands, and 450-500 MHz UHF band, for police, fire, ambulances, Amateur 2-meter FM, marine, emergency vehicles, U.S. Gov't weather stations and more. Has extra-large lighted channel indicators, priority channel feature and channel lockout buttons, built-in antenna for all three bands, provision for external antenna. Built-in speaker, volume and squelch controls.

## NEW! CI-1096 Deluxe Auto Timing Light with built-in Tachometer and Advance

The fast, easy way to keep tabs on your car's engine timing and distributor advance functions for smoother operating and better fuel economy. Single, compact unit houses a timing light, advance meter and tachometer. Measures up to 60° mechanical or vacuum advance from 1500 to 4500 RPM and indicates engine speed to 4500 RPM. Bright xenon flash tube lets you set timing even in daylight. Inductive pickup snaps around #1 sparkplug wire for easy hookup.

## NEW! Advanced Test and Service Equipment

Three new test instruments will bring advanced service capability to any test or hobby bench. The IG-1275

is a deluxe Swept-Function Lin/Log Generator. The IG-1273 is a voltage-controlled Lin/Log Generator, and the IG-1272 is a low-distortion audio frequency oscillator perfect for audio testing. All three offer professional performance and specifications at low kit-form prices.

PLUS nearly 400 other superb, easy-to-build, money-saving products. You'll find a complete line of digital electronic clocks and weather instruments, plus useful and unique items for your car, home or office.

Our learn-at-home courses are now in use by the thousands! A really effective and low-cost way to teach yourself about electronics for fun, for knowledge, or for profit. We also have a wide selection of popular books covering almost everything in electronics.

There are many more exciting products to read about too! Home convenience items like a practical freezer alarm, a touch-control light switch, intercoms and a unique programmable doorbell. Automotive instruments and accessories, marine equipment, model aircraft Radio Control gear, security systems and more. Plus our world-famous Amateur Radio equipment and test and service instruments.

These are among the nearly 400 quality, fun-to-build kits described in this new Heathkit catalog. Kits for every interest. All with the world-famous Heathkit assembly manual — a step-by-step instruction guide that makes kitbuilding easy and leaves nothing to chance. And all backed by our "We won't let you fail!" promise. Find out about the satisfaction, savings and FUN of kitbuilding.

Send for your  
**FREE copy today!**

HEATH <b>Schlumberger</b>	Heath Company, Dept. 10-29 Benton Harbor, Michigan 49022
Please send me my FREE Heathkit Catalog. I am not on your mailing list.	
Name _____	
Address _____	
City _____	State _____
Zip _____	
CL-632	

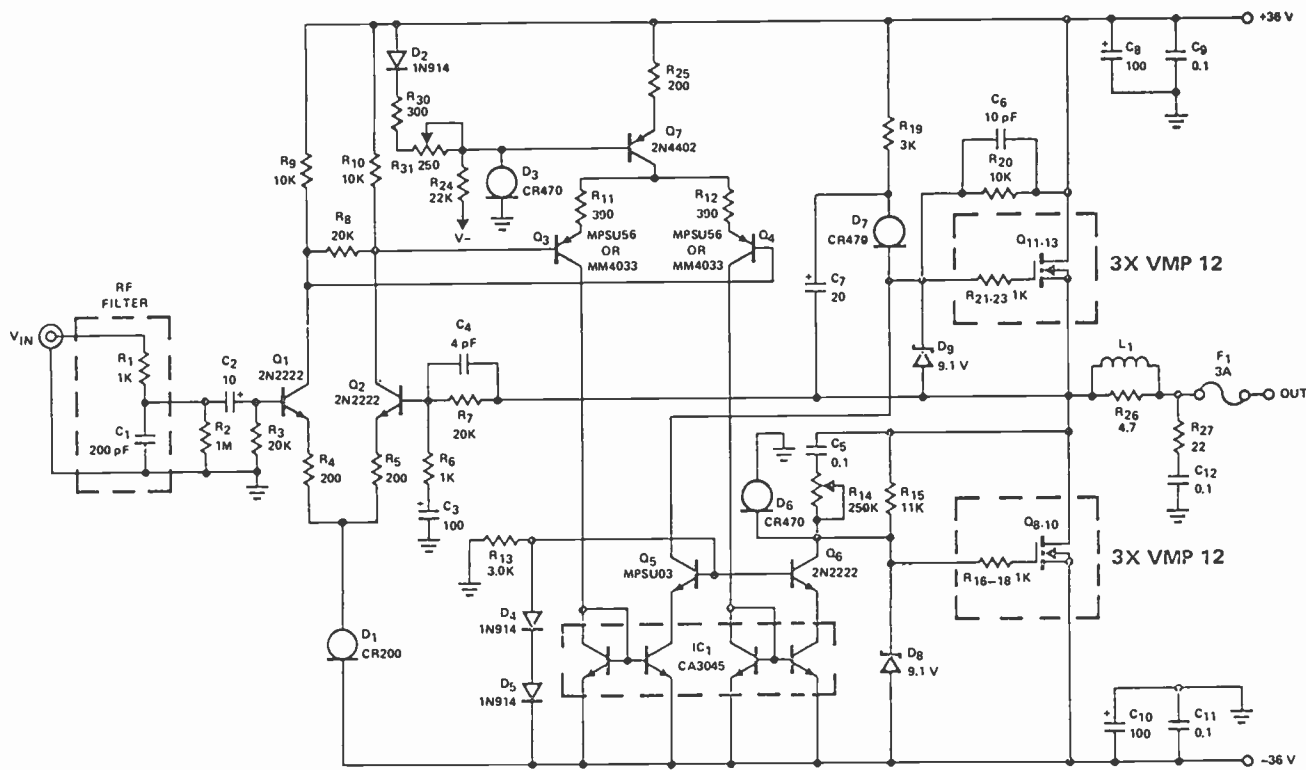


Fig. 6. 40-watt audio amplifier featuring a VMOS transistor output stage.

member the reflex circuit concept with a touch of nostalgia. Popular in the early to middle 50's, when good quality r-f transistors cost as much as fifty dollars each (pre-inflation dollars, at that!), the reflex circuit permits a single device to amplify two different signals—r-f and audio—*simultaneously*.

In operation, r-f signals picked up and selected by tuned circuit L1-C1 are applied to Q1, serving, initially, as an r-f amplifier. An amplified signal is developed across r-f collector load L2 and coupled through C3 to a detector network consisting of D1, R2, D2 and r-f bypass C2. The resulting demodulated (audio) signal *also is applied* to Q1, now serving as an audio amplifier and developing an amplified signal across the audio collector load, T1's primary winding. The RFC (L2) acts virtually as a short as far as audio signals are concerned. The audio signal is next coupled through gain control R3 and dc blocking capacitor C4 to op amp IC1, which serves to drive the final power output stage, Darlington connected pair Q2-Q3. A PM loudspeaker, shunted by R9, serves as the output load. Inverse feedback is provided across the power output and driver stages through R8 to minimize distortion and optimize over-

all performance. Reflex amplifier (Q1) base bias is furnished through R1, the op amp's offset biases through R5 and R6 with, finally, the Darlington receiving its base bias directly from IC1 through current limiting resistor R7, bypassed by C6. Circuit operating power is supplied by B1, controlled by S1.

Except for the hand-wound loop antenna coil, L1, William has specified standard, readily available components in his design. Transistor Q1 is a general purpose pnp device similar to Radio Shack's type RS-101, IC1 is one section of an inexpensive type LM3900 quad op amp, Q2 and Q3 are hobby-grade type 2N3055 npn power transistors, and D1 and D2 are general-purpose diodes similar to types 1N34 or 1N60. A 2.5-mH RFC is used for L2, while T2 is a small 10-k to 2-k inter-stage audio transformer similar to Radio Shack's No. 273-1378. Tuning capacitor C1 is a standard 365-pF unit and all other capacitors are low-voltage disc ceramics except for C4, which is a 15-volt electrolytic. The fixed resistors are all one-quarter or one-half watt types. Any standard PM loudspeaker with an 8- or 16-ohm voice coil may be used as the output device. The power switch, S1, is a spst toggle, slide or

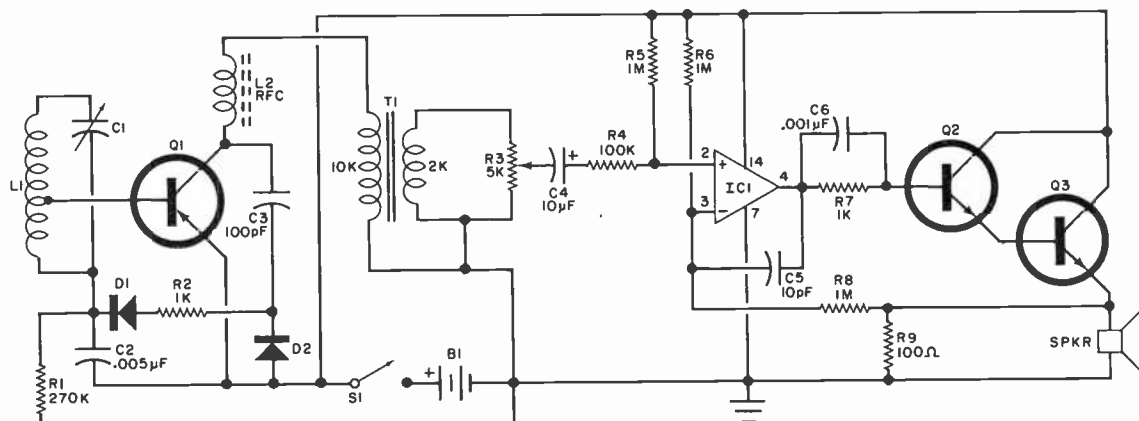


Fig. 7. Broadcast band receiver has reflex front end and IC op amp audio amplifier.



rotary type, with the power pack, *B1*, made up of six series-connected size "C" or "D" flashlight cells. William describes *L1* as a loop antenna consisting of 16 turns of #22 solid copper insulated hook-up wire tapped at 12 turns and close-wound on a wooden frame measuring 10 in. high by 13 in. long by 3 in. wide.

Although neither layout nor lead dress should be critical when duplicating the circuit, good wiring practice should be followed, with signal carrying leads kept short and direct, heat sinks provided for the power transistors (*Q2* and *Q3*), and all dc polarities observed. The reader suggests that the entire circuit, including the loudspeaker and power pack, can be assembled conveniently within the wooden frame supporting the loop antenna. Depending on *Q1*'s individual characteristics, some experimentation with *R1*'s value may be required for optimum performance. Some hobbyists also may wish to experiment with the number of turns on the loop antenna coil or with *C1*'s value to obtain coverage of other radio bands. If desired, a multiple tapped coil and suitable selector switch can be provided for multi-band operation.

**Device/Product News.** Suitable for use in instruments, audio systems, controls, and similar analog applications, a new low-cost dual operational amplifier with a unity gain bandwidth over 2.5 MHz has been introduced by *Motorola Semiconductor Products, Inc.* (P.O. Box 20912, Phoenix, AZ 85036). Designated types MC4558/MC4558C, the new devices are offered in round metal cases as well as in ceramic and plastic 8-pin MiniDIP's. Internally compensated, the new op amps feature a typical large-signal voltage gain of 200 V/mV at 25°C and a CMRR of 90 dB. The two amplifiers within each package are closely matched with respect to both gain and phase, and both are protected against load short circuits.

If your requirements are for a quad rather than dual unit, you should be interested in the RC/RM4156 announced recently by *Raytheon Semiconductor* (350 Ellis St., Mountain View, CA 94040). Supplied in plastic or ceramic 14-pin DIP's, the op amps are short-circuit protected and feature a minimum unity gain bandwidth of 2.8 MHz.

The *Fairchild Camera and Instrument Corp.* (LSI Group, 464 Ellis St., Mountain View, CA 94042) is now offering a new dynamic bipolar 4096-bit random access memory (RAM) designed for operation on a single 5-V dc supply. Two versions of the new RAM are in production. Both are organized as 4096 × 1 bits and have a power consumption of 350 mW active, 70 mW standby, and 500 mW in page mode. The standard 93481 has a maximum access time of 120 ns with a 280-ns cycle time, and a page mode access and cycle time of 75 ns. The faster version, type 93481A, has a maximum access time of 100 ns with a 240-ns cycle time, and a page mode access and cycle time of 65 ns. Manufactured using Fairchild's Isoplanar Integrated Injection Logic process, the new RAM's are TTL compatible and are supplied in standard 16-pin ceramic DIP's.

*National Semiconductor Corp.* (2900 Semiconductor Drive, Santa Clara, CA 95051) has developed a new single-chip IC containing a pair of monolithic npn transistors matched to within 50 μV of each other. Identified as type LM194, the matched pair has a noise figure so low that it is virtually immeasurable and features a minimum current gain of 500, a current-gain match of better than 2%, a CMRR of better than 120 dB, and a low drift of less than 0.1 μV/°C. With a maximum collector-emitter voltage rating of 40 V and a maximum power dissipation of 500 mW, the LM194 is supplied in a 6-lead TO-5 style metal case. ◇

## MIND-ABSORBING PROJECTS FOR ELECTRONIC EXPERIMENTERS AND HOBBYISTS



1977  
ELECTRONIC  
EXPERIMENTER'S HANDBOOK

Helps you get it together  
with a score of  
build-it-yourself projects.

This latest edition includes a host of exciting construction projects for audio buffs—Audio-Controlled Detailed Power Shut Off; 9-Channel Stereo Equalizer . . . For fun and games—FLIP, a CMOS Logic Game; Sound Effects with the 555 IC Timer . . . for experimenter's—ESP Testing Machine; How to Make Double-Sided PC Boards; IC Digital Logic Memory Probe . . . for computer/calculator enthusiasts—An Under-\$30 Scientific Calculator; Microcomputer Primer; Bits-to-Dots Computer Video. There's a host of other projects including The Executive Digital Temper Countdownner • Versatile Nickel-Cadmium Battery Charger • Shirt-Pocket Metronome • Hall Effect Magnetometer • Low-Cost Metal Locator • 3-Way Photo Flash Tripper • The 99-cent Wonder IC • High-Value Electrolytic Capacitor Meter • Guitar Sound Intensifier • IC Photo Tachometer • R-F Transistor Tester • And more! PLUS: Microcomputer product buying guide and a basic digital logic course. All with complete construction plans, parts lists and printed-circuit board patterns. Many projects are unique designs not available elsewhere. Only \$1.85!

Ziff-Davis Publishing Co. PE-577  
Consumer Service Division  
595 Broadway, New York, N.Y. 10012

Please send the 1977 ELECTRONIC EXPERIMENTER'S HANDBOOK. I'm enclosing \$1.85 (\$1.50 plus 35c for postage and handling). Outside U.S.A. \$3.00, postpaid.

Residents of Calif., Col., Fla., Ill., Mich., Mo., N.Y. State, D.C. and Tex. add applicable sales tax (postage and handling charges non-taxable).

print name \_\_\_\_\_

address \_\_\_\_\_

city \_\_\_\_\_

state \_\_\_\_\_

zip \_\_\_\_\_

COMING UP IN THE JUNE

# Popular Electronics®


## SPECIAL FOCUS ON TEST INSTRUMENTS

DIGITAL IC TESTER PROJECT  
BUYER'S GUIDE TO SCOPES  
40-MHz DIGITAL FREQUENCY COUNTER  
MILLIAMMETERS ON A BUDGET

POWER AND MODULATION CAPABILITY  
OF 40-CHANNEL CB TRANSCEIVERS

HOW TO PROGRAM CALCULATORS  
FOR FUN AND GAMES

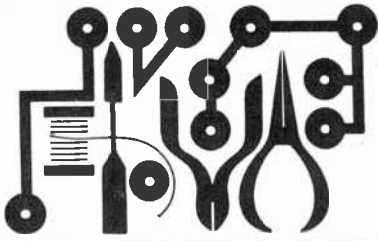BUILD A STATE-OF-THE-ART  
BATTERY CHARGE MONITOR



# Experimenter's Corner

By Forrest M. Mims

## USING LED'S AS LIGHT DETECTORS

**L**IGHT emitting diodes have many applications including status indication, digital readout, signal isolation, and light-beam communication. But did you know LED's can also be used as light detectors?

You can easily demonstrate the pho-

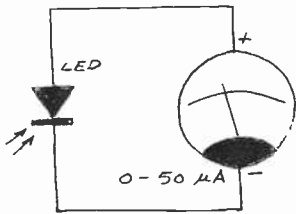


Fig. 1. Simple LED detector demonstration circuit.

tosensitivity of a LED by using the simple circuit in Fig. 1. An infrared emitting LED such as the Texas Instruments TIL32 is connected directly to the terminals of a 0-50 microampere meter. This forms a *photovoltaic* circuit, and when the LED is placed near a desk lamp or other bright light source, the meter will indicate a photocurrent of at least 10 or 15 microamperes.

Though gallium-arsenide infrared emitting diodes make the best light detectors, visible emitters made from gallium arsenide phosphide, gallium phosphide, and other materials also work. For best results, use LED's with clear encapsulants. Remember that just as LED's emit a narrow spectrum of light,

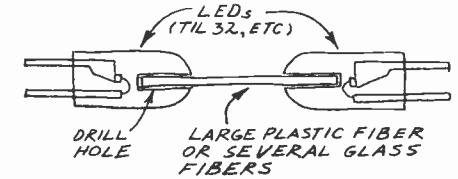


Fig. 2. LED-LED optoisolator using optical fiber coupling.


toisolator can then be used in either direction since the LED's can both emit and detect infrared.

You can also couple two epoxy-encapsulated LED's with a short length of plastic or glass optical fiber. Just bore a small hole in the top of each LED, using care to avoid striking the chip or its

## Treat yourself to a new direct reading DVM today.



**DVM35**  
POCKET PORTABLE  
ANALOG REPLACEMENT  
3-digit, 1% DCV  
Battery or AC  
Only \$134

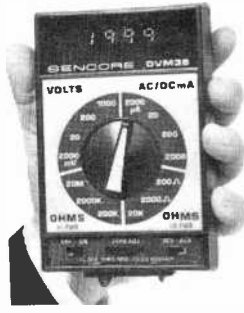

**DVM36**  
LAB ACCURATE  
POCKET PORTABLE  
3½ digit, .5% DCV  
Battery or AC  
Only \$158



**DVM32**  
BENCH & FIELD MASTER  
3½ digit, .5% DCV  
Battery or AC  
Only \$198



**DVM38**  
"PRIME" STANDARD AT  
YOUR FINGERTIPS  
3½ digit, .1% DCV  
Auto-Ranging  
Only \$348

## A COMPLETE LINE OF DVMs TO FILL YOUR EVERY NEED OR WANT.

You can be sure more times in more circuits, under more adverse conditions, with greater versatility, accuracy, and meter protection than any other digital multimeters on the market today; and for less money, too. 10 Day Free Trial: Try any of these famous DVMs for 10 days. If the DVMs in use don't prove exactly what we say, return them to your Sencore FLPD Distributor.

# SENCORE

Want more information? We would like to tell you all about the Sencore DVMs by sending you a 24-page Sencore News, a six-page brochure, and the name of your nearest Sencore Distributor today... simply write or circle reader's service number.

3200 Sencore Drive, Sioux Falls, SD 57107



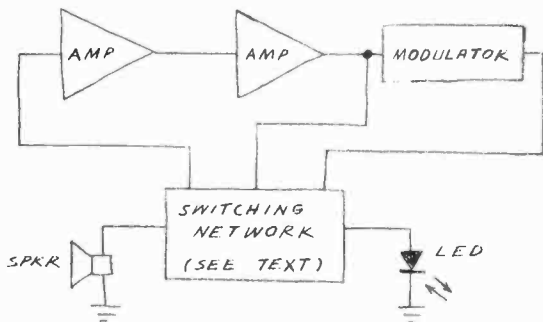


Fig. 3. Block diagram for single LED transceiver.

upper electrode wire. Then insert some clear epoxy, the fiber, and secure the fiber in place until the epoxy has cured. Figure 2 shows how two LED's are coupled together using this method.

Another possible application for a LED in the detector mode is to monitor the light intensity arriving from the sun or artificial sources at the face of a seven-segment LED display. An unused decimal-point LED could be used as the light detector for a circuit which could automatically control the brightness of the display.

The most intriguing application for


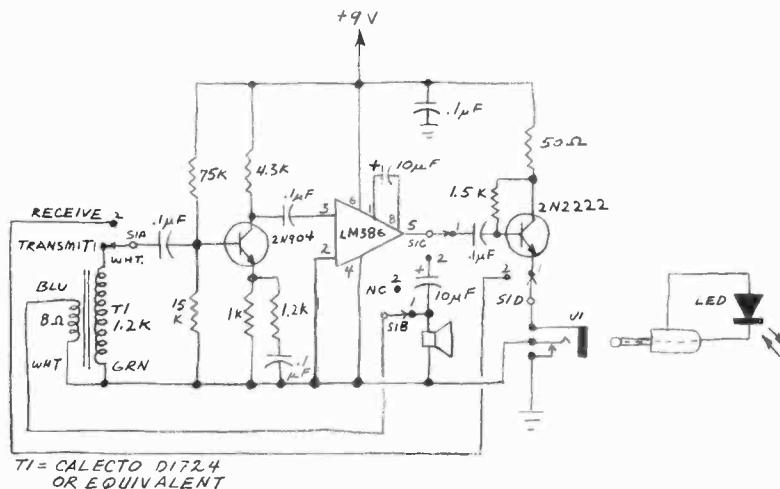


Fig. 4. Schematic diagram of a practical LED-LED transceiver.

LED's operated as detectors lies in the field of light-beam communications. One problem with light-beam communicators designed to operate through the atmosphere is optical alignment. (The most perplexing problem, of course, is the atmosphere itself.) Conventional light-beam communicators with separate LED transmitters and photodetector receivers must use two lens systems or complicated optics which allows both to use the same lens or lenses.

LED-LED communicators, however, need only one lens per transceiver. Then when the transmitter of one unit is aligned with the receiver of a second unit, the transmitter of the second unit is automatically aligned with the receiver of the first.

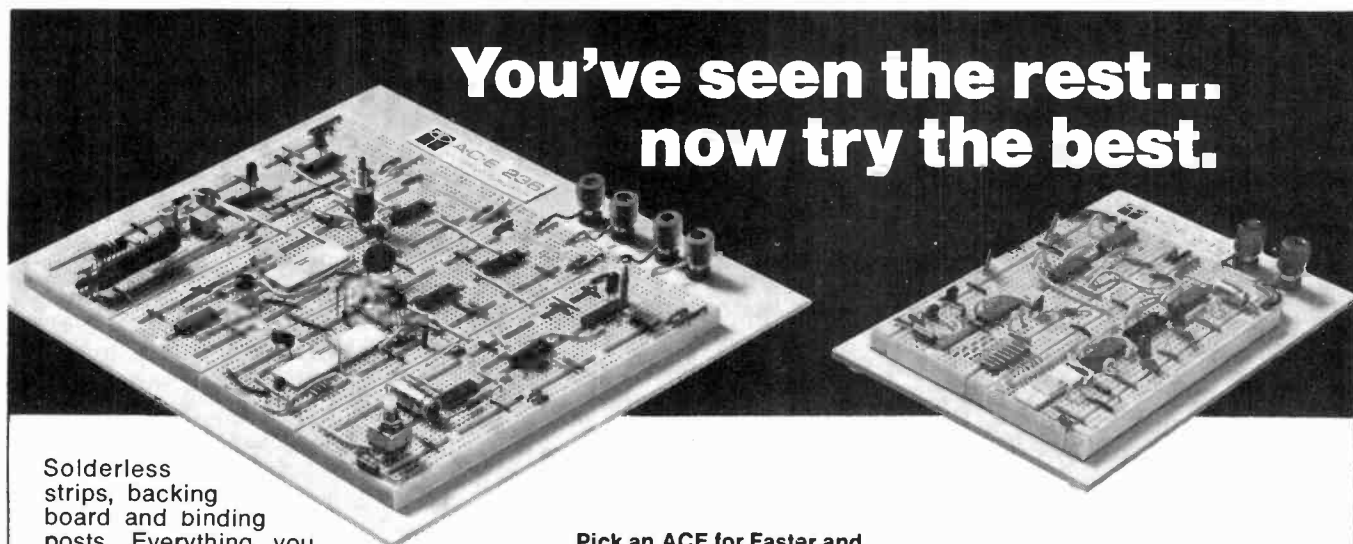**A Practical LED-LED Transceiver.** The block diagram for a basic amplitude-modulated light beam transceiver using a single infrared LED as both a



Solderless strips, backing board and binding posts. Everything you need to build and test your own circuit. Used to be you'd get a circuit idea, lay out a pc board, print it, solder everything together, trouble-shoot, change your layout, try a new board, and spend absolutely too much time breadboarding. Now A P ACE All Circuit Evaluators let you breadboard in a fraction of the time. Make your changes immediately. Keep full leads on your components. Avoid the heat damage possible with repeated soldering and de-soldering. A P made the first modern solderless breadboard, and we still make them best.

Pick an ACE for Faster and Easier solderless circuit building and testing.

Send for our complete A P catalog, The Faster and Easier Book.

Part No.	ACE Model No.	Tie Points	DIP Capacity	No. Buses.	No. Posts	Board Size (inches)	Price Each
923333	200-K (kit)	728	8 (16's)	2	2	4-9/16x5-9/16	\$18.95
923332	208 (assem.)	872	8 (16's)	8	2	4-9/16x5-9/16	28.95
923334	201-K (kit)	1032	12 (14's)	2	2	4-9/16x7	24.95
923331	212 (assem.)	1224	12 (14's)	8	2	4-9/16x7	34.95
923326	218 (assem.)	1760	18 (14's)	10	2	6-1/2x7-1/8	46.95
923325	227 (assem.)	2712	27 (14's)	28	4	8x9-1/4	59.95
923324	236 (assem.)	3648	36 (14's)	36	4	10-1/4x9-1/4	79.95

Order from your A P distributor today. Our distributor list is growing daily. For the name of the distributor nearest you call Toll-Free 800-321-9668.

**A P PRODUCTS INCORPORATED**

Box 110 Painesville, OH 44077  
(216) 354-2101 TWX: 810-425-2250





By John McVeigh

source and a detector is illustrated in Fig. 3. The circuit consists of a preamplifier, amplifier, LED driver and a switching network to switch the LED from the input of the preamplifier (receive mode) to the output of the driver (transmit mode). Several years ago I described a LED-LED communicator patterned upon this basic design in POPULAR ELECTRONICS ("Communicate Over Light Beams with the First Single-LED Transceiver," March 1974, p. 66). While this transceiver worked quite well, it used a relatively large audio amplifier module.

Figure 4 is the circuit diagram for a more up-to-date LED-LED transceiver made with an LM386 audio amplifier IC. Thanks to the LM386, the new circuit is much smaller and somewhat simpler than the original version. Also, the new circuit incorporates a simplified one-transistor modulator, a single 8-ohm speaker which doubles as a microphone, and a 9-volt battery.

I have assembled a working version of the circuit in Fig. 4 and installed it in a miniature bakelite cabinet measuring 3-1/4" x 2-1/8" x 1-1/8" (8.26 x 5.4 x 2.86 cm). There isn't enough room here to include all the construction details, but here are a few assembly tips: Use a perforated board measuring 2" x 1-15/16" (5.08 x 4.92 cm) to leave room for the 9-volt battery. Remove the upper two corners of the board to make room for the cabinet's cover screws. A 2" speaker fits perfectly in the space between battery and the upper end of the cabinet. All the components except the LED can be installed in a circle on the circuit board around the base of the speaker. The 4pdt switch fits between the upper two cover screw receptacles. Because of the limited space, the switch handle will have to emerge from the side of the cabinet opposite the front of the speaker.

Use a miniature phone jack to connect the LED to the circuit. Besides providing an automatic on-off switch, this will allow you to experiment with various kinds of LED's. It will also let you place the LED some distance from the circuit and simplify experimentation with different lenses.

I've used the transceiver in Fig. 4 for communications through the atmosphere and a fiber optic cable. Results with a 10-meter (32.8') length of glass fiber with an attenuation of a few hundred dB per kilometer were excellent. This cable should soon be available from some of the firms which specialize in experimenters' electronics components. Until then, you can try high-loss plastic fibers or stick to the atmosphere. ◇

## SUPPRESSING BLOWER HASH

**Q.** *I built the CB converter described in the October issue and have installed it in a 1976 Plymouth Fury. However, the blower fan motor (for air conditioning, heating, and defrosting) creates so much static that it is impossible to operate it and the converter simultaneously. I do not have this problem when I use the AM/FM radio "straight through." Can you suggest a filter that will suppress this interference?—W. B. Grandjean, Baton Rouge, LA.*

**A.** I recommend the installation of 0.25- $\mu$ F coaxial capacitors across the terminals of each blower motor. The capacitor will act as a short circuit to the r-f hash generated by the sparking at the motor brushes, but will not affect the system from a dc point of view. The capacitors can be obtained from most auto supply houses, and can also be used to silence noisy gauges and sender units. Be sure that the case of the converter and the shield of the antenna lead-in are well grounded.

## FM STATION LISTINGS

**Q.** *I would like to obtain a listing of FM radio stations. Do you know where I could get one?—Mrs. Don Ginest, Lakin, KS.*

**A.** As I recall, a very comprehensive list of FM broadcasters is offered by the Worldwide TV-FM DX Assoc., Box 163, Deerfield, IL 60015. Also, there's a listing in *North American Radio-TV Station Guide*, by Vane A. Jones, published by Howard W. Sams & Co.

## NIXIE INTERFACE

**Q.** *How can I trigger 170-volt Nixie tubes with the 12-to-14-volt "digit enable" pulse from a 5313 clock chip?—LeRoy Lee, Altus, OK.*

**A.** I think the most inexpensive way to do this is to have the digit enable pulses turn on high-voltage npn switching transistors. These in turn would apply the

high voltage to the individual tubes. A suitable transistor is the Motorola HEP S0027. It has a collector-to-emitter breakdown voltage rating of 300 volts, maximum collector current of 500 mA, and a typical cut-off frequency of 50 MHz. However, if you go this route, be sure to include current limiting resistors at the base and collector of each transistor. Of course, some chips provide BCD outputs which can be decoded by suitable IC decoder/drivers. For example, the 7441 is specifically designed for use with Nixies.

## TTL VS. CMOS

**Q.** *The circuit for the "Westminster Chime" clock (November 1976) uses CMOS IC's. Is it possible to use TTL IC's in place of them, or a mixture of the two?—Murray Voakes, Essex, Ontario.*

**A.** Although similar CMOS and TTL gates and sequential logic circuits perform the same functions—a CMOS 2-input NAND gate is logically equivalent to a TTL 2-input NAND—there are differences in input and output impedances, drive capabilities, operating voltages, etc. The great advantage of TTL over CMOS is operating speed. However, CMOS has it all over TTL in the areas of power consumption at slow speeds and noise immunity when higher operating voltages are used. In this application, switching speeds are low enough to allow CMOS to run significantly cooler than TTL. This means that a smaller power supply can be used. In fact, CMOS is becoming so popular that several manufacturers are offering MOS devices that have the same pinouts as the 7400 TTL series. This allows one to convert from TTL to CMOS with a minimum of pc board modifications. So I really don't see going TTL or hybrid in this circuit. Surplus CMOS is inexpensive, an all-CMOS design requires no level interfacing, and power supply demands are greatly reduced. As a final note, many CMOS devices are now zener diode "clamped" and won't self-destruct when you touch them!


Logic Probe 1 is a compact, enormously versatile design, test and troubleshooting tool for all types of digital applications. By simply connecting the clip leads to the circuit's power supply, setting a switch to the proper logic family and touching the probe tip to the node under test, you get an instant picture of circuit conditions.

LP-1's unique circuitry—which combines the functions of level detector, pulse detector, pulse stretcher and memory—makes one-shot, low-rep-rate, narrow pulses—nearly impossible to see, even with a fast scope—easily detectable and visible. HI LED indicates logic "1", LO LED, logic "0", and all pulse transitions—positive and negative as narrow as 50 nanoseconds—are stretched to 1/3 second and displayed on the PULSE LED.


By setting the PULSE/MEMORY switch to MEMORY, single-shot events as well as low-rep-rate events can be stored indefinitely.

While high-frequency (5-10MHz) signals cause the "pulse" LED to blink at a 3Hz rate, there is an additional indication with unsymmetrical pulses: with duty cycles of less than 30%, the LO LED will light, while duty cycles over 70% will light the HI LED.

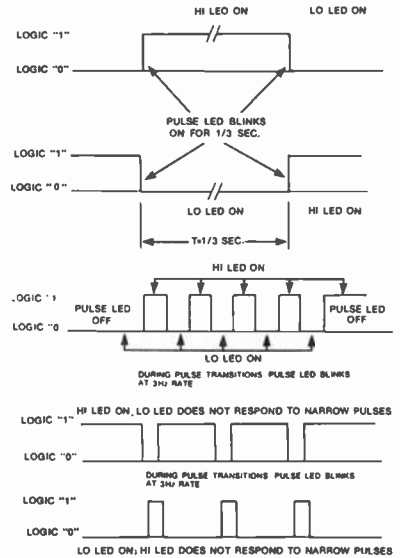In all modes, high input impedance (100K) virtually eliminates loading problems, and impedance is constant for all states. LP-1 also features over-voltage and reverse-polarity protection. Housed in a rugged, high-impact plastic case with strain-relieved power cables, it's built to provide reliable day-in, day-out service for years to come.


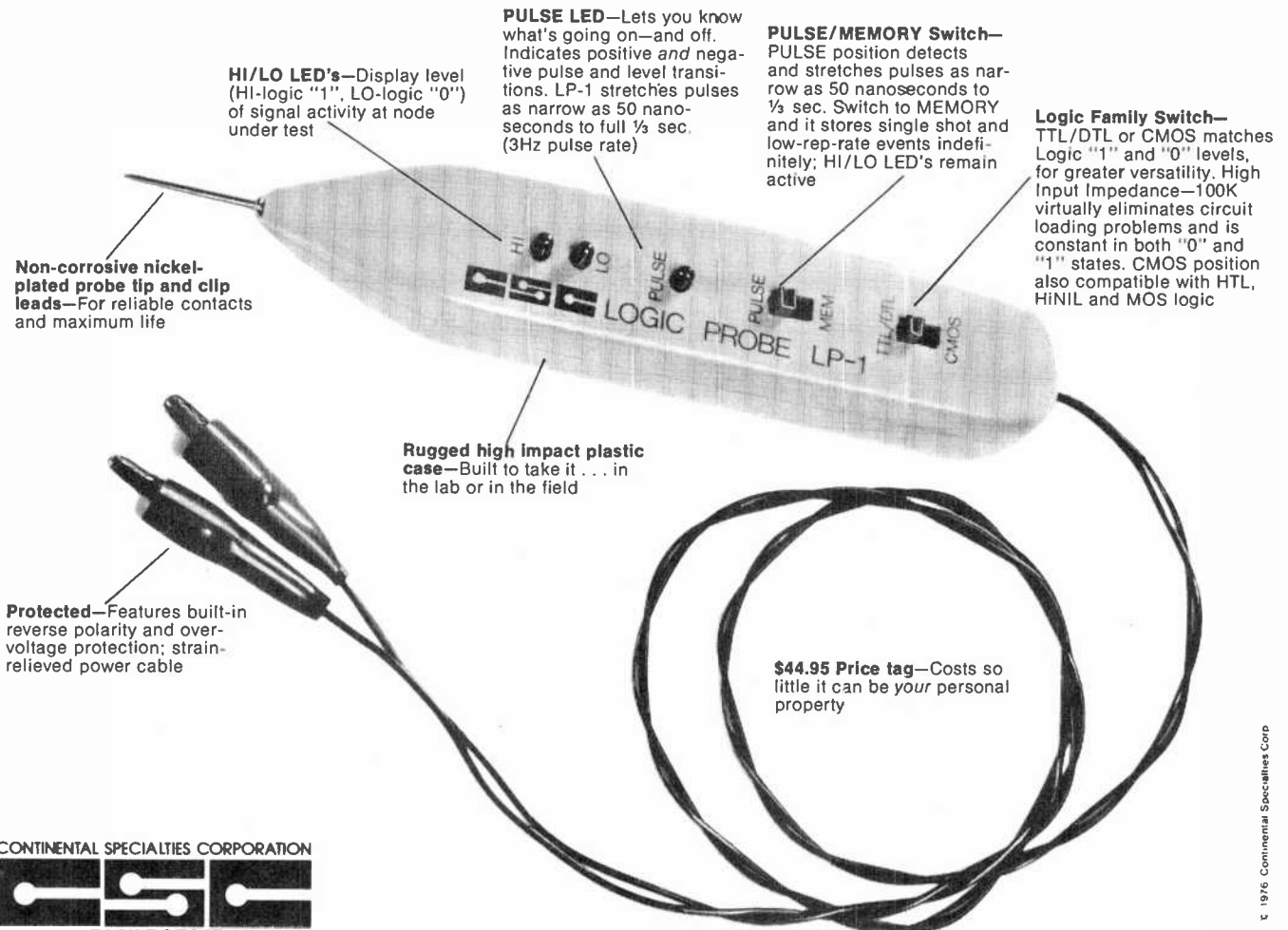
## CSC'S MULTI-FAMILY LOGIC PROBE 1. AT \$44.95, IT DIGGS UP A LOT OF INFORMATION WITHOUT BURYING YOUR BUDGET.



CONTINENTAL SPECIALTIES CORPORATION



44 Kendall St, Box 1942, New Haven, CT 06509  
 TWX: 710-465-1227  
 West Coast office: Box 7809, San Francisco, CA 94119  
 TWX: 910-372-7992; Canada: Len Finkler Ltd.,  
 Ontario; Mexico: Elpro, S.A., Mexico City, 5-23-30-04

See your CSC dealer or call 203-624-3103 (East Coast) or 415-421-8872 (West Coast) 9 AM to 5 PM local time. Major credit cards accepted. Add \$2.50 for shipping and handling in the U.S. and Canada on direct orders of \$50.00 or less; \$3.00 for orders over \$50.00. On all foreign orders add 15% to cover shipping and handling.



# Product Test Reports

## KENWOOD MODEL TS-820 TRANSCEIVER

*All-band hf transceiver has operating versatility and built-in speech processor.*



**A**LTHOUGH Kenwood's new Model TS-820 160 - through - 10 - Meter SSB/CW amateur transceiver physically resembles its popular Model TS-520, the two are very different in terms of circuit design and built-in features. Also, the TS-820 can accommodate an optional digital frequency readout, whereas the TS-520 cannot. Other new features (discussed later) clearly make the new transceiver Kenwood's "top of the line."

The transceiver is housed in a rugged, gray-finished cabinet that measures 13-3/16" D x 13 1/8" W x 6" H (33.5 x 33.3 x 15.3 cm). A versatile (110- or 220-V, 50- or 60-Hz) ac power supply is built-in, as well as a small loudspeaker. A handle on the right side of the cabinet provides a means for carrying the 35.2-lb (16-kg) transceiver. The basic TS-820 transceiver is priced at \$830. The optional DG-1 digital frequency readout, which mounts inside the TS-820's cabinet and can be added at any time, is \$170. Other options include the CS-820-20 500-Hz CW crystal filter (\$45), the DS-1A dc/dc converter for mobile use (\$59), and the VFO-820 external vfo (\$139).

**General Description.** The transceiver circuitry is solid state, except for a 12BY7A driver and two S-2001A (a pin-for-pin 6146B equivalent) final amplifier tubes. The usual complement of transmitter and receiver tuning controls is provided. The multi-function, switch-controlled meter indicates final amplifier

plate current or voltage, relative r-f output, alc circuit operation, compression level from the built-in r-f speech processor, and S units.

When the MODE switch is set to TUN or FSK, power input to the finals is automatically reduced so that the tubes' rated plate dissipation is not exceeded. The r-f speech processor is activated by pulling out the COMP LEVEL/PROC control. The amount of the compression (indicated on the meter) is adjusted by rotating this control.

The transmitter pi network and transceiver preselector controls are grouped together. The PLATE tuning control uses a vernier for easy adjustment. The LOAD control is concentric with a FIX CH switch that selects any one of four crystal-controlled channels in the FIX mode (crystals optional).

The center-detented IF SHIFT control is concentrically paired with the receiver incremental tuning (RIT) control, the latter activated by a pushbutton. The CW CAR level and SSB MIC gain controls are also paired, as are the RF GAIN and AF GAIN controls. An RF ATT push-button switch inserts a 20-dB attenuator at the receiver's antenna input to combat overload and desensitization by strong local signals.

The BAND switch has positions for all amateur bands between 1.8 and 29.7 MHz, as well as JY/WWV (reception only) on the 15-to-15.5-MHz band. The 10-Meter band is covered in four 500-kHz segments. (There is also a position on the BAND switch labelled AUX, which

apparently can be used for operations outside the regular ham bands, although the manual does not mention it.)

The FUNCTION switch is normally left in the VFO position to allow the internal vfo to control the transceiver frequency. When set to FIX, both frequencies are controlled by internal crystal oscillators, with up to four frequencies selectable by the FIX CH switch. The VFO:R position uses the internal vfo to control the receiver's frequency, while the FIX:R position puts the receiver under crystal control and the transmitter under vfo control. When either the transmitter or the receiver is on vfo control, the FIX and RMT positions are used with the AUX crystal-controlled channels of the remote vfo to zerobeat the vfo to channel frequency.

A separate HEATER switch is provided to shut off the tube heaters when the transceiver is used for reception only. All VOX controls are mounted on the front panel for ready access. Because the VOX circuit controls the changeover relay on CW (semi-break-in) as well as SSB, it is most convenient to have the DELAY control up front for easy adjustment as conditions warrant.

The large tuning knob operates two circular dial scales, one calibrated at 1-kHz intervals (numbered every 10 kHz), and the other calibrated at 50-kHz intervals and numbered from 0 to 500 every 100 kHz. The dial index can be moved to calibrate the scale against the 25-kHz marker oscillator or WWV. The dial set-up uses Kenwood's "mono-scale" kilohertz dial system which fits the full 500-kHz tuning range on a single small dial with 1-kHz calibration intervals. The scale is rotated 10 turns for edge-to-edge coverage of each band segment.

When the optional digital frequency display is installed, as it was on our test model, the fluorescent readout appears in a window above the mechanical dial scales. Above the numeric display are four LED's that indicate when the ATT (attenuator) is on and when FIX, VFO, and RIT functions are active.

A button labelled DH (display hold) permits the numeric display to be "frozen" to store a frequency for quick retuning. When the display is frozen, you can tune about using the mechanical dial. To return to the original frequency, you simply note the counter display, release the DH button, and tune until that number again appears in the display.

The single-conversion receiver has an 8830-kHz i-f. A phase-locked-loop (PLL) circuit gives the benefits of both single and multiple conversion with few of the disadvantages of either. The local oscil-

lator consists of 11 separate band-switch-selected voltage-controlled oscillators or vco's (one for each band). These oscillators employ varactor diodes. The output of the vco is heterodyned with a crystal oscillator to produce a frequency between 3.33 and 3.83 MHz. The heterodyne oscillator also consists of 11 separate oscillators. The 3.33-to-3.83-MHz signal is then heterodyned with the output of a crystal-controlled carrier oscillator operating near 8830 kHz to generate an output between 5.0 and 5.5 MHz.


Tuning is by a conventional 5.0-to-5.5-MHz, highly stable and linear Clapp vfo. The vfo's output is compared with a down-converted vco signal by a phase comparator whose output trims the output frequency of the vco. Thus, the vco is phase locked to the 5.0-to-5.5-MHz tunable oscillator to effectively transfer the linearity and stability of the latter to the 10.5-to-39-MHz local oscillator. A phase-lock sensor disables the vco if PLL action fails, preventing off-frequency operation.

There are two separate carrier oscillators. One, controlled by two switchable crystals, operates on SSB transceive and on CW receive. The other functions in the transmit FSK and CW modes, when the receive and transmit frequencies are slightly separated.


A very useful feature is the IF SHIFT, which allows the i-f passband to be moved approximately  $\pm 1.7$  kHz without affecting the pitch of the received signal. The IF SHIFT electronically varies the frequency of the carrier oscillator in the PLL system. This causes the vco to move exactly as much as the carrier frequency, resulting in no net change in the relationship between the signal and oscillator frequencies. Because the filter is fixed, the signal is moved through the filter passband.

The built-in r-f speech processor provides up to 50 dB of compression. Here's how it works. The audio input signal is applied to a balanced modulator operating at 455 kHz and is then passed through a filter to remove one sideband. The remaining sideband is compressed—not limited—by an agc amplifier. It is further filtered to remove distortion products beyond the desired modulation passband, down-converted to audio, and finally applied to the main balanced modulator of the transmitter.

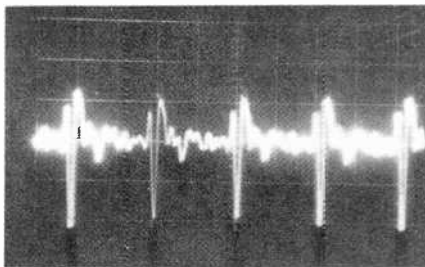Some 10 dB of r-f negative feedback is used in the driver and output stages to reduce odd-order IM products by 6 to 10 dB. This makes the signal unusually clean and free from splatter that could



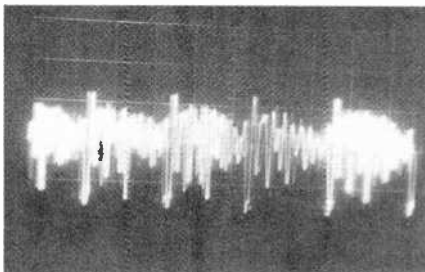*10-W avg. output with sustained "Ahhh" driving transmitter.*



*Average power increased to 40 W with 20 dB of compression.*

interfere with QSO's on nearby frequencies. Alc is also used to prevent driving the output tubes into nonlinearity.

The transceiver has a built-in SSB receiver that is always tuned to the transmitter frequency so the operator can monitor his transmitted signal. R-f is sampled just before the driver stage, heterodyned down to audio by a product detector, and injected into the receiver's audio amplifier when the MONITOR switch is on. This is a good way to determine the effects of the r-f processor and to determine how much background noise is increased when compression is introduced.

The optional digital frequency display module counts the frequency to the nearest 10 Hz, then rounds off and displays the operating frequency to the nearest 100 Hz. Accuracy of the display is guaranteed to be 1 ppm/month.

**Transmitter Tests.** On 80 Meters, a two-tone test resulted in 200 W PEP input to the final amplifiers. PEP output into a 50-ohm dummy load was 115 to 120 W. Key-down CW input power measured 165 W, and CW output 100 to 110 W. On SSB, carrier suppression varied from 53 dB (LSB) to 58 dB (USB). The unwanted sideband was 60 dB down when a 1000-Hz modulating signal was applied. Distortion products measured as follows: third order -32 to -34 dB referenced to the two tones, -38 to -40 dB referenced to PEP; fifth order -56 dB referenced to the two tones, -62 dB

referenced to PEP. An audio input of 1 mV at 1000 Hz was sufficient to fully modulate the transmitter on the 7-MHz band.

The r-f speech processor produced some interesting results. A sustained "Ahhh" driving the transmitter to full PEP yielded an average power output of 10 W when no compression was applied. With 20 dB of compression (as indicated on the transceiver's meter), the average power output increased to 40 W. Peak power remained at the same level with or without compression. This translates to a 6-dB increase in "talk power," equivalent to an increase of one "ideal" S unit at the receiving end. This increase is nearly equivalent to switching in a 1000- or 1200-W PEP linear.

Of course, the processor (like all processors) introduced some a-f distortion and degraded the unwanted sideband suppression. At a modulating frequency of 1000 Hz, and at 10 dB of compression, the second harmonic of the modulating frequency was 30 dB down—equivalent to 3.2% of distortion. Unwanted sideband suppression measured 50 dB. At 750 Hz, the second harmonic measured -28 dB (4% distortion) when 10 dB of compression was introduced. The third harmonic (2250 Hz) was 20 dB down (10% distortion), and unwanted sideband suppression measured 30 dB. When a 500-Hz tone was used to modulate the transceiver, the unwanted sideband suppression improved to -35 dB. Finally, when a 400-Hz modulating tone was applied, the second harmonic measured -40 dB (1% distortion) at 10 dB of compression. The third harmonic was 10 dB down (32% distortion), and the unwanted sideband suppression measured 25 dB.

Alc action was very good. Flat-topping simply did not appear, even at maximum alc. Audio response measured (at the 6-dB points) 325-2800 Hz (USB) and 240-2700 Hz (LSB). When the speech processor was used, the response was slightly altered. Maximum VOX release time was approximately one second. When the release was shortened to allow semi-break-in CW keying, no shortened first dot or dash occurred. That is the exception, rather than the rule, among today's amateur rigs!

To check the transceiver's frequency stability (rated at better than 100 Hz/hour after a one-hour warmup and less than 1000 Hz of drift in the first hour after a one-minute warmup), the transceiver was attached to a dummy load and placed in the TUNE mode at 7 MHz, yielding an r-f power output of about 15

## RESULTS OF RECEIVER TESTS

Frequency (MHz)	Sensitivity ( $\mu\text{V}$ ) for 10 dB (S+N)/N		Image Rejection (dB)	I-f Signal Rejection (dB)	Band-to-Band Gain* (dB)
	SSB	CW			
1.8	0.1	0.05	96	100	0
3.5	0.1	0.063	92	90	-3
7	0.08	0.05	86	96	0
14	0.1	0.056	70	92	-3.5
21	0.1	0.063	66	96	-3
28	0.1	0.063	68	96	-1

(+1 dB on  
29.5-MHz  
segment)

\*Overall gain—not affecting sensitivity—determined by comparing audio output on each band, referenced to 1.8 and 7 MHz, produced by a given input signal. Variations in band-to-band gain occur below the agc threshold and have no effect above it.

W. The frequency of this output signal was measured by coupling a frequency counter to the dummy load. After a brief stabilization period (much less than the allowable hour), the drift averaged about 96 Hz/hour for the next few hours. The final transmitter test we performed was the measurement of r-f harmonics at the antenna output jack. They were consistently 40 dB below the fundamental.

**Receiver Tests.** Results of our measurements of sensitivity, image rejection, i-f signal rejection, and difference in band-to-band gain appear in the Table. Note that sensitivity measurements at these very low signal levels are usually accurate to within  $\pm 3$  dB. However, even within this margin, the TS-820's receiver tested extremely "hot." A 50- $\mu\text{V}$  signal (nominal) was required for an S9 meter reading; a 1- $\mu\text{V}$  signal produced an S2.5 reading. Inserting the r-f attenuator in the input line (by means of the front panel pushbutton) dropped signal levels 20 dB. The receiver incremental tuning varied the receive frequency  $\pm 3000$  Hz. Unwanted sideband rejection measured 60 dB at 1000 Hz and 50 dB at 500 Hz.

No crossover birdies were found when signals below 10,000  $\mu\text{V}$  were applied to the input. Internal spurious signals measured 0.2  $\mu\text{V}$  (equivalent) at 21.200 MHz and less than 0.1  $\mu\text{V}$  (equivalent) at 2 and 21 MHz. Two 320- $\mu\text{V}$  signals (-57 dBm, or 70 dB above the SSB sensitivity) spaced 25 kHz apart created third-order IM (intermodulation) products equivalent to the rated sensitivity (0.1  $\mu\text{V}$  for 10 dB (S+N)/N). An undesired 32,000- $\mu\text{V}$  (-17 dBm) signal 110 dB above a 0.1- $\mu\text{V}$  desired signal desensitized the receiver by depressing the desired signal 1 dB. The receiver section was very

resistant to blocking (overload). No loss of output level or increase in distortion was detected when input signals of up to 100,000  $\mu\text{V}$  (-7 dBm) were applied.

When the r-f input signal varied from 0.1 to 1  $\mu\text{V}$  (a 20-dB change), the audio output rose 18 dB. When the input signal was raised from 1  $\mu\text{V}$  to 10  $\mu\text{V}$ , the agc came into play and the audio output rose only 1 dB. A 100-dB change in r-f (from 1 to 100,000  $\mu\text{V}$ ) caused the audio output to increase only 2 dB. Release time from an S9 signal level to full recovery was approximately 0.75 second when the agc switch was in the FAST position and 4.5 seconds in the SLOW mode.

Nominal overall response—which included the i-f passband and audio responses—measured as follows: 400 to 2150 Hz at -6 dB, 200 to 3525 Hz at -60 dB (USB); 275 to 1850 Hz at -6 dB, 75 to 3300 Hz at -60 dB (LSB); 700 to 1250 Hz at -6 dB, 335 to 1685 Hz at -60 dB (CW). These measurements were made below the agc threshold. The differences between USB and LSB are easily explained by the fact that the frequency of the carrier oscillator feeding the balanced modulator is deliberately shifted for proper generation of USB and LSB signals. It is the change of the relationship between the skirts of the fixed crystal filter and this carrier oscillator that causes different overall responses in the USB and LSB modes. However, in both modes the unwanted sideband suppression was 60 dB at 1000 Hz and 50 dB at 500 Hz.

The transceiver produced 1.5 W of audio output into 8 ohms. A 1000-Hz sine wave was used for this test, and at the start of clipping total harmonic distortion was less than 2%.

In our final receiver test, we applied a pulse train composed of 0.0005- $\mu\text{s}$ -wide pulses at a 60-Hz rate. This pulse train

(at 100 dB above 1  $\mu\text{V}$ /MHz bandwidth) completely obliterated a 3- $\mu\text{V}$  input signal. A 10- $\mu\text{V}$  signal was depressed by at least 10 dB due to agc capture by the noise pulses. However, when the TS-820's noise blanker was activated, normal agc action was restored and undisturbed copy of even 0.1- $\mu\text{V}$  signals became possible! But the blanker had no effect on low-level pulses (less than 50 dB above 1  $\mu\text{V}$ /MHz bandwidth).

**On The Air.** With few exceptions, we confined our on-the-air testing to the 7-MHz band. Operation was equally divided between SSB and CW. During the weeks we operated this transceiver, we never felt the need to use our linear.

It seemed as natural to scan the bands with the digital numeric frequency display as it was to observe the position of a dial scale against an index line. Let us assure anyone who is not ready to make the added investment in the digital display that the mechanical dial is accurate to within about 100 Hz of the digital display.

We were pleased to note that the transceiver can be tuned with its own meter, and modulated within the maximum limits defined by its alc meter scale without compromising performance. The front-panel VOX controls proved to be rock stable. On CW, the delay could be set so that the transmitter would drop out between characters below 20 wpm and between words at higher speeds. This is not really QSK (full break-in keying), but it's pretty close! Both the keying and modulation received numerous unsolicited compliments from stations contacted. Only rarely useful on SSB, the IF SHIFT proved to be valuable on CW. It let us move QRM off the skirts of the 500-Hz filter to the point of inaudibility, without changing the pitch of the desired signal.

During our tests, an idling truck blanketed us with ignition noise at S9. Switching in the noise blanker effectively eliminated—not just reduced—the interference! This was a most impressive demonstration, which left us regretting that the blanker could not dispose of types of noise other than impulse noise.

In actual QSO's, we verified that the r-f speech processor gave a one to two S-unit improvement in signal strength. However, the processor does cause some signal distortion. Thus, the processor should be used (and is intended for use) only under conditions that warrant it. Under strong-signal conditions, all speech processors impair intelligibility to some degree. On the other



hand, when the going gets tough, a good processor like the one in this transceiver can make the difference between contact and no contact.

No sound at all could be heard from the transceiver's cooling fan. The "silent" fan's cooling effectiveness was undeniable, however. After almost two hours of either SSB or CW operation, the cabinet was cool to the touch everywhere except directly above the final tubes, where it was faintly warm.

The TS-820 is certainly a full-feature all-band ham transceiver. The only gripe we do have concerns the top-facing speaker, which managed to lose much

of its meager output in our acoustically treated ceiling. For fixed-station operation, the owner would do well to connect an external speaker to the rear-panel output jack.

In sum, the TS-820's versatility and fine performance and the obvious top craftsmanship that has been spent on its design will fill any ham with pride of ownership. If we had to pick the most attractive feature among so many admirable ones, it would be the "digital hold." With this "memory" function, we'll never again fail to return exactly to a QSO frequency after a brief listen off-channel.

CIRCLE NO. 103 ON FREE INFORMATION CARD

## MURA MODEL PRX-100 "PRM" CB MICROPHONE

*Peak-redistribution modulation effectively increases signal power.*



**T**HE MURA PRM microphone contains a conditioning system that redistributes the asymmetrical sharp-peak portions of speech to make the signal more symmetrical. At the same time, it also holds down the peaks to allow the lower-energy components of the signal to be effectively higher in energy than would be possible with a "straight" microphone. This peak-redistribution modulation (PRM) is accomplished electronically by delaying the large sharp-peak components of the signal for minute amounts of time in relation to the lower-energy signals before passing them on to the transmitter's modulator. The result can be an effective *average* modulated signal without adverse distortion.

One of the new PRM microphones for CB use is the push-to-talk Model PRX-100. It has a gain control for setting up the optimum output level for any particular CB transmitter according to the operator's voice amplitude. (The microphone cannot be used with certain CB transceivers on the market. These are

detailed by manufacturer and model on the card on which the microphone is packaged.) Operating impedance is 0 to 2500 ohms. Power for the microphone system is obtained from an internal 9-volt battery. Price is \$39.95.


**Test Results.** We checked the Model PRX-100 with the aid of a dual-trace oscilloscope to observe simultaneously the output of the transducer cartridge and the conditioned output signal from the PRM circuit. Asymmetry at the cartridge was demonstrated with the maximum sharp-peak excursions in the positive direction. The conditioned output still produced some asymmetry, but in the opposite direction and to a lesser degree. However, the peak ratios, compared to the in-between lower-energy components, were reduced sufficiently to permit an overall higher average output level which potentially increased the average power of the modulated signal.

We also made comparisons with other microphones and with different voices. We noted that less improvement was obtained when compared to the output of the poorer-quality microphones than was the case with better units. (Lower-quality, less-expensive microphones usually exhibit their best symmetry, with lower positive/negative-peak ratios.) It should be noted that the advantages gained by using a PRM microphone apply mostly to limited-level amplifying or modulating systems in which operation is below the overload or clipping level. Systems that employ clippers or some form of automatic modulation control (amc) generally tend toward symmetry and higher average signal levels.

# The "Click and Pop" machine

only by

**SAE**

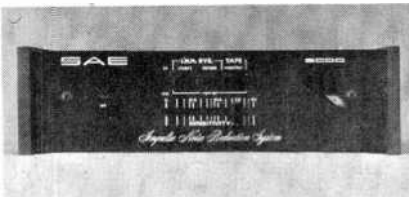

Ever since the invention of the recorded disc annoying "clicks" and "pops" caused by scratches, static and imperfections have consistently disturbed the listening pleasure of music lovers.

Now, SAE introduces the unique model 5000, an Impulse Noise Reduction System which eliminates those unwanted sounds with no adverse effect on the quality of the recorded material.

This breakthrough in electronic circuitry is so demonstrably effective that the SAE 5000 is destined to become an essential part of any sound system.

The SAE 5000 is compact and sleek, built to SAE's exacting standards, and ready to enhance the performance of any system, from the standard receiver/turntable combination, to the most sophisticated audiophile components.

SAE is proud to add the 5000 to their broad line of *Components for the Connoisseur*.

**SAE**

Scientific Audio Electronics, Inc.  
P.O. Box 60271, Terminal Annex  
Los Angeles, Cal. 90060

Please send more information on the 5000.

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_

State \_\_\_\_\_ Zip \_\_\_\_\_

PE-577

CIRCLE NO. 53 ON FREE INFORMATION CARD

## Empire's Blueprint For Better Listening

No matter what system you own, a new Empire phono cartridge is certain to improve its performance.

The advantages of Empire are threefold.

One, your records will last longer. Unlike other magnetic cartridges, Empire's moving iron design allows our diamond stylus to float free of its magnets and coils. This imposes much less weight on the record surface and insures longer record life.

Two, you get better separation. The small, hollow iron armature we use allows for a tighter fit in its positioning among the poles. So, even the most minute movement is accurately reproduced to give you the space and depth of the original recording.

Three, Empire uses 4 poles, 4 coils, and 3 magnets (more than any other cartridge) for better balance and hum rejection.

The end result is great listening. Audition one for yourself or write for our free brochure, "How To Get The Most Out Of Your Records." After you compare our performance specifications we think you'll agree that, for the money, you can't do better than Empire.



# EMPIRE

Already your system sounds better.

Empire Scientific Corp.  
Garden City, New York 11530

The polarity and characteristics of the existing microphone, as well as the frequency response or phase shifts in the modulating system, play an important role as to whether or not any significant improvement can be obtained with the use of a PRM microphone with a given degree of maximum modulation.

We noted that the low-frequency response of the microphone was somewhat less than usual. This resulted in a slightly crisper signal for better intelligence under adverse conditions.

**User Comment.** In many situations, with the gain control of the microphone set at maximum, the output level can be high enough to severely overload the modulator. This can produce heavy clipping or overmodulation, the latter beyond the signal-handling capabilities


of an amc system. Although the use of the microphone can make a signal sound somewhat louder, it may possibly do so at the price of high distortion and excessive adjacent-channel splatter. Therefore, caution should be taken in setting the microphone's gain. This is best done while observing the modulated r-f waveform on an oscilloscope and setting the level control so that the signal does not cause excessive or distorted modulation.

Whether or not a change to this type of microphone will be of benefit in any particular case can be determined by listening to the CB signal under maximum-modulation conditions. (The Model PRX-100 is rated to deliver up to a 4-dB increase in average modulated power, which we confirmed.)

CIRCLE NO. 104 ON FREE INFORMATION CARD
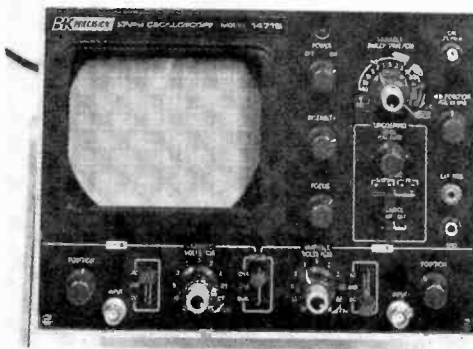
## B&K PRECISION MODEL 1471B OSCILLOSCOPE

*Has dual-trace and trigger functions desirable in testing modern circuits.*



**A** GOOD general-purpose oscilloscope for servicing and electronics experimenting should have a linear triggered sweep with a broad selection of sweep rates and triggering sources. It should also have two independent traces to permit observation of both the input and output signals of a circuit under test. Moreover, its vertical amplifiers should have sufficient bandwidth and sensitivity to enable the user to work with high-frequency signals with very low and very high amplitudes. The vertical amplifiers should be dc coupled to permit the scope to double as a voltmeter, and both amplifiers should have identical characteristics to permit the instrument to be used for a vector display. Finally, if the scope is to be used in TV servicing, it should have provisions for frame and line sweeps to serve as a vectorscope for chroma alignment.

All of these characteristics can be found in B&K Precision's Model 1471B dual-trace oscilloscope.

The scope measures 16"D × 9.6"W ×

7.7"H (40.4 × 24.5 × 19.6 cm) and weighs 18 lb (8.2 kg). Price is \$495.

**General Details.** Each of the vertical amplifiers in this dual-trace solid-state oscilloscope has a bandwidth that goes from dc to at least 10 MHz, risetime of 35 ns, 3% or less overshoot and ringing with a 100-kHz square-wave input, and 1 megohm paralleled by 22 pF input resistance. The deflection factor of the vertical amplifiers is from 0.01 volt/cm to 20 volts/cm in 11 calibrated ranges, fully variable between range settings.

Either amplifier (trace) can be selected separately, or the scope can be operated in the dual-trace (simultaneous display of both channels) mode. In the dual-trace mode, the traces are chopped at a 200-kHz rate at all sweep rates up to 1 ms/cm, while alternate-trace operation is automatically switched in for all faster sweep rates. Channel separation in the dual-trace mode is better than 60 dB at 1000 Hz.

The sweep circuit shared by both

POPULAR ELECTRONICS

channels can be automatically triggered without an input signal to the scope. The sweep range is from 1  $\mu$ s/cm to 0.5 s/cm, with full variability between ranges. In addition, the sweep can be magnified 5 $\times$ , yielding a maximum sweep speed of 0.2 s/cm. There is less than 3% (typical) horizontal linearity distortion.

The switch-selectable sweep triggering can be either internal or external and from the channel in use. (Channel A is selected in the dual-trace mode.) At almost all levels, either the positive or the negative slope of the input signal can be selected to initiate the triggering. Alternatively, the triggering can be automatic. The sweep can be triggered from 20 Hz to better than 10 MHz in the internal mode (1-cm deflection on the CRT's graticule) or dc to 10 MHz from an external trigger signal. A built-in sync separator is provided to permit observation with high stability of any portion of a complex TV waveform.

The horizontal amplifier can be accessed through the channel-B connector on the front panel of the scope and is selected by one position on the sweep speed control when the instrument is in the vectorscope mode. The horizontal amplifier then has a deflection factor of from 0.01 volt/cm to 20 volts/cm, which is the same as that of the vertical amplifier, and a frequency response from dc to 1 MHz.

Intensity modulation on the Z axis is available via a TTL-compatible connector on the rear panel of the scope. A logic low increases trace brightness, while a logic high decreases the brightness. The input resistance to the Z axis is 10,000 ohms.

The scope features a 5" (12.7-cm) flat-screen CRT. Over the face of the CRT is an 8  $\times$  10 cm blue-colored engraved graticule. The bezel that holds the graticule in place can be removed easily to allow insertion of the vector overlay needed for color TV alignment. A 1-volt p-p square-wave source permits checking and calibration of the vertical amplifiers without having to use external sources.

**User Comment.** The Model 1471B oscilloscope is an excellent general-purpose instrument. Calibration was originally performed with a very accurate external voltage source. After operating the scope for six hours a day over a period of two weeks, we again calibrated the scope and found it to be still "on the head."

During our in-service tests, we deter-

mined that the scope's sync holds up under even very-low-level and relatively high-frequency signals. The trace was steady, and we experienced no trace break-up in the chop mode. The light blue color of the graticule was very easy on the eyes and permitted relatively long term waveform observation without causing optical fatigue.

All controls on the scope are clearly identified, the knobs are shaped and sized for comfortable user "feel," and the controls have positive, smooth action. The combination tilt stand/carrying

handle features a solid locking mechanism in both the carry and tilt positions.

During our tests, we used a pair of optional No. PR-31 combination 10:1/direct probes (\$25) that proved to be excellent for general-purpose work. They feature miniature spring-loaded clip-tips that enable use in circuits where terminals are very tightly spaced.

If you need fast risetime, extended bandwidth, critical circuit timing, and accurate and stable waveform viewing, the Model 1417B is an excellent choice.

CIRCLE NO. 105 ON FREE INFORMATION CARD

An exciting, new magazine!

# Personal Computing


If you don't have your own computer by now, chances are there's one in your immediate future. Personal computers are now being sold at about the price of home stereo systems. Experts project that 1,000,000 personal systems will be up and running by 1980.

*PERSONAL COMPUTING* will serve as your guide into this exciting new technology. We'll provide you with all the up-to-date information on new computer products, computer clubs, computer stores, and important personal computing events. In addition, each issue contains easy-to-follow, nontechnical articles on computer programming and computer jargon. These articles illustrate how you can use personal computers at home, school, and work.
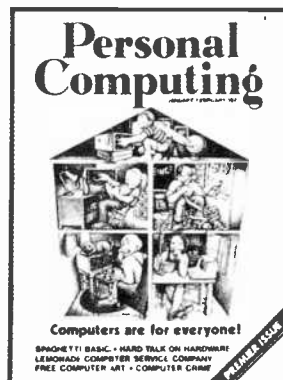
## Get your FREE issue now

Fill out the subscription form below, and we'll send you a complimentary copy. If you don't agree that *Personal Computing* is everything we say it is, simply write "Cancel!" on the invoice and return it to us. If you do want to subscribe, simply pay the bill. In any case, the first issue is on us!

A one year subscription to *PERSONAL COMPUTING* is just \$8.00



Please enter my subscription to *Personal Computing*. I understand that the first issue is free.

Bill me     Enclosed is my check for \$ \_\_\_\_\_  
 BankAmericard     Master Charge     Am Express  
 Credit Card # \_\_\_\_\_

Credit Card Expiration Date \_\_\_\_\_

Name (print) \_\_\_\_\_


Address \_\_\_\_\_

City \_\_\_\_\_

State \_\_\_\_\_ Zip \_\_\_\_\_

Note: *PERSONAL COMPUTING* is a bi-monthly publication (6 issues per year). Rates: \$8/year in the United States. Mexico and Canada: \$10 surface mail and \$12 airmail. All others: \$26 airmail.

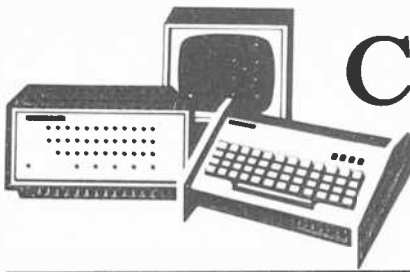**PERSONAL COMPUTING/167 Corey Road, Brookline, MA 02146, USA**



# Computer Bits

By Hal Chamberlin

## DEBUGGING AIDS

**W**HAT DO you use your computer's front panel for? Loading programs into memory, monitoring their execution, altering their execution with the sense switches, single-stepping the program to find errors ("bugs"), changing memory locations, and troubleshooting hardware are some examples. Last month, the role of monitor programs such as Motorola's Mikbug in performing routine computer operation tasks was described here. It should have been apparent that the use of a monitor for such functions is far more convenient than using a traditional front panel. But what about non-routine, troubleshooting tasks such as tracing the execution of a new, untried program or locating a hardware malfunction on a new board? Many hobbyists feel that a control panel is indispensable in such situations. Let us examine how monitor software can be used to perform even these "debugging" functions more effectively than a front panel.

**Breakpoints.** Assume that you have just finished writing a relatively complex program of 200 instructions in machine

language and are ready to test it. First you load it into memory, hopefully using a monitor and keyboard. After loading by hand, you save the program on tape just in case it wipes itself out in memory as errant programs often do. Then using the monitor's "G" command you execute the program. Chances are it does not execute properly. In fact, it's probably not even close. At this point debugging begins, which can take considerable time without good debugging tools.

If you have an Altair, Imsai or other front-panel oriented computer you will probably single-step your way through the program in an effort to find out where it goes awry. This means simply that the computer is placed in a single-step operating mode where every operation of the "single-step" switch causes exactly one machine cycle to be executed. Generally, as each cycle is executed, you can see in the console lights the memory or input/output address referenced by the cycle and the data transferred. Additional status lights identify the type of cycle out of about a half-dozen possibilities. However there are many things that the

panel lights fail to show. For example, when executing an "add register B to register A" instruction in single-step mode, you will only see the memory address of the instruction and the operation code, 200 in octal. You will not see the contents of register A, register B, or the result of the addition. Even the condition flags such as overflow are hidden from view. Obviously the panel is of limited value if you think the root of a particular bug lies in incorrect register contents or if there is an uncertainty as to what a specific instruction does. If this information is critical (as it often is), you must temporarily modify your program to store the necessary data into memory and then halt so that it may be examined.

Another often encountered difficulty is that single-stepping through a loop a dozen times to catch an error that occurs on the thirteenth iteration can take a long time. If the problem occurs on the 387th iteration it would not even be practical to single-step. Again the program must be temporarily modified to make it halt close to the error condition. Such temporary patches are called "breakpoints."

Many monitors have commands or functions that make inserting and keeping track of breakpoints much easier. A command like "3:213B" might insert a breakpoint at location 213 in page 3 (octal notation). What would actually happen is that the monitor would first look at the indicated address and save whatever was there. Next it would store a CALL instruction in the same location which would transfer control to a "breakpoint subroutine" in the monitor. This monitor

\*

### TEST OF DOUBLE PRECISION SUBTRACT

```
001:000 006 123
001:002 016 156
001:004 026 356
001:006 036 312
001:010 315 000 003
001:013 311
```

```
MVI B,123Q          SET BC TO 123:156 = 21358 DECIMAL
MVI C,156Q
MVI D,356Q          SET DE TO 356:312 = -4405 DECIMAL
MVI E,312Q
CALL DSUB           DO THE SUBTRACTION
RET                 RETURN TO THE MONITOR
```

\*

### DOUBLE PRECISION SUBTRACT REGISTERS B AND C FROM D AND E WITH RESULT PLACED IN D AND E

\*

```
003:000 173      DSUB
003:001 221
003:002 137
003:003 172
003:004 230
003:005 127
003:006 311
```

```
MOV A,E           SUBTRACT LOWER BYTES
SUB C
MOV E,A           MOVE RESULT INTO E
MOV A,D           SUBTRACT UPPER BYTES
SBB B
MOV D,A           MOVE RESULT INTO D
RET               RETURN
```

Fig. 1. Program to be traced.

```

002:232 123 3:0,3:6T      (Command to trace between 003:000 and 003:006
002:232 123 1:0G         (Command to start execution at 001:000

003:000 173  A=312 B=123 C=156 D=356 E=312 H=113 L=002 SP=017:374 FLG=
003:001 221  A=130
003:002 137  E=130
003:003 172  A=356
003:004 230  A=203 FLG=SA
003:005 127  D=203

002:232 123 (next command)

```

Fig. 2. Monitor printout with trace.  
Underlined portion typed by user.

routine prints the contents of all registers and the condition flags.

Now that the breakpoint is set up, the program would be entered with the normal "G" command. When it got to the "CALL BREAKPOINT" instruction that was inserted, the registers and flags would be printed. After the printout, the monitor would be waiting for another command. When the breakpoint is no longer needed, an "E" command might erase the breakpoint and restore the instruction it saved.

A more sophisticated monitor could allow multiple breakpoints. It would automatically keep track of the instruction displaced by each breakpoint and identify the breakpoint when the registers were printed. A really good breakpoint routine might even execute the saved instruction after printing and then automatically return to the program being debugged. In this case, a breakpoint could not be placed on top of a JUMP or CALL instruction.

A breakpoint routine can also take care of the "error on the 387th loop" problem mentioned earlier. Each time the breakpoint routine is entered, a software counter is decremented. If the counter is not zero, the user program is re-entered without printing the registers. Only when the counter finally does become zero do the registers get printed—thus saving a lot of time and paper. There would, of course, be a command to set the initial value of the counter.

Some microprocessors make the task of implementing a breakpoint facility in a monitor much easier. In the 8080 a normal CALL instruction is three bytes long. When placed in a breakpoint location, the three bytes that were there have to be saved. These three bytes might represent as many as three separate instructions making the "print registers and continue" function very difficult to implement. The 6800 or 6502, on the other hand, has a one-byte BREAK instruction that seems to be custom designed for just this function.

**Software Single-Step.** Although breakpoint capability in a monitor greatly simplifies the debugging of machine language programs, it is not real single-stepping. A different class of monitor routines called "trace routines" allows the software equivalent of single-stepping. It is interesting to note that some microprocessors are "dynamic" and cannot be stopped to allow the usual hardware single-step function. With these, a trace routine is the only way to get a single-step operation.


Tracing is really equivalent to putting a breakpoint at every instruction in a program. Then when the program is executed, a printout of the location, instruction, and all registers would be given for each instruction executed. This would be exactly equivalent to manual single-stepping with the bonus of a written record of every aspect of the program execution. In a machine with a lot of registers, time and paper may be saved by only printing the registers that have *changed* since the last printout. A useful trace feature in a monitor would allow the setting of *trace limits* so that only the program section of interest would be traced. A fancy trace feature might even allow multiple sets of trace limits with possibly a counter to delay the printing until a specified number of traced instructions has been executed.

How are trace routines actually implemented? One simple method is to use the interrupt feature of the microprocessor itself. With this method, a simple circuit added to the computer is activated to issue an interrupt whenever an instruction is executed. This interrupt would prohibit further interrupts and cause execution of the monitor trace print subroutine. The print routine would not re-enable interrupts until just before it returns to the interrupted program, the one being traced. This prevents the trace print routine from being traced itself. The trace limit feature is implemented by having the trace print routine check if the instruction about to be print-

ed is within the trace limits. If it is not, printing is suppressed and a return to the program is executed. An example is shown in Figs. 1 and 2.

Another method involves *interpreting* the instructions of the traced program rather than executing them. An interpreter is a program that acts just like the microprocessor itself. It literally looks at the operation codes, addresses, and other components of the instruction and, through software, accomplishes the same result as the real microprocessor would have. The purpose of this is that the interpreter program may also store or print detailed information about the instructions it "executes", something the real microprocessor, of course, would not do. This technique requires much more complex software than breakpoints or trace using interrupts does but it has an important advantage. Since the interpreter routine *simulates* the machine, it can also simulate hardware features that the real machine may not have, such as memory protect. While debugging, the simulator would trap any instruction that attempts to jump outside of the protected area as well as any instruction that tries to write into protected memory.

Unfortunately the standard, readily available monitors in read-only memory generally do not have these debugging functions. If anything, a simple breakpoint facility is all that is offered. Specialized monitors, designed primarily for debugging rather than routine operations, on the other hand can probably do everything that has been discussed as well as other handy functions. These monitors are often found in the microprocessor manufacturer's development systems, such as Intel's MDS or Motorola's Exorciser (meaning to "exorcise" bugs) and are quite expensive. However the functions described are not difficult to implement and are certainly worth the effort needed to write them. Club meetings provide opportunities to exchange such software with fellow hobbyists. ◇

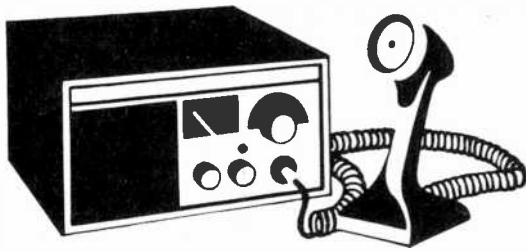

# CB Scene

By Ray Newhall, KW16010

## UNCLE CHARLIE IS SNOWED-IN

**T**HEY tell us that even the ladies' room at Gettysberg is stacked high with mailbags. The FCC offices there process all Class D (now the "Citizens Band Radio Service") license applications and, between January 1st and 26th, had received more than 832,000 new CB license applications. However, reports are that their computer facility has been working so effectively that expected delays in processing those applications which were properly filed are only two to four weeks. To the FCC's delight, no more than 20% of applications received have included fees, which have to be returned since there is no longer a license charge.

Best estimates are that the FCC will issue more than 990,000 CB licenses in January. That represents an increase of more than 50% above the next greatest month (March 1976). The FCC believes that more than 8,000,000 new CB'ers will go on the air during 1977 and that the total number of licenses issued will exceed 16 million by the end of the year.

Total sales do not appear to account for the flood of license applications received. It appears that many would-be CB'ers are taking advantage of the fee amnesty and are being joined by many others who have been operating without a license. Also, different members of the same family are applying for their own licenses. FCC people tell me that, in many cases, a half dozen or so applications are arriving in the same envelope.

**Why Were the Fees Dropped?** As most of you know, the FCC handed CB'ers a nice Christmas present by suspending all fees, effective January 1st 1977. That sudden move was not entirely in the spirit of Christmas, however. It was prompted by a court decision ordering the FCC to suspend *all* fees until fee schedules are restructured, based upon the actual costs for issuance of licenses. In fact, they were ordered to refund all fees collected since January 1975, but don't hold your breath in anticipation; the

FCC's records on CB licensees do not go back that far in many cases. It is likely that fees will be reestablished again within a few months, and Congress might even pass legislation which permits the Commission to charge fees to help support the enforcement effort.

**Some New Developments.** When the fourth general meeting of PURAC was adjourned on January 27, it marked the halfway point in the advisory group's two-year Congressional charter. Earlier that morning the meeting was opened with an address by Al Gross, the first licensed CB'er (19W-0001). He recounted all the early efforts to get CB rolling, dating back to World War II. He showed us a pocket-sized walkie-talkie which had been used by the OSS during the war. It was this tiny radio transceiver that convinced the FCC and others that there was a viable future in personal radio communications.

Based on discussions at the meeting, quick FCC action is likely on a proposal by the public safety task group that the four callsign digits, "0911", be set aside for the exclusive use of state-level public service agencies as an emergency-aid callsign. These special calls, a "K" followed by the State's two-letter abbreviation and the four digits "0911," would be issued to any State applying for licensing under the National Emergency Radio Aid (NEAR) program. For example, in Connecticut the NEAR callsign to summon emergency road assistance on channel 9 would be KCT-0911.

The advisory committee was told that the FCC's Office of Plans and Policy would soon release a radio spectrum inventory report which would study areas of the spectrum for future expansion of Personal Radio Services, including:

- A new FM band somewhere between 218 and 225 MHz.
- Future allocation of a portion of the reserved spectrum near 900 MHz.

A new band of FM frequencies at about 220 MHz ("Class E") was first pro-

posed nearly ten years ago; it now appears that it will be considered anew, but prospects are dim for its adoption. In contrast, the possibility of using 900 MHz for distant CB expansion is viewed more optimistically by the FCC. In any event, the FCC pronounced that the recently expanded 27-MHz band "... won't be eliminated ... is here to stay."

Meanwhile, how many CB'ers have considered moving up to the old Class A band around 465 MHz (now redesignated the General Mobile Radio Service)? Here you can use up to 50 watts of power and antenna heights up to 200 feet. Repeaters and automatic phone patches are permitted. It offers nearly all the features now enjoyed by the hams on the 2-Meter band. However, the equipment is several times the cost of present CB equipment.

From the "Future Needs" Task Group, Cary Hershey, a sociologist at Columbia University, made an interesting observation. In response to a question from the floor regarding the damaging effect of Smokey reports by mobile CB units, he said:

"We have considered the 'Smokey Syndrome' in depth and weighed its negative effects against other factors relating to personal use radio. We have concluded that the sociological advantages to the American public in talking and listening, in direct communication with one another as opposed to all listening only to the media, far outweigh the opportunities offered a minority of criminals using CB to evade the law."

He continued by pointing out that the more inventive law-enforcement agencies have found that the so-called Smokey Syndrome can actually assist their enforcement efforts.

In the area of "Rules Compliance," the committees noted that rules infractions have dropped significantly. They rate the most serious violations as those involving the continued use of "linears" to exceed r-f power output limits and deliberate interference with communications. Though FCC members rate the non-use of callsigns high on their list of violations, the non-FCC members of PURAC tend to down-grade the seriousness of this violation and are examining alternate means of transmitter identification. The primary argument against the Automatic Transmitter Identification Signal (ATIS) involves the management of a data base of information on 30-million or more transmitters. This writer, who is also a data-processing consultant, believes that the FCC will eventually have

## ORGANIZATION OF THE PERSONAL RADIO SERVICES, Part 95

Old Class Designation	New Designation	Part 95 Sub-part
Class A	General Mobile Radio Service	A
Class C	Radio Control (R/C) Service	C
Class D	Citizens Band (CB) Radio Service	D
—	All Technical Specifications	E

to bite the bullet and spend the money to do the job properly. It is an expensive operation.

The FCC is determined to make it very risky to operate overpowered rigs. The reason it is so up-tight about external power amplifiers (linears) is because laboratories operating in both the government and private sectors have now determined that more than 60% of all CB-caused TVI results directly from the use of these illegal devices. This is particularly true with the "cheapie" import varieties that are being sold illegally in the United States. They cause all sorts of havoc on frequencies outside of the CB band, and are illegal to manufacture, sell, or even to own in this country. In spite of this, someone managed to slip a packet of sales material onto the FCC reception table at the PURAC meeting! TVI complaints, mostly CB-related, have increased more than ten-fold over the past two or three years.

It has now also been determined through extensive field tests that modern TV receivers are less susceptible than was originally thought to fundamental signals. Most TVI occurs under conditions of severe front-end overloading of the receiver, whether caused by an antenna preamplifier or by an extremely powerful CB signal. In a recent field test by the FCC's Field Operations Bureau, where 32 randomly selected CB-related TVI complaints were examined in depth, 63% were the direct result of external power amplifiers used to boost the CB signal well above the legal limit.

**Rules Simplification.** I have just completed a review of the reorganized version of Part 95, as reported earlier in this column, and I find it a great improvement over the older versions. These should be readily available through the GPO by the time this column is published. The three classes of personal-use radio services have been renamed under the overall designation of "Personal Radio Services" as shown in the Table listing. The 27 MHz CB service (Class D) has been designated the "Citi-

zens Band (CB) Radio Service." All of Part 95 required to be read and understood by a CB operator is contained in *Sub-part D*. This sub-part will be available as a separate publication.

The PURAC efforts to simplify Part 95 are still not complete. Work is already underway to simplify the language as well as the structure. It is expected that this work will be completed and available to the public by late summer 1977.

**Legal Problems For CB'ers.** As more and more CB'ers go on the air, their legal problems appear to be growing by leaps and bounds. Throughout the country, individual communities are attempting to outlaw CB by the use of local zoning or nuisance ordinances. In Connecticut, for example, there is a statute which was enacted long before CB was authorized making it illegal to operate a radiotelephone in a moving vehicle. Taxis, amateur radio operators, business radio users and commercial radiotelephone are exempted from the law, which appears to leave only CB'ers who can and have been arrested by the State Police. However, there are State Representatives who have pledged to work for the repeal of this law during the current legislative session.

But the number of legal actions which have reached the courts, involving either CB'ers or hams, has increased ten-fold within the past ten years, and a consid-


erable amount of legal precedent is being accumulated. The *Personal Communications Foundation* is a new non-profit legal organization which was formed recently for the purpose of collecting and redistributing all the legal data available on such cases. Its services are free except for the actual cost of reproducing and mailing materials to those attorneys who request it in defense of a personal radio user. If you should have a legal problem, your lawyer may contact them in Lancaster, CA 93534 (805-942-0144). ◇
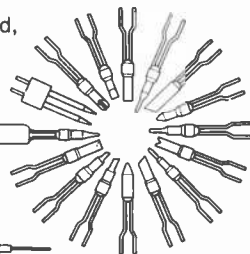
### The quick charge iron with 16 different quick change tips.



**ISO-TIP®**  
**QUICK CHARGE**  
Cordless  
Soldering Iron  
completely  
recharges in  
3½ -4 hours.  
Low voltage,  
battery powered,  
ground free  
isolated tip  
design.

16 snap-in tips  
to fit any job  
plus a PC  
Drill.



**WAHL CLIPPER CORPORATION**  
ORIG. NATORS OF PRACTICAL CORDLESS SOLDERING  
• Sterling, Illinois 61081 • (815) 625-6525  
"Manufacturing Excellence Since 1919"

CIRCLE NO. 66 ON FREE INFORMATION CARD



RAS, our "seeing eye dog," gives drivers ample time to slow down before "the man" records his speed.

This system, the most advanced detector on the market, is designed to minimize false signals.


Simply plug into lighter or wire direct. Select audio/visual or visual only with a flip of a switch.

**ENJOY TRAVEL MORE  
AND WORRY LESS!**

Retail \$109.95

**SPECIAL AT  
\$89.95**

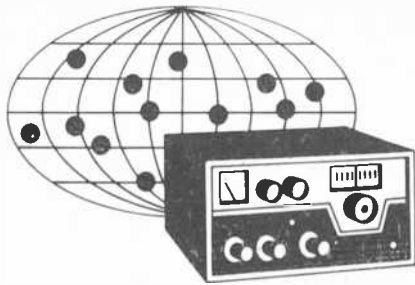**ELECTRONICS UNLIMITED**  
P.O. BOX 73  
LEBANON, TN. 37087  
(615) 449-1901



# DX Listening

By Glenn Hauser

**Secret Shortwave Stations.** If you scan the non-broadcast bands with a good, sensitive receiver for evidence of broadcast programming, you should discover, as we did last fall, a number of tropical-band harmonics in the 18–25 MHz range. Some of them are listed below. As the sunspot count picks up, so should harmonic reception, even up to 31 MHz. Whether you hear the stations listed depends on skip conditions, but there is likely to be less interference on weekends. F<sub>2</sub> propagation peaks around noon, but sporadic E (short skip) can extend into the evening.

In regular out-of-broadcast-band tuning, you'll also find broadcast programs transmitted on SSB. Most feed the remote retransmission sites. Guyana Broadcasting Service is seldom armchair copy on 3.290 or 5.950 MHz, but when they activate 16.454 MHz, listening is easy. Radio Monte Carlo feeds Arabic programs of pop music to its MW relay on Cyprus, via 15.575 or 17.555 MHz frequently heard during the morning in North America. Chilean stations such as Radio Colo-Colo and Radio Cooperativa can be heard on 12.250, 6.6845 or 4.885 MHz at irregular hours.

MHz	Harmonic	Fundamental (MHz)	Station
24.3298	4	6.08245	R. Nacional, Peru
24.024	4	6.006	R. Reloj, Costa Rica
24.020	4	6.005	BBC, Ascension
23.850	2	11.925	Rdif. Portuguesa
23.630	2	11.815	BBC, Ascension
23.610	2	11.805	WYFR, Massachusetts
23.540	2	11.770	BBC, Ascension
19.860	4	4.965	R. Santa Fe, Colombia
19.480	2	9.740	Rdif. Portuguesa
19.328	4	4.832	R. Reloj, Costa Rica
19.210	2	9.605	Deutsche Welle, Antigua
19.100	2	9.550	R. Habana Cuba
19.050	2	9.525	R. Habana Cuba
18.5688	3	6.1896	La Voz de los Centauros, Colombia
18.3456	3	6.1152	La Voz del Llano, Colombia
18.315	3	6.105	La Pantera, Mexico
18.2262	3	6.0754	La Voz del Junco, Honduras
14.835	3	4.945	R. Colosal, Colombia
12.320	2	6.160	Em. Nueva Granada, Colombia

**The World Station.** Matching its image as the "number one" SW service in English, the BBC also publishes the best program guide, "London Calling." New subscribers to the illustrated free monthly had been turned down due to rising costs. But in April BBC began accepting subscriptions from anyone paying the new charge of \$10 per year (630 Fifth Ave., New York, NY 10020). Alternatively, you can consult our fortnightly column, *Short Waves*, in the Roundup section of the Sunday Denver Post.

A few late-April features we can tell you about here: *Theatre of the Air*, Sa-

turdays at 1830 GMT, Sundays at 0030 and 1130, presents Anouilh's "Antigone," Apr. 23/24. *Radio Theatre*, Sun. 1900, Thurs. 1345, Fri. 0030 has James Fairfax plays, "No Holds Barred," Apr. 17/21/22, and "Let's Play Politics," Apr. 24/28/29. Documentaries, Sun. 1709, Tues. 0030, Thurs. 1130 are "The Right Sort of Food," Apr. 17/19/21, and "The Changing Role of the Ambassador," Apr. 24/26/28. And Wed. 1430, Thurs. 0030, Fri. 2030, "One Hundred Years of Recorded Sound," Apr. 20/21/22, and "Shakespeare on Record," Apr. 27/28/29.

**DX Programs.** Radio Nederland is broadcasting a "Communications System Course" covering radio, TV, radar, navigation and radio astronomy, written by Jim Vastenhou. Besides broadcasting each lesson two weeks in a row, printed lessons and illustrations are available free. You can still enroll in this course, which began April 7 on the Thursday "DX Juke Box" programs, and continues through the summer. R. Nederland is also celebrating 50 years of SWBC with a special QSL card, and yours truly is celebrating his 10th anniversary as a DX correspondent on the April 21 program. You can also hear our DX report in Spanish, the second Friday of each month on "Espacio DX-ista."

DX listeners are invited to participate in or monitor a ham net discussing all phases of DX'ing and SWL'ing, Wednesdays at 2130 GMT on 7.275 ± 0.005 MHz (perhaps an hour earlier by GMT during daylight time). NCS is Charles, WB9NWF. Medium-wave DX'ers exchange tips Monday mornings at 0700 (0600 GMT, starting in May) on 3.900 MHz; listen for Skip, K0SBV, or Ross, W9BG.

The hams also operate a well-organized "intruder watch" designed to expunge non-ham stations from their bands, and qualified SWL's are invited to help. Contact the ARRL Intruder Watch, E. H. Conklin, K6KA, 402 Oliveta Pl., Box 1, La Cañada, CA 91011.

**Mark Your Calendar.** The International Committee of the Red Cross broadcasts only 4 hours a day, 3 days a week, 6 weeks a year, making its QSL more of a prize than others from Switzerland. Here's the schedule, via SBC on 7.210 MHz, for the rest of 1977: May 23/25/27; July 25/27/29; Sept. 26/28/30; Nov. 21/23/25, at 0600-0700, 1130-1230, 1700-1800, 2200-2300 GMT. The last, and possibly the first, have a chance of being heard in North America this time of year. Mondays are in English; Wednesdays, French/German; and Fridays, Spanish/Arabic.

If you make a point of listening to certain stations on important dates, you may hear extended or special programming. For a starter, try 5.047 MHz on April 27, Togo's National Day. Deutsche Welle is 24 years old on May 3. Liberation Day in Czechoslovakia is May 9, and R. Prague itself marks 54 years on May 18. Cameroun stations on 4.9725 and 5.010 MHz may observe National Day on May 20. Guyana Independence Day is May 26, a good time to check



16.454 MHz. May 31 is Republic Day in South Africa. Tunisia's National Day is June 1, and June 2 is Italy's Day of the Republic. Haiti's 4VEH celebrates 27 years on the air June 2—check 9.770 and 11.834 MHz. FEBC, Philippines is

29 on June 4, while Philippine Independence Day is June 12. Republic Day in Iceland, June 17, just might bring some special transmission on 12.175 MHz. (Dates were compiled by Cees van der Zalm for the Benelux DX Club.)

## MAY-AUGUST ENGLISH-LANGUAGE SW B'CASTS by Richard E. Wood

### TO EASTERN NORTH AMERICA

TIME-EDT	TIME-GMT	STATION	QUAL*	FREQUENCIES, MHz
6:28 a.m.-8:00 p.m.	1028-2400	**Montreal, Canada (Northern Service)	G	9.625, 11.72 (includes French, etc.)
7:00-7:25 a.m.	1100-1125	Tirana, Albania	F	9.50, 11.865
7:00-9:00 a.m.	1100-1330	Melbourne, Australia	G	9.58
7:00-9:30 a.m.	1100-1330	London, England	G	5.99 (via Sackville), 6.195 (via Antigua), 11.79 (via Antigua, tentative by midsummer) 15.07
7:00-10:00 a.m.	1100-1400	**VOA, Washington, USA	G	5.955, 9.73
7:05-8:25 a.m.	1105-1225	Trans-World Radio, Bonaire, N.A.	G	11.815
7:45-8:05 a.m.	1145-1205	**Montreal, Canada	G	9.56, 11.72
8:00-8:30 a.m.	1200-1230	Jerusalem, Israel	G	11.655, 15.10, 15.485, 17.685
8:00-8:55 a.m.	1200-1255	Peking, China	F	11.685
8:10-8:30 a.m.	1210-1230	**Santiago, Chile	F	9.566, 11.81, 15.15
8:15-8:30 a.m.	1215-1230	Athens, Greece	F	15.345, 17.83
		HCB, Quito, Ecuador	G	11.745
8:30-9:00 a.m.	1230-1300	Stockholm, Sweden	G	15.305
8:30-10:00 a.m.	1230-1400	Trans-World Radio, Bonaire, N.A.	G	15.255 (Sat., Sun.)
8:30-11:30 a.m.	1230-1630	HCB, Quito, Ecuador	G	11.745, 15.115
9:15-9:45 a.m.	1315-1345	Berne, Switzerland	G	15.14
9:30-10:00 a.m.	1330-1400	Helsinki, Finland	G	15.11
9:30-11:00 a.m.	1330-1500	**London, England	G	15.07
10:00-10:15 a.m.	1400-1415	**Montreal, Canada	G	15.325, 17.74
10:00-10:30 a.m.	1400-1430	Oslo, Norway	G	15.175 (Sun.)
		Stockholm, Sweden	G	15.305
10:30-11:00 a.m.	1430-1500	Helsinki, Finland	G	15.11
11:00 a.m.-12 noon	1500-1600	London, England	G	17.84 (via Ascension), 9.58 (via Sackville Sat., Sun.)
11:15-11:30 a.m.	1515-1530	Athens, Greece	P	11.73, 15.345, 17.83
12 noon-12:15 p.m.	1600-1615	London, England	G	9.58 (via Sackville)
		Oslo, Norway	G	17.84 (via Ascension)
12:00 noon-12:30 p.m.	1600-1630	Oslo, Norway	G	15.175 (Sun.)
12:04-12:56 p.m.	1604-1656	**Paris, France	G	15.20, 15.30, 15.425, 17.72, 17.80, 17.82, 21.62
12:15-2:30 p.m.	1615-1830	London, England	G	9.58 (via Sackville), 15.07
1:00-4:00 p.m.	1700-2000	**Kuwait, Kuwait	F	9.555, 9.58, 11.845
2:00-2:30 p.m.	1800-1830	**Montreal, Canada	G	11.855, 15.325, 17.82
		**Kampala, Uganda	F	15.325 (Tues., Thur., Sat., Sun.)
		**Montreal, Canada	G	11.855, 15.325, 17.82
2:30-3:00 p.m.	1830-1900	**Abidjan, Ivory Coast	G	11.92 (Sun.)
2:50-4:00 p.m.	1850-2000	**Montreal, Canada	G	11.855, 15.325, 17.82
3:00-3:30 p.m.	1900-1930	**Algiers, Algeria	F	11.91, 15.42 (variable)
3:00-4:00 p.m.	1900-2000	**Jeddah, Saudi Arabia	F	11.855
3:00-6:00 p.m.	1900-2200	**Montreal, Canada	G	11.855, 15.42, 17.82
3:30-4:00 p.m.	1930-2000	**Montreal, Canada	G	15.29, 15.325, 17.82
4:00-4:30 p.m.	2000-2030	**Tehran, Iran	F	9.022, (11.77 alternate)
		Jerusalem, Israel	G	9.009, 9.425, 9.815, 11.655, 15.10
4:00-5:00 p.m.	2000-2100	Accra, Ghana	F	11.85 (irregular)
4:00-5:20 p.m.	2000-2120	**Hilversum, Holland	G	11.73 (via Talata)
4:50-5:50 p.m.	2050-2150	**Havana, Cuba	G	11.865, 17.75
5:00-5:30 p.m.	2100-2130	**Brazzaville, Congo	G	15.19
5:00-5:50 p.m.	2100-2150	**Johannesburg, S. Africa	F	5.98, 9.585
5:00-6:00 p.m.	2100-2200	**Brasilia, Brazil	G	15.24 (11.78, 15.245 alternate)
5:15-6:45 p.m.	2115-2245	London, England	G	9.58, 11.75
5:30-6:50 p.m.	2130-2250	Hilversum, Holland	G	9.715, 11.73 (exc. Sun.)
6:00-6:15 p.m.	2200-2215	**Belgrade, Yugoslavia	F	6.10, 7.24, 9.62
6:00-6:30 p.m.	2200-2230	**Montreal, Canada	G	11.855, 15.325
		Oslo, Norway	F	15.175 (Sun.)
		**Caracas, Venezuela	F	15.40 (varies, Mon.-Fri.)
6:00-7:15 p.m.	2200-2315	**Cairo, Egypt	G	9.805
6:00-8:30 p.m.	2200-0030	Ankara, Turkey	G	5.515, 11.88
6:30-7:00 p.m.	2230-2300	Jerusalem, Israel	G	9.435, 9.815, 11.655, 15.10, 15.485
		Moscow, U.S.S.R.	G	7.105, 7.15, 7.355, 7.40, 9.655, 9.685
		Johannesburg, S. Africa	F	11.735, 11.75, 11.87, 12.05
6:30-7:20 p.m.	2230-2320	Johannesburg, S. Africa	F	5.98, 9.585, 11.90
6:45-7:00 p.m.	2245-2300	London, England	G	5.975, 7.325, 9.58, 11.75

MAY 1977

## CATCH-A-PULSE II<sup>®</sup> LOGIC PROBE

10 Nsec SPEED AT  
3.5 to 15V LEVELS  
ONLY \$39.95



Compatible with RTL, DTL, TTL, CMOS, MDS, and Microprocessors using a 3.5 to 15V power supply. Thresholds automatically programmed. Automatic resetting memory. No adjustment required. Visual indication of logic levels, using LEDs to show high, low, bad level or open circuit logic and pulses. Highly sophisticated, shirt-pocket portable [protective tip cap and removable coil cord]. Eliminates need for heavy test equipment. A definite savings in time and money for engineer and technician.

- 10 Nsec pulse response
- Open circuit detection
- Multi-family
- Replaceable tip & cord
- High input impedance
- Pulse stretching

Send \$39.95 (Calif. residents add 6% sales tax) to:

Pat. Pend. Dealer inquiries welcome  
**AR ELECTRONICS**  
Box 26205, San Diego, CA 92126, (714) 566-1570

CIRCLE NO. 2 ON FREE INFORMATION CARD

**\* SAVE GAS! SAVE on TUNE-UPS!**  
MODERNIZE and Bring Your Car "UP-TO-DATE" with the MOST EFFICIENT Ignition ever Invented!



**\* THE "XR-700" is a COMPLETELY NEW Ignition System that replaces the inefficient Breaker-Points and Condenser with a highly RELIABLE, Invisible "Infra-red" Light-Beam which CONTROLS the Latest design Solid-State POWER MODULE. This new "Patented" invention produces the HIGHEST ENERGY, Longest Duration Spark of ANY Ignition System manufactured TODAY!**

**\* CUSTOMERS REPORT: "THE XR-700 MORE THAN PAYS FOR ITSELF ...and KEEPS ON SAVING MONEY with..."**

- ★ INCREASED "GAS-MILEAGE" up to 30%!
- ★ ELIMINATING COSTLY "TUNE-UPS!"
- ★ IMPROVED ENGINE PERFORMANCE!
- ★ QUICKER STARTING IN ANY WEATHER!
- ★ FASTER ACCELERATION...SMOOTHER RUNNING!
- ★ PLUGS LAST UP TO 4-TIMES AND LONGER!

**\* THE XR-700 has NO moving parts to wear out...never needs adjustment! Engineered to OUTLAST Your Car...So RELIABLE...So PERFECTED...that we give you a LIFETIME WARRANTY... "FREE Repair or Replacement" for as long as you OWN the Unit...even if you change Cars, we will supply the necessary Parts FREE.**

- \* FITS ALL ENGINES...Domestic or Foreign...4, 6 or 8-Cylinder
- \* EASY INSTALLATION...Completely Factory ASSEMBLED!

Thousands sold at \$59.95  
**\* NOW... ONLY... \$39.95** (Cal. Res. add Tax)  
THAT'S EVERYTHING... INCLUDING POSTAGE & INSURANCE

**\* SAVE! ORDER FACTORY DIRECT!**  
Send Check or M/O, State Car Make, Year and No. of Cylinders.

**\* MASTERCHARGE or BANKAMERICARD Cardholders**  
Order by TOLL FREE PHONE (800) 423-6525 Ext. 3

**\* CALL or WRITE for FREE BROCHURE**

**\* America's Oldest and Largest Manufacturer of Opto-Electronic Ignition Systems. ©**



**ALLISON AUTOMOTIVE CO.**

1267 - PO, East EDNA PL., COVINA, CAL. 91722


CIRCLE NO. 7 ON FREE INFORMATION CARD
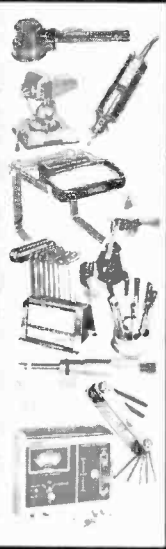
# FREE catalog

of over  
**2000**  
small tools,  
measuring  
instruments,  
and supplies



- ELT. COL. DRILLS
- FILM LOADERS
- PS. PAGES GRAVERS
- GRINDERS HAMMERS
- INCLINOMETERS JACKS
- KNIVES LATHES LEATHER
- ETTES LOUPES MINIATURE
- TOOLS METRIC TOOLS MULTI
- TESTERS NEGATIVE FILES
- NIPPERS OILERS PIN VISES
- PLIERS PROBES RIFFLERS
- SCISSORS SNARES SOLDER
- ING SUPPLIES TEST INSTRU
- MENTS TWEEZERS VIEWERS
- VISES WRENCHES
- AOH ABRASIVES
- G BOOKS
- LIMATORS
- EPOXIES
- CALIPERS



**National Camera**  
2000 West Union Ave. Dept. GGA  
Englewood, Colo., U.S.A. 80110

CIRCLE NO. 39 ON FREE INFORMATION CARD

# SAVE!

MONEY • TIME • FREIGHT

QUALITY STEREO EQUIPMENT  
AT LOWEST PRICES.

YOUR REQUEST FOR QUOTA-  
TION RETURNED SAME DAY.

FACTORY SEALED CARTONS—  
GUARANTEED AND INSURED.

SAVE ON NAME BRANDS LIKE:  
A.D.C. KLH  
A.R. SHURE  
DYNACO KOSS  
SONY FISHER

PIONEER  
AND MORE THAN 50 OTHERS  
BUY THE MODERN WAY  
BY MAIL—FROM



Department 217S  
12 East Delaware  
Chicago, Illinois 60611  
312-664-0020

CIRCLE NO. 31 ON FREE INFORMATION CARD


6:50-7:10 p.m.	2250-2310	**Santiago, Chile	F	9.56, 11.81, 15.15
7:00-7:30 p.m.	2300-2330	Stockholm, Sweden	G	6.12, 9.695, 11.705
		Moscow, U.S.S.R.	G	7.105, 7.15, 7.355, 7.40, 9.685, 11.735, 11.75, 11.87, 12.05, 9.655, 9.72, 9.745, 11.77, 11.90 (Sat., Sun.)
		Vilnius, U.S.S.R.	G	11.71 (Mon.-Fri.)
7:00-7:50 p.m.	2300-2350	**Buenos Aires, Argentina	G	11.755
7:30-8:00 p.m.	2330-2400	Helsinki, Finland	P	
		**Radio Clarin, S. Domingo, Dom. Rep.	G	11.70 (irregular)
		London, England	G	5.975, 6.12 (via Antigua, tent. by midsummer) 7.325, 9.58
7:30-8:30 p.m.	2330-0030	Moscow, U.S.S.R.	G	7.105, 7.355, 7.40, 9.655, 9.685, 9.72, 9.745, 11.735, 11.75, 11.77, 11.87, 11.90, 12.05
7:45-8:45 p.m.	2345-0045	Tokyo, Japan	F	15.27, 15.30
8:00-8:25 p.m.	0000-0025	Tirana, Albania	G	7.065, 9.75 (varies)
8:00-8:30 p.m.	0000-0030	Oslo, Norway	F	9.645, 11.86 (Sun.)
8:00-8:55 p.m.	0000-0055	Sofia, Bulgaria	G	9.70 (alternate 9.705)
		Peking, China	F	11.675, 11.945, 15.06
8:00-9:00 p.m.	0000-0100	**VDA, Washington, USA	G	6.19, 9.67, 11.83, 11.895
8:00-10:45 p.m.	0000-0245	**Luxemburg	F	6.09
8:00 p.m.-1:06 a.m.	0000-0506	**Montreal, Canada (Northern Service)	F	6.065, 9.625
8:15-8:30 p.m.	0015-0030	Brussels, Belgium	G	9.725
8:30-8:55 p.m.	0030-0055	Prague, Czechoslovakia	F	6.055, 9.74
8:30-9:00 p.m.	0030-0100	Stockholm, Sweden	F	11.955
		Kiev, U.S.S.R.	G	9.60, 9.61, 11.69, 11.735, 12.05
8:30-9:30 p.m.	0030-0130	Moscow, U.S.S.R.	G	7.15, 9.53, 9.655, 9.685
		**Trans-World Radio, Bonaire, N.A.	G	11.925
8:30-11:30 p.m.	0030-0330	London, England	G	5.975, 6.12 (via Antigua, tent. by midsummer) 7.325, 9.51, (via Greenville), 9.58 (via Ascension)
8:40-11:00 p.m.	0040-0300	HCJB, Quito, Ecuador	G	9.56, 11.915
9:00-9:15 p.m.	0100-0115	Vatican, City	G	5.995, 9.605, 11.70
9:00-9:20 p.m.	0100-0120	Rome, Italy	G	9.575, 11.91
9:00-9:30 p.m.	0100-0130	Vilnius, U.S.S.R.	G	7.15, 7.215, 9.61, 11.69, (Sat., Sun.) 9.535
9:00-9:45 p.m.	0100-0145	Berlin, Ger. Dem. Rep.	P	9.73
9:00-9:55 p.m.	0100-0155	Peking, China	G	7.12, 9.78 (via Tirana), 9.94, 11.945, 15.06
9:00-11:00 p.m.	0100-0300	Prague, Czechoslovakia	G	5.93, 7.345, 9.54, 9.63, 9.74, 11.99
9:00-11:30 p.m.	0100-0330	Melbourne, Australia	G	15.32, 17.795
9:00 p.m.-12 mdt.	0100-0400	Havana, Cuba	G	11.725, 11.93
		Madrid, Spain	G	6.08, (alternate 6.065) 11.88 (exp. Sun)
9:10-9:30 p.m.	0110-0130	**Santiago, Chile	F	9.566, 11.81, 15.15
9:30-9:50 p.m.	0130-0150	Cologne, Ger. Fed. Rep.	G	6.01, 6.04 (via Antigua), 6.075, 9.565, 9.605
9:30-9:55 p.m.	0130-0155	Tirana, Albania	G	6.20, 7.30
		Vienna, Austria	P	6.155, 9.77
9:30-10:25 p.m.	0130-0225	Bucharest, Rumania	F	5.99, 9.57, 9.68, 11.775, 11.94
9:30-10:30 p.m.	0130-0230	Moscow, U.S.S.R.	G	7.15, 7.215, 9.53, 9.685, 9.70 (via Sofia)
9:45-10:15 p.m.	0145-0215	Berne, Switzerland	G	5.965, 6.135, 9.725, 11.715
10:00-10:30 p.m.	0200-0230	Budapest, Hungary	G	6.00, 7.215, 9.585, 9.833, 11.91 (Exc. Sun.)
		Oslo, Norway	F	9.645, 11.86, 15.175 (Sun.)
		Montreal, Canada	G	6.085, 9.535
		Warsaw, Poland	P	6.095, 6.135, 7.27, 9.675, 11.815, 11.84, 15.12
10:00-10:55 p.m.	0200-0255	Peking, China	F	9.94, 12.01, 12.055
10:00-11:20 p.m.	0200-0320	Hilversum, Holland	G	6.165 (via Bonaire)
10:00-11:30 p.m.	0200-0330	Cairo, Egypt	G	9.475
10:10-10:30 p.m.	0210-0230	**Santiago, Chile	F	9.566, 11.81, 15.15
10:15-10:30 p.m.	0215-0230	Athens, Greece	F	9.75, 9.76, 11.73
10:30-10:55 p.m.	0230-0255	Tirana, Albania	G	6.20, 7.30
10:30-11:00 p.m.	0230-0300	Stockholm, Sweden	F	9.695, 11.705
		Moscow, U.S.S.R.	G	7.39, 9.50, 9.53, 9.61, 9.685, 9.70 (via Sofia)
10:30-11:15 p.m.	0230-0315	Berlin, Ger. Dem. Rep.	P	9.73
11:00-11:30 p.m.	0300-0330	Budapest, Hungary	F	6.00, 7.215, 9.585, 9.833, 11.91 (Tues., Fri.)
		Kiev, U.S.S.R.	G	7.39, 9.61
		Lisbon, Portugal	F	6.025, 11.935
		Moscow, U.S.S.R.	G	9.50, 9.685, 9.70 (via Sofia)
11:00-11:35 p.m.	0300-0335	Warsaw, Poland	P	6.095, 6.135, 7.27, 9.675, 11.815, 11.84, 15.12
11:00-11:55 p.m.	0300-0355	Peking, China	G	7.12, 9.78 (via Tirana)
11:00 p.m.-12 mdt.	0300-0400	Buenos Aires, Argentina	G	9.69 (Mon.-Fri.)
		Prague, Czechoslovakia	G	5.93, 7.345, 9.54, 9.63, 9.74, 11.99
11:00-12:25 a.m.	0300-0425	**Johannesburg, S. Africa	F	5.98, 7.27
11:00 p.m.-1:00 a.m.	0300-0500	HCJB, Quito, Ecuador	G	6.095, 9.56, 11.915
11:10-11:30 p.m.	0310-0330	**Santiago, Chile	F	9.566, 11.81, 15.15

11:30-11:55 p.m.	0330-0355	Tirana, Albania	G	6.20, 7.30
		Vienna, Austria	P	6.155, 9.77
11:30 p.m.-12 mdt.	0330-0400	Moscow, U.S.S.R.	G	7.39, 9.50, 9.61, 9.685, 9.70 (via Sofia)
11:30 p.m.-12:30 a.m.	0330-0430	London, England	G	5.975, 6.12 (via Antigua, tent. midsummer)
11:30 p.m.-12:50 a.m.	0330-0450	Havana, Cuba	G	11.725, 11.76, 11.93
12:00 mdt.-12:15 a.m.	0400-0415	Budapest, Hungary	G	6.00, 7.215, 9.585, 9.833, 11.91 (Tues., Fri.)
12:00 mdt.-12:25 a.m.	0400-0425	Bucharest, Rumania	F	5.99, 6.155, 6.19, 9.57, 9.68, 11.775, 11.94
12:00 mdt.-12:30 a.m.	0400-0430	Oslo, Norway	F	9.645, 11.86 (Sun.)
12:30-1:00 a.m.	0430-0500	London, England	G	6.175 (via Antigua)
12:50 p.m.-2:00 a.m.	0450-0600	Havana, Cuba	G	11.725, 11.93
1:00-1:15 a.m.	0500-0515	Jerusalem, Israel	G	7.412, 9.815, 11.655
1:00-1:30 a.m.	0500-0530	Lisbon, Portugal	G	6.025, 11.935
1:00-3:00 a.m.	0500-0700	HCJB, Quito, Ecuador	G	6.095, 9.56
1:00-3:30 a.m.	0500-0730	London, England	G	6.175, (via Antigua) 9.51 (via Antigua, tent. by midsummer)

**TO WESTERN NORTH AMERICA**

TIME-PDT	TIME-GMT	STATION	QUAL*	FREQUENCIES, MHz
4:00-4:15 a.m.	1100-1115	Tokyo, Japan	P	5.99
4:00-5:25 a.m.	1100-1225	Trans-World Radio, Bonaire, N.A.	G	11.815
4:00-6:30 a.m.	1100-1330	London, England	G	5.99 (via Sackville), 6.196 (via Antigua), 11.75 (via Tebrau), 11.79 (via Antigua tent. midsummer)
4:00-7:00 a.m.	1100-1400	**VOA, Washington, USA	G	5.955, 9.73
		**4VEH, Cap-Haitien, Haiti	G	9.77, 11.835
5:00-5:15 a.m.	1200-1215	Tokyo, Japan	P	5.99
5:00-5:30 a.m.	1200-1230	**Tashkent, U.S.S.R.	G	9.60, 11.925
5:10-5:30 a.m.	1210-1230	**Santiago, Chile	F	6.195, 9.566, 11.81, 15.15
5:15-5:30 a.m.	1215-1230	HCJB, Quito, Ecuador	G	11.745
5:30-7:00 a.m.	1230-1400	Trans-World Radio Bonaire, N.A.	G	15.255 (Sat., Sun.)
5:30-9:30 a.m.	1230-1630	HCJB, Quito, Ecuador	G	11.745, 15.115
6:00-6:15 a.m.	1300-1315	Tokyo, Japan	P	5.99
6:30-6:50 a.m.	1330-1350	**Santiago, Chile	F	6.195, 9.566, 11.81, 15.15
6:30-8:00 a.m.	1330-1500	**Delhi, India	F	11.81
7:00-7:30 a.m.	1400-1430	Tokyo, Japan	G	9.505
		**Tashkent, U.S.S.R.	G	9.60, 11.925
7:00-8:20 a.m.	1400-1520	**Hilversum, Holland	G	11.73 (via Talata)
7:00-9:55 a.m.	1400-1655	Manila, Philippines (VOP)	F	9.58 (Closes 1555 Sun.)
8:00-8:15 a.m.	1500-1515	Tokyo, Japan	G	9.505
8:00-9:00 a.m.	1500-1600	London, England	G	17.84 (via Ascension) also 9.58 (via Sackville Sat., Sun.)
9:00-9:15 a.m.	1600-1615	Tokyo, Japan	G	9.505
		London, England	G	9.58, 15.365 (via Sackville), 17.84 (via Ascension)
9:04-9:56 a.m.	1604-1656	**Paris, France	G	15.20, 15.30, 15.425, 17.72, 17.80, 17.82, 21.62
9:15-10:09 a.m.	1615-1809	London, England	G	9.58, 15.365 (via Sackville)
9:42-9:51 a.m.	1642-1651	Hilversum, Holland	G	15.19, 17.775 (Mon.-Fri.)
10:00-10:15 a.m.	1700-1715	Tokyo, Japan	G	9.505
10:00 a.m.-1:00 p.m.	1700-2000	**Kuwait, Kuwait	F	9.555, 9.58, 11.845
10:09-11:00 a.m.	1709-1800	London, England	G	9.58, (via Sackville)
11:00-11:09 a.m.	1800-1809	London, England	G	9.58 (via Sackville), 11.815 (via Ascension)
11:00-11:15 a.m.	1800-1815	Tokyo, Japan	G	15.105
11:00-11:30	1800-1830	**Kampala, Uganda	F	15.325, (Tues., Thur., Sat., Sun.)
		Oslo, Norway	F	11.895 (Sun.)
11:45 a.m.-1:00 p.m.	1845-2000	**Abidjan, Ivory Coast	G	11.92 (Sun.)
12 noon-12:15 p.m.	1900-1910	**Papeete, Tahiti	F	11.825, 15.17 (exc. Sun.)
12:00-12:15 p.m.	1900-1915	Tokyo, Japan	G	15.105
1:00-1:15 p.m.	2000-2015	Tokyo, Japan	G	15.105
1:00-2:20 p.m.	2000-2120	Hilversum, Holland	G	11.73 (via Talata)
1:30-1:50 p.m.	2030-2050	**Santiago, Chile	F	9.566, 11.81, 15.15
1:30-2:00 p.m.	2030-2100	**Kampala, Uganda	F	9.73 (Sat., Mon. Wed., Fri.)
2:00-2:15 p.m.	2100-2115	Tokyo, Japan	G	15.105
2:00-2:30 p.m.	2100-2130	**Brazzaville, Congo	G	15.19
2:00-3:00 p.m.	2100-2200	**Brazilia, Brazil	G	15.24 (alternates 11.78, 15.245)
2:30-3:30 p.m.	2130-2230	**Taipei, Taiwan	F	15.225
3:00-3:15 p.m.	2200-2215	Tokyo, Japan	G	15.105
3:00-3:30 p.m.	2200-2235	**Caracas, Venezuela	F	15.40 (varies; Mon.-Fri.)
3:00-5:00 p.m.	2200-2400	**VOA, Washington, USA Montreal, Canada	G	17.82, 17.895, 21.61 F 5.96 (Mon.-Fri.)
3:30-4:00 p.m.	2230-2300	Jerusalem, Israel	G	9.435, 9.815, 11.655, 15.10, 15.485
3:30-4:20 p.m.	2230-2320	Johannesburg, S. Africa	F	5.98, 9.585, 11.90
3:30-5:30 p.m.	2230-0030	Moscow, U.S.S.R.	G	9.635, 9.78, 12.05, 15.14, 15.18, 15.455, 17.72
3:50-4:10 p.m.	2250-2310	**Santiago, Chile	F	9.566, 11.81, 15.15
4:00-4:30 p.m.	2300-2330	Tokyo, Japan	G	15.105
4:00-5:00 p.m.	2300-2400	**Pyongyang, Dem. Rep. Korea	F	11.535, 15.63 (variable)

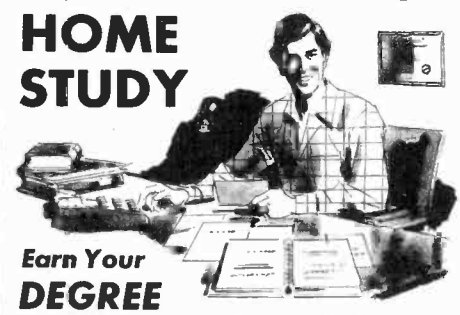Put Professional Knowledge and a  
**COLLEGE DEGREE**  
in your Electronics Career through  
**HOME STUDY**



**Earn Your DEGREE**

by correspondence, while continuing your present job. No commuting to class. Study at your own pace. Learn from complete and explicit lesson materials, with additional assistance from our home-study instructors. Advance as fast as you wish, but take all the time you need to master each topic. Profit from, and enjoy, the advantages of directed but self-paced home study.

The Grantham electronics degree program begins with basics, leads first to the A.S.E.T. degree, and then to the B.S.E.E. degree. Our free bulletin gives complete details of the program itself, the degrees awarded, the requirements for each degree, and how to enroll. Write for *Bulletin E-77*.

**Grantham College of Engineering**

2000 Stoner Avenue  
P. O. Box 25992  
Los Angeles, CA 90025

Worldwide Career Training thru Home Study  
CIRCLE NO. 27 ON FREE INFORMATION CARD

**COMPUTER MUSIC?**



**OUR EQUALLY TEMPERED D/A CONVERTER**

**MAKES IT EASY!**

- : 5+ octaves of control voltage from 6 bits of data.
- : hand-shaking logic.
- : use with any processor.
- : drives even the simplest linear oscillators & filters.

**8780 D/A CONVERTER KIT . . . \$34.95**  
(plus \$1.00 postage for mail orders)

**8782 ENCODED KEYBOARD . . . \$109.95 . . . wt. 20 lbs.**  
**COMPLETE SYNTHESIZER PACKAGES AS LOW AS \$239**  
**MODULES; VCO's, VCF's, NOISE SOURCES, & MORE**  
• keyboards shipped freight collect

**DETAILS IN OUR FREE CATALOG**



DEPT 5-P  
1024 W. WILSHIRE BLVD.  
OKLAHOMA CITY, OK 73116

CIRCLE NO. 45 ON FREE INFORMATION CARD


# HEAR-IT-YOURSELF KIT



This is a Speakerlab 7, a 4-element acoustic suspension speaker kit you can assemble yourself in an hour with simple tools.

It saves you up to 50% over comparable ready made systems. Read about the S7 and other systems and raw speakers we sell in a new 40 page catalog. It's a fact-packed manual with chapters on acoustic theory, enclosures, choosing drivers and design principles.

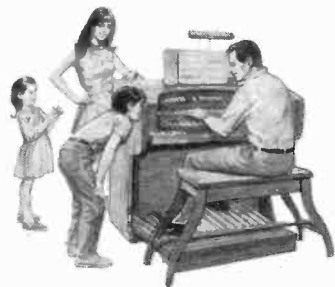And it's free. Just write us and ask for the most complete catalog/manual ever written on speaker building.



## Our whole family helped assemble this wonderful Schober Organ... and now we all play it!

Talk about real family fun! We all worked together, for a few hours almost every day. Almost too soon, our Schober Organ was finished. Our keen-eyed daughter sorted resistors. Mom soldered transistor sockets, although she'd never soldered anything before. And it did our hearts good to see the care with which our son—he's only 12—installed the transistors. Me? I was the quality control inspector—they let me do the final wiring.

Our completed Schober Organ compares favorably with a "ready-made" one costing twice as much! (The five models range from \$650 to \$2850.)

Just send the coupon for the fascinating Schober color catalog (or enclose \$1 for a 12-inch LP record that lets you hear as well as see Schober quality).

The Schober Organ Corp., Dept. PE-71  
43 West 61st Street, New York, N.Y. 10023

- Please send me Schober Organ Catalog.  
 Enclosed please find \$1.00 for 12-inch L.P. record of Schober Organ music.

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

CITY \_\_\_\_\_ STATE \_\_\_\_\_ ZIP \_\_\_\_\_

4:00-4:30 p.m.	2300-2330	London, England	G	6.175, 9.51 (via Sackville), 9.58 (via Ascension)
4:30-5:00 p.m.	2330-2400	**Radio Clarin, S. Domingo, Dom. Rep.	G	11.70 (irregular Mon.-Fri.)
4:30-5:30 p.m.	2330-0030	London, England	G	6.12 (via Antigua tent. by midsummer) 6.175, 9.51 (via Sackville)
5:00-5:15 p.m.	0000-0015	Tokyo, Japan	G	15.105
5:00-6:00 p.m.	0000-0100	**VOA, Washington, USA	G	11.83, 11.895, 15.40
5:30-6:00 p.m.	0030-0100	Moscow, U.S.S.R.	G	9.635, 9.78, 12.05, 15.14, 15.18, 15.455, 17.72
5:30-6:30 p.m.	0030-0130	**Trans-World Radio, Bonaire, N.A.	G	11.925
5:30-8:30 p.m.	0030-0330	London, England	G	6.12 (via Antigua, tent. by midsummer) 6.175 (via Sackville), 9.51 (via Greenville), 9.58 (via Ascension)
5:40-8:00 p.m.	0040-0300	HCJB, Quito, Ecuador	G	9.56, 11.915
6:00-6:15 p.m.	0100-0115	Tokyo, Japan	G	15.105
6:00-6:30 p.m.	0100-0130	Moscow, U.S.S.R.	G	9.635, 9.78, 12.05, 15.14, 15.18, 15.455
6:00-7:00 p.m.	0100-0200	Taipei, Taiwan	F	15.425, 17.89
6:00-8:00 p.m.	0100-0300	Melbourne, Australia	G	15.32, 17.795
6:00-9:00 p.m.	0100-0400	Madrid, Spain	F	6.08, (alternate 6.065), 11.88
6:10-6:30 p.m.	0110-0130	**Santiago, Chile	F	6.195, 9.566, 11.81, 15.15
7:00-7:30 p.m.	0200-0230	Moscow, U.S.S.R.	G	9.635, 9.78, 11.86, 12.05, 15.14
7:30-8:00 p.m.	0230-0300	Stockholm, Sweden	F	9.695, 11.705
8:00-8:15 p.m.	0300-0315	Tokyo, Japan	G	9.635, 9.78, 11.86, 15.14
8:00-8:30 p.m.	0300-0330	Kiev, U.S.S.R.	G	15.105
8:00-8:55 p.m.	0300-0355	Seoul, Rep. Korea	G	9.58, 9.635, 9.78, 11.86
8:00-9:20 p.m.	0300-0420	Moscow, U.S.S.R.	F	11.86
8:00-10:00 p.m.	0300-0500	**Johannesburg, S. Africa	F	9.655, 12.05
8:10-8:30 p.m.	0310-0330	HCJB, Quito, Ecuador	G	7.12, 9.78 (via Tirana), 11.445, 12.055, 15.06, 15.385, 17.735, 17.855
8:20-9:25 p.m.	0320-0425	**Santiago, Chile	F	5.98, 7.27
8:22-8:28 p.m.	0322-0328	**TIFC, San Jose, Costa Rica	G	6.095, 9.56, 11.915
8:30-9:00 p.m.	0330-0400	Erevan, U.S.S.R.	F	6.195, 9.56, 11.81, 15.15
8:30-9:15 p.m.	0330-0415	Moscow, U.S.S.R.	F	6.035, 9.645, (opens 0300 Sat., Sun.)
8:30-9:30 p.m.	0330-0430	Berlin, Ger. Dem. Rep.	G	9.54, 9.735, 11.69, 15.14 (Sat./Tue./Wed./Fri.)
9:00-9:15 p.m.	0400-0415	Tokyo, Japan	G	9.54, 9.58, 9.635, 9.735, 9.78, 11.69, 15.14, 11.87, 12.00, 12.05, 15.10, 15.21
9:00-9:30 p.m.	0400-0430	Oslo, Norway	F	11.89, 12.00
9:00 p.m.-12:30 a.m.	0400-0730	Budapest, Hungary	G	6.12 (via Antigua tent. midsummer) 6.175 (via Sackville)
9:30-10:00 p.m.	0430-0500	Montreal, Canada	G	15.105
9:30-12:30 a.m.	0430-0730	Moscow, U.S.S.R.	F	6.18, 9.55, 9.645
10:00-10:15 p.m.	0500-0515	Berne, Switzerland	F	6.00, 7.215, 9.585, 9.833, 11.91 (Tue., Fri.)
10:00-10:30 p.m.	0500-0530	Sofia, Bulgaria	G	9.655, 11.765
10:00-11:20 p.m.	0500-0620	London, England	G	9.54, 9.58, 9.635, 9.71, 9.78, 11.69, 11.87, 12.00, 12.05, 15.10, 15.21
10:00-12 mdt.	0500-0700	Jerusalem, Israel	G	9.725, 11.715
10:00 p.m.-12:30 a.m.	0500-0730	Tokyo, Japan	F	9.70 (alternate 9.705)
10:30-10:50 p.m.	0530-0550	Lisbon, Portugal	G	6.175 (via Antiqua)
11:00-11:15 p.m.	0600-0615	Hilversum, Holland	F	7.412, 9.815, 11.655
11:00-11:30 p.m.	0600-0630	HCJB, Quito, Ecuador	G	15.105
11:00 p.m.-12 mdt.	0600-0700	London, England	F	6.025, 11.935 (varies)
11:25 p.m.-1:25 a.m.	0625-0825	Cologne, Ger. Fed. Rep.	G	6.165, 9.715, (via Bonaire)
11:30 p.m.-12:50 a.m.	0630-0750	Tokyo, Japan	G	6.095, 9.56
12:00-12:15 a.m.	0700-0715	Oslo, Norway	G	6.175 (via Antiqua)
1:00-1:15 a.m.	0800-0815	Seoul, Korea	G	9.51 (via Antiqua tent. by midsummer)
1:00-2:20 a.m.	0800-0920	Buenos Aires, Argentina	G	5.96 (via Antiqua)
1:00-3:00 a.m.	0800-1000	**Kuala Lumpur, Malaysia	G	6.10 (via Malta), 6.185, 9.545
1:00-7:00 a.m.	0800-1400	**Hilversum, Holland	G	9.505
2:00-2:15 a.m.	0900-0915	Tokyo, Japan	F	6.18, 9.645 (Sun.)
2:30-2:50 a.m.	0930-0950	Manila, Philippines (FEBC)	P	9.73
3:00-3:30 a.m.	1000-1030	**Port Moresby, Papua-New Guinea	G	9.69 (Mon.-Fri.)
3:50-4:10 a.m.	1050-1110	Tokyo, Japan	G	15.275
		**Santiago, Chile	G	9.63 (via Bonaire)
		Tokyo, Japan	G	9.505
		**Santiago, Chile	G	9.505
		Tokyo, Japan	G	9.715 (via Bonaire)
		**Santiago, Chile	G	11.92
		Tokyo, Japan	G	4.89
		**Santiago, Chile	G	9.505
		Tokyo, Japan	G	6.195, 9.566, 11.81, 15.15
		**Santiago, Chile	G	5.99
		Tokyo, Japan	G	6.195, 9.566, 11.81, 15.15

\*Reception quality, East Coast (West Coast) location: G good, F fair, P-poor

\*\*Not intended for North America, but receivable satisfactorily  
Days refer to local date in target area.

# ELECTRONICS MARKET PLACE

**REGULAR CLASSIFIED: COMMERCIAL RATE:** For firms or individuals offering commercial products or services, \$2.25 per word. Minimum order \$33.75. **EXPAND-AD CLASSIFIED RATE:** \$3.35 per word. Minimum order \$50.25. Frequency discount: 5% for 6 months; 10% for 12 months paid in advance. **READER RATE:** For individuals with a personal item to buy or sell, \$1.35 per word. No minimum! **DISPLAY CLASSIFIED:** 1" by 1 column (2-1/4" wide), \$260.00. 2" by 1 column, \$520.00. 3" by 1 column, \$780.00. Advertiser to supply film positives. For frequency rates, please inquire. **GENERAL INFORMATION:** Payment must accompany copy except when ads are placed by accredited advertising agencies. First word in all ads set in caps. All copy subject to publisher's approval. All advertisers using Post Office Boxes in their addresses **MUST** supply publisher with permanent address and telephone number before ad can be run. Advertisements will not be published which advertise or promote the use of devices for the surreptitious interception of communications. Ads are not acknowledged. They will appear in first issue to go to press after closing date. Closing Date: 1st of the 2nd month preceding cover date (for example, March issue closes January 1st. Send order and remittance to **POPULAR ELECTRONICS**, One Park Avenue, New York, New York 10016. Attention: Hal Cymes

## FOR SALE

**FREE!** Bargain Catalog—I.C.'s, LED's, readouts, fiber optics, calculators parts & kits, semiconductors, parts, Poly Paks, Box 942PE, Lynnfield, Mass. 01940.

**GOVERNMENT** and industrial surplus receivers, transmitters, snooper scopes, electronic parts, Picture Catalog 25 cents, Meshna, Nahant, Mass. 01908.

**LOWEST Prices** Electronic Parts, Confidential Catalog Free, KNAPP, 3174 8th Ave. S.W., Largo, Fla. 33540.

**ELECTRONIC PARTS**, semiconductors, kits, **FREE FLYER**, Large catalog \$1.00 deposit, **BIGELOW ELECTRONICS**, Bluffton, Ohio 45817.

**RADIO—T.V. Tubes**—36 cents each. Send for free catalog, Cornell, 4213 University, San Diego, Calif. 92105.

**AMATEUR SCIENTISTS**, Electronics Experimenters, Science Fair Students... Construction plans—Complete, including drawings, schematics, parts list with prices and sources... Robot Man — Psychedelic shows — Lasers — Emotion/Lie Detector — Touch Tone Dial — Quadraphonic Adapter — Transistorized Ignition — Burglar Alarm — Sound Meter... over 60 items. Send 50 cents coin (no stamps) for complete catalog, Technical Writers Group, Box 5994, University Station, Raleigh, N.C. 27607.

**METERS**—Surplus, new, used, panel or portable. Send for list, Hanchett, Box 5577, Riverside, CA 92507.

**MECHANICAL, ELECTRONIC** devices catalog 10 cents. Greatest Values — Lowest Prices, Fertik's, 5249 "D", Philadelphia, Pa. 19120.

**SOUND SYNTHESIZER KITS**—Surt \$12.95, Wind \$12.95, Wind Chimes \$17.95, Electronic Songbird \$6.95, Musical Accessories, many more. Catalog free, PAIA Electronics, Box J14359, Oklahoma City, OK 73114.

**BUGGED???** New locator finds them fast. Write, Clifton, 11500-L N.W., 7th Avenue, Miami, Florida 33168.

**YOU WILL SAVE BIG MONEY!** Surplus, Clearouts, Bankruptcy, Inventory, Deals. Catalog \$1 (redeemable), ETCOA Electronics, Box 741, Montreal, H3C 2V2, U.S. Inquiries.

**HEAR POLICE/FIRE Dispatchers!** Catalog shows exclusive directories of "confidential" channels, scanners. Send postage stamp, Communications, Box 56-PE, Commack, N.Y. 11725.

**UNSCRAMBLERS:** Fits any scanner or monitor, easily adjusts to all scrambled frequencies. Only 4" square \$29.95, fully guaranteed. Dealer inquiries welcomed, PQO Electronics, Box 841, North Little Rock, Arkansas 72115.

**RECONDITIONED** Test Equipment, \$0.50 for catalog, Waller's Test Equipment, 2697 Nickel, San Pablo, CA 94806.

**POLICE, Fire** monitors, scanners, crystals, CB Transceivers, New Crystal-less scanners. Discount priced, Box 19224, Denver, CO 80219.

**TELETYPE EQUIPMENT** for sale for beginners and experienced computer enthusiast. Teletype machines, parts, supplies. Catalogue \$1.00 to: ATLANTIC SALES, 3730 Nautilus Ave., Brooklyn, NY 11224, Tel: (212) 372-0349.

**JAPANESE TRANSISTORS**, all transistors original factory made. Free catalog, West Pacific Electronics, P.O. Box 3879, Torrance, CA 90510.

**ELECTRONIC ignition:** Capacitor-Discharge, pointless, Auburn Sparkplugs, Wheel Stabilizers, Information 20 cents, Anderson Engineering, Epsom, N.H. 03234.

**WHOLESALE C.B.**, Scanners, Antennas, Catalog 25 cents. Crystals: Special cut, \$4.95, Monitor \$3.95. Send make, model, frequency. G. Enterprises, Box 461P, Clearfield, UT 84015.

**COMPUTER HOBBYISTS**—classified advertising newsletter, \$3.75/year. Free Sample, ON\_LINE, 24695 Santa Cruz Hwy., Los Gatos, CA 95030.

**SURPLUS COMPONENTS**, Communication and test equipment. Illustrated catalog 25 cents, E. French, P.O. Box 249, Aurora, Illinois 60505.



## ORGAN KITS KEYBOARDS

THE ULTIMATE IN DESIGN AND SOUND

Demo Record & Brochure \$1.00

Wurlitzer reproductions

**DEVTRONIX ORGAN PRODUCTS**, Dept. C  
5872 Amapola Dr. • San Jose, CA 95129

**SURPLUS 'SMART' TERMINALS**, components, serious music synthesizer kits, plans, parts, and more. Send SASE for **FREE INFO** Package. CFR Associates, POBF, Newton, N.H. 03858.

**CB RADIOS**, monitors, crystals, CD ignitions, Southland, Box 3591-B, Baytown, Texas 77520.


**CB CRYSTALS** over 20,000 standard and specials in stock from 6.0 MHz to 45.0 MHz. Call or write for information package. Dealer inquiries invited. Roberts Electronics Sales, 73563 29 Palms Highway, 29 Palms, California 92277. (714) 367-6235.

**SURPRISES GALORE!** Projects, ham radio, music synthesizers, etc. IC's pots, hardware, crystals, keyboards, resistors, etc. Send 13 cents stamp for catalogue. UTEP, Box 26231B, Salt Lake City, Utah 84125.
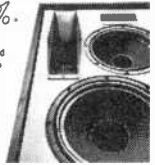
## BUILD YOUR OWN SPEAKERS AND SAVE UP TO 50%.

Send for our free fact packed 40 page catalog manual and learn how to assemble your own multi element stereo speakers from scratch or from kits. Our catalog includes chapters on design construction, a gloss enclosure midrange, woofers, tweeters and horns. Write us today.

**SPEAKERLAB**  
Dept. PE A 5500 35th St E  
Seattle, Washington 98105



**BUILD AND SAVE. TELEPHONES, TELEVISION, DETECTIVE, BROADCAST** Electronics. We sell construction plans with an Engineering Service. Speakerphones, Answering Machines, Carphones, Phonevision, Dialers, Color TV Converters, VTR, Games, \$25 TV Camera, Electron Microscope, Special Effects Generator, Time Base Corrector, Chroma Key, Engineering Courses in Telephone, Integrated Circuits, Detective Electronics. **PLUS MUCH MORE.** NEW Super Hobby Catalog PLUS year's subscription to Electronic News Letter, \$1.00. Don Britton Enterprises, 6200 Wilshire Blvd., Los Angeles, Calif. 90048.

**NAME BRAND** Digital/Analog Test Equipment. Discount prices. Free catalog, Salen Electronics, Box 82, Skokie, Illinois 60076.

**TELEPHONES UNLIMITED**, Equipment, Supplies, All types, Regular, Keyed, Modular. Catalog 50 cents. Box 1147E, San Diego, California 92112.

**CB RADIOS**—Police Scanners. Wholesale only!! Send letterhead for lowest prices anywhere. Four Wheeler, 10PE New Scotland, Albany, N.Y. 12208.



## THERE IS NO OTHER TELESCOPE LIKE IT! THE NEW EDMUND 4 1/4", f/4 NEWTONIAN WIDE FIELD REFLECTOR TELESCOPE

Clear, bright, spectacular wide angle views of stars, moon, comets... easy to use... portable!

**IN SECONDS YOU'RE SCANNING THE ASTOUNDING UNIVERSE**, able to see and study the breath-taking cosmos as perhaps you never have before... awesome vastness, unbelievable orderliness, stark silent beauty. All the fascinating heavenly mysteries are yours to enter and explore. This new reflector telescope makes it easy for everyone to span a thousand light-years to space-age enjoyment of the heavens and outdoors. No complicated set up! Just insert the eyepiece, focus, and its big 3 1/2" field of view gives you more stars in a single view than any other type of telescope. Bright, crisp, finely resolved images to capture your interest and imagination. It's probably the easiest to use telescope ever... over your shoulder, in your lap, on a tripod. Or just rotate the spherical base on its own mount for use on a table, car hood. Take it anywhere (only 17", 10 lb.). Top quality optical system 4 1/4", f/4 parabolic primary mirror (1/4 wave, 17" F.L.); prealigned 1/4 wave diagonal on a coated optical window seals optics from moisture and dust. 28mm Kellner eyepiece (gives 15X, higher without other eyepiece or Barlow). Fast focusing (25" to infinity). Bright Scharfian red (doesn't impair night vision); adj. carrying strap. A "first" scope "must" an ideal second scope!

There is no other telescope like it.

NO. 2001AV

**\$149<sup>95</sup>**  
Ppd.

### COMPLETE AND MAIL COUPON NOW

**EDMUND SCIENTIFIC CO.** 300 Edscorp Bldg., Barrington, N. J. 08007

SEND FREE 164 PG CATALOG  AV  unique Edmund Telescope(s)

#2001AV @ \$149.95 ea \$ \_\_\_\_\_

Service & Handling Charge \$ 1.00

Enclosed is  Check  M O For TOTAL of \$ \_\_\_\_\_

Interbank No. \_\_\_\_\_ Signature \_\_\_\_\_

Card No \_\_\_\_\_ Name \_\_\_\_\_ (Please Print)

Expiration Date \_\_\_\_\_ Address \_\_\_\_\_

City \_\_\_\_\_

State \_\_\_\_\_ Zip \_\_\_\_\_

**30-DAY MONEY-BACK GUARANTEE.** You must be satisfied or return any purchase in 30 days for full refund.

HELPING TO DEVELOP AMERICA'S TECHNOLOGY FOR OVER 30 YEARS.

**GIANT FREE 164 PG. CATALOG**



**4500 UNUSUAL BARGAINS FOR HOBBYISTS, SCHOOLS, INDUSTRY**

**EDMUND SCIENTIFIC CO.**  
300 Edscorp Bldg.  
Barrington N.J. 08007

America's Greatest  
Science • Optics • Hobby Center  
(609) 547-3488













# S.D. SALES CO.

P. O. BOX 28810 - D  
DALLAS, TEXAS 75228

## JUMBO LED CAR CLOCK

**\$16.95**

KIT



Alarm Option - \$1.50  
AC XFMR - \$1.50

**THE HOTTEST SELLING KIT WE EVER PRODUCED!**  
You requested it! Our first D.C. operated clock kit. Professionally engineered from scratch. Not a makeshift kluge as sold by others. Features:

- A. Bowmar Jumbo -.5 inch LED array.
- B. MOSTEK - 50250 - Super Clock Chip.
- C. On board precision crystal time base.
- D. 12 or 24 Hr. Real Time Format.
- E. Perfect for cars, boats, vans, etc.
- F. P.C. Board and all parts (less case) included.

**50,000 SATISFIED CLOCK  
KIT CUSTOMERS CANNOT  
BE WRONG!**

**THIS MONTH'S SPECIALS**  
AMD - 8080A \$14.95  
Z-80 CPU 49.95  
82S129 1K PROM 2.50

**1702A 2K EPROM**  
We tell it like it is. We could have said these were factory new, but here is the straight scoop. We bought a load of new computer gear that contained a quantity of 1702 A's in sockets. We carefully removed the parts, verified their quality, and are offering them on one heck of a deal. First come, first served. Satisfaction guaranteed! U.V. Eraseable. \$6.95 ea. 4/\$25

**UP YOUR COMPUTER!**  
**21L02-1 1K LOW POWER 500 NS  
STATIC RAM** Time is of the essence!  
And so is power. Not only are our RAM's faster than a speeding bullet but they are now very low power. We are pleased to offer prime new 21L02 1 low power and super fast RAM's. Allows you to STRETCH your power supply farther and at the same time keep the wait light off. 8 for \$12.95

## 60 HZ CRYSTAL TIME BASE S.D. SALES EXCLUSIVE!

KIT FEATURES:

- A. 60HZ output with accuracy comparable to a digital watch.
- B. Directly interfaces with all MOS Clock Chips.
- C. Super low power consumption (1.5 ma typ.)
- D. Uses latest MOS 17 stage divider IC.
- E. Eliminates forever the problem of AC line glitches.
- F. Perfect for cars, boats, campers, or even for portable clocks at ham filed days. **2/\$10.00**
- G. Small size; can be used in existing enclosures. Kit includes Crystal, Divider IC, PC Board, Plus all necessary parts and specs. At last count - over 20,000 sold!

**\$5.95**

**S.D. SALES EXCLUSIVE**  
**\$12.95 MOS 6 DIGIT UP-DOWN COUNTER \$12.95**  
40 PIN DIP. Everything you ever wanted in a counter chip. Features: Direct LED segment drive, single power supply (12 VDC TYP.), six decades up/down, pre-loadable counter, separate pre-loadable compare register with compare output, BCD and seven segment outputs, internal scan oscillator, CMOS compatible, leading zero blanking, 1MHZ. count input frequency. Very limited quantity! WITH DATA SHEET

7400-19c	7411-29c	7451-19c	7490-65c	74153-75c
741500-49c	7413-50c	7453-19c	74LS90-95c	74154-1.00
7402-19c	7416-69c	7473-39c	7492-75c	74157-75c
74LS02-49c	7420-19c	7474-35c	7493-69c	74161-95c
7404-19c	7430-19c	74LS74-59c	7495-75c	74164-1.10
74L04-29c	7432-34c	7475-69c	7496-89c	74165-1.10
74S04-44c	7437-39c	7476-35c	74121-38c	74174-95c
74LS04-49c	7438-39c	7480-49c	74123-65c	74181-2.50
7406-29c	7440-19c	7483-95c	74132-1.70	74191-1.25
7408-19c	7447-85c	7485-95c	74S138-1.95	74192-1.25
7410-19c	7448-85c	7486-45c	74141-75c	74193-1.00

TTL INTEGRATED CIRCUITS 74195-69c

**1000 MFD  
Filter Caps**  
Rated 35 WVDC Upright style with PC leads. Most popular value for hobbyists. Compare at up to \$1.19 ea. from franchise type electronic parts stores. S.D. Special 4/\$1.

**Slide Switch Assortment**  
Our best seller. Includes miniature and standard sizes; single and multi-position units. All new, first name brand. Try one package and you'll reorder more! Special 12/\$1.00

**RESISTOR ASSORTMENT**  
1/4W 5% & 10% PC leads. A good mix of values. 200/\$2.

**P.C. LEAD DIODES**  
1N4148/1N914 100/\$2.00  
1N4002-1A, 100 PIV 40/\$1.

**HEAVY DUTY Full Wave Bridge**  
25 AMP 50 PIV \$1.25

**DISC CAP ASSORTMENT**  
PC leads. At least 10 different values. Includes .001, .01, .05, plus other standard value. 60/\$1.00

**TRANSISTOR SPECIALS**  
EN2222 NPN 8 for \$1.00  
EN2907 PNP 8 for \$1.00  
2N3904 NPN 8 for \$1.00  
2N4400 NPN 10 for \$1.00  
2N4402 PNP 8 for \$1.00

**LED's WITH CLIPS**  
Jumbo Red. RL-2 by Litronix. With plastic mtg. clips which are very scarce. 4 for \$1.00

**C&K MINI TOGGLE SWITCH**  
No. 7101. S.P.D.T. Panel mount or P.C. mount. 79c 3 for \$2.

**SIX DIGIT LED ALARM CLOCK KIT**  
We made a fantastic kit even better. Redesigned to take advantage of the latest advances in I.C. Clock technology. Features: Litronix Dual 1/2 inch displays, Mostek 50250 super clock chip, Single I.C. segment driver, SCR digit drivers. Greatly simplified construction. More reliable and easier to build. Kit includes all necessary parts (except case). P.C.B. or XFMR optional. ALL NEW DESIGN! P.C. Board - \$3.00 AC XFMR - \$1.50 KIT - \$9.95

**Motorola SCR**  
2N4443. 8 AMP 400 PIV. P.C. Leads 3/\$1.

**FAIRCHILD - TBA 641**  
4W. Audio power Amp. Just out! In special heat sink DIP. One super audio IC. \$1.50 with data

**FND-359 - Led Readout**  
.4 IN. Common Cathode. High efficiency. Has FND-70 PIN OUT. 59c

**OUR CATALOG**  
is chocked full of rare parts bargains, deals, RAM or CPU kits, plus much more. Yours FREE!

**PRICES SHOWN SUBJECT TO CHANGE WITHOUT NOTICE.**

**\$15.95**



**COMPUTER POWER SUPPLY**  
A very fortunate purchase. One of the best industrial quality REGULATED supplies we have seen. High performance, small size. Input is 120 VAC 60 HZ. Has the following regulated outputs: -5VDC@800MA; -15VDC @ 1.25 AMP; -25VDC @ 180 MA. Sold at a fraction of original cost. Do yourself a favor and order NOW. We expect a quick sellout.

**NEXT MONTH:**  
S.D. will have music for your ears. Watch our ads.  
For your Imsai or Altair 8080 Computer:  
Z-80 CPU Kit - \$149. 4K Low Power Ram Kit - \$89.95

Terms: Money back guarantee. No COD. Texas residents add 5% sales tax. Add 5% of order for postage & handling. Orders under \$10. add 75c. Foreign orders: US funds only!

Call your Bankamericard or Master Charge order in on our continental United States toll free Watts:  
**1-800-527-3460**  
Texas Residents Call Collect:  
**214/271-0022**

Special Thanks to: Dennis, Fred, Abe, Bill, Sam, Hal, Tom, Alex, John, Ely, and Larry

**S.D. SALES CO.**  
P. O. BOX 28810  
Dallas, Texas 75228

ORDERS OVER \$15.00 - CHOOSE \$1.00 FREE MERCHANDISE

**INSTRUCTION**

LEARN ELECTRONIC ORGAN SERVICING at home all makes including transistor. Experimental kit—trouble-shooting. Accredited NHSC. Free Booklet. NILES BRYANT SCHOOL, 3631 Stockton, Dept. A. Sacramento, Calif. 95820.

SELF-STUDY CB RADIO REPAIR COURSE. THERE'S MONEY TO BE MADE REPAIRING CB RADIOS. This easy-to-learn course can prepare you for a career in electronics enabling you to earn as much as \$16.00 an hour in your spare time. For more information write. CB RADIO REPAIR COURSE, Dept. PE057, 531 N. Ann Arbor, Oklahoma City, Okla. 73127.

LEARN WHILE ASLEEP! HYPNOTIZE! Astonishing details, strange catalog free! Autosuggestion, Box 24-ZD, Olympia, Washington 98507.

UNIVERSITY DEGREES BY MAIL, Bachelors, Masters, Ph.D.'s ... Free revealing details. Counseling, Box 317-PE5, Tustin, California 92680.

INTENSIVE 5 week course for Broadcast Engineers. FCC First Class license. Student rooms at the school, Radio Engineering Inc., 61 N. Pineapple Ave., Sarasota, FL 33577 and 2402 Tidewater Trail, Fredericksburg, VA 22401.

PRACTICAL Electronic Training. FCC license. Free home study catalog. Genn Tech., 5540 Hollywood Blvd., Los Angeles, CA 90028. Or, Ra-Tel Electronics, P.O. Box 167, "P" Toronto, Ont., Canada. U.S. Inquiries.

LEARN BASIC Digital Troubleshooting by correspondence. Course includes text and demonstration modules. Educational Technologies, Box 224, Reynoldsburg, Ohio 43068.

CB'ERS—Be a "Ham"—We'll teach you! Life Membership: \$400. American Radio Council, Box 1171-K, Garland, Texas 75040.

HIGHLY EFFECTIVE Degree Program in Electronics Engineering. Advance rapidly! Our 31st Year. Free literature. Cook's Institute, Box 20345, Jackson, Miss. 39209.

BURGLAR/FIRE EXPERTS NEEDED for cars, homes, industry. Learn high profit systems installation at home spare time. Simple, quick complete. Free information by mail. No salesmen. Security Systems Management School (home-study), Dept. 7373-057, Little Falls, N.J. 07424.

GET YOUR COMMERCIAL FCC License. New exams by author of successful published workbooks of FCC Practice Tests. 500 Questions Second Class, \$11.95; 200 First Class, \$7.95; 100 Radar, \$4.95, postpaid. Save all three \$19.95. Complete mathematical solutions. Free counselling service. Victor Veley, P.O. Box 14, La Verne, Calif. 91750.

GRANTHAM'S FCC LICENSE STUDY GUIDE — 377 pages. 1465 questions with answers/discussions — covering 1st, 2nd, first radiotelephone examinations. \$13.45 postpaid. GSE, P.O. Box 25992, Los Angeles, California 90025.

**F.C.C. EXAM MANUAL**

PASS FCC EXAMS! Memorize, study — Test Answers! for FCC 1st and 2nd class Radio telephone licenses. Newly revised multiple-choice questions and diagrams cover all areas tested in FCC exams plus "Self-Study Ability Test." \$9.95 postpaid. Moneyback Guarantee.

COMMAND PRODUCTIONS P.O. BOX 26348-P  
RADIO ENGINEERING DIVISION SAN FRANCISCO, CALIF. 94126

BROADCAST STATION? Operate your own FM, Cable, Carrier-Current from home, school, church or as money making business. Free details. "Broadcasting", Box 5516-AE, Walnut Creek, CA 94596.

GO FIRST CLASS! Complete FCC examination questions — diagrams — answers, plus "topical study" guide. \$8.95. EGW Publications, Box 5516-AE, Walnut Creek, CA 94596.

SCORE high on F.C.C. Exams... Over 300 questions and answers. Covers 3rd, 2nd, 1st and even Radar. Third and Second Test, \$14.50; First Class Test, \$15.00. All tests, \$26.50. R.E.I., Inc., Box 806, Sarasota, Fla. 33577.

**PERSONALS**

MAKE FRIENDS WORLDWIDE through international correspondence. Illustrated brochure free. Hermes-Verlag, Box 110660/Z, D-1000 Berlin 11, Germany.

WARTS, Vergo® Cream is painless, safe, easy to mix. Buy Vergo® at better pharmacies.

**INVENTIONS WANTED**

INVENTORS: Manufacturers Need New Products. Free "Recommended Procedure," by a creative fee-based invention service company. Washington Inventors Service, 422-T Washington Building, Washington, D. C. 20005.

**INVENTORS**

**RECOGNITION...FINANCIAL REWARD...OR CREDIT FOR "INVENTING IT FIRST" MAY BE YOURS!**

If you have an idea for a new product, or a way to make an old product better, contact us. "The idea people" We'll develop your idea, introduce it to industry, negotiate for cash sale or royalty licensing. Write now without cost or obligation for free information. Fees are charged only for contracted services. So send for your FREE "Inventor's Kit." It has important Marketing Information, a special "Invention Record Form" and a Directory of 1001 Corporations Seeking New Products.

**RAYMOND LEE ORGANIZATION**  
230 Park Avenue North, New York, NY 10017

At no cost or obligation, please rush my FREE "Inventor's Kit No. A-112"

Name \_\_\_\_\_  
Address \_\_\_\_\_  
City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_  
Phone No. \_\_\_\_\_ Area Code \_\_\_\_\_

**AUTO BURGLAR ALARM KIT**

KIT #ALR-1 \$9.95

#ALR-1WT WIRED & TESTED \$19.95

AN EASY TO ASSEMBLE AND EASY TO INSTALL ALARM PROVIDING MANY FEATURES NOT NORMALLY FOUND. KEYLESS ALARM HAS PROVISION FOR POS. & GROUNDING SWITCHES OR SENSORS. WILL PULSE HORN RELAY AT 1/2 Hz RATE OR DRIVE SIREN. KIT PROVIDES PROGRAMMABLE TIME DELAYS FOR EXIT, ENTRY & ALARM PERIOD. UNIT MOUNTS UNDER DASH. REMOTE SWITCH CAN BE MOUNTED WHERE DESIRED. CMOS RELIABILITY RESISTS FALSE ALARMS & PROVIDES FOR ULTRA DEPENDABLE ALARM. DO NOT BE FOOLED BY LOW PRICES! THIS IS A TOP QUALITY COMPLETE KIT WITH ALL PARTS INCLUDING DETAILED DRAWINGS AND INSTRUCTIONS OR AVAILABLE WIRED AND TESTED.

**JUMBO DIGIT CLOCK KIT**  
A complete Kit (less Cabinet) featuring: six .5" digits, MM5314 IC, 12/24 Hr. time, 50/60 HZ., Plug-Transformer, Line Cord, Switches, and all Parts. (Ideal Fit in Cabinet II) Kit # 5314-5 \$19.95 ea. WITH PC Boards \$27.98.

**JUMBO DIGIT CONVERSION KIT**  
Convert small digit LED clock to large .5" displays. Kit includes 5 .5" LEDs, Multiplex PC Board & easy hook up info. Kit # JD-1CC for common Cathode Kit # JD-1CA for common Anode \$9.95 ea.

**DISCRETE LED'S**  
JUMBO RED  
10 FOR \$1.00  
100 FOR \$9.95

**DIGITAL CLOCK IC'S**  
MM5312 \$ 4.95  
MM5314 3.95  
MM5375 AB 3.95  
CT-7001 7.95  
CT-7002 13.95  
MM5369 2.95

**PC TRIM POTS**  
25K 6 \$1.00  
47K 6 \$1.00  
SPECTROL 10K 10 TURN 95c  
4752 2.00

**MOBILE LED CLOCK**  
12 OR 24-HOUR OPERATION MODEL #2001  
12 VOLT AC or DC POWERED  
SIX LARGE 4" DIGITS

\* MOUNTING BRACKET INCLUDED  
KIT #2001 COMPLETE KIT (Less 9V Battery) 29.95 ea. 3 OR MORE \$27.95 ea.

ASSEMBLED UNITS WIRED & TESTED  
ORDER #2001 WT (LESS 9V BATTERY) WIRED FOR 12 HR OP. IF NOT SPECIFIED OTHERWISE \$39.95 ea. 3 OR MORE \$37.95 ea.

115 VAC Power Pack #ACT1 \$2.50 ea.

MEMORY	21L02	OR SUBSTITUTED	OP AMPS	DIODES
PRIME .450NS LOW POWER	1-24 \$1.95	25-99 1.75	301 TO-5	IN 4002 1A, 100 PIV 12/\$1.00
	100-199 1.60	709 DIP	IN 4005 1A, 600 PIV 11/\$1.00	IN 4007 1A, 1000 PIV 10/\$1.00
	200-499 1.45	741 DIP	RECTIFIER 2.5A, 1000 PIV 4/\$1.00	IN 914 SIL SIGNAL 20/\$1.00
	Over 500 1.40	741 M-DIP	IN 4148 SIL SIGNAL 20/\$1.00	DIAC 28V 4/\$1.00
		741 TO-5		
		747 TO 5		

**PROM**  
1702 E Prom \$8.95  
5203 E Prom \$8.95

**60 HZ. XTAL TIME BASE**  
Will enable Digital Clock Kits or Clock-Calendar Kits to operate from 12V DC. 1"x2" PC Board. Power Req. 5-15V (2.5 MA. TYP.) Easy 3 wire hookup Accuracy: ± 2PPM #TB-1 (Adjustable) Complete Kit \$4.95 ea. Wir & Cal \$9.95

**VARIABLE REGULATED 1 AMP POWER SUPPLY KIT**  
• VARIABLE FROM 4 to 14V  
• SHORT CIRCUIT PROOF  
• 723 IC REGULATOR  
• 2N3055 PASS TRANSISTOR  
• CURRENT LIMITING AT 1 AMP  
KIT IS COMPLETE INCLUDING DRILLED & SOLDER PLATED FIBERGLASS PC BOARD AND ALL PARTS (LESS TRANSFORMER) KIT #PS-01 \$8.95  
TRANSFORMER 24V CT will provide 300MA at 12V and 1 Amp at 5V with #PS-01. \$3.50

**RED OR GREY PLEXIGLAS**  
3"x6"x1/8"  
FOR DIGITAL BEZELS  
95¢ ea. 4/\$3

**25 AMP BRIDGE**  
\$1.95 ea.  
3/\$5.00  
100 PIV

**NYLON WIRE TIES**  
8" TIE-WRAP 100/\$1.95  
4" TIE-WRAP 100/\$1.75

**IC SOCKETS**  
PINS 1-24 25 100  
8 5 25 22 20  
14 25 22 20  
16 28 25 23  
18 31 28 26  
24 50 45 40  
28 60 55 50  
40 75 70 65

**MOLEX PINS**  
Form inexpensive Sockets  
100 for \$1.25  
Reel of 1000 - \$8.50

**NEW LSI TECHNOLOGY FREQUENCY COUNTER KIT**  
8 LARGE .4" RED LED DIGITS

• ONLY 8 IC'S! • XTAL TIME BASE  
A truly "State of the Art" counter using quality components throughout.  
KIT INCLUDES: DETAILED INSTRUCTIONS, XTAL, TOP QUALITY FIBERGLASS DOUBLE SIDED PC BOARD, IC'S WITH SOCKETS AND ALL PARTS LESS POWER SUPPLY AND CABINET.

50 MHZ COUNTER KIT #FC-50 \$69.95  
5 VOLT REGULATED 1 AMP POWER SUPPLY KIT #PS-02 \$9.95  
350 MHZ PRESCALER KIT #PSL-350 23.95  
650 MHZ PRESCALER KIT #PSL-650 \$29.95  
CABINET (& MTG HARDWARE) #CAB III \$19.95  
[CABINET WILL HOUSE #FC-50, #PS-02, AND A PRESCALER]

DELIVERIES TO START IN MAY, 1977

ORDER BY PHONE OR MAIL Orders Under \$15 Add \$1.00 Handling  
COD ORDERS WELCOME Fla. Res. Please Add 4% Sales Tax.

**OPTOELECTRONICS, INC.**  
BOX 219 • HOLLYWOOD, FLA. 33022 • (305) 921-2056

master charge BANKAMERICARD

**MAGNETS**

MAGNETS. All types. Specials-20 disc. or 10 bar, or 2 stick or 8 assorted magnets. \$1.00. Magnets, Box 192-H Randallstown, Maryland 21133.

**WANTED**

GOLD, Silver, Platinum, Mercury wanted. Highest prices paid by refinery. Ores assayed. Free circular. Mercury Terminal, Norwood, MA 02062.







**NEW!** SPDT SWITCH

500 KHz, 2 lead crystal.....\$4.95  
 8PST DIPSWITCH.....\$1.95  
 S100 bus edge connector (specify solder tail or wirewrap)...\$5.00  
 Lopropile solder tail sockets:  
 8 pin.....10/\$1.85  
 14 pin.....10/\$3.70  
 16 pin.....10/\$3.85

**WE DON'T CHARGE EXTRA FOR THE TRANSFORMER OR BOARD, LIKE OTHERS: YOU GET EVERYTHING EXCEPT CASE, AND THAT INCLUDES .3" DIGITS, SOCKETS FOR ICs and READOUTS, MUCH MORE. +1 LB POST.**

**GODBOUF** READOUT SPECIAL!  
 BRIGHT .5" DIGIT  
 FND503 COM CATHODE  
 FND510 COM ANODE  
 → 10/\$8.50 or 95¢ each

**12 Volts, 8 Amps**  
**POWER! CB, HAM, BENCH--\$39.95**

Now you can connect CB and ham transceivers...auto tape players...portable TVs...anything requiring a solid, stable DC voltage...to your AC house current: also makes a superb lab or bench supply. Crowbar overvoltage protection, short protection, .05V regulation, current limiting, adjustable output 11-14V, RF bypassing, and EASY ASSEMBLY---heat sinks, power transistors, etc. mount on board. PLEASE INCLUDE POSTAGE.

NEW, PC MOUNT TYPE (BUSHING NOT THREADED). INCLUDES MOUNTING FRAME FOR EXTRA SUPPORT. LTD QTY!

PART #SW3

036 CIRCLE NO. 26 ON FREE INFORMATION CARD

**PLANS AND KITS**

**AMAZING ELECTRONIC PRODUCTS**

LASERS SUPER POWERED, RIFLE, PISTOL, POCKET - SEE IN DARK - PYRO TECHNICAL DE BUGGING - UNCRAMBLERS GIANT TESLA - STUNWAND - TV DISRUPTER - ENERGY PRODUCING - SCIENTIFIC DETECTION, ELECTRIFYING, CHEMICAL, ULTRASONIC, CB AERD, AUTO AND MECH DEVICES, HUNDREDS MORE - ALL NEW PLUS INFO UNLTD PARTS SERVICE

**INFORMATION unlimited**  
 Box 626 Loid Jeffrey P2 • Amherst, N.H. 03031

CATALOG \$1

FREE KIT Catalog contains Test and Experimenters' Equipment. Dage Scientific Instruments, Box 1054P, Livermore, CA 94550.

**TIGER SST SIMPLI-KIT**

**FOR THE DO-IT-YOURSELFER**

**NOW!** a high quality CD Electronic Ignition System in kit form.

Contains all components and solder to build complete Solid-State Electronic CD Ignition System for your car. Assembly requires less than 3 hours.

- Increases MPG 15%
- Increases horsepower 15%
- Plugs and Points last 50,000 miles
- Eliminates 4 of 5 tune-ups
- Instant starting, any weather
- Dual system switch

Fits only 12 volt neg ground Only \$21.95 postpaid

**Tri-Star Corporation**  
 P.O. Box 1727 Grand Junction, Colorado 81501

**For faster service**

**USE ZIP CODE**

**on all mail**

**BULLET ELECTRONICS**  
 (214)823-3240  
 PO BOX 19442 P DALLAS TX 75219

**ULTRASONIC SENDER-RECEIVER KIT**

A special buy on a high quality ultrasonic transducer allows us to offer this kit at a super price - but hurry, quantities are limited! You can build intrusion alarms, motion detectors, remote controls, echo ranging or liquid level measurement equipment. We supply the basic transmitter or receiver electronics including a drilled and plated PC board. The units work at 23KHZ with a range of 20 ft. and can be positioned opposite each other or side-by-side and bounced off a solid surface. The output will sink up to 300ma to drive a relay, alarm circuit, etc.

ORDER US-01 \$19.95

**AUTOMATIC TIME-OUT CIRCUIT** for ultrasonic or mechanical switch alarms. Provides a five second entry delay. Sounds alarm for one minute, then re-arms itself. Requires 6-15VDC. \$3.95

**MK-03 AIRCRAFT CLOCK/TIMER KIT**

24 hour real time and up to 24 hrs. elapsed time are available independently on the same set of 6 .4" LED readouts. Clock has presettable alarm. Timer has reset, hold and count functions. Size 4 1/2" L X 2 1/2" H X 1 3/8" W. Allows mounting in standard instrument case. Because of the many options and mounting variations the kit is sold less case & switches. The unit has noise and over voltage protection. For 9 to 14VDC. \$26.95 QUALITY PC BOARD & COMPONENTS.

**MINI GRANDFATHER CLOCK KIT**

Would you give over one hundred dollars for a completely ELECTRONIC GRANDFATHER CLOCK KIT? Well, what if it had large 1/2" LED readouts... and LED SWINGING PENDULUM A TICK-TOCK SOUND & a super SYNTHESIZED OSCILLATOR with frequency volume and sustain adjust and it CHANGED THE HOURS (like 3 times for 3 o'clock)? What if we gave you all the components, xfmr, spkr, & a set of quality plated boards; and told you it was 6.5" X 4.5" ? Still not good enough??? Then how about for \$39.95? Now that's a DEAL.

**BUILD A COMPLETE CDI IGNITION KIT AT A FRACTION OF THE COST OF OTHER UNITS.** A special buy allows us to sell the complete kit at this low price! Up to 40,000 volts from your present ignition without changing the coil. Simple connections.

INCLUDES: Special toroid transformer  
 Drilled and Plated board  
 Complete instructions  
 All resistors and caps  
 All semiconductors

**\$9.95**

(Does not include heatsink or case.) For 12V negative ground

TERMS: NO COD'S \* Send check or M.O. \* Add 5% postage Tx. res. add 5% tax \* Foreign add 10% (20% airmail) \* Orders under \$10. add 60¢ handling \* Repair service available \* Accepting phone orders on Master Chg & BAC.

CIRCLE NO. 11 ON FREE INFORMATION CARD

**COMMUNICATIONS HANDBOOK 1977**

**CB... and everything else you want to know in the... 1977 COMMUNICATIONS HANDBOOK**

Here's everything you want to know—need to know—about Citizens Band Radio, Amateur Radio, Short-wave Listening, Police-Fire Monitoring, Marine Radio, Features, specifications, latest prices and photos of equipment on the market are at your fingertips in the Handbook's directory buying sections. CITIZENS BAND—The new modified FCC rules, how to get started (no test, no fee), how it's used, buying tips, the 40-channel transceivers... PUBLIC SERVICE BAND—Monitor radios for listening in on police, fire, mobile telephone, airline conversations and weather reports... AMATEUR RADIO—How to get started, license privileges and study tips, slow-scan TV, satellite communications, new Novice rules... MARINE RADIOTELEPHONE—Rules and regulations for pleasurecraft, two-way radio equipment types... SHORT-WAVE 1977—Latest happenings in the SW field, international stations to listen to, SW clubs, utility broadcast listening without knowing Morse Code. IN ALL, A ONE-STOP BUYING GUIDE FOR ALL CONSUMER COMMUNICATION RADIOS AND TRANSCEIVERS! Only \$1.95!

COMMUNICATIONS HANDBOOK, PE-577  
 Consumer Service Division,  
 595 Broadway, New York, N.Y. 10012.

Please send the 1977 Communications Handbook. I'm enclosing \$2.50 (\$1.95 plus 55¢ for postage and handling). Outside U.S.A. \$3.00, postpaid. Residents of CA, CO, FL, IL, MI, MO, NY STATE, DC and TX add applicable sales tax. Postage and handling charges non-taxable.

Print name \_\_\_\_\_  
 Address \_\_\_\_\_  
 City \_\_\_\_\_  
 State \_\_\_\_\_ Zip \_\_\_\_\_

**MORSE-A-LETTER KIT** Decodes/displays Morse code See January Popular Electronics Complete parts kit except chassis/cabine \$109.95 Etched, drilled PC board \$17.95. SELECT CIRCUITS 1411 Lonsdale Road, Columbus, Ohio 43227

**TAPE-SLIDE** synchronizer tap-dissolve, multiprojector programmer plans. \$5.50 Free catalog Millers, 1896 Maywood, S. Euclid OH 44121

**DIGITAL Circuits** Timers. Clocks. combination lock meters. testers New and advanced Stamp for catalog GeeBee, Box 1661, Downey, Calif. 90240.

**WERSI KITS**

Organs, Pianos, Strings Rhythms, PA Systems

**104-page catalog \$2**

WERSI electronics, Inc.  
 Dept. A2, Box 5318, Lancaster, PA 17601

**POCKET COLOR/BAR GENERATOR** kit. 16 patterns. \$49.95. Plans \$4.95 Workshop. Box 393PA, Bethpage, New York 11714

**FIVE OCTAVE Touch Sensitive Electronic PIANO** Kit Components \$245 airmail U.S.A. Canada Cief Products 31 Mountfield Road, Bramhall, Cheshire, England

**THE KING OF KITS** Artisan Organ Kits feature all new modular construction with logic-controlled stops and RAM Preset Memory System. Write for brochure to A O K Manufacturing, Inc. P.O. Box 445 Kenmore WA 98028

**AMPLIFIER KITS** 35 watts output 0.5" THD \$15.00 Benchmark, 2149 Stuart St., Berkeley, CA 94705

**TESLA COIL—40' SPARKS** Plans \$7.50 Information 75 cents Huntington Electronics Box 2009-P, Huntington, Conn 06484.

**250MHZ PRESCALER** for 25 Mhz counters. Protected 50 ohm input \$19.95. Free literature MLG Enterprises, P.O. Box 788, Laconia, N.H. 03246.

**CATALOGS**

FREE! Consumer Service Division Catalog. Includes a wide variety of products associated with the special interests of readers of Ziff-Davis magazines — PSYCHOLOGY TODAY, POPULAR PHOTOGRAPHY, STEREO REVIEW, POPULAR ELECTRONICS, BOATING, FLYING, CAR & DRIVER, CYCLE, SKIING. Send for YOUR free catalog today. Consumer Service Div.: 595 Broadway, Dept. CL, N.Y., NY 10012.



# Radio Hut

Money back guarantee. NO COD'S. Texas residents add 5% sales tax. Add 5% of order for postage and handling. Orders under \$15.00 add 75 cents. Foreign orders add 10% for postage.

For your convenience, call your BankAmericard or Master Charge orders in on our Toll Free Watts Line: 1-800-527-2304. Texas residents call collect: 1-214-271-8423.



P. O. Box 64783P  
Dallas, Texas 75206



Memorex computer boards  
with IC's, diodes, transistor, etc.  
5 Boards containing  
100 - 200 IC's  
**ONLY \$4.25**

## BRIDGE RECTIFIERS

1 Amp	50V	.85
6 Amp	50V	1.10
10 Amp	50V	1.25
25 Amp	50V	1.39

## READOUTS

FND70	.4" C.C.	.59
FND800	.8" C.C.	1.69
TI 6 digit array	C.C.	3/1.00
MAN 8	.3" CA Yellow	.89
LT767	.7" C.C. 4 digit stick	3.25

## POSITIVE VOLTAGE REGULATORS

LM340-5	LM340-15
LM340-6	LM340-18
LM340-8	LM340-24
LM340-12	

To-220 case. Your Choice  
.75 Each

## NEGATIVE REGULATORS

7905	7915
7912	

To-220 case. Your Choice  
.75 Each

## FINNED HEATSINK for above regulators

2-3/4" High 2-1/2" Wide  
1" Depth **ONLY .39 Each**

HEATSINK with pass transistor to increase regulator to 5 amps.  
**ONLY .99 Each**

## BATTERY CLIPS

Standard 9V battery clip with 4 1/2" tinned leads.  
**25/\$1.00**

## LINEARS

LM309 K	.95
LM380 (8 Pin)	.75
LM380 (14 Pin)	1.00
LM3900	.30
LM710	.25
LM711	.25
LM723	.40
LM748	.25
NE555	.35
NE556	.95
NE565	.95
NE566	.95
NE567	1.10
1458	.49
RCA 3043	.75
75491	.25
75492	.25

60Hz Crystal Time Base Kit - Kit enables a MOS clock circuit to operate from a DC power source. Ideal for car, camper, van, boat, etc.

60Hz output with an accuracy of .005% (typ.) Low power consumption 2.5 ma (typ.). Small size will fit most any enclosure. Single MOS IC oscillator/divider chip 5-15 volts DC operation.

**ONLY \$4.95**  
**2 for \$9.00**

## RESISTORS

Over 50,000,000 in stock

330 ohm	1/8W	20K	ohm	1/4W
470 ohm	1/4W	22K	ohm	1/4W
680 ohm	1/2W	27K	ohm	1/4W
1K ohm	1/4W	33K	ohm	1/4W
1.2K ohm	1/4W	39K	ohm	1/4W
2.2K ohm	1/4W	43K	ohm	1/4W
3.3K ohm	1/4W	47K	ohm	1/4W
4.7K ohm	1/4W	82K	ohm	1/4W
6.8K ohm	1/4W	100K	ohm	1/4W
10K ohm	1/4W	150K	ohm	1/4W
		220K	ohm	1/4W

All resistors are PC lead, but are not pull offs. 100 min. order for each value. No Mix. **100/.99 Cents**

## RADIO HUT GUARANTEE

If you are not satisfied with any of our products **NO MATTER WHAT THE REASON** we offer you a full money back guarantee if the product or products are returned within 14 days after you receive them.

## PLASMA DISPLAY KIT

Kit Includes: 12 digit display .4" Character Power supply for display above Complete specs for hookup.

Line cord Not Included. **ONLY \$3.95**



## TRANSISTORS - DIODES

*MJE1103	3/1.00
MJ3001	1.30
2N2222	6/1.00
2N2369	6/1.00
2N2905	4/1.00
*2N2907	15/1.00
2N3906	6/1.00
2N4400	6/1.00
2N4443 SCR	3/1.00
RCA 200V 115W NPN	.95
1N4004	15/1.00
1N4007	10/1.00
1N4148 (1N914)	20/1.00
3N201 VHF Pre amp	.80
D40C1 Power Darl	5/1.00

\*House numbered and P.C. Lead

## WATERGATE SPECIAL

Telephone Relay automatically starts and stops tape recorder. No batteries required. Kit complete with drilled P.C. Board.

Parts and Case **ONLY \$9.95**

## TI CALCULATOR CHIPS

TMS103 w/specs.	.99
TMS107 w/specs.	.99

## HARDWARE

New, includes 2-56, 4-40, 6-32 and 8-32 screws and nuts. A very usable selection.

1/2 pound	\$1.50
1 pound	\$2.60

## PROJECT CASES

SMALL \$1.50 MEDIUM \$2.00 LARGE \$2.75

D - 2-1/2"	D - 2"	D - 2-1/2"
W - 4-3/4"	W - 4-7/8"	W - 7"
H - 1-7/8"	H - 3-1/2"	H - 4"

All cases have a sloped front, white with black wrinkle finish.

## LOW POWER SHOTTY

74LS00	.25	74LS74	.49
74LS02	.25	74LS90	.85
74LS04	.30	74LS132	.90
74LS08	.25	74LS138	.89
74LS10	.25	74LS139	.89
74LS11	.32	74LS155	.90
74LS20	.31	74LS157	1.00
74LS21	.33	74LS162	1.39
74LS22	.33	74LS163	1.39
74LS27	.30	74LS175	1.09
74LS30	.31	74LS193	1.09
74LS32	.33	74LS258	1.09
74LS37	.40	74LS367	.70
74LS38	.35	74LS368	.70

**ORDER BY PHONE.** Charge your order to BankAmericard or Master Charge.  
Use our Toll Free Watts  
1-800-527-2304

## UNSCRAMBLER KIT

for all Scanners

- Tunes easily
- Full instructions included
- Easy to install
- 3 1/2" x 3 1/2" x 1 1/2"

**ONLY \$14.95**

## CLOCK KIT

- Kit includes • LT701 clock module
- Power Supply
  - Punched case
  - 12 or 24 hour operation

Complete except for line cord

LT701E	12 hour clock
LT701G	24 hour clock

**ONLY \$14.95**

## CMOS SALE

CD4000	.16	CD4040	1.00
CD4001	.16	CD4041	.69
CD4002	.16	CD4042	.59
CD4007	.16	CD4043	.60
CD4009	.45	CD4044	.59
CD4010	.45	CD4047	.59
CD4011	.16	CD4049	.35
CD4012	.16	CD4050	.35
CD4013	.29	CD4051	.90
CD4014	.75	CD4053	.90
CD4015	.75	CD4056	1.00
CD4016	.29	CD4058	.90
CD4017	.80	CD4060	1.00
CD4018	.80	CD4066	.69
CD4019	.39	CD4069	.30
CD4021	.90	CD4071	.16
CD4022	.90	CD4076	.99
CD4024	.70	CD4077	.39
CD4025	.19	CD4102	.68
CD4027	.39	CD4116	.39
CD4028	.75	CD4507	.40
CD4029	.99	CD4512	.50
CD4030	.16	CD4516	.85
CD4034	2.30	CD4518	.85
CD4035	.99	CD4520	.85

# World's Lowest IC Prices

## \* SPECIAL PRICES \*

MEMORIES			HIGH SPEED	
7400	12*	74152	90	4007
7402	14	74155	60	4008
7403	14*	74157	60	4011
7404	16*	74160	75	4012
7407	20	74161	75*	4013
7410	12*			4015
7420	12*	74163	75*	4016
7427	25	74165	80	4019
		74173	1.25	4021
7438	20*	74174	75*	4023
7440	12*	74175	75*	4028
7441	65*	74177	70	4029
		74180	80	4030
7445	60	74181	1.50	4040
7447	75			4042
7450	14			4043
7451	14*			4044
7473	28			4049
7474	28			4050
7475	40			4056
7480	40*			4068
				4071
7493	50			4073
7495	49			4075
74107	29			4516
74109	30			4528
74116	1.50			
74123	45*			
74141	90*			
74145	75			
74150	60*			
74151	60			

Order Minimum \$10.00. Add \$1.00 shipping and handling charge per order. California residents add 6% sales tax. All orders shipped First Class within 24 hours.

Order the famous lasix 6 volume programmed Learning Course "Microcomputer Design is a Snap" for \$99.50 and receive a special \$10.00 credit on any group of IC's.

Satisfaction 100% guaranteed.

C.O.D. Orders Phone (day or night) 408-354-1448

# ELTRON

PO BOX 2542 - A  
Sunnyvale, CA 94087

Free catalog—Just send us your name and address.

CIRCLE NO. 23 ON FREE INFORMATION CARD

For faster service  
USE ZIP CODE  
on all mail

## BURGLAR ALARMS

DIALING UNIT automatically calls police. \$29.95. Free security equipment catalog. S&S Systems, 5619-C St. John, Kansas City, MO 64123. (816) 483-4612.

## Burglar Smoke Fire Alarm Catalog

• Billions of dollars lost annually due to lack of protective warning alarms.

**FREE CATALOG** Shows you how to protect your home, business and person. Wholesale prices. Do-it-yourself. Free engineering service.



**Burd Security Co.**

Box 82209 Dept. PE Lincoln, Ne. 68501

## HOME ENTERTAINMENT FILMS

HOW ARE YOU FIXED FOR 16MM SOUND FILMS? Special Event! Operation Tall Ships, 16mm color sound, special. \$57.95 (you save \$2 + shipping), limited offer. Byron Nelson Golf, 1/4 hr 16mm B&W snd film, \$25. ea! While they last (+ \$2. ea shipping). W.C. Fields. If I Had A Million; Abbott & Costello, Midget Car Maniacs, \$37.95 ea (+ \$1 shipping — you save about \$2.). Home Movie Collectors — Stock Car 500, 200' Stand, 8 color, \$14.95 ea ppd; Foreman/Frazier — Murder in Venezuela, \$15.95 ea ppd, 200' Stand, 8 color. NFL Football Follies or the Moore/Maxim fight, St. 8 B&W, \$7.95 ea (+ \$0.75 shipping). Get started collecting now, or select from new 54-pg Columbia catalog, \$1.00 refundable with order; Castle catalog \$0.50 incl order form; Sportlite forms \$0.35 (coins, stamps, pls). SPORTLITE, Elect-5, 20 N. Wacker, Chicago, IL 60606.

## PRINTED CIRCUIT BOARD

4 1/2" x 6 1/2" SINGLE SIDED EPOXY BOARD 1/16" thick, unetched \$5/\$2.20

7 WATT LD-65 LASER DIODE IR \$8.95

2N 3820 P FET	\$ .45
2N 5457 N FET	\$ .45
TIS 43 UJT	\$ .35
ER 900 TRIGGER DIODES	4/ \$1.00
2N 6028 PROG. UJT	\$ .65
8 PIN DIP SOCKETS	\$ .24
14 PIN DIP SOCKETS	\$ .25
16 PIN DIP SOCKETS	\$ .28
18 PIN DIP SOCKETS	\$ .30
24 PIN DIP SOCKETS	\$ .40
40 PIN DIP SOCKETS	\$ .60

VERIPAX PC BOARD  
This board is a 1/16" single sided paper epoxy board, 4"x6"x.5" DRILLED and ETCHED which will hold up to 21 single 14 pin IC's or 8, 16, or LSI DIP IC's with busses for power supply connector. \$4.00

MV 5691 YELLOW GREEN BIPOLAR LED \$1.25  
FP 100 PHOTO TRANS. \$ .50  
RED, YELLOW, GREEN OR AMBER LARGE LED's ea. \$ .20  
MOLEX PINS 1000/ \$7.50

10 WATT ZENERS 3.9, 4.7, 5.6, 8.2, 10, 12, 15, 18, 22, 100, 150 or 200V ea. \$ .60  
1 WATT ZENERS 4.7, 5.6, 8.2, 10, 12, 15, 18 OR 22V ea. \$ .25  
MC6860 MODEM CHIP \$9.95

**Silicon Power Rectifiers**  
PRV 1A 3A 12A 50A 125A  
100 06 14 30 80 3.70  
200 07 20 35 1.15 4.25  
400 09 25 50 1.40 6.50  
600 11 30 70 1.80 8.50  
800 15 35 90 2.30 10.50  
1000 20 45 1.10 2.75 12.50

**SILICON SOLAR CELLS**  
2 1/4" diameter  
4V at 500 ma. \$4.00 / 2V at 200 mls \$2.00

**REGULATED MODULAR POWER SUPPLIES**  
+ 15 VDC at 100ma \$27.95  
115VAC INPUT \$27.95  
5VDC at 1A, 115VAC INPUT \$24.95  
12 VDC at 5 AMP \$24.95  
IN 4148 (IN914) 15/\$1.00

Send 25¢ for our catalog featuring Transistors and Rectifiers 145 Hampshire St., Cambridge, Mass.

## TANTULUM CAPACITORS

.22UF 35V 5/8 1.00	6.8UF 35V 3/8 1.00
.47UF 35V 5/8 1.00	22UF 35V \$ .40
.68UF 35V 5/8 1.00	30UF 6V \$ .40
1UF 35V 5/8 1.00	33UF 5V \$ .40
2.2UF 20V5/8 1.00	47UF 20V 5/8 1.00
3.3UF 35V 4/8 1.00	100UF 5V \$ .35
4.7UF 35V 4/8 1.00	150UF 15V \$ .50

M7001 ALARM CLOCK CHIP \$5.75

**NATIONAL MOS DEVICES**  
MM1402-1.75 MM5057-2.25  
MM1403-1.75 MM5058-2.75  
MM1404-1.75 MM5060-2.75  
MM5013-2.50 MM5061-2.50  
MM5016-2.50 MM5555-4.75  
MM5017-2.70 MM5556-4.75  
MM5055-2.25 MM5210-1.95  
MM5056-2.25 MM5260-1.75

**TTL IC SERIES**  
7400-15 7445-70 74151-70  
7401-15 7446-70 74153-65  
7402-15 7447-70 74154-1.10  
7403-15 7448-70 74155-70  
7404-20 7450-20 74157-70  
7405-20 7472-33 74161-85  
7406-25 7473-35 74163-80  
7407-25 7474-35 74164-95  
7408-25 7475-49 74165-1.05  
7409-21 7476-35 74173-1.40  
7410-15 7480-35 74174-95  
7411-20 7483-70 74175-92  
7412-20 7485-88 74176-75  
7413-45 7486-30 74177-79  
7414-70 7489-1.85 74180-70  
7416-25 7490-45 74181-2.10  
7417-25 7491-70 74190-1.20  
7420-20 7492-50 74191-1.20  
7425-28 7493-45 74192-85  
7426-25 7494-70 74193-85  
7427-30 7495-70 74194-85  
7430-20 7496-70 74195-75  
7432-25 74107-32 74196-88  
7437-25 74121-38 7425-1.25  
7438-25 74123-65 74279-90  
7440-16 74125-40 75324-1.75  
7441-85 74126-40 75491-85  
7442-82 74132-82 75492-65

**MINIATURE DIP SWITCHES**  
CTS-206-4 Four SPST switches in one minidip package. \$1.75  
CTS-206-8 Eight SPST switches in a 16 pin DIP package. \$1.95

5-BV SPST Miniature reed, relay, normally open, 330 Ohm coil resistance \$75, 3/\$2.00

**ALCO MINIATURE TOGGLE SWITCHES**  
MTA 106 SPDT \$1.20  
MTA 206 DPDT \$1.70

## Full Wave Bridges

PRV 2A	6A	25A
200	75	1.25
400	95	1.50
600	1.20	1.75

**SANKEN AUDIO POWER AMPS**  
SI 1010 G 10 WATTS \$ 7.95  
SI 1020 G 20 WATTS \$15.95  
SI 1050 G 50 WATTS \$27.95

CCD 110 LINEAR 256 XI BIT SELF SCANNING CHARGE COUPLED DEVICE \$65.00  
CCD 201 - 100 x 100 CHARGE COUPLED DEVICE \$99.00

**LINEAR CIRCUITS**  
LM307 - Op. Amp. \$ .30  
LM 309K 5V 1A REGULATOR \$ .95  
723 - 40 + 40VVF REGULATOR \$ .50  
301/748 HI Per. Op. Amp. \$ .31  
320T 5, 12, 15, or 24V NEG REG. \$1.25  
790C Op. Amp. \$ .31  
78MG5-Pns 5 to 30V, 500 ma reg. \$1.35  
79MG5-Neg 5 to 30V, 500 ma reg. \$1.35  
CA 3047 HI Per. Op. Amp. \$ .95  
340T 5, 6, 8, 12, 15, 18, 24V POS REG. TO-220 \$1.10  
741A or 741C OP AMP \$ .31  
LM 308 Oper. Amp., Low Power \$ .95  
747 - DUAL 741 \$ .65  
556 - DUAL TIMER \$1.00  
1456 - Oper. Amp. \$ .95  
LM 3900 - QUAD OP. AMP \$ .49  
LM 324 - QUAD 741 \$1.50  
560 - PHASE LOCK LOOP \$2.00  
561 - PHASE LOCK LOOP \$2.00  
565 - PHASE LOCK LOOP \$1.25  
566 FUNCTION GEN. \$1.65  
567 - TONE DECODER \$1.50  
LM 1310N FM STEREO DEMOD. \$2.75  
8038 IC VOLTAGE CONT. OSC. \$1.95  
LM 370 - AGC SQUELCH AMP \$1.50  
555 - 2nd - 2 HR. TIMER \$ .45  
553 QUAD TIMER \$ .45  
IL5 (MCT-2) OPTO-ISOLATOR \$ .80  
1458 DUAL OP AMP. \$ .60  
LM 380 - 2W AUDIO AMP. \$ .95  
LM 377 - 2W Stereo Audio Amp. \$2.50  
LM 381 - STEREO PREAMP \$1.50  
LM 382 - DUAL AUDIO PREAMP \$1.50  
LM 311 - HI PER. COMPARATOR \$ .90  
LM 319 - Dual HI Speed Comp. \$1.25  
LM 339 - QUAD COMPARATOR \$1.50

**TRIACS** SCR'S  
PRV 1A 10A 25A 1.5A 6A 35A  
100 40 70 1.30 40 50 1.20  
200 70 1.10 1.75 60 70 1.60  
400 1.10 1.60 2.60 1.00 1.20 2.20  
600 1.70 2.30 3.60 1.50 3.00

2708-BK EPROM \$45.00  
2522 STATIC SHIFT REG \$ 1.95  
2513 CHARACTER GEN \$ 9.95  
2518 HEX 32 BIT SR \$ 3.50  
2102-1 1024 BIT RAM \$ 1.49  
5280-4K DYNAMIC RAM \$ 6.95  
5202A UV PROM \$ 3.95  
MM5203 UV PROM \$ 6.95  
1702A UV PROM \$ 6.95  
5204 4K PROM \$10.95

MINIATURE MULTI-TURN TRIM POTS 100, 500, 1K, 2K, 5K, 10K, 100K, 200K, 1 Meg. \$75 each  
MULTI-TURN TRIM POTS Similar toourns 3010 style 3/16"x5/8"x1-1/4", 50, 100, 1K, 10K, 50K ohms \$1.50 ea. \$3/4.00

LIGHT ACTIVATED SCR'S TO-18, 200V 1A. \$ 1.75

**TRANSISTOR SPECIALS**  
2N3585 NPN Si TO-66 \$ .95  
2N3772 NPN Si TO-3 \$ 1.60  
2N456A PNP Ge \$ 1.95  
2N4908 PNP Si TO-3 \$ 1.00  
2N6056 PNP Si TO-3 Darlington \$ 1.70  
2N5086 PNP Si TO-92 4/5 1.00  
2N4898 PNP TO-66 \$ .60  
2N404 PNP Ge TO-5 5/5 1.00  
2N3919 NPN Si TO-3 RF \$ 1.50  
MPSA 13 NPN Si TO-92 3/5 1.00  
2N3767 NPN Si TO-66 \$ .70  
2N2222 NPN Si TO-18 5/5 1.00  
2N3055 NPN Si TO-3 \$ .80  
2N3904 NPN Si TO-92 5/5 1.00  
2N3906 PNP Si TO-92 \$ 1.00  
2N5296 NPN Si TO-220 \$ .50  
2N6109 PNP Si TO-220 \$ .95  
2N3638 PNP Si TO-5 5/5 1.00  
2N6517 NPN TO 92 Si 3/5 1.00

**C/MOS (DIODE CLAMPED)**  
74C02 - 22 4015- 95 4029- 1.10  
74C10 - 22 4016- 40 4030- 1.22  
74C193-1.50 4017- 1.05 4033- 1.50  
4001 - 22 4018- 1.00 4035- 1.10  
4002 - 22 4019- 25 4042 - 70  
4006 - 1.00 4020 1.05 4047 - 2.00  
4007 - 22 4022 - 95 4049 - 4.00  
4009 - 42 4023 - 22 4050 - 4.00  
4010 - 42 4024 - 75 4055 - 1.50  
4011 - 22 4025 - 22 4066 - 80  
4012 - 22 4026 - 1.25 4071 - 22  
4013 - 40 4027 - 40 4076 - 1.05  
4028 - 88

MCA-81 OPTICAL LIMIT SWITCH \$1.50

**LED READOUTS**  
FND 500-5" C.C. \$1.25  
HP 7740-3" C.C. \$ .95  
MAN 7-3" C.A. \$ .95  
NS 33-3 dig. array \$ .75  
DL 747 \$1.60

Terms: FOB Cambridge, Mass. Send Check or Money Order. Include Postage. Minimum Order \$5.00, COD'S \$20.00



## SOLID STATE SALES

P.O. BOX 74A  
SOMERVILLE, MASS. 02143 TEL. (617) 547-4005

WE SHIP OVER 95% OF OUR ORDERS THE DAY WE RECEIVE THEM

**LM-4**  
• 0.03% Accuracy • 13 ranges: 4 vdc, 4 vac & 5 ohms • Automatic zeroing & polarity with 0.03% accuracy • Overload indication • Battery powered with batteries & charger unit included • Test leads included • 1.9"H x 2.7"W x 4.0"D \$227.00

**NON-LINEAR SYSTEMS, INC.**



**LM-3.5**  
The Voltmeter + 0.5% Accuracy • 100% over-range • 19 ranges: 4 vdc, 4 vac, 5 ohms and, with the 3 current shunts which are included, 3 dc amps and 3 ac amps. • Automatic zeroing and polarity with 0.5% accuracy • Overload indication • Battery powered with batteries & charger unit included • Test leads included • 1.9"H x 2.7"W x 4.0"D \$147.00

**FM-7**  
• Rugged, portable & battery powered with batteries & charger unit included • High sensitivity: 30 mV - 50 Hz to 30 MHz (100 mV - 10 Hz to 50 Hz & 30 MHz to 60 MHz) • Input overload protection • 1.9"H x 2.7"W x 4.0"D \$195.00

**SC-5**  
• Extends the range of the NLS FM-7 Frequency Meter - and almost any 50 MHz frequency meter - to upper VHF and UHF frequency bands • 30-mV sensitivity • Accurate to 1 ppm • Rugged, portable & battery powered with batteries & charger unit included • 1.9"H x 2.7"W x 4.0"D • Interface cable & input cable included \$127.00

**LM-40**  
• 0.1% Accuracy • 13 ranges: 4 vdc, 4 vac & 5 ohms • Automatic zeroing and polarity with 0.1% accuracy • Overload indication • Battery powered with batteries & charger unit included • Test leads included • 1.9"H x 2.7"W x 4.0"D \$190.00

**SGS-ATES - Audio Power Amplifier IC's**

TBA800	5 watt	\$1.95
TBA810S	7 watt	2.10
TBA810AS	7 watt	2.10
TBA820	2 watt	1.35
TBA830S	4.2 watt	1.95
TCA940	10 watt	3.30
TDA2002	8 watt	4.20
TDA2010	12W HI-FI	5.25
TDA2020	20W HI-FI	6.20

Our Ancrona Information Book 101 contains 92 pgs of data & application notes on using SGS-ATES Audio Amps. Get your copy now. Only \$4.95

**ACE 236**  
3,648 Solderless Plug-In Tie Points CAPACITY: Up to 36-14 Pin DIP's • 4 5-way binding posts • 10-1/4" x 9-1/4" • Fully assembled - 512 separate 5-tie point terminals, 32 vertical distribution buses (each with 5 connected 5-tie-point terminals) plus 4 horizontal buses (each with 18 connected 4-tie-point terminals). \$79.95

**555C FROM FAIRCHILD**  
MINI-DIP PKG 3 for \$1.00

MN6040 C-MOS PLL - a single-chip phase-locked loop intended for use as a frequency synthesizer in CB transceivers and other communications equipment. \$7.90

**AMD 2900 SERIES BIPOLAR MICROPROCESSOR CIRCUITS**

1-9	10-up
AM2901DC	\$42.00 \$31.50
AM2902PC	3.82 3.18
AM2905PC	10.10 8.10
AM2906PC	11.20 8.95
AM2907PC	11.00 7.00
AM2909PC	8.95 7.15
AM2911PC	5.95 4.75
AM2913PC	4.15 3.15
AM2914DC	60.00 45.00
AM2918PC	5.40 3.20
AM2919PC	4.50 3.81
AM29704PC	15.75 12.60
AM29705PC	15.75 12.60
AM29720PC	5.00 4.20
AM29721PC	5.00 4.20
AM29750DC	4.50 3.60
AM29751DC	4.50 3.60
AM29760DC	6.80 5.50
AM29761DC	6.80 5.50
AM29803DC	7.65 5.95
AM29811DC	4.85 3.90

**INTERISL 8038 PRECISION WAVEFORM GENERATOR & VCO**  
P/N 8038CCPD \$3.90



**CLIPLITE 10 for \$1.50**  
New LED Mounting System

- CLIPLITE mounts from the front of the Panel in a .250 hole on 3/8" centers. Panel thickness from 1/16" to 1/8".
- CLIPLITE equalizes and increases the brightness of commonly used wide beam LEDs.
- CLIPLITE is to be used with 200" dia. LEDs.
- Specific colors - red, green, amber, or yellow when ordering.

**FLUKE MODEL 8030A DIGITAL MULTIMETER**  
3-1/2 digit, six-function multimeter. Measurement functions include ac volts (true rms), dc volts, ac current (true rms), dc current, resistance, and diode test. Each function, except the diode test, is supplemented by 5 selectable ranges for a total of 26 ranges (one range for diode test). \$250.00

**FLUKE MODEL 80T-150C**  
Temperature Probe Converts a dc voltmeter into a thermometer with a range of -55°C to +150°C. \$125.00

**JAPANESE TRANSISTORS**

2SC1973	3.00	2SC2828	.75
2SC1974	1.30	2SC2829	.75
2SC1975	3.10	2SC1226A	1.00
2SC2034	3.40	2SC1359	.90

**MICROPROCESSOR KITS**

AMD AM2900K1 - Evaluation & Learning Kit \$289.00  
SIGNETICS 2650KT9000 - Microprocessor Kit 99.00  
FAIRCHILD FB Microprocessor Kit 185.00  
INTERISL IM6100 Microprocessor Tutorial System Includes following modules: 6950 Intercept Jr, 6951 Jr RAM, 6952 Jr Programmable ROM-P/ROM & 6953 Jr Serial I/O 583.00  
INTERISL 6957 Audio Visual Module for IM6100 125.00

**SAM'S BOOKS**

TTL Cookbook/No. 21035/336 pgs \$8.95  
IC OP-AMP Cookbook/20969/592 pgs \$12.95  
Second Class Radio Telephone License Handbook/21092/256 pgs \$3.95  
5th Ed./2111/448 pgs \$7.50  
Transistor Substitution Handbook, 16th Ed. 21333/384 pgs \$4.95  
Reference Data for Radio Engineers, 6th Ed. 21218/1344 pgs \$30.00  
Basic Electricity/Electronics Series, Vol. 1 Basic 1081/160 pgs \$4.50  
Principals and Application/20167/320 pgs \$5.50  
Transistor Specifications Manual, 8th Ed. 21335/224 pgs \$6.95

**8080A/9080A 8-BIT MICROPROCESSOR COMPONENTS**

C8080A	\$19.50
AM9080ADC	21.00
P8212	4.00
P8216	3.40
AM8224PC	5.90
P8226	3.50
AM8228PC	8.20
AM8238PC	8.20
C8251	14.30
C8255	13.50

**AUDIO POWER AMPLIFIERS 5.5 WATT AN315**  
Designed for mobile radios, tape players, etc. Easy to use, High Gain - 53 dB (Closed Circuit) \$3.90 ea

**MICROPROCESSOR KITS**

AMD AM2900K1 - Evaluation & Learning Kit \$289.00  
SIGNETICS 2650KT9000 - Microprocessor Kit 99.00  
FAIRCHILD FB Microprocessor Kit 185.00  
INTERISL IM6100 Microprocessor Tutorial System Includes following modules: 6950 Intercept Jr, 6951 Jr RAM, 6952 Jr Programmable ROM-P/ROM & 6953 Jr Serial I/O 583.00  
INTERISL 6957 Audio Visual Module for IM6100 125.00

**MICROPROCESSOR KITS**

AMD AM2900K1 - Evaluation & Learning Kit \$289.00  
SIGNETICS 2650KT9000 - Microprocessor Kit 99.00  
FAIRCHILD FB Microprocessor Kit 185.00  
INTERISL IM6100 Microprocessor Tutorial System Includes following modules: 6950 Intercept Jr, 6951 Jr RAM, 6952 Jr Programmable ROM-P/ROM & 6953 Jr Serial I/O 583.00  
INTERISL 6957 Audio Visual Module for IM6100 125.00

**SANKEN HYBRID AUDIO POWER AMPLIFIERS**

SI-1010G (10W output) ... \$ 6.90  
SI-1020G (20W output) ... \$13.95  
SI-1050G (50W output) ... \$26.80

Data Sheet with Application Notes - \$0.50

**CARBON FILM RESISTORS (5%)**  
Only in Multiples of 100 pcs per value (ohms)

XW	...	\$1.69 per 100
XW	...	\$1.79 per 100

10	100	1.0K	10K	100K	1.0M
11	110	1.1K	11K	110K	1.1M
12	120	1.2K	12K	120K	1.2M
13	130	1.3K	13K	130K	1.3M
15	150	1.5K	15K	150K	1.5M
16	160	1.6K	16K	160K	1.6M
18	180	1.8K	18K	180K	1.8M
20	200	2.0K	20K	200K	2.0M
22	220	2.2K	22K	220K	2.2M
24	240	2.4K	24K	240K	2.4M
27	270	2.7K	27K	270K	2.7M
30	300	3.0K	30K	300K	3.0M
33	330	3.3K	33K	330K	3.3M
36	360	3.6K	36K	360K	3.6M
39	390	3.9K	39K	390K	3.9M
43	430	4.3K	43K	430K	4.3M
47	470	4.7K	47K	470K	4.7M
51	510	5.1K	51K	510K	5.1M
56	560	5.6K	56K	560K	5.6M
62	620	6.2K	62K	620K	6.2M
68	680	6.8K	68K	680K	6.8M
75	750	7.5K	75K	750K	7.5M
82	820	8.2K	82K	820K	8.2M
91	910	9.1K	91K	910K	9.1M

**1" (26mm) GaAsP LED NUMERIC DISPLAY**

EP1000 (Common Anode)

1 Place - \$4.90  
3 Places - \$13.00  
5 Places - \$19.00

**PLESSEY SL1600 APPLICATIONS MANUAL**  
Contains 114 pages circuit data, system design and technical data for SL1600 Series Radio Communications Integrated Circuits. \$1.95

**CONTINENTAL SPECIALTIES**

**PROTO BOARDS & EXPERIMENTERS**

Build & test circuits as fast as you think

PB-6	\$15.95	PB103	\$59.95
PB100	19.95	PB104	79.95
PB101	29.95	EX300	9.95
PB102	39.95	EX600	10.95

**PLESSEY SAMPLER**  
300 METALIZED CAPACITORS 18 DIFFERENT STD. VALUES \$26.00

**MATSUO DIPPED TANTALUM CAPACITORS**

MF V	MF V	MF V	MF V	MF V	MF V
1	35	33	6.8	16	40
15	35	33	6.8	35	45
22	35	33	10	16	42
33	35	33	10	25	45
47	35	33	10	35	90
68	35	33	15	20	45
10	35	33	15	35	1.32
15	35	33	20	16	45
22	35	33	20	1.32	0.15
33	35	33	40	17	20
47	35	33	42	68	1.52
68	35	33	45	100	1.60
100	35	33	45	100	1.60

**PLESSEY POLYESTER (CAPACITOR) MINI BOX**

MF V	MF V	MF V	MF V	MF V	MF V
0.01	1000	14	0.39	250	15
0.012	1000	14	0.47	250	15
0.015	1000	14	0.56	250	15
0.018	1000	14	0.68	250	15
0.022	1000	14	0.82	250	17
0.027	1000	14	1.00	17	100
0.033	1000	14	1.12	100	18
0.039	630	14	1.5	100	20
0.047	630	14	1.8	100	21
0.056	630	14	2.2	100	23
0.068	630	14	2.7	100	26
0.082	630	14	3.3	100	30
0.100	630	14	4.0	15	100
0.12	630	14	4.7	100	33
0.15	630	14	5.6	100	36
0.18	630	14	6.8	100	41
0.22	630	14	8.2	100	45
0.27	630	14	10.0	15	100
0.33	630	14	12.0	15	100
0.40	630	14	15.0	100	54
0.47	630	14	18.0	100	60
0.56	630	14	22.0	100	66
0.68	630	14	27.0	100	75
0.82	630	14	33.0	100	84
1.00	630	14	40.0	15	100
1.2	630	14	47.0	15	100
1.5	630	14	56.0	15	100
1.8	630	14	68.0	15	100
2.2	630	14	82.0	15	100
2.7	630	14	100.0	15	100
3.3	630	14	120.0	15	100
4.0	630	14	150.0	15	100
4.7	630	14	180.0	15	100

**PROTO BOARDS**

With built-in regulated short-proof power supplies

PB203	5V, 1 amp regulated power supply	\$ 75.00
PB203A	5V, 1 amp and 15V, 1/2 amp regulated power supply	120.00

**LOGIC MONITOR 1**  
Simultaneously displays static and dynamic logic states of DTL, TTL, HTL or CMOS DIP ICs. Pocket size. \$74.95

**LOGIC MONITOR 2**  
Displays static and dynamic states of digital ICs such as CMOS, HTL, TTL, DTL & RTL. Selectable threshold control. \$124.95

**LOGIC PROBE LP-1**  
Compact, circuit-powered multifunction logic probe. Multi-family compatibility. DTL/TTL/HTL/CMOS. Traces logic levels and pulses through digital circuitry. \$44.95.

**RESISTOR KITS 5% CARBON FILM RESISTORS**

**1/4 WATT KIT**  
42 Different Values (68Ω to 4.7MΩ)  
20 Each Value

**1/2 WATT KIT**  
42 Different Values (68Ω to 4.7MΩ)  
20 Each Value

1/4W - \$24.90 PER KIT  
1/2W - \$26.90 PER KIT

**COMPLETE WITH STORAGE BIN**

**DIP SOCKETS**

**LOW PROFILE, SOLDER, TIN**

Pin	1-24	25-49	50 UP
8 Pin	16	15	14
14 Pin	19	18	17
16 Pin	21	20	19
18 Pin	28	27	26
20 Pin	34	32	32
22 Pin	36	36	34
24 Pin	37	36	35
28 Pin	44	43	42
36 Pin	59	58	57
40 Pin	62	61	60

**STANDARD, SOLDER, TIN**

Pin	25	23	22
8 Pin	25	23	22
14 Pin	27	25	24
16 Pin	30	27	25
18 Pin	35	32	30
22 Pin	40	36	34
24 Pin	49	45	42
28 Pin	59	54	51
36 Pin	75	72	68
40 Pin	99	96	93
36 Pin	139	126	115
40 Pin	159	146	130

**STANDARD, SOLOER, GOLD**

Pin	30	27	24
8 Pin	30	27	24
14 Pin	35	32	29
16 Pin	38	35	32
18 Pin	52	47	43
22 Pin	70	63	57
24 Pin	70	63	57
28 Pin	110	100	90
36 Pin	175	160	126
40 Pin	175	159	145

**WIREWRAP GOLD (Level No. 3)**

Pin	45	41	37
10 Pin	45 <td>41</td> <td>37</td>	41	37
14 Pin	39	38	37
16 Pin	43	42	41
18 Pin	75	68	62
24 Pin	105	95	85
28 Pin	140	125	110
36 Pin	159	145	130
40 Pin	175	155	140

**FAIRCHILD TECHNOLOGY KITS**  
Complete Specifications on Back of Each Kit

**DIGITS**

FTK0001	0.5" High Common Cathode Digit	\$ 1.00
FTK0002	0.5" High Common Anode Digit	1.00
FTK0003	0.357" High Common Cathode Digit	0.75
FTK0004	0.8" High Common Cathode Digit	2.00
FTK0005	0.8" High Common Anode Digit	2.00

**0.8" HIGH DISPLAY ARRAYS**

FTK0010	12 Hour, 3 1/2 Digit Clock Display	7.00
FTK0011	24 Hour, 4 Digit Clock Display	8.00

**LED LAMPS**

FTK0020	10 Red LED Lamps	1.00
FTK0021	5 Mixed Colored LED Lamps	1.00
FTK0022	10 LED Mounting Clips	1.00
FTK0023	5 Three Place LED Mounting Adapters	1.00

**PHOTO TRANSISTORS**

FTK0030	5 Flat Lens Photo Transistors	1.00
FTK0031	5 Round Lens Photo Transistors	1.00
FTK0032	3 Flat Lens Photo Darlington	1.00
FTK0033	3 Round Lens Photo Darlington	1.00

**PHOTOARRAYS**

FTK0040	9-Element Tape Reader Array	15.00
FTK0041	12-Element Card Reader Array	24.00
FTK0042	Reflective Opto Coupler	4.00

**COUPLERS**

FTK0050	3 General Purpose Opto Couplers	1.00
FTK0051	Darlington Opto Coupler	1.00

**MOS CLOCK CIRCUITS**

FTK0400	Digital Clock/Calendar Circuit (FCM7001)	7.00
FTK0401	Digital Clock/Calendar with BCD Outputs (FCM7002)	7.00
FTK0402	Direct Drive Digital Clock Circuit with AC Output (FCM3817A)	5.00
FTK0403	Direct Drive Digital Clock Circuit with DC Output (FCM3817D)	5.00
FTK0405	Direct Drive Digital Clock/Calendar Circuit (FCM7015)	6.00

**KITS**

||
||
||

**BOOKS AND MAGAZINES**

FREE book prophet Elijah coming before Christ. Wonderful bible evidence. Megiddo Mission, Dept. 64, 481 Thurston Rd., Rochester, N.Y. 14619.

BACK ISSUE MAGAZINES. 1890 to 1976. Free list. Send stamped envelope to Everybody's Bookshelf, Dept. PE, 317 West 6th, Los Angeles, CA 90014.

**BUSINESS OPPORTUNITIES**

I MADE \$40,000.00 Year by Mailorder! Helped others make money! Free Proof. Torrey, Box 318-NN, Ypsilanti, Michigan 48197.

FREE CATALOGS. Repair air conditioning, refrigeration. Tools, supplies, full instructions. Doolin, 2016 Canton, Dallas, Texas 75201.

MAILORDER MILLIONAIRE helps beginners make \$500 weekly. Free report reveals secret plan! Executive (1K\$), 333 North Michigan, Chicago 60601.

GET RICH with Secret Law that smashes debts and brings you \$500 to \$5 Million cash. Free report! Credit 4K5, 333 North Michigan, Chicago 60601.

**HIGHLY PROFITABLE ONE-MAN ELECTRONIC FACTORY**

Investment unnecessary, knowledge not required, sales handled by professionals. Postcard brings facts about this unusual opportunity. Write today! Barta-DR, Box 248, Walnut Creek, CA 94597.

FREE SECRET BOOK "2042 UNIQUE, Proven Enterprises" Fabulous "Little Known's". Work home! Haylings-B, Carlsbad, Calif. 92008.

HOW TO MAKE \$2,000 WEEKLY at home using other people's money. Guaranteed. Free Details. Richlieu, Box 25357, Dept. F5, Houston 77005.

MAKE BIG MONEY in spare time selling: Tubes, Antennas, Speakers, Test Equipment, Lite Bulbs, Hi-Fi, etc. No investment. Free information: Allied Sales, Pimento, IN 47866. (812) 495-6555.

LIFETIME OPPORTUNITY for mechanically/electronically inclined individuals. Operate Successful Manufacturing Business. Mark, 92-K Brighton 11th, Brooklyn, New York 11235.

NEW LUXURY Car Without Cost. Free Details! Codex-ZZ, Box 6073, Toledo, Ohio 43614.

STUFF ENVELOPES \$250+ /Thousand, supplies. Enclose stamped, addressed envelope. Enterprises, Route One, Box 263-E5, Pauls Valley, OK 73075.

**MISCELLANEOUS**

WINEMAKERS: Free illustrated catalog yeasts, equipment. Semplex, Box 12276P, Minneapolis, Minn. 55412.

POPULAR ELECTRONICS INDEXES For 1976 now available. Prepared in cooperation with the Editors of "P/E." this index contains hundreds of references to product tests, construction projects, circuit tips and theory and is an essential companion to your magazine collection. 1976 Edition, \$1.50 per copy. All editions from 1972 onward still available at the same price. Add \$.25 per order for postage and handling. \$.50 per copy, foreign orders. INDEX, Box 2228, Falls Church, Va. 22042.

**TTL 7400N**

SN7400N	.13	SN74125N	.40
SN7401N	.14	SN74126N	.40
SN7402N	.14	SN74128N	.59
SN7403N	.14	SN74132N	.69
SN7404N	.17	SN74136N	.59
SN7405N	.17	SN74141N	.88
SN7406N	.25	SN74142N	3.70
SN7407N	.25	SN74143N	3.98
SN7408N	.17	SN74144N	3.98
SN7409N	.17	SN74145N	.69
SN7410N	.14	SN74147N	1.58
SN7411N	.20	SN74148N	.19
SN7412N	.21	SN74150N	.95
SN7413N	.39	SN74151N	.61
SN7414N	.64	SN74153N	.61
SN7416N	.24	SN74154N	.95
SN7417N	.29	SN74155N	.70
SN7420N	.14	SN74156N	.64
SN7421N	.20	SN74157N	.59
SN7422N	.20	SN74159N	2.50
SN7423N	.25	SN74160N	.85
SN7425N	.25	SN74161N	.85
SN7426N	.22	SN74162N	.85
SN7427N	.25	SN74163N	.85
SN7428N	.28	SN74164N	.98
SN7430N	.14	SN74165N	.97
SN7432N	.23	SN74166N	1.09
SN7433N	.30	SN74167N	2.75
SN7437N	.21	SN74170N	1.69
SN7438N	.21	SN74172N	8.75
SN7440N	.14	SN74173N	1.24
SN7442N	.37	SN74174N	.94
SN7443N	.68	SN74175N	.84
SN7444N	.85	SN74176N	.77
SN7445N	.65	SN74177N	.76
SN7446AN	.70	SN74178N	1.19
SN7447AN	.67	SN74179N	1.49
SN7448N	.69	SN74180N	.67
SN7450N	.14	SN74181N	1.94
SN7451N	.14	SN74182N	.59
SN7453N	.14	SN74184N	1.75
SN7454AN	.14	SN74185AN	1.74
SN7460N	.14	SN74186N	6.95
SN7470N	.26	SN74188N	2.98
SN7472N	.25	SN74190N	1.04
SN7473N	.29	SN74191N	1.04
SN7474N	.29	SN74192N	.84
SN7475N	.46	SN74193N	.84
SN7476N	.30	SN74194N	.89
SN7480N	.35	SN74195N	.54
SN7481AN	.95	SN74196N	.87
SN7482N	.59	SN74197N	.73
SN7483AN	.65	SN74198N	1.64
SN7484AN	1.50	SN74199N	1.64
SN7485N	.84	SN74221N	1.14
SN7486N	.30	SN74246N	1.95
SN7489N	1.85	SN74247N	1.70
SN7490AN	.43	SN74248N	1.75
SN7491AN	.59	SN74249N	1.75
SN7492AN	.44	SN74251N	1.05
SN7493AN	.44	SN74265N	.85
SN7494N	.69	SN74278N	1.99
SN7495AN	.67	SN74279N	1.57
SN7496N	.65	SN74283N	1.39
SN7497N	.25	SN74284N	4.50
SN74100N	.97	SN74285N	4.50
SN74104N	.42	SN74290N	.85
SN74105N	.42	SN74293N	.83
SN74107N	.28	SN74298N	1.64
SN74109N	.47	SN74351N	1.92
SN74110N	.52	SN74365N	.65
SN74111N	.69	SN74366N	.65
SN74116N	1.50	SN74367N	.65
SN74120N	1.40	SN74368N	.65
SN74121N	.34	SN74390N	1.40
SN74122N	.38	SN74393N	1.40
SN74123N	.48	SN74490N	1.90

**TTL LOW POWER SCHOTTKY**

SN74LS00N	.23	SN74LS138N	1.25
SN74LS01N	.23	SN74LS139N	1.35
SN74LS02N	.23	SN74LS145N	.19
SN74LS03N	.23	SN74LS151N	.99
SN74LS04N	.28	SN74LS153N	.99
SN74LS05N	.28	SN74LS155N	1.45
SN74LS08N	.23	SN74LS156N	1.45
SN74LS09N	.23	SN74LS157N	.99
SN74LS10N	.23	SN74LS158N	1.10
SN74LS11N	.23	SN74LS160N	1.50
SN74LS12N	.25	SN74LS161N	1.50
SN74LS13N	.65	SN74LS162N	1.50
SN74LS14N	1.25	SN74LS163AN	1.50
SN74LS15N	.23	SN74LS164N	1.60
SN74LS20N	.23	SN74LS168N	2.25
SN74LS21N	.23	SN74LS169N	2.25
SN74LS22N	.23	SN74LS170N	2.70
SN74LS26N	.37	SN74LS174N	1.25
SN74LS27N	.27	SN74LS175N	1.25
SN74LS28N	.30	SN74LS181N	3.30
SN74LS30N	.23	SN74LS190N	1.80
SN74LS32N	.33	SN74LS191N	1.80
SN74LS33N	.37	SN74LS192N	1.80
SN74LS37N	.37	SN74LS193N	1.80
SN74LS38N	.37	SN74LS194AN	1.30
SN74LS40N	.27	SN74LS195AN	1.40
SN74LS42N	.89	SN74LS196N	1.40
SN74LS47N	1.10	SN74LS197N	1.40
SN74LS48N	1.10	SN74LS221N	1.30
SN74LS49N	1.10	SN74LS240N	2.50
SN74LS51N	.23	SN74LS241N	2.40
SN74LS54N	.23	SN74LS242N	2.40
SN74LS55N	.23	SN74LS243N	2.40
SN74LS63N	1.75	SN74LS244N	2.50
SN74LS73N	.45	SN74LS247N	1.30
SN74LS74N	.45	SN74LS248N	1.30
SN74LS75N	.65	SN74LS249N	1.30
SN74LS76N	.45	SN74LS251N	1.50
SN74LS78N	1.39	SN74LS252N	1.50
SN74LS83AN	1.60	SN74LS257N	1.40
SN74LS85N	.89	SN74LS258N	1.40
SN74LS86N	.48	SN74LS261N	2.95
SN74LS89N	.89	SN74LS266N	.95
SN74LS91N	1.15	SN74LS279N	.75
SN74LS92N	.85	SN74LS283N	1.35
SN74LS93BN	.85	SN74LS290N	1.30
SN74LS95AN	1.50	SN74LS293N	1.30
SN74LS96N	1.65	SN74LS295AN	1.75
SN74LS107N	.45	SN74LS298AN	1.75
SN74LS109N	.50	SN74LS324AN	2.25
SN74LS112N	.45	SN74LS352AN	1.45
SN74LS113N	.45	SN74LS353AN	1.70
SN74LS114N	.45	SN74LS365AN	.69
SN74LS122N	.89	SN74LS366AN	.69
SN74LS123N	.99	SN74LS367AN	.75
SN74LS124N	1.95	SN74LS368AN	.69
SN74LS125N	.75	SN74LS375AN	.59
SN74LS126N	.75	SN74LS386AN	1.95
SN74LS132N	1.19	SN74LS395AN	1.95
SN74LS136N	.50	SN74LS670AN	2.75

**CMOS**

CD4000BE	.09	CD4035BE	.99	CD4507BE	.52
CD4001BE	.18	CD4040BE	.99	CD4510BE	1.05
CD4002BE	.13	CD4041BE	.67	CD4511BE	1.25
CD4006BE	.99	CD4042BE	.63	CD4512BE	1.15
CD4007BE	.17	CD4043BE	.45	CD4514BE	2.50
CD4008BE	.80	CD4044BE	.45	CD4515BE	2.50
CD4009BE	.37	CD4046BE	2.45	CD4516BE	1.10
CD4010BE	.37	CD4047BE	2.45	CD4518BE	.90
CD4011BE	.18	CD4049BE	.37	CD4519BE	.79
CD4012BE	.17	CD4050BE	.37	CD4520BE	.79
CD4013BE	.37	CD4051BE	1.15	CD4522BE	1.98
CD4014BE	.89	CD4052BE	1.15	CD4526BE	1.50
CD4015BE	.89	CD4053BE	1.19	CD4527BE	1.50
CD4016BE	.37	CD4055BE	1.29	CD4528BE	1.20
CD4017BE	.94	CD4060BE	1.40	CD4531BE	1.25
CD4018BE	.99	CD4066BE	.59	CD4539BE	1.20
CD4019BE	.42	CD4068BE	.24	CD4555BE	.75
CD4020BE	1.04	CD4069BE	.24	CD4556BE	.75
CD4021BE	.99	CD4070BE	.24	CD4585BE	1.80
CD4022BE	.89	CD4071BE	.24	74C85/40085PC	1.20
CD4023BE	.18	CD4072BE	.29	74C160/40160PC	1.50
CD4024BE	.67	CD4073BE	.29	74C161/40161PC	1.50
CD4025BE	.17	CD4075BE	.29	74C162/40162PC	1.50
CD4026BE	1.39	CD4076BE	1.05	74C163/40163PC	1.50
CD4027BE	.39	CD4078BE	.24	74C174/40174PC	1.40
CD4028BE	.75	CD4081BE	.24	74C175/40175PC	1.40
CD4029BE	.79	CD4082BE	.29	74C192/40192PC	1.50
CD4030BE	.37	CD4085BE	.75	74C193/40193PC	1.50
CD4033BE	1.60	CD4086BE	.75	74C195/40195PC	1.40
CD4034BE	2.95	CD4502BE	1.15		

**MOS AND BI-POLAR MEMORIES**

P/N	Description	Price
C1702A	(1 Microsecond) 256 x 8 EPROM	8.95
C1702A	(1.5 Microsecond) 256 x 8 EPROM	5.95
C2708	1K x 8 EPROM (450 NS)	49.00
8080A	8 Bit MOS CPU (2 microsecond)	14.95
2102-1P	1K Static Ram 1024 x 1 (450 NS)	2.50
3342PC	Quad 64 Bit Static Shift Register	4.50
3347PC	Quad 80 Bit Static Shift Register	4.50
3341APC	4 x 64 MOS FIFO 1 MHz Shift Register	4.50
TMS0117NC	Decimal Arithmetic Processor	10.00
LCM1001	Microprocessor Learning Module	149.95
TMS4024NC	64 x 9 FIFO	8.95
TMS4050NL	4K Dynamic RAM Plastic 300NS (18 Pin)	6.95
TMS4060NL	4K Dynamic RAM Plastic 300NS (22 Pin)	6.95
AY5-1013P	8 Bit UART	6.95
SEMI 4804A	4K STATIC RAM 1024 x 4 (450 NS) single 5V supply	14.95
93415PC	1K RAM 40 NS Open Collector	11.00
93425PC	1K RAM 40 NS Tri-State	11.00
AM2901DC	4 Bit Bi-Polar Microprocessor slice	31.50
AM2902PC	Carry Look Ahead Circuit	3.18
AM2905PC	Quad 2 Input Bus Transceiver	8.10
AM2907PC	Quad Bus Transceiver with Tri-State Receiver and Parity	7.00
AM2909PC	4 Bit Cascadable Microprogram Sequencer	7.15
AM2918PC	Quad Deregister with Standard and Tri-State Outputs	4.32
F8 Kit	8 Bit Microprocessor Evaluation Kit with Software	185.00

**TEXAS INSTRUMENTS DATA BOOKS**

LCB1011	Understanding Solid State Electronics	2.95
LCB1891	Software Design for Microprocessors	12.95
LCC4041	Power Data Book	3.95
LCC4112	TTL Data Book	4.95
LCC4131	Transistor and Diode Data Book	4.95
LCC4151	Linear and Interface I.C. Data Book	3.95
LCC4200	Semiconductor Memories Data Book	2.95
LCC4230	Optoelectronics Data Book	2.95
LCC4241	Linear Control Circuits Data Book	2.95

**FAIRCHILD DATA BOOKS**

Power Data Book	3.00
Bi-Polar Memory Data Book	2.50
Linear Integrated Circuit Data Book	2.95
Low Power Schottky and Macrologic TTL Interface Data Book	1.75
Raytheon Linear Integrated Circuit Data Book	1.50
Solid State Scientific CMOS 'B' Series Data Book	2.50
Unitrode Semiconductor Data Book	4.95

**"ONLY MAJOR MANUFACTURERS SUPPLIED"**

"This is a partial listing. Our complete catalogue lists many more device types & series which are available." "Our quality cannot be surpassed". "How can you beat the combination — the finest quality; current production; latest date code devices from the major manufacturers as Texas Instruments & Fairchild Semiconductor — At the lowest prices — Surely an unbeatable combination. Get the most value for your Dollar". Active Electronic provides the three essentials in Semiconductor

Distribution — 1. QUALITY  
2. INVENTORY  
3. PRICE  
We now offer the lowest mix pricing for major manufacturers devices only, with the largest variety of devices available from stock, from one source.  
We offer Rolls Royce quality at Volkswagen pricing.

We offer the largest variety of current production Texas Instruments and Fairchild Semiconductor only 74LS devices from stock. Even though the competition for current production major manufactured 74LS devices is limited, we are dedicated to provide the best prices possible. As our costs decrease, we pass the savings on to you, our customer.

**Active Electronic Sales Corp.**  
P.O. BOX 1035 FRAMINGHAM, MASSACHUSETTS 01701  
Telephone Orders & Enquiries (617) 879-0077 New Catalogue available on request  
**NOW IN CANADA** 5647 Ferrier st. 44 Fasken Dr-Unit 25  
Montreal, Quebec Roxdale, Ontario  
2 Locations Tel. (514) 735-6429 Tel. (416) 677-4287

MINIMUM ORDER \$10.00 \* ADD \$1.00 TO COVER POSTAGE & HANDLING \* Canadian customers add 30% for duty and handling. All federal and provincial taxes extra.

READER SERVICE NO.      ADVERTISER      PAGE NO.

1	A P Products, Inc	87
2	AVR Electronics	101
	Acoustic Fiber Sound Systems, Inc	25
3	Active Electronic Sales Corp	122
6	Advanced Microcomputer Products	106
7	Allison Automotive Company	101
8	Ancrona Corp	121
	Audio Products, Inc	74
10	B&K Product of Dynascan	60
11	Bullet Electronics	118
12	Byte Publications	39

	CREI Capitol Radio Engineering Institute	70, 71, 72, 73
	Cleveland Institute of Electronics, Inc	28, 29, 30, 31
15	Cobra, Product of Dynascan	SECOND COVER
13	Continental Specialties Corporation	89
14	Crown	6

16	Delta Products, Inc	65
17	Digi-Key Corporation	115
	Digital Concepts	77
18	Digital Group, The	42
67	Digital Group, The	69
19	EICO	14
20	Edlie Electronics	112
21	Edmund Scientific Co	105, 124
22	Electronic Book Club	7
64	Electronics Unlimited	99
23	Eltron	120
24	Empire Scientific	94
25	Extron LIFESCREEN Projection System	39

26	Godbout Elecs., Bill	118
27	Grantham College of Engineering	103
28	Handic U.S.A. Inc.	41
5	Health Company	80, 81, 82, 83
30	IMSAI Manufacturing Corporation	54
31	Illinois Audio	102
32	International Electronics Unlimited	116

33	James Electronics	110, 111
34	Leader Instrument Corp	63
35	McIntosh Laboratory Inc	63
36	Mallory & Co., Inc., P.R.	23
37	Midland International	5
38	Motorola	27

	NRI Schools	8, 9, 10, 11
39	National Camera	102
40	New-Tone Electronics	117

41	DK Machine & Tool Corporation	51
42	OK Machine & Tool Corporation	58
43	Olson Electronics	116
44	Optoelectronics	114
45	PAIA Electronics	103
46	Pace CB	FOURTH COVER
47	Pearce-Simpson, Inc	2
48	Personal Computing Magazine	95
49	Pickering & Co.	THIRD COVER
69	Poly Paks	109

50	Quest Electronics	123
51	Radio Hut	119
	Radio Shack	37
52	Radio Shack	79

53	S A E	93
54	S.D. Sales Co.	113
55	Schober Organ Corp. The	104
56	Scientific Research	59
57	Secore	86
58	Shakespeare Company	35
60	Solid State Sales	120
60	Southwest Technical Products Corporation	13
61	Southwest Technical Products Corporation	15
	Speakerlab, Inc	104
62	Superscope, Inc	16, 17

29	Texas Instruments Incorporated	7
	Triple i	1
65	U.S. Pioneer Electronics	52, 53
4	United Audio Products, Inc	33
66	Wahl Clipper Corporation	99
68	Weatheralert, Inc	24

CLASSIFIED ADVERTISING  
105, 106, 112, 114, 116, 118, 120, 122

# PLANNING TO MOVE?

Let us know 8 weeks in advance so that you won't miss a single issue of **POPULAR ELECTRONICS**.

Attach old label where indicated and print new address in space provided. Also include your mailing label whenever you write concerning your subscription. It helps us serve you promptly.

Write to: P.O. Box 2772, Boulder, CO 80323, giving the following information:

Change address only     Extend my subscription

**ENTER NEW SUBSCRIPTION**

1 year \$9.98     Payment enclosed (1 extra BONUS issue)  
 Bill me later

**AFFIX OLD LABEL**

If you have no label handy, print OLD address here.

Name \_\_\_\_\_ please print

Address \_\_\_\_\_

City \_\_\_\_\_

State \_\_\_\_\_ Zip \_\_\_\_\_

NEW ADDRESS HERE    0206

Name \_\_\_\_\_ please print

Address \_\_\_\_\_

City \_\_\_\_\_

State \_\_\_\_\_ Zip \_\_\_\_\_

Additional postage per year For Canada add \$3. For countries outside U.S. and Canada add \$5—cash in U.S. currency only.

**Same day shipment.** First line parts only. Factory tested. Guaranteed money back. Quality IC's and other components at factory prices.

## INTEGRATED CIRCUITS

7400 TTL	74LS00 TTL	LM309K	NE555V	CD4026	3.95		
7401	17 74LS02	28 LM311H	NE568A	1.00	CD4028	1.50	
7402N	17 74LS02N	28 LM311N	NE568V	1.00	CD4028	1.50	
7403	17 74LS03	28 LM311N	NE567V	1.25	CD4030	.42	
7404N	18 74LS04N	34 LM318	7805	3.00	CD4015	2.00	
7405	42 74LS05	28 LM323K-5	7805C	3.00	CD4040	3.00	
7407N	42 74LS07N	28 LM323K-5	7805C	3.00	CD4042	1.50	
7409N	23 74LS10N	67 LM324N-12	7810	3.75	CD4043	2.00	
7410N	17 74LS10N	1.30 LM324N-15	7815	4.50	CD4044	2.00	
7411N	28 74LS12N	67 LM324N-15	7815C	3.75	CD4049	.39	
7412N	18 74LS12N	67 LM324N-15	7815C	3.75	CD4050	.55	
7414N	63 74LS12N	41 LM324N-15	7815C	3.75	CD4051	2.10	
7416N	17 74LS13N	28 LM324N-15	7815C	3.75	CD4060	2.10	
7417N	18 74LS13N	39 LM324N	7815C	3.75	CD4066	.85	
7420N	20 74LS13N	39 LM324N	7815C	3.75	CD4068	.75	
7423N	39 74LS13N	48 LM324N-5	7815C	3.75	CD4069	.40	
7438N	25 74LS17N	65 LM340K-1	DISCRETES	IM001	7.00	8787	2.75
7440N	17 74LS18N	1.10 LM340K-15	IM002	0.08	CD4071	4.0	
7442N	78 74LS18N	1.10 LM340K-15	IM002	0.08	CD4072	4.0	
7445N	85 74LS19N	LM340K-2A	IM003	0.08	CD4073	4.0	
7446N	1.04 74LS19N	LM340K-2A	IM003	0.08	CD4074	4.0	
7447N	60 74LS19N	LM340K-15	IM005	0.08	CD4075	1.75	
7448N	78 74LS19N	LM340K-15	IM005	0.08	CD4076	1.75	
7449N	1.04 74LS19N	LM340K-15	IM005	0.08	CD4077	1.75	
7450N	1.04 74LS19N	LM340K-15	IM005	0.08	CD4078	1.75	
7451N	1.04 74LS19N	LM340K-15	IM005	0.08	CD4079	1.75	
7531N	1.04 74LS19N	LM340K-15	IM005	0.08	CD4159	1.75	
7532N	1.04 74LS						

# AMAZING & HARD-TO-FIND SCIENCE BUYS! ALTERNATE ENERGY SPACE AGE • HOBBIES

## 3000 MI. POWER FOR AM RADIOS



Remarkably clearer reception of ball games far off, your old hometown, up to 3000 mi. away "subject to local cond." deluxe Ultrasensitive indoor directional AM Antenna for hi-fi, tuner inputs.

No. 72,263AV ... (9 $\frac{3}{4}$ x9 $\frac{1}{2}$ x11").....\$117.50 Ppd.

## SAVE 50%! 8 x 20 MONOCULAR



Top quality Spy Scope, a \$30 value, now \$14.95! Special purchase saves you 50%. 100% coated optics; 393 ft. field of view. Only 2 oz.—stores in pocket, purse, glove box.

No. 1568AV .. \$14.95 Ppd.

## SAVE 50%—DELUXE AM/FM WALL RADIO



Surplus Philco-Ford radio chassis (14 $\frac{1}{4}$ x13 $\frac{1}{2}$ x3 $\frac{1}{2}$ ") mounts anywhere. 11 transist., AM/FM hi-sens. tuner, AFC, 2 $\frac{3}{4}$ " dia. speaker. Orig. cost \$30 ea. in 3,000 quant. Retail over \$40.

No. 72,275AV (NEW! READY TO PLAY!) \$19.95 Ppd.  
SAVE \$6 MORE! BUY 3 OR MORE @ \$17.95 Ppd.

## NASA-CHOSEN FOR APOLLO/SOYUZ



The Astronauts used this super 20X60 binocular (modified) to view Earth! Big 60 mm objective lenses. 173-ft. field of view at 1000 yds. Relative brightness, 9.0. Fully coated optics, more!

No. 1556AV ..... (9 $\frac{1}{4}$ x8 $\frac{1}{2}$ "); 47.5 oz) \$99.95 Ppd.

## SOLAR ENERGY CUBE



Demonstration of sunlight converting to kinetic energy! Clear plastic cube in sun with its 3 silicon solar cells powers motor to whirl the propeller. Actually produces 1.5v DC, 825 ma.

No. 42,287AV (4x4x4") ..... \$23.95 Ppd.

## LOW COST PORT. INFRA-RED EYE



Self-cont. scope (90° nite vision) has 6032 IR converter tube. f/3.5 telephoto lens, adjust. triplet eyepiece. 1.6X Not avail. to Cal. res. except spec. auth'd.

No. 1683AV (6,12v DC) ..... \$299.95 Ppd.  
No. 1685AV (SUPER 2.5X BINOC.) \$329.95 Ppd.

## PRO ELECTRONIC SOUND CATCHER



Parabolic mike w/ 18 $\frac{3}{4}$ " transparent reflecting shield & 2 I.C.'s in amplifier magnifies signals 100X over omni-direction mikes. Catch sounds never bef. heard; highest signal to noise ratio poss. 5 $\frac{1}{2}$  lb.

No. 1649AV (REQ. 2 9V BATT.) ..... \$299.00 Ppd.

## 15% EFFICIENT SOLAR CELL!



Largest, most powerful ever for terrestrial use, to build solar panels where max. power per unit area is req. Output up to 12w per sq. ft. Produces .8A @ .45 v; .38w output. 2" x 2" sq. 2 Oz.

No. 42,514AV. \$39.95 Ppd.

## MEASURE WIND SPEED ANYWHERE



Hold handy (16 oz.) low cost Anemometer into the wind, quickly read wind speed on its big dial—from 5 to 70mph. Acc. to  $\pm$  3% of full scale (2.1 mph); no balts., adjustments, recalibration req.!(7 $\frac{1}{2}$ " HIGH)

No. 42,428AV..\$19.95 Ppd.

## QUALITY DETECTOR UNDER \$40




Our fully transistorized BFO unit can locate a quarter at 18". Powerful 6 trans.-oscillator-amplifier circuit. Comp. to others priced 50% more! Aluminum, just 2 lb.

No. 80,222AV \$39.95 Ppd.
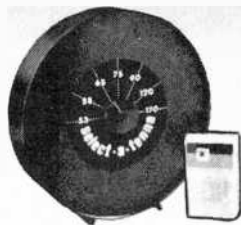
## EDMUND SCIENTIFIC CO.

300 Edscorp Bldg., Barrington, N.J. 08007 • (609) 547-3488  
America's Greatest Science • Optics • Hobby Center



# SUPER POWER FOR ANY AM RADIO

## New Antenna Assist Turns A Tiny Transistor Into A Tiger!

This amazing antenna assist has pulled in stations up to 1000 miles away! Just set it beside your radio (no wires, clips, grounding) and fine-tune Select-A-Tenna's dial to the same frequency—"gangbusters"! Terrific for sportsmen, vacationers, shut-ins, radio & electronics buffs. Service men & women—anyone who wants to "get" home to a favorite station. Great for clearing weak signals in radio depressed areas, off-coast islands, stations in crowded frequencies, hard-to-tune stations way up on the dial. Solid state—no tubes to replace. Uses no electricity or batteries—works almost forever! Tough, break-resistant plastic case blends with any decor.

## ULTRA SELECT-A-TENNA (TUNES OVER 1000 MILES AWAY)

Currently in use on Alaska's north slope where radio reception is very difficult. Has jack input & jack to which you attach 50 ft. of antenna wire (not included).

STOCK NO. 72,095N JUST \$19.95 Ppd.

STOCK NO. 72,147AV ONLY \$24.95 Ppd.

## The Edmund BIOSONE II

turns brainwaves into an audible or visual signal. \$149.95

## KNOW YOUR ALPHA FROM YOUR THETA!

For greater relaxation, concentration... monitor your alpha/theta brainwaves.

## Features Normally Found Only In Units Selling For More Than \$200.00—And 3 Feedback Modes.

The portable, professional quality Edmund Biosone II boasts 3 feedback modes—LED FM tone, threshold tone; a test mode to check overall system of operation. Easy to use, this beautiful 4-pound, simulated walnut unit (9 $\frac{1}{2}$  x 5 $\frac{1}{4}$  x 4 $\frac{1}{4}$ ") can be operated at home, in office or clinic. It gives you outputs to allow further monitoring of logic signal, raw EEG, filter output, meter, and FM. Total brainwave monitoring capability, incl. filter select feedback, with wide range calibration sensitivity control (5-100 microvolts). Completely safe, the Edmund Biosone II is similar to an electroencephalograph (EEG), enabling you to identify the electrochemical activity that exists at all times in the human brain. In addition to letting you know when you're most relaxed, Biosone II is a great conversation piece. Included at its low price are a set of electrodes, an earphone jack for private use. Uses latest advances in linear circuitry, runs on two 9v transistor batteries (not included).

STOCK NO. 1668AV ..... Just \$149.95 ppd.  
LOW COST STARTERS' UNIT, No. 71,809AV ..... \$59.95 ppd.



## "SEE" MUSIC IN PULSATING COLOR



## The Edmund 3-Channel Color Organ \$18.50

COMPLETELY ASSEMBLED! LESS THAN HALF THE PRICE OF OTHER MODELS!

Create your own audio "light show", add a new dimension to your music listening pleasure with the bargain-priced Edmund 3-Channel Sound To

Light Control. Lets you modulate 3 independent strings of colored lamps with the intensity of your music. They flash and vary in brightness related to the music's rhythm, pitch and volume—a pulsating light performance to music! You get volume and frequency sensitivity to a peak rating of 300 watts per channel. Just plug in your favorite colored flood or spotlight, and turn on! Great price, too. This high quality, fully assembled unit in metal housing, with 3 individually controlled circuits, is priced at less than half that of others. Complete instructions are included with this terrific value.

ASSEMBLED \$18.50 Ppd.  
NO. 42,309AV

UNASSEMBLED, IN KIT FORM \$15.95 Ppd.  
NO. 42,336AV ONLY

## GIANT FREE 164 PG. CATALOG



4000 UNUSUAL BARGAINS  
FOR HOBBYISTS,  
SCHOOLS, INDUSTRY

## COMPLETE AND MAIL COUPON NOW

EDMUND SCIENTIFIC CO. 300 Edscorp Bldg., Barrington, N. J. 08007


Send me the following:

Stock No.	Quantity	Price Ea.

Charge my  American Exp  BankAmericard  Master Chg  
Interbank No. \_\_\_\_\_  
Card No. \_\_\_\_\_

Expiration Date \_\_\_\_\_  
30-DAY MONEY-BACK GUARANTEE. You must be satisfied or return any purchase in 30 days for full refund.  
Signature \_\_\_\_\_  
Address \_\_\_\_\_  
City, State, Zip \_\_\_\_\_
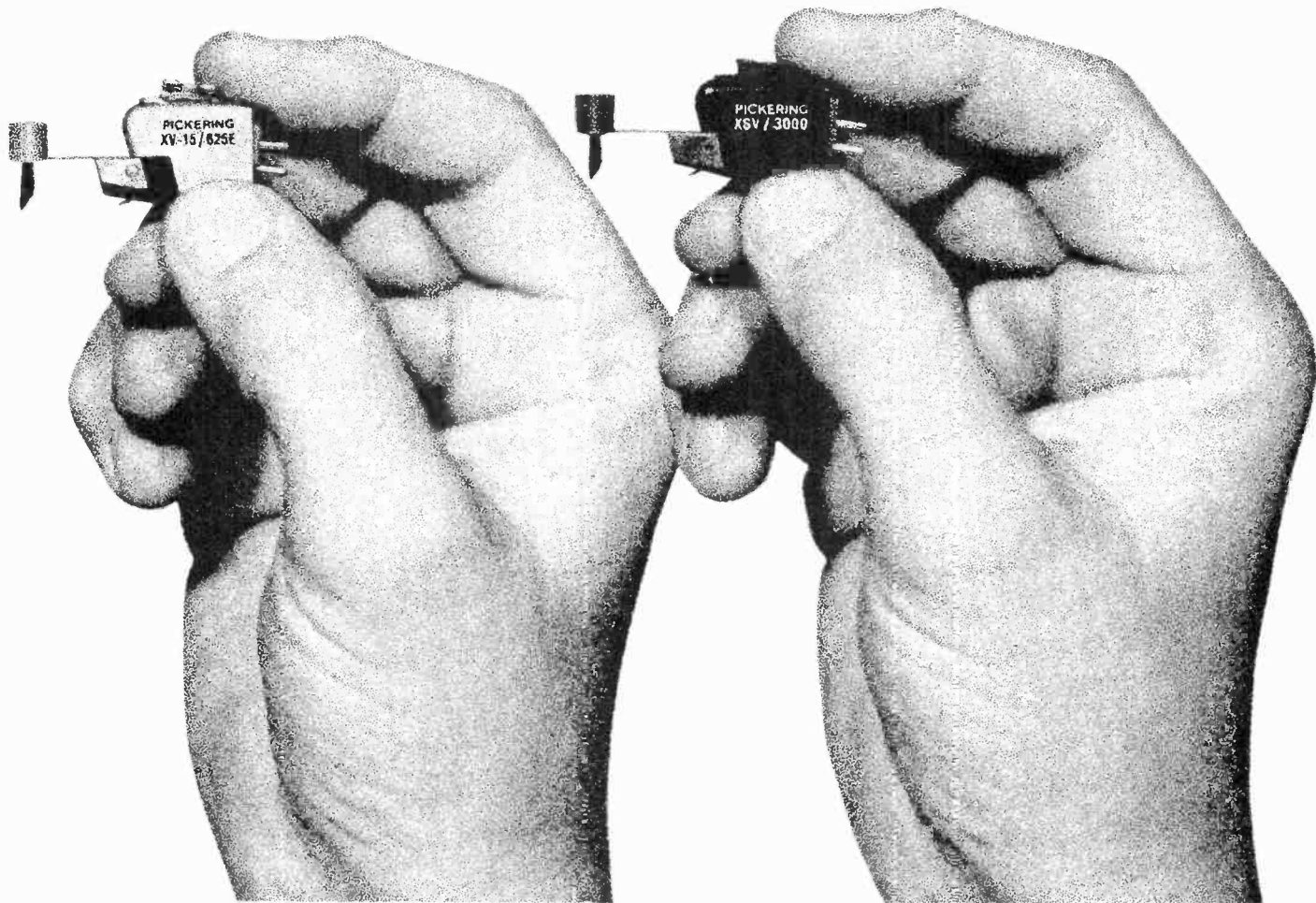
# Two sources of perfection in stereo sound.



## Match one to your equipment

**"The right Pickering Cartridge for your equipment is the best Cartridge money can buy."**

We've been saying that for years, and tens of thousands of consumers have profited by applying this principle in assembling their playback systems.

If you have a fine manual turntable, the XSV/3000 is a perfect choice.

If you have a high quality automatic turntable, then installing an XV-15/625E in its tone arm is a perfect choice.

The summary advice of **Stereo's Lab Test**, in an unusual dual product review, we think brilliantly states our position: "The XV-15/625E offers performance per dollar; the XSV/3000, the higher absolute performance level." That makes both of these cartridges **best buys!**



### FREE!

Pickering's new XSV/3000 is a remarkable development. It possesses our trademarked Stereo-hedron Stylus Tip, designed to assure the least record wear and the longest stylus life achievable in these times with a stereo cartridge. Its frequency response is extraordinarily smooth and flat; its channel separation is exceptional; its transient response affords superb definition. It represents a whole new concept of excellence in stereo cartridges.

Read the whole evaluation report. Send for your free copy of the **Stereo "Lab Test"** reprint; write to Pickering & Co., Inc., 101 Sunnyside Blvd., Plainview, N. Y. 11803. Department PE-5

 **PICKERING**

*"for those who can hear the difference"*

PICKERING & CO., INC., COPYRIGHT 1977

CIRCLE NO. 49 ON FREE INFORMATION CARD



**That bad language on your CB  
may not be bad language.**

**It may be bad CB.**

Every CBer knows who the enemy is.  
Static.

And while nobody yet has come up with a way to  
kill it, Pace has hurt it. A lot.

Because every Pace CB has a minimum  
of six noise suppressors built into it.  
Some as many as nine!

So, while there's still no  
such thing as noise-free  
CB, a Pace comes as close  
to it as you're going to get.



PACE 40 CHANNEL MODEL #8015

Pace. We're very bluenosed about bad language.  
So we're doing everything  
we can to clean up the  
CB airwaves.

**pace CB**

PACE CB/PACE TWO-WAY RADIO PRODUCTS  
BY PATHCOM INC., HARBOR CITY, CA 90710

**When you've got a Pace  
40-channel CB,  
you've got the world by the ears.**

For your convenience there are seven Pace regional warranty centers, plus more than 300 independent Pace service repair centers around the nation.

CIRCLE NO. 46 ON FREE INFORMATION CARD