FEBRUARY 1960

TWO SHILLINGS

Wireless World

ELECTRONICS

Radio · Television

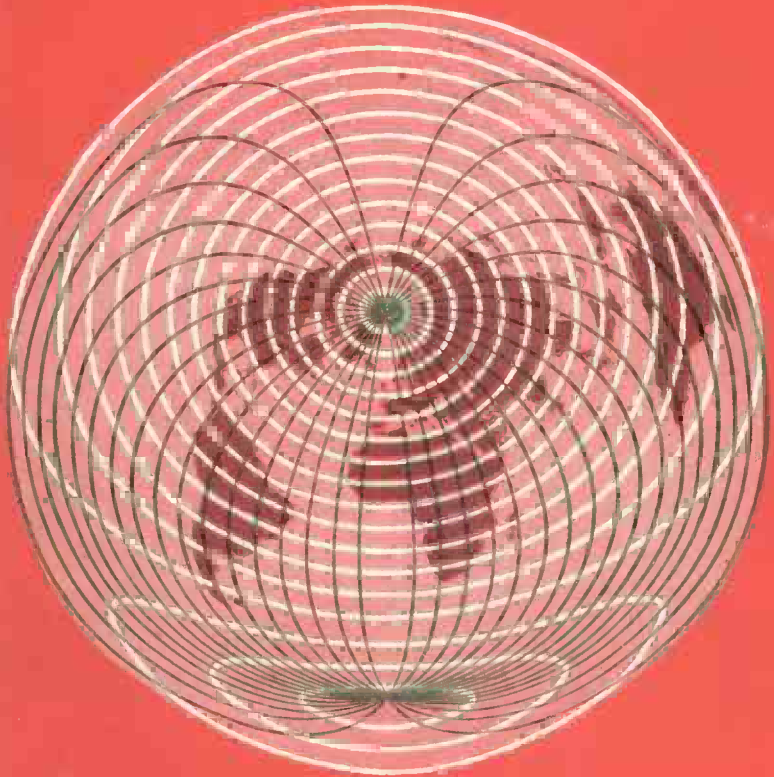

FORTY-NINTH YEAR OF PUBLICATION

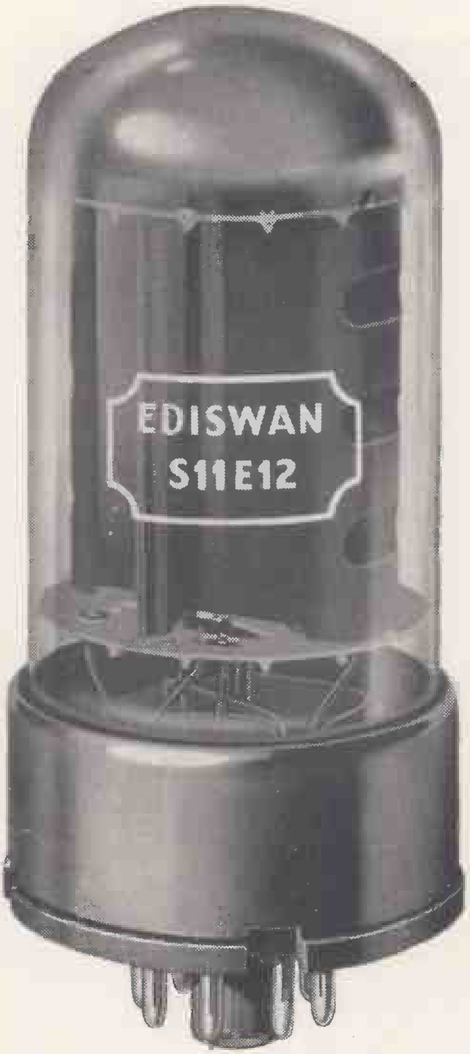

THE EDISWAN S11E12 (CV4060)
Special Quality Beam Tetrode

a newcomer with a first class reference

The S11E12 is the latest addition to the range of Ediswan valves designed specifically for use in series or shunt control circuits.

The S11E12 has an international octal base and the important parameters are as follows:

Heater Voltage (volts)	V_h	6.3
Heater Current (amps)	I_h	1.6
Anode Voltage, maximum (volts)	V_a (max)	800
Screen Voltage, maximum (volts)	V_{g2} (max)	300
Mutual Conductance (mA/V)	g_m	13.5
Anode Dissipation (watts)	P_a (max)	28
Cathode Current (mA)	I_k (max)	300

The new valve is specially designed to resist shock and is quality tested at all stages of manufacture to ensure maximum reliability and life expectancy.

Further information on this and other valves in the CV 4000 range will be gladly sent on request.

EDISWAN
MAZDA
INDUSTRIAL VALVES
AND CATHODE RAY TUBES

Associated Electrical Industries Ltd
Radio and Electronic Components Division
PD 16, 155 Charing Cross Road, London, W.C.2.
Tel: GERrard 8660. Telegrams Sieswan Westcent London

CRC 16/9

Wireless World

ELECTRONICS, RADIO, TELEVISION

FEBRUARY 1960

Managing Editor:

HUGH S. POCOCK, M.I.E.E.

Editor:

F. L. DEVEREUX, B.Sc.

Assistant Editors:

H. W. BARNARD

T. E. IVALL

VOLUME 66 NO. 2

PRICE: TWO SHILLINGS

FORTY-NINTH YEAR
OF PUBLICATION

Offices: Dorset House, Stamford Street, London, S.E.1

Please address to Editor, Advertisement Manager, or Publisher, as appropriate

PUBLISHED MONTHLY (4th Monday of preceding month) by ILIFFE & SONS LTD., Dorset House, Stamford Street, London, S.E.1. *Telephone:* Waterloo 3333 (65 lines). *Telegrams:* " Ethaworld, Sedist, London." *Annual Subscriptions. Home and Overseas,* £1 15s. 0d. *Canada and U.S.A.,* $5.00. Second-class mail privileges authorised at New York, N.Y. BRANCH OFFICES: *BIRMINGHAM:* King Edward House, New Street, 2. *Telephone:* Midland 7191. *COVENTRY:* 8-10, Corporation Street. *Telephone:* Coventry 25210. *GLASGOW:* 26B, Renfield Street, C.2. *Telephone:* Central 1265. *MANCHESTER:* 260, Deansgate, 3. *Telephone:* Blackfriars 4412. NEW YORK OFFICE: *U.S.A.:* 111, Broadway, 6. *Telephone:* Digby 9-1197.

FRAME GRID VALVES FOR TELEVISION

5

The PCC89 is a variable-mu double triode of frame grid construction, intended for use as a cascode amplifier at frequencies up to 220Mc/s. Its heater is designed for inclusion in a 300mA series heater chain. The valve may be used in tuners with the conventional PCF80 mixer valve or with the frame grid PCF86. In either arrangement it provides reduced noise and improved gain. As in the other valves in the new television series, the most obvious effect of introducing the frame grid is doubling of the slope. Thus the slope of each triode in the conventional PCC84 is 6·0mA/V, while under comparable conditions the PCC89 achieves 12mA/V.

IMPROVED GAIN

A tuner designed round the PCC89 and PCF80 can have a gain of about 52 to 56dB on the various channels, compared with a maximum of about 48dB in a tuner using the conventional PCC84 and PCF80. With the PCC89 and PCF86, the maximum gain is increased to about 60dB, and the noise factor of the tuner is reduced to about 6dB at 200Mc/s. This 'frame grid' tuner can be used in receivers designed for service area or fringe operation. The circuit differences between these two receivers would be in the i.f. amplifier stages.

PCC89

For optimum performance in a tuner the PCC89 must be operated under carefully chosen conditions. There must be sufficient power gain in the grounded cathode stage to overcome the noise of the grounded grid stage. There must also be sufficient a.g.c. voltage available to allow optimum signal handling and the required delay.

OPTIMUM CONDITIONS

Optimum noise factor is obtained with —0·8 to —1·2V bias on the first triode, which is best realised by using cathode bias. Optimum gain is obtained with rather less bias, which can be realised only under grid current bias conditions. This second mode of operation shows up to 2dB more gain on Band III than that obtainable with cathode bias, and just over 1dB on Band I, at the cost of a small increase in noise factor. However, the d.c. feedback effect of the cathode bias resistor is lost, and the spreads in gain will be a little greater with grid current bias. A tuner gain of 60dB (with PCC89 and PCF86) can be achieved on Band I with either system of biasing; but on Band III this figure is attainable only with grid current bias.

TAIL AND A.G.C.

The PCC89 has been given a variable-mu characteristic so that it can handle large signals without introducing perceptible cross-modulation. The valve can be operated with any tail length between —9V and —22V (which are the voltages for 1/100th slope reduction.)

Signal handling ability, limited by sound on vision or vice versa, can be better than 1·0V at the grid of triode 1 (250mV at the aerial) with long tail conditions and with cathode or grid current bias for triode 2. In fringe areas, with adverse sound to vision ratios, half this figure is realistic.

Many different operating conditions are possible for the PCC89. The choice is based on the gain-slope relationship which is required, the available a.g.c. voltage, and the i.f. arrangements to which the cascode has to be matched.

The high gain of frame grid tuners means that the designer should give special attention to the question of stability in both parts of the cascode circuit. Neutralisation of the anode-to-grid capacitances is advisable.

Mullard

MULLARD LIMITED

MULLARD HOUSE,
TORRINGTON PLACE,
LONDON, W.C.1

MVM 429

FEBRUARY 1960
Vol. 66 No. 2

Wireless World

Radio Horizons

WHEN Heinrich Hertz confirmed experimentally the mathematical predictions of Clerk Maxwell that electromagnetic waves could be generated and would be propagated with the speed of light he was too preoccupied with the physics of the phenomenon to give much thought to the possible application of cause and effect across the width of a room to the transmission and reception of messages over greater distances. It was left to others to develop the possibilities of this new knowledge and in particular to pioneers like Henry Jackson and Marconi whose vision and persistence were strong enough to break through the contemporary restrictions of inadequate techniques and official scepticism.

Once the first few yards had been extended to miles, the course of future development seemed clear. All that remained was to increase transmitter power and to improve receiver sensitivity. But before ranges had reached hundreds of miles the curvature of the earth's surface appeared as a possible limiting factor. It was once again the persistence of Marconi which cut through all pessimistic arguments and successfully sent a signal from Cornwall to Newfoundland in 1901. Yet another triumph of practice over precept was scored in 1920 by American and British amateurs in spanning the Atlantic on the "useless" short wavelengths of 200 metres or so; this several years before Appleton had established the existence and started to explore the exact nature of the ionosphere.

In the years since 1924 the ionosphere has been the subject of intensive study by means of continuous-wave and pulsed reflections from ground-based stations and the results form the basis of precise forecasting of optimum frequencies and paths of transmission for economical point-to-point radio communications over the whole surface of the globe. The work of the I.G.Y. has considerably extended this study, particularly near the magnetic poles, and the early results, reported elsewhere in this issue, show that the possibilities of conventional sounding techniques are by no means exhausted. But from the scientific point of view they have one serious limitation, namely, that while they give information of the underside of the laminated ionospheric "mirror" they cannot tell us anything about the backing. Signals of frequencies capable of penetrating the ionosphere are either lost in space or, if they are reflected from the moon or if signals originating from satellites are used, they can give only the total electron content of the intervening space. This has proved to be many times greater than the known numbers below the F layer, a fact which suggests a much further extension of the earth's atmosphere (or alternatively of the sun's atmosphere) than had hitherto been supposed. The whistling atmospherics investigated by L. R. O. Storey* led to the conclusion that atmospheric conduction extended to a height equivalent to at least two earth radii, and the recent discovery by van Allen and his colleagues of radiation belts at distances up to seven or eight earth radii now confirms the extent and complexity of the earth's immediate environment.

Although these discoveries may have little impact on day-to-day terrestrial radio communications they will be of great interest to radio astronomers, for it is through the window of the earth's atmosphere that they must receive their signals from the limits of the universe. A detailed knowledge of the structure of the window and of possible aberrations is vital. The bandwidths of the visual and radio "holes" in the transmission spectrum of the atmosphere are relatively narrow and the electromagnetic information which penetrates to the earth's surface is often blurred by scintillation. Optical observatories are sited on mountain tops to get as far as possible above thermal turbulence, and it has been suggested that future radio observatories working on frequencies above 30 kMc/s and below 1 Mc/s would have to be mounted on satellites and other space vehicles. It now seems likely that they will have to travel much further than was at first thought necessary in order to get a clear "view."

All this has some bearing too on the possibility of interplanetary communication with civilizations in other solar systems, a topic much discussed recently and the subject of a note on page 87 of this issue. Knowing the diversity of planetary atmospheres in our own solar system we must hope that the radio "windows" of other planets supporting intelligent life will coincide with or overlap our own at least to the extent of including the 21-cm hydrogen line.

That interplanetary communication between different solar systems can be now seriously considered is due in large measure to the novel methods of amplification such as masers and mavars† (parametric amplifiers) which do not depend primarily on electronic emission currents with their discrete and random noise generating properties. This is a landmark in receiving technique comparable with the change from wiring to "plumbing" and the transfer of energy in confined fields rather than as currents in conductors.

We have travelled a long way since Hertz, and the history of our progressive extension of the range of radio communication is punctuated by successive "break-throughs" in our knowledge, not only of the techniques of generating and receiving signals, but of the medium through which they are propagated.

* See *Wireless World* July 1953, p. 338.
† See *Wireless World* April 1959, p. 197, and May 1959, p. 242.

RADIO AND THE I.G.Y.

By *R. L. SMITH-ROSE,** *C.B.E., D.Sc., Ph.D., F.C.G.I., M.I.E.E.*

THE International Geophysical Year denotes the period 1st July, 1957, to 31st December, 1958, during which the scientists of some 66 nations worked at over 4,000 observatories throughout the world on a co-operative programme concerned with the physical properties of the earth and its atmosphere, and with the related solar and terrestrial phenomena. As described in an earlier article,[1] the I.G.Y. was the direct descendant of two earlier enterprises known as the First and Second International Polar Years which took place in 1882-83 and 1932-33 respectively. In the second of these, radio was used for the first time to study the characteristics of the ionosphere in Arctic regions; and as it happens, this took place during a period of minimum sunspot activity, whereas the I.G.Y. was conducted 25 years later during what turned out to be an epoch of the highest solar activity for the past 200 years.

In addition to a calendar of observation days drawn up in advance, provision was made during the progress of the I.G.Y. for the declaration of Special World Intervals when the state of the sun indicated the likelihood of a geophysical disturbance which might affect, for example, the ionosphere, and the earth's magnetic field. For this purpose an international network of radio and line communications was used to alert all participating observers and warn them that such a S.W.I. might, subject to confirmation, begin sixteen hours later. During the I.G.Y. 44 such alerts took place; of these, 22 culminated in a Special World Interval, during 17 of which, major solar and terrestrial disturbances occurred. In addition, there were 6 severe and 33 mild disturbances for which no previous warning or alert had been issued.

Provision was also made in advance for the setting up of a number of World Data Centres. The two main centres in U.S.A. and U.S.S.R. collect data relating to all disciplines in the programme; while in the radio field two additional centres in England and Japan were set up. The former is at the D.S.I.R. Radio Research Station at Slough, where, up to date, over a million sheets of ionospheric records and results, together with atmospheric noise and auroral data, have been received. It is likely that the mass of material brought together in this way will provide the basis of research in geophysics for many years to come, and in this brief review it is possible to refer to only one or two examples of the results which have already been achieved.

Physics of the Lower Atmosphere

The first International Polar Year, 1882-83, arose from the desire of meteorologists to know more about the physical characteristics of the atmosphere in the less accessible places. This applied particularly to the regions of the north and south poles, as it was considered that a knowledge of atmospheric conditions in these areas would lead to a better understanding of the factors which determine weather and the climate of the world. Today the network of meteorological observatories provides the basis of what is probably the most detailed international scientific organization throughout the world. Under the auspices of the World Meteorological Organization, with its comprehensive radio and line communications system, a very rapid reporting system has been developed which provides the most up-to-date weather and forecasting information for the needs of the whole world.

The primary aim of the meteorological programme for the I.G.Y. was to obtain a more nearly complete global picture of the mechanism of the general circulation in the atmosphere and its smaller-scale systems. To this end special stations were established in the polar regions, equatorial areas and on oceanic islands to supplement the observations made at permanent stations. Efforts were made at aerological stations to extend radio-sonde measurements to greater heights—to about 30 km where practicable—and to make more frequent soundings during the World Meteorological Intervals and on other World Days. Special mention should perhaps be made of the great expansion of observational facilities in the Antarctic. Some 50 stations made surface weather observations at least four times each day: added to this there were twice-daily upper-air soundings at 16 stations to an average height of about 20 km. For the first time in history it has now been possible to construct charts showing broad circulation patterns at various atmospheric levels above the Antarctic.

Thunderstorms and Atmospheric Radio Noise.—For many years past, the meteorologist has used a network of radio direction-finding stations to locate the existence and movement of thunderstorms which make themselves evident by the emission of radio waves from lightning flashes. Having provided this kind of tool to the meteorologist, the radio scientist is further interested in obtaining measurements of the intensity and structure of the waves comprising atmospherics, which can so disturb radio reception in various parts of the world. As a result of past work involving international co-operation, tentative charts[2] have been produced indicating the order of magnitude, and probable frequency of occurrence, of the atmospheric radio noise likely to be encountered at different seasons throughout the world.

The main objective of the I.G.Y. noise programme has been the establishment of a network of stations for the measurement of a specific characteristic of the atmospheric noise received from lightning flashes. The characteristic chosen was the received noise power, averaged over a period of about an hour. The measurement of various parameters, including the noise power which is related to the r.m.s field strength, was made at 13 stations during the I.G.Y. At a few of these the observations were made by

* Director of Radio Research, Department of Scientific and Industrial Research.

both manual and automatic recording methods, and some apparent discrepancies between the two sets of results are under investigation. A third method, which has been in use for many years at 15 stations in different parts of the world, was continued during the I.G.Y. In this, the strength of a locally generated signal is determined which is just sufficient to be intelligible through the noise.

Other I.G.Y. projects were designed to study the nature of the noise as it is radiated by the source—the lightning flashes—and the manner in which it is modified as it is propagated through the atmosphere. Records of the noise near to the source have been made, at several frequencies, on magnetic tape, and are being analysed to determine their energy, and other characteristics. Fig. 1 shows a record of atmospherics recorded at the D.S.I.R. Radio Research Station, Slough, on two frequencies, from a flash which struck the ground half a mile away. The upper record shows characteristic large impulses at 6 kc/s, from the ground strokes, and the more complex nature of the records at 11 Mc/s. Reproduction of the records at higher gain shown below, reveals that the atmospherics are more complex than first appeared even at 6 kc/s. Many of the features of these records cannot be readily explained on present theories of the lightning discharge.

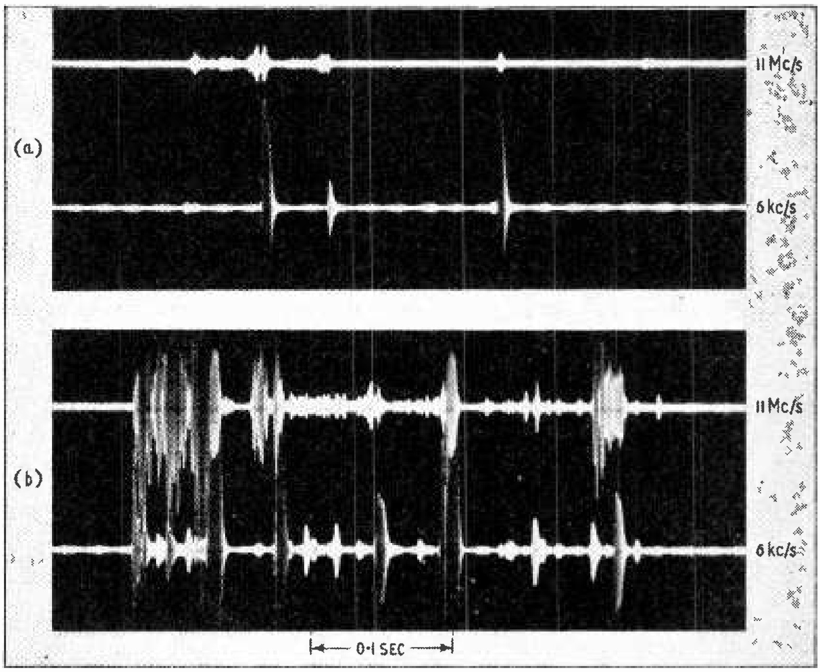

Fig. 1. Waveform of atmospherics from a very near lightning flash. Peak amplitudes 1.4mV/m at 11 Mc/s, 3.5 V/m at 6kc/s

As an example of the studies of the effects of propagation, low-frequency atmospherics from the same lightning flash were recorded at several stations in Europe; and comparisons are now in progress to examine how their form changes with the distance, and possibly with the direction of propagation.

Study of the Ionosphere

The exploration of the ionosphere by vertical soundings using pulse techniques was established on a regular basis in the U.K. and U.S.A. over 25 years ago. Only two or three stations were working during the second International Polar Year, but some 80 were in regular operation before the I.G.Y. began, and about twice this number were established during the I.G.Y. The work of these stations has produced over one million tables of measurements and photographic records which refer to the period of the I.G.Y. The study and assimilation of this vast accumulation of data will take many years; but to illustrate how some of these data have already been used, two examples may be referred to here. One of these deals with small quantities of data which have been examined in great detail and very accurately: the other is concerned with the approximate statistical treatment of a large amount of data referring to specific ionospheric characteristics.

Distribution of Ionization and M.U.Fs.—The calculation of maximum usable frequencies (M.U.F.) for radio communication circuits is based on the assumption that the electron density in the F2 layer increases with height according to a parabolic law. The refractive properties of a non-parabolic layer might be expected to lead to maximum usable frequencies above or below those at present in use. Now it is arduous to derive the actual distribution of electron density from the observational records by manual methods. During the I.G.Y., first in the United Kingdom and later in other countries, digital computers have been programmed to calculate these distributions of electron density with height on a routine basis. These distributions are termed N(h) profiles, and they are often found in practice to be far from parabolic in form[3]. By tracing the ray-paths through ionized layers conforming with the measured profiles, it has been shown that, although the actual M.U.F. factors do not differ by an appreciable amount from those calculated assuming a single parabolic F2 layer, the angle of arrival of the waves for a given distance between the transmitter and receiver tends to be greater than that for a parabolic layer of the type usually assumed. Thus the practical conclusions reached are that while the maximum usable frequencies now in use are not seriously affected by the shape of the layer, it may be desirable to use aerial systems which project the radiation at a greater angle of elevation than has hitherto been considered the most appropriate.

Solar-Cycle Changes in f_oF2.—In the previous example, the whole of the observational data for about ten ionograms have been studied in very great detail. The next example deals with the critical frequency of the F2 region using data obtained from many thousands of ionograms from all parts of the world.

During the I.G.Y., solar activity was considerably higher than it has been since regular visual observations of the number and magnitude of sunspots were begun about 200 years ago. As a consequence, the ionization and hence the critical frequencies of the ionospheric layers have reached unprecedented high levels as illustrated in Fig. 2 which shows the critical frequencies observed at the Radio Research Station, Slough, during the past 27 years. This new information on ionospheric behaviour at very high solar activity is unique and is unlikely to be repeated for many years to come. This is important because it adds a great deal to earlier knowledge on the relations between solar activity and critical frequencies, an understanding of which is essential to the accurate forecasting of M.U.Fs for communications.

Drifts.—The normal methods of sounding the ionosphere pay no attention to the fact that the reflecting layers are not at rest, but appear to be moving with horizontal velocities which vary with the height of reflexion. Special techniques are required for the measurement of these velocities and these have only been developed in the last decade to a stage where they can be used with some confidence. Although only 20 to 30 observatories undertook measurements of ionospheric drifts during the I.G.Y., the information already available has given results which tend to fall in to a consistent pattern.

The drifts of ionization follow a diurnal variation; for example, at Ibadan in Nigeria, the prevailing directions are to the west by day and to the east by night at all seasons. It was also found that on magnetically disturbed days the drifts are less pronounced than on the quiet days. At the more temperate latitude of Cambridge, there is also a marked north-south component in the drift velocity. This has been found to have a long term variation related to the solar cycle; at the period of maximum activity the drift was towards the equator, whereas at the epoch of minimum activity the direction was reversed. It is likely also that the vertical movement was subject to similar changes in direction.

It is becoming increasingly evident that in some parts of the world the vertical and horizontal movements of clouds of ionization play an important part in determining the characteristics of the ionosphere, which are not simply related in time to the locally incident radiation from the sun.

Ionospheric Investigation in the Antarctic

The I.G.Y. provided the impetus for a scientific survey of Antarctic and Arctic ionospheric conditions on a scale which had not previously been attempted. In the Antarctic, British ionospheric stations were operated by the Royal Society, at Halley Bay in the Weddell Sea, and by the Falkland Islands Dependencies Survey, at Port Lockroy in Grahamland. Other stations were operated by France, U.S.S.R., and other countries, including one at the South Pole where the U.S.A. had a large base.

The Jodrell Bank radio astronomy observatory made a continuous survey of auroral and meteor activity in co-operation with Halley Bay throughout the I.G.Y. Preliminary results have already shown that radio echo auroral activity at Jodrell Bank corresponds to the peaks in activity at Halley Bay. The incidence of meteors was observed by the range of reflection of radio echoes produced by the trails

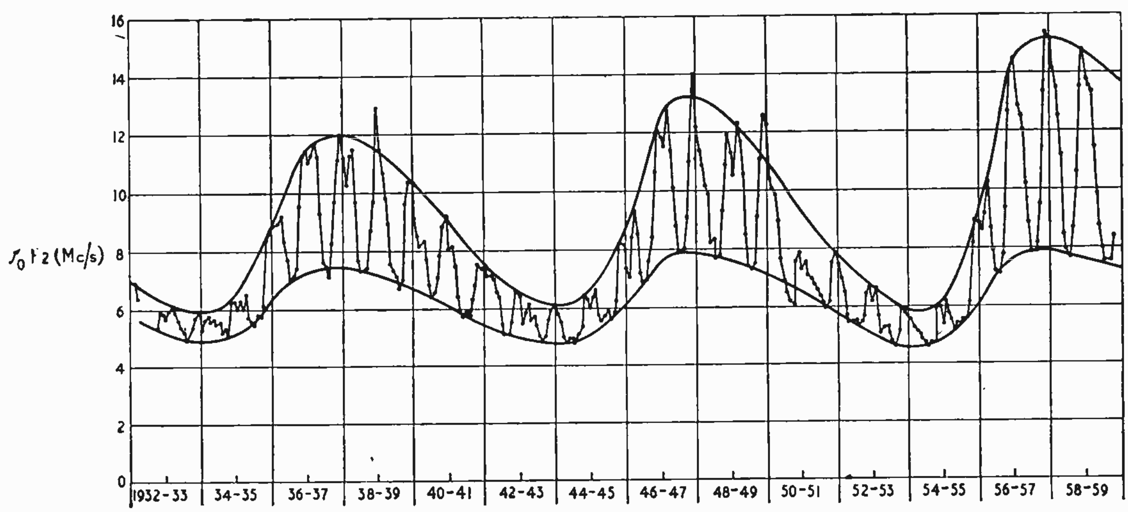

Fig. 2. Measured noon values of f_oF2 at Slough, 1932-1959

of ionization left behind the meteors as they burnt up in the atmosphere. Drifts of ionization were measured at heights of 85 to 105 km; the resulting pattern of these drifts or "winds" in the ionosphere was found to be very regular, unlike the winds at the surface of the earth. The speeds of these ionospheric drifts are about 100 miles per hour[4], and their directional vector rotates clockwise twice each day. They are towards the north at 6.0 a.m., to the east at 9.0 a.m., south at noon, west at 3.0 p.m., and so to the north again at 6.0 p.m. local time. This regular behaviour is due to tidal and heating effects of the sun in the upper atmosphere, which cause the atmosphere to expand and contract twice per solar day in the same way that the moon causes the seas to rise and fall twice each lunar day.

Ionospheric observations made at high latitudes have a special significance; and the complicated behaviour of the F layer in the Antarctic may be clarified considerably by attempting to separate those phenomena due to electrons produced by the sun's radiation on the upper atmosphere from those due to horizontal or vertical movements of electrons from other locations.

Movements of ionospheric layers are almost entirely generated by electrical forces interacting with the earth's permanent magnetic field; and the velocity of the movement therefore depends on the direction of this field, and, in particular, on the angle of dip. The interpretation of detailed studies of a layer thus depends on the magnetic dip in the ionosphere above the sounding station. There is a unique dip anomaly in the Weddell Sea area due to the asymmetry of the magnetic field in relation to the centre of the earth. This anomaly is so great that the dip angle at the Royal Society Base at Halley Bay, 75° S, is the same as that at Canberra, 35° S, or at similar latitudes in Florida in the northern hemisphere. As a result the interpretations of ionospheric phenomena are relatively simple for such a high latitude where the rate of photo-ionization in the F layer near midwinter is zero. For the same reason, it varies only slightly through the day near midsummer. Thus any changes in ionization generated by movements in the layer are more easily seen and interpreted than in locations where photo-ionization may be changing rapidly during the day.

The diurnal variation of the F2 layer critical frequency at Halley Bay in midwinter is shown by the curves linking the circles in Fig. 3, which also shows the corresponding midsummer curve marked by crosses. It is to be noted that, despite the absence of any photo-ionizing radiation from the sun in midwinter, the noon critical frequency exceeds that found in midsummer, when the sun never sets[5]. Clearly the behaviour of the layer must be almost entirely determined by movements of ionization and not by direct solar influences. The curves also show that the critical frequency of the F layer is over three times as high at noon as at midnight in midwinter; this corresponds to an increase of about ten times in the ionization density.

The changes in shape of the layer show that the total electron content below the maximum is also much increased at noon. Detailed studies of the ionograms confirm that these changes are mainly due to horizontal movements of ionization; a new layer moving in and replacing the old during a period of about eight hours. This is the cause of the discontinuity in the curve; for several hours there

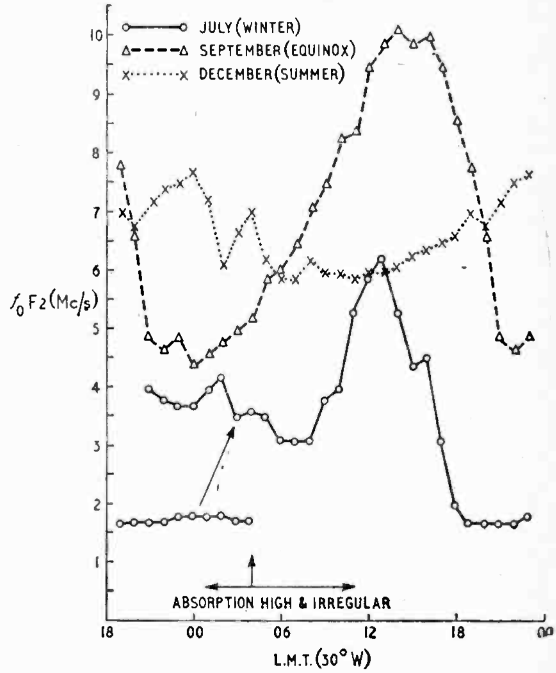

Fig. 3. Monthly median values of f_0F2 at Halley Bay

are simultaneous reflections from a regular layer which is already overhead and from a second, much denser layer which gradually moves into an overhead position.

The differences between the summer and winter diurnal variations at Halley Bay illustrate a world-wide phenomenon, namely that the phases of the diurnal components of velocity reverse with season. This is responsible for most of the seasonal variations found in practice. Considerable further work will be needed before the regularities discovered during the I.G.Y. can be used as the basis for a theory of the F layer, since the density and shape of this layer in any part of the world depend on the difference between the amount of ionization moved into a zone and that moved out of it. Very small changes in these components can cause enormous differences in the shape of the resultant layer. Nevertheless, the data from the high-latitude stations during the I.G.Y. provide a firm and useful starting point for fuller investigations.

Use of Rockets and Satellites

During the past decade rockets have been used for research purposes to investigate the phenomena and characteristics of the upper atmosphere by direct measurement in a manner which ground-based experiments are unable to provide. Following this work, it was recommended that during the I.G.Y. observations with rockets should be supplemented by means of artificial earth satellites carrying instruments for the measurement of solar radiation—ultra violet, X and cosmic rays—and its effect on the ionosphere. This recommendation culminated in the successful launching on 4th October and 3rd November, 1957, respectively, by the U.S.S.R., of the instrumented earth satellites known scientifically as 1957α and β, or more popularly as Sput-

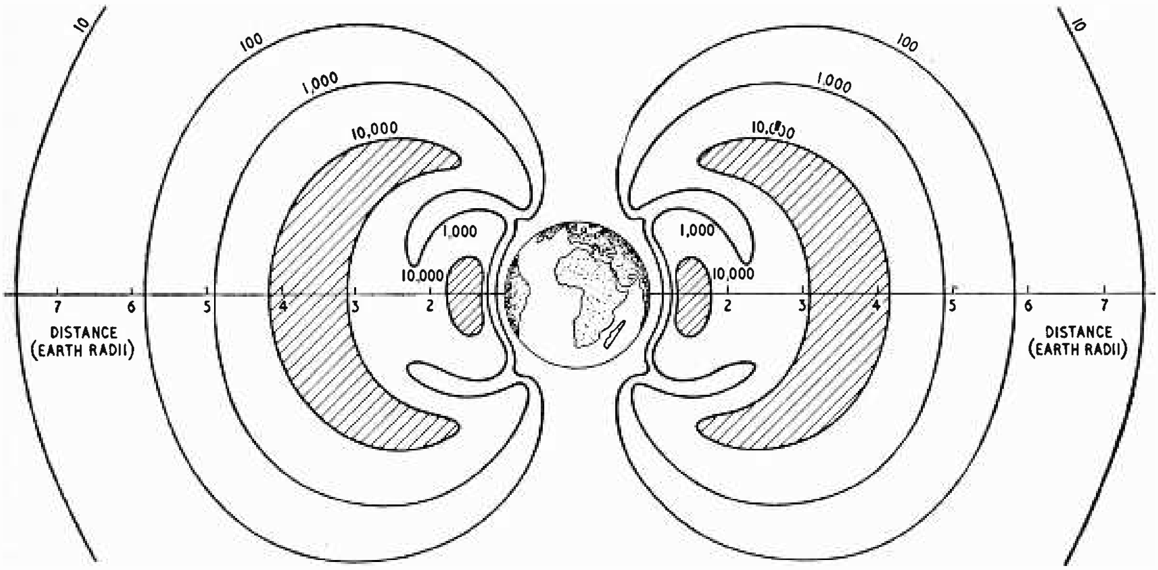

Fig. 4. Structure of radiation belts around the earth (J. A. van Allen). The figures shown indicate the particle density in counts per second.

niks I and II. This was followed on 31st January, 1958 by the U.S.A. satellite 1958α—Explorer I; and others have followed at intervals during the past two years. At the present time, there are about a dozen satellites in orbit round the earth, while two others are pursuing courses round the sun and moon.

These space vehicles contain instruments for the measurement of the properties of the atmosphere, the electron density of the ionosphere and the intensity of cosmic and solar radiation in outer space. The output of these instruments is in electrical form and is either transmitted directly by radio[6] to the ground observing stations, or is recorded on magnetic tape and sent later on receipt of a command signal from a radio station on the earth. Some of the telemetry systems are relatively simple, providing information in only a few channels; others are more complex and use up to 48 channels. For example, the system used on the 20 Mc/s transmissions from Sputnik III (1958δ) contains three channels, one to indicate whether solar or chemical batteries are in use, and two to record cosmic-ray data. A pulse width system of modulation is used, the information being given by the time interval between successive changes of the pulse width from one discrete value to the next. The American satellites have transmitted the information on a frequency of 108 Mc/s supplemented more recently with higher frequencies. In one of the systems used, the modulation consists of 16 bursts of tone, the information being carried by the tone frequency (5 to 12 kc/s), the duration of the bursts and the interval between them, giving 48 channels in all. The power of transmitters in continuous operation varies from 10 to 100 mW, while for intermittent operation on command, a few watts have been used.

Apart from the need to extract the observational information from the satellite, radio transmission is used to track it and to supplement the positional information which may be obtained visually under favourable clear sky conditions. Radio interferometers and tracking equipment have been installed in a number of countries to give round-the-world coverage by international co-operation. Additional information provided by the radio signals includes a determination of successive orbit periods, from a knowledge of which information is obtained as to the shape of the earth, variations of gravity at different altitudes and the drag of the rare atmosphere at the orbit levels. Moreover, measurements of the total electron density between the earth and the satellite have been made by comparing the speed of the received waves at a frequency just above the critical frequency of the ionosphere, and at a much higher frequency. The difference in speed at these two frequencies depends upon the total number of free electrons along the path; so the distribution of this number with height can be determined from a continuous record of the difference between the two received frequencies. Both the U.S.A. and U.S.S.R. results have shown no clearly defined minimum in the electron density between the E and F layers; and in the U.S.S.R. results there has been a negligible decrease from the maximum of the F layer up to a height of about 470 km. British experiments with Skylark rockets used a different technique, the change in conductivity and dielectric constant of the ionized air being used to change the frequency of an oscillator. This system has a very rapid response and is capable of showing the fine structure of the ionosphere. In view of the fact that radio methods of sounding the ionosphere from the earth's surface are limited to the lower portion up to the maximum of the F layer, and that it is estimated that there is at least as much more ionization above this layer, the satellite clearly provides a very powerful tool for future ionospheric research.

While research on cosmic rays at high altitudes was in progress before the I.G.Y. by means of balloons and rockets, the scope of the work has been considerably extended by the use of satellites carrying instruments for measuring the intensity and the energy distribution of the radiation. Observations made by U.S. Explorers I and III showed a steady increase in intensity with increase of both altitude and geomagnetic latitude. Similar trends were shown by observations made with the U.S.S.R. Sputniks II and III. The American observers also noted a very rapid increase in intensity at a height of about 1,000 km; and further observations with Explorer IV have confirmed the existence of regions of intense radiation extending partly round the earth. The release of information on the coding of the telemetry signals used in both U.S.A. and U.S.S.R. satellites has enabled confirmatory observations to be made at Slough on Sputnik III in transit over this country, and on Explorer I in Japan.

The discovery by van Allen[7] and his colleagues of the high-intensity radiation belts which surround the earth is one of the outstanding results of the I.G.Y. Later observations made with Explorer IV and Pioneer III have indicated the existence of two belts[8] of high-intensity radiation around the geomagnetic equator, the first at a height of about 10,000 km and the second at about 22,000 km, as illustrated in Fig. 4. These belts consist of charged particles, the density of which, measured by the rates recorded on a Geiger counter, varies over a range of 10,000 to 1 under different conditions. Much speculation has taken place as to the origin of the radiation, but it is thought that the charged particles are trapped in the earth's magnetic field. On this hypothesis, the particles, travelling towards the earth, are subject to a force at right angles to both their initial motion and the magnetic field, causing them to pursue a spiral path. As they approach the earth, the increasing strength of the field results in a steadily increasing transverse velocity and the particles move in a closer and closer spiral. This is the result of the gradual translation of the initial energy of the particles from that of forward motion along the path into transverse rotational form. At a point in the earth's outer atmosphere where the magnetic field is sufficiently intense, the motion of the particles along the lines of force is reduced to zero (see Fig. 5). This, however, is virtually an unstable condition, from which the particles can be displaced by collision with other particles or molecules. Since they cannot advance further towards the earth, the streams of particles start to retrace their spiral path along the lines of magnetic force to the conjugate point of the earth's field, where the process is repeated. Thus, although there may be some leakage of particles in the course of their travel, the incoming streams of particles may be regarded as virtually trapped in the earth's magnetic field, and as travelling in spiral paths about the lines of force and being subject to reflection between the conjugate points of the field near the earth's surface. As the earth rotates these spiral paths may be regarded as revolving in a direction depending on the sign of the charged particles, so that toroidal belts of high intensity will be formed around the earth as indicated in Fig. 5. Further research and observations are required to establish the properties and structure of these radiation belts, but the knowledge of their existence must be taken into account in future investigations of the space beyond the earth's atmosphere.

In concluding this section, attention may be drawn to the fact that radio signals from the American satellite Pioneer IV (1959 δ) sent in orbit round the sun on 3rd March 1959 were received out to a distance of 400,000 miles[9]. This has established a record for direct radio communication with man-made sending and receiving equipment. Furthermore, the Russian satellite, Lunik III, which made a circuit of the moon towards the end of October, established a distance record for photographing the far side of the moon from a distance of the order of 300,000 miles, and transmitting the pictures back to earth by radio technique.

Although it was not strictly part of the I.G.Y. programme, reference may be made to the Argus experiment conducted by the U.S. authorities in August and September, 1958, when three small nuclear devices were detonated at an altitude of about 480 km (300 miles) in the South Atlantic. One of the I.G.Y. satellites, Explorer IV (1958 ε), contained instruments designed to measure the natural radiation in the van Allen belts. On 27th August a large increase in the intensity of the radiation was recorded by the satellite as it passed through the locality of the explosion some 3½ hours later. Similar, though smaller, effects were observed after the second explosion four days later, together with residual effects from the first event. Although observations were made on very low frequency radio propagation and on the atmospheric noise level, no definite results were recorded.

Conclusion

In concluding this very brief review of the manner in which the I.G.Y. was associated with radio, two points must be emphasized. First, that the successful exploration of our atmosphere and the outer space beyond depends to an increasing extent on the technique of electronics and radio communications. Secondly, it is clear that the international exercise which was designated the I.G.Y. did not end on 31st December, 1958. The following year was termed

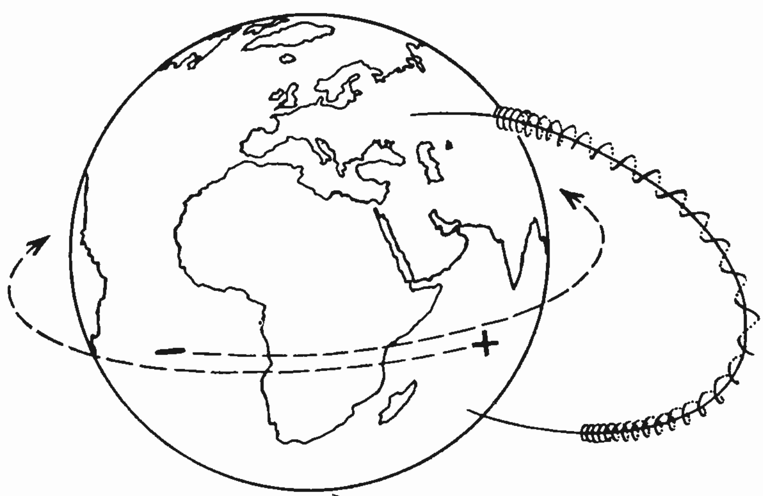

Fig. 5. Diagram showing spiral path of charged particles trapped along magnetic lines of force

International Geophysical Co-operation—1959; and it has also been recommended that as far as practicable the various observatories should continue to work in their respective disciplines to extend our knowledge of the earth and its surroundings. It has further been recommended that the World Data Centres established for the I.G.Y. and extended for the results obtained with rockets and satellites, should be continued indefinitely as international repositories of the observational information which is to be freely available for research workers in the future.

REFERENCES

[1] R. L. Smith-Rose "Geophysical Research" *Wireless World*, April, 1955, Vol. 61, pp. 188-190.

[2] "Revision of Atmospheric Radio Noise Data" *C.C.I.R. Documents of the VIIIth Plenary Assembly*: Warsaw 1956, Vol. 1, pp. 324-358.

[3] J. O. Thomas and M. D. Vickers "The Conversion of Ionospheric Virtual Height-Frequency Curves to Electron Density-Height Profiles" D.S.I.R. Radio Research Special Report No. 28, H.M. Stationery Office, London.

[4] J. S. Greenhow and E. L. Neufeld "Measurements of Turbulence in the Upper Atmosphere" *Proc. Phys. Soc.*, 1959, Vol. 74, pp. 1-10.

[5] W. R. Piggott and W. H. Bellchambers "Ionospheric Measurements made at Halley Bay" *Nature*, Vol. 182, pp. 1596-1597, Dec. 6, 1958.

[6] J. A. Ratcliffe "Information by Radio from the Satellites" *Journal I.E.E.*, 1958, Vol. 4, pp. 603-8.

[7] J. A. van Allen and L. A. Frank "Radiation around the Earth to a Radial Distance of 107,400 km" *Nature*, February 14, 1959, Vol. 183, pp. 430-434.

[8] J. A. van Allen, Carl E. McIlwain and G. H. Ludwig "Radiation Observations with Satellite 1958" *Journal of Geophysical Research*, 1959, Vol. 64, pp. 271-286.

[9] J. A. van Allen and L. A. Frank "Radiation Measurements to 658,300 km with Pioneer IV" *Nature*, July 25, 1959, Vol. 184, pp. 219-225.

NEW BOOKS

High Fidelity Sound Reproduction. A collection, edited by E. Molloy, of essays by leading authorities on subjective and objective judgment of performance, acoustics of sound reproduction, multiple-channel systems, amplifiers, moving-coil and electrostatic loudspeakers, disc and tape records and radio reception. Pp. 208; Figs. 155. Price 20s. George Newnes Ltd., Tower House, Southampton Street, London, W.C.2.

Topics in Electromagnetic Theory by Dean A. Watkins. Unified treatment of aspects of field theory having a direct bearing on the design of microwave valves and allied devices. Sections include periodic transmission systems, the helix, coupled-mode theory and anisotropic media (ferrites). Pp. 118; Figs. 185. Price 52s. Chapman & Hall, 37 Essex Street, London, W.C.2.

The Calculation of the Median Sky Wave Field Strength in Tropical Regions by W. R. Piggott, O.B.E., B.Sc. D.S.I.R. Radio Research Special Report No. 27 on the principles and method of predicting the field strength of h.f. broadcast transmissions at low latitudes. Pp. 37; Figs. 28. Price 2s 6d. H.M. Stationery Office, York House, Kingsway, London, W.C.2.

Modern Electronic Components by G. W. A. Dummer, M.B.E., M.I.E.E., S.M.I.R.E. Comprehensive and concise survey of components with chapters on panclimatic testing, specifications laid down by Industry and the Services and an extensive bibliography. Pp. 472; Figs. 225. Price 55s. Sir Isaac Pitman & Sons Ltd., Parker Street, London, W.C.2.

Principles of Frequency Modulation by B. S. Camies. A comprehensive account of the theory of f.m. broadcast transmission and reception, interference rejection, methods of detection and the applications of f.m. in radar and communications systems, including facsimile. Pp. 147; Figs. 78. Price 21s. Iliffe & Sons Ltd., Dorset House, Stamford Street, London, S.E.1.

General Circuit Theory by Gordon Newstead. Compact account of the mathematical tools used in the analysis of complex circuits. Circuit elements, general network theorems, four-terminal network in the steady and transient states and some extensions of linear circuit theory to non-linear elements. Pp. 144; Figs. 20. Price 15s. Methuen & Co. Ltd., 36 Essex Street, London, W.C.2.

Fundamentals of Transistors by Leonard M. Krugman. Second (Revised) edition now includes references to surface barrier, intrinsic, drift, avalanche and spacistor types; and illustrative circuits in the amplifier, oscillator and h.f. application sections have been brought up to date. Pp. 168; Figs. 120. Price 25s. Chapman & Hall, 37 Essex Street, London, W.C.2.

Théorie et Practique des Circuits de l'Electronique et des Amplificateurs. Tome I: Applications du calcul des imaginaires à l'étude des circuits. By J. Quinet. Comprehensive treatise on the use of complex algebra and circuit theorems in the analysis of radio and electronic circuits. Pp. 256; Figs. 160. Price, 1960F. Dunon-Editeur, 92 rue Bonaparte, Paris 6 ème.

Radio Studies of the Universe by R. D. Davies and H. P. Palmer. Broad survey against the background of optical astronomy of the methods and results of radio astronomy, by two members of the staff of Jodrell Bank observatory. Pp. 200; Figs. 50 and 14 plates. Price 25s. Routledge & Kegan Paul Ltd., 68-74 Carter Lane, London, E.C.4.

Bringing the Aerial Down to Earth by R. S. Roberts, M.Brit.I.R.E., S.M.I.R.E. Simple exposition of the technical background of television aerials and their installation. Pp. 33. Available from Wolsey Electronics Ltd., Cray Avenue, St. Mary Cray, Orpington, Kent.

My Story of the B.B.C. by Freddy Grisewood. A first-hand account of the B.B.C. from the inside from 1929 to the present day; primarily from the programme point of view but with much interesting technical information. Pp. 224; 29 illustrations. Price 21s. Odhams Press Ltd., 96 Long Acre, London, W.C.2.

Rapid Radio Repair by G. Warren Heath. Illustrated guide to bench techniques in locating and remedying faults in sound broadcast receivers. Subject matter arranged alphabetically for quick reference. Pp. 224; Figs. 81. Price $2.90. Gernsback Library Inc., 154 West 14th Street, New York, 11.

Abbreviations of Associations, Institutions, Research and Trade Associations. B.E.A.M.A. Publication No. 159 with more than 400 entries giving the titles and addresses of organizations in the electrical and allied fields. Pp. 16. Price 1s 6d. The British Electrical and Allied Manufacturers' Association, 36 Kingsway, London, W.C.2.

Principles of Electronics by M. R. Gavin, M.B.E., D.Sc., F.Inst., M.I.E.E., and J. E. Houldin, B.Eng., Ph.D., A.M.I.E.E. Book of first principles designed to provide the common background for physicists and electrical engineers prior to specialization in any of the many branches of electronics. A collection of 250 examples based on typical examination questions is given. Pp. 348; Figs. 309. Price 30s. The English Universities Press Ltd., 102 Newgate Street, London, E.C.1.

Signal-Flow Diagrams

I.—Graphical Aids to the Solution of Complicated Circuits

By THOMAS RODDAM

A SIGNAL-FLOW diagram is a topological model of a system of linear simultaneous equations. In less dignified language, like what you expects of the likes of me, it is a map of what goes on inside a circuit and, like all good maps, it gives you a chance of finding a short-cut or two. The signal-flow diagram is starting to become fashionable in America, where it was first described six years ago by S. J. Mason in *Proc. I.R.E.* for Sept. 1953 (p. 1144), so that in any event you need to know something about it. This article is an attempt to explain what signal-flow diagrams are and how you use them without actually being blinded by science. It does not quite follow the line taken by R. F. Hoskins in *Electronic and Radio Engineer* (August 1959, p. 298) for a reason I shall make clear when I get to it.

We must start off with some rather dreary-looking G.C.E. or O.N.C. algebra before getting to a practical circuit. Bear with me, because it is necessary to get this first step clear: after all you would never have learned French if you had let your aunt's gardener keep that pen. Suppose we have a system with three points, which could be anode, cathode and grid of a valve, and we associate a variable, which could be voltage, with each. The variables are x_0, x_1, x_2 and by ordinary circuit methods we find that:

$$a_0x_0 + a_1x_1 + a_2x_2 = 0$$
$$b_0x_0 + b_1x_1 + b_2x_2 = 0$$

where the a's and b's are constants.

These equations can be solved by ordinary algebra, or by using determinants. We could write

$$x_0 = -\frac{a_1}{a_0}x_1 - \frac{a_2}{a_0}x_2$$

which Hoskins virtually does, but there is a risk in starting off like this because you then need to apply special tests for stability if $a_0 = 0$. It seems a pity to be forced to choose between doing this and manoeuvring round the concealed infinities which may be scattered through the algebra. Another method seems indicated and it is found by writing

$$\left.\begin{aligned} x_1 &= a_0x_0 + (a_1+1)x_1 + a_2x_2 \quad .. \\ x_2 &= b_0x_0 + b_1x_1 + (b_2+1)x_2 \quad .. \end{aligned}\right\} \quad (1)$$

Now let us construct the signal-flow diagram, starting from x_0, the input signal. Operating in easy stages, Fig. 1(a) shows the three points, x_0, x_1, x_2. Notice that the points on the signal-flow diagram have the same names as the variables, because this is essentially a map of the signals. Looking at the first equation of (1) we see that we reach x_1 by taking a_0x_0 so in Fig. 1(b) we draw a line from x_0 to x_1, put an arrow on it to indicate "to x_1" and write a_0 alongside the arrow; we add the line a_2x_2 from x_2 and the "round-the-houses" line $(a_1+1)x_1$ from x_1 to x_1. From x_0 to x_2 involves the same sort of operations and is shown in Fig. 1(c). Since the equations are simultaneous the two partial maps must be put together and they then form Fig. 1(d).

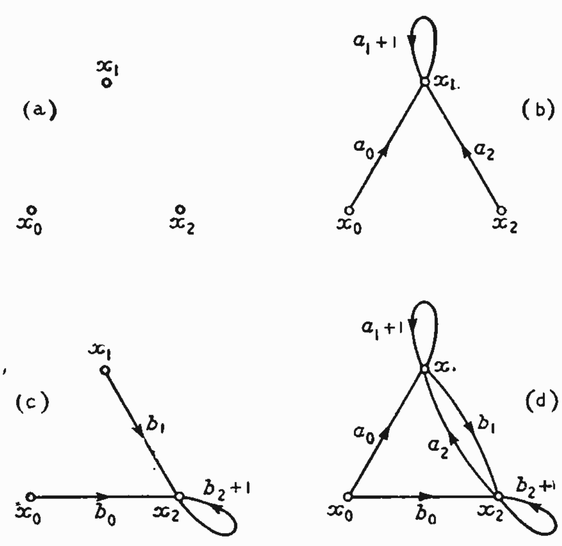

Fig. 1. Construction of the signal flow diagram of the two equations (1) in the text.

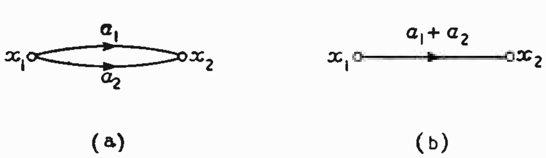

Fig. 2. Simplification of a signal-flow diagram with parallel branches.

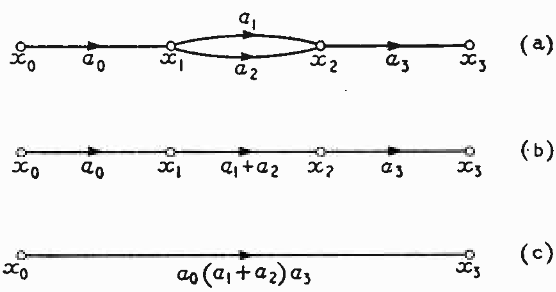

Fig. 3. Simplification with series and parallel branches.

We can now use this map to study the way in which maps of this kind can be simplified. Suppose we look at Fig. 2(a). The signal entering x_2 is provided by two branches and gives us

$$x_2 = a_1x_1 + a_2x_1 = (a_1 + a_2)x_1$$

so that we can reduce this little map to the even

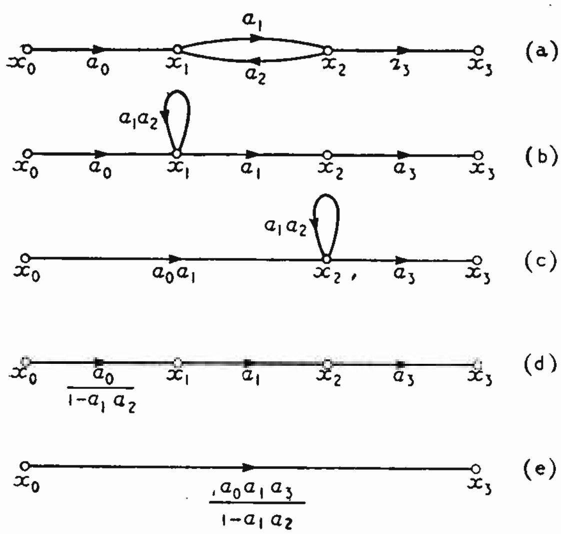

Fig. 4. Simplification with a reversed loop does not just mean writing a minus sign.

simpler form shown in Fig. 2(b). This same simplification has been carried out to get from Fig. 3(a) to Fig. 3(b), from which we see that

$$x_1 = a_0x_0$$
$$x_2 = (a_1 + a_2)x_1$$
$$x_3 = a_3x_2$$

so that $\quad x_3 = a_3(a_1 + a_2)a_0x_0$

which has the map shown in Fig. 3(c).

The diagram shown in Fig. 4(a) is deceptively like the one shown in Fig. 3(a) and it is very tempting to write $-a_2$ in place of a_2 and twist the arrow round. This is quite fatal. You just mustn't drive backwards down a one-way street. Signal-flow, like traffic flow, has its own rules and it is no good trying to use the rules you learnt for something else. Let us see what Fig. 4(a) means. We have

$$x_1 = a_0x_0 + a_2x_2$$
$$x_2 = a_1x_1$$
$$x_3 = a_3x_2$$

so that substituting in the first equation

$$x_1 = a_0x_0 + a_1a_2x_1$$
$$x_1(1 - a_1a_2) = a_0x_0$$
$$x_2 = a_1x_1$$
$$x_3 = a_3x_2$$

The first of the equations for x_1, taken with the last two, gives us the diagram shown in Fig. 4(b). This has a self-loop at x_1. We could have made the substitution in the second equation, giving

$$x_2 = a_0a_1x_0 + a_1a_2x_2$$
$$x_3 = a_3x_2$$

which gets rid of x_1 altogether and produces the diagram shown in Fig. 4(c). Alternatively we could go on from the form

$$x_1 = a_0x_0/(1 - a_1a_2)$$
$$x_2 = a_1x_1$$
$$x_3 = a_3x_2$$

to get Fig. 4(d), which contains no self-loop. You see how the self-loop a_1a_2 at x_1 reacts on the a_0 term entering x_1 from x_0 to give $a_0/(1 - a_1a_2)$. This agrees with the idea of a self-loop, or indeed a reversed loop like the one we began with, as a feed-back loop. The last step in the reduction is shown in Fig. 4(e).

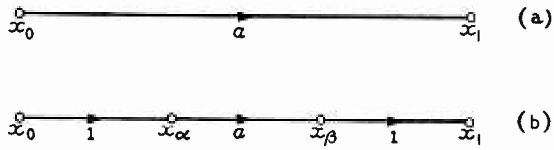

Fig. 5. Introducing test points in a signal-flow diagram.

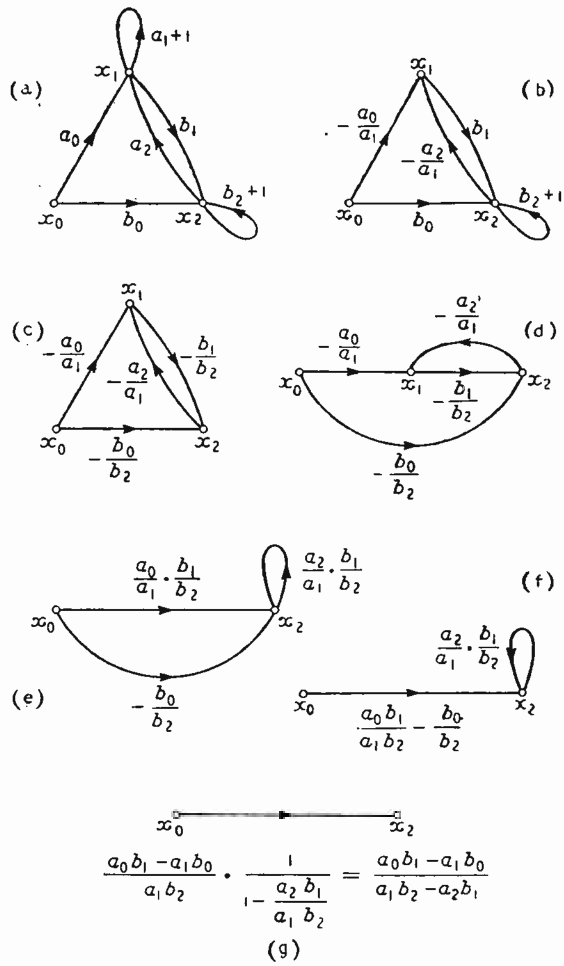

Fig. 6. The step-by-step reduction of (a) (Fig. 1(d)) representing the equations (1) leads to the solution (g).

Before we go back to try and simplify Fig. 1(d) we might notice a trick which is convenient in avoiding confusion. We can do the reduction of Fig. 3(b) to Fig. 3(c) in reverse in the way shown in Fig. 5. Here I have put in a couple of test-points x_α and x_β without altering the overall flow from x_0 to x_1.

Back, then, to Fig. 1(d). If we look first at x_1 we see that we have a self-loop and two entering signals: the figure is redrawn as Fig. 6(a) and the self-loop has been eliminated in Fig. 6(b) by dividing both entering signals by $1 - (a_1 + 1) = -a_1$. In Fig. 6(c) the second loop has been eliminated and this figure is then redrawn as Fig. 6(d). To get this even

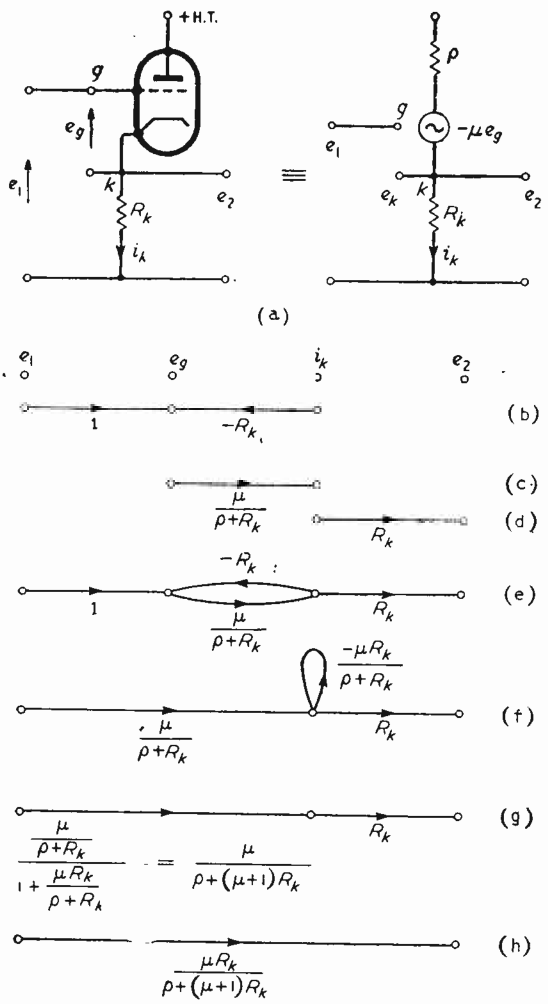

Fig. 7. Circuit of a cathode follower and the construction and reduction of its signal-flow diagram.

simpler we collapse the top-half of the map as in Fig. 4(c) to give Fig. 6(e). The two branches from x_0 to x_2 are then run together in Fig. 6(f) and in Fig. 6(g) the self-loop at x_2 is eliminated by the method we have already described. The answer we have reached is

$$x_2 = \frac{a_0b_1 - a_1b_0}{a_1b_2 - a_2b_1} \cdot x_0$$

which those skilled with determinants could have written down right away. Of course, the whole operation is merely the elimination of x_1 between the two original equations and in this particular case it would have been much easier to solve the problem directly. When you turn to more complicated problems, however, there is a lot to be said for working on each small area of the equations without having to carry all the rest along with you and without needing to make a lot of substitutions. You do not need Kirchhoff's laws or Maxwell's circulating currents to calculate a voltage divider but you will get thoroughly tied up without these aids if you are dealing with a three-stage ladder network with a bridge across the top. So with the signal-flow diagram the more complex the problem the more powerful the tool appears to be.

The moment has come to write down some of the rules of the game in a neat list. As given by J. G. Truxal in "Automatic Feedback Control System Synthesis" (McGraw-Hill, 1955) they are:

1. Signals travel along branches only in the direction of the arrows.
2. A signal travelling along any branch is multiplied by the transmittance of that branch.
3. The value of the variable represented by any node (intersection point) is the sum of all signals entering that node.
4. The value of the variable represented by any node is transmitted by all branches leaving that node.
5. The diagram is always drawn so that no branch enters the input node and none leaves the output node.

There is nothing like a practical example to clarify matters. The mapping and reduction exercise above was devised, like all good exercises, to feature all the procedures you may need. We may permit ourselves something a little simpler, with one of the lessons only a practical case can involve, in preparation for a real problem next month. The circuit is shown in Fig. 7(a) and is, of course, our old friend the cathode follower. We can write down some equations for this:

$$e_g = e_i - i_k R_k$$
$$i_k = \mu e_g/(\rho + R_k)$$
$$e_2 = i_k R_k$$

These three equations give us the partial maps of Figs. 7(b), (c) and (d), which we can put together in the form of Fig. 7(e). This time one of the nodes is i_k, a current, although all the others are voltages. It does not matter, the rules are still obeyed, but you will notice that when an arrow points from e_1 to e_g it bears a transmittance which has zero dimensions but from e_g to i_k the dimensions are conductance, 1/R, and from i_k to e_2 they are resistance. Clearly if two nodes are joined by several branches they must all have the same dimensions and this forms a useful check in complex systems.

The results which have been obtained and the conclusions which may be drawn are worth recapitulation. The signal-flow diagram provides a map of the passage of signals through the circuit. Feedback loops are indicated very clearly, as you can see in Fig. 7(e), and this is true even if there are a number of loops. Although there is nothing in the diagrams which was not in the simultaneous equations, elimination of the dependent variables is often much easier because attention can be concentrated on them one at a time.

Next month I propose to deal with a fairly complicated circuit which most of us would think twice about in its conventional treatment. This will give the signal flow diagram a chance to show its advantages.

"**From Us To View,**" a new Mullard film, sets out to show something of the skill and care that go to ensure the high quality of television pictures. It traces the progress of the picture from its beginning in the studio to its appearance in the living room. The 16-mm black and white sound film, which runs for 23 minutes, is available to clubs and other interested organizations on free loan from Mullard House, Torrington Place, London, W.C.1.

WORLD OF WIRELESS

Servicing Examinations

THE Radio Trades Examination Board's syllabuses for sound radio and television servicing have been in operation virtually unchanged since the examinations were first set some years ago. During the past year (reviewed in the Board's 15th annual report) a complete revision of the two syllabuses took place. Apart from revising the material itself an opportunity was taken to combine the sound radio and television subject matter so that there is one syllabus leading up to the issuing of one certificate covering both subjects. The Board will now provide an intermediate examination at the end of the third year of a part-time course and a final examination at the end of the fifth year.

The Board's proposed scheme for certificates for those engaged in installing and servicing "non-domestic" electronic equipment has moved a stage further and a syllabus has now been prepared. It is arranged so that the syllabus for the first two years is common with that for sound radio and television servicing, but separate intermediate and final examinations in electronics are to be held. The first examination will be at the intermediate level in 1961.

The domestic radio and television manufacturing side of the industry is already represented on the Board by B.R.E.M.A. and an invitation has now been extended to the Electronic Engineering Association to be represented.

At the annual general meeting of the Board on December 30th, E. A. W. Spreadbury, technical editor of *Wireless & Electrical Trader*, was elected chairman in succession to E. M. Lee (Belling & Lee).

I.T.A. Masts

MODIFICATIONS to the aerials at three I.T.A. stations are mentioned in the Authority's recently published report for 1958/59. "Whatever finally happens about the siting of television stations in London, there are good technical reasons for making improvements as soon as possible at Croydon" where there is a temporary 200-foot tower. The Authority is satisfied that experience has allayed earlier fears that the radiation of signals from two high towers, one at Crystal Palace (B.B.C.) and one a mile away at Croydon (I.T.A.), might be harmful to reception because of mutual reflection between the two towers. Plans for a new 500-foot tower and "tailored" aerial system have been referred to the Television Advisory Committee. It will be recalled that the height of the B.B.C.'s mast was extended at the instigation of the P.M.G., in order to accommodate the aerials of both the B.B.C. and I.T.A. stations.

At Black Hill, central Scotland, where the aerial is unusual in that the elements are located centrally within the 750-foot mast, both the aerial and the mast are to be replaced; it is hoped by the autumn of this year. The present mast will subsequently be dismantled for use elsewhere.

At Lichfield the existing 450-foot tower is to be replaced by a 1,000-foot mast with a new aerial designed particularly to improve reception in the south-westerly direction.

"Wireless World" Index

The index to Volume 65 (1959) is now available price 1s (postage 3d). Cloth binding cases with index cost 9s including postage and packing. Our publishers will undertake the binding of readers' issues, the cost being 25s per volume, including binding case, index and return postage. Copies should be sent to Iliffe & Sons, Ltd., Binding Department, c/o 4 Iliffe Yard, London, S.E.17, with a note of the sender's name and address. A separate note, confirming despatch, together with remittance should be sent to the Publishing Department, Dorset House, Stamford Street, London, S.E.1.

Dip. Tech.—A second list of students on whom the National Council for Technological Awards has conferred Diplomas in Technology, has been issued. Of the 82 successful candidates, 49 took electrical engineering at the Birmingham College of Advanced Technology, and all but three of these received their industrial training with the G.E.C. The total number of holders of the Dip. Tech. is now 207. There are now 3,320 students studying for the Diploma compared with 1,786 a year ago.

Space Science Symposium.—A British delegation of 40 people led by Professor H. S. W. Massey, F.R.S., chairman of the British National Committee on Space Research, attended the first International Space Science Symposium held in Nice from January 11th to 16th. Organized by the Committee on Space Research (COSPAR) of the International Council of Scientific Unions, it was attended by delegations from nearly 20 countries.

Stereophonic Broadcasting.—A time-multiplex system for broadcasting stereophony has been developed by G. D. Browne, of Mullard Research Laboratories, and has been submitted to the European Broadcasting Union for assessment. Details of the system have not yet been released but it is known that stereophonic v.h.f. receivers could be produced with the addition (apart from the extra loudspeaker and audio stage) of not more than two valves or possibly one transistor and two diodes. The system is compatible for mono and stereo broadcasts.

B.S.R.A.—A one-day convention covering post-war developments in recording, pickup design and cinema sound systems, is being organized by the British Sound Recording Association during the forthcoming Audio Fair. It will be held on April 23rd at the London School of Hygiene and Tropical Medicine, Keppel Street, W.C.1. Registration will cost 5s for B.S.R.A. members and 10s for non-members. Details are obtainable from S. W. Stevens-Stratten, Greenways, 40 Fairfield Way, Ewell, Surrey.

"The Computer in Production."—The Institution of Mechanical Engineers is arranging an informal discussion on the computer in production in order to introduce mechanical engineers and managers to the latest techniques involving the application of computers in production and to provide a forum for users to present their views to computer manufacturers. The meeting will be held on March 21st and 22nd. Further details are available from the Secretary, Institution of Mechanical Engineers, 1 Birdcage Walk, London, S.W.1.

Receiving Licences.—There were twice as many combined television and sound broadcasting licences in force in the U.K. at the end of November as sound-only licences. The comparative figures were 9,987,005 and 4,960,788.

Information Engineering is among the subjects for which M.Sc. degree courses are being conducted by the University of Birmingham. These courses, which are "primarily intended for honours graduates of approved universities" differ from the traditional one of original research leading to the degree of M.Sc. Suitably qualified students (preferably with some industrial experience) can obtain the degree on the satisfactory completion of the 12-month course, of which the next session starts on October 1st, 1960. Subjects available in the information engineering course include communications, radar, computers and control systems, with some degree of choice to suit individual requirements. Full details are obtainable from Dr. D. A. Bell, Supervisor of Graduate Courses, The University, Edgbaston, Birmingham, 15.

The CIBA Fellowship Trust, which was founded for the purpose of furthering the exchange of ideas between scientists in the United Kingdom and on the Continent, announces that several fellowships will be awarded for tenure during the academic year 1960/61 at Continental universities or institutions for research in chemistry, physics or some allied scientific subject. They will be awarded to graduates of U.K. universities or to members of those universities graduating this year. The basic award for Fellows will be £800 per annum, plus allowances. Details are available from the secretary of the CIBA Fellowship Trust, CIBA (A.R.L.), Ltd., Duxford, Cambridge.

T.E.M.A. Awards.—For the third year the Telecommunication Engineering and Manufacturing Association has held a competition for the best final year apprentices (graduate, student and technician) among their member-firms. Awards to the value of £25 will be presented to each of the following at the Association's annual dinner on February 17th: P. J. Langlois, graduate in training, of S.T.C.; P. N. T. Wells, student apprentice, of G.E.C.; and J. R. Bryden, technician apprentice, of Ericsson.

Hendon Technical College, London, N.W.4, is holding a ten-lecture evening course on electronic measurements on Tuesdays from January 26th. Fee £1.

Twickenham Technical College, Middx., is providing a special course of ten evening lectures on printed circuit techniques. The course begins on February 3rd. Fee £1.

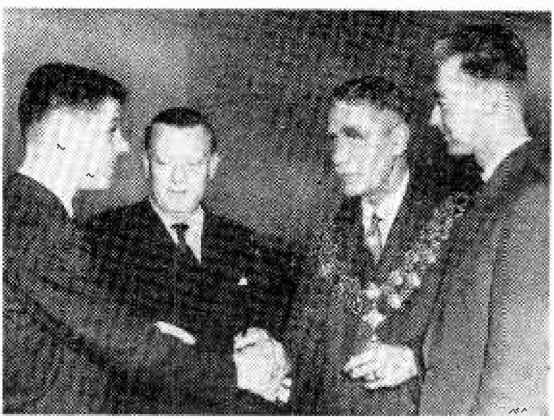

U.S.A. Tour.—*Malcolm Church (left) a 21-year old ex-apprentice of Plessey, Swindon, being congratulated by the Mayor of Swindon on his selection for a six-month tour of America to study engineering techniques and production methods. On the right is F. B. Langworthy, "the best apprentice to complete his training" in 1959. The Mayor presented prizes to nearly 50 apprentices. A. E. Underwood, the company's resident director at Swindon, is second from the left.*

Craftsmanship and Draughtsmanship.—With the object of encouraging craftsmanship and draughtsmanship in the scientific instrument industry a competition mainly for young workers of either sex is held each year by the Physical Society. Twenty-four prizes were awarded to successful entrants at the Society's recent exhibition at which the entries were on display. The Silvanus P. Thompson prize was awarded to Christopher Samms of Marconi's W/T Co. for a mechanical drive unit. In the electronic circuitry section prizes were won by David Elliot (Marconi's), John Butler (Hilger & Watts) and John Mills (Marconi's), and in the microwave components section by James Danbury (Services Electronics Research Lab.), Roy Tucker (Hilger & Watts) and Adrian Short (Services Electronics Research Lab.).

Paris Components Show.—Although listed in the diary of conventions and exhibitions in our January issue as the French Components Show, the exhibition to be held in Paris from February 19th to 23rd is international in character. This is the third International Components Exhibition to be organized by the Industries' Association for Radio and Electronic Components and Accessories (S.I.P.A.R.E.) under the patronage of the National Federation of Electronic Industries (F.N.I.E.).

Nigeria's first two television stations, which have been in service since the beginning of November, operate on 625-lines in Band I. The station at Ibadan, the regional headquarters of Western Nigeria, radiates on 66.25Mc/s vision, and 67.75Mc/s sound (European channel 4), with an e.r.p. of 1.5kW. The station at Abafon, serving the Lagos area, operates on 55.25 and 60.75Mc/s (channel 3) with a 15kW e.r.p.

ELSIE, the Post Office Electronic Letter Sorting and Indicator Equipment, will be among the features in the display at this year's Ideal Home Exhibition (Olympia, March 1st to 26th), depicting the 300 years' growth of the G.P.O. since the King Charles II "Act for the Erection and Establishing a Post Office."

"Teletype."—The Western Electric Company have informed us that the word "Teletype," used in our report of the Radio Hobbies Exhibition (January, 1960, issue) is a registered trade mark of the Teletype Corporation who are associates of Western Electric Co.

CLUB NEWS

Bexleyheath.—At the February 11th meeting of the North Kent Radio Society, W. J. Green (G3FBA) will discuss the design and construction of a multi-band transmitter which will not interfere with television. On the 25th there will be a demonstration of mono and stereo equipment. Meetings are held at 8.0 at the Congregational Hall, Chapel Road.

Birmingham.—A 160-metre mobile rally at Lickey Beacon, Rednal, has been arranged by the South Birmingham Radio Society for 10.30 a.m. on February 7th. The monthly club lecture meeting will be held on the 18th at 9.30 at Friends Meeting House, 220 Moseley Road, Birmingham, 12.

"15 watts in 50 countries" is the title of the talk to be given by R. Roberts, of the B.B.C., to members of the Midland Amateur Radio Society on February 16th. Meetings are held at 7.0 at The Birmingham Midland Institute, Paradise Street.

G. T. Peck, of Ernest Turner Electrical Instruments, will lecture on electronics in the search for oil at the February 26th meeting of the Slade Radio Society which meets on alternate Fridays at 7.45 at The Church House, High Street, Erdington.

Bradford.—David Pratt (G3KEP), secretary of the Bradford Amateur Radio Society will give a talk entitled "Inexpensive sound fidelity" at the club meeting on February 9th at 7.30 at Cambridge House, 66 Little Horton Lane.

Reading.—A representative of E.M.I. Sales & Service is giving a lecture-demonstration of high-quality sound equipment to members of the Calcot Radio Society on February 18th. Monthly meetings are held at 7.45 at St. Birinus Church Hall, Calcot.

News from the Industry

Ultra Reorganization.—Two subsidiary companies have been formed by Ultra Electric (Holdings) Ltd. Mr. E. E. Rosen, chairman and managing director of the company since its formation forty years ago, will continue as chairman of the holding company and of the subsidiaries, with A. V. Edwards as managing director of each of the subsidiaries. The two new companies are Ultra Radio and Television Ltd. (which has its own subsidiary, Pilot Radio and Television Ltd.), handling domestic sound and television equipment, and Ultra Electronics Ltd., which will handle the activities formerly covered by the Special Products Division. Trevor C. Standeven, who joined Ultra eighteen months ago from Radio and Allied Industries, is general manager of Ultra Radio and Television, A. Bamford, technical manager, and W. H. De Val, works manager. They are also members of the board. L. R. Crawford is general manager of Ultra Electronics, Dr. F. W. Stoneman, who joined the organization from Smith's Aircraft Instruments last June, is chief engineer, J. S. Williams is works manager and E. R. Wright, commercial manager. They are also members of the board.

Camp Bird's 57th annual report and statement of accounts presented at the annual general meeting on December 31st records that the group's consolidated earnings before taxation were the highest in the company's history—£666,709, compared with £578,840 the previous year. Reference is made by John Dalgleish (chairman) in his review to the activities of the subsidiaries, including Hartley Baird (see below), Electronic Reproducers (previously known as E.V. Ltd., but not to be confused with E.V. Industrials) and A. Prince Industrial Products, distributors of a number of overseas products, including such names as Blue Spot, Dual and Akkord.

Hartley Baird Ltd., in their report for the year ended last April, record a group profit of £54,402 after taxation. During the year under review the company disposed of its share holding in Ambassador Radio and Television Ltd., which is now owned jointly by Camp Bird and an unnamed company. It is understood Ambassador are not continuing in the domestic sound and television receiver field. The Hartley Baird group includes Hartley Electromotives Ltd., manufacturers of the Taperiter dictating machine, and Duratube & Wire Ltd.

H.M.V. and Marconiphone sound and television receivers and radio-gramophones will in future be distributed by British Radio Corporation Ltd. (21 Cavendish Place, London, W.1, Tel.: Langham 9291) instead of by the sales companies ("His Master's Voice" Radio & TV Sales and Marconiphone Radio & TV Sales), which ceased to operate on January 1st. Matters relating to accounts will be handled by B.R.C. at 270 Great Cambridge Road, Enfield (Tel.: Enfield 5353).

Radio Rentals Ltd. announce a group net profit for the year ended last August of £1,098,616, just over £273,000 above the previous year. This was after allowing £2,968,104 for depreciation and £851,279 for taxation.

Decca's recently introduced river radar, type 215, meets the internationally agreed Rhine Radar Specification issued by the Commission Centrale de la Navigation du Rhin. Compliance with this specification allows vessels fitted with radar to continue their passages up or down the Rhine under conditions of poor visibility.

G.E.C.—The Leeds branch of the General Electric Co. has moved from Wellington Street to a new building in Gelderd Road.

Firth Cleveland Group has recently acquired two organizations in the radio and electronics field. With the acquisition of Broadmead Ltd. on January 4th the group now controls over 500 retail radio stores, including Max Stone, Civic Radio Services and Escott Brothers. The purchase price for Broadmead was £5.8M. John James, the founder and chairman of Broadmead, has joined the board of Firth Cleveland Ltd. The Firth Cleveland Group has also acquired a 53% interest in the Solartron Electronic Group Ltd., which includes fourteen companies in this country and abroad. Charles W. Hayward, chairman of Firth Cleveland, becomes chairman of Solartron. John E. Bolton, who is 39 and was chairman and managing director of the Solartron group, which he joined in 1951, retains his managing directorship but becomes deputy chairman.

Solartron Electronic Business Machines, a subsidiary of the Solartron Electronic Group, have received an order for an Electronic Reading Automaton from Domestic Electric Rentals Ltd. The E.R.A. will read directly, at a speed of up to 300 characters per second, information recorded by National Cash Register machines at each branch of the radio-TV rental organization. This information will then be automatically punched on to 80-column cards for subsequent use in a standard punched-card installation.

Daystrom Ltd. have moved to new premises at Two Mile Bend, Bristol Road, Gloucester, from their temporary address at Glevum Hall, and an official opening ceremony by the Mayor of Gloucester took place on December 7th. A. E. B. Perrigo, who is managing director, disclosed that 25% of their output of British "Heathkits," of which there are now twenty-two types, is exported.

Wayne Kerr have set up a new section to be known as the applications group of the Industrial and Electronics Division. It will be under the direction of G. G. Gouriet, the company's technical director. The administration offices of the new group are at 44 Coombe Road, New Malden, Surrey.

Wolsey Electronics Ltd., of St. Mary Cray, Orpington, Kent, have been appointed sole distributors in the U.K. for Grundig measuring instruments. The range of equipment being handled includes b.f.o's, wobbulators, valve voltmeters, grid-dip oscillators, resistance and capacitance decades and stabilized power supplies.

G. V. Planer Ltd. have recently completed an extension to their research laboratories at Sunbury-on-Thames, Middlesex. The additional accommodation has been allocated to the growing solid-state physics section and associated X-ray crystallographic group. The research facilities for printed circuit and related techniques under L. S. Phillips have also recently been enlarged.

Modac connectors, hitherto produced by Plessey's associate company, Modern Acoustics Ltd., at Boreham Wood, Herts., will in future be manufactured at Plessey's Wiring and Connectors Division at Cheney Manor, Swindon.

E.M.I. closed-circuit television is being used to enable one policeman to control four busy traffic lanes at West Drayton, Middx., during reconstruction of a railway bridge spanning the High Street and Station Road.

Electro Methods Ltd. have moved their Electrical Connector Division to new premises at Hitchin Street, Biggleswade, Beds., (Tel.: Biggleswade 2086). The divisional manager is D. P. Wright.

General Electric Co. has reorganized its General Products Group into five new groups each under the control of a group managing director. The groups, with the name of the managing director in parenthesis, are:—Domestic Equipment Group, incorporating the domestic equipment division (E. A. Fowler); Installation Equipment Group, incorporating the installation equipment division and Pirelli-General cable division (R. H. Phillips); Lighting and Heating Group, incorporating the lighting division and industrial heating department (D. L. Tabraham); Osram Group, incorporating the Osram lamp division and all glass and lamp component units (A. E. Page); and Radio Group, incorporating the radio division (M. M. Macqueen).

EXPORT NEWS

Sweden.—Alma Components Ltd. have appointed AB Solartron, of Hedinsgatan 9, Stockholm NO, as their agents for precision wirewound resistors in Sweden.

Multi-channel u.h.f. communication equipment is being supplied by Plessey for installation in vessels of the South African Navy.

Ghana.—The Government of Ghana has awarded Marconi's the contract for the design and erection of the transmitting station buildings, the supply and installation of the four 100-kW short-wave transmitters and ancillary equipment, the masts, aerial and feeder systems—in short, an entire external broadcasting station on a "turnkey" basis. In addition Marconi's have contracted to supply technical staff for the supervision and maintenance of the station for a period of four years and to be responsible for training personnel of the Ghana Broadcasting System. Valves for the transmitters will be supplied by English Electric Valve Co. The contract for the complete station at Tema, near Accra, is valued at over £600,000.

Canada.—A new microwave link between Moncton and St. John, New Brunswick, using G.E.C. equipment and operating around 2,000Mc/s, was commissioned on December 12th. The installation was carried out by Canadian General Electric Co. The link is primarily for telephones but can be used for television, and work has already begun on extending it from Moncton to Campbellton and from St. John to Halifax and Sydney, Nova Scotia.

Personalities

George Macfarlane, Dr.Ing., B.Sc., A.M.I.E.E., F.Phys.Soc., a Deputy Chief Scientific Officer at the Royal Radar Establishment, Malvern, has been appointed Deputy Director of the National Physical Laboratory. He succeeds **Dr. Edward Lee,** who becomes Director of Stations and Industry Divisions at the Headquarters of the D.S.I.R. Dr. Macfarlane, who is 43, graduated in electrical engineering at Glasgow University in 1937, and then did two years' post-graduate research at Dresden, where he gained the Dr. Ing. degree. He joined the Telecommunications Research Establishment (now R.R.E.) in 1939. Throughout the war he concentrated on mathematical problems in radar and microwave physics and in 1945 became head of the Mathematical Group. Since 1953 he has been carrying out individual research in the Physics Department. Dr. Lee graduated in physics at Manchester University, and after taking his M.Sc. at the University and his Ph.D. at Cambridge University, he joined the Royal Naval Scientific Service in 1939 and was posted to the Admiralty Research Laboratory. He was director of Operational Research at the Admiralty for three years before becoming Deputy Director at the N.P.L. in March, 1958.

Dr. G. Macfarlane

W. G. C. Denny, A.M.Brit.I.R.E., who since the war has been in South Africa, has returned to this country and joined the telecommunications division of Elliott Brothers (London) Ltd. as technical sales manager. He was commissioned in the R.N.V.R. in 1941 and from 1942-46 was radar liaison officer on the staff of the Director of Radio Equipment, the Admiralty, Bath. For six years before joining the Navy he was with Western Electric Co., and prior to 1935 was with E. K. Cole and Murphy Radio. Mr. Denny was chairman of the South African section of the Brit.I.R.E. on its formation in 1949.

M. M. Macqueen, who has been with the G.E.C. since 1923 when he was appointed assistant to the manager of the company's newly formed Radio Department, has become managing director of the Radio Group under the company's reorganization scheme (see "News from the Industry"). He is 61. Mr. Macqueen has also been appointed a director of General Piped Television, Ltd., a new company (in which G.E.C. has an interest) formed to provide a television relay service to viewers. He has several times been chairman of B.R.E.M.A. and has also served on the council of the R.C.E.E.A. (now E.E.A.).

M. M. Macqueen

D. W. Heightman, M.Brit.I.R.E., chief engineer of the Radio Rentals group since 1956, has been appointed to the board of Radio Rentals Ltd. as technical director. He was from 1951 to 1956 chief television engineer at the Liverpool works of the English Electric Co. Prior to joining English Electric he was on the board of Denco (Clacton) Ltd., which he formed in 1938.

Lieut. P. Cave, A.M.I.E.E., R.N., who contributed an article on guided weapon techniques to our August, 1958, issue, writes in this issue on beam-riding. Lt. Cave, who is 35, started his technical career at the Post Office Research Station, Dollis Hill, where he was mainly employed on acoustical development work. This was followed by a short period at the laboratories of British Acoustic Films Ltd., before he entered the Electrical Branch of the Royal Navy in 1949.

G. J. Pope, author of the article on page 88 describing a transistor constant volume amplifier, is in the local lines branch of the Post Office Engineering Department, where he is concerned with the design of carrier receivers and amplifiers. He joined the Post Office soon after leaving the R.A.F. He is 35.

P. Ransom, B.Sc., recently joined International Rectifier Co. (Gt. Britain) Ltd., as engineering manager. He was previously in the A.E.I. semiconductor research laboratories at Rugby. He joined the A.E.I. group in 1945 and since 1954 has been directly concerned with the development of power diodes.

F

V. G. P. Weake has relinquished his directorships of Pamphonic Reproducers Ltd., W. Bryan Savage Ltd., and Pye Marine Ltd., to become chairman of a new group of companies to be known as the Derritron Group. No details are yet available regarding the companies constituting this group. Mr. Weake, who is chairman of Audio Fairs Ltd. and of the recently formed Society of Environmental Engineers, is also a director of Eastern Nigeria Broadcasting Ltd.

G. S. Taylor, commercial director of Grundig (Great Britain) Ltd., which he joined on its formation in 1952, has been appointed chairman and managing director of the company in succession to the late A. E. Johnson (see "Obituary"). Mr. Taylor has also joined the board of Gas Purification and Chemicals Ltd., of which Grundig is a subsidiary.

J. F. Golding, contributor of the article in this issue on alignment equipment for mobile radio, started work in the test department of Marconi Instruments when he left school in 1936. During the early part of the war he joined the design department and, after the war, he spent a short period in technical sales and publicity. He then became a designer with E.M.I. Ltd., at Wells, Somerset, but five years ago returned to Marconi's as a technical writer.

OBITUARY

Philip R. Coursey, B.Sc.(Eng.), M.I.E.E., F.Inst.P., F.Phys.Soc., at one time chief engineer and later technical director of the Dubilier Condenser Company, which he joined in 1923, died on January 3rd in his 68th year. In 1957 he retired from the position of technical director, which he had held since 1931, but remained on the board as an ordinary director and was retained by the company as technical consultant. He was educated at University College, London, where he became assistant to Sir Ambrose Fleming. During the first world war he was Admiralty Inspector of Wireless Telegraphy in H.M. Auxiliary Patrol, and in 1919 became technical research assistant at H.M. Signal School. From 1920 to 1923 he was assistant editor of *Radio Review* and research editor of *Wireless World* until 1925. He has contributed many fundamental articles to *Wireless World* and was the author of several books.

John R. (Jack) Binns, who, as mentioned by "Free Grid" last month, was the first ship's wireless operator to demonstrate the value of radio in saving life at sea, died in New York on December 8th, aged 75. Jack Binns, who was born in this country and was a Marconi operator from 1905 to 1912, had been associated with the Hazeltine Corporation since 1924. He was president in 1942 and chairman of the board from 1952. He was operator in the liner *Republic* when it was in collision in January, 1909, with the Italian vessel *Florida*. His wireless messages relayed by the American station at Nantucket Island resulted in the *Baltic* rescuing all the passengers on board the two ships. Medals were struck for the officers and crews of the three vessels, and Binns was the recipient, at the hand of the Marchese Marconi, of one of four struck in gold (the others went to the three captains).

Admiral Arthur J. L. Murray, C.B., D.S.O., O.B.E., at one time during the war Director of the Signal Department at the Admiralty, died on December 26th, aged 73. He was in command of the Signal School, Portsmouth, from 1937 to 1939. Admiral Murray was president of the British Wireless Dinner Club in 1952.

Albert E. Johnson, chairman and managing director of Grundig (Great Britain), Ltd., which he formed in 1952, died on November 25th after several months' illness. He was also a director of Gas Purification and Chemical Co., and a number of its subsidiaries. Mr. Johnson had been associated with the radio industry for over thirty years.

NEW YEAR HONOURS

Sir George Nelson, chairman of the English Electric Co. and a number of companies within the group, including English Electric Valve, Marconi's W/T and Marconi Marine, is to be a Baron.

Lt. Gen. Sir Ian Jacob, K.B.E., C.B., Director-General of the B.B.C. from 1952 until the end of last year, and president of the European Broadcasting Union since its formation in 1950, is appointed a Knight Grand Cross of the Order of the British Empire (G.B.E.).

Robert J. P. Harvey, C.B., Deputy Director-General of the Post Office since 1955, and previously director of the Radio and Accommodation Dept., becomes a Knight Commander of the Order of the British Empire (K.B.E.).

Joseph F. Lockwood, chairman of Electric and Musical Industries and a director of the National Research Development Corp., receives a Knighthood.

Dr. Harrie S. W. Massey, F.R.S., Quain Professor of Physics at University College, London, and a member of the Radio Research Board, receives a Knighthood.

Among those appointed Commanders of the Order of the British Empire (C.B.E.) are: **L. J. Davies,** director of research and education, B.T.H. (now A.E.I., Rugby); **D. C. Martin,** assistant secretary, Royal Society; **W. Stubbs,** Director-General of Telecommunications, Malaya; **F. Williams,** controller of sound broadcasting engineering, B.B.C.

Newly appointed Officers of the Order of the British Empire (O.B.E.) include: **F. E. B. Clark,** Director of Posts & Telecommunications, Ghana; and **A. W. H. Cole,** manager, communications division, Marconi's W/T Co.

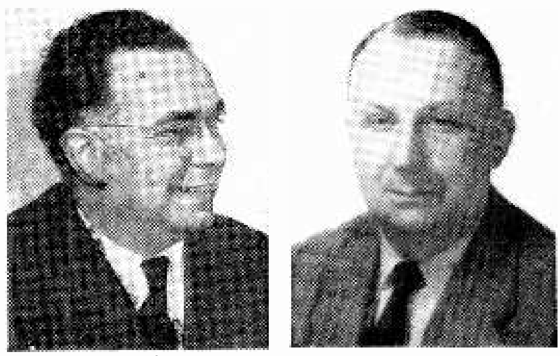

A. W. H. Cole (O.B.E.) *L. G. Fowell (M.B.E.)*

The following are among the new M.B.E.s: **A. Allen,** chief development engineer, Cossor Radar and Electronics, Harlow; **S. R. Brown,** signals officer, Ministry of Aviation; **F. N. Chadwick,** higher executive officer, London Communications-Electronics Agency; **R. W. Chandler,** chief telecommunications supt., G.P.O.; **A. Draper,** vice-principal Rugby College of Engineering Technology; **L. G. Fowell,** executive engineer and general manager, Pye Ltd., West Drayton; **M. H. Hall,** engineer-in-charge, B.B.C. television studios; **D. A. Hewetson,** telecommunications technical officer, Ronaldsway Airport, Isle of Man; **J. H. Kirk,** executive engineer, G.P.O.; **W. J. Marshall,** senior executive engineer, Engineer-in-Chief's Office, G.P.O.; **N. G. Payne,** engineer-in-charge, I.T.A. station at Lichfield; and **G. H. Prince,** head of Apparatus Engineering Dept., Ericsson Telephones, Nottingham.

Recipients of the British Empire Medal include: **J. Armitage,** civilian instructor, R.A.F. Technical College, Henlow; **F. A. Loomes,** technical officer, Post Office Research Station; and **J. N. N. Murray,** civilian radio operator, War Office, Cyprus.

Ionosphere Review 1959

DECLINING SOLAR ACTIVITY

*By T. W. BENNINGTON**

THE present cycle of solar activity reached its maximum at the epoch February/March, 1958, and since then the average activity, as evidenced by the twelve-month running average of the sunspot number, has been declining. Throughout 1959, however, the decrease in sunspot activity has been relatively slow, so that, at the end of the year, the running average sunspot number was still above 160, a value which is higher than that reached even at the maximum of any other solar cycle of which we have records. The year 1959 was, therefore, one of exceptionally high solar activity, and, consequently, a year during which the frequencies of use for long-distance communication remained particularly high.

Course of the Sunspot Cycle.—The graphs will give an idea of the present situation. In the upper graph are plotted the sunspot numbers (indicative of the degree of solar activity) from the minimum year of 1954 until the end of 1959, and in the two lower graphs the noon and midnight F2-layer critical frequencies as measured at the D.S.I.R. station at Slough (indicative of the level of F2 ionization) are given. The full lines in each graph give the monthly mean, or median, values and the dashed lines show the twelve-month running average of these, and so indicate the average conditions and the general variation in each quantity.

Since sunspot maximum early in 1958 there have been some large fluctuations in the monthly value of the sunspot number, but towards the end of 1959, lower values were reached than for some years past. The twelve-month running average has, during this period, shown an almost continuous, but generally slow, decrease.

The noon critical frequency was only slightly lower during the summer of 1959 than during that of 1958, but the winter values at the end of the year were considerably lower than at the beginning, and during 1958. The midnight critical frequency peaked during the summer at a higher value than during 1958, but towards the end of the year it, also, had reached values lower than those for the previous winter. The change in critical frequency since sunspot maximum has thus, on the average, been a rather slow decrease, as is shown by the dashed-line curves both for noon and midnight, and the implication is that, during the year, the frequencies of use for communications should have remained relatively high. In practice this was found to be so.

Usable Frequencies.—The highest broadcast frequency band of 26Mc/s remained usable over many daylit circuits throughout the year, and the 28-Mc/s amateur band, whilst very often above the m.u.f. during the summer months, became workable again in most directions during the autumn. The highest frequencies receivable over the North Atlantic circuits, which were of the order of 50Mc/s at the beginning of the year, decreased to about 26Mc/s during the summer, and increased again to about 44Mc/s during the autumn. The Crystal Palace sound channel (41.5Mc/s) was very frequently receivable in South Africa during March but such reception became rare in the period May to August. During the September to November period it became more frequent, but much less so than during March. The annual pattern for the ionospheric propagation of these high frequencies is thus that of good propagation of the highest frequencies at the beginning of the year, a big frequency decrease in the summer, and an autumnal increase to frequencies which, whilst relatively high, were considerably lower than those propagated at the beginning of the year.

Ionospheric and Magnetic Disturbances.—The magnetic and ionospheric data for 1959 show that the number of magnetically and ionospherically disturbed days was somewhat greater than during 1958. On the other hand the number of sudden ionospheric disturbances (which are associated with the occurrence of solar flares near sunspots) was slightly less than during the previous year. As the frequency of occurrence of sunspots and solar flares decreases during the next few years so is the number of sudden ionospheric disturbances likely to continue to decrease. The same is not true for magnetic and ionospheric storms, however, for, during the decreasing phase of the sunspot cycle, many of these are caused by corpuscles emitted from solar regions where there is no sunspot activity.

The Coming Year.—During 1960 it is probable that

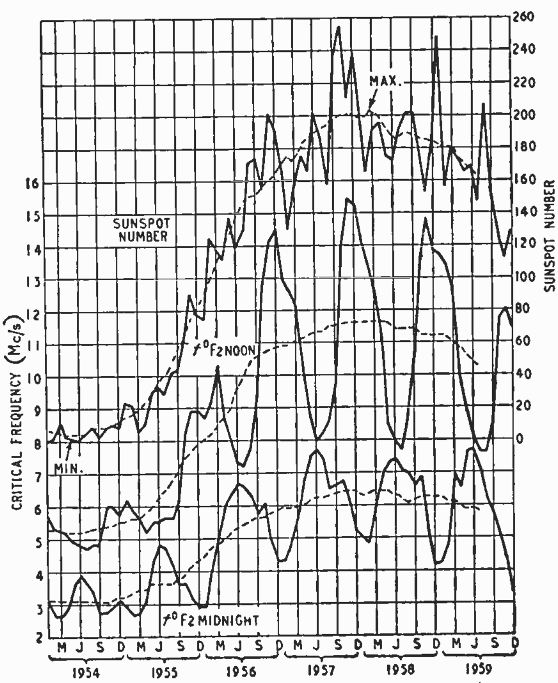

Variations in sunspot activity with corresponding variations in ionospheric conditions, 1954 to 1959.

* Research Department, British Broadcasting Corporation

the solar activity will follow a slow decline, but at a somewhat greater rate than during 1959, and that the twelve-month running average sunspot number at the end of the year (applicable to the epoch June/July) will be somewhere in the region of 115. If this be so we may expect the higher daytime frequencies to remain usable until early summer, and then, following on the seasonal decrease which takes place at that time, for there to be a definite tendency for somewhat lower frequencies to be of more use during the autumn and winter, and for the higher frequencies to fail over certain circuits. For example, over North Atlantic circuits the 26-Mc/s broadcast band is unlikely to be usable after March, and with the 17-Mc/s or even the 15-Mc/s band being best during the summer, the 21-Mc/s band is likely to be the highest usable from September onwards. For communication in more southerly directions the 26-Mc/s band may be usable at the end of the year as well as at the beginning, though during the summer the 21-Mc/s band is likely to be best. As to the night-time frequencies there is already a tendency towards more use of somewhat lower frequency bands, and, following on the summer frequency increase, this is likely to continue in the autumn, resulting in the greater use, over all circuits, of lower night-time frequencies at the end of the year than at the beginning.

Demonstrating Electron Spin Resonance

A Simple Apparatus for Use in the Lecture Room

By G. B. CLAYTON,* B.Sc.

THE techniques of nuclear magnetic resonance and electron spin resonance, both branches of radio-frequency spectroscopy, are now firmly established as research methods and are finding an increasing number of applications in many fields of science[1]. It would therefore seem desirable that the basic principle of the magnetic resonance effect, which is common to both n.m.r. and e.s.r., should be more widely known. The phenomenon may be demonstrated with modest apparatus; this article describes such an apparatus and gives a simple explanation of the effect.

The phenomenon of magnetic resonance is essentially a quantum mechanical effect, but its description in terms of classical mechanics is very instructive and leads to results that are in agreement with those found quantum mechanically. Nuclei and electrons may be thought of as spinning particles having both charge and mass. Consider a spinning sphere having positive charge uniformly distributed over its surface (Fig. 1). The whirling charge on the surface of the sphere represents in effect a circulating electric current, which will produce a magnetic field. The spinning mass of the sphere will give it an angular momentum, so that we may think of the spinning charged sphere as acting in a sense like a flywheel with a bar magnet pointing along its axis.

Fig. 1. Spinning charged particle (a), producing a magnetic field (b), acting like a flywheel with an axial bar magnet (c).

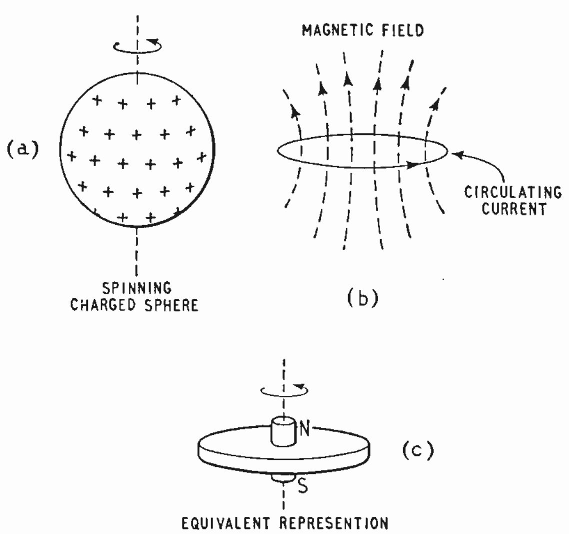

Now consider this system placed in a steady magnetic field H, with the magnet inclined at some angle to the field (Fig. 2). The magnet will experience a torque tending to turn it into alignment with the magnetic field, but this will not take place because the magnet is attached to the flywheel. The torque acting on the angular momentum of the flywheel will cause the flywheel to precess about the direction of the magnetic field.

A mathematical treatment of the motion gives the relationship:

$$\omega = \gamma H \quad \ldots \quad \ldots \quad \ldots \quad 1$$

for the angular velocity ω at which the precession takes place. γ is a constant called the gyromagnetic ratio and is equal to the ratio

$$\frac{\text{angular momentum of particle}}{\text{magnetic moment of particle}}$$

A simple analogy for the effect may be found in the behaviour of a spinning top (Fig. 3). The weight of the top acting through its centre of gravity produces a torque tending to make it topple over, but because the top is spinning this torque actually causes it to precess, as shown in the sketch.

Return now to the system considered in Fig. 2 and imagine that, in addition to the steady magnetic field H, a second magnetic field H_1 ($H_1 \ll H$) is applied, and that this field is rotating in a plane at right angles to H with angular velocity ω_1 (Fig. 4). This rotating field will also produce a torque on the magnet, but if the field is rotating at a rate that differs appreciably from the rate at which the

* Liverpool College of Technology

magnet is precessing, the direction of the torque will be rapidly changing and its value will average to zero. In this case the rotating field will have no resultant effect. On the other hand, if H_1 is rotating at the same rate as the magnet is precessing it will produce a steady torque on the magnet. This steady torque will cause the magnet to precess about H_1 while continuing in its precession about the steady field H (Fig. 5).

The result of this precession about H_1 will be a change in the angle between the magnet and the steady field H. If the magnet was initially pointing in the direction of the steady field the rotating field would cause it to tip up and down; this tipping of the magnet represents the phenomenon of magnetic resonance.

The resonance condition is that the field H_1 should rotate at the same rate that the magnet precesses about H, and is given by the equation

$$\omega_1 = \omega = \gamma H \quad .. \quad .. \quad .. \quad 2$$

The energy of the magnet in the steady field H depends on the angle that it makes with this field. It will be a minimum when the magnet points in the same direction as H and a maximum when the magnet points in the opposite direction to H.

The magnet will thus absorb energy from the rotating field H_1 as it turns against the steady field H and will return this energy as it lines up with the steady

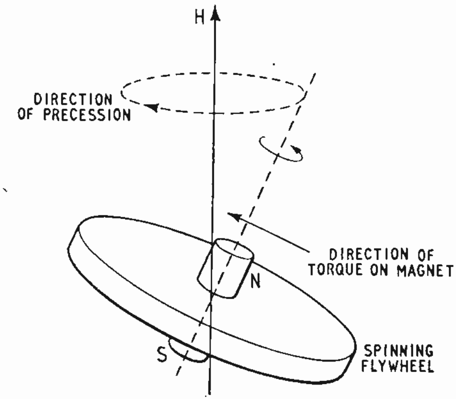

Fig. 2. The magnet-flywheel of Fig. 1 placed in a steady magnetic field.

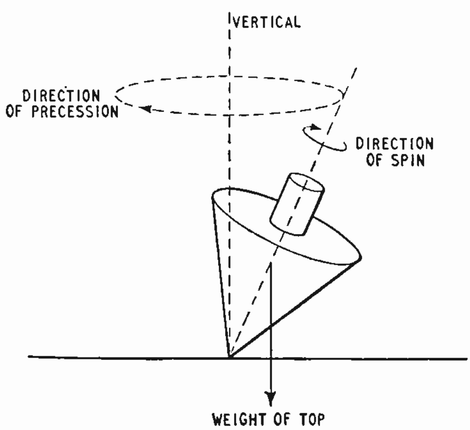

Fig. 3. Spinning top analogy for the action in Fig. 2.

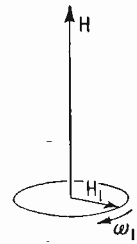

Fig. 4. Showing how the second magnetic field H_1 rotates relative to H.

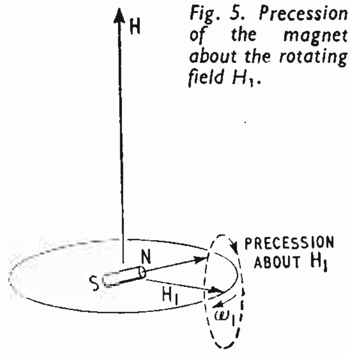

Fig. 5. Precession of the magnet about the rotating field H_1.

field. In a system containing a large number of such magnetic particles there will be a resultant absorption of energy from a small field rotating at the resonance frequency if there is always an excess number of particles pointing in the direction of the steady field. In practice this excess is initially established and then maintained as a result of energy exchange between the thermal vibrations of the material containing the particles and the magnetic energy of the particles.

The effect has been described for positive particles (e.g., protons). A similar treatment is appropriate for negatively charged particles (electrons). Values of constants substituted in eq.2 give for the resonant frequencies:

for proton resonance f(kc/s) 4.26H (oersteds)
for electron resonance f(Mc/s) 2.80H (oersteds)

Nuclear magnetic resonance observations are usually carried out in a field of the order 10,000 oersteds, in which field the proton resonance takes place at 42.6Mc/s. Electron spin resonance observations are usually made in fields of the same order, making the resonant frequency lie in the microwave region.

In certain cases where a narrow absorption line is produced e.s.r. may be observed in quite small magnetic fields. For a field of 10 oersteds the resonance occurs at 28Mc/s. Observations of e.s.r. at these frequencies have been reported in metals[2], in metal ammonia solutions[3], and in organic free radicals[4]. The apparatus to be described has been used to observe the e.s.r. absorption arising from the unpaired electron spins in the organic free radical diphenyl-picryl hydrazyl.

Free radicals are formed when one of the covalent bonds in an organic molecule is broken. Each fragment takes with it one electron from this bond, and these fragments are called free radicals. The distinguishing feature of free radicals is that they have an unsaturated valency bond; that is, they have associated with them an electron whose spin and magnetic moment is not compensated by another electron with spin and magnetic moment pointing in the opposite direction. It is the presence of these uncompensated electrons that makes the observation of e.s.r. possible.

Free radicals, because of their unsaturated valency bond, are very reactive and are normally short lived. Diphenyl-picryl hydrazyl, the specimen used, is a substance that has an unsaturated valency bond, but it is quite stable. It is a crystalline solid and no difficulties are involved in handling it†.

† Diphenyl-picryl hydrazyl should be obtainable from any supplier of fine chemicals. The organic free radicals tri-p-anisyl-aminium perchlorate, and tri-p-aminophenyl-aminium perchlorate have also been reported as giving an absorption signal at the frequencies used and should be suitable for use in the apparatus.

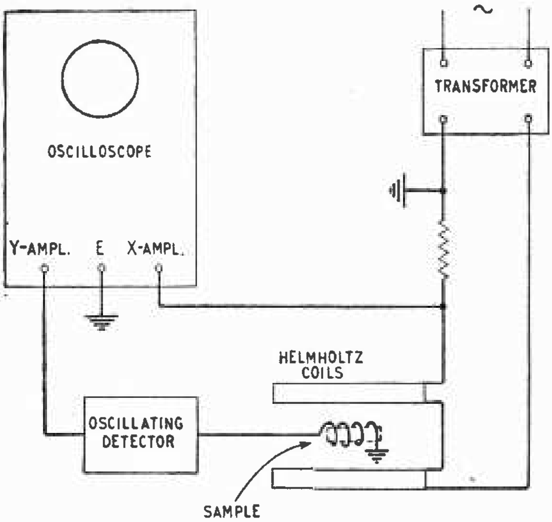

Fig. 6. Basis of the apparatus for demonstrating electron spin resonance.

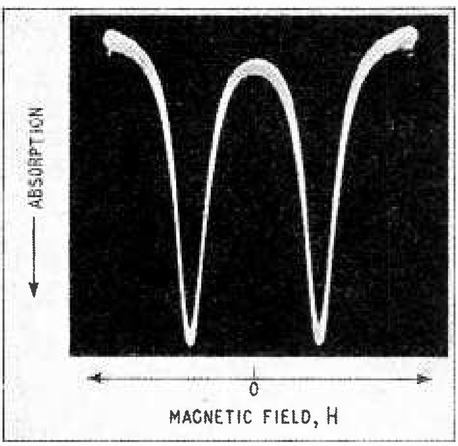

Fig. 7. Double absorption curve given by the oscilloscope in Fig. 6.

The apparatus consists essentially of an oscillating detector. The tank coil of this oscillator contains the specimen and is positioned at right angles to the magnetic field produced by a pair of Helmholtz coils. The oscillating magnetic field produced by the coil of the oscillator will, of course, be linearly polarized, but a linearly polarized field may be thought of as consisting of two fields rotating in opposite directions, and the effect of the component rotating in the opposite direction to the precessing spins is negligible. In order to observe the absorption the frequency of the oscillator is fixed and the magnetic field produced by the Helmholtz coils is swept through its resonance value. The detected output of the oscillator is made to produce a vertical deflection on an oscilloscope trace while the magnetic field sweep is used to produce the horizontal deflection (Fig. 6).

The current for the magnetic field sweep is supplied by a transformer connected to the 50-c/s mains. This a.c. sweep produces the double absorption hump shown in the oscillogram Fig. 7. The double hump in fact represents only one absorption line,

Fig. 8. Circuit of the oscillating detector used in the apparatus.

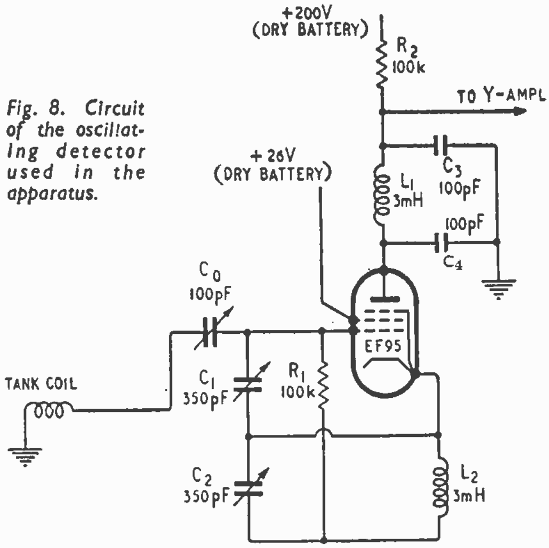

for the magnetic field is made to pass through its resonant value first in one direction and then in the opposite direction.

The circuit of the oscillating detector used is given in Fig. 8. It is a modified Clapp oscillator. Absorption by the specimen lowers the Q of the tank coil and produces a change in the level of oscillations which is detected by a change in the voltage across R_2. Approximately 1 gm of the diphenyl-picryl hydrazyl placed inside the oscillator tank coil has been found to give a change of 400mV in the voltage across R_2 when the magnetic field is swept through its resonance value.

Radio frequency oscillations are eliminated from R_2 by the filter $C_3L_1C_4$. Capacitors C_1C_2 are adjusted until oscillations just commence; the circuit is then most sensitive to changes in the Q of the resonant circuit. C_1 is kept approximately equal to C_2.

There is nothing very critical about the design of the oscillator tank coil. It consists of several turns of enamelled copper wire wound on the ½-in diameter tube containing the specimen. The coil is connected to the oscillator circuit by a short length of coaxial cable. Several coils were, in fact, wound to cover the frequency range 15 to 30Mc/s. Plywood formers, of diameter approximately 8in, were used for the Helmholtz coils, each being wound with 100 turns of No. 24 s.w.g. enamelled copper wire. An a.c. amplitude of 1 amp was found sufficient to sweep right through the resonance.

The apparatus described is comparatively simple and inexpensive, and the large and costly magnet normally used in magnetic resonance investigations is not required. It should be emphasized that the primary purpose of the apparatus is for the demonstration of magnetic resonance absorption. If it is required to detect very small absorptions or to study broad absorption lines it is necessary to work with much larger magnetic fields than can be produced with simple coils.

REFERENCES

[1] "Spectroscopy at Radio and Microwave Frequencies," by D. J. E. Ingram, Butterworth (1955).
[2] *Phys. Rev.*, **94**, (1954), p. 1067.
[3] *J. Chem. Phys.*, **21**, (1953), p. 1429.
[4] *Phys. Rev.*, **95**, (1954), p. 607.

BEAM RIDING

By LIEUT. P. CAVE, A.M.I.E.E., R.N.

PRINCIPLES OF RADIO GUIDANCE TECHNIQUE FOR MISSILES

THE missile guidance system known as beam riding is a popular method for medium range missiles and has advantages over some other systems. It is used in modern weapons and probably its use will continue with longer range missiles even if it has to be combined with some other form of guidance for the latter stages of its flight to provide the necessary accuracy.

The system relies on the automatic centring of the missile in a radio beam, and hence the missile flight path may be controlled by moving the beam. In the simplest case the beam is pointed continuously at the target either manually or automatically and hence the missile will fly up the centre of the beam to the target. It will be seen that this guidance system is in two stages, viz.:—

1. Pointing the beam at the target.
2. Making the missile "ride the beam," i.e. follow the beam centre.

For short range missiles, e.g. air-to-air weapons such as FIREFLASH, the first step may be accomplished by pointing the radio beam at the target using an optical sight. For longer range missiles it is necessary to establish the sight line by the use of a lock-and-follow radar. In theory it is not necessary to have any connection between the tracking radar and the radio beam other than that they must both point in the same direction. There is generally a close connection between the two transmissions from a viewpoint of mechanical and electrical convenience. For instance, to lock the aim of the two transmissions it is convenient to use the same radar aerial, and electrical synchronisation is necessary to overcome interference problems. In addition, there is a similarity between the method used to obtain the automatic following action and that used in riding the beam. To develop this idea further let us examine the working of a typical automatic following radar.

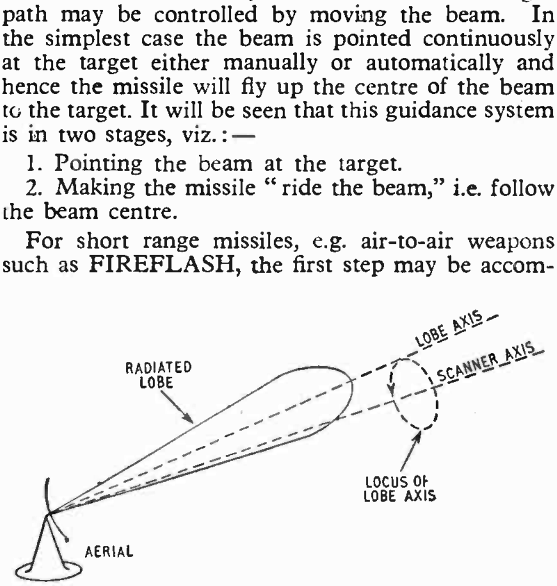

Fig. 1. Production of a conical scanning pattern.

The most commonly used system is by conical scanning of the radar beam, but other methods that are used include "sequential lobing" and "simultaneous comparison" systems. In the conical scanning system the radar transmissions are focused into a pencil beam and this beam is offset from the axis of the scanner by a fixed angle. If the beam is now rotated about the scanner axis it will trace out a conical pattern with the apex of the cone at the aerial as shown in Fig. 1.

Consider now the radar echo obtained from a target which is within the conical scan but displaced from the aerial reflector axis as shown at T in Fig. 2. Since the echo received by the radar depends on the misalignment between the centre of the radar lobe and the line of sight to the target, the echo received will vary as the lobe rotates according to the distance PT between the target T and the instantaneous position of the lobe centre P. The shorter this distance the greater the echo, reaching a maximum when the distance is zero, i.e. when the radar lobe is pointing directly at the target. In the case shown in Fig. 2 this distance does not fall to zero but is at a minimum when the centre of the lobe is at A. This is the instant of maximum echo and similarly a minimum echo is received as the lobe passes through B and PT is a maximum. Thus the echo strength will vary from a maximum to a minimum and return to a maximum once per revolution of the scanning lobe.

If a pulsed radar system is to be used, the output of the radar receiver will consist of a series of pulses, amplitude modulated at the conical scanning frequency. The depth of the modulation is approximately proportional to the error of the target from the reflector axis and especial note must be made of the condition when this error is zero. In this case the target is always displaced from the radar lobe by the same amount and hence the echo modulation is zero. Similarly the maximum modulation occurs when the target is on the circle formed by the focus of the centre of the rotating lobe.

Following the block diagram of a simple automatic following system as shown in Fig. 3, the echo modulation signal may be extracted from the radar receiver output by a filter tuned to the conical scanning frequency. In order to discriminate against unwanted echoes, the radar receiver must include a gated amplifier whose operation is controlled by the target range. The filter output signal contains two pieces of information, viz.: (a) its amplitude is proportional to the magnitude of the target misalign-

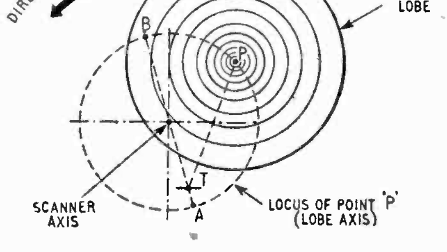

Fig. 2. Cross-section of a conical scan.

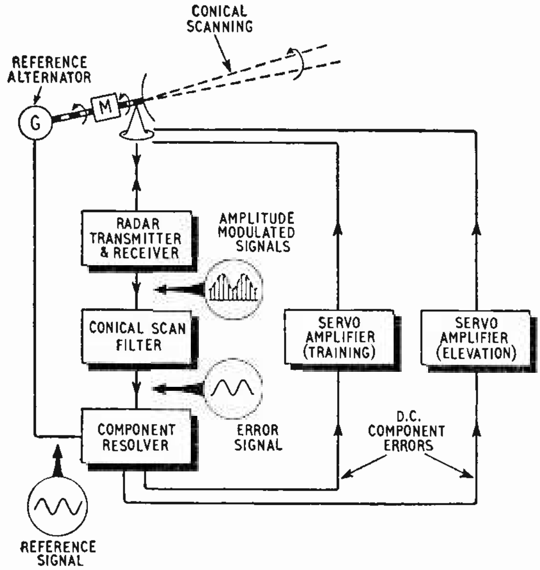

Fig. 3. Simple automatic following radar system.

ment; (b) its peak positive swing indicates the instant in the conical scanning cycle when the lobe sweeps closest to the target.

In order to correct the error in aim, the error along the target axis must now be resolved into component errors along the elevation and training axes of the aerial. In the same way that the target axis is defined by the peak in the error wave, so may the elevation (and hence training) axis be defined by the positive peak of a local reference signal. This is derived from a generator driven from the conical scanning motor and phased so that the positive peak of the generator output occurs as the radar lobe passes through the elevation axis. The phase angle between the reference and error signals is equal to the angle between the elevation and target axis as shown in Fig. 4.

The component errors in elevation and training are given by:—

$$\text{Training error} = E \sin \phi$$
$$\text{Elevation error} = E \cos \phi$$

where E = peak value of error signal and ϕ = phase of error signal with respect to the reference signal. These component errors are calculated in the resolver which may be of the resistance modulator or of the phase comparison variety. The outputs of the resolver are used to actuate the training and elevation motors via suitable amplifiers which in turn will be made up of a combination of an electronic amplifier and an electric amplifier such as a metadyne or amplidyne system. The polarity of the system is arranged so that the motors train and elevate the aerial in the correct direction.

It will be seen that the overall arrangement is a servo system whose input and output are the target and aerial positions respectively and where the radar and associated resolver form the error measuring device. The performance of this servo may be regulated by the usual servo devices, e.g. phase correcting networks. These are frequently incorporated into the amplifier section. Thus when the automatic following system is working correctly, we have the condition where the target lies on the scanner axis whilst the beam performs a conical scan around it.

In order to guide the beam-riding missile, a separate conically scanning pulsed radio beam is radiated and aimed in the same direction as the automatic following beam. The missile is equipped with a receiver and rear pointing aerial capable of detecting the transmitted pulses when it has been launched into the conical scanning pattern.

In theory, there is no reason why the transmission used for the automatic following radar should not be used to guide the missile, but in practice several factors combine to make this undesirable and to give better results when separate beams are used.

The displacement of the missile from the beam centre will cause the missile receiver output to be amplitude modulated at the conical scanning frequency since the instantaneous output will be governed by the displacement of the missile from the centre of the lobe. An error signal may now be derived by detection of this amplitude modulation. The amplitude of the error signal will be indicative of the missile's displacement from the beam centre and the peak positive swing will indicate the instant when the lobe centre is closest to the missile. The production of this error signal is a close parallel to the case of the automatic following radar.

The majority of missiles use a Cartesian control system, i.e., they are controlled by four control surfaces, which, by operating in pairs, cause the missile to move in the pitch and yaw planes. Three further steps are necessary to bring the beam riding missile to the target axis.

(a) The error signal must be resolved into component errors along the radar vertical and horizontal axes.

(b) The missile must be stabilized in the roll plane in such a position that its pitch and yaw axes are in alignment with the radar vertical and horizontal axes throughout the flight.

(c) The control surfaces must be deflected by an amount proportional to the component errors in each case in the correct direction to accelerate the missile towards the centre of the beam.

In the case of the automatic following radar, resolution of the error signal was accomplished with the aid of a reference signal which defined the radar axes. To enable the same process to be used in the

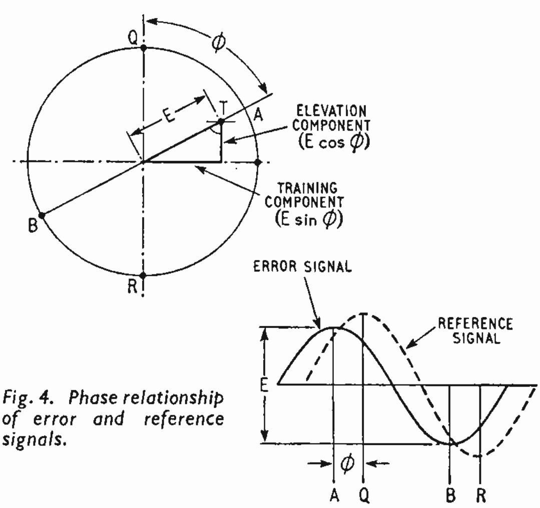

Fig. 4. Phase relationship of error and reference signals.

missile, the reference signal must be transmitted independently to the missile. Whilst this could be accomplished by the use of a separate radio link, a more reliable and less bulky method is to pulse-position-modulate the guiding beam with the reference signal, thus transmitting the reference signal to the missile without interference to the amplitude modulation/error signal process. This means that when the instantaneous value of the reference signal is positive the spacing between pulses of the guiding transmitter will be small and hence the pulse repetition frequency will rise, but when the signal is instantaneously negative, the spacing will be larger and hence the pulse repetition frequency will be lower.

In short, the reference wave is conveyed to the missile by a sinusoidal modulation of the pulse repetition frequency of the guiding transmitter. Reference to Fig. 5 will show that the output of the missile guidance receiver is taken to separate a.m. and f.m. detectors which produce the error and reference signals respectively. The signals are then fed to the resolver whose outputs are the pitch and yaw component error signals.

Another method whereby a reference may be produced in the missile is to rotate the plane of polarization of the guidance beam in step with the conical scan. The small dimension of the rectangular waveguide horn radiating the guiding transmitter signals is kept radial to the scanner axis whilst it is rotated. Hence the conical scan is produced simultaneously with the rotation of the plane of polarization and the instantaneous direction of the polarization (which is parallel to the small dimension of the waveguide) indicates the position of the lobe.

The direction of the polarization can be detected in the missile by the use of two aerials. One aerial is a circular waveguide horn which is not sensitive to the changing polarization. This will enable the amplitude modulation signal to be detected directly. The second aerial consists of a rectangular horn from which the received signal will vary as the polarization rotates and thus the reference signal will be produced. If this system is used, it is not essential to roll-position-stabilize the missile to keep it in line with the radar axes, since the reference signal is being produced with respect to the missile vertical as defined by the rectangular waveguide aerial. A disadvantage of this system is that the rotating plane of polarization introduces the problem of reflection of energy from the surface of the earth at low angles of elevation.

The overall accuracy requirement for a missile system, i.e., the maximum permissible miss distance, is determined by the effective range of the warhead, and the design of the guidance system must be governed by this parameter. For instance, for the beam riding missile to have a maximum miss distance of 150 feet at 20 miles range requires that it must not deviate from the line of sight from radar to target by more than four minutes of arc as measured at the radar aerial. The guidance accuracy is determined by two factors, viz:—

(1) The tracking accuracy of the automatic following radar, i.e., the maximum deviation of the scanner axis from the actual line of sight.

(2) The maximum deviation of the missile from the scanner axis.

In both cases the accuracy achieved depends on the performance of a complicated servo system. The block diagram of the automatic following radar as shown in Fig. 3 has already been discussed; the diagram of the overall missile servo is shown in Fig. 6. In this servo the input, or required position, is the scanner axis as defined by the beam, whilst the output is the actual position of the missile. The missile receiver is the error measuring device and the error signal produced initiates movements of the control surfaces in such a direction as to correct the error and thus bring the missile position (output) into line with the scanner axis (input).

The performance of both servos will eventually be limited by the signal/noise ratio of the receivers, i.e., the minimum error signal that can be detected.

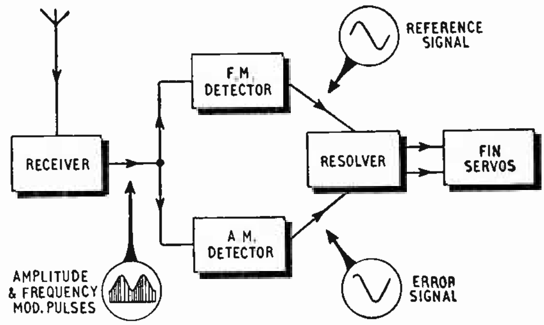

Fig. 5. Overall block diagram of control system in a beam riding missile.

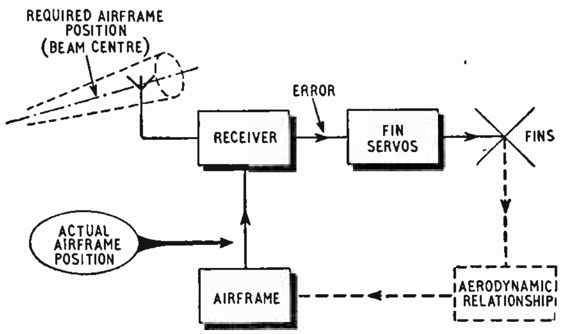

Fig. 6. The beam rider as a servomechanism.

Since the maximum signal is fixed at 100 per cent modulation of the pulse amplitude, corresponding to a missile or target located on the locus of the centre of the rotating beam, the minimum detectable error signal may be expressed as a fraction of the conical scanning angle. A figure of 1/20 will be used in this example. If the overall error of four minutes, referred to above, is split equally between the two servos (two minutes each), then the radius of the conical scan pattern must correspond to 40 minutes of arc, i.e., $\frac{2}{3}$ degree, and the total conical scan angle will be $1\frac{1}{3}$ degrees.

Unfortunately it is not possible to launch the missile directly into this beam as the flight path of the missile when launched may differ by several degrees from the aim of the launcher. This is partly due to the low speed of the missile when leaving the launcher and to manufacturing tolerances in the air-frame and propulsion system. In addition, it is not possible to design the aerodynamics of the missile so that it can be controlled at low speeds, and in most missiles the control system is not effective until the boost motor is exhausted and the missile is at full speed. As the missile thus travels for the first few seconds without control, movements of the target will cause the tracking beam to move and hence the missile may not be within the guiding beam when the control system is energized.

The launching errors may be summarized as (a) predictable—such as wind effects and target movement, and (b) unpredictable—covering manufacturing tolerances. Where the errors can be predicted a computer can be used to "aim off" the launcher to correct the missile's flight path, but for unpredictable errors the method generally adopted is to use a wide-angle, low-accuracy beam whose conical-scan angle is wide enough to cover all possible firing dispersions. This beam must be identical to the narrow-angle high-accuracy beam in lobe position, scanner axis and reference transmission, so that the missile may be smoothly transferred from one beam to the other when it comes into the coverage of the narrow beam. The problem of reflections from the ground denies the system designer the chance of dealing with both predictable and unpredictable errors by this means as the conical scan required to do this would be very large.

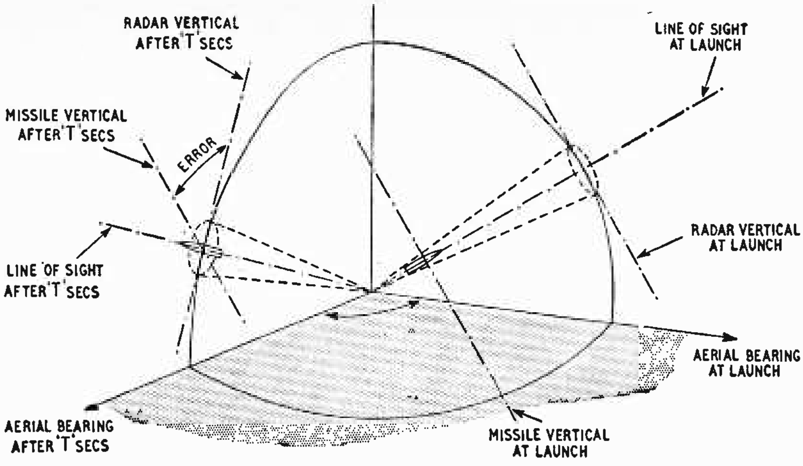

Fig. 7. Three-dimensional diagram showing change of radar vertical with aerial bearing.

It was mentioned earlier that roll stabilization was used to keep the missile axes in alignment with the radar axes, and although the roll gyro can have negligible wander during the time of flight, it is possible for the two sets of axes to become misaligned. This can be due to a variety of reasons, but assuming that the axes are aligned when the missile is launched, the main cause of error is due to the fact that whilst the roll gyro axis is stationary in space, the radar vertical direction will change as the aerial trains away from the launching bearing in order to follow the target. This effect is illustrated in Fig. 7. The result of this error, as shown in Fig. 8, is to cause the missile to fly in a spiral path to the beam centre instead of in a straight line. This occurs because the steering orders are derived with respect to the radar vertical (as defined in the missile by the reference signal) but executed with respect to the missile vertical.

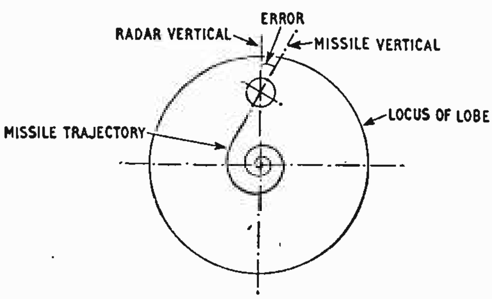

Fig. 8. Cross-se-tion of beam showing spiral trajectory due to misalignment of verticals.

The inherent time lag in the missile response will now permit the missile to fly in the direction determined by its own axes before the modified steering orders generated by the guidance receiver can be effected, and hence the spiral trajectory depends on the stiffness of the overall missile servo as well as on the misalignment of the axes.

As this error occurs after launching, modification of the missile vertical would necessitate extra radio command signals to the missile to initiate precession of the gyro, and this is inconvenient as well as increasing the amount of equipment carried in the missile. Since the radar vertical is defined in the missile by the positive peak of the reference signal the apparent position of the radar vertical may be changed by altering the phase of the reference signal, i.e., by varying the point in the conical scanning cycle at which the positive peak occurs. The axis misalignment is computed at the launcher and the phase of the reference signal as transmitted by the guiding beams is corrected by the amount of the computed misalignment. This correction is most important since not only does this error reduce the missile range but the stability of the overall missile servo is affected and loss of control can easily result.

Broadcasting Stations Guide

THERE are now well over 1,000 v.h.f. sound broadcasting stations in Europe and most of these are listed in order of frequency in the 12th edition of our book "Guide to Broadcasting Stations" just published. This edition, which has been completely revised, also lists all the major television stations on the Continent as well as giving operating characteristics of Europe's long- and medium-wave stations and over 2,000 short-wave broadcasting stations of the world. The long-, medium- and short-wave stations are listed both geographically and in order of frequency.

Also included in the 112 pages of this enlarged edition, costing 3s 6d, is standard time throughout the world, international allocation of call signs, a wavelength-frequency conversion table and other useful information for the broadcast listener.

Mobile-Receiver Alignment Equipment

DEVELOPMENT OF SPECIAL SIGNAL GENERATORS

By J. F. GOLDING*

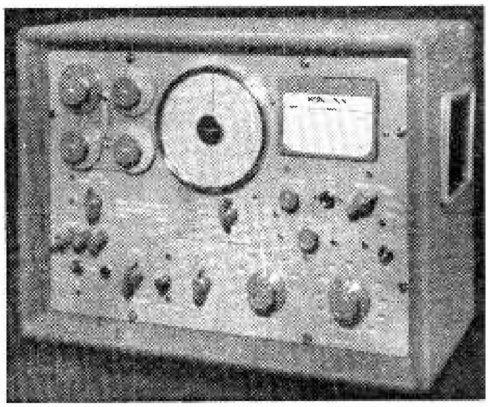

Marconi Instruments Type TF995A/5 f.m./a.m. signal generator.

THE primary problem arising from the continuing increase in the number of mobile-radio operators is that of congestion of the available bands of frequencies. Two possible solutions to this problem are the reduction of channel spacing and the use of hitherto unallocated frequency bands. Both of these solutions are being exploited; the allocated frequency bands and the specified channel spacings in Great Britain and the United States are shown in Tables I and II respectively.

TABLE I

Mobile-radio Frequency Allocations in Great Britain

Classification	Frequencies (Mc/s)	Channel Spacing (kc/s)
General Land Mobile (low band v.h.f.)	71.5–72.8 76.95–78.0 85.0–86.7 86.95–88.0	25 25 25 25
Police, Fire, Ambulance	80.0–84.0 95.0–100.0	100 100
Marine v.h.f.	156.0–165.0	50
General Land Mobile (high band v.h.f.)	165.0–173.0	50
General Land Mobile (u.h.f.)	460.0–470.0	100

TABLE II

Mobile-radio Frequency Allocations in the U.S.A.

Classification	Frequencies (Mc/s)	Channel Spacing (kc/s)
Land Mobile (low band v.h.f.)	27.51–28.0 29.71–49.98	40 40
Land Mobile (high band v.h.f.)	152.03–156.21 157.53–161.79	60 60
Marine v.h.f.	156.3–157.4 161.9 and 162.0	50
Land Mobile (low band u.h.f.)	452.05–459.95	100
Land Mobile (high band u.h.f.)	890.0–960.0	—

In Great Britain all land-based mobile systems, with the exception of certain of the police forces, employ amplitude modulation. Marine (shipborne) radio uses frequency modulation, and aeronautical mobile radio uses a.m.—both by international agreement. In most other countries frequency modulation predominates for all mobile radio except, of course, aeronautical.

It is outside the scope of this article to discuss the merits and demerits of either type of modulation. Indeed, it has become evident that the type of modulation used has very little effect on the special requirements of the mobile receiver as they affect the signal generator design. These special requirements appear as secondary problems arising from the steps taken to overcome the primary problem of congestion.

The most important special requirement is that of adequate suppression of adjacent-channel interference. A mobile station may well be operating physically close to a transmitter of some other system; and unless there is sufficiently good rejection of the strong signal from this transmitter, the wanted signal may be masked by interference. At the same time it is obvious that the receiver bandwidth must accommodate not only the modulated signal; but also the combined permitted drift of the receiver and transmitter.

The narrow receiver bandwidth mandatory to close channel spacing produces a further requirement for accurate tuning and high stability, a requirement which is met by using crystal-controlled local oscillators. Most mobile receivers are of the double-superheterodyne type using a comparatively low second intermediate frequency; so there is little likelihood of drift in the i.f. amplifier causing any appreciable change in the tuning frequency of the receiver. Nevertheless, the i.f. amplifier must be accurately aligned to the correct frequency: the reason for this will be pointed out later.

These requirements have two common effects on the design of signal generators; a very high order of stability is required, and the output must be free from unwanted modulation—either a.m. or f.m. Very naturally, the purpose of the signal generator also influences its design to a considerable degree; and, in this connection, signal generators can be divided into two main categories—those intended for routine maintenance and service, and the more elaborate instrument intended for acceptance tests and design measurements.

Of the second category the most stringent requirements are those introduced to produce a signal

* Marconi Instruments Ltd., St. Albans.

generator capable of measuring adjacent-channel rejection. For this reason the method of measurement is outlined together with a brief description of a suitable signal generator.

Adjacent-channel Rejection Measurements

Assuming that the stability of a f.m. mobile-radio system is the same as that of its a.m. counterpart, the inherently lower sensitivity of the f.m. receiver to adjacent-channel interference is largely offset by its necessarily wider bandwidth. In practice, it has been found that similar adjacent-channel-rejection performance can be expected for the two types of modulation. For this reason the requirements laid down by the G.P.O. in the U.K. can be regarded as being largely representative of common practice in congested areas throughout the world.

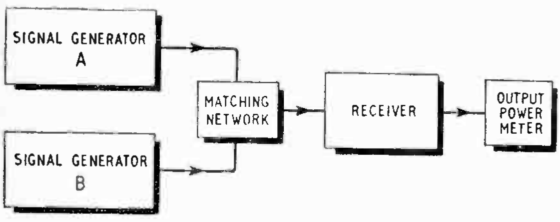

Fig. 1 Block schematic diagram of two-signal method of measurement of adjacent-channel-rejection ratio.

Single-signal Method of Measurement.—Originally the rejection ratio was determined by plotting the frequency-response characteristic of the receiver using a single signal generator and comparing the response at the centre of the acceptance band with the response at the centre of the adjacent channel. But the figures obtained in this way are not very realistic; for, when the receiver is in the presence of a strong unwanted signal—such as that produced by a nearby transmitter of another system—the early stages of the receiver may become overloaded. Receiver "blocking" can reduce sensitivity whilst not altering materially the noise level so giving an effect similar to a weak signal and poor signal-to-noise ratio. Thus the interference actually produced can be worse than is indicated by the single-signal response measurement.

Two-signal Method.—A standard method of measurement has been evolved: this uses two signal generators. The output of one signal generator represents the wanted signal and that of the other represents the interfering signal. The two signal generators are connected, via a matching network, to the input of the receiver as shown in Fig. 1. Signal generator "A," delivering the "wanted" signal, is tuned to the centre frequency of the receiver's acceptance band. Signal generator "B" is set to a frequency separated from that of "A" by slightly less than the channel spacing. A predetermined level of modulation is applied to both signals—either a.m. or f.m. as appropriate—a different modulating audio frequency being used for each of the signal generators in order that the wanted component may be distinguished from the interference component in the receiver's output.

With the output of signal generator "B" reduced to zero, the output of signal generator "A" is adjusted to give a signal-to-noise ratio of 10 dB. The output level of "B" is then increased until the signal-to-noise ratio is reduced by 3 dB, the interference breakthrough from signal generator "B" being deemed part of the noise. The adjacent-channel-rejection ratio is then equal to the ratio of the output levels of the two signal generators.

This is the method of test approved by the G.P.O. for mobile receivers: a rejection ratio of 70 dB[1] is required.

Signal Generator.—Until recently, much difficulty was experienced in making this type of measurement at v.h.f. due to the impure outputs of available signal generators. It is not difficult to appreciate that, if the output of signal generator "B" contains components within the ideal acceptance band of the receiver, the rejection ratio will appear to be less than the true figure. So it is important that the suppression of any such components should not be less than the required rejection ratio of the receiver.

These unwanted components are caused in various ways. Random noise may originate in the oscillator or subsequent stages of the signal generator. If amplitude modulation is used, harmonic distortion of the modulating waveform may produce high-order sidebands outside the channel bandwidth. Such sidebands can also be caused by microphony, which effectively produces both a.m. and f.m.

Good short-term stability is also essential. Although the carrier frequencies are in the v.h.f. range, it is necessary to maintain the tuning to within a few per cent of the channel width. In other words, for reliable measurement, facility for tuning in small increments with an accuracy of a few hundred c/s is necessary. So it is evident that, at the higher frequencies used, the maximum drift that can be tolerated is of the order of 0.0025% of the carrier frequency during the time taken to make a measurement—say 10 min.

These essential requirements for high stability and purity are, in general, not met by the standard type of v.h.f. signal generator. Therefore Marconi Instruments, Ltd., developed a special narrow-deviation version of their f.m./a.m. signal generator—type TF 995A/5—which is suitable for these acceptance tests and laboratory measurements on mobile receivers. This signal generator and the problems that led to its development are described in some detail elsewhere[2, 3]. It is a signal generator of the type employing a single-range oscillator followed by a series of harmonic-multiplier stages. The basic electrical arrangement of both signal generators is shown in Fig. 2.

There are several v.h.f. signal generators of this basic form available, a form which is very suitable for general v.h.f. work. Not only does the arrangement permit the use of the reactance-valve type of frequency modulator; also, due to the application of amplitude modulation to an output stage which is virtually isolated from the oscillator, an a.m. signal can be produced which is sensibly free from f.m. Furthermore, the frequency modulator of an f.m. signal generator offers a convenient means of providing a calibrated fine frequency control by the application of a variable direct-potential bias.

The TF 995A/5 signal generator employs a variable oscillator covering the frequency range 4.5 to 9.16 Mc/s. This is followed by a frequency-trebler stage and three doubler stages in cascade. Range switching is accomplished by selecting the output of the appropriate multiplier and feeding it to the resistive output attenuator. These stages produce four 2:1 frequency ranges covering from 13.5 Mc/s to 216 Mc/s, and an i.f. range covering 1.5 Mc/s to 13.5 Mc/s is provided by beating the output from the first doubler stage with that of a fixed frequency 30-Mc/s oscillator.

A very high order of frequency stability is another requirement; this has been met by the use of temperature-compensated components and the drift has been reduced to 0.002% in a 10-min interval.

Random noise in the r.f. oscillator is inversely proportional to the Q of its tuned circuit. This is inevitably reduced to some extent by the loading of the reactance valve. However, the maximum deviation required for mobile-radio use is 15 kc/s, compared with 75 kc/s for general purpose use; and advantage has been taken of this reduction in maximum deviation to reduce the coupling between the reactance valve and the oscillator, so achieving an improvement in circuit Q. This improvement, together with the use of low-noise valves, has reduced the random noise to a level well below the maximum permissible.

The instrument is equipped with a special directly calibrated incremental-tuning arrangement comprising a switched potentiometer for coarse adjustment of frequency and a continuously variable fine control. There is also an uncalibrated fine-tuning control which varies the screen-grid potential of the oscillator itself. This control enables the operator to tune accurately to the centre frequency of a receiver's acceptance band with the incremental tuning controls set to zero. A simplified diagram of the tuning arrangements is shown in Fig. 3.

These facilities are of considerable importance when the instrument is used for the two-signal method of measurement. In order to tune the signal generator to the "interference" or adjacent channel frequency, the operator first tunes accurately to the receiver frequency and then changes the signal generator frequency by the specified separation, using the calibrated incremental controls. This would be very difficult without the special incremental tuning system.

In order to meet the requirement that the "interference" signal should be modulated at a different audio frequency from the "wanted" signal, the Marconi TF 995A/5 gives the choice of three switch-selected modulating frequencies. Attention has been given to the purity of the modulating waveforms to prevent high-order sidebands on a.m. and the f.m. content is naturally very small.

General Maintenance of Mobile Receivers

In signal generators for the general maintenance of mobile receivers the requirement for a high-

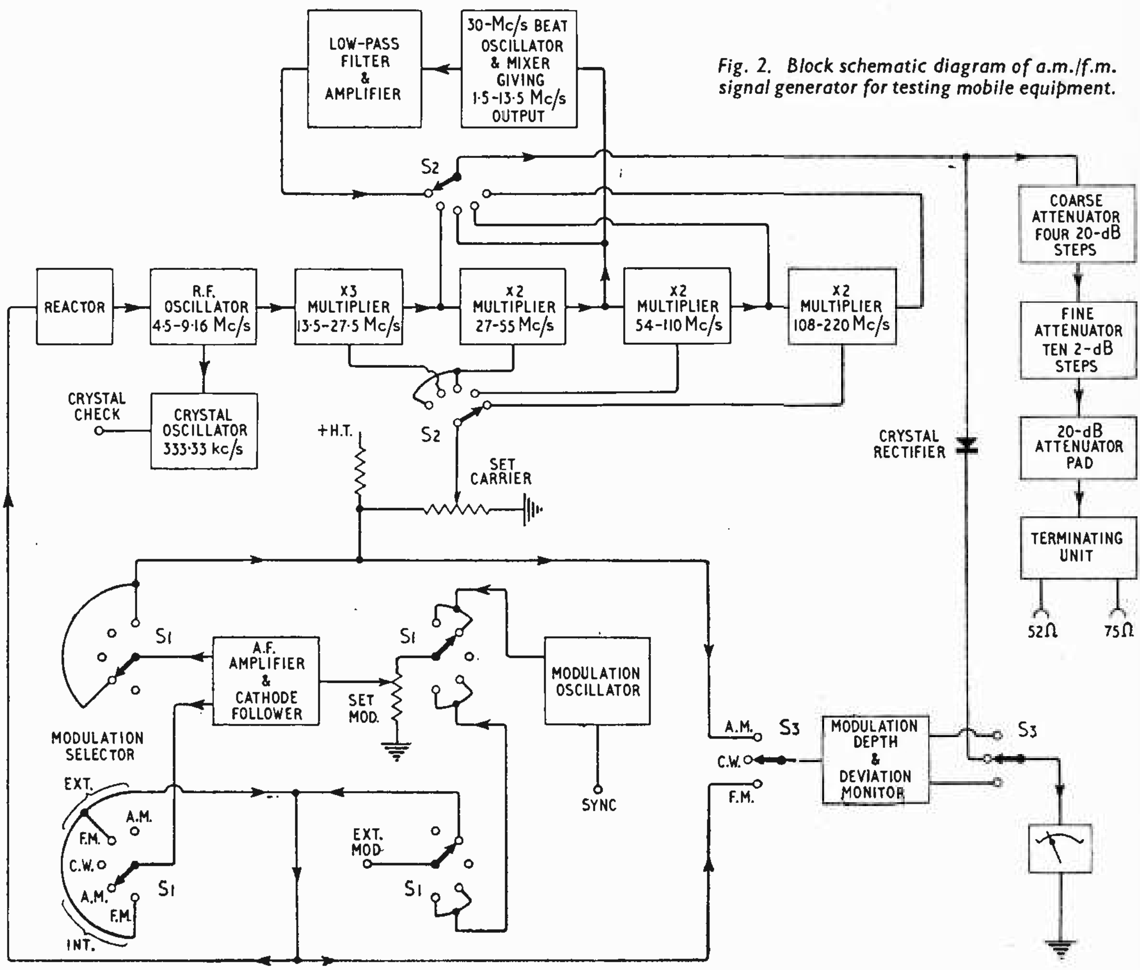

Fig. 2. Block schematic diagram of a.m./f.m. signal generator for testing mobile equipment.

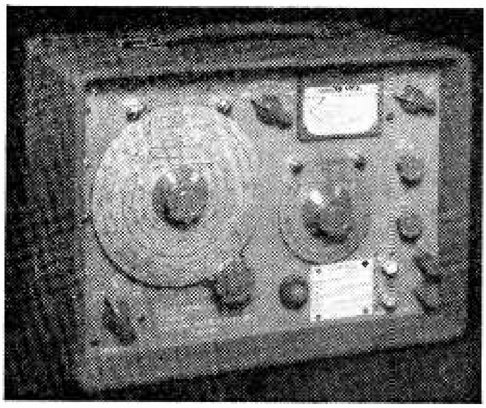

Marconi Instruments signal generator Type TF 1064/2 for the servicing of mobile receivers.

purity output is rather less stringent than for the acceptance-test type of instrument. The necessity for high stability, however, remains. For general maintenance purposes the operator of mobile radio equipment requires a rather simpler and less expensive signal generator than that used for acceptance tests, so that the demand is for an economically-priced instrument with the special features necessary for the testing of narrow-band mobile receivers.

It is well known that high stability can be achieved in a restricted-range variable-frequency oscillator which has no switched r.f. connections i.e. the tuned inductor is soldered directly to the tuning capacitor. Accordingly, several manufacturers have adopted the principle of producing a series of single-range signal generators, each covering a narrow band of frequencies. This principle is particularly applicable to mobile-radio servicing owing to the allocation of discrete, comparatively-narrow frequency bands for this type of communication.

The development of the ferrite modulator and semiconductor techniques for frequency modulation has permitted the direct generation of f.m. signals at u.h.f. and v.h.f. without the use of frequency-multiplier stages. The design of these single-range signal generators is thus simplified with consequent reduction in cost.

An aspect of the alignment of mobile receivers which requires particular attention is the precise tuning of the i.f. amplifier. For, with crystal-controlled local oscillators, the correct tuning of the receiver ultimately depends on the tuning of the i.f. amplifier. There is, therefore, a distinct advantage in the use of a crystal-controlled test oscillator for i.f. alignment.

A crystal-controlled oscillator operating at the i.f. also provides an extremely convenient means of accurately setting the signal generator to the correct centre frequency of the receiver's acceptance band, even though the receiver may be misaligned so that this does not correspond to maximum response. The output of the signal generator is applied to the aerial-input socket of the receiver in the usual way; and the output of the crystal-controlled test oscillator is loosely coupled to the i.f. amplifier. When the signal generator is accurately tuned to the receiver, the i.f. signal due to the r.f. input passing through the frequency changers beats with the loosely coupled i.f. test signal to produce an audible note in the receiver's loudspeaker (with f.m. receivers, the limiter is seldom good enough to suppress this beat note completely). Adjustment of the signal generator tuning for zero beat gives a maximum possible tuning error equal to the combined maximum errors of the crystal-controlled test oscillator and the crystal-controlled local oscillators of the receiver.

Catering for Several Bands.—Where various different mobile systems are serviced in the same establishment these single-range instruments are somewhat inadequate, and there is a demand for an inexpensive signal generator which possesses the necessary stability and covers a number of mobile-radio bands. Such an instrument is virtually a combination of several narrow-range signal generators housed in the same case and, of course, utilizing some common components.

The Marconi v.h.f. signal generators of the TF 1064 series conform to this description; they also include built-in crystal-controlled i.f. test oscillators. These instruments, which are basically similar, have three separate and independent r.f. oscillators covering respectively the high and low v.h.f. bands and the low (450 to 470 Mc/s) u.h.f. band. The electrical arrangement is shown in Fig. 4. This instrument is described in detail in an article by its designer[4].

Each of the two v.h.f. ranges is covered by a fundamental-frequency oscillator using half of a double-triode valve. Frequency modulation and incremental frequency shift are achieved by a ferrite modulator which is common to the two ranges.

The u.h.f. signal is derived from a frequency trebler. It has been found that the frequency sta-

(*Continued on page* 79)

Fig. 3. Simplified circuit diagram of tuning arrangements in Type TF.995A/5 signal generator. Left hand pair of controls are incremental adjustments, right hand pair are "set carrier frequency" fine control and main coarse tuning control.

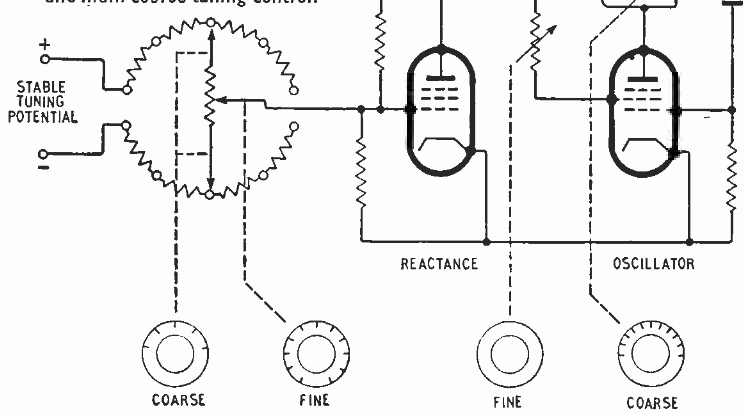

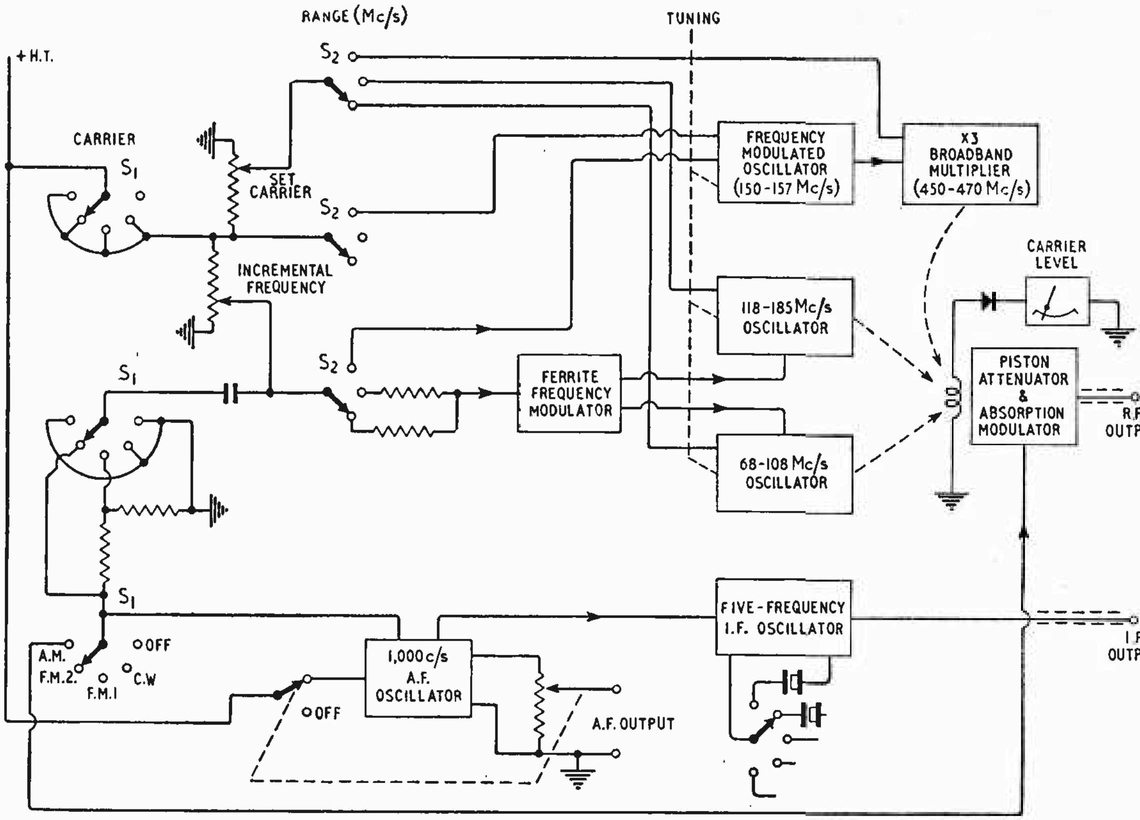

Fig. 4. Block schematic diagram of special signal generator for checking of mobile-radio receivers.

bility of lumped-circuit oscillators is generally poor at frequencies much above 200 Mc/s: for this reason, the u.h.f. range operates from an oscillator covering the band 150 Mc/s to 156.7 Mc/s. This oscillator feeds a double-triode push-pull trebler with a low-Q broad-band fixed-tune anode circuit. Frequency modulation and incremental frequency shift are produced by anode modulation of the oscillator valve and the limiting action of the trebler eliminates the small a.m. component.

The three sections of a standard three-gang variable capacitor act as tuning capacitors for the three oscillators. The outputs of the three sources are applied to a common piston attenuator. Frequency-range changing is achieved by the switching of the h.t. supply to the oscillator covering the selected range.

The crystal-controlled i.f. test oscillator is a completely separate unit housed in the same case. A switch selects any one of five crystals; these crystals fit into sockets at the rear of the instrument, the actual crystal frequencies being predetermined to suit the operational equipment with which the signal generator is to be used.

Future Developments

The special signal-generator techniques that are being developed for mobile-receiver testing illustrate one aspect of the continuous demand for new types of test gear as progress is made in the operational equipment.

In the U.S.A. mobile-radio frequency allocations have been made in the 890-Mc/s to 960-Mc/s band. At these frequencies, the signal-generator technique is noticeably different from that at low frequencies. The lumped-circuit type of oscillator is not very satisfactory; and signal generators tend to be rather elaborate mechanically, utilizing resonant-line oscillators and special valves.

REFERENCES

1. G.P.O. Specification W6187, W6188 and W6130.
2. "An F.M./A.M. Signal Generator Specially Designed for Testing Mobile Radio Equipment," by J. C. Hill, *Marconi Instrumentation*, Vol. 6, No. 7, p. 187.
3. "Signal Generator Design Occasioned by Mobile Radio Services Expansion," by L. R. Head, *Marconi Instrumentation*, Vol. 6, No. 8, p. 228.
4. "New Test Equipment for Mobile Radio," by J. M. Parkyn, *Marconi Instrumentation*, Vol. 5, No. 8, p. 201.

BATTERY SUBSTITUTE

IN *Murphy News* for December 1959 D. Lee describes the "battery substitute" or power supply which Murphy Radio Ltd. use for production tests on transistor receivers. To avoid damage should the output be short-circuited a current limiter is incorporated in the compound-emitter-follower output stage. The limiter consists of a resistor in series with the emitter of one output transistor, and a junction diode joins the "output side" of this resistor and the transistor base. If a large current is drawn the p.d. across the diode causes it to conduct: this "freezes" the base/emitter potential, so limiting the output current to a safe value. Also the high resistance of a run-down battery may be stimulated by a series resistor.

LETTERS TO THE EDITOR

The Editor does not necessarily endorse the opinions expressed by his correspondents

"Wien Bridge Oscillators"

MR. HICKMAN'S treatment (December 1959 issue) is almost perfect so far as it goes, but I fear he has based his article upon experience of building a fixed-frequency oscillator possibly with power from d.c. sources. Having for my own interest once built an a.f. oscillator, admittedly of the phase shift type, covering 5-100,000c/s, I feel he might well issue a warning and general advice.

The same basic problems of avoiding unwanted phase shifts and spurious couplings arise, as well as the desirability of feeding the frequency-determining networks from low-impedance sources. Attention seems to be called for to these matters.

(1) Power supply. Ripple or heater leakage, etc., can lead to interaction at 50c/s and harmonics.

(2) Power supply. Impedance of h.t. source can cause serious trouble, and even at 50c/s a regulated source seems desirable if variable frequency working is called for.

(3) Coupling of amplifier to Wien Bridge. This capacitor obviously has its influence by introducing a phase shift. Over wide-range working it will need to be switched, because otherwise the effect of capacity to earth will be important. For precision work electrolytics are out, so size becomes physically troublesome.

(4) Other stray capacitance and loading effects, mainly at the h.f. end, call for the lowest possible circuit impedances and cathode follower output, but this of course aggravates (3).

In my case I used 1% tolerance switched capacitors for hand switching, with variable resistance for fine control in steps of 1, 3 and 10. It was not possible to obtain accurate scale matching for each range without considerable attention to the above matters, and, in fact, unless one is content with a frequency accuracy of 5% at the extremes, it is ridiculous to rely upon accuracy of bridge components. C.R.O. checking is required, but this breaks down rather beyond a few kc/s owing to the difficulty of determining the multiple of 50c/s in question. Probably the best system is a circular display from 50c/s with grid brightening from the oscillator, but an auxiliary oscillator is called for to work beyond a few kc/s to the 100kc/s mark. Such methods, carefully used of course, are good to 0.1%, which is no doubt your contributor's goal, but they do show up no end of imperfections in the design. Incidentally, before I am attacked I would point out that I know well that variable resistance control has its own problems since the potentiometers must be wire-wound components possessing by no means negligible inductance and stray capacitances. The alternative of variable condensers and switched resistances for range multiplying leads to high circuit impedance and hum pick-up. It seems to be a case of finding the lesser evil!

London, N.W.11. L. STREATFIELD.

The author comments:

I am most grateful to Mr. L. Streatfield for the points which he raises in connection with, in particular, the difficulties associated with the design of Wien bridge oscillators to cover wide frequency ranges. Such considerations should certainly be borne in mind when dealing with variable frequencies.

With regard to power supplies, I would agree that good stabilization and freedom from hum are certainly desirable qualities, but may I point out that the effects of power supply variations and hum are both considerably reduced by negative feedback.

In practice the choice of gain factor for the amplifier must be a compromise; to reduce the effects of coupling time constants the gain should be large in order to allow a large amount of negative feedback to be applied, but in order to reduce the effects of stray couplings such as hum, etc., the gain should in fact not be too large. These considerations apply equally for any high-gain feedback amplifier and therefore, in general, the same precautions are applicable, such as hum bucking or, if necessary, use of d.c. heater supplies and screening of high-impedance bridge components. D. E. D. HICKMAN.

"Alternatives to the Wien Bridge"

I SHOULD like to comment on the article by J. F. Young which appeared in your issue of February 1959.

The article is of considerable interest but, unfortunately, the author did not review the case[1] when $n>1$, and thus a condition contrary to that described in the article (Fig. 7). The increase of damping which takes place when $n>1$ is not of great importance, because it can be easily compensated by the amplifier. It is clear

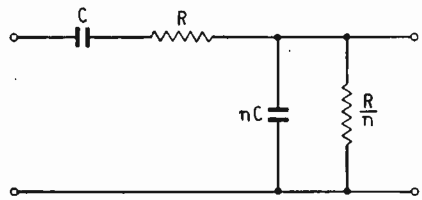

that the increase of selectivity can be attained for $K=0$ (Fig. 10).

With great interest from a constant reader of your journal.

E. KUCHIS,
Institute of Physics & Mathematics,
Academy of Sciences of L.S.S.R.

Vilna,
Lithuanian S.S.R.

[1] T. Zagalewski. Optimum Parameters for RC Generator in Wien Bridge, *Archiwum Electrotechniczne* (Polish), 1958, Vol. 7, No. 2, pages 273-288.

Crystal Oscillator Pulling

THE division of crystal oscillator circuits on page 534 of the December 1959 issue contains errors which may mislead some readers. In particular S/Ldr. de Visme states that the amount by which the frequency may be pulled is f/Q, and thus implies that it depends on Q. The circuit he shows, however, is the Pierce (1923) circuit, the pulling conditions for which were described in *Wireless Engineer* (June 1941). In this paper it is shown that the pulling range is limited by the ratio of capacitances in the conventional representation of the crystal, a ratio which is always degraded by external circuit capacitances. Certainly ranges of a good deal more than f/Q can be obtained, for the limit of the ratio of capacitances is below 200, rather than over 20,000.

The alternative circuit with the crystal connected between anode and grid is analysed in a similar manner to that of the reference above by J. Coulon in a Toulouse University doctorate thesis, March 1948 (C_3 is incorrectly labelled in Fig. 1).

London, W.8. H. JEFFERSON.

The author comments:

I am much indebted to Mr. Jefferson for pointing out my error in saying that the greatest degree of mistuning possible is of the order of f/Q.

The error arose from confusion in my mind between the response of a tuned circuit to a forcing frequency other than its resonant frequency—"pulling"—which naturally depends on the circuit Q, and the very different case of directly altering the reactive parameters of a self-oscillating circuit, thereby tuning it.

Taking the minimum possible crystal shunting capacity as about 180 times its equivalent series capacity, the frequency of oscillation of a loss-free crystal can be tuned through a range of $f/360$, corresponding to a change in shunt capacity from its minimum value to infinity. For f equal to 1 Mc/s, this comes to 2.8 kc/s. In fact, I was able to tune the crystal used in the calibrator through about 500 c/s; the difference between the two figures must be attributed mainly to additional capacitive shunting imposed by the associated circuit.

G. DE VISME.

Inexpensive Photographic Timer

I NOTED with interest the ingenious circuit offered by your correspondent K. Hardisty in the December 1959 issue, whereby clean operation of the relay is obtained.

By the addition of a voltage stabilizer valve (85A2) to the original circuit (August 1958 issue) as shown in the sketch, a similar result is achieved, and calibration of the timing ranges is scarcely affected. As a result of this modification, most types of relay become suitable, including some which previously had a tendency to chatter. Further, the timing period becomes more precise.

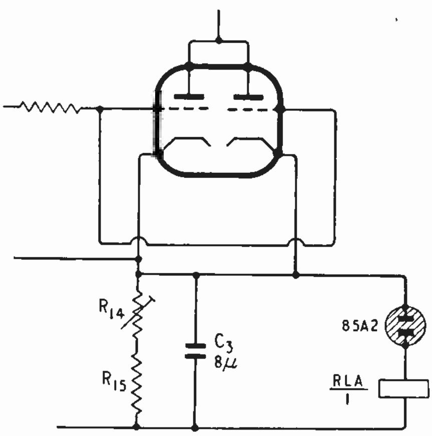

Among relays successfully tested in this system are:

(a) The original Siemens h.s. relay with a 1,700+ 1,700Ω coil;

(b) a P.O. type—600 relay with 5,000Ω coil;

(c) a P.O. type—3,000 relay with 6,000Ω coil.

Lower resistance coils for the above relays may be suitable, but were not available for test.

Harrow. J. H. JOWETT.

[Mr. Hardisty has asked us to point out that the relay contact RLA/2 in his diagram should have been shown as normally closed. The sequence of operations is: 1—push-button operated, 2—capacitor discharges, 3—neon-lamp extinguishes and relay releases, 4—RLA/2 opens and capacitor begins to re-charge, 5—push-button released. As in Mr. Jowett's design, the enlarger lamp is off (RLA/2 open) when the relay is energized.—Ed.]

"Servicemen's Pay"

ON page 540 of your issue for December, 1959, you publish details of an agreement between the R.T.R.A. and a body called the Association of Radio and Electronic Engineers.

No intelligent television service engineer will be impressed by the published terms of this so-called agreement. First, because the rate of pay for a man who has served a five-year apprenticeship is under rate by £1 15s 2d in the provinces and £1 6s in the London area compared with E.T.U. agreements in England and Scotland*.

Secondly, by its emphasis on the possession by radio and television engineers of the R.T.E.B. certificate, the agreement fails to face up to the fact that the overwhelming majority of skilled television servicing is carried out by highly skilled but, nevertheless, uncertificated engineers†.

This is due to the rapid growth of television and the continued refusal on the part of the Radio and Television Retailers' Association, and the industry, to face up to the need for proper industrial relations and an adequate apprenticeship and training scheme.

Striking evidence of the refusal on the part of the R.T.R.A. to face realities and negotiate with the Electrical Trades Union was to be seen at this year's Radio Exhibition where the R.T.R.A. stand displayed literature advertising a Joint Apprenticeship Council for the industry and proclaiming that the employees were represented on that body by the Guild of Radio Service Engineers, a body (according to the report of the Registrar of Friendly Societies) that has not got a single member and that has ceased to function as a trade union for more than five years.

This Association of Radio and Electronic Engineers represents the latest effort on the part of the R.T.R.A. to offset the growing television membership of the Electrical Trades Union, and consequently its justifiable claims for recognition as the appropriate body to represent the interests of television engineers.

Television service engineers will be all the more reluctant to place much confidence in the claims of the A.R.E.E. to represent them when they learn from the Registrar of Friendly Societies that its contribution income for 1957 was £29 for a total membership of 32. In 1958, however, they claimed a membership of 285, but, strangely enough, they only produced an income of £28 11s 6d.

Other useful information available in the Registrar's report disclosed the fact that neither in 1957 nor in 1958 did this organization engage in any expenditure on benefits, wages, rent or working expenses, in spite of the fact that it has a General Secretary and a registered office at 17, Tottenham Court Road, London, W.1 (just round the corner from the R.T.R.A.'s office).

A. C. BATCHELOR,
National Officer, Electrical Trades Union.
Hayes, Bromley, Kent.

* It is learned on enquiry from the Electrical Trades Union that the R.T.R.A./A.R.E.E. rate is here compared with "the national minimum rate [£13 2s 6d] established under the E.T.U. agreement with the Electrical Contractors' Association of Scotland." Reference was made in the Report to the Union's 1959 Policy Conference to the need for "the laying down of a minimum rate of pay for radio and television service engineers."

† The R.T.R.A./A.R.E.E. rate for a certificated television service technician is above the minimum basic E.T.U. rate by 5s 2d in the provinces and 16s 2d in London.—Ed.

Editors and Editing

I WAS interested to see your comments in the January issue on my letter on editors and editing. You will see that I have taken to heart your comment No. 4 about capital letters for common nouns and have addressed this letter to the editor of "wireless world," although I regret to notice that in your comment No. 10 you have yourself suffered a lapse. Comment No. 8 has enlightened me on many points—I had not previously realized that sub-editing is carried out by dull mechanics.

Comment No. 5 illustrates very well the sort of thing I am often up against. I don't use words that I don't know the meaning of, but I often find that editors think they know what I mean better than I do myself.

Finally, your suggestion in comment No. 6 makes me shudder. The style is the scientific equivalent of the officialese that Government Departments are continually bombarding us with, and although the sentence is finite I find it difficult to comprehend as a whole.

Chelmsford. R. A. WALDRON.

THE SMITH CHART

2.—Effects of Load, Input Impedance and Matching on Transmission Lines

By R. A. HICKSON*

(*Continued from page 9 in the January issue*)

IT was explained in the first part of this article how the Smith chart is derived. We can now turn to a consideration of some of its principal applications in connection with transmission lines and aerial systems.

Effect of Load on Transmission Line.—(*i*) *Magnitude and Phase Angle of Reflection Coefficient at the Load.*—Given Z, locate it on the chart and draw a line from the centre through the point to the edge. The distance of the point from the centre, transferred to the reflection coefficient scale, gives the magnitude. The phase angle is read from the scale round the edge.

Given y, locate it on the chart and draw a line from the point through the centre to the edge of the chart. The distance of the point from the centre, transferred to the reflection coefficient scale, gives the magnitude. The phase angle is read from the scale round the edge.

Example (*a*).—A load of 45 + j30 ohms is connected to a 75-ohm line.

$$z = \frac{Z}{Z_0} = \frac{45 + j30}{75} = 0.6 + j0.4$$

(Point A Fig. 11). From this it can be seen that the reflection coefficient is 0.34 (+121°).

Example (*b*).—A load of 0.02 − j0.03 mho is connected to a 50-ohm line:

$$y = \frac{Y}{Y_0} = \frac{0.02 - j0.03}{0.02} = 1 - j1.5$$

(Point B Fig. 11). It can be seen that the reflection coefficient is 0.60 (+127°).

(*ii*) *Voltage Standing Wave Ratio.*—Given z or y, locate it on the chart and draw an arc of a circle centred on the centre of the chart moving clockwise from the point. The arc will cross the pure resistance axis at a normalized resistance equal to the v.s.w.r. at the load.

The v.s.w.r. at any point along the line may be obtained by moving towards the centre of the chart by an amount indicated by the "Effect of Line Attenuation" scale.

Example.—Load = 0.6 + j0.4 (normalized); v.s.w.r. at load = 2.05 (Fig. 12). To find the v.s.w.r. at the end of 150 feet of cable having a loss of 4dB/100 feet at the operating frequency. Line attenuation = 150 × 4/100 = 6dB. Moving from 2.05 on the v.s.w.r. scale on to the "Effect of Line Attenuation" scale, 6dB towards the generator on this scale and then back to the v.s.w.r. scale, we find: v.s.w.r. at end of line = 1.18.

Input Impedance of a Transmission Line.—(*i*) *Mismatched Line.*—Given z and l, locate z on the chart and draw an arc of a circle centred on the centre of the chart moving clockwise from the point. The length of the arc, measured on the wavelengths scale, should be l; if l is greater than a half-wavelength, an integral number of half-wavelengths should be subtracted from it. The normalized input impedance is indicated at the end of the arc (Point A, Fig. 13).

The effect of line attenuation may be obtained by moving toward the centre of the chart by an amount indicated by the "Effect of Line Attenuation" scale. (Transmission Loss)

Example.—

Normalized load = 0.6 + j0.4.
Length of line = 30 metres.
Velocity factor = 0.833.
Operating frequency = 209.75 Mc/s.

$$l = \frac{209.75 \times 30}{300 \times 0.833} = 25.17 \text{ wavelengths.}$$

Moving clockwise 0.17 wavelength from 0.6 + j0.4 brings us to 2.05 − j0.03 (Point A). The radial distance of this point from the centre of the chart is transferred to the "Effect of Line Attenuation" scale (Point A′). Assuming that the line loss is 6dB we move six 1-dB steps along this scale to point B′. The radial distance of this point from the centre of the circle, along the line from the centre to point A, gives us point B, the input impedance allowing for line losses. This is 1.2, and has a slight capacitive component (j = − 0.01) but the chart cannot be read to such a degree of accuracy.

(*ii*) *Length of Line Required to Produce a Required Reactance.*—A short-circuited line will have a reactance of zero at the short circuit. The reactance at the input of a short-circuited line may be found by moving round the outside of the chart from the zero point by a distance on the "Wavelengths Towards Generator" scale corresponding to the length of a stub.

Similarly with an open-circuited line, we start at the infinity point and move round the outside of the chart in the same direction.

If the shortest possible line is required, an open-circuited line will be chosen when a capacitive reactance is required and a short-circuited line for an inductive reactance.

The effect of line losses is generally negligible for such short sections of line, producing a resistive component in the input impedance of at most 0.01. More important is the fact that the open or short circuit is not always ideal and may itself contain a resistive component. Fringing effect in open circuits is a cause of this. With balanced lines, a short circuit must extend over an area of dimensions comparable with a wavelength to be effective, and for measurements the most reliable termination is a short circuit on a coaxial line.

(*iii*) *Line Characteristics.*—The procedures described in (*i*) and (*ii*) require a knowledge of the characteristic impedance, attenuation and velocity factor of the

* Belling and Lee Ltd

line. By a converse process we can deduce the characteristics of the line from measurements of the input impedance of a known length of line at six or eight known frequencies: ideally two frequencies would suffice, but, as always, redundancy improves reliability.

Characteristic Impedance.—The normal method for this is to take the geometric mean of the input impedances with the far end of the line first short circuited and then open circuited. These impedances are sometimes made resistive by cutting the line to resonance and/or varying the frequency of measurement. The effect of measurements at resonance is reproduced by means of the Smith Chart, using an arbitrary length of line and a set of arbitrary frequencies. The use of different frequencies allows the input impedance of the line at various electrical lengths to be measured. The frequency band over which measurements are made should be such as to give a change in electrical length of one half-wavelength. A larger band than necessary will introduce changes in attenuation per unit length which must be allowed for in plotting the results (on the basis, attenuation (dB) = $k\sqrt{\text{frequency}}$). The input impedances relative to the measuring system will lie on a circle which crosses the pure resistance axis at points representing a line length of (*a*) an exact number of half-wavelengths (each repeating the load) and (*b*) an exact odd number of quarter-wavelengths (each inverting the load). The line impedance relative to the measuring system is the geometric mean of these two resistance values.

Velocity Factor.—The measured impedances may now be replotted relative to the line impedance, making a new circle centred on the centre of the chart.

The velocity factor is given by:—

$$\text{v.f.} = \frac{\delta F \times L}{\delta l \times 300}$$

where δF in Mc/s is the change in frequency required to produce a change δl in the length of the line in wavelengths, and L is the physical length of the line in metres. The wavelength change δl is determined from the replotted points with the aid of the "Wavelengths" scale.

Attenuation.—The attenuation in decibels of the length of line used is given by the radial distance of the replotted points from the edge of the chart, measured on the "Effect of Line Attenuation" scale.

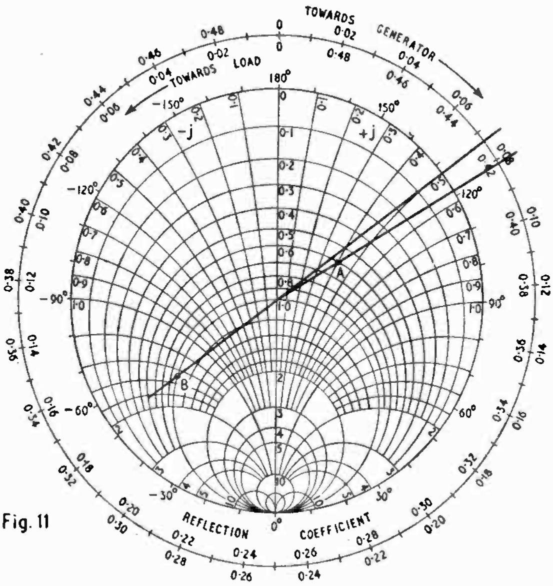

Fig. 11

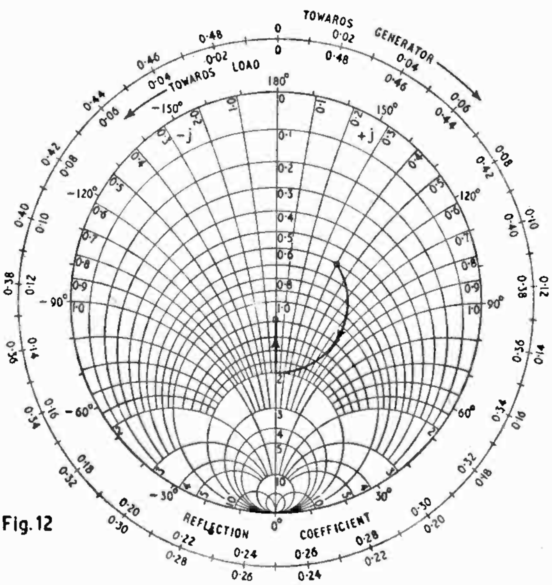

Fig. 12

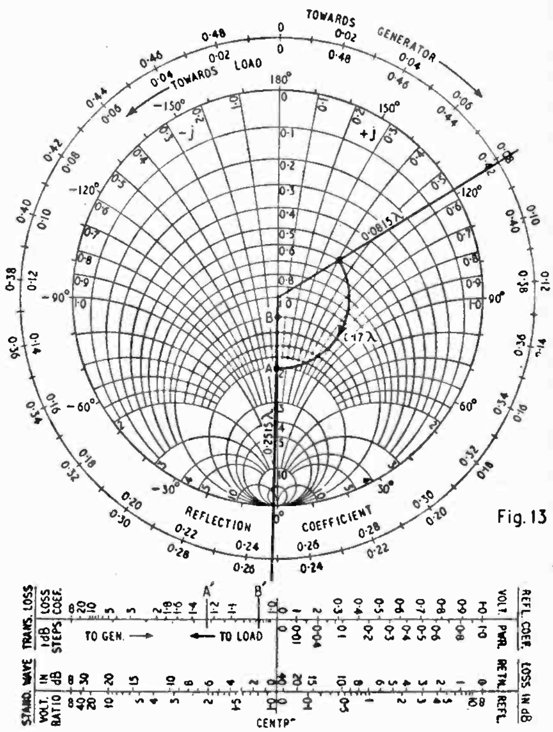

Fig. 13

Fig. 11. Reflection coefficient of an impedance (A) and an admittance (B).

Fig. 12. V.S.W.R. at the generator end of a line.

Fig. 13. Input impedance of a mismatched line: neglecting losses, A; allowing for losses, B.

As an example of the use of the foregoing method we will refer to Fig. 14. Points marked with a cross are the input impedances, relative to 50 ohms of a 14-metre length of short-circuited line. Figures adjacent to each point indicate the frequency in Mc/s. The circle through these points crosses the pure resistance axis at 0.05 and 5.0. The characteristic impedance of the line is therefore:—

$$Z_o = \sqrt{0.05 \times 5.0} \times 50 = 25 \text{ ohms.}$$

The velocity factor is:—

$$\frac{(95 - 88) \times 14}{0.49 \times 300} = 0.67$$

The attenuation is:—

0.85dB per 14 metres
or 1.85dB per 100 feet.

For the most accurate results the loss of the length of cable used should be between 2.5dB and 10dB.

Nature of an Unknown Load.—Using a slotted line, the v.s.w.r. produced by the load may be measured directly, as may the change in position of the standing wave pattern produced by replacing the unknown load with a short circuit. Normally the change in position of a voltage minimum is

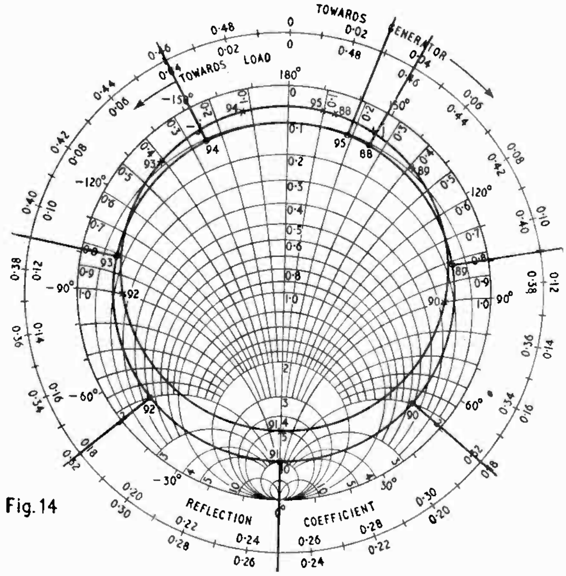

Fig. 14

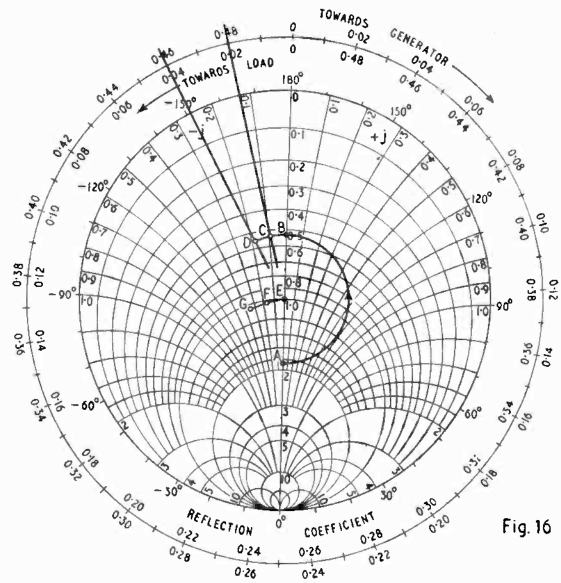

Fig. 16

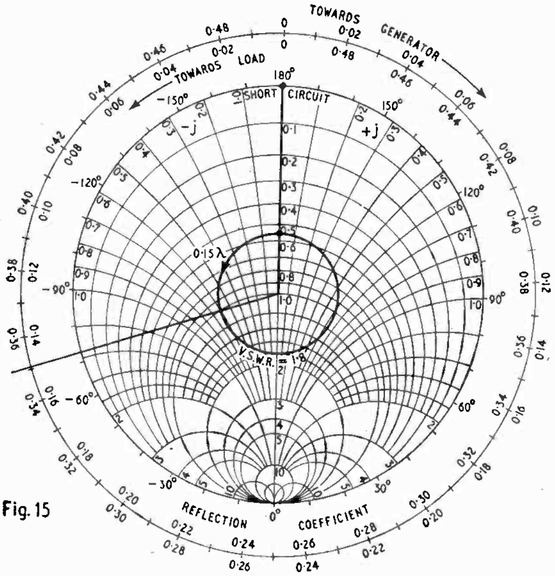

Fig. 15

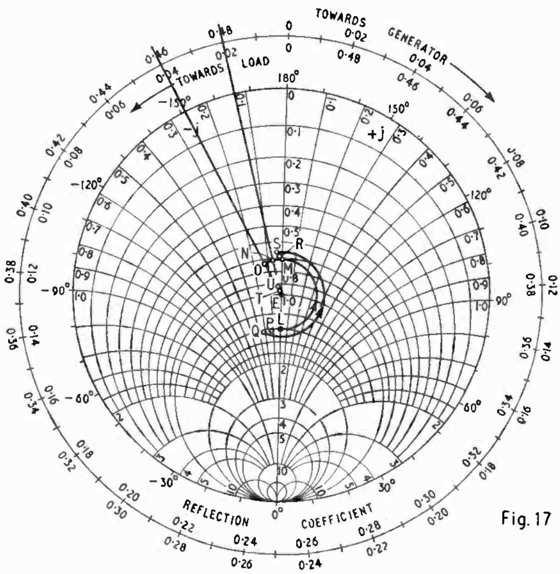

Fig. 17

Fig. 14. Input impedance of a short-circuited line at various frequencies: X = relative to test gear; ⊙ = relative to Z_o

Fig. 15. Slotted-line method for determining load impedance.

Fig. 16. Matching with single quarter-wavelength section.

Fig. 17. Matching with two quarter-wavelength sections, over the same frequency range as in Fig. 16.

chosen, as the minima are sharper than the maxima. The procedure is as follows:—

Measure the v.s.w.r. with the load in place and note the position of a convenient voltage minimum. Replace the load by a short circuit and note the position of new voltage minima, selecting the minimum which is not more than a quarter-wavelength from the first minimum. The wavelength in the slotted line is determined by measuring the distance between adjacent minima, which corresponds to one half-wavelength.

The load lies on the circle corresponding to the v.s.w.r., so this circle is drawn in, using the pure resistance scale or the separate v.s.w.r. scale. Starting at the point where this circle cuts the pure resistance axis at a value less than 1, move along the circle a distance corresponding to the distance moved by the voltage minimum, in the direction (towards the generator or the load) in which the minimum moved when the load was replaced by a short circuit. The point reached represents the load impedance. *Example.*—The indicated v.s.w.r. is 1.8, the distance between adjacent voltage minima is 20cm and the replacement of the load by a short circuit shifts the minima 6cm toward the generator. The shift in terms of wavelengths is $6/20 \times 2 = 0.15$ wavelength (Fig. 15).

Moving this distance toward the generator along the " v.s.w.r. = 1.8 circle " brings us to a load impedance of $1.0-j0.6$. If a 50-ohm slotted line is used the impedance is $50-j30$ ohms.

Matching Two Resistive Impedances.—As shown in the section " Impedance Variations along a Mismatched Line " in Part 1, a quarter-wavelength section of line will match two resistive impedances z_1 and z_2 such that $1/z_1 = z_2$. For example, to match a 300-ohm line to an 80-ohm line, a quarter-wavelength section would be required of such an impedance that $Z_o/80 = 300/Z_o$, i.e., $Z_o = 155$ ohms.

This matching will of course only be correct at the one frequency for which the length of the matching section is exactly a quarter-wavelength. Referring to Fig. 16, Point A represents 300 ohms with respect to 155 ohms. This point is transformed to B at the correct frequency, to C at the frequency for which the line is 0.27 wavelength long and to D at the frequency for which the line is 0.29 wavelength long. These points, when normalized with respect to 80 ohms, become points E, F and G.

The matching may be improved by using two quarter-wavelength sections to change the impedance in two stages. In this case, matching 300 to 155 ohms with a 216-ohm section, and matching 155 to 80 ohms with a 111-ohm section. Referring to Fig. 17, Point L represents 300 ohms with respect to 216 ohms. This point is transformed to M at the correct frequency, to N at the frequency for which the line is 0.27 wavelength long and to 0 at the frequency for which the line is 0.29 wavelength long. These points represent the output impedance of the first section normalized with respect to 216 ohms. To represent the input impedance of the second section they must be renormalized with respect to 111 ohms, when they become points L (again), P and Q respectively. These points are transformed to M (again), R and S, by the 111-ohm section. When normalized with respect to 80 ohms they become points E (again), T and U.

The improvement obtained by use of two sections is apparent: the v.s.w.r. represented by point U is less then 1.1, compared with 1.4 for point G. The use of more sections will give a further improvement, leading in the long run to an infinity long line, the impedance of which changes exponentially. Short tapered sections of line have been used in which the length and character of the taper are usually determined experimentally. Exponential, linear and Gaussian tapers have been used. A recent paper (Ref. 6) contains details of the design of a practical exponential-line transformer.

REFERENCES

[6] S. G. Young. " H.F. Exponential-Line Transformers." *Electronic & Radio Engineer*, February 1959, Volume 36, No. 2, pp. 40-44.

SHORT-WAVE CONDITIONS

Prediction for February

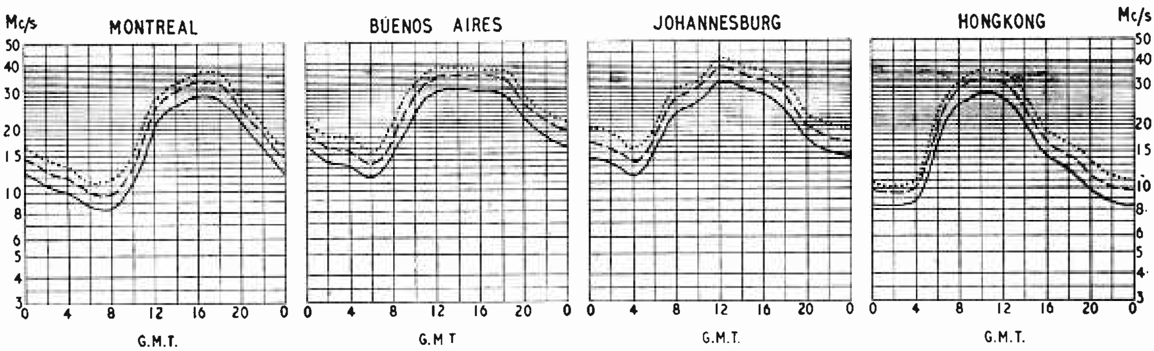

.... FREQUENCY BELOW WHICH COMMUNICATION SHOULD BE POSSIBLE FOR 25% OF THE TOTAL TIME

— — — PREDICTED MEDIAN STANDARD MAXIMUM USABLE FREQUENCY

——— FREQUENCY BELOW WHICH COMMUNICATION SHOULD BE POSSIBLE ON ALL UNDISTURBED DAYS

THE full-line curves indicate the highest frequencies likely to be usable at any time of the day or night for reliable communications over four long-distance paths from this country during February.

Broken-line curves give the highest frequencies that will sustain a partial service throughout the same period.

Tunnel Diode

NEW SUPER-HIGH-FREQUENCY SEMICONDUCTOR DEVICE

A NEGATIVE resistance characteristic which can be made use of at super-high frequencies (>3,000Mc/s) is the main feature of tunnel diodes. These diodes consist of heavily-doped (impurity content as high as $\approx 10^{20}$ atoms/c.c.) p- and n-type regions connected by a very thin ($\approx 10^{-6}$cm wide) depletion layer sometimes called a space-charge region. When a voltage is applied to such diodes from the p- to the n-region (forward bias) the current at first increases with increasing voltage and then, at a potential of a few hundred millivolts, decreases again before finally increasing as in an ordinary conducting diode (see diagram). The region of decreasing

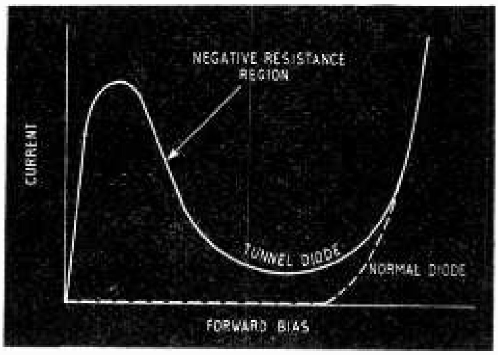

General voltage/current characteristics of tunnel and normal diodes for forward bias voltages (adapted from Fig. 1 of the article by H. S. Sommers et al. *in Part 3 of the* 1959 I.R.E. Wescon Convention Record *(p.3)).*

current corresponds to a negative dynamic resistance. This negative resistance in tunnel diodes was first reported by L. Esaki in *Physical Review*, Vol. 109, p. 603 (1958).

At low voltages, before the normal conduction current level in these diodes is reached, the current is provided by the majority carriers going through a quantum-mechanical process known as tunnelling—hence the name given to these diodes. Using the picture of atomic particles as waves of probability, tunnelling may be looked upon as being due to the fact that the waves of a charged particle can penetrate partially a potential barrier even when the particle does not have enough energy to surmount the barrier. Now a wave on the other side of the barrier represents a finite probability of finding the particle on the other side of the barrier. If and when this probability is realized, and the particle appears on the other side of the barrier even though it did not have sufficient energy to surmount the barrier, the particle is said to have tunnelled through the barrier. Of course, the particle can only tunnel through the barrier if it can fill a vacant energy level on the other side. In the tunnel diode certain energy levels cannot be filled and are said to be forbidden. It is the effect of the applied voltage on these forbidden levels which produces the low-voltage/current characteristic of the tunnel diode. For example, at certain small forward applied voltages, the forbidden levels in the p-region overlap the electron energy levels in the n-region. Thus the electron flow from the n- to p-region is decreased and a negative resistance characteristic produced. To complicate the picture still further, in certain directions relative to the semiconductor crystal lattice structure phonons (ultrasonic vibrations of the crystal lattice) can interact with the electrons so as to assist the electron tunnelling process.

One advantage of tunnel diodes is that they can operate at super-high frequencies (>3,000Mc/s). Since these diodes are majority rather than minority carrier devices, the maximum operating frequency of minority carrier devices (such as the transistor) set by the minority carrier transit time does not apply to tunnel diodes. In the case of tunnel diodes, the maximum operating frequency increases with increasing doping (impurity concentration). Since as the doping increases the impedance decreases, the maximum practical operating frequency of the tunnel diode may be set either by the minimum usable circuit impedance, or by the maximum achievable doping. Such practical considerations are likely to limit operation to below 10,000Mc/s in the case of germanium tunnel diodes, but higher frequencies should be achievable by using other semiconductors such as germanium arsenide as the tunnel diode material. Germanium tunnel diodes have in fact already been made which can oscillate at 4,000Mc/s. Such oscillations can be obtained by biasing the diode to a point on the negative resistance portion of its characteristic and placing it across a resonant circuit. The capacitance in the resonant circuit can be obtained from the tunnel diode junction capacitance, and the inductance, at these high frequencies, from a short length of conducting material. Alternatively, the diode can be placed at a suitable position across a short-circuited transmission line.

Since the tunnel diode characteristic consists of a negative resistance region separating two positive resistance regions, such diodes can also be used as very fast switches, and switching times of less than 1mμsec have already been achieved. Besides their very high maximum operating frequency, another advantage of tunnel diodes is their wide possible range of operating temperature. Tunnel diodes can in fact operate from about 4° absolute up to about 200°C in the case of germanium, or up to about 400°C in the case of silicon diodes. One disadvantage of tunnel diodes inherent in all two-terminal devices is the difficulty of separating input and output circuits. Various aspects of the tunnel diode are described in *Proc. I.R.E.* for July 1959 (p. 1201) by H. S. Sommers, and in papers by H. S. Sommers *et al.* and I. A. Lesk *et al.* in Part 3 of the 1959 *I.R.E. Wescon Convention Record.*

Automatic D.F. Aids Radar Identification

NOW in operation at De Havilland's Hatfield aerodrome are a Marconi Type S232 50-kW 50-cm radar and Automatic Fixer. This latter uses two Type AD200 v.h.f. direction finders, one at Hatfield, the other near Chelmsford (controlled by a v.h.f.-radio link).

The outputs of the two direction finders are fed into the Automatic Fixer which uses a 17-in c.r.t. display covered by a transparent map of the area. When an aircraft calls Hatfield on v.h.f. two traces, which originate from the positions of the d.f. stations and indicate the aircraft's bearing, are produced. These traces intersect at the aircraft position, so enabling the radar-display point to be identified without recourse to an aircraft manœuvre.

Technical Notebook

Handwriting Recognizer, capable of identifying any one of ten words, "zero," "one," "two"... etc., to "nine," written in cursive script, has been devised at Bell Telephone Laboratories. To use the device the words have to be "written" with a metal stylus on an electrode system. Then, when an "Identify" button is touched with the stylus, a light appears beside the numeral corresponding to the word just written. The device examines words as a whole, not by their individual letters. It picks out features of the overall shapes of the words, including the length of word, the dotting of "i's" and the number and position of vertically extended letters such as "h" and "g." The electrode system consists of 15 horizontal metal strips alternately sandwiched between strips of electrical insulating material. Up-an-down movements of the writing stylus gives a sequence of electrical connections with the metal strips. The sequence and number of connections are an indication of which of the ten words has been written. To provide the writer with horizontal guide lines, two of the 15 horizontal bars on the writing surface are made of brass, making a colour contrast with the others, which are copper. The two brass conductors enclose the middle one-third of the writing space, in which the user writes small letters, such as "e" and "n." Vertically extended letters, such as "t" and "g," are carried beyond these limits. The middle bar of the surface is connected to a counter, which gives a rough horizontal location of features. If a recognition feature comes before the

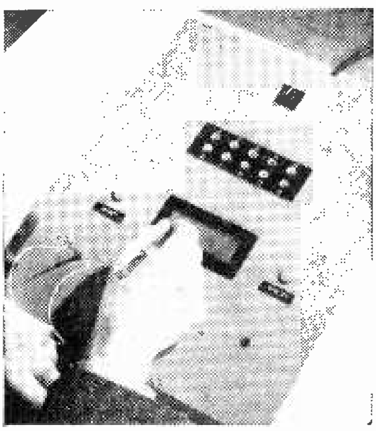

stylus has crossed this middle bar six times the feature is considered to be in the left-hand portion of the word; if later, it is considered to be in the centre or right portion. A logic circuit, consisting of 12 relays and eight diodes, examines each word for six features. These are: a lower vertical extension, as in "g," within the left-hand portion of the word; a lower extension in the middle or right-hand portion; an upper extension, as in "t," in the left-hand portion; the presence of more than one upper-left extension; a large number (more than nine) crossings of the middle bar; and a dotted "i." As examples, "zero" is identified by a lower-left extension; "four" by both upper- and lower-left extensions; "seven" by more than nine crossings of the middle bar. Theoretically, four separate tests for features are sufficient to identify ten words. This system, however, applies two extra or redundant tests to allow for the great variation in writing styles. The accuracy of the recognizer is said to be 97% of words correctly identified in a test of 1,000 words written by 20 people.

Interstellar Communications in the form of radio transmissions from any civilizations that may exist on planets revolving around neighbouring stars may be receivable according to G. Cocconi and P. Morrison in *Nature* for Sept. 19, 1959 (p. 844). Frequencies below about 1Mc/s and above about 3×10^4Mc/s are unlikely to be used for such transmissions either because they are absorbed too greatly in planetary atmospheres or, where this absorption is not serious (at frequencies in or near the visible region), because the power required to produce a receivable signal is impracticably large. In the remaining useful frequency band from about 1Mc/s to 3×10^4Mc/s interfering radiation is produced by the galaxy as a whole and also by the neighbouring star (since any feasible size of radio telescope will have a resolving power which will almost certainly be too small to separate a source on a planet from its neighbouring star). These two sources of interfering radiation in the useful frequency band produce a total received power which varies with frequency and is a minimum at frequencies of the order of 10^4Mc/s. Frequencies which would be easy to find are provided by molecular or atomic resonances since these occur at the same frequencies throughout the universe. Such a frequency is provided in the region of minimum interfering radiation by the hydrogen line at 1,420Mc/s. The authors thus suggest a search around this frequency for such transmissions. The transmitter power and aerial size required for producing a signal stronger than the interfering radiation at this frequency are not much beyond even the present technical capabilities of this earth, and are within what is already planned. The authors suggest that the most likely form of modulation for such a signal would be pulse modulation. The modulation period is unlikely to be very much greater or much less than a second owing to bandwidth and planetary rotation period restrictions. An easily identifiable message would be provided by modulations forming a standard numerical series such as the first few prime numbers. From our present knowledge it is thus quite practicable to receive signals from any civilizations that may exist on planets of neighbouring stars. The authors feel that the importance which the reception of such signals would have overrides the probability that a search for them would prove fruitless.

F.M. Receiver Distortion in the i.f. stages and discriminator can be reduced by decreasing the maximum i.f. signal frequency deviation. This can be done by changing the local oscillator frequency in phase with the changes in the transmitted signal frequency produced by the audio modulation. The required changes in the local oscillator frequency can be obtained by using the audio output from the discriminator as a frequency control signal. Circuit details of how this is done in the American Allied Radio Knight tuner are given in *Electronic Equipment Engineering* for July 1959 (p. 25). This system decreases the distortion in proportion to the reduction in the i.f. deviation at normal deviations and by a much greater amount should the unreduced i.f. deviation exceed the i.f. and/or discriminator bandwidths. Two other advantages of reducing the i.f. deviation are that, since the bandwidths of the i.f. and discriminator stages can be decreased, the gain of these stages can be increased, and they can be more easily constructed. The signal-to-noise ratio is not changed by reducing the i.f. deviation, since most of the noise is produced in the r.f. stage.

Transistor Constant-Volume Amplifier

Gain Control by Input Resistance Variation

By G. J. POPE

VOLUME compressors or constant-volume amplifiers are commonly used in communications systems to equalize volume variations experienced when different operators are liable to broadcast announcements. Further, positioning of microphones becomes less critical and larger average modulation depths may be employed so that an improvement in the signal-to-noise ratio of the system is achieved.

The principle of such circuits involves the inclusion of some variable-gain element in the forward a.f. path, with provision for the automatic adjustment of the gain in inverse proportion to the strength of the incoming signal. By this arrangement, the output approaches a constant level irrespective of the *average* input level. In order to avoid overmodulation and excessive distortion, the device must be fast to respond to initial syllables of speech after a pause when the gain will have risen to a high level. The rate of recovery of the no-signal high-gain condition during pauses in speech must not be so fast that a disconcerting " snatching " effect occurs at every ensuing opening syllable.

Understandably, the rate of operation of the amplifier must take a finite time, since energy must be obtained from the incoming signal (suitably amplified of course) to charge a capacitor, the level of which charge decides the setting of the variable-gain device. An operating time of 100 msec for a maximum level input signal from silence has been found to be satisfactory in practice. The capacitor is arranged to discharge to any required lower level during pauses in speech over the space of 3-5 seconds, this period having been found to be satisfactory from an intelligibility and listening comfort point of view.

The constant-volume amplifier to be described has been designed to provide substantially similar output signal levels for various operator speech input levels. It is suitable for operation directly from a moving-coil microphone or via a pre-amplifier from a ribbon microphone.

The amplifier consists of four main sections (see Fig. 1):—

(1) Gain-controlled stages VT1 and VT2.
(2) Bias amplifier VT4, 5 and 6.
(3) Bias detector and buffer stages MR1 and VT3.
(4) A.F. amplifier VT7 and VT8.

Gain-controlled Stages.—Stages VT1 and VT2 are controlled-gain amplifiers, the input resistances of which are controlled by the a.g.c. bias fed back via the grounded-collector stage VT3. The same control principles are used as those in a well-tried a.g.c. circuit used in transistor broadcast receivers. Here the dependence of the input resistance of a transistor on the d.c. emitter current is used to control the a.c. input current supplied from the signal source. The best control range will be obtained when the signal source is of low resistance.

The overall feedback loop phase change at mid-band frequencies has been arranged to be 180 degrees, as this obviously aids the basic stability of the circuit when using the most convenient design of bias amplifier. Unfortunately, this means that the bias is fed into the emitter circuits of the controlled stages, which loses the power gain opportunities which would be obtained if the base circuit were fed. However, the present amplifier buffer-stage combination has adequate gain to provide a reasonable compression characteristic.

In accordance with well-established technique in constant-volume amplifier design, push-pull working of the controlled amplifier is arranged. Recombination of the two outputs in a transformer results in cancellation (depending on the degree of balance of the two transistors) of the d.c. " thump " transient that occurs in the collector circuit due to the sudden change of bias and thus collector current on the receipt of a signal level increase. This result is due to the application of the bias to the two emitter circuits in parallel whilst the a.f. is applied to the emitter circuits in a normal push-pull circuit fashion.

The noise level contributed by the controlled

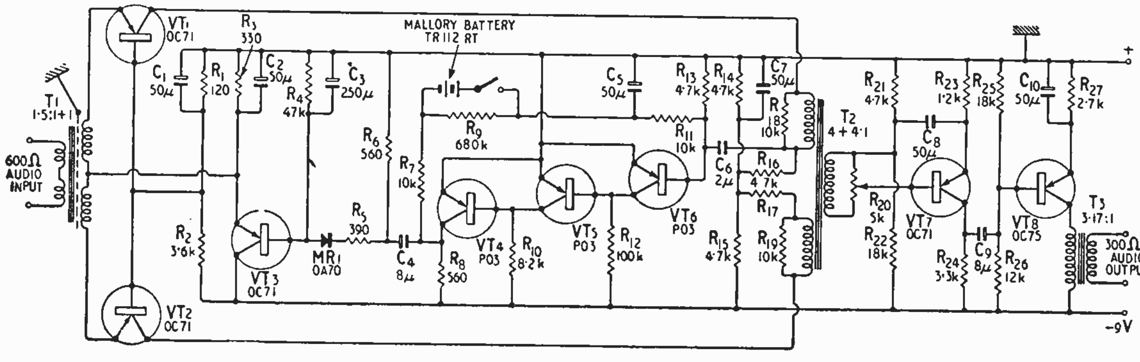

Fig. 1. Circuit diagram of constant-volume amplifier.

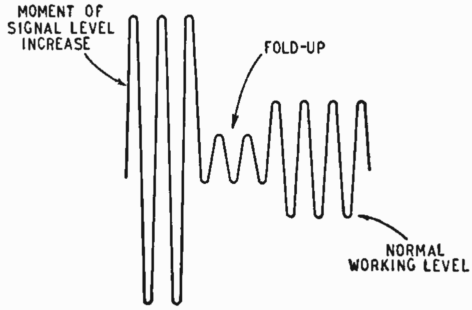

Fig. 2. Fold-up effect in output signal.

stage may be kept to a minimum by operating the collectors from a low d.c. voltage. However, due to the presence of the bias stage feed resistor R_{16} and the necessity for providing sufficient minimum operating voltage to the stage under maximum-current conditions, the collector supply voltage must not be lowered too far. Approximately 4.5V has been fixed upon as the best compromise. This potential is provided by the divider network R_{14} and R_{15} across the supply.

The no-signal standing biases in VT1 and VT2 are chosen so that the two stages are on the threshold of their maximum-gain condition. Any reduction in this bias value will also increase the effective input resistance and decrease the stage gain.

Bias Amplifier.—In order to avoid the phase change which would result at each end of the audio spectrum if the bias amplifier were fed from the secondary of T2, a resistor R_{16} is included in the collector circuit of VT1 and the bias amplifier fed from this. This procedure reduces phase changes between the bias amplifier and the forward a.f. loop to a minimum when the controlled transistors are operated in the grounded-base mode, since they will then be effectively constant-current generators.

Despite the fact that the feedback circuit to the gain-controlled stages VT1 and VT2 acts nominally only at d.c., it is good practice to ensure that the phase change around the bias feedback loop is a nominal 180 degrees at mid-band frequencies. Reactive elements must be chosen to avoid instability due to additional phase changes at the upper and lower extremities of the audio band.

For a good compression characteristic, a large gain around the feedback loop is required. In order to avoid as far as possible the extra phase change due to capacitive coupling which could be troublesome at low frequencies, d.c. coupling techniques have been used in the bias amplifier. The circuit design is based on material in articles by G. B. Chaplin and A. R. Owens (*Proc. I.E.E., Part B*, May 1958, p. 258) and by D. A. G. Tait (*Wireless World*, May 1958, p. 237), use being made of the fact that the α' of grounded-emitter stages is maintained down to a very low value of collector voltage so that direct connection between collector and next stage base circuits may be made. The first stage of the bias amplifier VT6 has its base circuit returned to earth via a 4.7kΩ resistor to keep I_{c0}' reasonably low, and obtains its bias from the collector of VT4, this connection providing negative feedback. This occurs only at d.c. since a.c. components are filtered out by capacitor C_5. The 2.6V Mallory battery in the bias lead effectively stabilizes the collector voltage of VT4 at a little above this figure, since any tendency of the bias applied to VT6 from the feedback chain to feed through the amplifier and increase the current in VT4 is removed if the collector voltage of VT4 falls below the potential on the bias line at this point. (Mallory battery potential +VT6 base potential = VT4 collector potential.) This value of collector voltage for VT4 ensures a sufficient a.c. swing without distortion in the presence of maximum signal input. The resistor R_9 across the Mallory battery provides a small discharge current to cancel the charge component which flows round the bias circuit during normal operation (5μA approximately).

Bias Rectification Circuit MR1 and Buffer Stage VT3.—As mentioned earlier, fast-to-operate and slow-to-restore features are necessary for the overall amplifier characteristic if distortion and loss of intelligibility are to be avoided. A series diode rectifier will charge its reservoir capacitor in a short time and discharge it at a rate dependent on the time constant of the load circuit, provided that the rectifier has a low forward and a high backward resistance. The circuit configuration of the bias amplifier necessitates R_6 as a "return" resistor for the diode circuit. The value of this resistor is a compromise decided on the one hand by the need to avoid undue shunting of the amplifier load R_8 and on the other by the fact that it must not unduly increase the charge time of reservoir capacitor C_3.

In practice, the charge time of C_3 must be degraded to a small extent however by the addition of a resistor R_5 in series with the bias rectifier. This has been found necessary to remove a fold-up effect (see Fig. 2) in the operating characteristic which is probably due to the "thump" voltage which is fed through the bias amplifier from the collector circuit of VT1, there being no thump cancellation in the bias path.

At first it might be considered that similar results could be obtained if R_5 were omitted and R_6 merely increased in value, but this was not found to be the case in practice. The present value of 390Ω for R_5 was found to be the best compromise value for use with the 250μF reservoir capacitor C_3, although some adjustment may be necessary in other models. The emitter circuits of VT1 and VT2 are of low impedance and it is necessary to apply the control bias to them via an impedance transformation stage VT3. This presents a fairly high impedance to the bias rectifier circuit which enables a practicably realizable value to be used for the reservoir capacitor. Capacitors C_1 and C_2 by-pass the biasing circuits to VT1 and VT2 at a.f.

A.F. Amplifiers.—In order to avoid distortion of the

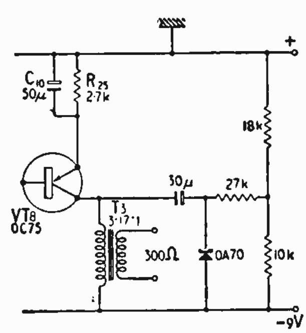

Fig. 3. Limiting circuit for removing residual "thump" signal in output stage.

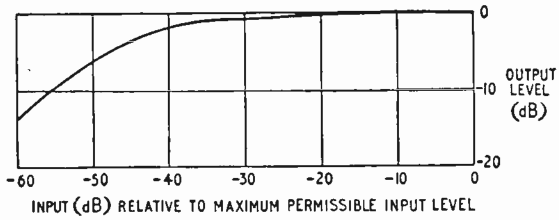

Fig. 4. Compression characteristic of constant-volume amplifier.

a.f. signal in the controlled stage, the a.f. level must be kept low, and therefore amplification of the compressed output from the secondary of T2 is necessary. VT7 and VT8 provide approximately 1mW maximum output in any convenient impedance, in the present case 300 ohms. Although the push-pull controlled stages remove most of the " thump " voltage from the signal up to the secondary of T2, the single-ended a.f. stage VT7 is driven to base cut-off on the positive half-cycle of its input by the very large transient signal which is applied after a pause in speech, when the gain of the VT1 and VT2 stages has risen to maximum. The large negative half-cycle at the base of VT7 is amplified and appears in the collector circuit of VT8 in the same phase. However, limitation of this half-cycle has already taken place in VT8 base circuit with the result that the initial transient in the collector circuit of this stage is only 6-10dB above the steady working level. In a practical application of this constant-volume amplifier used by the author, the effect was not considered bad enough to trouble about, but a simple peak limiting circuit as shown in Fig. 3 has been found effective in removing this small residual. The output signal using the above circuit modification is symmetrically limited to an r.m.s. power of approximately 1mW.

Temperature Stabilization.—The most vulnerable part of the circuit is the bias amplifier. Sufficient d.c. negative feedback has been applied to ensure adequate gain without serious shift of output stage working point over a temperature range from 0 to 40 degrees C, provided that transistors VT4, 5 and 6 have an α' of not less than 40. There is a G.P.O. specification of a transistor of this type, but if this is not available it may be necessary to select from a batch of OC71 or GET3, or alternatively to use the OC75 which has an average α' of 90 and will give excellent results in these positions.

VT1 and 2 stages are relatively unaffected by temperature due to the use of a low-value common-base resistor. The base return resistor R_4, together with the equivalent rectifier network resistance of MR1 and associated components, are low enough to ensure satisfactory operation of VT3 grounded collector stage over the forementioned temperature range.

Lowering the ambient temperature towards freezing point tends to lower the gain of the bias amplifier especially when the transistors in the VT4, 5 and 6 positions have α' in the region of 40. This drop is shown up as a worsening of the compression characteristic and hence as an increase in output which masks the fall in gain of the a.f. amplifiers VT7 and VT8 at low temperatures. At high temperatures, the gain of the bias amplifier increases and the overall output falls, so that at 40 degrees C the maximum power output of the amplifier may fall to approximately 1/3 mW using average α' transistors in VT7 and 8 positions and high α' transistors ($\approx$100) in VT4, 5 and 6 positions.

The table summarizes the results obtained on the prototype using transistors of α' as indicated.

Temperature Degrees C	Output change in dB for 30 dB input change when VT4, 5 and 6 have the following α':—		
	VT4, VT5, VT6 =40	VT4=74, VT5=62, VT6=50	VT4, VT5, VT6 = 100
0	4	0.6	3
20	1.5	0.5	2
40	1.3	0.7	2

Input and Output Circuits.—Unfortunately, due to the use of a controlled-gain amplifier of the variable input resistance type, the input impedance of the amplifier depends on the level of the input signal. Experiment has shown, however, that an average value of approximately 1kΩ provides a reasonable basis for transformer matching ratio calculation. With a 600Ω input, an input transformer having the ratio 1.5 : 1+1 will be suitable. The output transformer in the model described was designed to feed into a 300Ω load, but obviously it is quite a standard component. Transformer T2 may be bifilar wound on the primary side if desired, but this method of construction has not been used in the model described, since closely matched transistors have not been fitted in VT1 and VT2 positions. If a very accurate d.c. "thump" cancellation is required, it might be necessary to bifilar wind the transformer and provide separately adjustable bias supplies to VT1 and 2. This degree of refinement does not appear to be necessary judging from aural tests carried out with the constant-volume amplifier. Further, large "thump" voltages occur only after pauses in speech of 4-5 msec, the majority of "thump" signals consisting of small amplitude transients occurring between short pauses in speech or changes of input level, etc.

All the transformers have been designed for dealing with speech signals bandwidths only and thus have fairly low winding inductances.

The circuit of the 2.6 V bias battery must be broken when the main supply is disconnected in

Fig. 5. Overall frequency response of constant-volume amplifier.

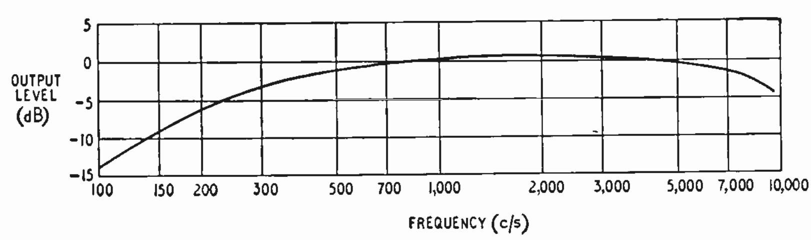

order to avoid excessive discharge through the various resistors across the supply.

In order to fully drive the constant-volume amplifier when a ribbon microphone is used, it may be necessary to use a simple single-transistor pre-amplifier. This course might also be adopted even when using adequate drive if the variations in impedance of the input circuit were required to be screened from the input signal source. However, this latter effect has not been found troublesome in applications of the amplifier used by the author.

Characteristics and Response.—Fig. 4 shows the compression characteristic of the amplifier. An isolating pad giving approximately 20 dB attenuation was inserted between the signal generator and the amplifier input in order to mask the input impedance changes which would otherwise upset the attenuator settings.

Fig. 5 shows the overall response which was measured with the bias amplifier inoperative, and a fixed voltage on the base of VT3.

The maximum input signal which the amplifier will handle without distortion depends to some extent on the transistors used, but is in the neighbourhood of 10-20 mV.

Transmission-Line Exchange

AUTOMATIC INTERCONNECTION OF TRANSMITTERS AND AERIALS

THE problem, at a transmitting station, of interconnecting the transmitters and several different aerials is an old one and one to which there does not seem to be an easy answer. However, P. & L. Miller, Ltd., have recently completed two automatic transmission-line exchanges at the Royal Navy W/T station at Inskip, near Preston and the flexibility of each installation allows the connection of any ten transmitters—with outputs of up to 40kW—to any one of twenty aerials.

The transmitter outputs are carried on open wire balanced line to a 15-ft high "tower" at the centre of the semicircular exchange. From this tower there is an extension of each feeder line to a horizontally-travelling carriage, *via* a flexible feeder link, each carriage being at a different height. The carriages, which can be driven to any one of 21 preset positions by a "Teleflex" flexible drive system, have mounted upon them a pair of feed-through insulators bearing domed contacts on the side remote from the tower. Opposite 20 of the stopping points for the horizontal carriages, mounted on the other side of the framework, are 20 similar carriages capable of vertical movement, this time driven by a lead screw, to any of the ten levels at which the horizontal carriages travel. These vertically-moving carriages are connected through a hanging loop of flexible feeder to the outside aerial feeders and, when brought up to a horizontal carriage the contacts engage, so completing a feeder circuit between any one of the transmitters and any aerial.

Electric motors drive the carriages, and these are controlled from a panel in front of the exchange. On this panel are thirty sockets and ten internally-wired plugs, each plug representing a transmitter. If a plug is removed from its "at rest" socket, when the transmitter carriage is parked in the twenty-first position with its feeder earthed, and placed in a socket corresponding to an aerial the following sequence of events takes place. First, the appropriate horizontal-drive motor is energized and the carriage travels round until it operates a micro-switch opposite the chosen aerial feeder. Then the horizontal motor is stopped by an electromagnetic brake, and the vertical drive is energized, similarly being stopped when the aerial-feeder carriage reaches the transmitter-line carriage. On returning the plug to its "at rest" socket the carriages return to their rest positions, with the transmitter feeder earthed and the aerial-feeder carriage below the arc of travel of the transmitter-feeder carriage on the lowest track.

The control system, which operates on 50V d.p. uses 440 micro-switches and six miles of cable, is interconnected with the transmitter interlock safety system. The drive motors are three-phase, 50-c/s, $\frac{1}{4}$-h.p. 1440-r.p.m. units using spur and helical gear reduction trains and each has a reversing contactor. The approximate weight of each exchange is about 8 tons.

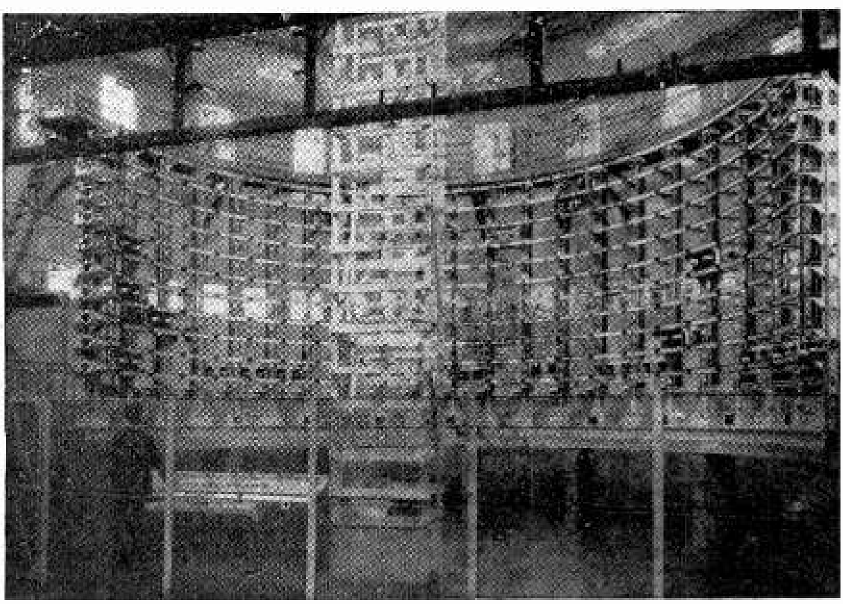

General view of the P. & L. Miller transmission-line exchange at Inskip R.N. W/T station, seen from back of tower to which flexible feeders are anchored.

Manufacturers' Products

NEW ELECTRONIC EQUIPMENT AND ACCESSORIES

Artificial-echo Unit

IN the Binson Echorec artificial echoes are produced by magnetically recording the original sound and replaying it a suitable time later to form an echo. The signals are recorded on the magnetically-coated edge of a rotating disc and replayed through one or more of four fixed replay heads near the disc edge as the recorded signal on the disc edge passes under these heads. The replay heads are spaced apart from each other so as to provide four echoes at approximately 0·15-sec intervals from 0·15 to 0·6 sec after the original sound. An erase head erases signals as they pass under it, the total available continuous recording time on the disc being approximately 1½ sec. Repeated echoes may be obtained if desired by feeding the replay heads' echo outputs back into the recording head so as to later produce echoes of the echoes. Such repeated echoes can be made to sound like reverberation. The echoes can also be made louder than the original sound as to produce "swell" effects. The replay heads are spaced about $2{\cdot}5\times10^{-4}$in from the edge of the disc and provide a response up to about 6kc/s. Echoes from any of as many as 12 different combinations of one or more of the four replay heads may be selected. Three other controls allow variation of the total time during which multiple echoes take place, as well as of the mean levels of both the echoes and the original signal independently. Up to three different input signals can be accepted and processed together; alternatively, any of these inputs can be passed through unchanged. As many as six mains-voltage tappings from 110 to 280V are provided. The unit measures $16\frac{1}{2}\times11\times$ 8in and weighs 28lb. It costs 140 guineas and is imported by Modern Electrics (Retail), Ltd., of 164, Charing Cross Road, London, W.C.2.

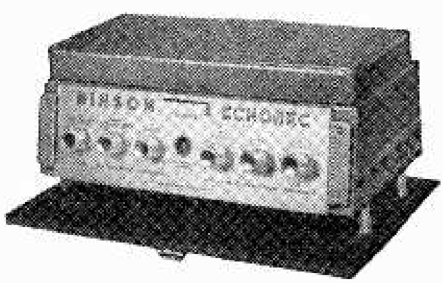

Binson Echorec artificial-echo unit.

Wide-range Insulation Tester

SHOWN in the illustration is a completely self-contained portable insulation test set with the remarkably wide range of 200MΩ to 20 million megohms ($2\times10^{13}\Omega$). Test voltages variable from 1 to 10kV are generated internally by means of a battery-operated transistor r.f. unit, step-up transformer and a voltage-multiplying stack of rectifiers.

Voltage and resistance measurements are read by a built-in valve-voltmeter with a large rectangular-faced microammeter directly calibrated in megohms (4 ranges) and in kilovolts (one range).

High-stability and "potted" components are used to ensure stability of operation under all conditions. The self-contained batteries are standard-type and easily replaceable.

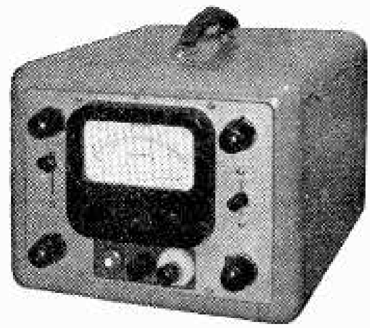

Miles Hivolt 20-million megohm insulation test set.

The makers are Miles Hivolt, Ltd., 13 Mortimer Road, Hove 3, Sussex, and the price is £99 10s 0d.

Band-pass I.F. Filters

FILTERS designed to fix the band-pass characteristics of v.h.f communications receivers have been introduced by Salford Electrical, a subsidiary of G.E.C. Known as the Types 455KBP50 and 455KBP25 they provide the selectivity necessary to meet G.P.O. recommendations for use in communications systems of 50-kc/s and 25-kc/s channel spacing respectively. Both centre on an i.f. of 455kc/s with a frequency stability better than ±400c/s over the temperature range −20°C to +70°C.

The filters are completely encapsulated and enclosed in metal boxes. A brief specification of the 455KBP25 is as follows:—

Minimum bandwidth at −6dB points	16kc/s,
Maximum bandwidth at −85dB points	44kc/s,
Minimum out-band attenuation	85dB,
Insertion loss	12dB,
Termination resistance	22kΩ.

They weigh approximately 1lb each.

The makers are Salford Electrical Instruments, Ltd., Pool Works, Silk Street, Salford 3, also at Magnet House, Kingsway, London, W.C.2.

Band-pass characteristic of Salford Type 455KBP50 i.f. filter.

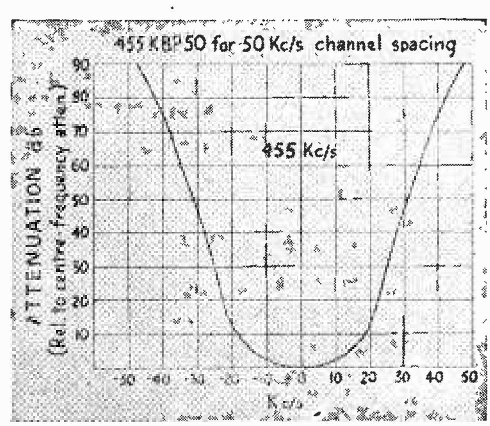

Elements of Electronic Circuits

10.—TRIGGERED TWO-STATE CIRCUITS

By J. M. PETERS, B.Sc. (Eng.), A.M.I.E.E., A.M.Brit.I.R.E.

A WELL-KNOWN type of two-state circuit is the cathode-coupled multivibrator. The operation of this circuit is similar to that of the conventional multivibrator described in previous issues, and the same kind of cumulative action occurs. Fig. 1 shows the basic circuit, which is that of a two-valve amplifier with overall positive feedback, the valves being arranged in what is known as a " long-tailed pair " configuration.

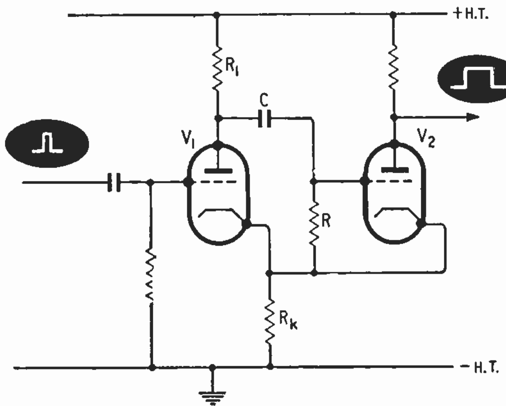

Fig. 1

A change in grid-cathode voltage gives rise to a series of events leading to a similar, but amplified, voltage variation being added to the grid-cathode voltage; hence the circuit is unstable and will under normal circumstances oscillate freely. However, if there is too great a bias difference between V1 and V2, the oscillations will stop and the circuit will become stable with one of the valves non-conducting (see also the description of the operation of the " long-tailed pair," November, 1959, issue, p. 510). A suitable initiating signal to V1 grid will cause the circuit to perform a single cycle of oscillation. A freely running oscillator therefore becomes a trigger circuit.

Let us consider the operation of the circuit when the bias voltages are similar and when positive sync pulses are applied to V1 grid, see Fig. 2. Initially V1 is assumed to be cut off by V2, the grid and cathode of V2 being at the same potential. The anode current of V2 flowing through R_k produces the necessary voltage to cut off V1. A positive sync pulse of sufficient amplitude causes V1 to conduct, V1 anode voltage falls and is transferred to V2 grid by C.

Because anode current starts to flow in V1, the anode current of V2 will be reduced. The potential across R_k will fall but will be partly compensated by the rise in anode current of V1. *Note:* If the drop in anode current of V2 is greater than the rise in anode current of V1, then V2 will be cut off and V1 will continue to conduct.

With V2 cut off, V2 anode rises to h.t. C discharges through R and the conducting V1 until V2 grid rises through cut-off. V2 then conducts and V1 is cut off by the bias on R_k. C now charges through R_1, V2 and R_k; thus the rise in the V2 anode waveform is curved. It will be noted that because the cathode potential can follow the grid potential during its positive excursion, no grid current flows. The grid waveform at V2 is therefore not squared by grid current as in the conventional multivibrator and it appears as a " differentiated " square wave.

No buffer amplifier is required with this method of connection since the sync voltage is isolated from

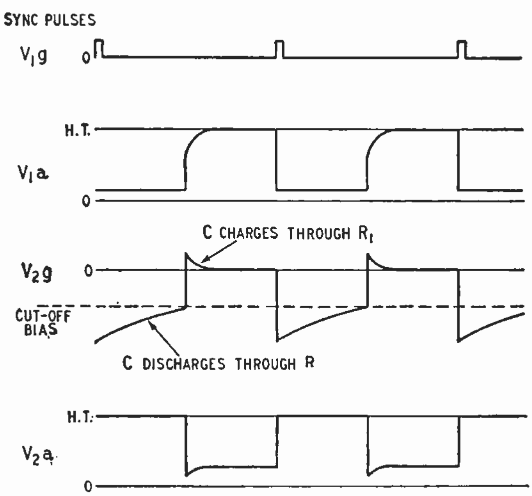

Fig. 2

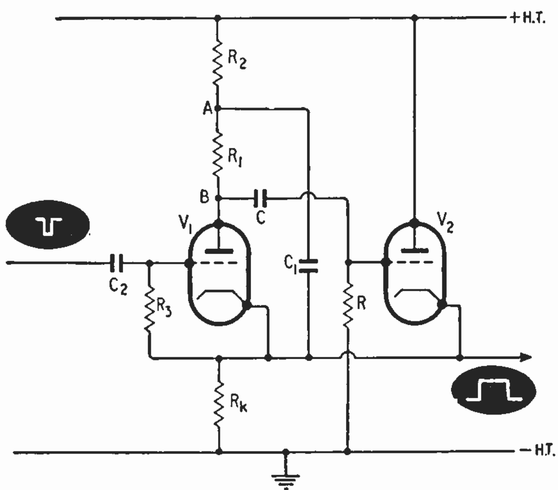

Fig. 3

the oscillatory circuit proper. Similarly, an undistorted square wave output may be taken from V2 anode without disturbing the action of the oscillator.

Fig. 3 illustrates a variation of the cathode-coupled multivibrator by which it is possible to obtain a large positive pulse output at the common cathode with a *negative* sync input. In the cathode-coupled multivibrator described above the positive pulse appears at the *anode* of V2 when V2 is cut off. In the Fig. 3 circuit V2 is conducting and the positive pulse appears at the *cathode*. By tying the cathode as well as the grid of V2 to the varying anode circuit potentials of V1 it is possible to add to the action of positive pulse generation, thereby obtaining a greater positive-going voltage than if the link were omitted. Such a connection, via C_1 in the diagram, is called a " bootstrap " connection (derived from the notion of pulling oneself up by one's bootstraps—or boot-laces when in Britain).

The action is explained as follows. Let us assume that in the quiescent state V1 is conducting and V2 is cut off by the voltage developed across R_k. On the arrival of a negative sync pulse at the grid of V1 the anode voltage of V1 rises. V2 grid consequently rises and V2 starts to conduct. In so doing, however, it increases the common cathode potential, thereby cutting off V1.

The positive-going cathode voltage is back-coupled to point A in Fig. 3 via C_1. (To avoid any distortion of the pulse a long time constant " bootstrap " coupling circuit C_1R_2 is used.) From A the positive going voltage is transferred and added to that appearing at B, and thence back to V2 grid via C. The further increase in current in V2 results in a further rise in cathode potential. This is the " bootstrap " action, for because of the coupling via C_1, the resultant positive-going output voltage is very much greater than the positive going voltage initially developed across R_1.

It will be noted that any change in voltage across R_1, i.e. between A and B, will be applied between V2 grid and V2 cathode. V2 therefore acts fully as an amplifier *without* negative feedback and not as a cathode follower. The period which must elapse before the circuit resets is dependent on the time constant of the grid circuit of V1 (principally C_2R_3). When V1 grid approaches the cathode potential, V1 again conducts, thus continuing the action.

Vacuum Encapsulating Plant

SHOWN in the illustration is a self-contained plant developed primarily for vacuum encapsulation of radio and electronic components. This model, the Type VP200, consists of a cylindrical work tank assembled alongside a control unit in which is housed the motor-driven vacuum pump, low-voltage mains transformer, d.c. rectifiers, silica gel air driers, vacuum gauges and all switches and controls necessary for the operation of the plant.

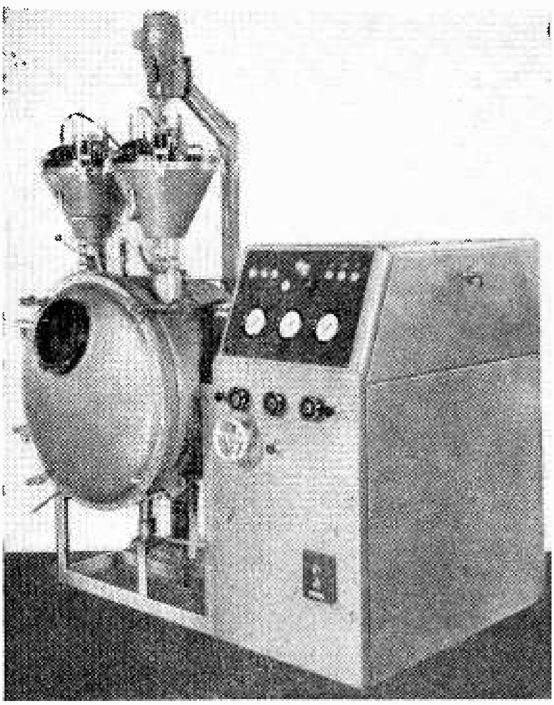

Self-contained plant for vacuum impregnating and encapsulating radio and electronic components.

Two conical-shaped hoppers are mounted on top of the work tank in which the epoxy or polyester " potting " resins are mixed, two being provided so that mixing can be done in one while the other is being poured into the moulds. Each hopper holds about 80 fluid oz of resin and is independently evacuated, heated and thermostatically controlled. Mixing is effected by a rotating vane driven by a variable-speed motor and mounted on a swinging arm so that the vane can be dropped into either hopper.

Access to the work tank for " loading " is by means of a domed end-door secured by six quick-action clamps. The tank is hermetically sealed when the door is closed and can be evacuated down to 1mm Hg in a little over 5 minutes. A 9-in glass inspection window enables the various moulds to be positioned below the pouring nozzles and the filling process observed and controlled.

Inside the work tank is an electrically heated and thermostatically controlled work turntable on which the moulds are placed. It has about 600 sq in of work space and will carry 240 lb of distributed load. It is rotated by means of a handwheel on the control unit.

Eventually it is proposed to produce the plant in various sizes and work is in hand on automatic plant for high rates of production. Further details can be obtained from Pipework and Engineering (Bristol), Ltd., Stanley Street South, Bristol, 3.

Talking Books—Tribute is paid in the annual report of the Royal National Institute for the Blind " to the two thousand amateur radio and sound recording enthusiasts throughout the country who render such magnificent help in servicing the [talking book] machines." Reference is also made to the voluntary transcribers who add each year some 1,000 Braille volumes, each hand embossed, to the students' library. Among them are a number of radio textbooks. These are, of course, in addition to the regular supply of mechanically embossed periodicals and books maintained by the Institute.

Omnis definitio periculosa est
(Every definition is dangerous)

ERASMUS

IMPEDANCE

By "CATHODE RAY"

IT is quite a thought that after 25 years of Cathode Radiation such a basic and elementary subject as impedance can still be found which (a) has not previously come under the beam, and (b) is sufficiently controversial. Yet so it is.

What started it off was my discovery that the meaning of impedance could provide material for argument in the pages of the *Journal of the Institution of Electrical Engineers* to a degree that the correspondents became quite heated—one might almost say personal—while other and cooler minds found in it an occasion for a vivid display of incomprehensible mathematics, bringing in such apparently (to me) unrelated matters as entropy and explosion.

Admittedly the subject discussed was actually *negative* impedance, but it began in the very first paragraph with the British Standard definition* of impedance:

"The ratio of the r.m.s. electromotive force in a circuit to the r.m.s. current which is produced thereby. Symbol: Z."

R. O. Kapp, Emeritus Professor of Electrical Engineering, University College, London, has said that physicists (in contrast to philosophers, who begin with names for their concepts before they have agreed on what the concepts themselves are) begin with precise concepts, then define them, and lastly standardize names and symbols for them. And, this being so, the definition is not quite as important as we thought it was, since it is needed more for identification of a concept which we are all supposed

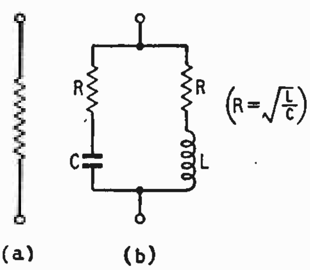

Fig. 1. (a) is a particular kind of impedance that is obviously independent of frequency. Though this is less obvious with (b), it too amounts to exactly the same thing.

to have agreed upon beforehand than as a watertight and precise statement.

This view may not be universally accepted, but even if it were there would still presumably be agreement that definitions ought to be made as precise as reasonably practicable. The B.S. definition of impedance, however, is so brief that one wonders whether it is really as general as it appears to be or whether various restrictions not mentioned must be taken as read. Does it apply to e.m.fs and currents of any waveform? In non-linear circuits? Under transient as well as steady-state conditions? Because it is in a context of general electrical engineering, in which restrictions on some or all of these things are often assumed, one (as I say) wonders.

But then the term "r.m.s." twice inserted, strikes the eye. We may be prepared to believe that detailed conditions might be left out of such definitions, on the ground that they are so commonly assumed that including them would look pedantic, as well as putting up the price of the publication. But the definers would hardly throw in an expression like "r.m.s." without due thought, just to give their work an air of distinction. And if this definition were meant to be confined to cisoidal waveforms (that is the currently favoured term, I believe, embracing pure sine or cosine forms) there would be no point in limiting it to r.m.s. values—peak values, or any fraction or multiple thereof, would do just as well, since any factor applying to both e.m.f. and current would cancel out on taking the ratio. Therefore, giving the definers the benefit of serious doubts raised on other occasions and assuming they were rational beings, we can infer that their definition of impedance is valid for any waveform.

Principle of Dependency

Your first reaction to this may be the same as mine was—to object. "Why!" you may exclaim, "most circuits would have quite different impedances to the separate components of, say, a square-wave e.m.f., so the value of Z would depend on what the waveform happened to be!" But after a little thought we can meet this objection with the retort "So what?" For even where the waveform is purely cisoidal and the details of the circuit are fully specified, its impedance is still (apart from a few special cases such as in Fig. 1) quite unknown—it depends on frequency. The principle of dependency having already had to be conceded, why worry because Z depends also on waveform? And having given way so far, surely no one is likely to make a stand against impedance being allowed to depend on yet another parameter of the applied e.m.f.—amplitude. So there is no need to bar non-linear circuits such as iron-cored coils.

Transients are different, though. An r.m.s. value being by definition not an instantaneous value, it implies a steady state.

So, if I interpret the collective mind of the relevant B.S. committee aright, their definition of impedance holds for any waveform and any circuit, but not for transients.†

Offhand, I suspect that not many people in our field take much advantage of this liberal interpretation of impedance. For one thing we seldom have the equipment for measuring the true r.m.s. values of signals. And we tend to regard impedance as a function only of frequency and to analyse non-cisoidal waveforms into their Fourier components for separate consideration. (We shall see one reason why in a minute.) I'm not very well up in high-power

*B.S.205: Part 1: 1943, Definition 1282.

†This appears to hold good on the other side of the Atlantic, for Henney's "Radio Engineering Handbook," 5th edition (1959), p. 1-107, defines impedance in practically the same way as B.S., and goes on to apply it specifically to non-cisoidal e.m.f. and current.

radio transmitter practice, but perhaps in that sort of work—and anywhere in which bolometers and other heat-operated measuring instruments are used—it is useful to know the impedance of a circuit to a given non-cisoidal e.m.f. for calculating how much heating current will flow therein.

The next thing is to point to the distinction between impedance (as hereinbefore defined) and impedance operator. I might have hesitated to do this, feeling that it verged on insulting the intelligence, had it not apparently been one of the causes of the confusion in *Jour. I.E.E.*, in spite of its high-class professional standing. So it must be emphasized that impedance, according to the B.S. definition, is just a number of ohms, which by itself reveals nothing of the phase angle between the e.m.f. and current. That comes as a separate piece of information. And right away that restricts one to cisoidal waveforms and linear circuits. For unless the e.m.f. is cisoidal and the impedance is linear, the resulting current has—in general—a different waveform. And unless the current and voltage waveforms are identical it is not possible to identify the phase difference between them. And just knowing Z without its phase angle is seldom enough.

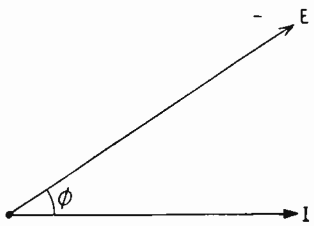

Fig. 2. The familiar vector method of representing the phase difference between e.m.f. and current.

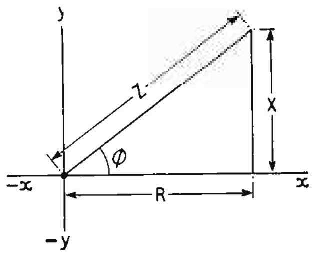

Fig. 3. Showing how a distance Z can be set off at any angle on squared paper (not primarily adapted for angles). Vertical or y-axis measurements (X) are distinguished from horizontal or x-axis (R) by the prefix j.

It is true that it does enable the current to be calculated, given the e.m.f., in the same manner as in "Ohm's law":

$$I = \frac{E}{Z}$$

Or the inverse:

$$E = IZ$$

And it is true that the impedance of a loudspeaker is often given just in ohms. But one can't calculate the power an amplifier can deliver to it without knowing or at least assuming its phase angle, ϕ.

There are quite a lot of different ways of taking account of ϕ. They are explained in any worth-while book on a.c. theory, and all that is needed here is a few words on the impedance operator. It is a mathematical concept, in contrast to impedance, which is a physical concept. It ties up with the representation of cisoidal currents and voltages by vectors (though physically they are not vector quantities, in circuits, anyway). For example, Fig. 2 represents the e.m.f. E in a circuit and the current I due to it. The value of E can be found by multiplying I by the impedance Z. But that leaves the phase relationship unknown. If the angle ϕ is also given, we have the whole story (for one particular frequency). Mathematical minds like to think of the process of arriving at the full information about the e.m.f. as operating on the current vector by the complex impedance operator **Z** (in heavy type to distinguish it from Z), specified by Z and ϕ combined. What this operator does to I in order to arrive at E is to alter its length (multiplying it by Z) and to rotate it positively (anticlockwise) through the angle ϕ.

One way of specifying **Z** is by what are technically called its modulus and argument; in other words, the magnitude Z and the phase angle of the vector E relative to the vector I, usually denoted by ϕ. (If I leads E, as it does in a capacitive impedance, ϕ turns out to be negative.) For example, **Z** might be 700 Ω $\angle +40°$. This is the polar presentation, because it uses polar co-ordinates—radius and angle.

But angles don't fit directly into algebra; nor on squared paper, which is made for cartesian co-ordinates—x and y. The only angle that can be said to fit into ordinary algebra is 180°, because that can be represented by a minus sign. It reverses the direction along a scale of numbers, say the x axis of a graph. What is called complex algebra extends this to include right angles. Quantities to be measured along the y axis are distinguished from those along the x axis by the prefix j. This scheme provides two dimensions, so that a distance can be specified in any direction on a graph and not only along one axis, by prescribing the appropriate numbers of units to be taken horizontally and vertically. So this is an alternative two-part specification for an angle. In the case of impedance, the x distance is what we know as resistance, and the y distance as reactance (Fig. 3). And so we have the well-known relationship

$$\mathbf{Z} = R + jX$$

(It may be a little confusing for beginners that the symbol for reactance, which is measured along the y axis, is X; but that is just one of those things to keep them alert!)

Quite often one does actually measure impedance by measuring X (or L and C, which are related to it) and R, in which case this second form is obviously appropriate. Sometimes there is a need to change over between it and the first. Tan ϕ is X/R, so ϕ is the angle whose tangent is X/R (written $\tan^{-1}X/R$) and can be found, knowing X and R. And our old friend Pythagoras, looking at Fig. 3, tells us that $Z = \sqrt{(R^2 + X^2)}$.

With the further help of trigonometry it is possible to work in terms of ϕ and Z even on a cartesian framework. Sin ϕ is X/Z and cos ϕ is R/Z, and $\mathbf{Z} = R + jX$. Putting these together we get

$$\mathbf{Z} = Z(\cos\phi + j\sin\phi)$$

In this, where Z of course is the magnitude of the

(*Continued on page 97*)

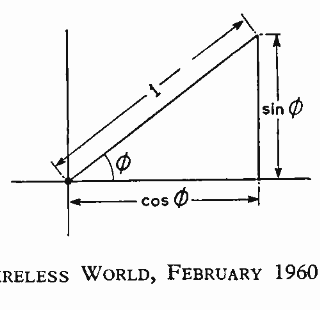

Fig. 4. If the length of the radius is 1 unit, its horizontal and vertical components are numerically equal to the cosine and sine of the angle ϕ.

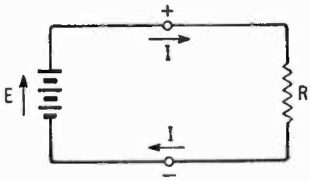

Fig. 5. Looking from R, the generator appears to be a negative resistance (not an ohmic one in this case!) because I is flowing against the voltage across R.

impedance, its phase angle is given in along-and-up terms by ($\cos\phi + j\sin\phi$). This can perhaps be seen even more clearly in Fig. 4, where a radius is drawn of length 1. The lengths of the two other sides of the right-angled triangle are, by trigonometrical definition, equal to $\cos\phi$ and $\sin\phi$. So " $\cos\phi + j\sin\phi$" means "move along a distance equal to $\cos\phi$ and upwards a distance equal to $\sin\phi$ (downwards if $\sin\phi$ happens to be negative)" and the total result is a unit-length radius rotated from the x axis position through the angle ϕ. Multiplying ($\cos\phi + j\sin\phi$) by the number Z gives an operator which multiplies the unit radius by Z as well as rotating it through ϕ. The whole operation is what is meant by **Z**. If used on an I vector the result is an E vector.

There is a fourth mode of expression which is quite often useful, but which is much less easily explained. In fact, it looks at first sight quite nonsensical, and if I explained it on the same elementary level it would leave no room for any more about impedance, so I will merely mention that an alternative mathematical form for ($\cos\phi + j\sin\phi$) is $e^{j\phi}$. It is derivable from the series forms of e^x, $\sin\phi$ and $\cos\phi$. Besides its welcome brevity, it is handy where multiplication or division has to be done, because those operations are performed simply by adding or subtracting indices.

Negative Impedance

Lastly we come to negative impedance; is there such a thing? Apparently feelings run high on the question. I'll try to put it objectively. We start with resistance, which is anything that needs an e.m.f. to drive current through it in phase with the e.m.f.—which means that the current always goes through it from positive terminal to negative. It absorbs power from the source or generator of the e.m.f. This is the situation viewed from the generator and looking into the resistance, which is a load on it. But suppose we turn round and look from the load into the generator. We see that the current is flowing through it from negative to positive (Fig. 5). This, being the reverse of what we saw when looking at the load resistance, is logically called a negative current, and so the resistance we are looking into must be a negative one.

That is quite a useful concept in connection with positive-feedback amplifiers, which when connected to suitable loads can generate alternating currents, or at least reduce load resistance already present. It is logical and convenient to regard such amplifiers as negative resistances. True, the practice has its little pitfalls, which ran to two instalments of " Cathode Ray " in January and February 1957. But I don't know of anyone who seriously objects to this concept in principle.

It is when the concept is extended to the wider range of impedance, as is sometimes done in America at least, that objection is aroused. I would expect the argument for negative impedance to arise from the fact that the current in an a.c. circuit is only exceptionally in exact phase or antiphase with the e.m.f. So if one connects to a " black box " and finds that current flows *out* of it—i.e., from its positive terminal—but not exactly 180° out of phase with the voltage, we may be tempted by analogy with negative resistance to call the contents of the box a negative impedance. It sounds plausible, but does it fit what has already been agreed about impedance?

The B.S. definition takes no account of the signs or directions of the e.m.f. and current whose ratio is declared to be impedance. So no sign attaches to that impedance. It is just a number of ohms—the ratio of a number of volts to a number of amps. Why is this, seeing that it is common practice to give a sign to resistance to show whether it is taking or delivering power, indicated respectively by positive and negative conventional direction of current in relation to applied e.m.f.? There is a very good reason. The current through an impedance, *except when that impedance is a pure resistance*, is neither exactly in phase nor antiphase with the e.m.f., so its relationship with the e.m.f. cannot be indicated simply by + or −. During part of each cycle the current is flowing with the e.m.f. and during the remainder against it—whether the impedance is on balance a load or a generator. Fig. 6 shows examples of both, in waveform and vector representations.

" Very well then," the negative-impedance advocate might say; " let's define negative impedance as impedance in which the resistive component is negative. What's wrong with that ? "

Well, it would certainly seem to be the most logical definition. But one or two difficulties arise. First, we are obliged to say what we are going to do about impedances which on this basis are neither positive nor negative: pure reactances. Impedance being an all-embracing term, including pure reactances and resistances, this lands us with an anomaly for a start. The fog thickens when we consider that reactances themselves are conventionally either positive or negative. In Fig. 6(b) the resistive component is negative and so is the reactive component.

(a)

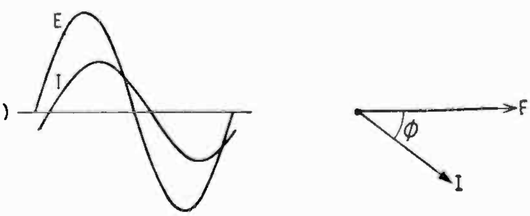

(b)

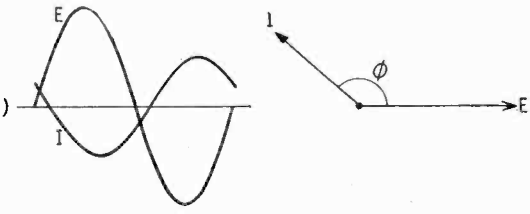

Fig. 6. Unless an a.c. is exactly in phase or antiphase with the e.m.f. there are parts of every cycle when it is flowing with and against the e.m.f., whichever way the net power flows.

The latter would be positive if ϕ were more than 180°. That real confusion arises from this is demonstrated unintentionally by Dr. B. R. Myers, who speaks up in *Jour. I.E.E.* for negative impedance, when he says "The only time I have seen the term 'negative impedance' misused is in connection with impedances whose real parts were negative. The latter are negative impedances only when their imaginary parts are negative reactances." ("Real" and "imaginary" refer to resistive and reactive components respectively.) So here we seem to have quite a different idea of negative resistance—one in which the reactive part is negative (capacitive). An arguable one, I suppose; but I should have thought that on the whole the direction of power flow was more important than whether the reactive part was positive or negative. One would, I think, tend to regard negative impedance as an extension of the idea of negative resistance rather than of negative reactance (which one more often calls capacitive reactance).

Not only do the negative-impedance advocates have to choose between one or other of the component parts of impedance to decide the sign of the whole (and probably divide into two schools of thought about it); they upset existing definitions and conventions, which sensibly (it seems to me) take the line that attaching a + or − to a complex quantity is an over-simplification, and it is better to use either the simple ratio (as in the B.S. definition) or go the whole hog by specifying the actual phase angle (as in the various forms of the impedance operator).

Condemnation

I therefore side with Mr. M. O. Williams, who first raised the matter by condemning "negative impedance." As for the consortium of B.B.C. brains who intervened, I'm so far from understanding their mathematical reasoning and its somewhat bizarre conclusions that I'm not even sure which side they finally come down on. It consoled me considerably to learn that my bewilderment was shared by no less an authority than Prof. Kapp. But I suspect that as regards negative impedance they too are agin' it.

Further research into American literature (especially three articles by E. L. Ginzton in *Electronics*, July-Sept. 1945) has led me to suspect that the interpretation which Mr. Williams (presumably) and I (certainly) put on the quoted remark of Dr Myers was quite wrong, and no wonder, for it seems that Dr. Myers and the few (let us be optimistic!) who take the same line about negative impedance have been as naughty as motorists who take a sudden turn on a crowded road without warning. Ignoring the long established convention (in U.S.A. as well as G.B.) that positive reactance means inductive reactance and negative means capacitive, they use the term negative reactance to mean a reactance which is either inductive or capacitive but varies with frequency like the opposite kind. Their "negative inductive reactance" increases directly with frequency but is capacitive (*negative* by standard convention, with current leading e.m.f.) and their "negative capacitive reactance" increases inversely with frequency like an ordinary capacitive reactance but is inductive (*positive* by standard convention, with current lagging e.m.f.). And "negative impedance" covers these elements along with negative resistance. The spokesmen for this curious perversion have not been remarkable for the openness and lucidity of their expositions, but as well as I can make out the foregoing is the basis of their creed.

By way of illustration I have been trying hard to think of any small arbitrary departure from common usage which would naturally tend to cause more confusion, but have had to give up. Perhaps that is the most sensible thing to do with the negative-impedance sect.

FEBRUARY MEETINGS

Tickets are required for some meetings; readers are advised therefore to communicate with the secretary of the Society concerned.

LONDON

2nd. I.E.E.—"Development of the formulæ of electromagnetism in the M.K.S. system" by Dr. P. Vigoureux supported by "The choice of basic dimensions in electromagnetism" by P. C. M. De Belatini at 5.30 at Savoy Place, W.C.2.

5th. I.E.E.—Medical Electronics Group discussion on "Computers in medical use" opened by Dr. R. A. Buckingham and Dr. J. M. Tanner at 6.0 at Savoy Place, W.C.2.

5th. Television Society.—"Automatic control systems in television receivers" by K. E. Martin and P. L. Mothersole (Mullard Research Labs.) at 7.0 at the Cinematograph Exhibitors' Association, 164, Shaftesbury Avenue, W.C.2.

8th. I.E.E.—Discussion on "Present views on ground-wave propagation" opened by G. Millington at 5.30 at Savoy Place, W.C.2.

9th. Brit.I.R.E.—"Drift correction of d.c. amplifiers" by D. Leighton Davies at 6.30 at the London School of Hygiene and Tropical Medicine, Keppel Street, W.C.1.

9th. Radar & Electronics Association.—"Transistors today and tomorrow" by E. Wolfendale (Mullard) at 7.30 at the Royal Society of Arts, John Adam Street, W.C.2.

17th. I.E.E.—Faraday Lecture on "Electrical Machines" by Professor M. G. Say at 6.0 at Central Hall, Westminster, S.W.1.

17th. British Kinematograph Society.—"Modern television studios" by W. H. Cheevers (Associated-Rediffusion) at 7.30 at the Colour Film Services Ltd. Theatre, 22-25, Portman Close, Baker Street, W.1.

19th. Institute of Navigation.—"Space navigation" by Dr. J. G. Porter (Royal Greenwich Observatory) at 5.15 at the Royal Geographical Society, 1, Kensington Gore, S.W.7.

19th. B.S.R.A.—"The sounds of music" by Dr. W. H. George at 7.15 at the Royal Society of Arts, John Adam Street, W.C.2.

22nd. I.E.E.—Discussion on "Are we making the best use of research resources?" opened by L. Rotherham at 5.30 at Savoy Place, W.C.2.

23rd. I.E.E.—Discussion on "Courses for electrical technicians" opened by Professor M. W. Humphrey Davies at 6.0 at Savoy Place, W.C.2.

23rd. Society of Instrument Technology.—"Back-scatter method of wall thickness measurement" by D. F. White and L. E. Taylor and "Ultrasonic resonance method of wall thickness measurement" by M. V. James at 7.0 at Manson House, 26, Portland Place, W.1.

24th. Royal Society of Arts.—Trueman Wood Lecture, "The exploration of outer space" by Professor A. C. B. Lovell (Manchester University) at 2.30 at John Adam Street, W.C.2.

FEBRUARY MEETINGS (contd.)

24th. I.E.E.—" Applications of microwaves " by Professor A. L. Cullen at 5.30 at Savoy Place, W.C.2.

24th. Brit.I.R.E.—" The unification of electronic clinical instruments " by Dr. F. D. Stott at 6.30 at the London School of Hygiene and Tropical Medicine, Keppel Street, W.C.1.

25th. Television Society.—" Science on television " by A. J. Garratt (International Scientific Research Exhibitions) at 7.0 at the Cinematograph Exhibitors' Association, 164 Shaftesbury Avenue, W.C.2.

BIRMINGHAM
17th. Institution of Production Engineers.—" The application of computers to production control " by R. G. Hitchcock at 7.0 at the James Watt Memorial Institute.

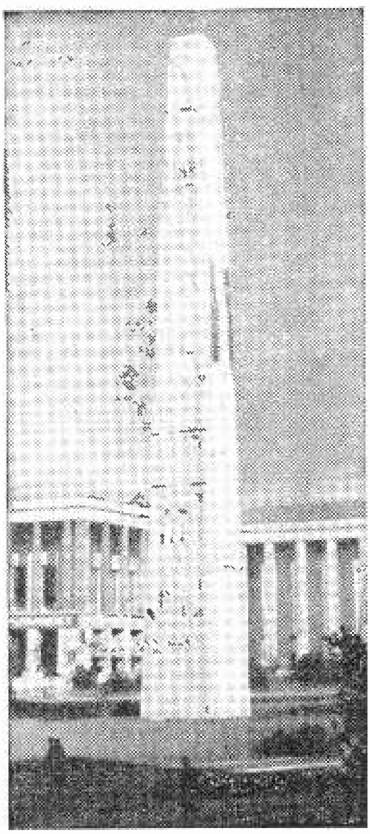

"Marconi Antenna" is the name given to this obelisk recently unveiled by Marconi's widow in the grounds of Permindex, the new world trade centre in Rome. Fifteen bas-relief panels depict incidents in the life of Marconi. A miniature gold reproduction of the obelisk and a diploma will be awarded each year from 1960 by the Centre to the person making "the greatest contribution to the progress and development of the ideas and discoveries of Guglielmo Marconi, in any field of human endeavour"

BOURNEMOUTH
8th. Association of Supervising Electrical Engineers.—" Television engineering " by a member of Southern Television at 8.0 at the Grand Hotel, Firvale Road.

BRISTOL
24th. Brit.I.R.E.—" Industrial magnetic recording and playing machine design " by J. Elliot at 7.0 at the School of Management Studies, Unity Street.

CARDIFF
10th. Brit.I.R.E.—" Low noise, low drift d.c. amplifiers " by V. L. Devonald at 6.30 at the Welsh College of Advanced Technology.
25th. British Computer Society.—" Basic principles of programming—part II, by Dr. R. J. Ord-Smith (S.T.C.) at 6.30 in the Small Shanlon Lecture Theatre, University College.

HALIFAX
3rd. Association of Supervising Electrical Engineers.—" Transistors " by a member of G.E.C. at 7.45 at The Crown Hotel, Horton Street.

HULL
10th. British Computer Society.—" ERNIE the electronic random number indicator " by W. E. Thomson (Post Office Research) at 7.30 at the Hull Chamber of Commerce, Samman House, Bowlalley Lane.

LIVERPOOL
2nd. Brit.I.R.E.—" Distribution of sound and television by wire " by A. W. Mews, at 7.0 at the University Club.

MALVERN
2nd. Brit.I.R.E.—" Electronics in medical and biological research " by W. J. Perkins at 7.0 at Winter Gardens.

MANCHESTER
4th. Brit.I.R.E.—" Acoustics in modern buildings " by E. S. Benson at 6.30 at Reynolds Hall, College of Technology, Sackville Street.
22nd. Institution of Production Engineers.—" Radio in space research " by Dr. J. A. Saxton at 7.15 at Reynolds Hall, College of Technology, Sackville Street.

NEWCASTLE-UPON-TYNE
2nd. British Computer Society.—" Data transmission in relation to computers and data processing systems " by W. S. Ryan (G.P.O.) at 7.0 at the University Computing Lab., 1 Kensington Terrace.
10th. Brit.I.R.E.—" Instrumentation in rocket propulsion " by R. E. Ross at 6.0 at the Institution of Mining and Mechanical Engineers, Neville Hall, Westgate Road.

OXFORD
16th. Association of Supervising Electrical Engineers.—" Radio astronomy " by Dr. A. D. Petford (Oxford University, Observatory Section) at 8.0 at the Employment Exchange.

SHEFFIELD
1st. Society of Instrument Technology.—" Feedback—the principle of control " by R. S. Medlock (president) at 7.0 at The University, St. George's Square.

WOLVERHAMPTON
10th. Brit.I.R.E.—" Electronic reading " by I. W. Merry at 7.15 at College of Technology, Wulfruna Street.

RANDOM RADIATIONS

By "DIALLIST"

What's in a Name?

AN area secretary of the Association of Radio and Electronic Engineers takes me to task for calling those who repair our sound and television sets servicemen. "This," he writes, "seems to fit with milkman and lavatory man." He would prefer service engineer. Well, I'm the last person ever to hurt anybody's feelings if I can help it; but I think he's quite wrong in suggesting that there's anything derogatory about "man." Think, for instance, of sportsman, Government spokesman, nobleman, chairman and so on. Myself, I've no objection at all to being called a writing man. In France the people who see to sound radio and TV sets, record reproducers and the like are called *dépanneurs*, which means simply those who put right *pannes*, or break-downs, and no one is offended by the term. I know, of course, the modern tendency is to use high-falutin titles; the rat catcher is a rodent operative, the dustman a refuse collector and even office boys are now "junior male management trainees"!

Hard to Define

It's not an easy business to define the meaning of "engineer" as the word is used in this country. Lots of people have had shots with varying success. There's no doubt that corporate members of our senior engineering institutions are engineers, chartered engineers in fact. But that by no means exhausts the list. I think I'd say that an engineer is one whose high qualifications, long learning and wide knowledge of his particular branch fit him to originate, to design, to co-ordinate and to direct. That, though, may be found too sweeping by some. To come back to the world of wireless, an alternative to "serviceman" might be "service technician," but that seems to me rather too much of a mouthful. If any readers care to send suggestions, they'll be most welcome. I'd be only too happy to find a concise term that is acceptable all round and doesn't cause any hackles to rise and at the same time isn't too pretentious. Give me that and I'll erase "serviceman" from my vocabulary.

No "Out-of-Stock" Here

THOSE well-known component manufacturers, A. F. Bulgin & Co., have just made a rather remarkable announcement. Under the heading "Continuity of Supply" they state: "Tools are stored and maintained for the future replacement of components shown in all our catalogues during the last 25 years." Now, that really is the stuff to give the troops and I hope that other makers will follow this excellent example. Few things are more exasperating than to find when some indispensable component in an expensive piece of apparatus packs up that replacements are no longer available. I expect most of us have had the sad experience. Well done, Bulgin's; that can't happen with your products.

Non-standard Colour Coding

THE I.E.E., I'm glad to see, has issued a warning about imported apparatus provided with triple flex leads which don't conform to our standard colouring. I'd no idea that so many different systems were in use on the Continent until I read an article on the subject by Philip Honey in *Wireless & Electrical Trader*. Germany uses red-covered earth leads, but in Holland they are grey, in Belgium black and in Switzerland yellow. Phase leads can be red, yellow or blue in Belgium, grey (as a rule) in Germany, and any colour but red or grey in Holland. Neutrals are usually grey or black, though in Holland they're red. Well, there's a fine mix-up for you! I suppose that apparatus imported from Germany with its red earth and grey phase leads is by far the most dangerous, for if a 3-pin plug were connected in our fashion to the leads, all metal parts that should be earthed would be at the full mains potential. But Grundig (Gt. Britain) Ltd. have already announced that the colour codings of all their machines with 3-core mains leads conform to the standard British practice.

Any dealer should verify that the colours mean what they suggest to British eyes before putting imported apparatus on sale, and purchasers would be well advised to obtain an assurance on this point. As it is, a number of people have received shocks, though I'm happy to say that no fatalities have been reported and I sincerely hope they won't be.

Approved Electrical Appliances

IT'S good to read that after discussions extending over a considerable time the electricity supply industry, the British Electrical and Allied Manufacturers' Association and the

British Standards Institution have formed a provisional board to manage a national organization for the approval of domestic electrical appliances. The board has been instructed to organize as quickly as possible machinery for safeguarding the British public by approving electrical appliances and publishing lists of those approved. All approved goods will carry a distinctive mark. The scheme is open to all domestic electrical gear manufactured here or imported, and one of the aims is to encourage people to buy only approved goods bearing the special mark. A pity that the plan wasn't in force before those appliances whose triple flex leads don't conform to our standard were imported.

F.M. in France

WRITING from Aylesbury, a reader tells me that he has been able to receive the f.m. transmissions from Caen ever since they started, and that he has noticed the poor quality to which I referred a month or two ago in these notes. I'd have been inclined to put the shortcomings down to multi-path reception but for the fact that he writes that he regularly receives some of the West German stations and that the quality of their transmissions is superb. His view is that the French broadcasting engineers are so enthusiastic to push the volume up that they're apt to over modulate. But the cause of the trouble could easily be in the links, radio or cable, between studios and transmitters. Anyhow, as I mentioned before, many French listeners are so dissatisfied with the quality that f.m. receivers are much less common than had been expected.

TV Hazards

UNTIL a doctor friend showed me a recent issue of *The Lancet* I'd no idea that watching the TV screen could be so hazardous an occupation! It appears, though, that prolonged viewing from a chair of the wrong height, or lounging in an easy chair as you watch can bring on pains in the neck and cause damage to veins and arteries. I'll admit that certain items can themselves be pains in the neck—or would be if you were compelled to watch them. There are about half-a-dozen other dire perils to the human frame included in the article. But I was relieved to read they are not serious threats provided that you don't view to excess, wear tight garments or sit in slouchy attitudes. Anyhow, I shall use my set as hitherto and risk it.

UNBIASED

By FREE GRID

Why Electron?

IN many textbooks on elementary electricity and magnetism we are told that when the ancient Greeks rubbed a piece of what they called electron, they found it produced what we to-day call electrostatic effects. From other sources we learn that two thousand years later Dr. William Gilberd, of Colchester, demonstrated this effect to Queen Elizabeth I by rubbing a piece of amber on her silk stockings.

Now this explanation is all right as far as it goes but the trouble is that it does not go far enough. None of the textbooks, as far as I am aware, go on to explain that long before Thales, of Miletus, discovered the electrostatic properties of amber, it had been given the name of electron because it had been observed that it exhibited what we today would call electromagnetic properties. In short, it was called electron because it exhibited electrical properties; and the contrary, that the electrical properties it exhibited were so-called because its name happened to be electron is *not* true.

Before you all seize your pens and bottles of H_2SO_4 to write vitriolic letters to the Editor saying "Free Grid must go," I would ask your indulgence while I amplify my remarks. Most authorities are agreed that amber was first brought to Greece by foreign traders, most probably the Phœnicians who would naturally have their own name for it. Since they spoke a Semitic tongue it wouldn't surprise me if it bore some slight resemblance to our own word amber which is also of Semitic origin, being a corrupted form of the Arabic word anbar.

Probably the Greeks would simply have Hellencised the Phœnician name but they noticed that it had the same property of "glittering" or reflecting light as was possessed by other substances they already had, namely gold, silver and certain alloys which had already been given the generic name of electrons simply because they glittered or, as we should say, reflected or re-radiated electromagnetic waves in a certain band of the spectrum which we call light waves.

To get at the exact meaning of the word electron we split it up into its component parts elec-tron, the first part being part of the Greek word elector meaning dazzling (and umpteen synonyms). The suffix "tron," as we were told years ago in the pages of *Wireless World* by the late L. H. Bainbridge-Bell*, means the agency by which a thing is brought about. In English, except in the case of thermionic valve nomenclature, we write "tron" as "tre" as in theatre, which simply means a place which enables us to view (a play, etc.).

* Letter to the Editor, April 1947.

Dr. Gilberd demonstrates

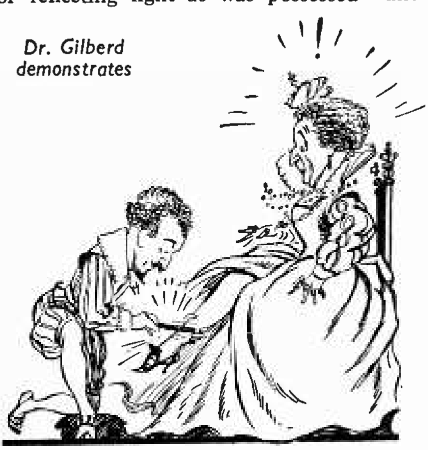

Is History Bunk?

NOWADAYS it has become fashionable to believe that it was the Duke of Richmond rather than Richard III who caused Edward V and his brother to be bumped off. This is very confusing to those of us who were brought up to regard wicked Uncle Richard as a nepoticide. We can't do much about all this confusion but what I think we can do is to be sure that we get our own contemporary history correct so that our descendants don't have to unlearn what they will be taught at school about things which happen in our time.

I am, of course, thinking more of the history of radio than of anything else because I recently read some startling statements about the history of the B.B.C. which ought not to go unchallenged. Recently a well-known journal has been serializing the life of Gordon Selfridge, the founder of what used to be called "a certain Oxford Street store" in the days when the B.B.C.'s 2LO transmitter was housed there.

The historian said in one of the instalments that the transfer of the 2LO transmitter from Marconi House to Selfridge's was effected and a more powerful transmitter built because of the coming into use of more and more *valve* receivers. The logic of this argument is so fatuous that I won't deal with it further except to say that the real reason for the transfer was that it was desired to increase power in order to extend the range of the transmitter. This could not be done at Marconi House without causing further interference with the Air Ministry receivers nearby. Also, of course, the aerial on the roof of Marconi House and the transmitter in the building were only lent by Marconi's.

Learned Lucubrations

OUR sister journal, until December 1959, *Electronic & Radio Engineer*, and now *Electronic Technology*, has had a career rather like that of a Hollywood star in the matter of nominal inconstancy, but it has never divorced itself from any of the principles with which it started its career in October, 1923, under the title of *Experimental Wireless.* Indeed, so far from any question of divorce arising in its career, it was quite early (September, 1924) joined in marriage with another journal, *Wireless Engineer* which, as in the case of many marriages, eventually ceased to be the nominal junior partner.

I well recollect discussing with the late P. K. Turner, at one time editor of the journal, the merits of a new tuning unit which had been marketed for the purpose of enabling a simple broadcasting receiver to be built with the minimum of trouble. A set was built with this unit, and details published in *Wireless World* (July 1st, 1925), the designer being a very august member of the world of wireless who preferred to hide his light under a bushel by adopting the pseudonym of Wilson.

I had expressed approval of the tuning unit on the grounds that it was neat and compact, in striking contrast to the mass of straggling wires and plug-in coils which were the curse of sets of those days. P. K. Turner treated my remarks with withering scorn on the ground that I had not measured the r.f. resistance of the coil and, therefore, was not in a position to express an opinion in favour of the tuning unit or otherwise.

However, as I told him, he and his journal were as far removed from the everyday world of the average none-too-technical set constructor and broadcast listener as a racing car enthusiast from the ordinary motorist. Yet, of course, were it not for the efforts of the racing motorist, and the mathematics with which the pages of *Electronic Technology* are bespattered by the backroom boys in their learned lucubrations we should never be able to enjoy the comforts of our family cars and domestic sound and television receivers.

more for less... with the MULTIMINOR

Designed to offer the widest possible range of accurate and reliable measurements at the lowest possible price, the versatility and usefulness of the Multiminor is now further extended by specially designed leads. These new leads, available at no extra cost, will accept crocodile clips or PRODCLIPS.

The Multiminor takes full advantage of the possibilities of printed circuit techniques to achieve outstanding compactness and economy of weight. The scale is clear and open. The fine red coloured pointer and effectively damped movement facilitate easy and rapid reading.

For use in Radio, TV, Electronics, Motor Vehicles, domestic appliances, workshop equipment, you'll find the Multiminor a great little meter!

Use PRODCLIPS *(Pat. No. 748811)* with the Multiminor

These cleverly designed spring-loaded insulated prods are the complete answer to a long-standing problem. Press the trigger to open, release to grip. Keep your hands free no matter how difficult of access your test points may be!

15/- *per pair*

19 Ranges

D.C. Voltage	A.C. Voltage
0 — 100mV.	0 — 10 V.
0 — 2.5 V.	0 — 25 V.
0 — 10 V.	0 — 100 V.
0 — 25 V.	0 — 250 V.
0 — 100 V.	0 — 1000 V.
0 — 250 V.	**D.C. Current**
0 — 1000 V.	0 — 100μA
	0 — 1mA
Resistance	0 — 10mA
0 — 20,000 Ω	0 — 100mA
0 — 2 MΩ	0 — 1 A

AVO *Regd. Trade Mark*

List price **£9:10s.**

Complete with Test Leads and Crocodile Clips.

Leather case if required 39/-.

Size: 5⅝ x 3⅝ x 1¼in

Weight: 1lb. approx.

MULTIMINOR FITS THE POCKET 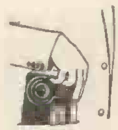 FILLS THE BILL

Write now for illustrated literature to:

AVO LTD. AVOCET HOUSE · 92-96 VAUXHALL BRIDGE ROAD · LONDON, S.W.1

VICtoria 3404 (12 lines)

A MEMBER OF THE METAL INDUSTRIES GROUP OF COMPANIES

MM12

Pioneering

T/V - FM RELAY AND COMMUNAL AERIAL SYSTEMS

Produced this high standard Today!

Backed by years of experience, Teleng is the ONLY complete range of equipment that enables any size of co-axial cable system to be built up to any number of outlets for standard T/V-F/M receivers. Such systems have known and measurable performance, and fully obey P.O. Engineering Department requirements.

Full advice and planning services are available without obligation of any kind.

● CO-AXIAL CABLES AND CABLE FITTINGS

Single and double screened Cables with or without embedded catenary. All Performance Certificated.

All types of indoor or outdoor Splitting, Teeing, Tapping, Outlet, Junction and Load Units for co-axial networks.

● MEASURING INSTRUMENTS

Mains operated V.H.F.-V.V. for amplifier and repeater alignment.

Battery operated Signal Level Meters for system servicing.

● AMPLIFIERS AND SIGNAL CONVERTERS

Mast Head and Boost amplifiers for all purposes and any channels, with gains from 12 to 56 db. Band 1/Band 1, or Band 3/1 converters with or without AGC and crystal control.

● REPEATERS

All types of Repeaters single channel or wide band with and without AGC and including channel or band combining networks.

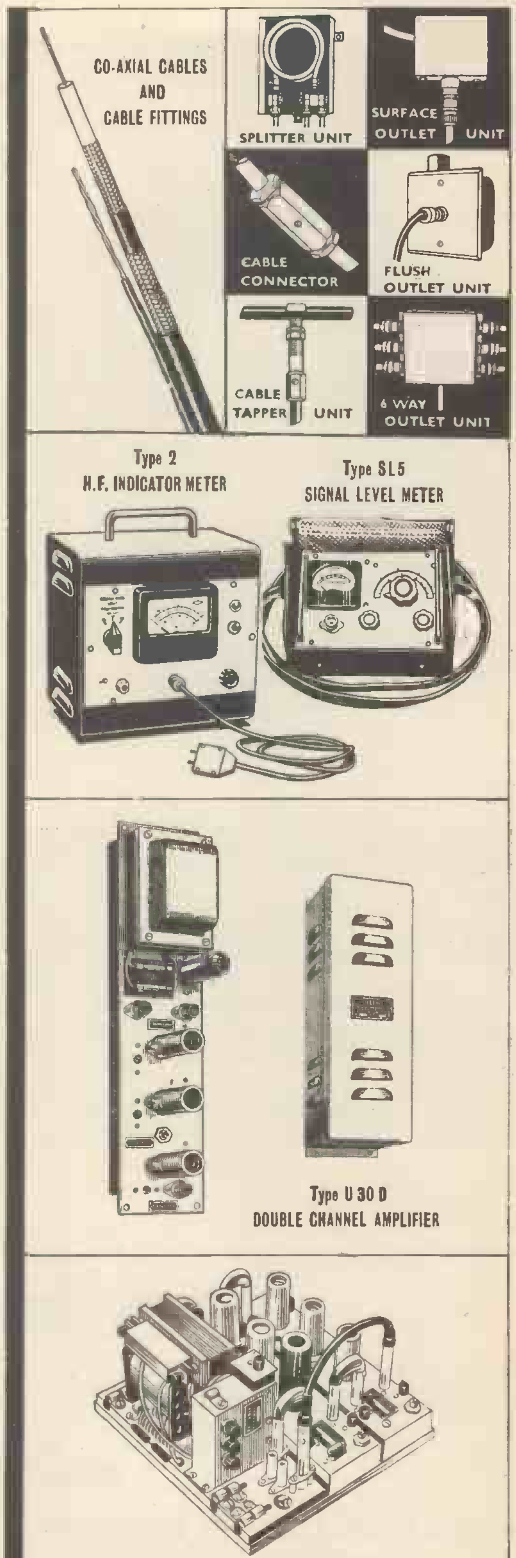

Specify TELENG

Send for lists—'W.T.' Series for Relay Systems
'U' Series for Communal Aerial Systems

TELENG LIMITED TELENG WORKS, CHURCH ROAD, HAROLD WOOD, ROMFORD, ESSEX

Ingrebourne 42901

DELAYED PULSE AND SWEEP GENERATOR

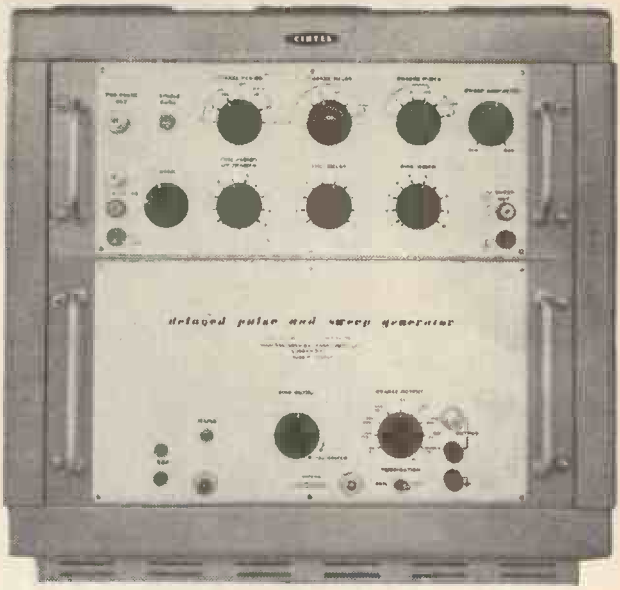

A versatile pulse generator designed to meet the need for a comprehensive instrument covering a wide range of pulse work. Four main facilities are provided: a pre-pulse, a main pulse delayed on the pre-pulse, a negative going sawtooth and a fast rising pulse formed from a pure line.

BRIEF SPECIFICATION

Period

Continuously variable from 0·9μsec to 1·05sec i.e. 0·95c/s to 1·1Mc/s. Accuracy ±5%.

Pre-pulse

40mμsec. 8V peak in 75Ω, positive going.

Main pulse

Width:	Variable from 0·09μsec to 105msec ±5%.
Amplitude:	Control gives 4:1 attenuation of each of four maximum outputs as follows:
	5V max in 75Ω rise time 10mμsec
	10V max in 150Ω rise time <20mμsec
	25V max in 600Ω rise time <40mμsec
	50V max in 1000Ω rise time 50mμsec
Polarity:	Positive or negative going.
Accuracy:	±2%.

Delay

Conclusion of pre-pulse to advent of main pulse, delay variable from 0·09μsec to 105msec. Accuracy ±5%.

Sweep

D.C. coupled negative going sawtooth same width and delay as main pulse.
15V peak max.

Cable pulse

Obtained from short circuited pure line.
One positive and one negative going pulse coincident with main pulse.
25mμsec wide 3V max in 75Ω, rise time <8mμsec.

Sync, trigger or single shot facilities provided.
Full data available on request.

CINTEL

RANK CINTEL LIMITED
WORSLEY BRIDGE ROAD · LONDON · SE 26
HITHER GREEN 4600

Sales and Servicing Agents: Atkins, Robertson & Whiteford Ltd., Industrial Estate, Thornliebank, Glasgow.
McKellen Automation Ltd., 122 Seymour Grove, Old Trafford Manchester, 16. Hawnt & Co., Ltd., 59 Moor St., Birmingham, 4.

Leading Radar Manufacturers use Ferranti T.R. Cells in Airborne, Ground and Marine Radar Systems. A comprehensive range of T.R. Cells is available covering frequencies from 1000 Mc/s. to 35,000 Mc/s.
Write for further information to:

FERRANTI LTD · KINGS CROSS ROAD · DUNDEE Tel: DUNDEE 87141

Ferranti

DS/T64

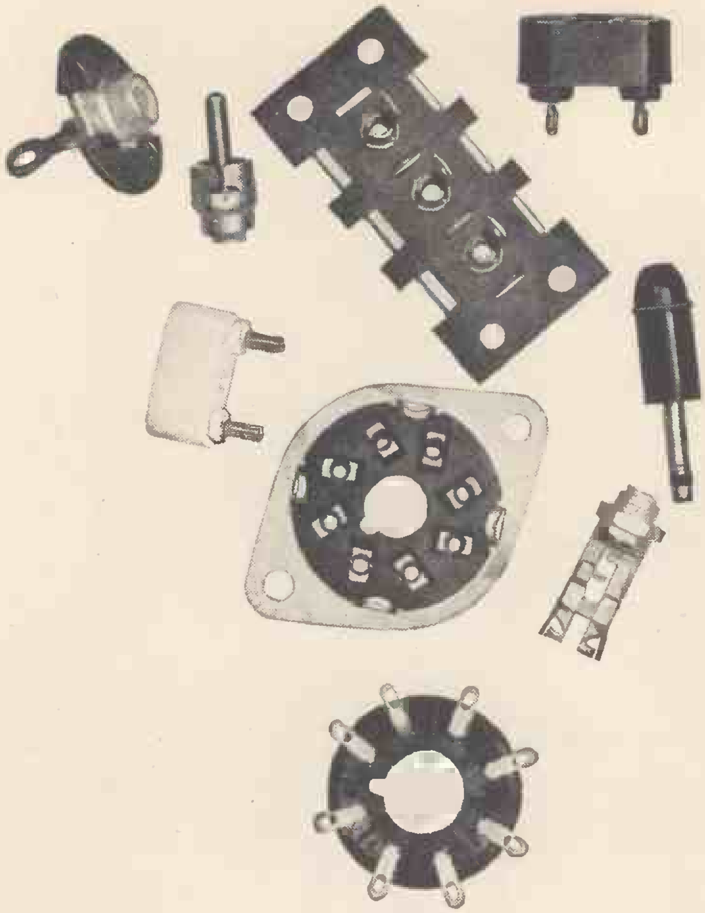

Heathkit

DAYSTROM

We can now import practically any American Heathkit model. Tell us what you want and we will send prices.

"GLOUCESTER" STEREO CABINET KIT

Will house Tape Deck and/or Record Player, F.M. Tuner and Stereo Amplifier. Storage space for records, tapes and power amplifier. 46½in. long, 30in. high, 21in. deep. "In the white" for finish to personal taste.

Mk. I for Tape Deck or Record/Player **£15.18.6**
Mk. 2 for both Tape Deck and Record Player **£17.8.6**

"COTSWOLD" HI-FI SPEAKER SYSTEM KIT

Acoustically designed enclosure "In the white" 26in. x 23in. x 15½in., housing a 12in. bass speaker with 2in. speech coil, elliptical middle speaker together with pressure unit to cover the full frequency range of 30–20,000 c/s. Complete with speakers, cross-over unit, level control, etc. **£19.18.6**

5 in. OSCILLOSCOPE KIT Model O-12U

Has wide-band amplifiers, essential for TV servicing, F.M. alignment, etc. Vertical frequency response 3 c/s. to over 5 Mc/s. without extra switching. T/B covers 10 c/s. to over 500 kc/s. in 5 steps **£34.15.0**

ELECTRONIC SWITCH KIT Model S-3U (Oscilloscope Trace Doubler)

Enables a single beam oscilloscope to give simultaneous traces of two separate and independent signals. Switching rates approx. 150, 500, 1,500, 5,000 and 15,000 c/s. Sig. freq. response 0–100 kc/s. ± 1 dB. Separate gain controls and sync. output. Sig. input range 0.1–1.8 v. r.m.s. **£9.18.6**

AMATEUR TRANSMITTER KIT Model DX-100U

Covers all amateur bands from 160–10 metres. Self contained including Power Supply, Modulator and V.F.O. **£78.10.0**

TRANSCRIPTION RECORD PLAYER Model RP-1U

4-speed A.C. motor. Ronette Stereo/Mono pick-up. Complete on plinth. **£12.10.0**

CAPACITANCE METER KIT Model CM-1U

Direct-reading 4½in. scale. Full-scale ranges 0-100μμF, 0-1,000μμF, 0-0.01μF and 0-0.1μF. **£14.10.0**

HI-FI STEREO AMPLIFIER KIT Model S-88

16 w. output, 10 mV. basic sensitivity (2 mV. available, 30/- extra). Ganged controls. Stereo/Monaural gram., radio and tape recorder inputs. Push-button selection. Two-tone grey metal cabinet **£25.5.6**

6-W STEREO AMPLIFIER KIT Model S-33

3 watts per channel, 0.3% distortion at 2.5 w/chnl., 20dB N.F.B. Inputs for Radio (or Tape) and Gram., Stereo or Monaural, ganged controls. Sensitivity 100 mV. **£11.8.0**

TRANSISTOR PORTABLE KIT Model UXR-1

Pre-aligned I.F. transformers, printed circuit and a 7x4in. high-flux speaker. Real hide case **£15.18.6**

"HAM" TRANSMITTER KIT Model DX-40U

From 80-10 m. Power input 75 w. C.W., 60 w. peak controlled carrier phone. Output 40 w. to aerial. Provision for V.F.O. **£29.10.0**

AUDIO VALVE MILLIVOLTMETER KIT AV-3U

1 mV. to 300 v. A.C. 10 c/s. to 400 kc/s. **£13.18.6**

VALVE VOLTMETER KIT Model V-7A

7 voltage ranges d.c. volts to 1,500, a.c. to 1,500 r.m.s. and 4,000 peak to peak. Resistance 0.1 ohm. to 1,000 M. ohms with internal battery. D.C. input impedance 11 megohms. dB measurement has centre-zero scale. Complete with test prods, lead and standardising battery. **£13.0.0**

R.F. PROBE KIT Model 309-CU

Extends the frequency range of our V-7A to 100 Mc/s. and enables useful voltage indication to be obtained up to 300 Mc/s. **£1.5.6**

AUDIO SIGNAL GENERATOR KIT Model AG-9U

10 c/s. to 100 kc/s., switch selected. Distortion less than 0.1%. 10 v. sine wave output metered in volts and dB's. **£19.3.0**

RESISTANCE-CAPACITANCE BRIDGE KIT

Model C-3U Measures capacity 10pF to 1,000μF., resistance 100Ω to 5 MΩ and power factor. 5-450 v. test voltages. With safety switch. **£7.19.6**

VF-1U

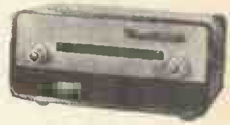

F.M. TUNER

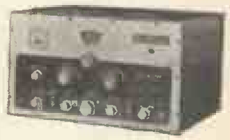

DX-100U

S-88

UXR-1

● *Please see last month's advertisements for fuller details of our kits* ●

STEREO-HEAD BOOSTER KIT Model USP-1

Hi-Fi Stereo pre-amplifier for low-output Hi-Fi P.U.'s. Input 2 mV. to 20 mV. Output adjustable from 20 mV. to 2 v. 40–20,000 c/s. Also suitable as low-noise R.C.-coupled high-gain monaural amplifier. **£5.19.6**

VARIABLE FREQUENCY OSCILATOR KIT MODEL VF-1U

From 160–10 m. Ideal for our DX-40U and similar transmitters. **£10.12.0**
Price less valves £8/19/6.

HI-FI SPEAKER SYSTEM KIT Model SSU-1

Ducted-port bass reflex cabinet "in the white." Twin speakers. With legs £11/12/6. **£10.5.6**

DUAL-WAVE TRANSISTOR RADIO KIT Model UJR-1

This sensitive headphone set is a fine introduction to electronics for any youngster. **£2.16.6**

★ *FREE ON REQUEST! A copy of our (British Heathkit Catalogue. Prices include free delivery in the U.K.*

HI-FI F.M. TUNER

Tuning range 88-108 Mc/s. For your convenience this is available in two units sold separately as follows:
Tuner Unit (FMT-4U) inc. P.T. With 10·7 Mc/s. I.F. output. **£3. 2.0**
I.F. Amplifier (FMA-4U) complete with case and valves. **£10.10.6**
TOTAL **£13.12.6**

MATCHED HI-FI STEREO KIT

We offer as a "packaged deal" the following matched Hi-Fi Stereo Equipment.

4-speed Record Player (RP-1U) ...	£12 10 0
6-W Amplifier (S-33)	£11 8 0
Twin Speaker System (SSU-1)	£20 11 0
Cost of Units	£44 9 0

At an "all-in" price of **£42.10.0**
Pedestal speaker legs £2/14/- optional extra.

AUDIO WATTMETER KIT Model AW-1U

Up to 25 w. continuous, 50 w. intermittent £13 18 6

● **Deferred terms available on all orders above £10.** ●

DAYSTROM LTD.

DEPT. W.W.2. GLOUCESTER, ENGLAND

A member of the Daystrom Group, Manufacturers of

THE WORLD'S LARGEST-SELLING ELECTRONIC KIT-SETS

Please tick the items in which you are interested and we will send you full details.

	S-88	Hi-Fi Stereo Amplifier Kit
	S-33	6-Watts Stereo Amplifier Kit
	UXR-1	Transistor Portable Kit
	DX-40U	"Ham" Transmitter Kit
	O-12U	5in. Oscilloscope Kit
	V-7A	Valve Voltmeter Kit
	SSU-1	Hi-Fi Speaker System Kit
	AG-9U	Audio Signal Generator Kit
	C-3U	Resistance-Capacitance Bridge Kit
	VF-1U	Variable Frequency Oscillator Kit
	USP-1	Stereo-Head Booster Kit
	UJR-1	Dual-Wave Transistor Radio Kit
	DX-100U	Transmitter Kit
	S-3U	Electronic Switch Kit
	FM-4U	F.M. Tuner
		Matched Hi-Fi Stereo Kit. *Complete*
		"Gloucester" Stereo Cabinet Kit
		"Cotswold" Speaker System Kit
	309-CU	R.F. Probe Kit
	RP-1U	Transcription Record Player
	CM-1U	Capacitance Meter Kit
	AV-3U	Audio Valve Millivoltmeter Kit
	AW-1U	Audio Wattmeter Kit

Please print name and address in margin below. W.W.2.

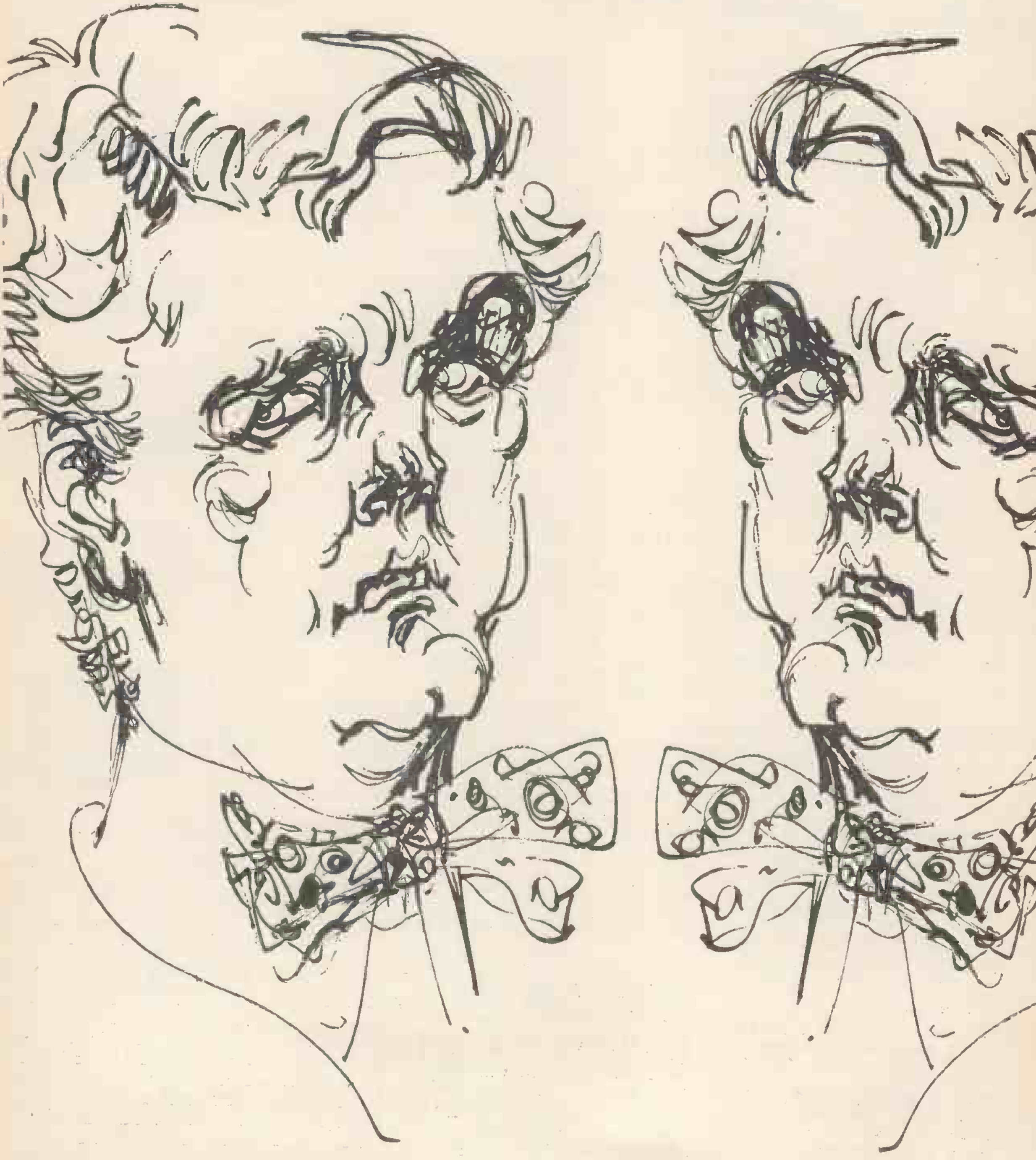

No. 21

Permanent Magnets

Design Advisory Service

Nuclear Magnetic Resonance Magnets

Advertisements in this series deal with general design considerations. If you require more specific information on the use of permanent magnets, please send your enquiry to the address below, mentioning the Design Advisory Service.

During the past three years, Mullard have pioneered the manufacture of permanent magnets for Nuclear Magnetic Resonance (N.M.R.) spectroscopy. These magnets are required to give a high order of magnetic uniformity in the gap and maintain extreme stability. This has been achieved in specially designed magnet assemblies using high energy 'Ticonal' G magnets.

N.M.R. may be detected as an absorption of radio frequency energy when a sample containing nuclei with non-zero spin is placed in a magnetic field. The resonant frequency is proportional to the magnetic field and for protons, occurs at 40 Mc/s in a field of approximately 9400 gauss.

The magnetic field at the various nuclei in the sample may be slightly different due to the interactions of the surrounding electrons and nuclei. Consequently, observation of the absorption of energy, produces either a modified line shape or a group of lines (N.M.R. spectra). N.M.R. spectra of liquids are of particular interest because of the relatively simple spectra which in many cases enable the structure of the molecule to be definitely prescribed. For spectra of this kind, resolution of the order of 1 in 10^8 must be obtained. Resolution of this order has been achieved using Mullard permanent magnets.

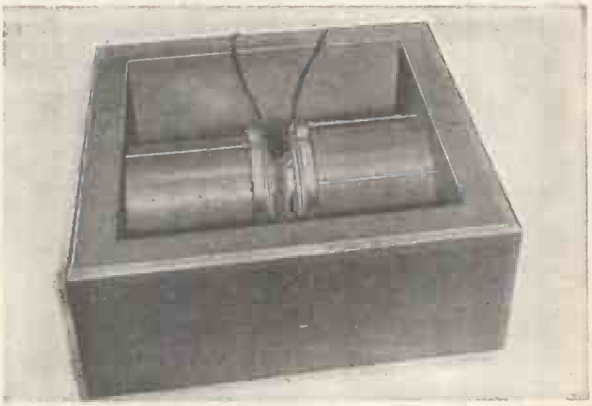

Mullard N.M.R. magnet type XA

Magnets type EA and type EB are supplied totally enclosed and temperature controlled at 30°C. to within milli-degrees. These types are also available without temperature control as types XA and XB. An abridged specification of these magnets is given in the table.

		XA	EA	XB	EB
Nominal gap flux	(gauss)	9400	9400	5500	5500
Min. uniformity of field over 1cm³	(gauss)	0.1	0.1	0.1	0.1
Working gap	(inches)	1.25	1.25	1.25	1.25
Pole diameter	(inches)	6.0	6.0	5.0	5.0
Weight (approx.)	(tons)	1.2	1.3	0.25	0.3
Field shift coils	(gauss)	±50	±50	±50	±50
Field sweep coils	(gauss)	±5	±5	±5	±5
Overall size	(inches)	30.5 x 38 x 16	47 x 47 x 38	22.5 x 24.5 x 10	38.5 x 40.5 x 33

If you wish to receive reprints of this advertisement and others in this series write to the address below.

Mullard

'TICONAL' PERMANENT MAGNETS
'MAGNADUR' CERAMIC MAGNETS
FERROXCUBE MAGNETIC CORES

MULLARD LIMITED, COMPONENT DIVISION MULLARD HOUSE, TORRINGTON PLACE, W.C.1. LANgham 6633

MC284

Sound all round to give you utmost realism . . . the true reproduction of the original! The new Brenell 3 star three speed record playback stereo is one of the most convincing recorders of sound over the full audio range and it not only records and replays stereo but monaurally too! Its use as a stereo or monaural amplifier from gram pick-ups is also a wonderful asset to the hi-fi user. Price 89 GNS. or with two microphones 95 GNS.—

★ Extremely simple to operate. All controls, input and output sockets grouped *at front of recorder*
★ Frequency compensation at 3 speeds ($7\frac{1}{2}$, $3\frac{3}{4}$ and $1\frac{7}{8}$ i.p.s.)
★ Two modulation indicators—one for each track
★ Two speakers contained within the cabinet
★ Two amplifiers with wide range bass and treble controls
★ Amplifiers may be used independently for reproduction of stereo disc recordings when connected to stero pick-up
★ Exceedingly low cross talk (−60 db)
★ Either track may be replayed whilst the other track is being recorded

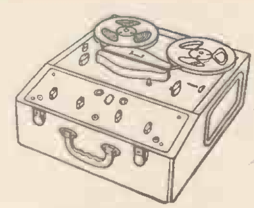
Mk. 5 64 GNS.

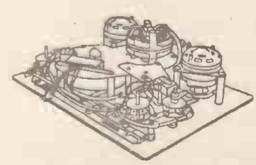
Tape Deck 28 GNS.

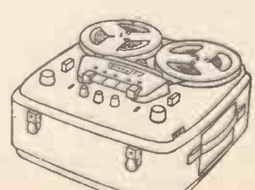
3 star 58 GNS.

Brenell

Brenell performance is true-to-life performance

Details from sole manufacturers:—

BRENELL ENGINEERING CO. LTD., IA DOUGHTY ST., LONDON, W.C.1. CHA. 5809 & HOL. 7358

GD29

DOUBLE ENDED STAINLESS STEEL VACUUM OVENS

- ★ Made throughout in polished stainless steel.
- ★ Single action door openings.
- ★ Rectangular with shelf spacings to suit.
- ★ Double ended controls.
- ★ Electrical interlocking of air inlet and isolation valves.
- ★ Outer cover hermetically sealed.
- ★ Temperature range 0°-300°C or equivalent F.
- ★ Temperature Control:
  Normal $\pm 7\frac{1}{2}$°C.
  Special ± 1C
- ★ Internal Spacing 7in. x 8in. x 18in. (can be altered to special requirements).
- ★ Vacuum Range: To 10–4.
- ★ Respective Vacuum Gauges incorporated.
- ★ Automatic air inlet valve on Backing Pump.
- ★ Visual Indicators and fuses on all switches.
- ★ Flanged for fitting into Dry Box.

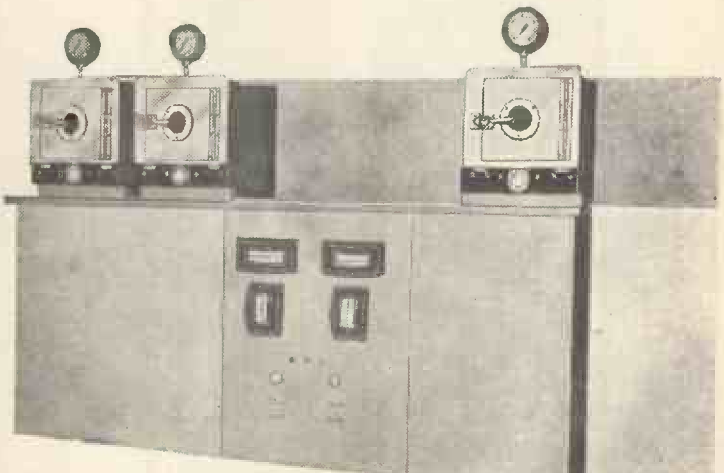

These photographs show how a complete sequence of production can be organised without exposure to atmosphere, by means of our Ovens.

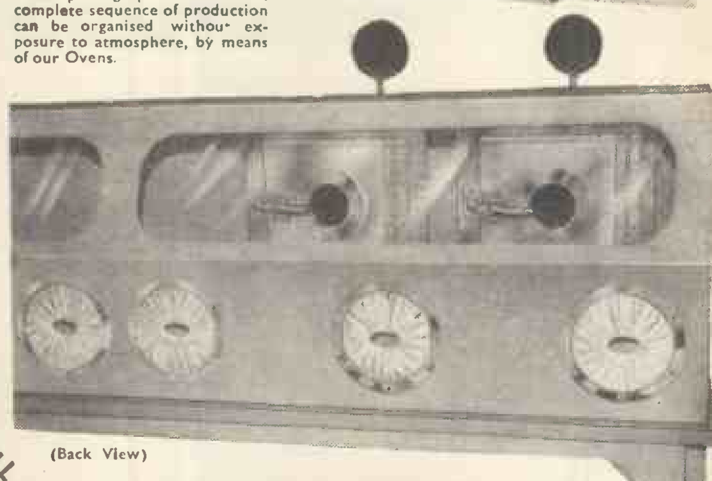

(Back View)

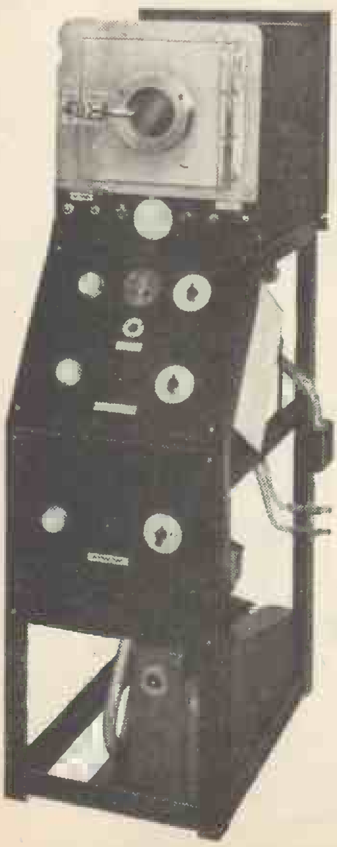

VACWELL ENG., CO. LTD.

We design and manufacture Ovens to Customers' special requirements. Should you have any problems in this field our Technical Department is always willing to help you solve them.

Vacuum Ovens with temperatures of up to 600°C are also manufactured by us on similar lines but with Sectional Heating and Water-Cooled Ends.

VACWELL ENGINEERING CO. LTD.

WILLOW LANE · MITCHAM · SURREY

PHONE, MITcham 8211 (3 lines)

joint responsibility...

To rely on Enthoven for *all* your soldering requirements is a policy that will take a load off your shoulders . . .

Superspeed and Superspeed 'XX' cored solders are unequalled for general assembly work on radio, television, electronic and telecommunication equipment:

Enthoven preforms, such as cored solder washers, rings and pellets, are available or can be designed to meet the precision requirements of the most advanced manufacturing techniques:

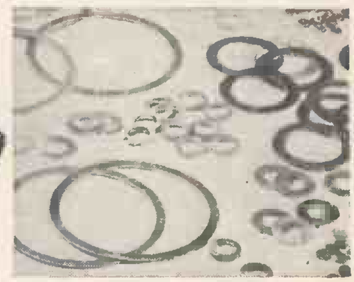

Enthoven aluminium cored solder is the perfect medium for soldering aluminium to aluminium — or aluminium to copper, tinned copper, tinned and silver-plated brass and most other non-ferrous metals:

ENTHOVEN

SOLDER PRODUCTS

The comprehensive Enthoven range of solder products comprises cored solder wire, solid solders, materials for soldering **aluminium** and for the processing of printed circuits, fluxes of all kinds, standard and special preforms and many other special-purpose products. For technical information on all these items please send today for your copy of "Enthoven Solder Products" — or for more detailed technical literature on any soldering material in which you are specifically interested.

ENTHOVEN SOLDERS LIMITED
Sales Office & Works: Upper Ordnance Wharf, Rotherhithe Street, London, S.E.16. Telephone: BERmondsey 2014

Head Office: Dominion Buildings, South Place, London, E.C.2.
Telephone: MONarch 0391

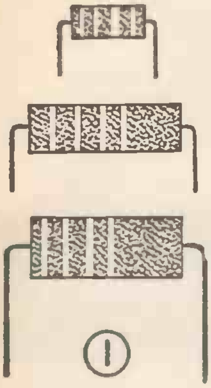

1

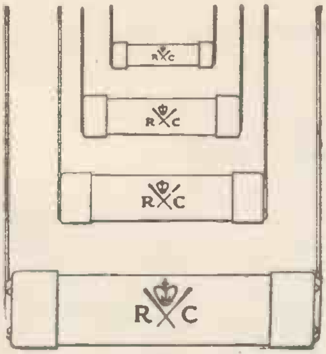

3

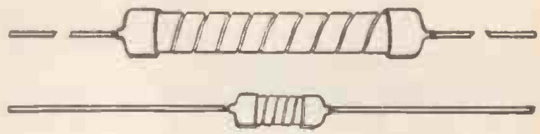

9

5

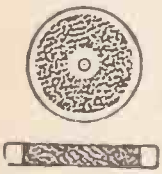

6

7

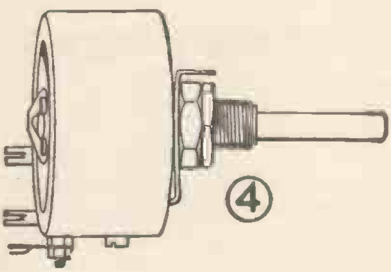

4

A SERVICE FOR DESIGNERS

The possibility of a component change—due to shortage of supplies, increased costs or failure to meet specific conditions—is a problem facing every designer of electronic equipment. However, one basic component can be "tailor-made" from the start, for LAB will supply the precise type of Resistor required, ex stock *and* at the right price. Write for full technical data, prototype samples and price schedules to:—

THE RADIO RESISTOR CO. LTD.,
50 ABBEY GARDENS, LONDON, N.W.8.
Telephone: Maida Vale 0888

CARBON	WATTS	OHMIC RANGE	TOLERANCES ±
1. Solid	½ 1 and 2	10—10M	5% and 10%
2. Cracked	1/30—20	1—500M	5% and 10%
3. * High Stability	1/10—3	1—50M	0.5% 1% 2% 5%
4. Variable	¼	5K—2M	—
5. V. High Resistance	¼—3	50M—10^{13}	5% and 10%
6. V.H.F. (Rods and Discs)	1/10—1	10—1K	1% and 2%
WIREWOUND			
4. Rheostats	4—500	10—18K	—
8. Vitreous	3—500	1—150K	1% 2% 5%
7. Cemented	1—15	1—25K	5% and 10%
9. Metal Oxide	¼—2	100—4.2M	1% 2% 5%

* The ubiquitous blue (1%) grey (2%) "HISTABS"

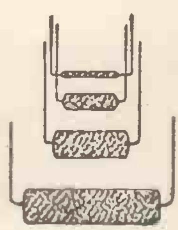

2

8

Do you KNOW

THAT Cracked Carbon Resistors (2) are more economical in the ±5% range than Solid Carbon.

THAT the sub-miniature 1/30th watt unit (2) is probably the smallest production Resistor made.

25 YEARS LAB
JUBILEE YEAR OF RESISTOR SPECIALISATION

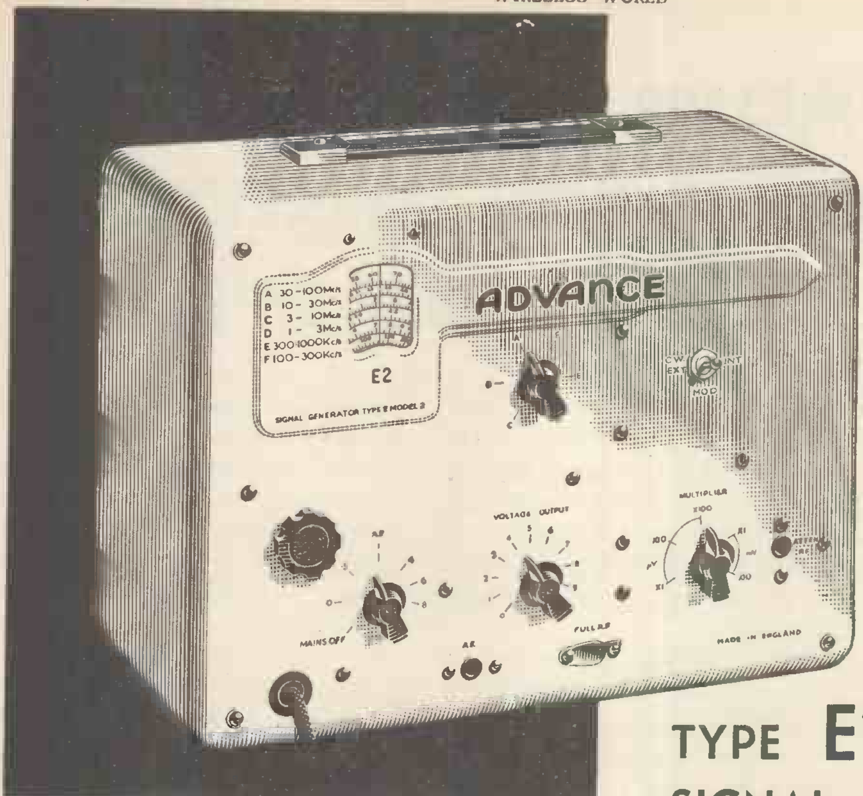

100 kc/s to 100 Mc/s
ON FUNDAMENTALS
(Amplitude Modulated)

TYPE E2 SIGNAL GENERATOR

by *Advance*

—to be sure!

The introduction of the Type "E" Series in 1946 set an entirely new standard in Signal Generators for the Service Engineer. To-day, over 10,000 models are being used throughout the world—from Antarctica to the Tropics.

Among this instrument's outstanding features are:—

Wide Frequency Range .... 100 kc/s to 100 Mc/s.
Exceptionally low leakage ... less than 3μV. at 100 Mc/s.
Reliable Attenuator ... Output variable over 100 dB from 1μV. to 100 mV.
Force Output .... providing 1 volt at all frequencies.

NETT PRICE **£34** IN U.K.
Full technical details in Leaflet No. W42

Advance COMPONENTS LIMITED
INSTRUMENTS DIVISION
ROEBUCK ROAD • HAINAULT • ILFORD • ESSEX TELEPHONE : HAINAULT 4444

GD 69

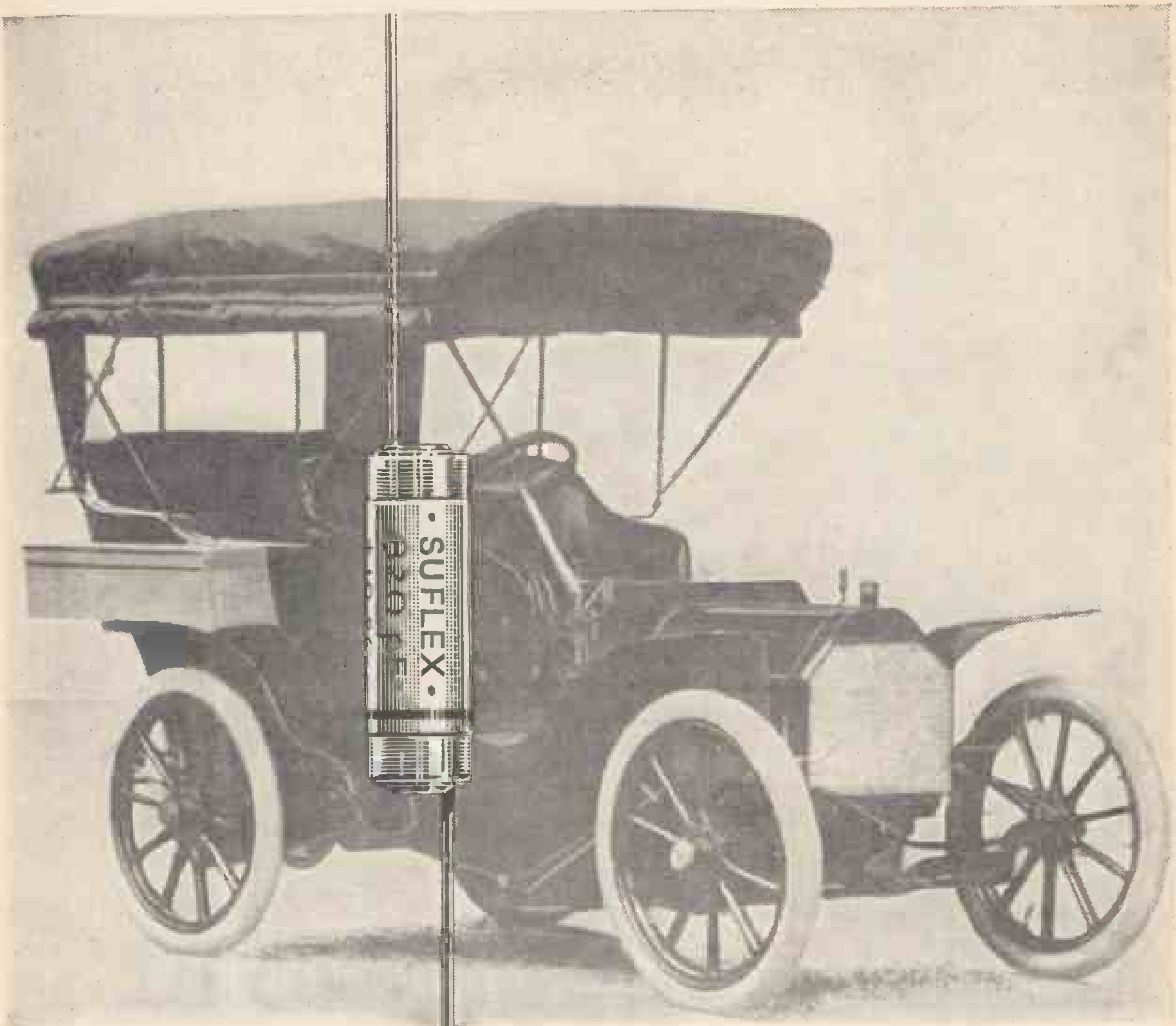

AGEING

The parameters of young capacitors tend to be changeable. Polystyrene capacitors are therefore exposed to extremes of climate (Russian winters and New York summers) in rapid succession. This would put years on anybody's life. By the time a Suflex Capacitor reaches you, it has left the frolics of youth and reached mature dependability: exceptionally good stability, high dielectric strength, low loss. And no middle-age spread whatsoever, for the Suflex Polystyrene Capacitor is as small as any for a given rating. Altogether, a capacitor in the prime of life, steady and fighting fit.

SUFLEX Limited LONDON

Suflex Polystyrene Capacitors

SUFLEX LTD

35 Baker Street, London W.1 Telephone: WELbeck 0791

Transistorised Four-Channel Mixing Units

This Pye fully transistorised 4-channel Audio Mixing Unit meets the need for a portable high-gain mixing amplifier which may be used with equal facility for sound and TV outside broadcasts, auxiliary studio installations or for augmenting and, in an emergency replacing, existing mixing facilities. The removable A.C. mains power unit can be quickly replaced by either an accumulator unit or a dry battery unit. Robust and light—it is easily carried in a brief case—this unit will prove invaluable to mobile recording and news-coverage teams.

Type 3053 Pye Audio Mixing Unit

The rear view of the Audio Mixing Unit (Type 3053) shows the A.C. mains unit partially withdrawn. Any of the power input units which can be supplied as accessories (shown below) to the mixer can be inserted in the position shown. As well as the mains input socket and fuses, the picture shows the 4 channel input; sockets, the output sockets and terminals.

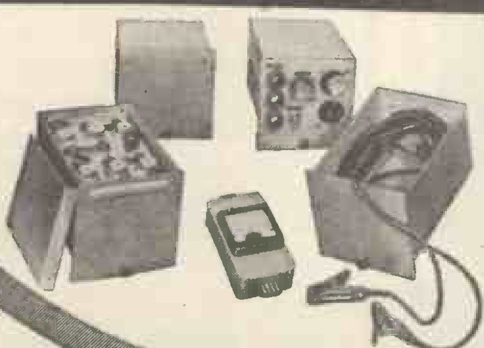

On the Audio Mixing Unit (Type 3803) a peak programme meter is provided in place of the VU Meter together with its associated PPM Amplifier.

PYE LIMITED
Sales Department
Television Transmission Division
CAMBRIDGE

Hermetic Sealing

STEATITE & PORCELAIN
NICKEL METALLISING

Quality Approved (Joint Service R.C.S.C.)

WILL MEET THE MOST EXACTING REQUIREMENTS

METALLISED BUSHES

Perfect Terminations

—made readily without special precautions by semi-skilled labour, employing simple hand soldering methods, R.F. Heating, Hot Plate, Tunnel Oven or similar mass production methods.

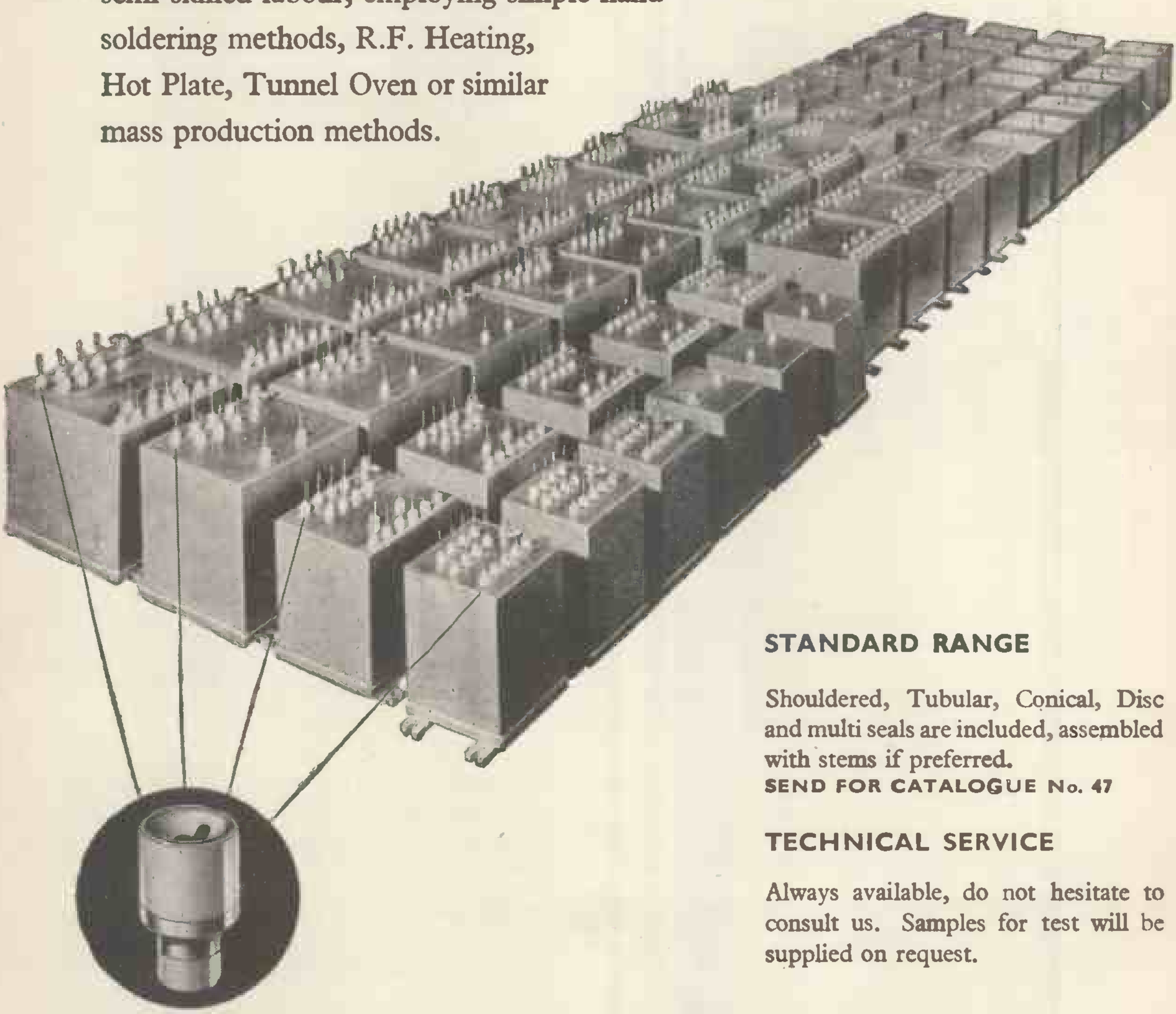

STANDARD RANGE

Shouldered, Tubular, Conical, Disc and multi seals are included, assembled with stems if preferred.
SEND FOR CATALOGUE No. 47

TECHNICAL SERVICE

Always available, do not hesitate to consult us. Samples for test will be supplied on request.

STEATITE & PORCELAIN PRODUCTS LTD.

STOURPORT ON SEVERN, WORCS. **Telephone: Stourport 2271** **Telegrams: Steatain, Stourport**

SP100

AMMONIA

From I.C.I. AMMONIA—

Nitrogen and Hydrogen for Industry

I.C.I. Ammonia provides industry with a cheap and reliable source of pure nitrogen and hydrogen. And I.C.I. gas generating plants are available to convert ammonia into a wide range of nitrogen/hydrogen gas mixtures.

Anhydrous Ammonia
with a guaranteed minimum purity of 99.98%, to meet more exacting requirements, is offered in bulk and in a wide range of cylinder sizes.

HYDROGEN

NITROGEN

Liquefied Ammonia *(Industrial Quality)*, a cheaper grade, is available in bulk and in two-ton containers for the larger consumer, and makes possible substantial economies in gas costs.

A bulk delivery of 10 tons of ammonia provides over 1¾ million cu. ft of nitrogen.

Full Information on request

IMPERIAL CHEMICAL INDUSTRIES LIMITED, LONDON, S.W.1.

ICI

BI.7

A higher standard of listening enjoyment and satisfaction in the home

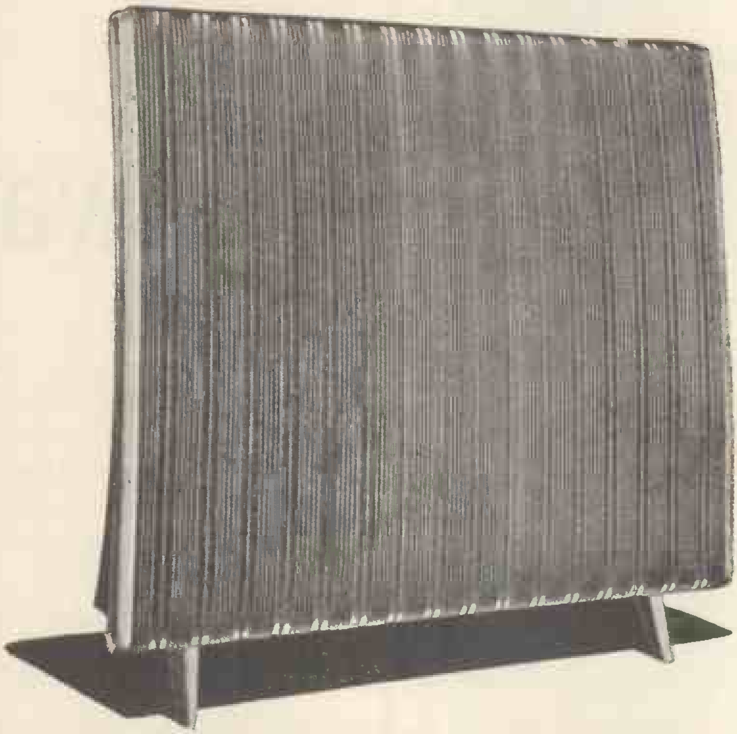

QUAD

ELECTROSTATIC LOUDSPEAKER

'For the closest approach to the original sound'

The Quad Electrostatic Loudspeaker is essentially an instrument designed for the home* of the music-lover with every emphasis towards the natural quality desirable for serious listening to music of all types. Of modest size, this loudspeaker is suitable for use in the average-sized lounge; it is capable of providing distortionless reproduction under such conditions up to a volume level similar to that experienced in the concert hall.

**Increasingly used in studios, monitor rooms and wherever standards have to be set—and maintained.*

Send a postcard marked W.W. for illustrated booklet.

ACOUSTICAL MANUFACTURING COMPANY LTD., HUNTINGDON, HUNTS. *Huntingdon 361*

Audio power output transistors

TYPES XC141 and XC142

These germanium p-n-p alloy junction transistors are designed for use in Class A and Class B power output stages of audio frequency amplifiers. Full particulars of these and other Ediswan Mazda semiconductor devices will be sent gladly on request. If you wish to be kept up to date with the latest developments in this field, please ask us to add your name to our semiconductor mailing list.

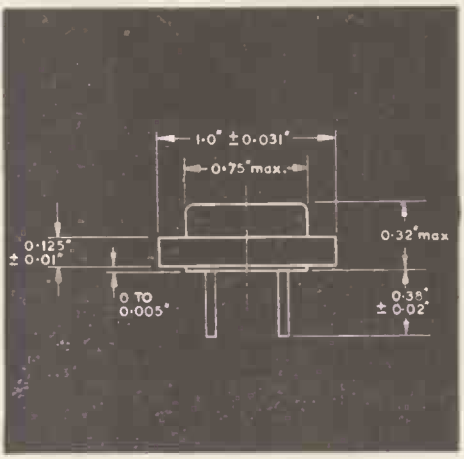

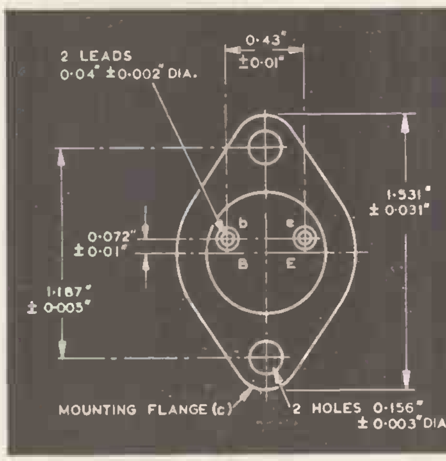

MAXIMUM RATINGS (Absolute Values)	XC141	XC142
Peak collector to base voltage (volts)	– 40	– 60
Peak collector to emitter voltage, emitter non-conducting (volts)	– 40	– 60
Peak collector to emitter voltage, emitter conducting (volts)	– 32	– 32
D.C. Emitter to base voltage (volts)	– 12	– 12
Peak collector current (amps)	– 3·0	– 3·0
D.C. Collector current (amps)	– 1·5	– 1·5
Collector dissipation (mounting flange temperature 80°C) (watts)	11	11

EDISWAN SEMICONDUCTORS
MAZDA

Associated Electrical Industries Ltd
Radio and Electronic Components Division
PD 15, 155 Charing Cross Road, London, W.C.2
Tel: GERrard 8660 Telegrams: Sieswan Westcent London

CRC15/58

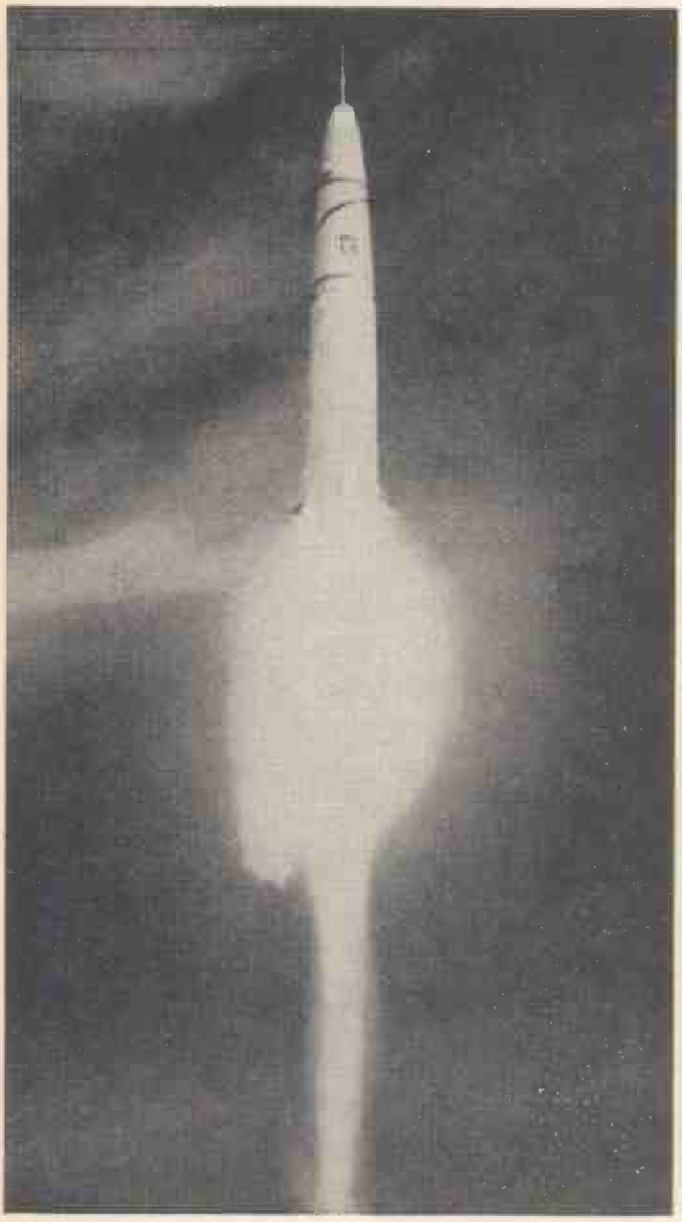

EIMAC CERAMIC-METAL REFLEX KLYSTRONS FOR SEVERE ENVIRONMENT APPLICATIONS

In modern airborne and missile systems, reflex klystrons must be capable of maintaining exceptional frequency stability under conditions of severe shock, vibration and acceleration. Eimac's new ruggedized X- and K-Band reflex klystrons achieve this stability through an advanced system of stacked-ceramic construction and integral brazed 'dual-cavity' design.

Ceramic construction permits internal electrodes to be supported on rigid concentric cones and allows the entire vacuum assembly to be furnace-brazed into a single rugged structure. The resonant cavity design consists of a fixed-tuned (and hence rugged) inner cavity closely coupled through a ceramic window to a secondary tunable cavity outside the vacuum envelope. The external cavity is tuned by means of a capacitive slug over a minimum range of 700 megacycles per tube.

This advanced design has resulted in a series of four exceptionally stable reflex klystrons covering the 8500 to 11,500 megacycle range at a typical output power level of 75 milliwatts. At vibration levels of 15 to 20G the peak-to-peak deviation of these tubes is less than 50 kilocycles for any vibrating frequency from 20 to 2000 cycles per second, with the force applied in any plane of the tube. The advantage of this low FM noise level in local oscillator service is obvious. Ceramic construction and the superior tube manufacturing techniques it makes possible permit tube or seal temperatures of 250°C without impairment of operation.

For severe environment microwave applications investigate the advantages of Eimac ceramic-metal reflex klystrons.

EITEL-McCULLOUGH, INC.
San Carlos, California
Cable Eimac

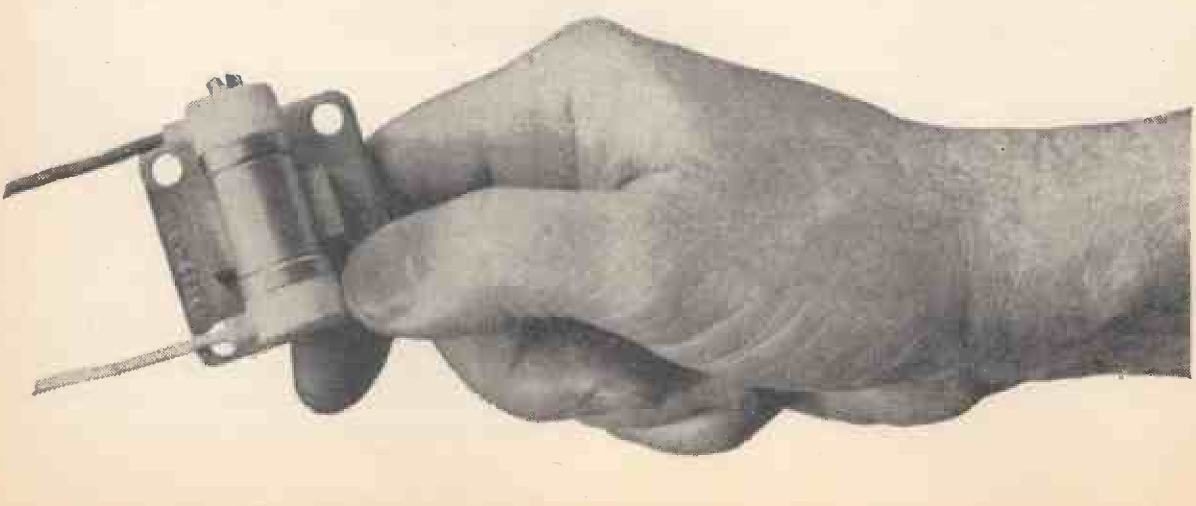

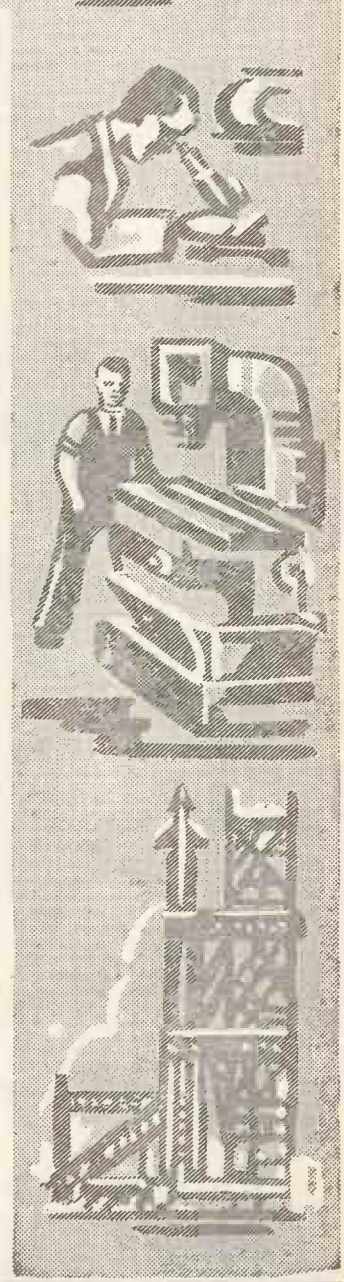

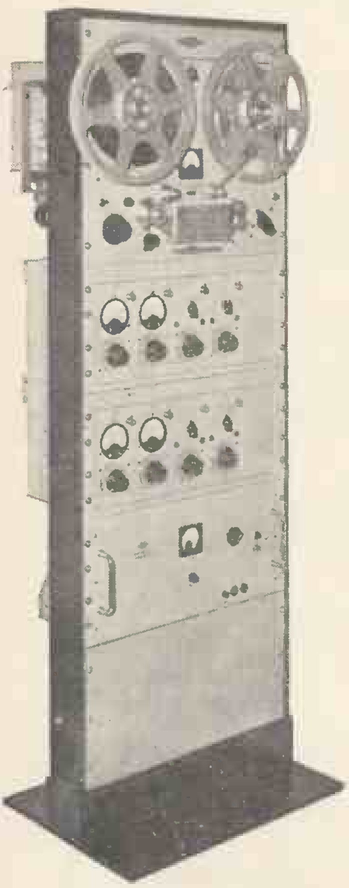

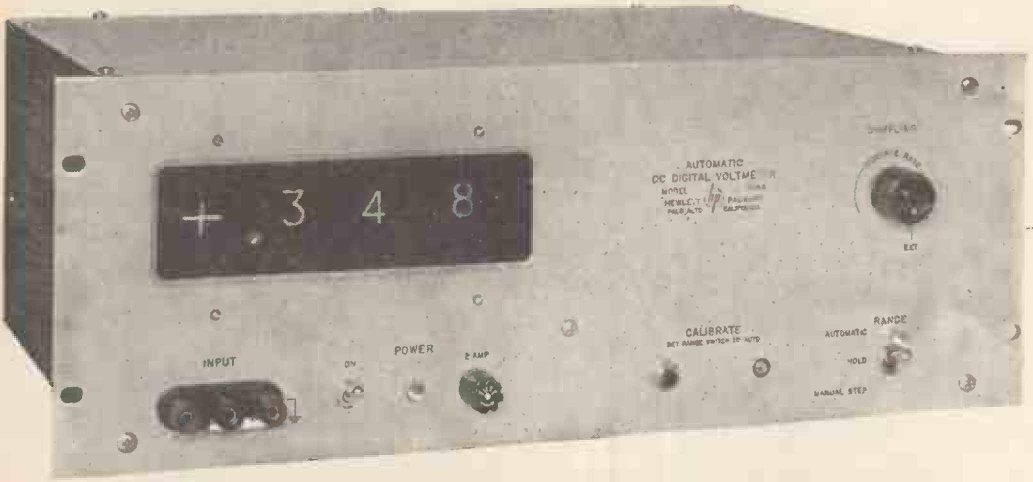

+ 3 4 8
AUTOMATIC
DC DIGITAL VOLTMETER
INPUT
POWER
CALIBRATE
RANGE
AUTOMATIC
HOLD
MANUAL STEP

TOP OF THE BILL

FOR EVERY PERFORMANCE

TRUVOX

ALL THAT THE NAME IMPLIES

Music or speech, " Pop " or classic . . . they're all on a good thing when they're Truvox taped. The young and gay will delight in the " Melody," the enthusiast will revel in the " Harmony " . . . whichever you choose, every programme will " top the bill " for you *and* your friends.

MELODY

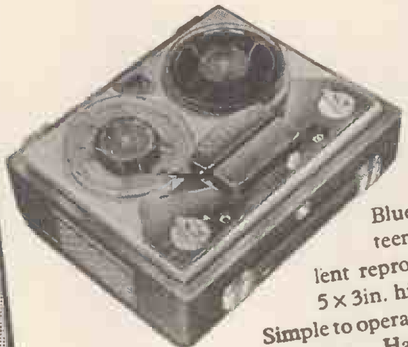

Has the size and elegance of a lady's vanity bag, finshed in Summer Blue. Ideal for teenagers. Excellent reproduction from 5×3in. hi-flux speaker. Simple to operate. Tape speed $3\frac{3}{4}$in. p.s. Half track. 4in. spools. Dimensions $11 \times 9 \times 5$in.

£36
Complete

HARMONY

Designed for the enthusiast Reproduction far in excess of that normally expected from an instrument of its size. Handsome, light tan leatherette case with gilt trim. Tape speed $3\frac{3}{4}$in. p.s. Half track. 6×4in. hi-flux speaker. 5in. spools. Dimensions $12 \times 9 \times 5\frac{3}{4}$in.

£44
Complete

Supplied with spool L.P. Tape and empty reel, crystal microphone and radio lead. For 110-240 v. A.C. mains.

MARK VI TAPE DECK

A worthy newcomer to the range of Truvox tape recording equipment, introducing refinements in appearance and facilities for higher quality recording with accurate timing and editing. Fully controlled by push buttons. Electrical and mechanical braking. Speed change knob. Pause control. Reels "locked" in "Off" position. Precision revolution counter. Contemporary colour scheme to harmonise with any cabinet finish.

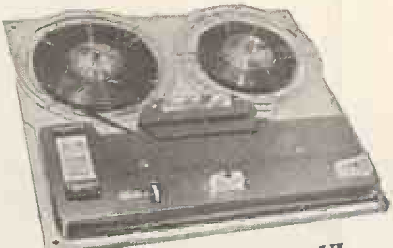

TAPE DECK Mk. VI
Fitted with Monaural Head, 25 gns.
Fitted with Stereophonic Head, 37 gns.

TRUVOX LIMITED NEASDEN LANE, LONDON, N.W.10, ENGLAND

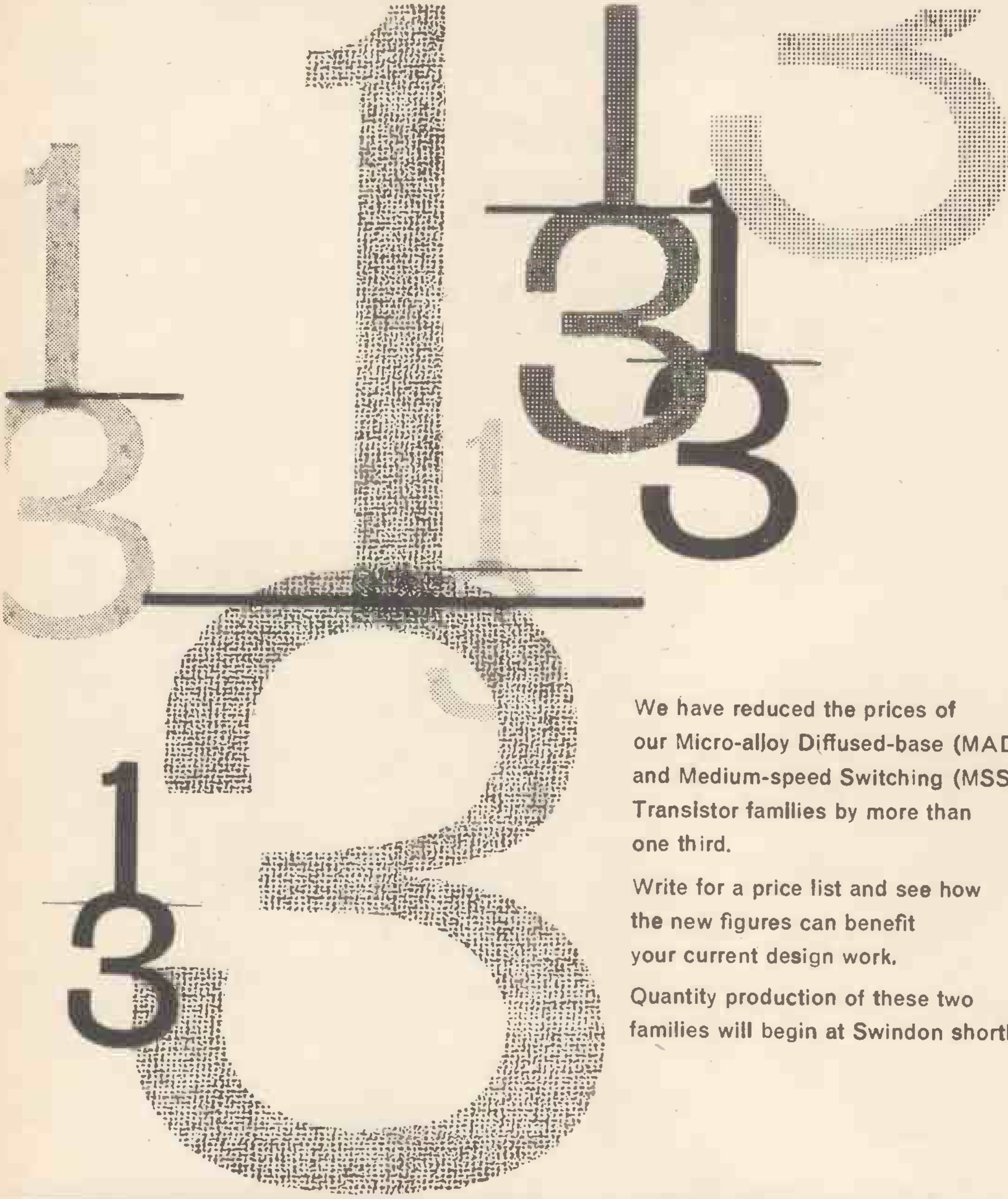

We have reduced the prices of our Micro-alloy Diffused-base (MADT) and Medium-speed Switching (MSS) Transistor families by more than one third.

Write for a price list and see how the new figures can benefit your current design work.

Quantity production of these two families will begin at Swindon shortly.

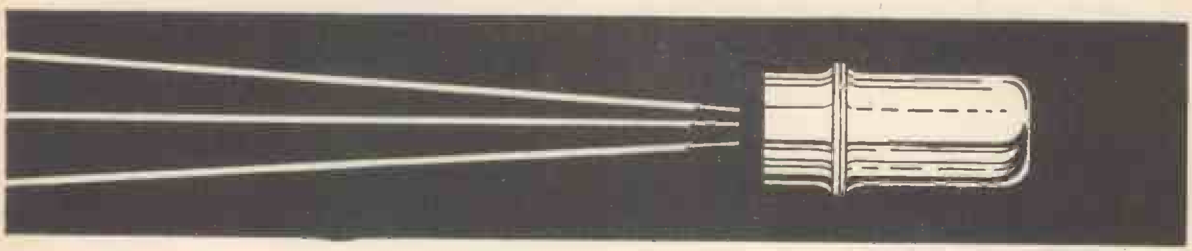

Semiconductors Limited

CHENEY MANOR · SWINDON · WILTSHIRE

Telephone: Swindon 6421

If you already own . . .

a Loudspeaker system which performs well in the bass and middle registers, but has inadequate or unsatisfactory High Frequency response—

You can ADD . . .

a precision built low distortion TREBAX High Frequency unit, and extend the frequency range of your loudspeaker to 20,000 c/s. *Two models are available.*

TREBAX 5K/20XL

Simplicity itself to install, since it contains its own L.C. crossover network in an integral assembly, and an L-pad level control (with knob and escutcheon) ready wired on flying lead. For use in systems handling up to 20 watts.

Price £7. 0. 0.

TREBAX 100

An even more efficient unit, for use in larger systems employing high flux bass units and handling powers up to 25 watts.

Price £6. 4. 0.

Both units, illustrated above, are horn-loaded and pressure driven, employing aluminium diaphragm and voice coils in self-aligning assemblies with air chambers and phase equalisers. The full range of each is 2,500 c/s to 20,000 c/s, and the crossover frequency advised is 5,000 c/s. In the TREBAX 5K/20XL the appropriate network is already built in ; for the TREBAX 100, separate network XO/5000 should be employed, together with a variable attenuator.

AND A FINAL STEP –

can be the addition of the MIDAX mid-range unit ; particularly appropriate if the reproduction of the middle register from your original loudspeaker is not fully satisfactory.

MIDAX 650

This is a horn-loaded pressure driven unit, with a smooth frequency coverage from 650 c/s to 8,000 c/s. Crossover to the bass unit should be at 950 c/s, and a special network — XO/950 — is produced for this purpose. The MIDAX may be used in systems handling up to 25 watts.

Price £9. 10. 0.

FULL DETAILS ARE GIVEN IN GOODMANS HIGH FIDELITY MANUAL

Fill in the coupon below and post NOW !

GOODMANS

GOODMANS INDUSTRIES LTD.,
Axiom Works, Wembley, Middx., England.
Tel. : WEMbley 1200 (8 lines). Grams : Goodaxiom, Wembley, England.
Distributors in all countries.
CANADA—A. C. Simmonds & Sons Ltd., 100 Merton Street, Toronto. 7.
U.S.A.—Rockbar Corporation, 650 Halstead Avenue, Marmoneck, N.Y.
Europe's largest manufacturers and the World's largest exporters of High Fidelity Loudspeakers.

Please send copy of High Fidelity Manual

Name ....

Address ....

....

....

G22WW

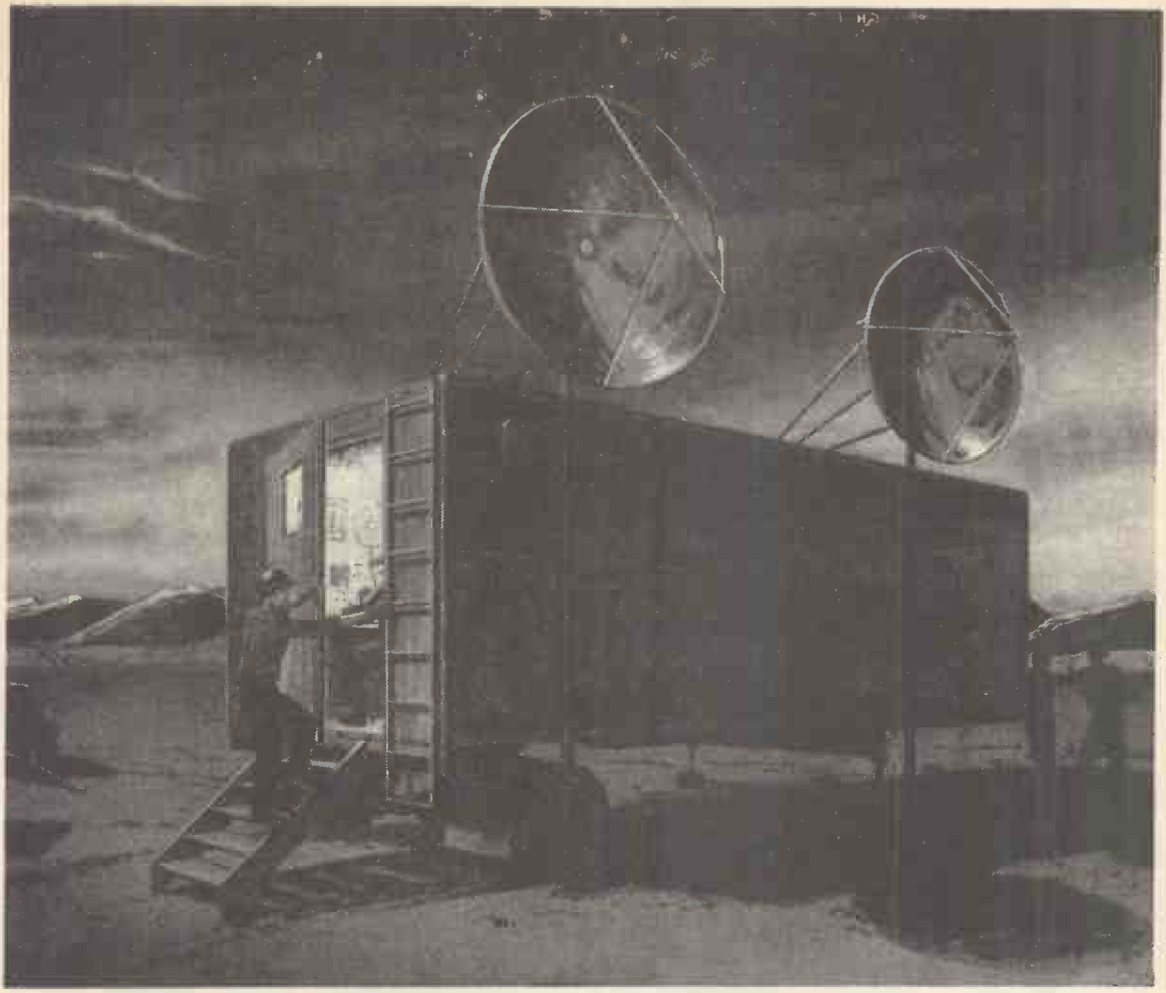

NEW TROPO SCATTER SYSTEMS

can be set up anywhere in 8 hours or less!

A new, transportable communication system has been developed by Canadian Westinghouse for sending two-way voice or teletype messages up to 200 miles *without* relay stations.

Its name is MICROSCATTER—the most *compact* system ever developed for low-cost, long range tropospheric scatter communications.

Now in production for customer orders, MICROSCATTER radio is a super high frequency system that can go *anywhere.* MICROSCATTER transmitters and receivers for quadruple diversity, including antennas, can be mounted in a standard 30 ft. truck trailer. Units designed for self-contained field shelters can be set down by helicopter in remote locations—and a MICROSCATTER installation can be set up ready for operation within 8 hours!

MICROSCATTER APPLICATIONS	
COMMERCIAL	**MILITARY**
Fixed Station —120 telephone channels —television and sound	Wide Band —radar —data —120 telephone channels
Transportable—48 telephone channels —teletype	Tactical and Transportable —48 voice channels —teletype —data

FEATURES

- Frequency—4400-5000 mc
- Antennas—10 to 28 ft. diameter
- Power—2 KW
- Range—100 to 200 miles

A Westinghouse communications specialist will gladly furnish complete information on MICROSCATTER radio. Phone your nearest Westinghouse office, or write to Canadian Westinghouse Company Limited, Electronics Division, Hamilton, Canada.

YOU CAN BE SURE...IF IT'S **Westinghouse**

59A748

Get it TAPED

— to perfection

SIZES	STANDARD			LONG PLAY			SIZES	DOUBLE PLAY		
	FEET	TOTAL RUNNING TIME (7½ I.P.S.)	PRICE £ S D	FEET	TOTAL RUNNING TIME (7½ I.P.S.)	PRICE £ S D		FEET	TOTAL RUNNING TIME (7½ I.P.S.)	PRICE £ S D
3"	150	8 mins	5 6	225	12 mins	8 6	3"	300	16 mins	10 6
4"	300	16 "	10 0	450	25 "	14 6	5"	1200	1 hr 4 "	2 5 0
5"	600	32 "	1 0 0	850	45½ "	1 8 0	5¾"	1800	1 " 30 "	3 0 0
5¾"	850	45½ "	1 7 6	1200	1 hr 4 mins	1 15 0	7"	2400	2 " 8 "	4 0 0
7"	1200	1 hr 4 mins	1 15 0	1800	1 " 36 "	2 10 0		SUPERGRADE		
8¼"	1750	1 " 33 "	2 10 0	2400	2 " 8 "	3 10 0	7"	1200	1 hr 4 mins	2 18 6

— naturally

on

MSS Mastertape

MSS RECORDING COMPANY LIMITED, COLNBROOK, BUCKS. TEL. COLNBROOK 2431
MSS SHOWROOM AND STUDIO: 21 BLOOMSBURY STREET, LONDON W1

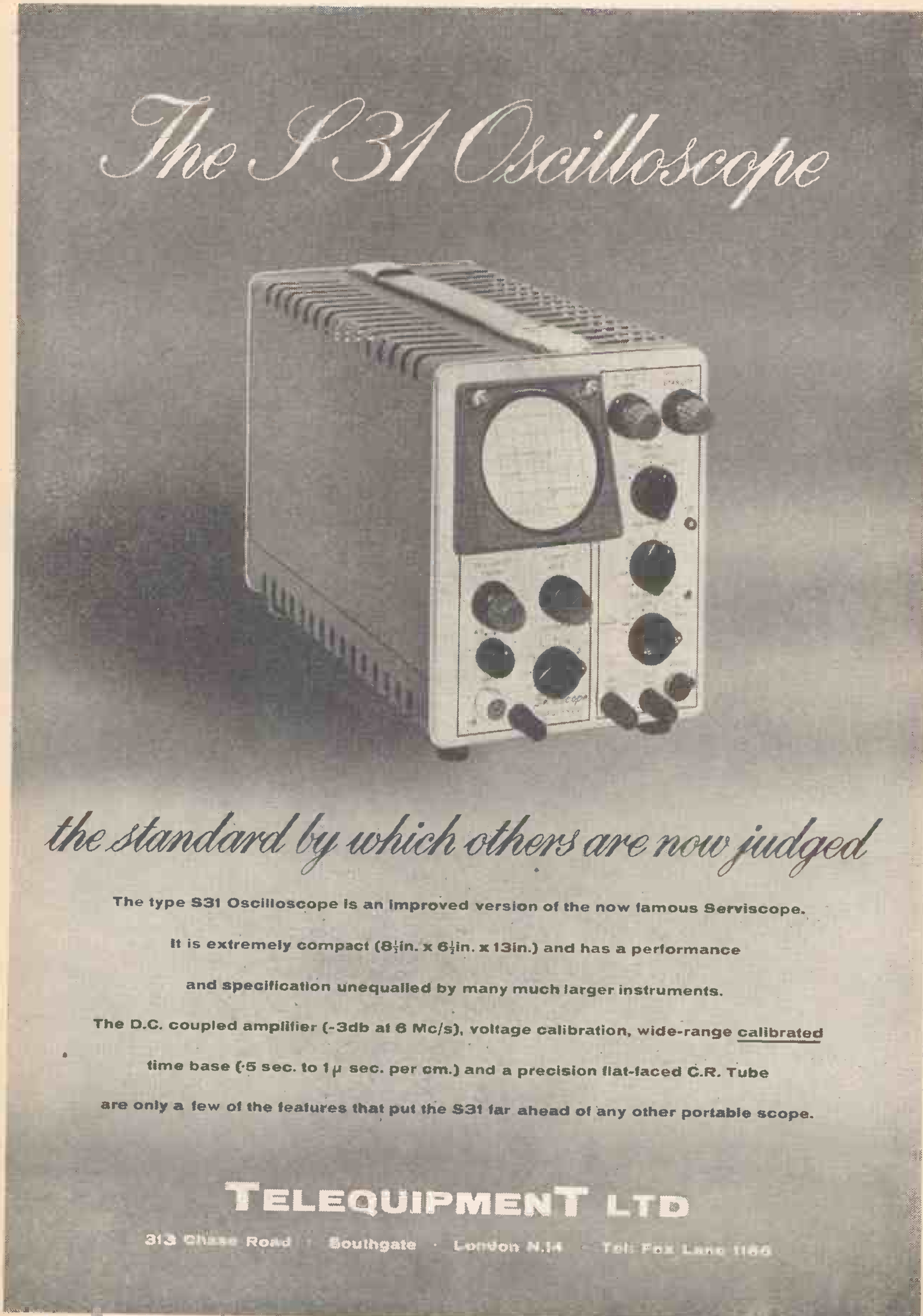
The S31 Oscilloscope
the standard by which others are now judged
The type S31 Oscilloscope is an improved version of the now famous Serviscope.
It is extremely compact (8½in. x 6½in. x 13in.) and has a performance
and specification unequalled by many much larger instruments.
The D.C. coupled amplifier (-3db at 6 Mc/s), voltage calibration, wide-range calibrated
time base (·5 sec. to 1μ sec. per cm.) and a precision flat-faced C.R. Tube
are only a few of the features that put the S31 far ahead of any other portable scope.
TELEQUIPMENT LTD
313 Chase Road · Southgate · London N.14 · Tel: Fox Lane 1166

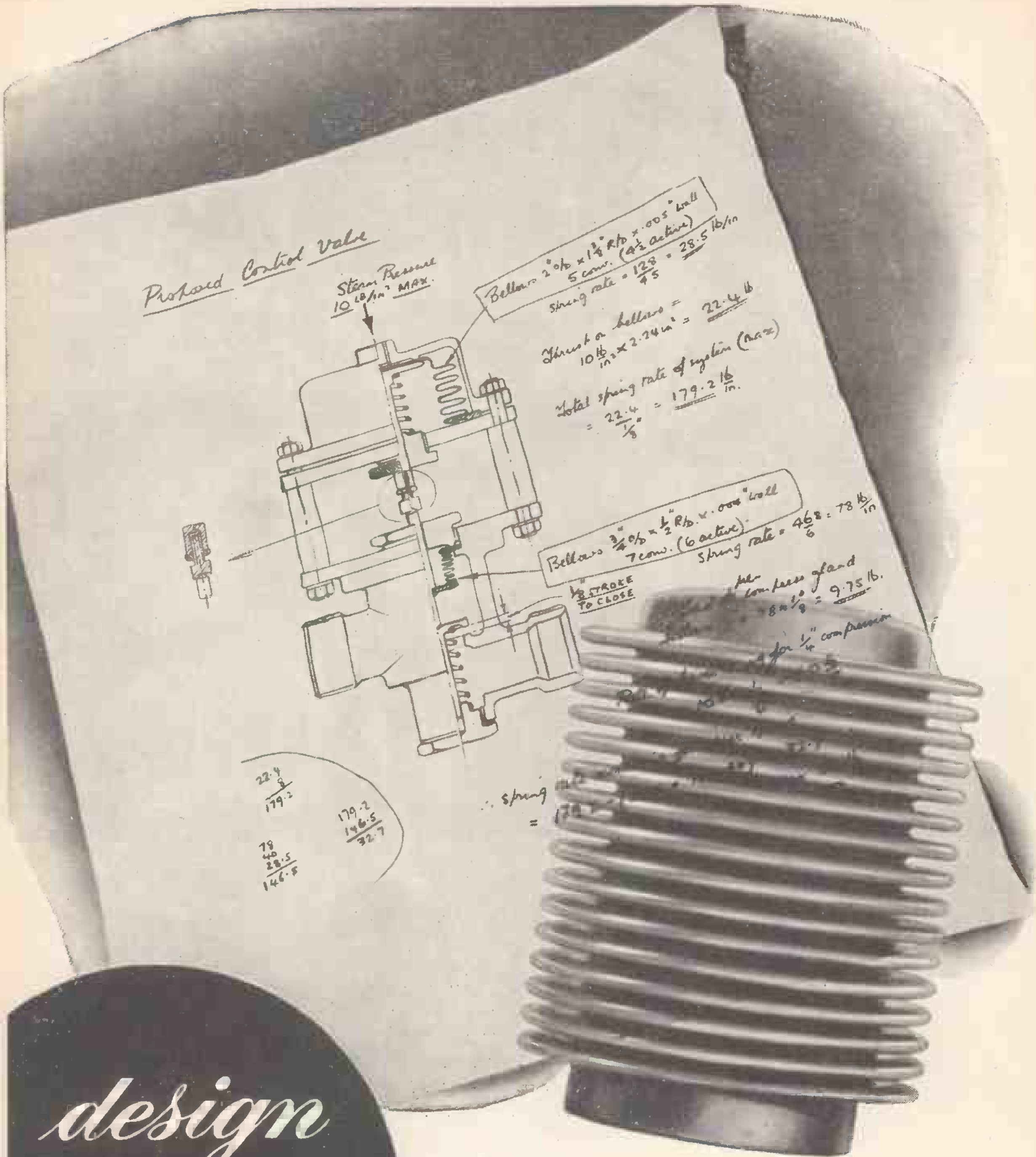
Proposed Control Valve
Steam Pressure 10 lb/in² MAX.
Thrust on bellows =
Total spring rate of system (max)
⅛" STROKE TO CLOSE

Greater versatility for the Redifon G.R. 400 TRANSISTORISED SSB Radiotelephone

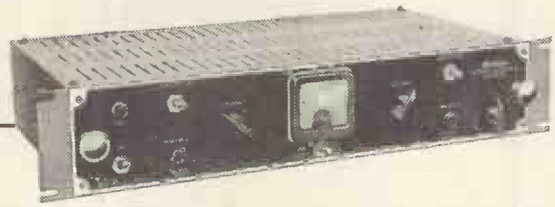

The Redifon **GK. 189** TRANSISTORISED

Two-Tone Keyer/converter, when used in conjunction with the GR. 400 gives the added facilities of TELEPRINTER working.

The Redifon **GR. 400**

TRANSISTORISED SSB Radiotelephone gives all the advantages of single side-band, yet is as simple to operate as an ordinary telephone. For R/T or CW operation. Compact. Reliable. Full tropical specification.

Redifon

THE WORLD'S LEADING MANUFACTURERS OF RADIOTELEPHONES

The Redifon **R. 401** TRANSISTORISED

SSB Receiver combines with GR. 400 to give full DUPLEX TELEPHONY.

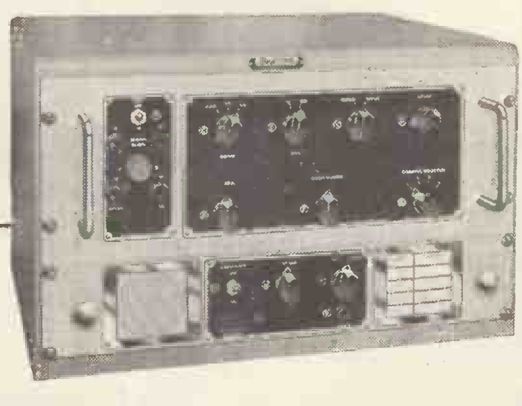

These 3 units are available for use with A.C. mains or D.C. 12 or 24 v. supplies.

REDIFON LIMITED Communications Sales Division,
Wandsworth, London S.W.18 Telephone : VANdyke 7281

A Manufacturing Company in the Rediffusion Group

AN ANNOUNCEMENT OF IMPORTANCE TO ALL TAPE RECORDER USERS

**Now available:
the complete range of
professional-quality**

audiotape

TRADE MARK

...on the sensational C-SLOT REEL!

AUDIOTAPE, manufactured in the U.S.A. by Audio Devices, Inc., is known the world over for its flawless perfection of sound reproduction throughout the entire audio range, and its *consistent, uniform quality* from reel to reel and from one type to another. Available in eight different types, with a base material and reel footage to meet every recording requirement, AUDIOTAPE has only *one* standard of quality—the finest obtainable. This sterling performance reflects Audio Devices' more than 10 years of experience in magnetic tape manufacture, and more than two decades of practical experience in the sound recording art.

All 5in. and 7in. reels of AUDIOTAPE are supplied on the exclusive C-Slot Reel—the fastest-threading tape reel ever developed. The tape end, dropped into a slot in the hub, anchors itself automatically at the first turn of the reel. AUDIOTAPE is also available on the popular-size 3in., 3¼in., 4in. and 5¾in. reels.

For the truest sound that your recording equipment can produce try AUDIOTAPE. *It speaks for itself!*

AUDIO DEVICES Inc., New York, N.Y.

Concessionaires to the United Kingdom and Eire.

LEE PRODUCTS (G.B.) LIMITED.
"Elpico House", Longford Street, London, N.W.1.
Tel: EUSton 5754 (all lines) Telegrams: Leprod, London.

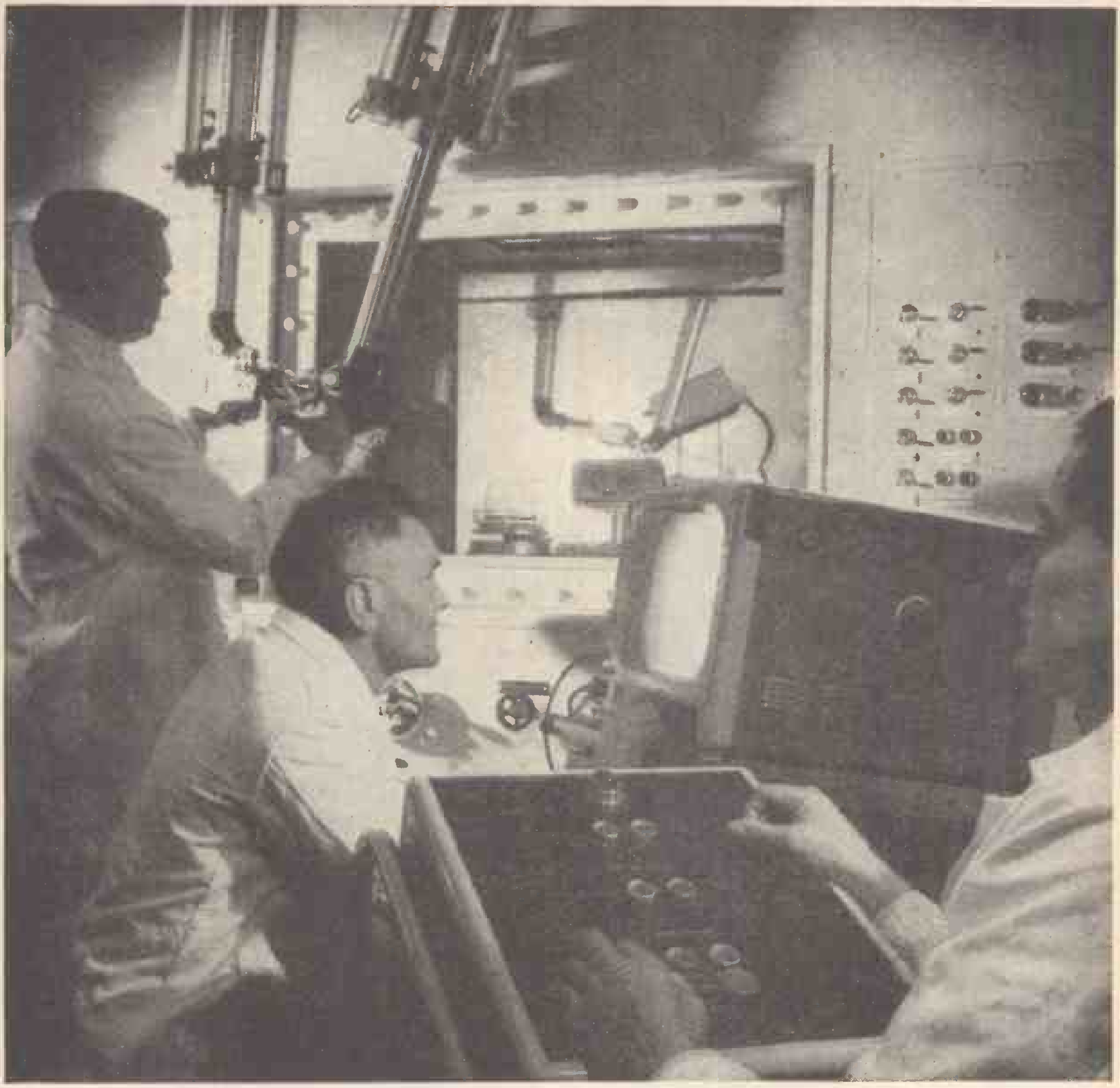

Pye at Dounreay

The Pye Instrument Group has supplied all the equipment to the U.K. Atomic Energy Authority for the irradiated fuel element laboratory at Dounreay. In addition to supplying equipment, Pye Ltd. acted as consultants and designers on all matters in that laboratory relating to instrumentation and remote handling. The illustration above shows manipulators working in conjunction with a television camera to handle and measure a sample from the fast reactor.

The Pye Instrument Group consists of: Pye Atomics Division; Pye Industrial Television Division; Faraday Electronic Instruments Ltd., Labgear Ltd.; W. G. Pye & Co. Ltd.; Pye Telecommunications Ltd.; Unicam Instruments Ltd.; W. Bryan Savage Ltd.; W. Watson & Sons Ltd.

RELIABLE
HYDROGEN THYRATRONS

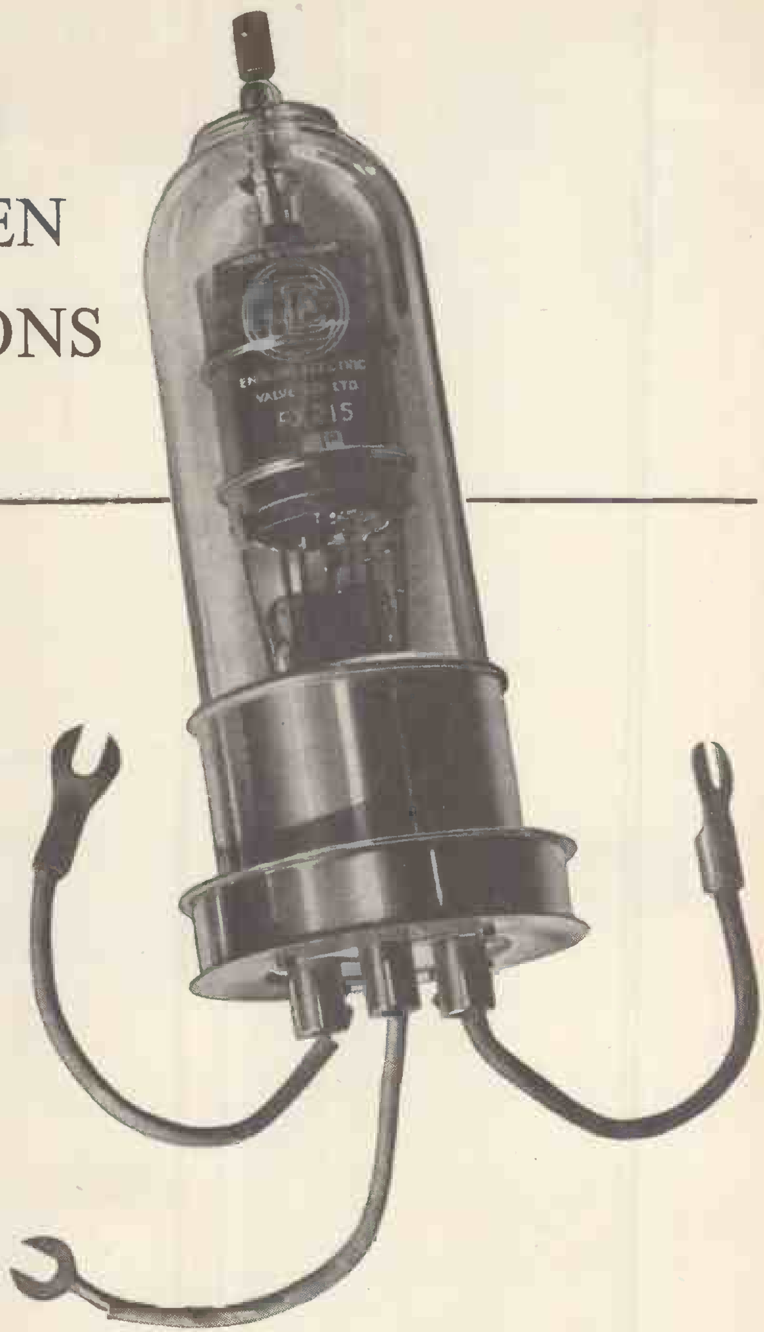

HYDROGEN-FILLED PULSE MODULATOR TRIODES

Designed to discharge pulse-forming networks in high power, high voltage pulse generators. Short deionization time and low time jitter provide for precise triggering at high repetition frequencies.

Listed below are some examples from our comprehensive range. Full technical data of these and other thyratrons will be sent on request.

E.E.V. Type		Peak Forward Voltage (Max)	Peak Anode Current (Max)
7384		25kV	1000A
4C35	CV1787	8kV	90A
FX215	CV2203	16kV	200A
5C22	CV2520 CV3540	16kV	325A
FX229	CV3521	25kV	500A
FX227	CV372 CV3629	3kV	35A

'ENGLISH ELECTRIC'

AGENTS THROUGHOUT THE WORLD

ENGLISH ELECTRIC VALVE CO. LTD.

Chelmsford, England
Telephone: Chelmsford 3491

AP300/39

TYPE W.3
(3 WATT)

This illustration is actual size.

★ *Also* available, the precision built
TYPE HA2500
providing exceptionally high law accuracy *without cam correction.* Range 100 to 100,000 ohms. Law Accuracy (Absolute) ±0.25% or ±0.10%.
Full details in Data Sheet No. 100.

Introducing . . .

ADDITIONAL TO THE RELIANCE RANGE

This latest addition to the Reliance range of Potentiometers has been designed to conform with specification DEF-5121 style RVW 7 & 3 (formerly RAC.RAD) and is fully sealed with integrally constructed moulded cover. A commercial unsealed version, with identical characteristics is also available. Both types can be supplied in ganged form.

BRIEF SPECIFICATION

RESISTANCE RANGES

Linear Law A......... 5 to 100,000 ohms
Laws B—G ....50 to 50,000 ohms
Non-Inductive ....50 to 10,000 ohms
(Ayrton Perry)

RESISTANCE TOLERANCE

Standard............over 100 ohms± 5%
under 100 ohms±10%
Also available (at extra) with tolerance to ± 1% and linearity to within ± 1%.

ROTATION

Electrical Effective..................280°±5°
Mechanical ....290°±5°

MAXIMUM WORKING VOLTAGE

Between spindle and track .... 1,000 V.d.c.

Full technical details and dimensional drawings in Data Sheet No. 9 available on request.

RELIANCE MANUFACTURING CO. (SOUTHWARK) **LIMITED**
SUTHERLAND ROAD, HIGHAM HILL, WALTHAMSTOW, LONDON, E.17. Tel: Larkswood 1118/9

GD61

Fully Guaranteed Components

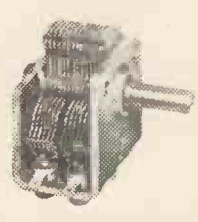

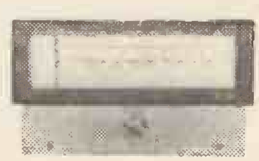

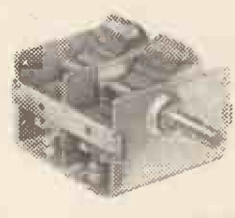

"OO" TWIN CONDENSER

Designed for use in miniature transistor receivers. The front (aerial) section is 208pf. to provide coverage for medium waves, and the rear section is 176pf., which may be padded to match the oscillator—very robust yet light weight. Front area 1⅜in. × 1 17/32in. × 1 1/32in. deep, price 9s. 6d.

SL. 16 DRIVE

A general purpose slide rule Drive for F.M./V.H.F. Units, short-wave converters, etc. Printed in two colours on aluminium, with a 0-100 scale and provision is made for individual calibrations. Complete with bronze escutcheon and glass. Price 13s. 9d.

F. GANG CONDENSER

A good general purpose gang. Robust, but small in size. "E" law to match our S.L.8 Full Vision, Square Plane and Air Plane Drives. Size 2¼in. × 1 21/32in. × 2 9/16in. long (3 gang 3 11/16in.). Price for 2 Gang 13s. 3d. 3 Gang, 17s. 6d. Complete with trimmers.

JACKSON BROS. (London Ltd.)
PRECISION BUILT COMPONENTS
KINGSWAY · WADDON · SURREY
Telephone: Croydon 2754/5

AMERICAN REPRESENTATIVE: Messrs. M. Swedgal Electronics, 258 Broadway, New York 7, U.S.A.

More WATTS PER lb £

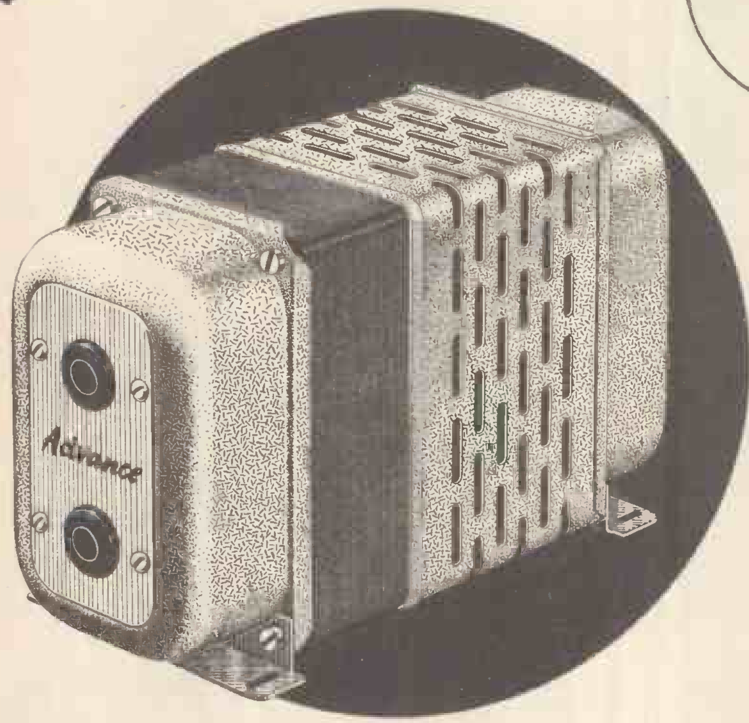

with the New CV SERIES

Take the best in Constant Voltage Transformer design and practice . . . maintain all those features proven by years "in the field" . . . . add still greater efficiency . . . . reduce size and weight . . . . and then drastically cut the cost — and you have the NEW CV Series.

Models now available with output capacities of 25, 50, 75 and 100 watts and range of outputs from 6 to 240 volts — all providing assured output voltage regulation within ± 1% for input variations of up to ± 15%

- **WEIGHT REDUCED** by over 25%
- **SIZE REDUCED** by over 40%
- **STRAY FIELD REDUCED** by over 75%
- **OPERATE AT ANY LOAD** from 'NO LOAD' to 'FULL LOAD'
- **WILL OPERATE CONTINUOUSLY AT AMBIENT TEMPERATURES** from −10 to +50° C.

CONSTANT VOLTAGE TRANSFORMERS

They are **SMALLER - LIGHTER** *and* **COST LESS!**

Here's a typical example-

	MODEL CV.25/E	MODEL MT.281/E
Input Voltage	190-260V	190-260V
Output Voltage	6V	6V
Output Capacity	25W	25W
Dimensions	5¼" x 3 3/16" x 4⅞"	7" x 5½" x 4⅜"
Weight	5lb	7lb
	PRICE £6. 5. 0	PRICE £8. 0. 0

Full details in Folder W-63 available on request

by **Advance** – to be sure!

Advance COMPONENTS LIMITED

MAINS STABILIZATION DIVISION

ROEBUCK ROAD • HAINAULT • ILFORD • ESSEX • TELEPHONE : HAINAULT 4444

GD 80

Elliott Brothers

use AMP Patchcord Programming System and Taper Technique

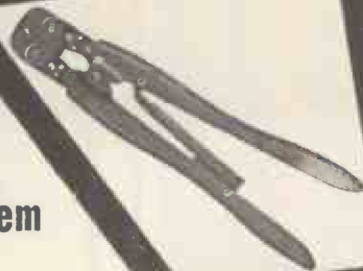

the means...

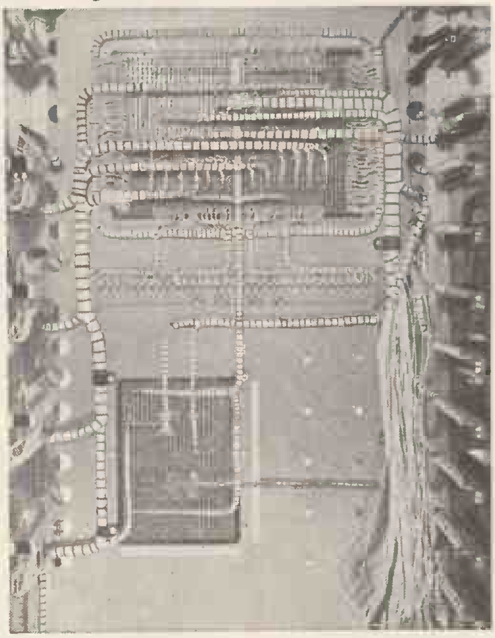

Rear view showing harness employing Taper Pin Connection.

"FIMAC" Computer at present in use in the Aviation Division of Elliott Brothers (London) Limited, Boreham Wood.

...to the end

Front view of Programme Boards.

Photographs by courtesy of Panellit Ltd., Member of the Elliott Automation Group.

▶ QUICKER APPLICATION
▶ LOWER APPLIED COSTS
▶ RELIABLE PERFORMANCE
▶ HIGH ELECTRICAL AND MECHANICAL STABILITY

AMP* TRADE MARK

WRITE NOW ABOUT THE **CREATIVE** APPROACH TO BETTER WIRING

AIRCRAFT-MARINE PRODUCTS (GT. BRITAIN) LTD.

Head Office: Amplo House, 87-89 Saffron Hill, London, E.C.1 Tel: CHAncery 2902 (7 lines)

Works: SCOTTISH INDUSTRIAL ESTATES, PORT GLASGOW, SCOTLAND

* Trade Mark of AMP Incorporated U.S.A.

AP323-93

All round the world

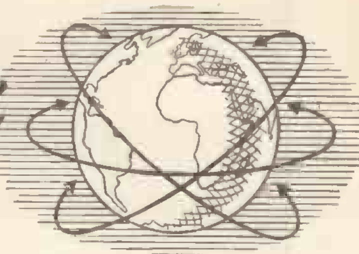

AIRMEC

COMMUNICATIONS RECEIVER Type C864

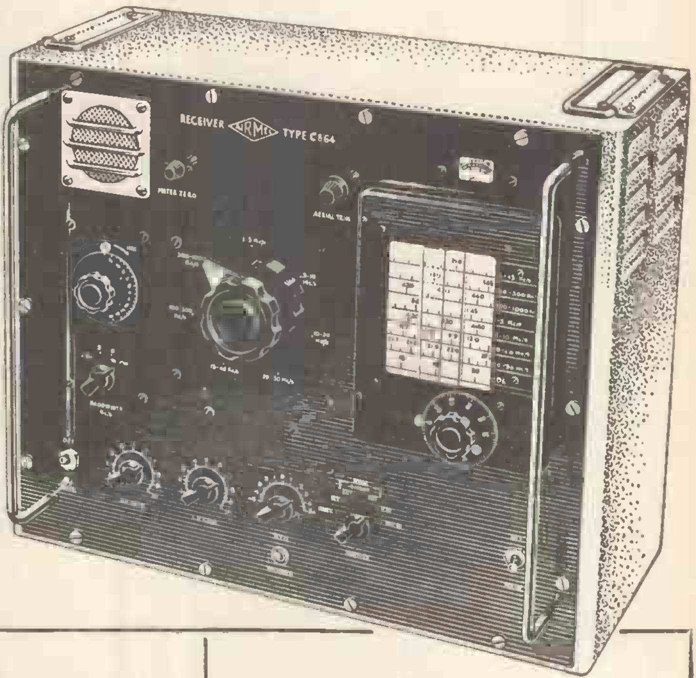

All round the World this Airmec receiver is known and used for its remarkable performance at an extremely low cost.

Superior Sensitivity
Superior Signal-to-Noise Ratio
Superior Second Channel Rejection

Main tuning control showing a portion of the seven frequency scales, the coarse and fine logging scales and the movable cursor.

- Frequency coverage from 15—45 kc/s and 100 kc/s—30 Mc/s.
- Frequency setting accuracy better than 1 kc/s.
- Film scale giving actual scale length of 4ft. on each frequency range.
- 90 : 1 slow motion drive with logging scale.

ADDITIONAL FEATURES

- **Separate incremental tuning control for use with crystal calibrator.**
- **Double frequency changer circuit.**
- **Stabilised local oscillator H.T. voltages.**
- **Image rejection over 100 db.**
- **Exceptionally high sensitivity and signal/noise ratio.**
- **Variable selectivity.**
- **S meter incorporated.**
- **Very stable B.F.O.**
- **Muting facilities provided.**
- **Built-in loudspeaker.**
- **2 watts output.**
- **Turret band switching.**

PRICE: £150 SEND FOR LEAFLET 160A

Airmec

RADIO AND ELECTRONICS

AIRMEC LIMITED · HIGH WYCOMBE · BUCKS
Telephone: High Wycombe 2060


Those who know
insist on . . .
TRADE MARK
SCOTCH
BRAND
RECORDING TAPE
SCOTCH WORLD'S LARGEST SALES OF MAGNETIC TAPE

CAPACITORS

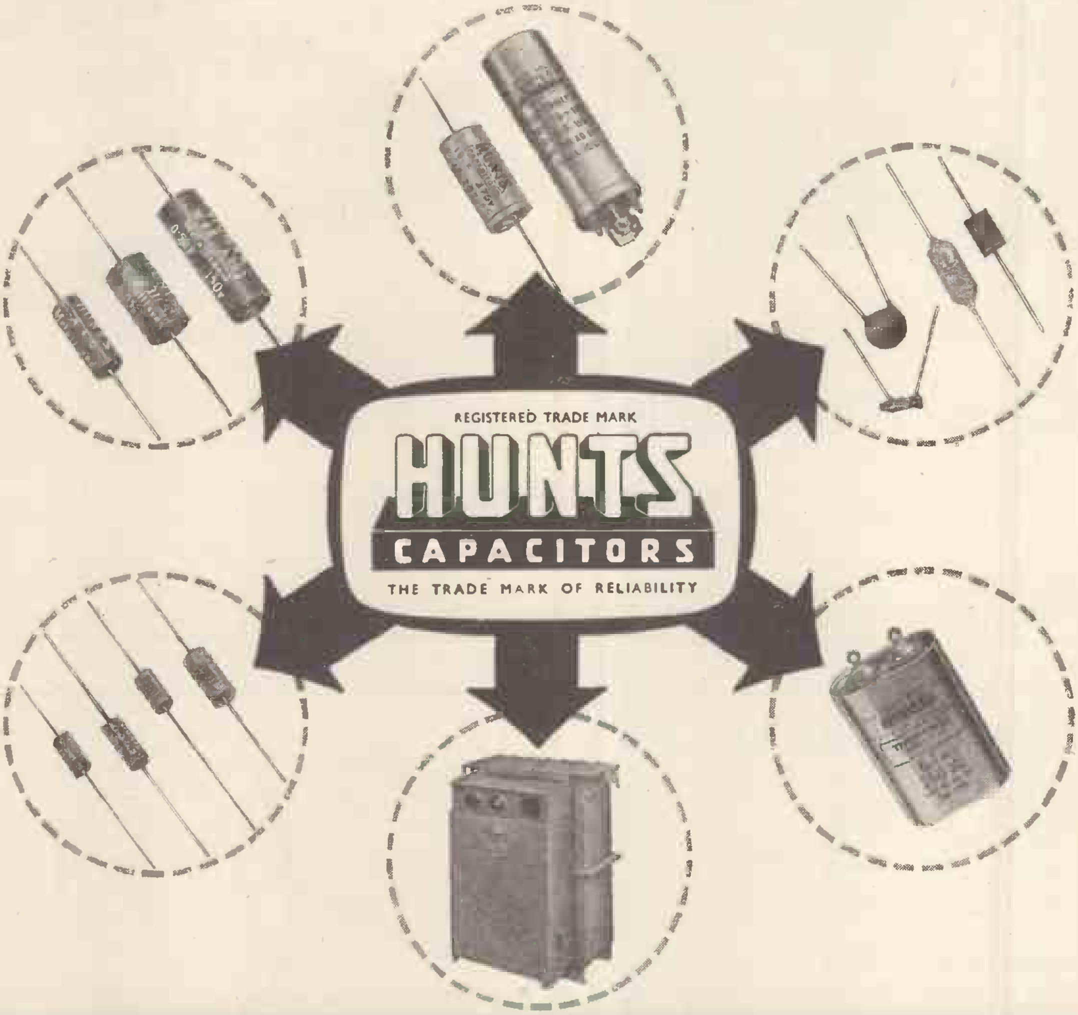

for all applications

TYPES

DRY ELECTROLYTIC · METALLISED PAPER (HUNTS PATENTS)
METALLISED PLASTIC FILM (HUNTS PATENTS)
PLASTIC FILM · FOIL & PAPER · SILVERED MICA
STACKED MICA · CERAMIC · POWER CERAMIC
TRANSMITTING AND SPECIAL R.F. TYPES

APPLICATIONS

RADIO AND TELEVISION EQUIPMENT · ELECTRONIC EQUIPMENT
POWER FACTOR IMPROVEMENT · CAPACITOR MOTORS
FLUORESCENT LIGHTING · PHASE SPLITTING
H.F. AND R.F. HEATING · IGNITION AND INTERFERENCE SUPPRESSION
TELEPHONE INSTALLATIONS

A. H. HUNT (Capacitors) LTD., WANDSWORTH, LONDON, S.W.18. Tel: VANdyke 6454

Factories also in Essex, Surrey and North Wales

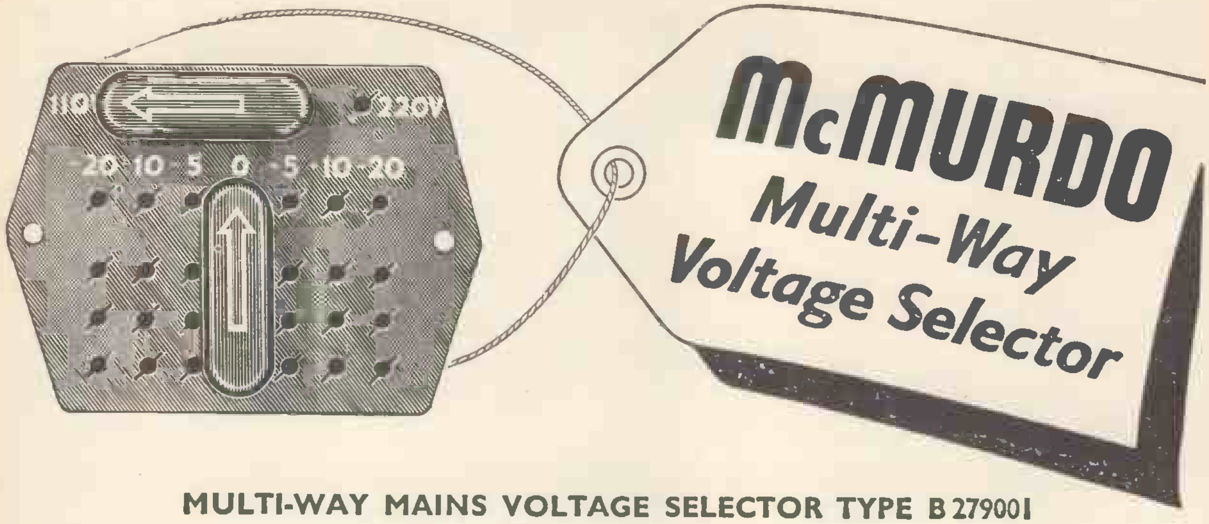

MULTI-WAY MAINS VOLTAGE SELECTOR TYPE B 279001

14 POSITIONS! 90, 100, 105, 110, 115, 120, 130, 200, 210, 215, 220, 225, 230, 240 VOLTS.

BLACK P.F. MOULDING.

Send for full details including circuit information to :—

THE McMURDO INSTRUMENT CO. LTD · ASHTEAD · SURREY · Tel: ASHTEAD 3401

5649

INTERCHANGEABILITY

of the 5 different sized bits with the 1 Precision iron, creates the most versatile soldering tool yet produced. Bit sizes of .040in., 3/32in., 5/32in., 3/16in. and 3/16in. heavy duty complete the range.

FINGERTIP CONTROL, sharp, regulated heat, ensures a quicker better job. Model C.240 (230/240 volts) illustrated, is available from the usual wholesalers or direct from the manufacturers at 29/6 (complete with one bit). Other models for voltages ranging from 6 to 230 volts also available.

Stands as illustrated at **12/6.**

SEND FOR DETAILED CATALOGUE TO

A.N.T.E.X.

7/8 Idol Lane, London, E.C.3.

Phone: Mansion House 2716

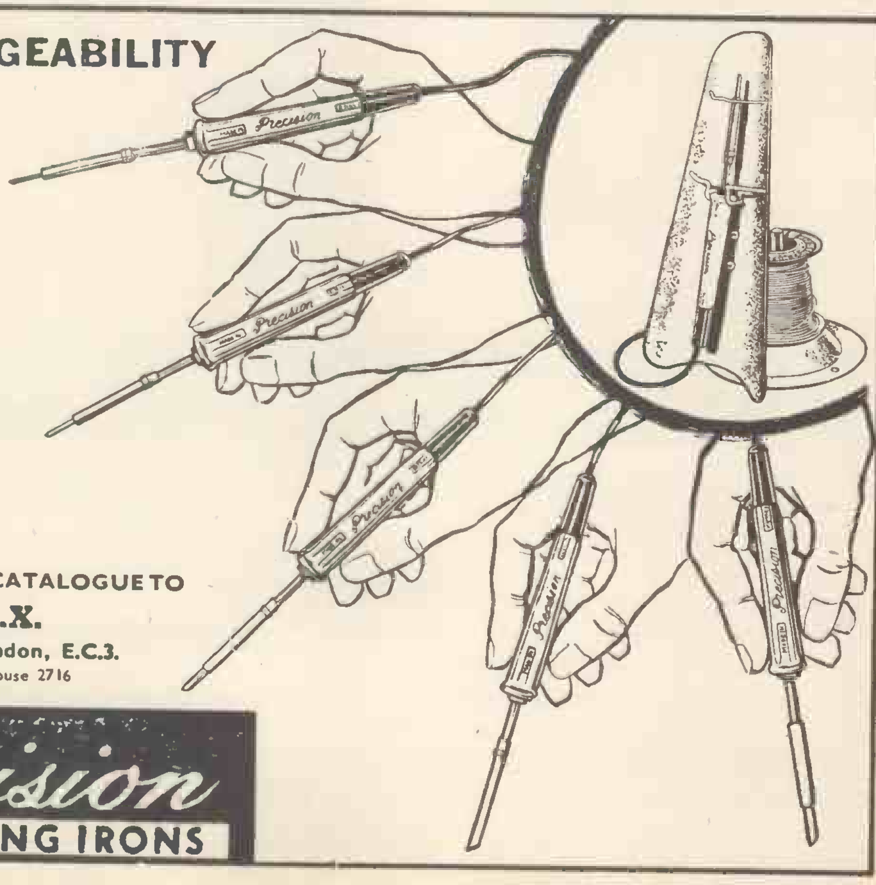

Precision

SOLDERING IRONS

TRANSFORMERS

All for 240 V Input, other Supply Voltages as Required
CONTINUOUS RATING. Short Rating Transformers also available

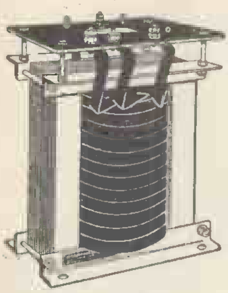

5 V 140 A	£11
110-120 V 10 A	£15
40 V 25 A	£15
5 V 300 A	£20
6-12 V 50 A	£10
12 V 60 A	£10
12 V 100 A	£16
50 V 60 A	£25
10-15-25 V 100 A	£26
6-12-18-24-30 V 12 A	£11
110 V Centre Tapped 55 V 25 A	£26
6-8-10-18-24 V 100 A	£32

EACH TRANSFORMER IN THIS GROUP £8-10-0

OUTPUTS

5 V	80 A
12 V	40 A
24 V	30 A
30 V	25 A
18 V	30 A
110–120 V	4 A
4 V	100 A
60 V	7 A
17.5 V	40 A
55 V	15 A

4 V 5,000 A	£100
2 V 10,000 A	£98
3.5 V 20,000 A	£127
2 V 30,000 A	£130
10 V 2,000 A	£103
10 V 1,000 A	£59
10 V 500 A	£38
10 V 750 A	£48
10 V 300 A	£28
10 V 900 A	£50
12 V 1,000 A	£64
15 V 1,000 A	£75
20 V 800 V	£80
5 V 1,000 A	£39

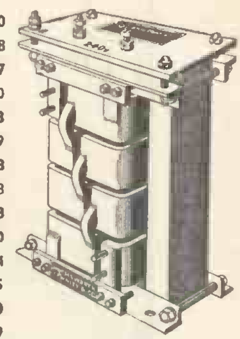

TRANSDUCTORS

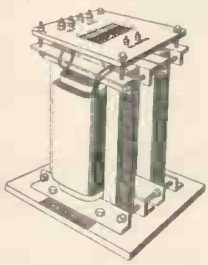

Saturable Reactors for controlling AC currents up to 220 A 100 kVA. Available for all standard AC supply voltages. Single-phase and three-phase. Standard DC control volts; 12, 24, 36 110 and 240 V.

AUTO-TRANSFORMERS

230–115 V 5 A	£8
250–240–230–220 120–115–110–105 V 12 A	£13
250–240–230–220–120–115–110–105 V 60 A	£35

HIGH-VOLTAGE TRANSFORMERS

4,250–4,750 V 25 mA	£14
2,050–4,000 V .5 A	£27
2,500–0–2,500 V 250 mA	£27
10 kV Ignition	£12

THREE-PHASE TRANSFORMERS

Input 400/440 V 40 V 60 Amps 3-Phase	£30
230 V 50 Amps 3-Phase	£78
110 V 100 Amps 3-Phase	£90
4 V 5,000 Amps 3-Phase	£130

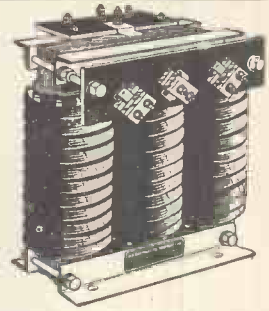

These and other Transformers can be supplied for 3-phase, 6-phase and 12-phase Rectifiers.

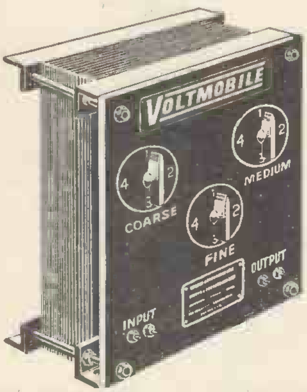

CONSOLES

AC and DC Supply Units with infinitely variable or tapped output. Manual or remote control with full instrumentation. The Console illustrated has a stabilized 230 V AC supply as well as several low voltage heavy current sources. Each source is independent of the others but where called for, interlocking, and protection devices can be included.

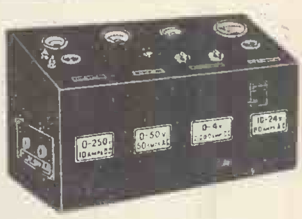

VOLTMOBILE

VOLTAGE REGULATING AUTO-TRANSFORMERS

Range from zero volts to supply volts in 64 steps. Change per step 1.6% ON LOAD SWITCHING.

	INPUT 240 V OUTPUT 0/250 V	INPUT 420 V OUTPUT 0/440 V
30 A	£32	£37
60 A	£62	£73
100 A	£98	£111

VOLTMOBILES can be used by themselves or in the primary of another transformer to give very fine changes of output.

RECTIFIER SETS

For 200/250 V A.C. Also available for 3-phase supply

6.3 V DC 13 A	£13
12/25 V DC 12 A with Choke Regulator	£18
12 V DC 210 A	£110
24 V DC 20 A	£26
24 V DC 26A with stabilizer	£36
24 V DC 105 A	£110
34 V DC 10 A	£30
36 V DC 50 A	£51
110/120 V DC 10 A	£34
110/120 V DC 25 A	£25
200/250 V DC 6 A	£39
200/250 v. DC 10 A	£44
200/250 V DC 18 A	£60
220 V DC 110 mA	£12
1,200 V DC 200 mA	£40
Fitted Ammeters and Voltmeters, per meter	£4
Built-in Rheostats	£4

SPECIFIC ENQUIRIES are invited for Transformers and Rectifiers. We specialize in HEAVY CURRENT EQUIPMENT.

HARMSWORTH, TOWNLEY & CO.
2 JORDAN STREET, MANCHESTER 15. CENTRAL 5069

NASHTON

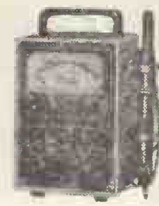

Flash Tester
500 - 2000V A.C.
£26.0.0

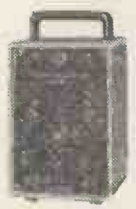

D.C. Stabilised. Supply
1 - 12V 1 amp.
£40.0.0

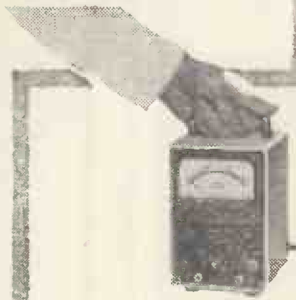

Ohmmeter
10Ω - 10,000MΩ
£52.10.0

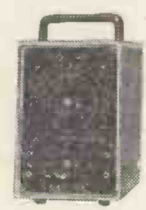

R.C.C. Bridge
5 pf - μf 5Ω - 500MΩ
£30.0.0

Sensitive Valve Voltmeter
3mV - 300V.
40 c/s - 500 kc/s
£49.10.0

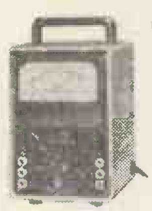

D.C. Valve Voltmeter
0.1 - 1000 volts
0.01 - 100μA
£58.10.0

NASHTON

precision measuring equipment means accurate economic buying

These six models are a selection from the wide range of NASHTON miniaturized electronic test instruments available for immediate delivery. Designed by Nash & Thompson to meet your everyday needs accurately, efficiently and economically, NASHTON units are compact, modern, streamlined, easy to read and operate. NASHTON give you what you need most — functional efficiency, not frills.

Others in the range include the A.C./D.C. Valve Voltmeter, Universal D.C. Meter, L.F. Quadrature Oscillator, 0.5 Amp. Stabilised D.C. Power Supply, Transistor Tester, Shorted Turn Detector, Digital Read-Out Meter, Preferred Value Resistance and Capacitance Boxes.

Nash and Thompson LTD

HOOK RISE, TOLWORTH, SURBITON, SURREY Tel. ELMbridge 5252

Arcolectric

SWITCHES & SIGNAL LAMPS

T.225: Miniature Slide Switch
Ideal T.V. mains switch

S.L.166: Very small low cost
mains neon indicator

T.280: Sensitive Snap Action Switch
Popular switch for tape recorders

T.626: Double pole 3-AMP switch
with tags to fit printed circuit boards


S.L.166


T.225

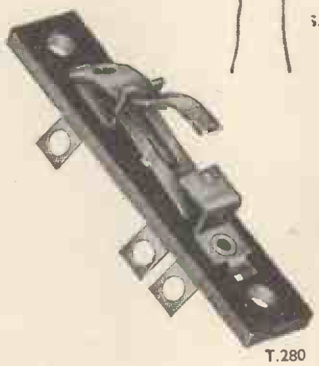
T.280

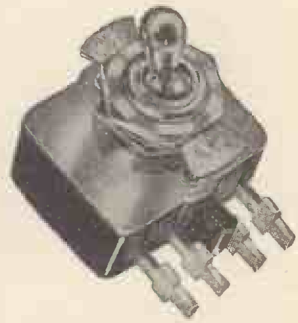
T.626

Write for Catalogue No. 132

ARCOLECTRIC SWITCHES · LTD

CENTRAL AVENUE, WEST MOLESEY, SURREY. Tel.: MOLESEY 4336

LINEAR

For HIGH SENSITIVITY!
HIGHEST FIDELITY!
MAXIMUM RELIABILITY!
REASONABLE COST!

MODEL L10 HIGH FIDELITY 10 WATT AMPLIFIER
WITH SEPARATE PRE-AMPLIFIER

Supplied complete only (i.e. Main Amplifier and Pre-amp.) **15** Retail Price GNS.

Size of main amplifier 9in. x 7in. x 5in., Pre-amp. 11in. x 4¾in. x 2½in. Front Plate 12in. x 3½in. Stoved Gold hammered finished chassis. Front Plate Polychromatic Gold. Weight of main amplifier 10lb. Pre-amp. 3lb. For 50/60 c.p.s. A.C. mains 200-230-250 v. or to order for export.

The Following Outstanding Test Figures include Pre-amplifier:

Sensitivity (for 10 watts)
L.P. 25 m.v.
78 r.p.m. 20 m.v.
Radio, 35 m.v.
Microphone, 2.5 m.v.

Input Impedance
All inputs 500k. Plus 10pfd.

Frequency Response
±2 d.b. 30—25,000 c.p.s.

Power Consumption
90 watts.

Maximum Power Output
In excess of 12 watts.

Negative Feedback
Total 32 d.b.

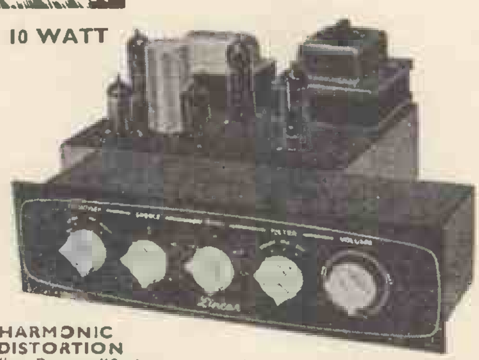

HARMONIC DISTORTION
(inc. Pre-amplifier)
0.09% measured at 10 watts.

Damping Factor 35

Bass Control
+9 d.b. to −9 d.b.
at 50 c.p.s.

Treble Control
+9 d.b. to −9 d.b.
at 12,000 c.p.s.

Hum Level
−70 d.b.

Filter
−7 d.b. at 9 Kc/s.
−10 d.b. at 5 Kc/s.

MULLARD VALVES:
EF86(1); ECC83(2); EL84(2); EZ81(1).

OUTPUT MATCHINGS
For 3 ohm and 15 ohm L/Speakers from high grade sectionally wound output transformer.

RESERVE POWER SUPPLY (for Radio Tuner) 300 v. 30 m.a. smoothed and 6.3 v. 1.5 a. at 4-pin socket.

Also Available

The L45. A compact High Quality 4-5 watt amplifier

Size approx. 7-5-5¾in. high. Sensitivity is 28 millivolts so that the input socket can be used for either microphone or gram., tape, radio tuner, etc. B.V.A. valves used are ECC83, EL84, EZ80. Controls are: Vol. Treble and Bass with mains switch. The Tone controls provide full compensation for long playing records. Output matching for 3 ohm loudspeaker. Retail price £5/19/6.

THE LT45 TAPE DECK AMPLIFIER. A complete unit (power pack and oscillator incorporated) ready for connection to A.C. mains. 3 ohm loudspeaker and practically any make of deck. Negative feedback equalization adjustment by multi-position switch for 3¾, 7½ and 15in. per sec. Retail price 12 gns.

DIATONIC 10-14 WATT. High Fidelity amplifier with integral pre-amplifier. Retail 12 gns.

CONCHORD 30 WATT. Hi-Fi amplifier with two separately controlled inputs. Retail 15 gns.

L50 50 WATT AMPLIFIER. Size approx. 13 x 9 x 7in. Sensitivity 25 m.v. Outputs for 3 and 15 ohm speakers. Retail price 19 gns.

L3/3 STEREOPHONIC AMPLIFIER. Sensitivity 150 m.v. Output 3 watts on each channel. Retail 7 gns.

TRADE AND EXPORT ENQUIRIES TO

LINEAR PRODUCTS LTD. ELECTRON WORKS, ARMLEY, LEEDS Tel.: Leeds 63-0126 (3 lines)

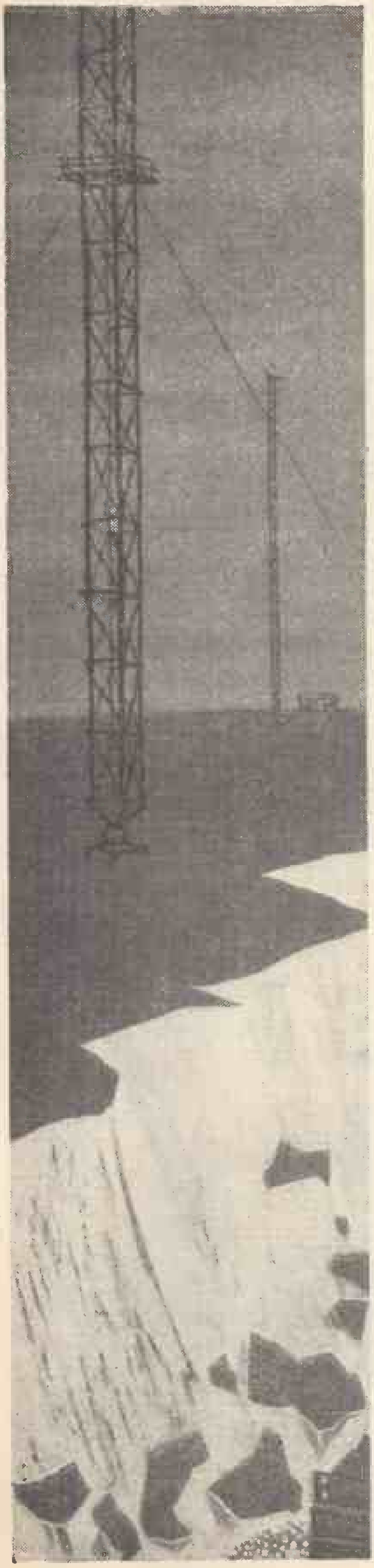

Independent sideband receiver type GFR.552

. . . developed to British Post Office specification and used on their international circuits.

This equipment is designed for operation on long distance, point-to-point short wave radio links forming part of the international trunk network. Special features of the GFR.552 include a high order of oscillator stability and freedom from cross-modulation through which cross-talk between channels or intermodulation between wanted and unwanted signals might occur.

Frequency range — 4 to 30 Mc/s.

Noise Factor — better than 8dB over the band.

A.F.C. — Motor driven with exceptionally high retuning speed and low residual mistuning.

Cross-talk attenuation between channels is greater than 45dB for modulation frequencies above 200 c/s.

Output — Variable up to +14dB relative to 1mW into 600 ohms.

A PRODUCT OF

MULLARD EQUIPMENT LIMITED

A COMPANY OF THE MULLARD GROUP

Mullard House · Torrington Place
London, W.C.1
Tel: Langham 6633

ME 602

meters à la carte

You will find most normal Avo, Crompton, E.A.C., Elliott, Pullin, Taylor Turner, Weir, Weston and other meters in stock at Anders — ready to be served up at once. But Anders take a special pride in their *à la carte* service: non-standard meters of all kinds, shapes, sizes, voltage or current ranges, are supplied within 7-14 days, accurately calibrated, with dials specially drawn. Service is quick and efficient.

Anders electronics LTD

103 Hampstead Road, London, N.W.1. Tel.: EUSton 1639

Contractors to G.P.O. and Government Departments

DGI/Ministry of Aviation approved

Meters, Electronic & Test equipment to individual specifications

REMOTE CONTROL ?

We cannot emulate the mystics of the East but with

FLEXIBLE SHAFTING

We can **operate any element requiring rotation or push-pull movement, or both, no matter if the controlled element is close to or at a distance from the control point.**

We can **operate from an accessible point, switches, valves and other electrical and mechanical devices located in inaccessible places.**

We can**, in fact, solve *your* problems.**

Flexible Shaft Handbook available to technicians on request to Dept. W.

INDUSTRIAL DIVISION

THE S. S. WHITE DENTAL MFG. CO. (G.B.) LTD.
Britannia Works, St. Pancras Way, London, N.W.1.
EUSton 5393 R.C.3

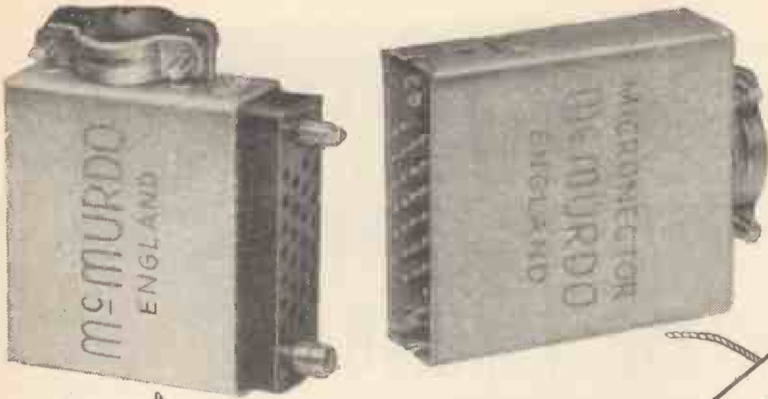

9 | 14 | 18
26 | 34 | 41

50 WAYS

McMURDO MICRONECTORS

- Alternative long plug cover provides pin shroud.
- Strengthened extruded aluminium cover with rigid cable clamp, top or end cable entry.
- Optional latch prevents accidental disengagement. Available for all combinations.
- Mask to protect pins of panel mounted plug.
- Gold plated sockets and pins.
- Dowels provide mechanical alignment. Special alternative dowel socket for electrical connection.

Send for full details to:

THE McMURDO INSTRUMENT CO. LTD., ASHTEAD, SURREY. Telephone: Ashtead 3401

JSP 5648

Wide range and variety of CERAMIC TRIMMERS

High Stability in most exacting conditions.

Are being increasingly incorporated in electronic equipment owing to their VERY COMPETITIVE prices, HIGH QUALITY and RELIABILITY.

Samples and Catalogues available on request.

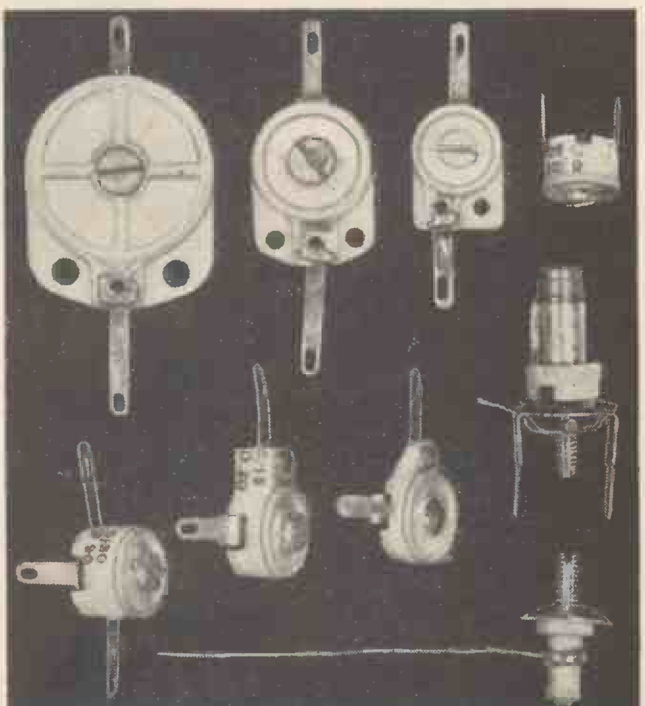

STEATITE INSULATIONS LTD.

31, George Street, Lozells, Birmingham 19.

Telephone: NORthern 8357/8.
Telegraphic address: "Steatite-B'ham, 19".

UNIQUE MONEY-BACK GUARANTEE!

So confident are we of the quality of our equipment that we are able to make the following unusual offer:—

If you are not entirely satisfied with any of the following lines bought from us, we will gladly refund purchase price if goods are returned to us as received within 14 days ! !

We know of no other supplier who makes such an outstanding offer!

No. 1 SYMPHONY AMPLIFIER, Mark III	£12 12 0
Steel Cabinet for above (if required)	£2 2 0
No. 2 SYMPHONY AMPLIFIER, Mark IV	£18 18 0
Steel Cabinet for above (if required)	£2 2 0
SYMPHONY STEREOPHONIC AMPLIFIER	£19 19 0
Steel Cabinet for above (if required)	£2 2 0
EXTRA FOR REMOTE CONTROL	
No. 1 and No. 2 Standard Symphony	£2 2 0
Stereo Symphony	£4 4 0
SYMPHONY No. 1 FM TUNER, Mark II	£14 14 0
Extra for heater transformer (if required)	7 0
SYMPHONY SWITCHED FM TUNER	£15 15 0
Tuner Power Pack (if required)	£3 7 6
SYMPHONY AM/FM TUNER	£24 3 0
Magic Eye (if required)	£1 0 0
DULCI H3-S STEREO RADIOGRAM CHASSIS	£27 6 0
SYMPHONY STEROPHONER	
3 or 15 OHMS Model	£4 19 6

SYMPHONY BASS REFLEX CABINETS:

	Plain Kit	Plain Built	Veneered Built
8in.	£4 15 0	£5 10 0	£10 10 0
10in.	£5 7 6	£6 2 6	£11 0 0
12in.	£5 17 6	£6 12 6	£11 10 0

SYMPHONY INFINITE BAFFLE CABINET (R. J. Enclosure) for 8in. speakers:	
In the white wood	£5 10 0
PST8, in walnut or mahogany by Wharfedale	£10 10 0
SYMPHONY COLUMN ENCLOSURE	
In the White	£13 13 0
SYMPHONY CONCERT GRAND EQUIPMENT CABINET	£19 0 0
Extra for pneumatic lid stay	19 0
SYMPHONY STEREO REPRODUCER KIT	
Symphony Stereo Amplifier	£19 19 0
Lenco GL.58 with Ronette Stereo cartridge and diamond	£24 5 7
Nordyk Haydn Cabinet with 4 legs	£10 19 0
Value	£55 3 7

Special offer:
The three items £52. Switched VHF Tuner 15 gns. extra if required

Specially recommended Speakers where required:

2 x Wharfedale Super 8/FS/AL	at £7 0 0 ea.
2 x Infinite Baffle Cabinets	at £5 10 0 ea.
or 2 x Column Enclosures	at 13 gns. ea.

Send cheque, M.O. or P.O.s now for your hi-fi equipment or request our Illustrated Catalogue and current Bargain List.

Trade Enquiries invited.

NORTHERN RADIO SERVICES

11 KING'S COLLEGE ROAD, LONDON, N.W.3.
Tel: PRImrose 3314

TAKE YOUR PICK

Our wide range of capacitors, incorporating all the latest developments, are described fully in these new leaflets . . .

SEND NOW for COPIES

DALY has succeeded in maintaining full capacity values and working voltages in more compact designs, specially suited to ultra modern equipment :—

PHOTO-FLASH EQUIPMENT • DEAF AIDS
PRIVATE TELEPHONE INSTALLATIONS
AMPLIFIERS • D.C. POWER UNITS
TRANSISTOR EQUIPMENT
MAGNETISATION EQUIPMENT
TEST GEAR

DALY
ELECTROLYTIC CAPACITORS

Condenser Specialists for over 20 years.

DALY (Condensers) **LTD.,** WEST LODGE WORKS,
THE GREEN, EALING, LONDON, W.5. Phone: Ealing 3127-8-9. Cables: Dalcyon, London


LOUD-SPEAKER MANUFACTURERS
FOR THE RADIO INDUSTRY SINCE 1930
REPRODUCERS AND AMPLIFIERS LTD.
WOLVERHAMPTON · ENGLAND
TELEPHONE: 22241/2/3/4 CABLES: AUDIO

the 'Professional' tape for the professional user

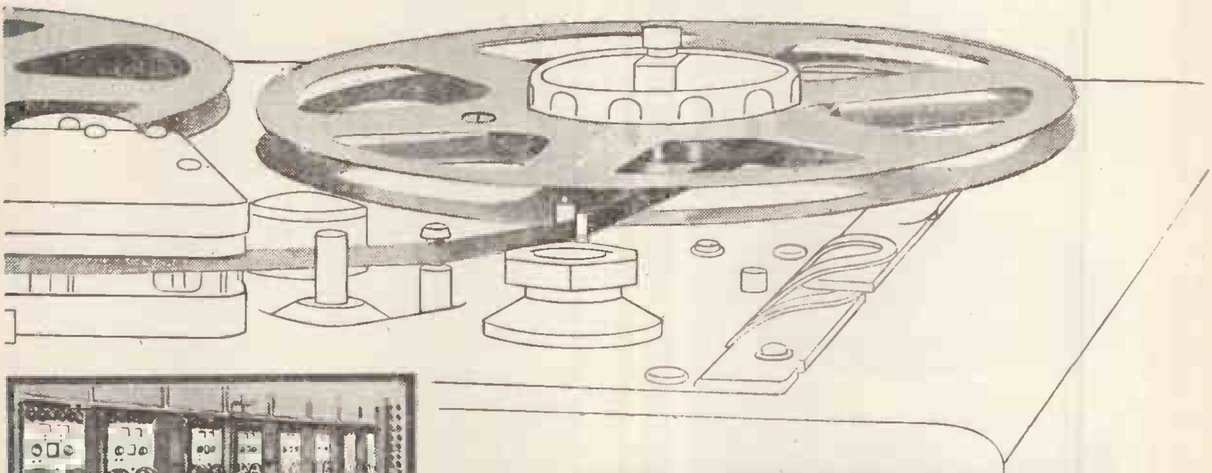

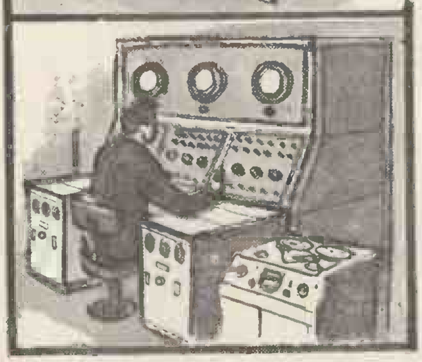

Emitape

"77" "88" "99"

Magnetic Recording Tape offering the highest technical standards. First choice of leading recording, broadcasting and television organisations and widely used in science and industry.

VIDEO

Emitape for Video recording now being supplied to BBC and ITA.

EMIFILM

Sprocketed magnetic recording film designed for all applications where absolute synchronisation is required. 16, 17.5 and 35 mm. Single or double perforation.

EMITAPE INSTRUMENTATION TAPE

Produced to the most exacting specifications and available in various standard widths. Electrostatic filtration down to a particle size of .00001 mms. ensures manufacture under cleanest possible conditions.

EMI SALES & SERVICE LTD. *(Recording Materials Division)* Hayes · Middlesex · SOUthall 2468

ES/R/98

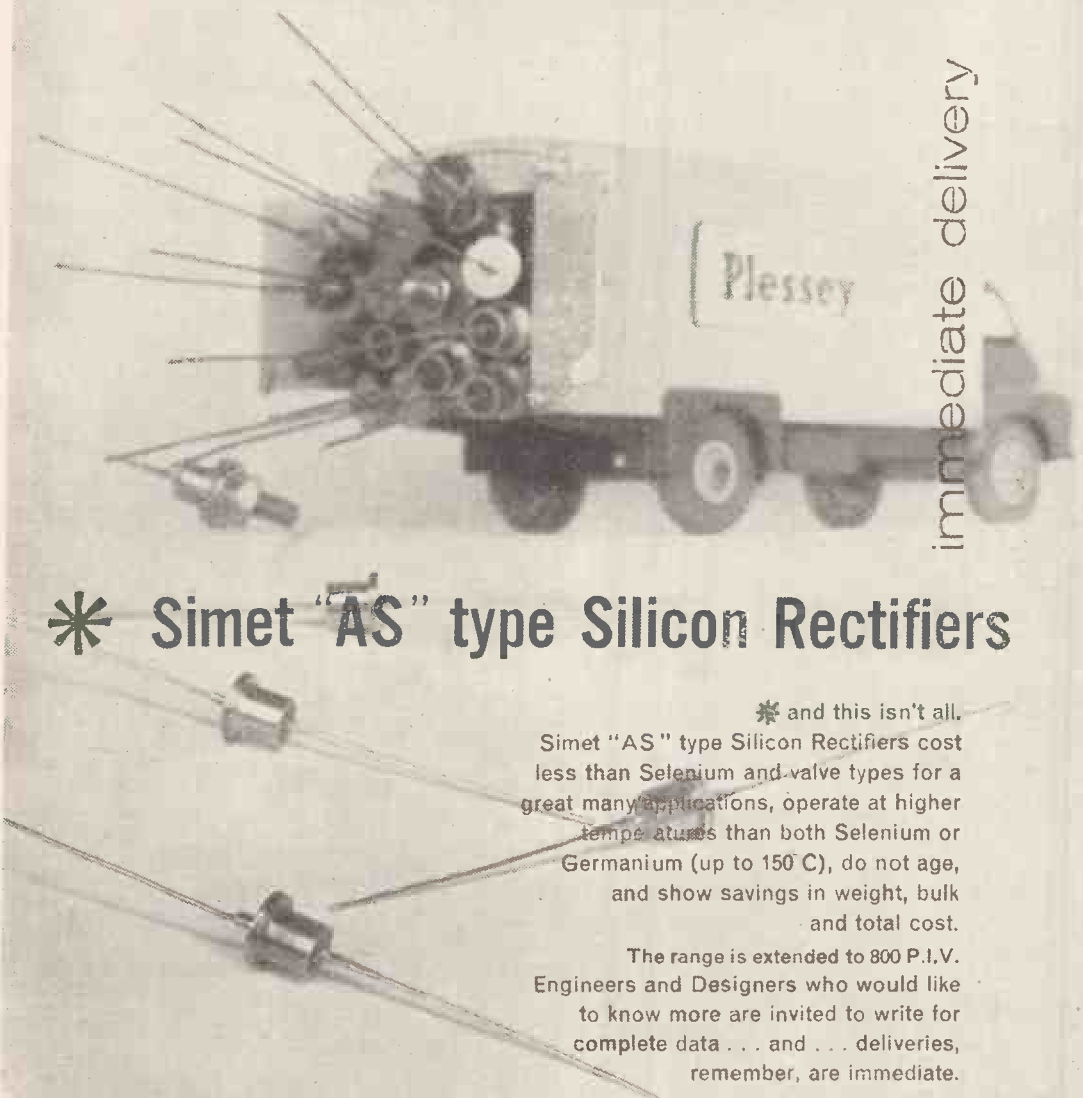

✱ Simet "AS" type Silicon Rectifiers

✱ and this isn't all.
Simet "AS" type Silicon Rectifiers cost less than Selenium and valve types for a great many applications, operate at higher temperatures than both Selenium or Germanium (up to 150°C), do not age, and show savings in weight, bulk and total cost.

The range is extended to 800 P.I.V.

Engineers and Designers who would like to know more are invited to write for complete data . . . and . . . deliveries, remember, are immediate.

SIMET

THE PLESSEY COMPANY LIMITED
Chemical & Metallurgical Division
WOODBURCOTE WAY, TOWCESTER, NORTHANTS
Telephone: TOWCESTER 312-6 Telegrams: Plessey, Telex, Towcester
Overseas Sales Organisation:
PLESSEY INTERNATIONAL LTD
ILFORD, ESSEX ENGLAND
Telephone: ILFORD 3040 Overseas Telegrams: Plessinter, Telex, Ilford

AUTOMAT

High-Stability RECTIFIERS

TRANSFORMERS · D.C. EQUIPMENT

Specially designed to your requirements

SPEEDY DELIVERIES

Send now for your copy of Technical Bulletin 58/1

AUTOMAT · MOORSIDE · SWINTON · MANCHESTER · TEL · SWINTON 4242/4

Issued by Northworks Ltd

All good 'labs' use Radiospares

quality components for design development and prototype work

Service Engineers!

Remember- Radiospares components are delivered absolutely "by return"

Knobs

AN EXCELLENT RANGE OF MOULDINGS FROM STOCK

Embellished types for domestic equipment

Instrument types for modern apparatus

WE ARE ACTUAL IMPORTERS of the popular "Pekalit" range and maintain adequate stocks of the more widely used patterns

UNCLES BLISS & CO., LTD.
CHERRY ORCHARD RD, EAST CROYDON, SURREY
TELEPHONE: CROYDON 3379/6390

CONTACT COOLED RECTIFIERS

SenTerCel

aid BUSH reliability

SenTerCel Contact Cooled Rectifiers have been selected by Bush for H.T. supply circuits in their domestic radio receivers. These belong to a comprehensive range of rectifiers which offer important reductions in size, weight and cost over the conventional metal rectifiers.
In addition greater facility in chassis layout is permitted since they can be mounted at any angle.
A table of ratings is shown below

Half-Wave and Voltage-Doubler Connections

Qty.	Type	Circuit	Maximum Input Volts (r.m.s.)	Max. Output Current mA (mean)	Typical O.C. Output Voltage 16 mfd. Resvr. Cap. Half Load		Typical O.C. Output Voltage 60 mfd. Resvr. Cap. Half Load	
					Half Load	Full Load	Half Load	Full Load
1	C2H	Half-Wave	125	60	135	115	135	120
1	C3H	" "	125	120	120	85	130	120
1	C2D	" "	250	60	275	245	280	255
1	C3D	" "	250	120	275	245	290	275
1	C2D	Volt-Doubler	125	60	275	245	280	255
1	C3D	" "	125	120	260	205	285	265

Push-Pull and Bridge Connections

Qty.	Type	Circuit	Maximum Input Volts (r.m.s.)	Max. Output Current mA (mean)	Typical O.C. Output Voltage 16 mfd. Resvr. Cap.		Typical O.C. Output Voltage 32 mfd. Resvr. Cap.	
					Half Load	Full Load	Half Load	Full Load
1	C2V	Push-Pull	125-0-125	120	140	120	140	130
2	C2D	" "	250-0-250	120	275	250	280	255
1	C3V	" "	125-0-125	240	130	115	140	130
2	C3D	" "	250-0-250	240	280	250	280	260
1	C3B	Bridge	250	120	275	250	280	255
2	C3D	"	250	240	280	250	280	260

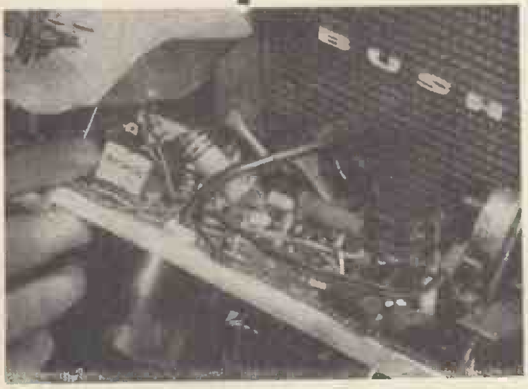

Send for leaflet MF/102

STC COMPONENTS GROUP

Standard Telephones and Cables Limited

Registered Office: Connaught House, Aldwych, London, W.C.2

RECTIFIER DIVISION: EDINBURGH WAY · HARLOW · ESSEX

New

ELAC speakers

RETAIL PRICE LIST

TYPE	FLUX	POWER RATING PEAK	PRICE	P'TAX
8 x 3G	6500g	2.5 WATTS	19/6	6/3
8 x 3C	8500g	2.5 WATTS	22/6	7/3
7 x 4G	6500g	3 WATTS	18/6	5/11
7 x 4C	8500g	3 WATTS	21/6	6/11
5G	6500g	3 WATTS	18/6	5/11
5C	8500g	3 WATTS	21/-	6/9

8"×3"

7"×4"

5"

ELECTRO ACOUSTIC INDUSTRIES LTD., Stamford Works, Broad Lane, Tottenham, N.15

Tel: Tottenham 0505/9 (5 lines)

WEYRAD P.50 TRANSISTOR COILS AND I.F. TRANSFORMERS

FOR 2-WAVE PORTABLE WITH PRINTED CIRCUIT AND ROD AERIAL

P50/1AC M.W. OSCILLATOR COILS. For 176pF TUNING CONDENSER .... PRICE **5/4d.**

P50/2CC 1st and 2nd I.F. TRANSFORMER. 470 Kc/s. OPERATION. "Q" = 150 .... PRICE **5/7d.**

P50/3CC 3rd I.F. TRANSFORMER. 470 Kc/s OPERATION. "Q" = 170 .... PRICE **6/0d.**

RA2W L.W. and M.W. ROD AERIAL 6in. long, flying-lead connections. For 280pF TUNING CONDENSER.. PRICE **12/6d.**

LFTD2 DRIVER TRANSFORMER. Split Secondary Type, semi-shrouded. With 6 connecting tags PRICE **9/6d.**

PCA1 PRINTED CIRCUIT PANEL, $2\frac{3}{4}$ x $8\frac{1}{4}$in. ready drilled with component positions and references printed on rear.. PRICE **9/6d.**

BOOKLET OF DETAILED ASSEMBLY INSTRUCTIONS AND CIRCUIT DIAGRAMS FOR 6-TRANSISTOR LONG AND MEDIUM WAVE SUPERHET .... PRICE **2/0d.**

ALL IN BULK PRODUCTION—TRADE ENQUIRIES INVITED

WEYMOUTH RADIO MFG. CO. LTD., CRESCENT STREET, WEYMOUTH, DORSET

The only Shop in London!

where you can buy

LEKTROKIT

This remarkable chassis construction system which is widely used by the Electronics Industry is now available to the Radio Amateur and can be purchased from:—

super RADIOTECH *limited*

38 MONMOUTH STREET, UPPER ST. MARTIN'S LANE, LONDON, W.C.2

We are proud to have been appointed the sole retail distributors in LONDON and invite you to visit our bright new premises where our manager, Mr. Jack Cunningham, will be pleased to demonstrate the system. We can, of course, supply most of your component requirements at the keenest prices.

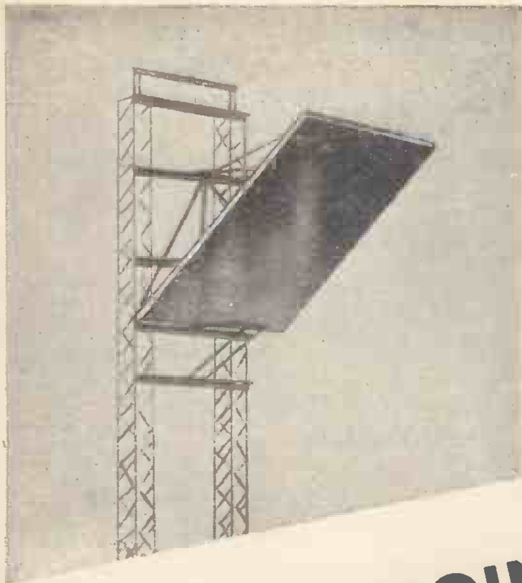

PYE

POINT TO POINT

AS SUPPLIED TO:

Associated Television Ltd.
Scottish Television Ltd.
Tyne-Tees Television Ltd.
Central Rediffusion Services Ltd.
Portuguese Television Service.
Atomic Weapons Research Establishment.
Southern Television Corporation, Adelaide, Australia.
and many other users.

MICROWAVE LINKS

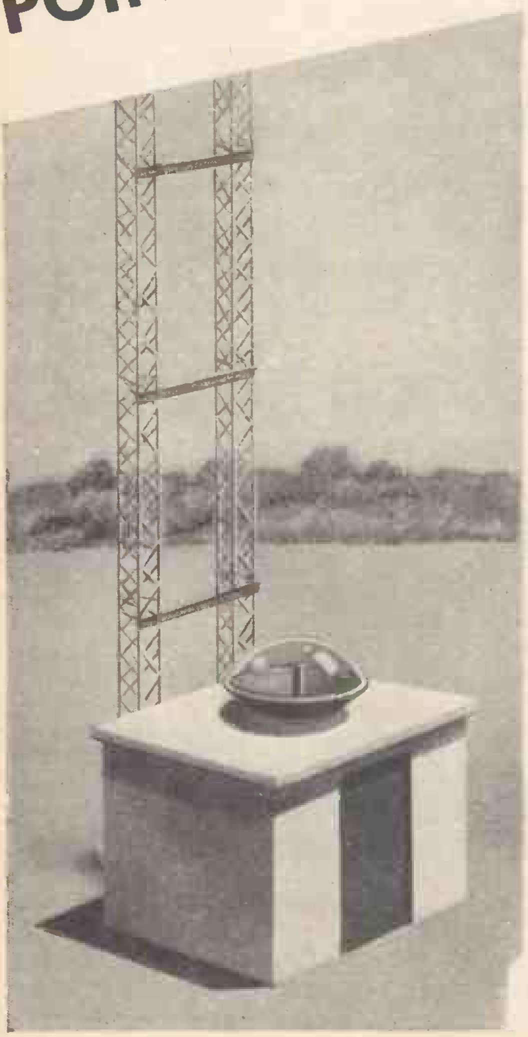

This Pye microwave television link Type PTC M1000 is suitable for use with the N.T.S.C., C.C.I.R. or the British 405-line systems. A sub-carrier f.m. music link circuit is incorporated. The normal frequency range is 6575 to 7425 Mc/s but models can be supplied to cover the range of 5925 to 6425 Mc/s. The r.f. power output is 1 watt. Wave guide or passive reflector installations available. Transportable link equipment is also available.

Please write for full details.

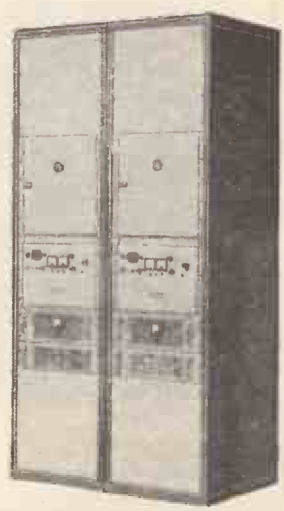

PYE MICROWAVE LINKS

PYE TELECOMMUNICATIONS LIMITED : NEWMARKET ROAD : CAMBRIDGE

Telephone: Teversham 3131 Telegrams: Pyetelecom, Cambridge

TA 41

Wireless World

ELECTRONICS, RADIO, TELEVISION

FEBRUARY 1960

Managing Editor:

HUGH S. POCOCK, M.I.E.E.

Editor:

F. L. DEVEREUX, B.Sc.

Assistant Editors:

H. W. BARNARD

T. E. IVALL

VOLUME 66 NO. 2

PRICE: TWO SHILLINGS

FORTY-NINTH YEAR OF PUBLICATION

Offices: Dorset House, Stamford Street, London, S.E.1

Please address to Editor, Advertisement Manager, or Publisher, as appropriate

PUBLISHED MONTHLY (4th Monday of preceding month) by ILIFFE & SONS LTD., Dorset House, Stamford Street, London, S.E.1. *Telephone:* Waterloo 3333 (65 lines). *Telegrams:* " Ethaworld, Sedist, London." *Annual Subscriptions. Home and Overseas,* £1 15s. 0d. *Canada and U.S.A.*, $5.00. Second-class mail privileges authorised at New York, N.Y. BRANCH OFFICES: *BIRMINGHAM:* King Edward House, New Street, 2. *Telephone:* Midland 7191. *COVENTRY:* 8-10, Corporation Street. *Telephone:* Coventry 25210. *GLASGOW:* 26B, Renfield Street, C.2. *Telephone:* Central 1265. *MANCHESTER:* 260, Deansgate, 3. *Telephone:* Blackfriars 4412. NEW YORK OFFICE: *U.S.A.:* 111, Broadway, 6. *Telephone:* Digby 9-1197.

FRAME GRID VALVES FOR TELEVISION

5

The PCC89 is a variable-mu double triode of frame grid construction, intended for use as a cascode amplifier at frequencies up to 220Mc/s. Its heater is designed for inclusion in a 300mA series heater chain. The valve may be used in tuners with the conventional PCF80 mixer valve or with the frame grid PCF86. In either arrangement it provides reduced noise and improved gain. As in the other valves in the new television series, the most obvious effect of introducing the frame grid is doubling of the slope. Thus the slope of each triode in the conventional PCC84 is 6·0mA/V, while under comparable conditions the PCC89 achieves 12mA/V.

IMPROVED GAIN

A tuner designed round the PCC89 and PCF80 can have a gain of about 52 to 56dB on the various channels, compared with a maximum of about 48dB in a tuner using the conventional PCC84 and PCF80. With the PCC89 and PCF86, the maximum gain is increased to about 60dB, and the noise factor of the tuner is reduced to about 6dB at 200Mc/s. This 'frame grid' tuner can be used in receivers designed for service area or fringe operation. The circuit differences between these two receivers would be in the i.f. amplifier stages.

PCC89

For optimum performance in a tuner the PCC89 must be operated under carefully chosen conditions. There must be sufficient power gain in the grounded cathode stage to overcome the noise of the grounded grid stage. There must also be sufficient a.g.c. voltage available to allow optimum signal handling and the required delay.

OPTIMUM CONDITIONS

Optimum noise factor is obtained with —0·8 to —1·2V bias on the first triode, which is best realised by using cathode bias. Optimum gain is obtained with rather less bias, which can be realised only under grid current bias conditions. This second mode of operation shows up to 2dB more gain on Band III than that obtainable with cathode bias, and just over 1dB on Band I, at the cost of a small increase in noise factor. However, the d.c. feedback effect of the cathode bias resistor is lost, and the spreads in gain will be a little greater with grid current bias. A tuner gain of 60dB (with PCC89 and PCF86) can be achieved on Band I with either system of biasing; but on Band III this figure is attainable only with grid current bias.

TAIL AND A.G.C.

The PCC89 has been given a variable-mu characteristic so that it can handle large signals without introducing perceptible cross-modulation. The valve can be operated with any tail length between —9V and —22V (which are the voltages for 1/100th slope reduction.)

Signal handling ability, limited by sound on vision or vice versa, can be better than 1·0V at the grid of triode 1 (250mV at the aerial) with long tail conditions and with cathode or grid current bias for triode 2. In fringe areas, with adverse sound to vision ratios, half this figure is realistic.

Many different operating conditions are possible for the PCC89. The choice is based on the gain-slope relationship which is required, the available a.g.c. voltage, and the i.f. arrangements to which the cascode has to be matched.

The high gain of frame grid tuners means that the designer should give special attention to the question of stability in both parts of the cascode circuit. Neutralisation of the anode-to-grid capacitances is advisable.

Mullard

MULLARD LIMITED
MULLARD HOUSE,
TORRINGTON PLACE,
LONDON, W.C.1

MVM 429

L.1387/P & S
(4 small & 4 large pins)

"BELLING-LEE"

L.1388/P & S
(8 small pins)

MINIATURE UNITORS

L.1389/P & S
(12 small pins)

Current rating:
Small pins 5 A. each, large pins 10 A. each, for a 20°C. rise in temperature.

Breakdown voltage:
(With shrouds L.1404/5/6).

	Sea-level.	At 68,000 ft.
Between pins:	3 kV.	500 V.
Pins to earth:	2.5 kV.	500 V.
Voltage proof:	2 kV.	

Max. working voltage:
500 V. peak (in dry conditions).

Contact resistance:
Less than 2 milliohms.

Insulation Resistance:
Greater than 2.5 x 10^{10} ohms.

Withdrawal force: 8 oz./pin.

Weights of mated pairs:
L.1387. 10 gms. L.1388 8 gms.
L. 1389 9.5 gms.

These items in our miniature range give three possible pin or socket arrangements, i.e. 4 small and 4 large pins, 8 small pins, or 12 small pins, each connector having a central earthing pin and polarising key. The sockets are gold- or silver-plated (-/Au or -/Ag) beryllium copper, four-slotted to give resilience and ensure good contact with the pins which are gold- or silver-plated brass.
These miniature Unitors have been designed to carry out the functions of the standard Unitor on miniaturized equipment where space and weight considerations prevent the use of the larger type. Their purpose is, of course, the inter-connection of units in an assembly.
Various pin combinations and arrangements are possible within the same chassis cut-out, giving a highly flexible method of obtaining an individual connector for each group of inter-connections. The moulding carries corresponding numbers on each side of both plugs and sockets, facilitating wiring and fault finding.

Most "Belling-Lee" products are covered by patents or registered designs or applications.

Regd.

BELLING & LEE LTD
GREAT CAMBRIDGE ROAD, ENFIELD, MIDDX., ENGLAND
Telephone: Enfield 3322 • Telegrams: Radiobel, Enfield

"BELLING-LEE" NOTES

No. 13 of a series

Some aspects of G: the effect of acceleration

This series of tests covers far more ground than we can ever hope to touch upon in one issue. One column might serve as an introduction to a very complex subject, that is about all.

Acceleration, i.e. the rate of change of velocity, can affect the performance and reliability of electronic equipment in many ways. The mechanical strain can result in damage, both when the acceleration is steady, and also when it varies, either periodically as with vibration or suddenly as with shock or bumping. These four headings; steady acceleration, vibration, shock and bumping summarize the most important mechanical tests that have to be made to electronic components. Let us look at each one separately.

A good example of steady acceleration is given when you ride in a car. While it is increasing its speed, you find yourself being pressed into the back of your seat. When travelling at uniform speed, although it may be fast, you feel no force acting on you, unless of course you turn a corner. If now the brakes are applied you are apt to crack your head on the dash board.

These same forces occur, but with much greater severity in aircraft and rockets. The forces can be in any direction, for example, backwards during take-off, sideways while manoeuvring and forwards during landing, and the magnitude of the force can be very much greater than the force due to the static weight of a component. In fact, the strain is often expressed in terms of "g," it being assumed that the equipment is being subjected to a *force "g" times its normal weight. In incorrectly designed equipment unretained valves might fly from their sockets, and heavy components such as transformers, if insecurely fixed, might come adrift from their mountings, in both cases causing serious failure of the equipment. All parts of the equipment, however small, have an apparent weight many times their normal weight, and care and good design are required for equipment to remain working under these conditions.

**The force acting on a body at rest i.e. gravity, is one 'g' times its mass.*

Advertisement of
BELLING & LEE LTD.
Great Cambridge Rd., Enfield, Middx.

we can get you out of a rectifier problem

We, that's the M-O Valve Co. Ltd., have spent over 40 years bottling up hard valves, soft valves, tough going-aloft valves, standard valves, valves to government specs . . . so we know how you feel in there. But we're used to it, because now we've acquired a rare collective know-how that can beat most valve problems. And of course, it's backed by the brilliant research, progressive development and flexible production you'd expect us to have. Next time you're enveloped in a valve problem, let us know—if we haven't a ready-made type for you, we'll see if we can make you one to measure.

XENON FILLED TYPE. *The G E C. range will keep going a long time—and has better PIV safety ratings too.*

MERCURY VAPOUR TYPE. *We've had over 30 years of know-how in making this type of rectifier. As you'd expect, they're the best you can get. There's a range of eight.*

VACUUM TYPE *Too many even to give you an outline. (Bi-phase, full-wave, high voltage, special quality, 450 to 28,000V rms.)*

Let us know what types you're interested in and we'll send you full details.

G.E.C. valves are obtainable from

THE M-O VALVE CO. LTD

BROOK GREEN · HAMMERSMITH · LONDON W.6

A subsidiary of the General Electric Co. Ltd

Aspects of design

19 AUTOMATIC FREQUENCY CORRECTION WITH A SEMICONDUCTOR JUNCTION DIODE

This is the Nineteenth of a series of special features dealing with advanced problems in television and radio circuit design to be published by The Ediswan Mazda Applications Laboratory. We will be pleased to deal with any questions arising from this or other articles, the twentieth of which will appear in the March 1960 issue.

Most television receivers of today employ a fine tuning control to enable the viewer to adjust the receiver to its optimum frequency. Manual tuning adjustments may be necessary when the receiver is switched on from cold or when switched from one channel to another, owing to local oscillator drifts caused by initial warming up and mains voltage fluctuations. Temperature compensation of oscillator capacitors reduces frequency drift appreciably but even so some external adjustment may be required to obtain the best picture quality. The fine tuner itself contributes in no small way to the drift in the oscillator circuit and its total elimination is an advantage. Optimum picture and sound quality can be achieved without the need for manual tuning adjustment of any kind if the receiver incorporates Automatic Frequency Correction. Briefly, the operation of AFC is carried out in the following manner. The sound IF frequency is fed to a frequency discriminator tuned to 38.15 Mc/s. Any drift of the local oscillator frequency results in an identical drift of the IF frequency. A d.c. voltage output is obtained across the discriminator load resistance, whose polarity depends upon the direction of the IF frequency drift about its centre value of 38.15 Mc/s. The output voltage from the discriminator is fed back to a variable reactance element which forms part of the oscillator circuit and it has the property of controlling the oscillator frequency when a d.c. bias voltage is applied to it. By proper arrangement, the d.c. output voltage from the discriminator can be used as the control bias and thus counteract the initial oscillator frequency drift.

Conventional valves have been used as variable reactance elements in FM receivers operating in Band II, but they are more difficult to apply for Band III television frequencies. However, one of the more recent semiconductor devices is the Junction Diode, such as the Ediswan Mazda XD901, which behaves as a voltage sensitive variable capacitor and this device opens up new design possibilities in oscillator control circuits. The Ediswan Mazda XD901 has been specially designed for AFC application and is ideally suited for use in Bands 1, 2 and 3. Its extreme compactness makes it possible to be incorporated in a conventional turret tuner with little modification. The Ediswan Mazda XD901 is a PN junction type germanium diode, hermetically sealed in a compact can and has axial stub leads. The series lead inductance has been made very small, an important feature for use at frequencies of up to 250 Mc/s.

JUNCTION DIODE CAPACITANCE

The capacitance of a reverse biased abrupt semiconductor function varies with voltage according to the law:

$$c = \frac{k}{(V+U)^{\frac{1}{2}}}$$

where k is a constant, U is approximately 0.4 V for the XD901 and V is the reverse bias voltage.

A typical curve of change of capacitance with reverse bias of the Ediswan Mazda XD901 is shown by curve A, Figure 1.

An oscillator circuit incorporating the Ediswan Mazda Junction Diode for AFC is shown in Figure 2. The diode is operated at a static reverse voltage of 5 V, on which is superimposed the controlling error voltage derived from the frequency discriminator. A d.c. blocking capacitor C_p, in series with the diode is used and its value is made small in order to increase the effective series resonant frequency and thus reduce the effective diode losses across the oscillator grid circuit. When the diode is used in the moulded nylon holder specially designed for the purpose the effective series resonant frequency of the Ediswan Mazda XD901 diode with a series capacitor of 7 pF is about 445 Mc/s at a bias of 5 V. This series capacitor however, reduces the effective capacitance sensitivity of the diode in the circuit. Typical capacitance-voltage curves, as seen across the oscillator grid circuit are shown in curves B, Figure 1, the typical value of C_p being 7 pF. Further, in order to achieve the highest possible capacitance sensitivity, fixed tuning capacitors are minimised in the oscillator circuit, so that a sizeable proportion of the tuning capacitance is formed by the diode and its series capacitor.

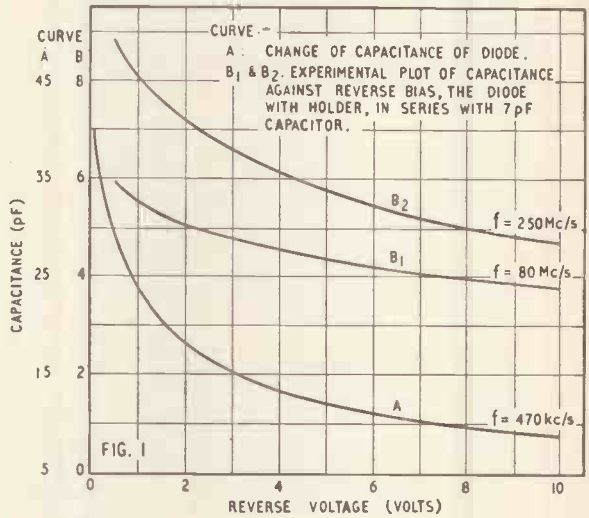

FIG. 1

FIG. 2

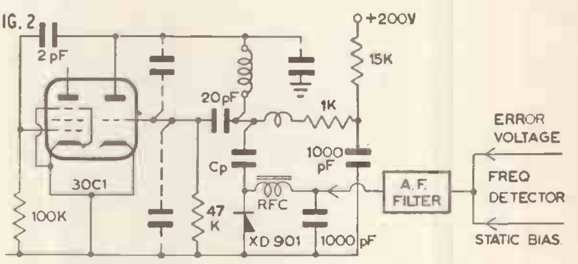

The diode series resistance r_s, which is not frequency sensitive, dissipates some available oscillator power. The grid circuit resistance of an oscillator is inherently low and to some extent this masks the damping effect that the diode series resistance may have on the circuit. But to ensure a low loss even at 250 Mc/s, the series resistance of the XD901 has been reduced to 5 ohms.

The undesirable effect of the flow of leakage current in the AFC diode is to cause a voltage drop across the decoupling resistors and thus to reduce the effective applied voltage to the diode. The leakage current of a germanium diode is sensitive to temperature changes but, apart from surface leakage, is almost independent of the applied reverse voltage until the breakdown region is reached. The magnitude of the surface leakage current is influenced by the state of cleanliness of the diode during manufacture. With modern production techniques, the leakage current of the Ediswan Mazda XD901 is controlled to a value which ensures that during life it does not exceed 10 μA at 55°C and at a reverse bias of 10 V.

In a TV receiver, an AFC loop designed on the basis of the above considerations can give a frequency drift improvement of 7 to 1 on Channel 9, and 3 to 1 on Channel 1, when compared with a similar receiver but without AFC.

Associated Electrical Industries Ltd
Radio and Electronic Components Division
Technical Service Department
155 Charing Cross Road, London, W.C.2
Tel: GERrard 8660. Grams: Sieswan, Westcent, London

EDISWAN MAZDA XD901 JUNCTION DIODE

The XD901 is a junction-type germanium diode having the property of a voltage sensitive variable capacitance. It is specially constructed to have a low internal series resistance and minimum residual inductance. These important features ensure successful operation at 250 Mc/s by providing a sufficiently high self-resonant frequency and high Q. The diode is hermetically sealed in a compact can and it has axial stub leads for clip-in connections.

A variable capacitance diode having the small size and low losses of the Ediswan Mazda XD901 has many useful applications in electronics, for instance, it is particularly suitable in Automatic Frequency Control circuits in Bands I, II and III.

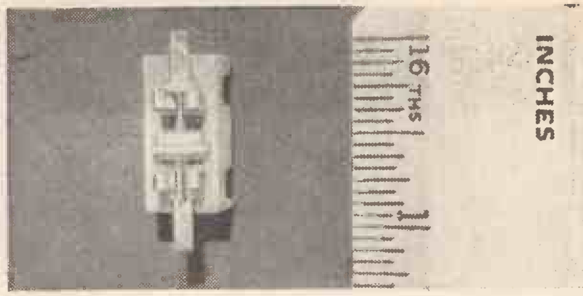

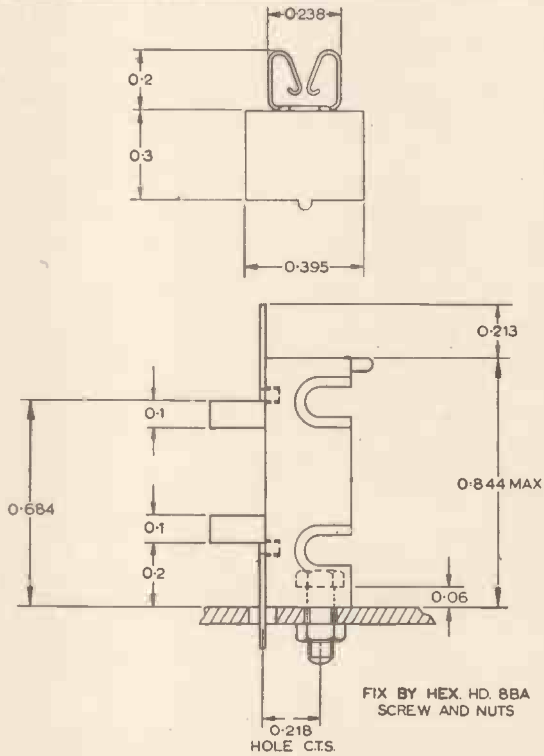

RATING (Absolute value for T_{amb} = 55°C)

Maximum reverse voltage (d.c.)	(volts)	10
Maximum reverse voltage (peak)	(volts)	14

GENERAL CHARACTERISTICS

Capacitance c at V = 5 V (Diode biased in reverse direction)	(pF)	12 ± 3
Resistance r (approx)	(ohms)	5
Inductance l (approx) (With connections made 1/8in. from the seals)	($m\mu H$)	7
Maximum leakage current V = 5 V at 55°C	(μA)	6
Maximum leakage current V = 10 V at 55°C	(μA)	10

EQUIVALENT CIRCUIT
For Diode Biased in the reverse direction.

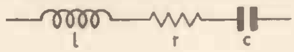

DIMENSIONS AND BASING

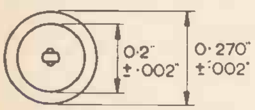

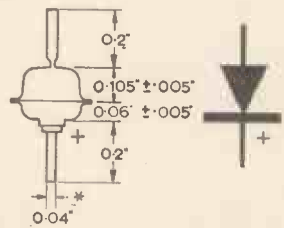

* To bias in reverse direction this lead should be positive with respect to the other lead.

The can is covered with a plastic sleeve of wall thickness 0.01in. which is not included in the above dimensions.

In Fig. 1 curve A shows the variation of diode capacitance at 470 kc/s with applied reverse bias, approaching very closely to the theoretical law relating diode capacitance to applied bias, viz.:

$$c = \frac{k}{(V + U)^{\frac{1}{2}}}$$

c = diode capacitance.
V = reverse bias in volts.
U ≈ 0.4 volt.
k is a constant ≈ 27.

Curves B_1 & B_2 show the capacitance change that would apply at VHF in a practical circuit, in this case an AFC circuit for a television receiver, with the diode mounted in a "Clix" holder in series with a capacitor of 7 pF.

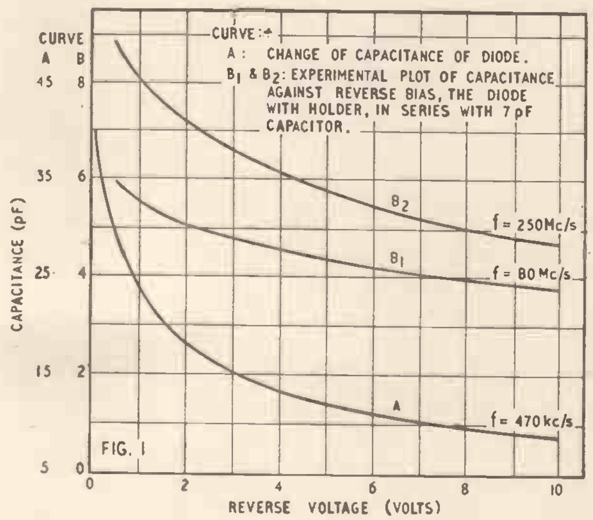

DIODE MOUNTING

To avoid any risk of damage to the diode, due to excessive heating, the diode should not be soldered directly into the wiring or be clamped in such a way as to impose excessive mechanical strain. It is preferable to use the diode in conjunction with a suitable holder making use of the short axial stub leads provided for this purpose.

A holder that has been specially designed for clip-in mounting of the XD901 diode is the "Clix" holder type 103/B2362 in which the spring clips, while giving good electrical contact, still provide a low inductance. The XD901 diode mounted in the special "Clix" holder is illustrated above.

The moulded nylon body of the holder is shaped to prevent the diode being accidentally inserted with incorrect polarity and it provides three alternative mounting positions. The illustration shows the mounting where one diode terminal can be directly earthed; alternatively, the holder can be fixed either on its broad or narrow side whichever is more convenient.

Associated Electrical Industries Ltd
Radio and Electronic Components Division
Technical Service Department
155 Charing Cross Road, London, W.C.2
Tel: GERrard 8660. Grams: Sieswan, Westcent, London

EDISWAN
MAZDA

CRC 15/52

MARCONI'S WIRELESS TELEGRAPH COMPANY LIMITED, CHELMSFORD, ESSEX, ENGLAND

M.8


203

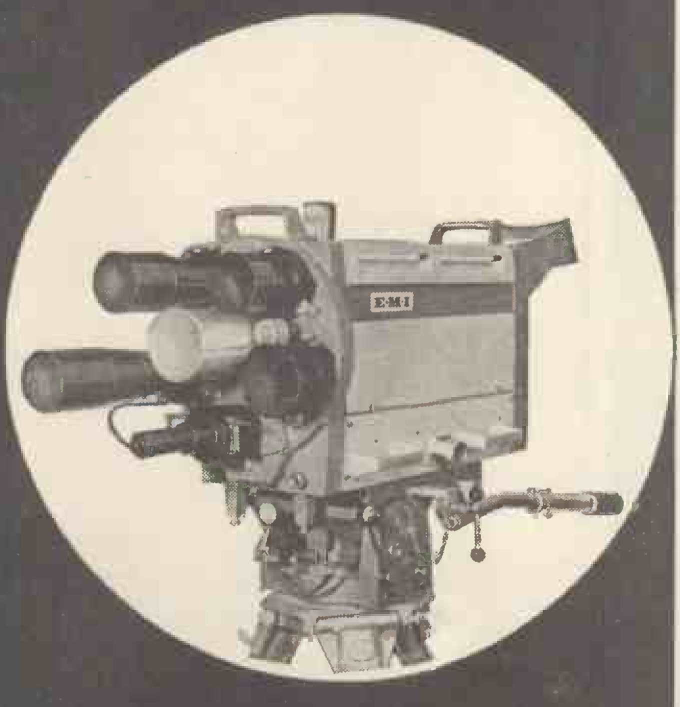
E·M·I

Model W.V.A.

Vortexion
quality equipment

120/200 WATT AMPLIFIER

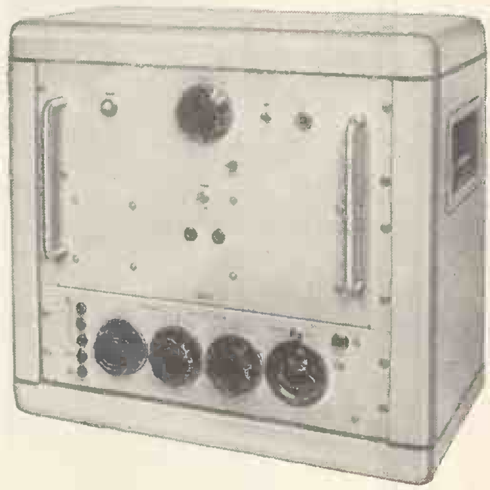

TAPE RECORDERS

The W.V.A. tape recorder now has provision for Stereo plug in heads to enable this recorder to replay Stereo. The regular models are retained with additions and improvements. Our high standard which has made these recorders famous has been maintained, resulting in their being chosen for the foremost musical centre in this country.

30/50 WATT AMPLIFIER

Gives 30 watts continuous signal and 50 watts peak Audio. With voice coil feedback distortion is under 0.1% and when arranged for tertiary feedback and 100 volt line it is under 0.15%. The hum and noise is better than—85 dB referred to 30 watt.

It is available in our standard steel case with Baxendale tone controls and up to 4 mixed inputs, which may be balanced line 30 ohm microphones or equalised P.U.s to choice.

Will deliver 120 watts continuous signal and over 200 watts peak Audio. It is completely stable with any type of load and may be used to drive motors or other devices to over 120 watts at frequencies from 20,000 down to 30 cps in standard form or other frequencies to order. The distortion is less than 0.2% and the noise level —95 dB. A floating series parallel output is provided for 100-120 V. or 200-250 V. and this cool running amplifier occupies 12¼ inches of standard rack space by 11 inches deep. Weight 60lb.

12-CHANNEL ELECTRONIC MIXER

This is similar to the 4-channel, but is fitted with 12 hermetically sealed controls, 12 balanced line microphone transformers potted in mu-metal boxes, and a mains transformer also potted in mu-metal. All components which can affect noise are tested and selected before insertion. It is supplied in standard steel case or 7in. rack panel.

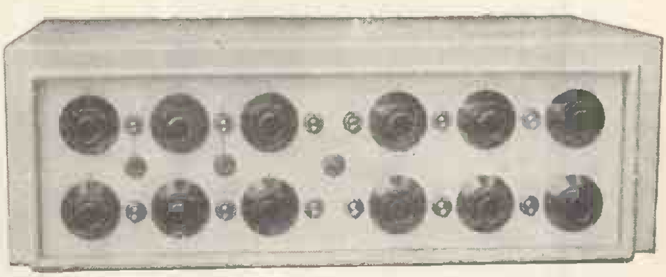

Full details and prices of the above on request

VORTEXION LIMITED, 257-263 The Broadway, Wimbledon, London, S.W.19

Telephones: LIBerty 2814 and 6242-3 Telegrams: "Vortexion, Wimble, London."

how many ohms in a shoelace...?

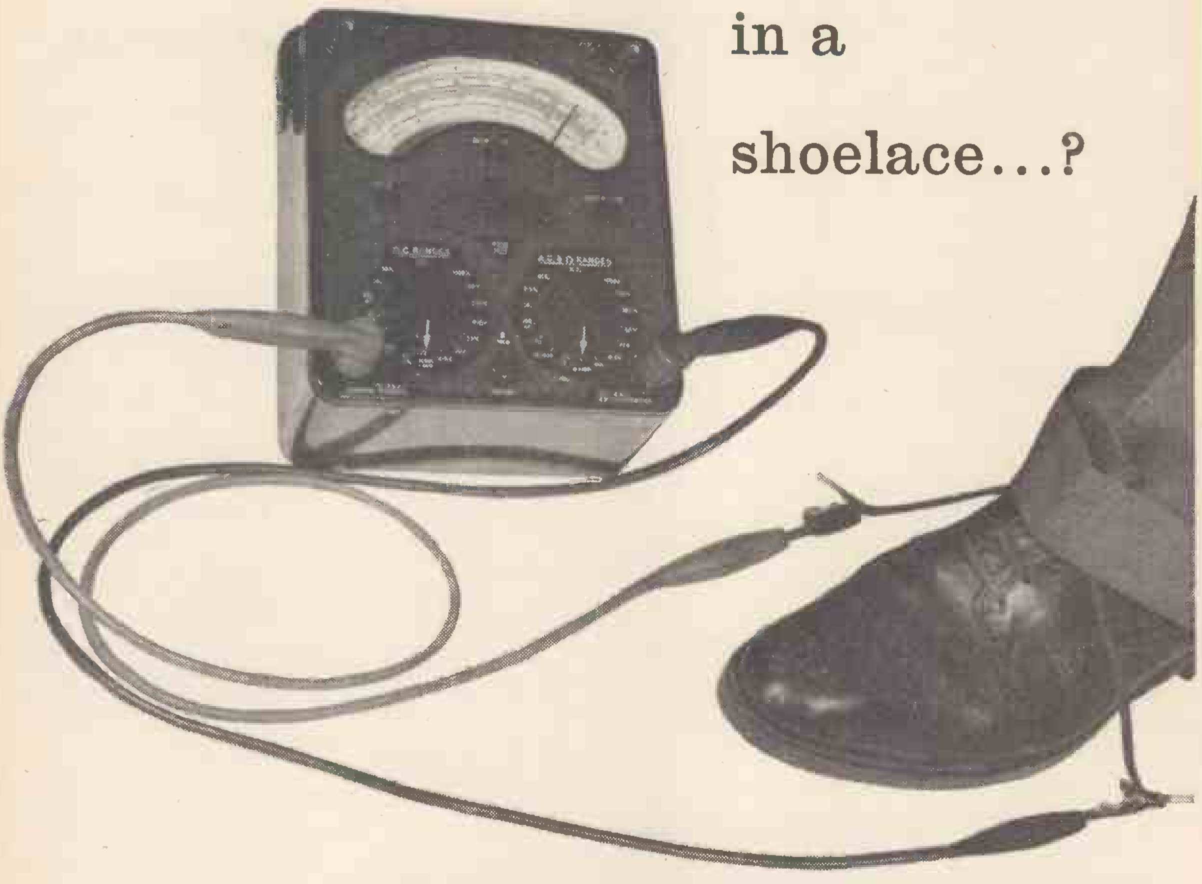

Fanciful? No, because as our photograph proves, a shoelace can be made electrically conducting by impregnating it with "dag"* colloidal graphite.
Unrealistic? As a practical proposition the shoelace test is just that; as a simple illustration of a fundamental idea we think it is effective enough.
Over-simplified? Perhaps, yet thousands of cars are fitted with a non-metallic conducting braid which has much in common with a shoelace impregnated with colloidal graphite.
A non-conducting material can be made conductive by treating it with "dag" colloidal graphite, either by impregnation (surface coating or dipping after manufacture) or incorporation (addition during manufacture).
Furthermore, you can impart any or all of the many other characteristics of colloidal graphite: low friction and "parting" properties, resistance to heat and wear, chemical inertness.

** Registered trade mark of Acheson Industries (Europe) Ltd: licensed user—Acheson Colloids Ltd.*

Acheson Colloids

LIMITED

P.O. BOX 12 · PRINCE ROCK · PLYMOUTH · DEVON

(a subsidiary of Acheson Industries (Europe) Limited)

Manufacturers of dispersions of colloidal graphite, molybdenum disulphide, silver, glass vermiculite in suitable carrier liquids including oil, water, white spirit, alcohol and toluene.

If your problem is basically how to make plastics, natural or synthetic fibres, leather, cloth, paper or wood electrically conducting, then you should get in touch with us.

ACHESON

Also Acheson Colloids Company, Port Huron, Michigan, U.S.A. and Acheson Colloiden N.V. Scheemda (Gr.) Netherlands

Amplifiers that are acclaimed throughout the world*

* *LEAK Amplifiers are the choice of professional engineers such as the B.B.C. (over 500 delivered), the South African Broadcasting Corporation (600), ITV and many other Commonwealth and Overseas broadcasting and TV systems, who use them for transmitting and/or monitoring the broadcasts to which you listen. Also, many of the gramophone records to which you listen are cut via LEAK Amplifiers.*

Extract from Test Report by J. C. G. Gilbert reprinted from the Music Trades Review, also reprinted in our advertisement in the October issue of this magazine. The full two-page Test Report and an illustrated brochure on the amplifiers will be sent you on request.

The "Point-One Stereo" pre-amplifier is designed so that it can be used with any Leak monaural power amplifier or a combination of any two Leak monaural power amplifiers additionally to its more normal use with the "Stereo 20" or "Stereo 50."

"The Point-One Stereo" pre-amplifier is probably the most comprehensive unit in existence covering every requirement for stereo tape, disc and radio plus monaural amplification for any form of input signal . . . it is difficult to think of any additional requirement that one would ever wish. The equipment performs with the high performance always associated with the tradition of Leak equipment. It is a fine example of design and construction, and the pre-amplifier can be used with any other Leak main amplifiers. How the pre-amplifier can be sold for a little as £21 can be answered only by Harold Leak . . .

Summing up, therefore, one can highly recommend the Leak stereo system for use with any current monaural or stereo input whether it be from pickup, tape, radio or microphone."

Ask your Dealer to show you Leak Equipment.

Monaural

- VARISLOPE III PRE-AMPLIFIER
- TL/12 PLUS POWER AMPLIFIER
- SOUTHDOWN CABINET

TOTAL £55 : 13s.

Stereo

- POINT-ONE STEREO PRE-AMPLIFIER
- STEREO 20 POWER AMPLIFIER
- SOUTHDOWN CABINET

TOTAL £72 : 9s.

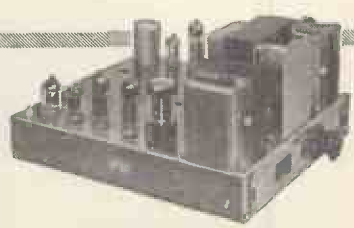

TL/12 Plus Amplifier 18 gns.

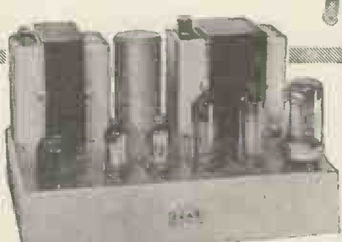

Point-One Stereo Pre-Amplifier £21.

Stereo 20 Amplifier 29 gns.

LEAK

the first name in High Fidelity since 1934

H. J. LEAK & CO. LTD., BRUNEL RD., WESTWAY FACTORY ESTATE, LONDON, W.3

Telephone: SHEpherds Bush 1173/4/5. *Telegrams: Sinusoidal, Ealux, London.*

Please send me Test Report ☐

Brochures ☐

NAME ....

ADDRESS ....

....

.... WW/2/60

INDUCTOR FLUORESCENTS

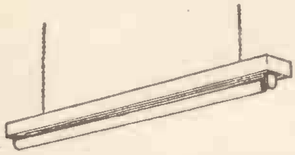

These represent today's best value in lighting. All models are complete with polyester-filled chokes (so far as we know not available in any other low-priced fittings) all are made from heavy gauge sheet steel, stove enamelled white, use all canister-type plug-in starters, and all are fitted with interference suppressors. Guaranteed for two years:

Inductor 80 for 5ft. 80-watt lamp 39/6+5/- carr. and ins.

Inductor 40 for 4ft. 40-watt lamp 32/6+4/6 carr. and ins.

The Three-Forty: for 3ft. 40-watt lamp 31/6 +3/6 carr. and ins.

Inductor 20 for 2ft. 20-watt lamp 29/6+3/6 carr. and ins.

Circle Light for 40-watt circular lamp 49/6 +3/- carr. and ins.

Note: Prices do not include tube but these are the latest bi-pin type easily obtainable from your local electrical shop or if you wish direct from us.

Special Offers:

Inductor 40 complete with tube ready to work 39/6+5/6 carr. and ins.

Three-Forty complete with tube ready to work 39/6+4/6 carr. and ins.

Miniature Microphone

American made. Dynamic type. Real bargain at 2/6, plus 6d. postage.

Building a Scope?

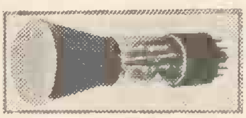

3in. oscilloscope tube. American-made type No. 3FP7, octal base 6.3 v. .6 amp. heater, electrostatic deflection, brand new and guaranteed, with circuit diagram of oscilloscope, 15/- each, plus 1/6 post and ins.

"Dim and Full" Switch

Particularly useful for controlling photoflood lamps which have only a short life at full brilliance. This toggle switch has three positions: the first position puts two lamps in series at half brilliance for setting up, the second position is off and the third position full brilliance for the operation shots. Also useful for controlling night lights, heaters, etc., etc. Price 3/9 each. Post 9d. Circuit diagram included.

Dulci DPA10 Amplifier

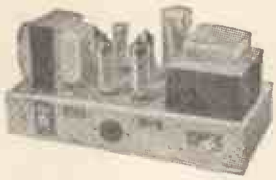

Made by the Dulci Company. It is laboratory designed and is of the highest fidelity, has superb reproduction and complete freedom from hum, high output sensitivity, 10-watt output and ample feedback all combined to give a truly linear output. Uses all-glass miniature valves, including two EL84s in push-pull. Price £12/12/-, or £1 down and 26 weekly payments of 10/-.

Our 68-page Hi-Fi Catalogue is now being sent out to customers—gives details of the latest and best Hi-Fi equipment with over 400 illustrations. Price 2/6 per copy which is refundable from purchases.

INFRA RED HEATERS

These latest type heaters are ideal for bathroom, kitchen, bedroom, etc. They are simple to make from our easy to follow instructions—uses silica enclosed elements designed for the correct infra-red wavelength (3 microns). Price for 750-watt element and instructions, 15/6 plus 2/6 post and insurance. Or made-up heater, 52/6 plus 3/6 post and insurance—fully tested and guaranteed.

Assure your future

The ownership of a good instrument has been the turning point in many a famous career. You can own the latest Pullin Series 100 Test Set which is undoubtedly a most useful instrument by a firm long famous for fine instruments, entirely redesigned, it has a square movement with diacon plastic cover, this makes for a brighter, more readable scale, extra scale length and wider angle of vision. With the test set is included a pair of combined test prods and crocodile clips also a stand for inclining the meter at the best reading positions. Ranges A.C. Volts: 0-10, 0-25, 0-100, 0-250, 0-500, 0-1,000, ditto D.C. A.C. Current 0-100 mA. D.C. Current 0-2.5, 0-10, 0-100, 0-500 mA. Resistance: 0-1M and 0-10K. All at 10,000 ohms per volts—Price £12/7/6 or £1/4/- deposit and 26 fortnightly payments of 10/-, non callers add 5/- carr. and insurance.

FREE GIFT.—All purchasers of the above items this month will receive Range Extender scale and data which add. capacity 2pF—1mFd., in two ranges. Inductance 0-100 henrys, etc., etc.

ANOTHER BATTERY CHARGER BARGAIN
Components Would Cost More

Car Battery Charger—ready-made high output battery charger in stove enamelled sheet steel louvred case. New, complete and ready to work. Rated at 12 v. 5 amps. and variable rate selector for trickle charging, also a meter to show charging rate. Suitable for 230/250 A.C. mains. Special snip price of 65/-, plus 3/6 post and ins.

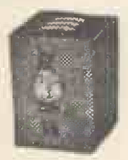

Unique Opportunity to build Fine Transistor Set

Constructor's parcel: to build Pocket 6 Transistor Set as currently being sold at £17/17/-. Parcel comprises motifed, two-tone cabinet as illustrated, tuning dial, two gang tuning condenser, combined bakelite chassis/printed circuit and easy-to-follow circuit. Costing value 57/6—offered while supplies last at only 29/6, plus 2/6 post. Suitable for your own circuit or to build original circuit. All parts available at highly competitive prices. Do not miss this tremendous bargain.

12-Channel Turret Tuner

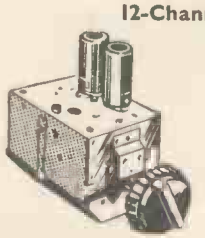

Ideal for converting an old or building into new T.V. These are brand new stock not surplus, supplied complete with valves and coils for local Band I and Band III stations. Model 1. I.F. Output 33/38 Mc/s. series heaters (parallel heaters, 5/- extra).

Model 2. I.F. Output 16/19 Mc/s parallel heaters (series heaters, 5/- extra). With instructions and circuit diagram. 79/6. knobs 3/6 extra. Postage and insurance 2/6.

FOR ADDRESSES SEE OPPOSITE PAGE

SPECIAL THIS MONTH

Battery Charger Rectifier—selenium 12-15 v., 5 amp., 12/6.

Blank Metal Chassis—all 2½in. deep from 18 gauge aluminium. Sizes: 6in. × 2in., 4/6; 7½in. × 5in., 6/-; 13½in. × 9in., 10in. × 7½in., 7/-; 11½in. × 7½in., 8/-.

Metal Chassis—punched for Mullard 510 Amplifier, complete with inner screening sections and stove enamelled, 12/6 set.

Geiger Counter Tubes—20th century type, Type No. G24, with circuit of geiger counter, 29/6.

Luminous Switch, double pole designed for electric blankets, neon indicators glow when appliance is switched on, 10/-.

Waterproof Heater Wire—suitable electric carpets, electric blanket, hand muffs, foot pads, etc., 7d. per yard.

Twin Twisted Lighting Flex—equivalent 14/36. rubber insulated, cotton covered, 17/6 per 100 yard coil.

Moving Coil Meters

0-500 microamp	2in. flush	17/6
250-0-250 microamp ..	2½in. surface	27/6
750 microamp	2½in. surface	17/6
5-0-5 microamp	2½in. flush ..	17/6
0-30 milliamp	2½in. flush ..	17/6
0-100 milliamp	2½in. flush ..	15/-
0-300 milliamp	2½in. flush ..	15/-
0-500 milliamp	2½in. flush ..	15/-

Unbreakable Mains Lead type of lead fitted to electric razors makes fine lead for test meters and any other devices where subject to continuous bending. Twin figure eight construction, soft cream p.v.c. covered. Normally costs 2/- per yard. Three 6-ft. leads for 2/-.

Metal Rectifier, 60/80 mA. 250/300 v., 4/6.

Filament Transformer, 6.3 v., 1½ amps. 6/6

.3 Amp Dropper—tappings marked 200/220/250, 3/6.

Output Transformer—standard pentode—4/6, multi ratio, 6/6.

Bi-metal Strip with heavy duty contact—ideal for thermostat, fire, lamp, etc., 2/6.

Neon Lamp—midget wire ended, ideal mains tester, etc., 2/-, ex Govt., 1/6.

Philips Trimmers—0-30pF, 1/- each, 9/- doz.

Set of 8 Allen Keys, 3/6.

Heavy Duty Test Prods—red and black with plug-in lead attachments, 8/6.

Install those extra points, 3.029 twin flat T.R.S. cable. Big purchase enables us to sell this at 45/- per 100 yds., carriage 3/6.

Low Resistance Head Phones. Ideal crystal sets, etc., 7/6, plus 2/6.

Goodmans Multi Ratio Output Transformer. 6 watt, 8 ratios, from 12-1 to 72-1. Centre tapped for push/pull, 7/6, plus 1/-.

Ditto, unbranded, 6/6, post 1/-.

Cold Cathode Valve CV413. Voltage regulator or trigger switch—unused but ex-equipment. 2/- each.

Tag Panels. Ideal for constructors, experimental circuits, etc., 3 of each of 12 different types. 5/-, post 1/6.

Slydlok Panel Mounting Fuses with carrier, 5 amp. 2/- each, 15 amp. 2/6 each. Belling Lee 2BA fully insulated terminals for mounting through metal panels. 2/- each.

Terminal Heads, insulated 4BA, 2/- doz.

.1 mFd. 350 v. Small tubular metal cased condensers made by Dubilier 2/6 doz.

50 Assorted Resistors. Well mixed and useful values ¼ and ½ watt, 5/- for 50.

Ditto, but 1 watt, 6/6 for 50.

Mains Transformer. Standard 230 v. input 250-0-250 at 80 mA., 6.3 v. at 5 A., 12/6, post 1/6.

Toggle Switch. Standard metal body, type with round dolly, fixing ring and on/off indicating plate. 1/3 or 12/- doz.

Metal Rectifier. 250 v. 60-80 milliamps., ideal for mains set or instrument or to replace that expensive valve, 5/6.

Screened Cable. Rubber covered flexible with metal braiding, ideal for microphone or gramophone extensions, 4d. per yd., 30/- per 100 yds.

Install 2-Way Switches. Our outfit comprises: 30 yd. multicore cable, two 2-way switches, two wood blocks. Full instructions, 9/6 each, post and insurance, 2/6.

Long, Medium and Short Wave Coil Pack. An exceptionally well made coil pack which covers the standard long, medium and short wavebands for 465 k/c I.F. complete with diagram of connections, 19/6, plus 1/6 postage and insurance—limited quantity only.

For the Record Enthusiast

New-four speed playing deck by E.M.I. has the following features:—

Velocity operated auto trip.

Pick-up on switch, cannot be damaged.

Remarkably low rumble achieved by single ball thrust and magnetic screen on motor.

Anti-microphony mounting.

The ideal unit to renovate old equipment or to build into new.

Size: 11¾in. wide, 1¾in. deep, 2¾in. high, depth 2¼in.

Mains model with stereo cartridge, £7/17/6. Or with monaural cartridge, £6/18/6, post and ins. 3/6.

H.P. Terms on request.

Cine Cameras

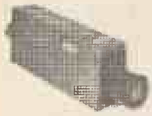

16 mm. motorised (24 VAC) for 16 frames per second, contains fine f/8.5 triple anastigmatic lens and spool to carry 25ft. of film—probable cost around £150, brand new and in sealed carton **£6/10/-** or **20/-** deposit and 13 fortnightly payments of **10/-**, post and insurance 3/6.

> **SUPER SENSITIVE (2,000 O.P.V.) MULTIMETER KIT**
> 17 ranges including D.C. volts to 1,000 V. A.V. volts to 1,000 V. D.C., milliamps to 500 ohms, to 2 meg. All the essential parts, including metal case, selected resistors, wire for shunts, selected switches, calibrated scale and instructions, **32/6**, plus 2/6 post and insurance.

Charging Switchboard

Offered at about one-twentieth of original cost. This is an ex-Government switchboard. It contains three reverse current relays, one voltmeter, one main ammeter, two secondary ammeters and three variable resistors for controlling circuits. These are original cases. Price **£2/15/-**. Carr. 10/-.

Band III Converters

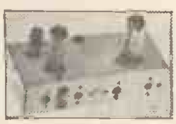

Suitable Wales, London, Midland, North, Scotland, etc. All the parts including 2 EF80 valves, coils, fine tuner, contrast control, condensers and resistors. (Metal case available as an extra). Price only **19/6**, plus 2/6 post and insurance. Data free with parts or available separately, 1/6.

Please send two more kits, the one you sent last week is performing magnificently. We receive this sort of letter every day of the week, so if you have hesitated because you thought our kits too cheap you need hesitate no longer.

Beginner's Superhet

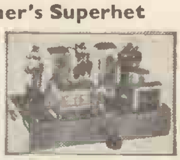

As supplied to many schools and colleges. A simple basic superhet—easy to understand and which can be progressively extended—ideal for students—components include—valves—metal rectifier tuning condenser—I.F. transformers, etc. In fact complete superhet except speaker. Price **£3** plus 3/- post and insurance. Data included free or sep., 1/6.

Avo Prodclips

The advantage of these test prods is that by pressing the trigger at the side they become crocodile clips and can be left in circuit. This is a great time saver when servicing. Price **15/-** pair.

Philips AG2009 Transcription Unit

Philips AG2009 Record Player a modestly priced 4-speed unit with many outstanding features, is ideal for the enthusiast who is assembling his own equipment or modernising an older installation. The pick-up arm is wired for stereo and the Philips stereo head is available as an optional extra. Eddy Current Brake gives ±2% fine adjustment on all four speeds. Continuously variable pick-up playing weight (2-12 gms.).

Supplied with Philips Hi-Fi crystal head, type AG3019 for microgroove and 78 r.p.m.

Frequency response 30-15,000 c/s.

Pick-up lifting and lowering device.

Individually balanced heavy turntable.

Muting switch fitted.

Can be used with any amplifier or radio set.

Complete with monaural pick-up, **£10/10/-**, or **£1** deposit and 21 fortnightly payments of **10/-**.

Available also with stereo head, diamond or sapphire stylus. Prices on request.

£100 WORTH OF EQUIPMENT 19/6

The famous R1154—unused but slightly soiled and not tested. Covers 200-500 kc/s. 3-5.5 Mc/s. and 5.5-10 Mc/s. Has unique "click stop" mechanism (7 stops) and permits selected frequency to be held, returned to, etc. Hartley oscillator, power amplifier, keying and speech. Wonderful breakdown value—meters, relays, switches. Complete with valves—real bargain at **19/6**, plus 10/- carriage.

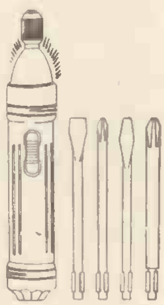

For Your Service Department

An invaluable tool for working inside a dark cabinet or cupboard. This is a screwdriver with torch and has four interchangeable bits, two for the ordinary slotted screws and two for Philips heads. The torch section operates from 1½ v. batteries in the handle and will save its cost in frayed tempers alone. Why not treat yourself to one of these now? Only **10/6**, plus 1/6 post and packing.

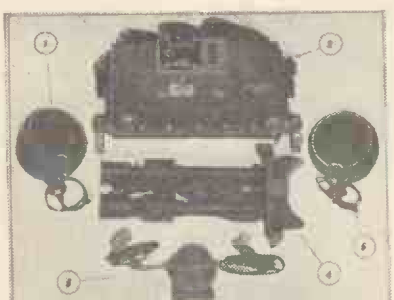

TABBY EQUIPMENT COMPLETE

Complete equipment for seeing in the dark, as fitted to Army vehicles for night driving, etc. Complete working equipment comprises: 2 Infra Red Radiators, adjustable binoculars, powerpack for 6 or 12 volts, control units and interconnection cables. Original cost, probably around £100. Unused and in perfect order—**£6/19/6** or **10/-** deposit and 15 fortnightly payments of **10/-**.

A.C./D.C. Multimeter Kit

Ranges: D.C. volts 0-5, 0-50, 0-100, 0-500, 0-1,000. A.C. volts 0-5, 0-50, 0-100, 0-500, 0-1,000. D.C. milliamps 0-5, 0-100, 0-500. Ohms 0-50,000 with internal batteries. 0-500,000 with external batteries. Measures A.C./D.C. volts. D.C. current and ohms. All the essential parts including metal case, 2in. moving coil meter, selected resistors, wire for shunts, range selector, switches, calibrated scale and full instructions, price **19/6**, plus 2/6 post and insurance.

Crystal Mike by Acos

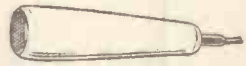

Model 39/1, this is ideal for tape or general amplifiers, complete with screened lead, **39/6**, plus 1/- post.

Radio Stethoscope

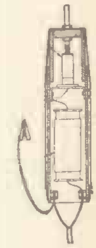

This can be slipped into the pocket rather like a fountain pen. With it in most districts a receiver can be checked from the grid of the first valve right through to the output without a signal generator, the stethoscope will operate in both L.F. and R.F circuits without alteration. It is a complete faultfinder.

All the necessary parts to make this tracer, **6/6**, post 1/-.

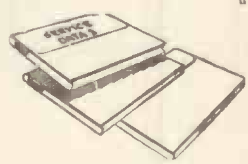

T.V. Service Sheets

200 sheets covering most popular post-war televisors by leading makers—Cossor, Ekco, Ferguson, Pye, etc., **£2** post free. PREVIOUS PURCHASERS OF THESE SHEETS PLEASE NOTE: WE CAN SUPPLY SHEETS Nos. 100-200, **£1**, or 150-200, **10/-**.

Tube Tester and Re-Activator

We can supply all the main components for making this unit which will not only test Cathode Ray Tubes but also will re-activate them, supplied complete with full instructions. Price **£3**, plus 2/6 post and ins.

Hi-Fi Snip

Infinite Wall Baffle

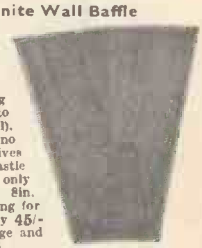

Nicely veneered and polished. Corner fitting (attaches to picture rail). Takes up no floor space. Gives really fantastic results with only low-priced 8in. speaker. Fitting for tweeter. Only **45/-** each. Carriage and insurance 3/6.

If ordering by post, address your order to the Company nearest to you. *Please include postage.*

Electronics (Croydon) Ltd.,
266 London Road,
Croydon.
Phone: CRO 6558.
Half day, Wednesday.

Electronics (Finsbury Park) Ltd.,
29 Stroud Green Road,
Finsbury Park, N.4.
Phone: ARChway 1049.
Half day, Thursday.

Electronics (Manor Park) Ltd.,
520 High Street North,
Manor Park, E.12.

Electronics (Ruislip) Ltd.,
42-46 Windmill Hill,
Ruislip, Middx.
Phone: RUISLIP 5780.
Half day, Wednesday.

ADDS A NEW DIMENSION TO SOUND

The Binson "Echorec", distributed by Modern Electrics, is a device for superimposing controlled echo on to any audio signal. It achieves within the size of a compact, fully portable instrument, effects normally requiring large echo chambers and associated equipment. Three working channels are provided for, the echo interval is variable, and swell and other effects are obtainable. The unit is of particular value in recording, for P.A., etc. Its characteristics will also no doubt lend themselves to other original applications.

THE BINSON "ECHOREC"

ABRIDGED DESCRIPTION

- Three inputs and outputs.
- Push-button channel selection for 1, 2 or 3 channels.
- Controls for echo intervals, volume of echo, swell effect, volume level on input channels, etc.
- Complete with fitted carrying case, leads, plugs.
- A.C. mains operated.

140 gns. *Leaflet on request. Trade enquiries invited.*

and of course, the best of Britain's Hi-Fi

We send tape-recorders by leading makers, and the best-known high fidelity equipment for all types all over the world. Our experience in exporting for individual requirements is second to none. Space prevents our publishing our usual detailed selections this month but your enquiries are invited without obligation. Prompt and careful attention given to all enquiries and orders.

MODERN ELECTRICS, (RETAIL) LTD.

We carry extensive and up-to-date stocks of equipment, components and accessories by Britain's leading makers. Enquiries dealt with by return.

164 CHARING CROSS ROAD, LONDON, W.C.2

(3 shops from Tottenham Court Road Station Underground)

Tel.: TEM 7587 & COV 1703 Cables: MODCHAREX, LONDON

---

15 Kc/s AT 3¾"/SEC.

TYPE DR HEAD. Illustrated actual size is 7/16in. square by 5/8in. long, curved front 1¼in. radius. Head available as medium impedance 120 mH (parallel connection) or high impedance 450 mH (series connection).
This novel design of head possesses many advantages over larger types—higher output—lower losses—extremely good treble response*—very low noise and hum pickup.

AN ERASE HEAD of the same dimensions also is available, our type "DR" double field erase head.
This is not simply a double gap, but effectively two heads side by side giving complete erasure of any signal with modest power consumption. The power required is approximately 0.5 watt at 50 Kc/s.

Both the above heads are used on many of the leading tape recorders on the market today.
.0001in. gap available to special order, this extends treble response up to 15 Kc/s at 3¾in. per sec.

HEAD TYPE DR

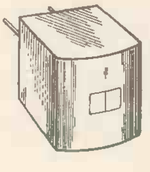

ENQUIRIES INVITED FOR QUANTITY QUOTATIONS. SEND FOR DETAILS TO

P. A. MARRIOTT & CO.

SUNLEIGH WORKS, SUNLEIGH ROAD
ALPERTON, MIDDLESEX
Phone : Wembley 7493

ATTENTION:

OWNERS OF TAPE RECORDERS

Here is an opportunity to learn foreign languages with your tape recorder. Full elementary courses in Italian, Spanish, German, French and Russian. Full recorded tape together with instruction book **29/6.**

Trade enquiries invited

Please apply for explanatory leaflets to your nearest retailer or direct from

FISHER ELECTRONICS CO. LTD.,
NATIONAL HOUSE,
WARDOUR STREET, LONDON, W.1.
Telephone : REG 7597

Garrard

are making under licence the famous AMERICAN

INTERNATIONAL T.R. SERIES WHICH ARE ALREADY BEING USED IN VAST QUANTITIES IN AMERICA AND OTHER COUNTRIES

I·E·R·C HEAT DISSIPATING VALVE SHIELDS

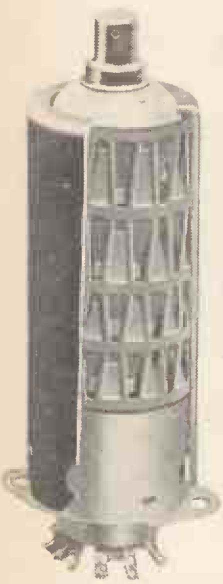

- International T.R. Series Shields reduce bare-bulb temperatures by 15% to 25%.
- International T.R. Series Shields eliminate vibration.
- International T.R. Series Shields fit standard sockets.
- International T.R. Series Shields are available in various sizes.

Full Technical information is available on request.

Joint service numbers have been allocated.

GARRARD TRADE MARK REG.

GARRARD

ENGINEERING AND MANUFACTURING CO. LTD.

Special Products Division,

23, Westminster Palace Gdns., Artillery Row, London, S.W.1

PULLER ELECTRONICS

PLESSEY SYNTHESIZER
Accuracy 1 part in 10^8 with a frequency coverage 500 cycles to 300 mc/s for signal calibration. Generates a signal of at least point one volt across 80 ohm load from 2 kc/s to 10 mc/s with an accuracy of 1 part in 10^6.

RADAR EQUIPMENT
TR8193 Rebecca Eureka.
TR3624 Rebecca Eureka.
TR3712 3CM Transmitter/Receiver (Pressurised).
S Band and X Band Echo Boxes.

SPECTRUM ANALYSER
TSX-4SE 3 cms. Klystron 2K25 Frequency range. 8702-9545mc/s.
TSK-ISE 1¼CM Spectrum Analyser.

POWER METERS
TBN-3EV. Thermistor W. Bridge.
Type 17. UHF-VHF 0–40 watts. Oil cooled.
CT-101. UHF.

VALVE VOLTMETERS
Balantine 10cy/s–150kc/s., voltage range .01–100V F.S.D. Can also be used as an amplifier with variable gain.
Cambridge Moulin Type F.S.D. 1½ volts.

KLYSTRON POWER SUPPLIES
Several types for high and low voltage klystrons, also associated selective amplifiers bridged T type.

RECEIVERS
Ferris 32A Field Strength Meter 200kc/s-20mc/s. Will measure down to 1 micro-volt.
R1294 500-300 mc/s. Local Oscillator CV52.
P58 300–600mc/s. with RF Stage.
AR–88D.

SIGNAL GENERATORS
Type 13/TF-948 CW/AM/FM/Pulse freq. 20-80mc/s.
C.T.–53 freq. 8–300 mc/s.
LAE1 CW/Pulse freq. 503–1330mc/s. Lab. Signal generator.
TTX–10–RH 3CM FM Test Set.

Service Facilities for Most Types of Electronic Equipment

PULLER ELECTRONICS
1A, WHITEHALL PARK, LONDON, N.19
ARChway 1678

TRANSFORMERS COILS CHOKES

LARGE OR SMALL QUANTITIES
TRADE ENQUIRIES WELCOMED

SPECIALISTS IN

FINE WIRE WINDINGS

MINIATURE TRANSFORMERS, PICK-UP, CLOCK AND INSTRUMENT COILS, ETC.
VACUUM IMPREGNATION TO APPROVED STANDARDS

ELECTRO-WINDS LTD.

CONTRACTORS TO G.P.O., M.O.S., L.E.B., ETC.

123-5-7 PARCHMORE ROAD, THORNTON HEATH, SURREY
LIVINGSTONE 2261 EST. 1933

TRANSISTORISED POWER AMPLIFIERS

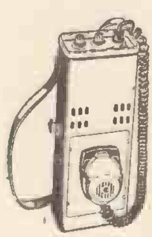

PORTABLE, MOBILE, MAINS

FOR ALL RADIO, AMPLIFIER & SOUND INSTALLATIONS

ENQUIRIES:—

Audix

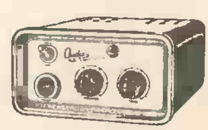

STANSTED, ESSEX. *STANSTED 3132*

SERVO SYSTEMS DEMONSTRATION UNIT

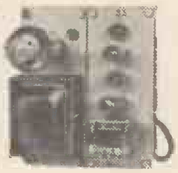


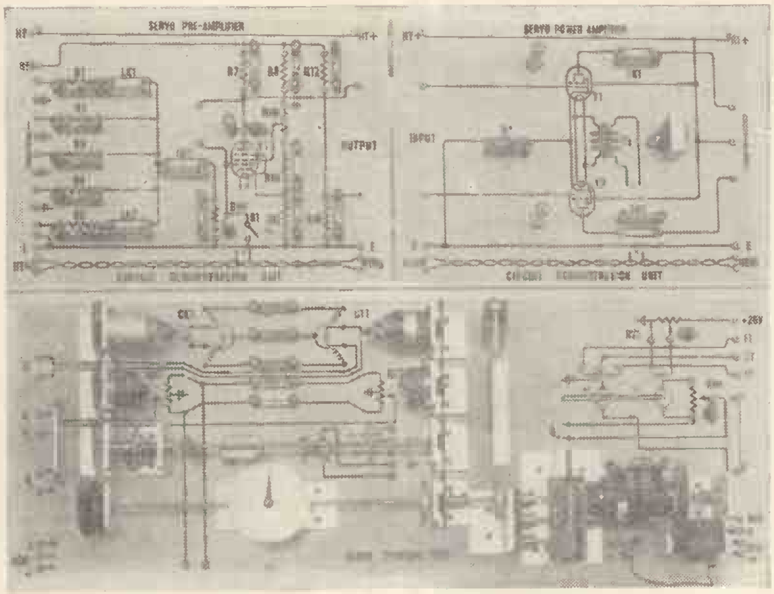
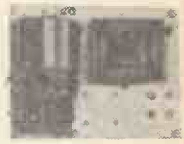

A new addition to the comprehensive range of training equipment produced by PHILCO whose products have been adopted by training establishments throughout the world.

This versatile set can be used at all levels of instruction in servo mechanisms for both qualitative and quantitative approaches to the subject, ranging from simple discontinuous systems through proportional and speed control to analoque computing functions. All the servo components characteristics, even to backlash and shaft whip, may be varied and their effects studied.

The system is self contained, HT, regulated HT, LT, 26v DC and 400 c/s supplies are provided so that only a mains connection is required. Many accessories are available including a low cost pen recorder specially designed for instructional use.

Write for full details of this and other items in the range (from components to microwave training aids) to:–

PHILCO

Electronic Training Equipment

PHILCO INTERNATIONAL LTD.,
135, SOUTH STREET,
BISHOP'S STORTFORD,
HERTS.,
Telephone: Bishop's Stortford 971.

- Up to 8 changeovers, 15 amp at 250V a.c.
- Light duty twin contacts can be incorporated.
- P.T.F.E. insulators on moving parts.
- Designed to withstand severe shock and vibration.
- Full tropical finish.
- **Prototypes available in 24 hours.**
- **Bulk deliveries commencing within 14 days.**

Manufacturers of the full range of Post Office Types 3000 and 600 relays.

L. E. SIMMONDS LTD
BYRON ROAD, HARROW, MIDDLESEX
TEL: HARROW 7797 P.B.X. TELEGRAPHIC ADDRESS: SIMRELAY HARROW

VITREOUS ENAMELLED RESISTORS

R.C.S.C. Style RWV4-L

FULLY R.C.S.C. TYPE APPROVED, 10Ω to 22KΩ, our RWV4-L style resistors conform to Inter-Services Spec. RCS III.

Other styles available. R.C.S.C. type approval applied for.

RCSC Style	CGS Style	Rating in watts: Service	Rating in watts: Commercial	Range
RWV4-J	VPF4	3	4	5Ω to 8KΩ
RWV4-K	VPF10	4.5	10	5Ω to 68KΩ
RWV4-L	VPF14	6	14	10Ω to 100KΩ

THE C.G.S. RESISTANCE CO.
EVERTON, LYMINGTON, HANTS. Tel. Milford-on-Sea 269
London Office: 30 Clarendon Rd., Harrow, Mddx. Tel. Harrow 4147

***STABILIZE** YOUR AC MAINS* with the finest equipment, *at a fraction of the normal cost:—*

FERRANTI $7\frac{1}{2}$-KVA MOVING COIL AUTOMATIC VOLTAGE REGULATORS

Any stabilized output voltage in the range 200-250 v. can be selected by plug-board tappings. The selected output voltage is automatically maintained constant within $\pm\frac{1}{2}$%, at all loads 0 to 30/$37\frac{1}{2}$ amps., when the supply voltage is varying over the range +8% to −12%.

- Frequency compensated 45-55 and 54-66 c/s.
- Excellent output wave-form.
- Can also be used as a variable transformer.
- **Unused.** Complete with spares and instruction book.

P. B. CRAWSHAY
94 Pixmore Way, Letchworth, Herts. 'Phone 1851

For Safety's Sake use AVO Prodclips

Patent No. 748811

Safety first every time with these patented spring-loaded AVO Prodclips.

Cleverly designed for use as insulated prods, they are invaluable for reaching and holding test points which are difficult of access.

Suitable for use with AvoMeter, Multiminor and Avo Electronic Test Meter Leads.

Order supplies from your usual wholesaler now! Post Free **15/-** per pair

AVO LTD **AVOCET HOUSE · 92-96 VAUXHALL BRIDGE ROAD, LONDON, S.W.1.**
VICtoria 3404 (12 lines).
A MEMBER OF THE METAL INDUSTRIES GROUP OF COMPANIES

G.W. SMITH & CO (RADIO) LIMITED

Phone: GERRARD 8204/9155
Cables: SMITHEX LESQUARE
3-34 LISLE STREET, LONDON, W.C.2

UNIVERSAL AVOMETER MODEL "D"

D.C. VOLTS	A.C. VOLTS	D.C. Current	A.C. Current
150 mv.	7.5 v.	15 ma.	75 ma.
300 mv.	15 v.	30 ma.	150 ma.
1.5 v.	75 v.	150 ma.	750 ma.
3 v.	150 v.	300 ma.	1.5 amp.
15 v.	300 v.	1.5 amp.	7.5 amp.
30 v.	600 v.	3 amp.	15 amp.
150 v.	750 v.	15 amp.	Resistance
300 v.	1,500 v.	30 amp.	1,000Ω
750 v.			10,000Ω
1,500 v.			

Supplied reconditioned as new, with internal battery, instructions and leads £8/19/6 each. P/P. 3/6.

WESTON MODEL 772 TESTMETER

A.C. VOLTS	D.C. CURRENT	A.C. CURRENT
2.5 v.	100 micro/a.	500 ma.
10 v.	1 ma.	1 amp.
50 v.	10 ma.	5 amp.
250 v.	50 ma.	RESISTANCE
1,000 v.	100 ma.	100 ohms
D.C. VOLTS	500 ma.	1,000 ohms
2.5 v.	OUTPUT METER	100k. ohms
10 v.		10 megohms
50 v.		
250 v.		
1,000 v.		

Supplied in perfect working order complete with internal batteries. £7/10/-. P/P. 4/-.

FIELD TELEPHONES TYPE F. Generator bell ringing. Supplied complete with batteries, fully tested, and complete with wooden carrying case. 59/6 each. P/P. 3/6.

24 AMP. VARIAC TRANSFORMERS. 230 v. input. Variable output 185-250 volts or 185-250 volts input, 230 volts out. £12 10/- each. P/P. 10/-.

MUIRHEAD PRECISION STUD SWITCHES. 4 bank, 4 pole, 24 positions. New, boxed, 17/6 each. P/P. 1/3.

AR 88. 1st I.F. Transformers 3/6. P/P. 1/-.

2 v. 3AH. ACCUMULATORS. Lead Acid, unfilled. 12 for 21/-. P/P. 4/6.

E.M.I. POTTED MIC. INPUT TRANSFORMERS. High quality, 50 : 1 ratio, 4/6 each. P/P. 9d.

LEACH 12 VOLT AERIAL CHANGE-OVER RELAYS. Double pole, 7/6 each. P/P. 9d.

AMERICAN H.T. BATTERIES. Tapped 90 v., 67½ v., 45 v., 22½ v. New, 5/- each. P/P. 2/-.

8 RANGE SUB-STANDARD D.C. AMMETERS. Ranges, 1.5 3, 7, 15, 30, 60, 300 and 450 amps. 8in. mirror scale. Meter housed in polished teak case. Supplied complete with all shunts and leather carrying case. £15 each. P/P. 7/6.

1,000 WATT MAINS ISOLATION TRANSFORMERS. 230 to 230 volts. Heavy duty, ex-Admiralty. New boxed, £5 each. P/P. 10/-.

750 WATT AUTO TRANSFORMERS. Tapped from 110 to 230 volts. Fine heavy duty type, 69/6 each. P/P. 5/-.

DEAF-AID EAR-PIECES. 250 ohm imp. 4/6; 1,000 ohm imp. 7/6. P/P. 6d.

R.C.A. PLATE TRANSFORMERS. Input 200/250 volts 50 cycles. Output 2,000/1,500/0/1,500/2,000 volts 500 m/a. Supplied brand new in transit cases, £6/10/- each. P/P. 10/-.

R.1155 RECEIVERS MODEL B. Perfect working order, fully tested, £7/19/6 each. P/P. 7/6. Combined power pack and output stage, 85/- extra.

AR.88 WAVE CHANGE SWITCH ASSEMBLY. Brand new with screens. 17/6 each. P.P. 2/6.

R.1155 N TYPE DRIVES. Improved geared version new, 12/6 each. P/P. 1/6.

POST OFFICE TELEPHONE HANDSETS. Std. type, new boxed, 12/6 each. P/P. 1/6.

METER BARGAINS

25 microamp D.C. M/C flush rd. 2½in.	69/6
25 microamp. D.C. M/C. proj. rd. 2½in.	59/6
50/0/50 microamp D.C. M/C., flush rd. 3½in.	79/6
50 microamp. D.C. M/C. proj. rd. 2½in.	49/6
100 microamp. D.C. M/C. flush rd. 3½in.	62/6
500/0/500 microamp. D.C. M/C. proj. rd. 2½in.	19/6
1 milliamp. D.C. M/C. flush sq. 2in.	22 6
1 milliamp. D.C. M/C. flush rd. 2½in.	25/-
1 milliamp. D.C. M/C. flush rd. 3½in.	50/-
1 milliamp. D.C. M/C., flush sq. 4in.	69/6
200 milliamp D.C. M/C. flush rd. 2½in.	9/6
30 amp. D.C. M/C. flush rd. 2½in.	9/6
15 volt D.C. M/C. flush rd. 1½in.	10/6
120 volt D.C. M/C. flush rd. 3½in.	32/6
300 volt A.C. M/I. flush rd. 2½in.	25/-
300 volt A.C. M/C. rect. flush rd. 2½in.	25/-
500 volt A.C. M/I. flush rd. 2½in.	25/-

CR.100 SPARES KIT. Contains 15 valves, resistors, pots, condensers, output trans., etc. All brand new, 59/6. P/P. 3/6.

DYNAMO EXPLODER UNITS. For detonating explosive charges. Hand generator operation. Brand new 29/6 each. P/P. 3/6. Hide leather cases 19/6 extra.

MARCONI TF.428 B/I VALVE VOLTMETERS. 5 ranges A.C. and D.C. 1.5, 5, 15, 50 and 150 volts. Operation 200/250 volts A.C. Supplied brand new complete with internal HF probe. £17/10/- each. P/P. 10/-.

EX-ADMIRALTY 12 VOLT D.C. MOBILE AMPLIFIERS. Std. mic. or gram. input. Push pull 10 watt, output matched to 3 or 15 ohms. Good working order. £8/19/6 each. P/P. 6/6.

MARCONI TF-373 IMPEDANCE BRIDGE. Reconditioned to maker's specification. 1,000 c/s. Ranges: 100 henry; 100 mfd.; 1 megohm; 100 Q. 200/250 volts A.C. operation. £35 each.

CRYSTAL MICROPHONE INSERTS, 4/6 each. P/P. 6d.

MARCONI STANDARD SIGNAL GENERATOR TF-144G. 85 Kc/s. to 25 Mc/s. Output 1 microvolt to 1 volt. 200/250 volts A.C. operation. Reconditioned to maker's specification. £55 each.

UNIVERSAL AVO METERS MODEL 7. Reconditioned perfect order, £12/19/6 each. P/P. 3/6.

FURZEHILL BEAT FREQUENCY AUDIO OSCILLATORS. Frequency range 0-10,000 c.p.s. Output 10 or 600 ohms. Separate 50 c.p.s. check. Set zero control. 200/250 volt A.C. operation. Supplied in perfect working order. £9/19/6 each. P/P. 10/-.

CV.967 1 IN. CR. TUBES. 4 volt heater suitable for 'scope, new. 19/6 each. P/P. 1/6.

230 VOLT A.C. MOTORS. Ideal for fan or blower. 15/6 each. P/P. 1/3.

R.1294 V.H.F. COMMUNICATION RECEIVERS. 500 to 3,000 mc/s. Perfect condition with handbook. £25. P/P. 10/-.

MARCONI TF-329 "Q" METERS. Range 0 to 500 Q. Frequency 50 kc/s. to 50 mc/s. Re-conditioned to maker's specification. 200,250 volts A.C. operation. £65 each.

GRESHAM POTTED L.T. TRANSFORMERS. 230 volts input. Secondary tapped 70, 75 and 80 volts 4 amps. New boxed, 42/6 each. P/P. 3/6.

FERRANTI FILAMENT TRANSFORMERS. Two types, both 200/250 volt input. Type 1: 6.3 volt CT. 5.6 amp., 6.3 volt CT. 4.8 amp., 6.3 volt CT., 1 amp., 19/6. Type 2: 6.3 volt CT. 3.3 amp., 6.3 volt CT. 1 amp., 6.3 volt CT. .9 amp., 6.3 volt CT. .6 amp. 15/6. P/P. 2/-., both types.

G.E.C. SELECTEST MULTI-RANGE TESTMETERS

D.C. Volts.	A.C. Volts.	D.C. Current	A.C. Current
150 mv.	7.5 v.	15 ma.	75 ma.
300 mv.	15 v.	30 ma.	150 ma.
1.5 v.	75 v.	150 ma.	750 ma.
3 v.	150 v.	300 ma.	1.5 amp.
15 v.	300 v.	1.5 amp.	7.5 amp.
30 v.	600 v.	3 amp.	15 amp.
150 v.	750 v.	15 amp.	Resistance
300 v.	1,500 v.	30 amp.	1 K. ohm
750 v.			10 K. ohm
1,500 v.			

Incorporated overload trip and special safety interlocking switches. Supplied in perfect condition with leads and battery at £7/10/- each. P/P. 3/6.

AMERICAN MULTI-RANGE TESTMETERS

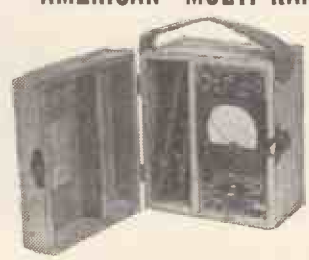

1,000 ohms per volt, 400 microamp basic movement.

A.C. VOLTS	D.C. VOLTS
2.5 v.	2.5 v.
10 v.	10 v.
50 v.	50 v.
250 v.	250 v.
1,000 v.	1,000 v.
5,000 v.	5,000 v.
D.C. CURRENT	RESIST'CE
1 ma.	500 ohms
10 ma.	100 k. ohms
100 ma.	1 megohm
1 amp.	DECIBELS
	−10 to +69

ALL BRAND NEW. COMPLETE WITH INTERNAL BATTERY, TEST PRODS AND INSTRUCTIONS. £3/19/6 EACH. P/P. 3/-.

UNREPEATABLE OFFER
DUE TO LARGE PURCHASE FROM GOVERNMENT
COSSOR 339 DOUBLE BEAM OSCILLOSCOPES
PERFECT WORKING CONDITION WITH HANDBOOK
ONLY **£15** EACH
Carriage 10/- extra.

PORTABLE PRECISION VOLTMETERS
Brand new and boxed instruments by famous manufacturer. Housed in polished teak case. Moving iron movement reading A.C. or D.C. volts on 2 ranges, 0-160 v. and 0-320 v. 8in. mirror scale. Accuracy within 2%. Supplied at a fraction of original cost. Only £5/19/6 each. P/P. 3/6.

MARCONI TYPE TF-340 OUTPUT POWER METERS. Meter calibration 50 MW/17DB F.S.D. Meter multipliers, 0.1-1-10-100. Impedance values, 25-30-40-50-60-80-100-125-150-200 ohms. Impedance multipliers. 0.1-1-10-100. Perfect condition. £9/19/6 each. 7/6 carriage.

SURPLUS HEADPHONES. R.C.A. chamois padded, moving coil, fitted jack plug, 19/6 pr. P/P. 1/6. AMERICAN HS.30 super light weight, 50 ohms. 15/- pr. P/P. 1/6. 4,000 ohms light duty, 12/6. P/P. 1/6.

DON MK. V FIELD TELEPHONES. Ideal for all inter-communication. Buzzer calling. Supplied fully tested complete with batteries and instructions. 39/6 each. P/P. 3/6 each.

PARMEKO TABLE TOP TRANSFORMERS. Input 230 volts. Output 620/550/375/0/375/550/620 volts 250 m/a. Also 2-5 volt 3 amp. windings. Size 6¾ x 6¼ x 5½in. New, boxed at 45/- each. P/P. 5/-.

24 VOLT ROTARY CONVERTERS. Input 24 volt D.C. Output 230 volts A.C. 50 cycles, 100 watts. Housed in metal case with inlet/outlet plugs. Brand new. 92/6 each. P/P. 7/6.

VORTEXION PORTABLE AMPLIFIERS Operation from 200/250 volts A.C. or 12 volts D.C. Separate inputs for microphone or gram. Push-pull 10 watt output matched to 7.5 15, 250 or 500 ohms. Incorporate volume control and full switch tone control. Not brand new but good working order, 10 guineas each. P/P. 6/-.

CRYSTAL CALIBRATORS NO. 10. Range 500 Kc/s. to 30 Mc/s. Compact size 7 x 7½ x 4in. Utilise 2-IT4, IR5 and CV286 valves and 500 Kc/s. crystal. Supplied in perfect condition with instructional handbook. 59/6 each. P/P. 3/6.

MARCONI TF868 UNIVERSAL IMPEDANCE BRIDGES. Ranges 1pf-100 mfd. 1μh-1h, .1Ω-10 megohm, 200-250 v. A.C. Perfect as new £65 each.

PARMEKO TRANSFORMER. Input 230 volts. Output 350/0/350 volts 150 m/a. 6.3 volts 3.5 amp. 5 volts 4 amp. New, boxed, 32/6 each. P/P. 2/6.

PHOTO VOLTAGE AMPLIFIERS. These special instruments incorporate a 1 microamp mirror galvanometer and a double selenium photo-electric cell. Housed in aluminium case complete with 12 volt lamp and housing. Brand new. £9/19/6 each. P/P. 7/6.

12 VOLT ROTARY CONVERTERS. Input 12 volt D.C. Output 230 volt A.C. 150 watts, 50 cycles. Housed in wooden case and fitted with voltage control slider resistance switch, plugs and A.C mains voltage output check meter. Supplied in perfect condition fully tested, £9/19/6 each. P/P. 10/-.

MARCONI TF410c VIDEO OSCILLATORS. Ranges 20 c/s.-30,000 c/s., 30 Kc/s- 5 Mc/s. Variable attenuator 200/250 v. A.C.

AVO POWER PACKS. 230 volts input. Output 67½ volts, 6 m/a. and 1.5 volts 250 m/a. Fully smoothed. New boxed 19/6 each. P/P. 2/6.

FIELD TELEPHONES TYPE L. Generator bell ringing, light and very portable. Supplied complete with batteries. Fully tested. As new, 59/6 each. P/P. 3/-.

POST OFFICE JUMPER LEADS. 4ft., fitted with two std. jack plugs, 3/- each. P/P. 9d. Standard jack sockets 9d. each.

SOUND POWERED TELEPHONE HANDSETS. No batteries required to use. Ideal for inter-com. New boxed 15/- each. P/P. 1/6.

MINE DETECTORS No 4a
Complete equipment comprises Search Head, Amplifier Headset, Control Box, Telescopic Rods for Search Head, Search Head Test Unit and Test Depth Measure and Haversack.
Operation is from a standard 60 v./1.5 v. combined dry battery. The unit will detect ferrous or non-ferrous metals to a depth of 24in. giving maximum signal but can be used at greater depths giving lower output. Ideal for tracing underground pipes or cables and any hidden metallic objects.
Complete equipment supplied brand new in original transit cases complete with circuit and operating instructions.

PRICE
99/6 EACH
Carriage 10/6.

MARCONI TF-517 SIGNAL GENERATORS. 10-18 Mc/s., 33-58 Mc/s; 150-300 Mc/s. 200/250 volts operation, 65/- each for callers only.

6 VOLT VIBRATOR PACKS. Output 120 volts 30 m/a. Fully smoothed. New, boxed 12/6 each. P/P. 2/-.

POTTED TRANSFORMER. Primary 230 volts. Secondary 350/310/0/310/350 volts. 220 m/a. 6.3 volts 13 amp., 5 volts 3 amps. 49/6 each. P/P. 3/-.

HOOVER ROTARY TRANSFORMERS. Miniature type. 12 volt D.C. input. Output 310 volts 30 m/a. New boxed 12/6 each. P/P. 1/3.

BATTERY CHARGING OR MODEL RECTIFIERS AND TRANSFORMERS. Rectifiers. All full wave and bridged. 12/18 volt 1.5 amp., 4/3; 12/18 volt 2.5 amp 6/9; 12/18 volt 4 amp. 9/9; 12/18 volt 6 amp. 18/6; 24/30 volt 1 amp. 12/6; 24/30 volt 4 amp. 22/6; 24/30 volt 15 amp. 62/6.
Transformers. All primaries tapped 200/250 volts. 3.5, 9 or 17 volt 1 amp. 9/9; 3.5, 9 or 17 volt 2 amp. 14/3; 3.5 9 or 17 volt 4 amp. 16/6; 9 or 17 volt 6 amp. 26/-; 3, 4, 5, 6, 8, 10, 12, 15, 18, 20, 24 or 30 volt 2 amp. 18/6. Please add postage.

EDDYSTONE MAINS POWER PACKS. 200/250 volts input. Output 175 volts 60 m/a. and 12 volts 2.5 amp. Double choke and condenser smoothed, 5Z4 rectifier. Supplied new and unused only 22/6 each. P/P. 3/6.

ROTARY TRANSFORMERS. Two models either 6 or 12 volt input D.C. Output 250 volts 80 m/a. 22/6 each. P/P. 2/6.

SPECIAL OFFER OF P.V.C. RECORDING TAPE. Brand new, boxed on 7in. universal spools. 600ft. std., 12/-; 1,200ft. std. 19/6; 1,800ft. long play, 30/-. P/P. 1/-

BRAND NEW R.C.A. EXTENSION LOUDSPEAKERS
8in., 3 ohm Quality Speaker mounted in attractive black crackle case to match AR88 Receivers, etc.

45/- each. P/P. 3/6.

G.W. SMITH & CO. (RADIO) LIMITED
Phone: GERRARD 8204/9155
Cables: SMITHEX LESQUARE
3-34 LISLE STREET, LONDON, W.C.2

BENEFIT FROM WHOLESALE BUYING! GET EQUIPMENT THAT'S IN TIP-TOP CONDITION. GET IT FROM IRONGATE — ENGLAND'S LEADING EQUIPMENT WHOLESALERS

HEAVY DUTY
20 AMP. L.T. SUPPLY UNIT

by **S.T.C.**

Normal cost over £100

Essential equipment for Electronic Engineering, research laboratories, schools. Ideal for battery charging, etc. Guaranteed for 20 amps.
Output: D.C. Variable up to 20 amps. and **24V** or trickle charge 125/350/700 ampere hours.
Input: A.C. 100/260 volts 45/65 cycles.
Size: 16 × 24 × 32in. high.
In attractive Grey Cabinet.

ex-Warehouse **£22-10-0**

(Circ. diags. and instru. loaned for 10/- deposit)

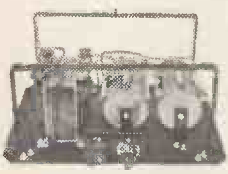

G.E.C. L.T. SUPPLY UNIT

OUTPUT: 24 volts 10 amps. D.C.
INPUT: 200 250 volts A.C.
New and in original cases
£13.10.0
Carr. 9/6

WORLD FAMOUS TELEPHONES

"F" Type
IN ATTRACTIVE CASE
The best portable telephone ever made. With a range of up to 5 miles is ideal for FACTORIES, BUILDING SITES, FARMS, CIVIL ENGINEERING PROJECTS, OUTSIDE BROADCAST UNITS AND OFFICES.

2 perfect sets in individual carrying cases, complete with long life batteries, bells, magneto and 100ft. telephone cable.
£7.10.0 per pair. Carr. 9/6

TELE "F" HIGH POWER as above, but complete with amplifier, £6/10/- each. Carr. 12/6

D3 STRANDED TELEPHONE CABLE, New Mile Drum 85/-. Carr. 17/6.

ENGLAND'S LARGEST STOCKS OF TELEPHONE EQUIPMENT

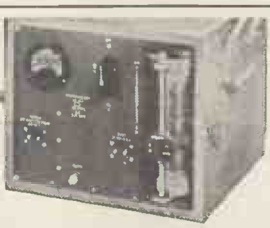

ROTARY CONVERTORS. 12 v. D.C. input. 230 volt A.C. 150 watts, 50 cycles output. Housed in wooden case and fitted with voltage control slider resistance, switch, plugs and A.C. mains voltage output check meter. Supplied in perfect condition, individually tested, **£9/19/6** each. P. & P. 10/-.

VARIAC TRANSFORMERS
Brand New

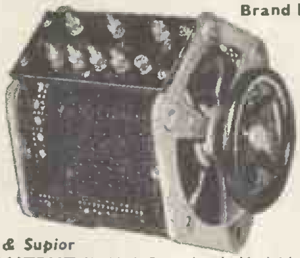

& Supior
OUTPUT (2KVA) Completely Variable 0 to 270 volts, 9 amps.
INPUT 230 Volts, 50/60~
A SHROUDED FULLY VARIABLE TRANSFORMER FOR BENCH OR PANEL MOUNTING.
SIZE:—Approximately 8½ inches Cube.
WEIGHT:—Approximately 30 lb.
PRICE: RIDICULOUS, ONLY £15.0.0
Plus 12/6 carr., supplied and boxed new.

CONSTANT VOLTAGE TRANSFORMERS

FERRANTI 7½-KVA MOVING COIL
Stabilized output voltage in the range 200-250 v. Plug-board tappings. The selected output voltage is constant with ±½% at all loads 0 to 30/37½ amps. when the supply voltage is varying over the range +8% to −12%.

- Frequency compensated 45-55 and 54-66 c/s.
- Excellent output wave-form.
- Can be used as a variable transformer.
- Unused. Complete with spares and instruction book at a fraction of the normal cost, only **£65.**

AUTO TRANSFORMERS

3 KVA Air Cooled (100% under-rated)
GUARANTEED 230/250 tapped, 12 amps.
6 KVA 105/120 tapped, 28.5 amps.
Made by well-known manufacturer and housed in strong metal case. Weight: 2 cwt. Brand new, in original maker's cases.
PRICE **£15.0.0** Carr. 25/-.

VERY SPECIAL OFFER— EXPORT ONLY

Just released by the Ministry of Supply. **"88" SETS.** Manufactured by E. K. Cole. Walkie Talkie and A.F.V.—3,000 available. **"22" SETS ALSO**—500 only.
TELEPRINTERS—120 Creed 7B for immediate disposal.
Enquiries are invited for Bulk supply at reducing low prices.

MICRO SWITCHES
BURGESS
BRAND NEW MINISTRY RELEASE
(MK. 4 BR. METAL BODY UNIVERSAL CONTACT A.M. Ref. 5C/4098)
Compare this remarkable almost half-price offer.
78/- per Doz. (min. quantity) **£25 per 100**

TRUVOX LOUD HAILERS

For public address from cars, boats, etc., similar to Police Type ex-H.M. Forces. Simply connect to a 6/12-volt. car battery and use. **Amazingly powerful.** Why pay £2 a day hire charge for amplifiers. Buy this complete unit.
only **£7.14.6**
by return
TWIN SPEAKER UNIT COMPLETE £10/14/6.

EX-GOVT.
PUBLIC ADDRESS SYSTEM

Complete with amplifier unit, 4 speakers, microphone, headphones and all spares packed in wooden cases. 6 or 12 volt D.C. handling capacity 8 watts. Ideal for cars, boats, factories, etc.
£15.15.0 Carr. 30/-.

AERIAL MASTS

IMPROVED TYPE 50 MK II
36 ft. HIGH

Kits comprise—6 2¼in. dia. Tubular Steel Sections of 6ft. length, top-section and base, Pickets, Guys and Fittings. **YOU** can purchase this normally expensive **MAST** for a fraction of its cost. Please add £1 for (returnable) wooden carrying case. The **MAST** is particularly suitable to take aerials for Tx., Rx., F.M. and T.V. (especially COMMERCIAL) and has many other uses. Extra 6ft. sections can be supplied at **17/6** per section.

£8.10.0 only Carr. 15/6

U.S.A. Type 45ft. TELECOM. AERIAL MAST. (7 sections, 6ft. 8in. × 2¼in., guys, etc.). This entirely complete set in carrying case 12½ Gns. Carr. 17/6. Or 2 sets for **£25.** Carr. extra. *British Manufacture only.*

ARMY TYPE 32ft. MASTS similar to above but 10 1in. screw-sections, suitable for permanent lightweight installation. Kit in canvas bag, £5/10/-. Carriage 12/6.

U.S.A. R-9B/APN-4 Radio Receivers.

First class for conversion, originally designed for R.D.F. Valve: 1-6SN7GT, 4-6SK7GT, 1-6SA7 GT, 1-VR105-30, 1-5U4G, 1-6H6-GT, 1-6SL7GT, 3-6B4G, 2-879 2-2, 1-6SJ7GT.
85/- P. & P. 12/6
Chassis size 20 × 9 × 11in. Weight 26lb. Brand new.
Components value (transformers, condensers, switchgear, etc.) far exceeds this remarkable low price. Buy now. Only 150 sets available.

THE IRONGATE (M.O.) CO., Dept. (WW4)
2/4 IRONGATE WHARF ROAD, PRAED STREET, LONDON, W.2. PAD 2231/2/3.

LASKY'S RADIO

FINEST RANGE OF GRAM AMPLIFIERS IN GT. BRITAIN

We have the type you need. Come and see our range or write for special Amplifier List. Two examples:—

3-WATT GRAM AMPLIFIER
2 valve, ECL 82 and EZ80 rectifier, double wound mains transformer 100-250 A.C., tone control, record equalisation switch. Size 7¾ × 3½in. max. height 4½in. Controls mounted separately. **LASKY'S PRICE** complete with knobs. **55/-** Post 3/6

MATCHED PAIR FOR STEREO...... 5 Gns. Post 5/-

2-WATT GRAM AMPLIFIER, uses ECL83, contact cooled rectifier.
LASKY'S PRICE 35/- Post 2/6

The VERDIK "Quality 10" Hi-Fi Amplifier

10 watt p.p., ultralinear, complete with Pre-Amplifier. 5 inputs, bass and treble controls, grey enamel finish. List £21.
LASKY'S PRICE £14.19.6 Carr. 7/6.

"LINEAR" AMPLIFIERS

"DIATONIC" 10-14 watt 12 Gns.
"CONCHORD" 30 watt 15 Gns.
L45 4-5 watt Amplifier £5/19/6
LT45 Tape Deck Amplifier 12 Gns.
L50 50 watt Amplifier 19 Gns.
L10 10-12 watt with pre-amplifier 15 Gns.
L3/3 Stereo Amplifier 7 Gns.

MULLARD 510 KIT

All specified components and your choice of transformers and chokes by Partridge, Haddon, W/B, Ellison or Gilson.
COMPLETE KIT and printed circuit as low as **£9.9.0**
Details on request.
Printed Circuit separately 22/6.
Also available built ready for use. Price according to transformers.

BUILD THE 3-3 AMPLIFIER

Complete kit of parts with 3 Mullard valves EL84, EF86 and EZ81, **£6.19.6** Post free.
All components available separately.

BARGAINS IN 4-SPEED MIXER AUTO-CHANGERS

B.S.R. 4-spd. mixer Auto-Changer type UA8, complete with latest B.S.R. "ful-fi."
Carr. & Pkg. 5/-. **£6.19.6**
Ditto, wired for Stereo and with Stereo cartridge, £7/19/6.

COLLARO. Incorporating auto and manual control. Complete with Studio crystal p.u. and sapphire stylus. LIST £13/17/-.
LASKY'S PRICE £7.19.6 Post 3/6

B.S.R. Latest Type UA12

4-spd. Wired for STEREO, complete with stereo cartridge. Post 5/-. **£8.19.6**

GARRARD 4-SPEED MIXER AUTO-CHANGERS

Model 121. Mk. II......	£10/19/6
121, Mk. II STEREO	£11/19/6
121, Mk. II, with monaural and Stereo heads	£12/10/0
RC.88..................	£12/19/6
RC.88, STEREO	£13/19/6

All the above Auto-Changers are new and unused in maker's cartons.

SINGLE PLAYERS

COLLARO Junior 4-spd. Motor 55/-
Collaro Pick-up for above 27/6
Motor & Pick-up together 75/-
Post free.
COLLARO 4/564 £6/9/6 Post 5/-
GARRARD 4SP., £6/9/6, Post 5/-

SINGLE STEREO PLAYER

E.M.I. 4-spd., wired for Stereo and fitted with Acos stereo t.o. cartridge.
LASKY'S PRICE £6.19.6 Post 5/-

COSSOR 554 TRANSISTOR RECORD PLAYER

Battery operated, using two 4½ v. AD28 batteries. Incorporates latest Garrard BA1 Turntable and Pick-up, fully-transistorised Amplifier, and high quality 7×4in. elliptical Speaker. Suitable for 7in. 45 r.p.m. records. Attractive two-tone Carrying Case, 11×8¾×5in.
LASKY'S PRICE £9.19.6 Post 4/-.
Batteries extra, 3/3 each.

STEREO CARTRIDGES

ACOS type 73-1A turnover, list 52/6.
LASKY'S PRICE 29/6 Post 1/-.
All makes and types in stock. Write for our bargain list.

PICK-UP CARTRIDGES

B.S.R. "ful-fi" TC8 or ACOS type HGP.59, turnover crystal cartridge with L.P. and standard styli. List 39/7.
LASKY'S PRICE 18/- Post free.

CONVERT YOUR ALL-DRY PORTABLE RADIO TO MAINS 200-250 v.

with the **COSSOR BATTERY ELIMINATOR.** Two separate units identical in size to the B126 and AD35 batteries. 1.5 v. L.T., 90 v. H.T. Suitable for the latest low consumption valves, fully stabilised. New in original cartons. Listed at 63/-.
LASKY'S PRICE 37/6 Post 1/6

A TRANSISTORISED RADIO FOR 25/10

The "DIODEON"—a high-efficiency 2-stage receiver using crystal diode detector and transistor in cascade. Covers 200-500 meters (medium wave). Chassis shows pictorially all components and connections. Built in minutes! Complete parcel including two U16 batteries. **25/10** Post free.
EARPHONES. High imp., 14/6. Low imp., 7/6. Post 1/6.

COMBINED AM/FM TUNER, CONTROL UNIT AND PRE-AMPLIFIER

(Self-powered)

Famous make Mdl. H11. See December issue or send for brochure. LIST £29/3/10.
LASKY'S PRICE 20 GNS. Carr. and Ins., 12/6. Available on H.P. terms.

7-VALVE AM/FM RADIOGRAM CHASSIS

Famous make. For 200-250 v. A.C., Output 4 watts matched to 3 ohms speaker. 7 valves: ECC85, ECH81, EF89, EABC80, EL84, EZ80, EM81, magic eye tuning indicator. Covers medium, long and FM bands. Length 12in., height 7¾in. front to back 8¾in. Limited number only.
LISTED AT 22 GNS.
LASKY'S PRICE £16.19.6 Carr. and Insur. 12/6

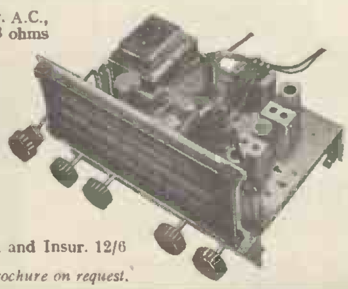

Available on H.P. terms. Brochure on request.

LONDON'S LEADING Hi-Fi SPECIALISTS

Visit either of our addresses for selective Demonstrations of the very latest Hi-Fi Equipment.

AMPLIFIERS
QUAD, ROGERS, LEAK, RCA, JASON, LINEAR, PAMPHONIC, DULCI, W/B, AVANTIC, ARMSTRONG, etc.

SPEAKERS
WHARFEDALE, GOODMANS, LOWTHER, G.E.C., LORENZ, PHILIPS, TANNOY, etc.

PICK-UPS
COLLARO, GARRARD, CONNOISSEUR, LEAK, B/J, ORTOFON, GOLDRING, etc.

TRANSCRIPTION TURNTABLES
COLLARO, GARRARD, LENCO, CONNOISSEUR.

TAPE RECORDERS
GRUNDIG, ELIZABETHAN, BRENELL, TRUVOX, SOUND, VORTEXION, FERROGRAPH, FIDELITY, HARTING, KORTING, SIMON, REFLECTOGRAPH, STUZZI, TANDBERG, TELEFUNKEN, STELLA, WALTER.

F.M. TUNERS
DULCI, QUAD, LEAK, JASON, ROGERS, etc.

CABINETS
Wide choice including G-PLAN, NORDYK and CAPRIOL.

Our Technical and Mail Order Depts are at your service.

SEE OVERLEAF FOR MORE NEWS FROM LASKY'S RADIO

LASKY'S RADIO

LASKY'S HIGHLY EFFICIENT EASY-TO-BUILD SETS : TUNERS : AMPLIFIERS

Circuit Diagram and Building Instructions, 1/6 each, post free.	COMPLETE PARCEL
7-TRANSISTOR PORTABLE, 250 milliwatts p.p. output. **NEW CIRCUIT,** medium and long wave.	£10/10/- Post 3/6
TRANSISTOR SUPERHET TUNER, uses 3 R.F. transistors, 1 germanium diode, etc. Printed Circuit 3⅞in. × 3½in.	£5/12/6 Post 3/6
4-TRANSISTOR AUDIO AMPLIFIER, Mk. II, 200/250 milliwatts, with 2 OC72 and 2 yellow/green. Size 5¼ × 2 × 1½in.	£3/19/6 Post 3/6
4-VALVE SUPERHET PORTABLE. Medium and long wave. Mains/battery version, £8/19/6. Battery version	£7/7/- Post 3/6
MIDGET T.R.F. for 200-250 v. A.C. mains. Uses two latest double-purpose valves. Plastic case, 8½ × 4½ × 5in.	£4/19/6 Post 5/-
LASKY'S F.M. TUNER. Printed Circuit version of the G.E.C. 912 " F.M. Plus," using 5 valves.	£7/19/6 Post Free
PORTABLE GRAM AMPLIFIER, 2 watts. Uses EL84 output and 6X4 rect. Size 6⅝in. × 3⅞in. × 5in. high.	49/6 Post 2/6

ALL JASON KITS IN STOCK. Send for Brochures

LASKY'S CAR RADIO
CAN BE BUILT ABSOLUTELY COMPLETE FOR £12.19.6

★ Small size. Will fit any car
★ 12 volt operation
★ New Hybrid circuit
★ Transistor output
★ New type Brimar valves
★ No Vibrator, 12 volt H.T. & L.T.
★ T.C.C. Printed Circuit and Condensers
★ Tuned R.F. stage
★ Medium and long waves
★ Permeability tuning
★ 7in. × 4in. elliptical speaker.

Send 1/6 for Instruction Booklet giving full details, illustrations, dimensions, circuit diagram and shopping list.

GREAT REDUCTIONS IN TRANSISTORS

P.N.P. Junction types.

AUDIO, suitable for high gain and low freq. amplifiers, and for output stages up to 250 milliwatts. Double spot—yellow and green. Each **5/-**

R.F. suitable for medium and low freq. oscillators, freq. changers and I.F. amplifiers (1.5 to 8 Mc/s). Double spot—yellow and red. Each **5/-**

Type TS1. Suitable for all audio applications. Each **3/6** Post 6d.

Special prices quoted for large quantities.

OC44 and OC45, **21/-**; OC70 and OC71 **12/6**; OC72, **17/-** (Matched Pair **30/-**); OC73, **15/-**; OC16, **45/-**.

EDISWAN MAZDA TRANSISTORS. The very latest types. XB/102, **10/-**; XB/103, **14/-**; XC/101, **16/-**; XA/101, **23/-**; XA/102, **26/-**.

SPECIAL OFFER. Set of 7 Ediswan Transistors: XA/101, XA/102, 2 XB/102 XB/103, 2 matched XC/101. Price **79/6**.

CRYSTAL DIODES. General Purpose GEX00, each **1/-**. Per doz. **9/-**. All other types in stock.

"GOLDTOP" POWER TRANSISTORS

All types in stock. Example:—
V15/10P. Ideal for output stage of car radio, will give approx. 3 watts operating from 12 v. Each **15/-** post free.
Suitable Output Transformer for above, correct ratio, matched to 3 ohms, **9/6**. Post 1/-.
Driver Transformer, **9/6**. Post 1/-.

SUB-MIN. RESISTORS, ⅛th watt, most values available. Each 3½d., per doz. **2/6**.

COSSOR Model 701K VHF/FM RADIO KIT

Everything to build a VHF/FM radio receiver for 200-250 v. A.C./D.C. mains. All components, printed circuit, valves and Goodmans 10×6in. elliptical speaker, in makers' carton with full assembly instructions. Valve line-up: UCC85, two UF89, UABC80, UL84, UY85. Complete Kit, listed at 15 gns.
LASKY'S PRICE £8.19.6 Post 2/6.

MULTI-TEST METER

Famous make, new and unused. AN/27. 27 range. 5,000 ohms per volt A.C. and D.C., in black leatherette-covered wood case, 7⅞ × 9¼ × 3⅞in.
LIST 15 GNS. **LASKY'S PRICE £9.19.6**
Post 5/-. Leads, 7/6 extra.

GET YOUR COPY PER RETURN!
THE FINEST COMPONENTS CATALOGUE

produced for the " ham " or service man. **OVER 100 PAGES, SIZE 8½in. x 5½in. WITH NUMEROUS ILLUSTRATIONS.**

Price **2/-** Post 6d.

Our latest " BARGAIN BULLETIN " free with each copy or available separately post free.

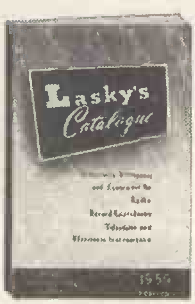

C.R. TUBE BARGAINS
NEW, UNUSED AND TAX FREE

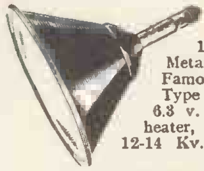

16in. Metal Cone. Famous make. Type T901/B. 6.3 v. .3 amp. heater, ion trap, 12-14 Kv. E.H.T.

LASKY'S PRICE £6.9.6
Carr. and Insur. 21/-.

FERRANTI, 9in. type T9/3. 4 v. heater triode, octal base, standard deflection LIST 9 GNS.
LASKY'S PRICE 50/- Carr. & Insur., 12/6.

FERRANTI 12in., types T12/44 and T12/54.
LIST £12. **LASKY'S PRICE 84/-** Carr. & Insur., 12/6

FERRANTI 17in. type TR17/10, 6.3 v. .3 amp. heater. Brand new and unused.
LASKY'S PRICE £7.19.6 Carr. & Insur., 12/6.

JUST ARRIVED!
17 in. 90 degrees C.R. TUBES

Seconds but in perfect working order and guaranteed.
Price on request.

RE-GUNNED C.R. TUBES
GUARANTEED FOR 12 MONTHS

Type	Price	Carr. & Ins.
12in. round	£6 10 0	12/6
14in. rect.	£6 10 0	12/6
15in. round	£6 19 6	21/-
17in. rect.	£6 19 6	21/-
21in. rect.	£7 19 6	25/-

20,000 VALVES

Mullard, Brimar, G.E.C., Mazda, Cossor, E.M.I., Philips, Pinnacle, Telefunken, etc.

Send for our New List of manufacturers' surplus, ex-Govt. and imported Valves at lowest prices. We save you money.

5-milliamp **METER RECTIFIERS.** Special offer of limited number at only **8/6** Post 9d.

SPEAKER COVERINGS

Large stocks of " Tygan " and " Someweave." Any size piece cut. Sample and prices post free.

SPECIAL OFFER OF SOLDER

1lb. reels of Ersin 5-core " Savbit " SOLDER. List 15/-. LASKY'S PRICE **10/-** Post 1/6.

ALL TYPES OF CHASSIS

Leading makes, including ARMSTRONG, DULCI, EMPRESS, etc.
A.M. chassis (l.,m.,s.) from 7 GNS.
A.M./F.M. chassis from 14 GNS.
A.M./F.M. STEREO from 22 GNS.

PLEASE NOTE 2 ADDRESSES FOR PERSONAL SHOPPERS

207 EDGWARE RD., W.2
Opposite Edgware Road Tube Station
Few yards from Praed Street
PADdington 3271/2

42 TOTTENHAM COURT ROAD, W.1
Nearest Station Goodge Street. MUSeum 2605

OPEN ALL DAY SATURDAY
Early Closing Thurs., 1 p.m.
(Both addresses)

Please address Mail Orders to Lasky's (Harrow Rd.) Ltd., Dept. W, 207 Edgware Rd., London, W.2.

SEE OVERLEAF FOR MORE NEWS FROM LASKY'S RADIO

GEE (Bros.) RADIO LTD.

15, LITTLE NEWPORT STREET, LONDON, W.C.2. *GER. 6794/1453*

ADJOINING LEICESTER SQUARE TUBE STATION—Open 9-6 Weekdays, 9-1 Sat.

G.P.O. RACKS

19in. Heavy duty, all steel. Standard drilling. Two types: 5ft. 6in. angle uprights, **£3/10/-**, carr. 10/-. 6ft. channel uprights (as illustrated), **£5**, carr. 10/-.

19in. x 14in. PANEL SHELF in 14 s.w.g. steel. Suitable for above racks. 15/-. P. & P. 5/-.

OLDHAM MINERS' LANTERN (all steel). 9½in. tall, 3¾in. dia. Complete with bulb and rechargeable accumulator. Ideal inspection lamp for garages, outhouses, etc. **19/11.** Post 2/6.

TELESCOPIC AERIAL MAST. 20ft., 4 sections of 5ft. each. Independently locking at any height. Tapering from 2in. to ⅞in. (less accessories). **50/-**, carr. 5/-.

AERIAL MAST (Army type). 32ft. high. Lightweight kit comprising 10 steel screw-in sections (approx. 1in. dia.). Complete with guys, insulators, pegs, etc. All in canvas carrying bag. Only **£4**. Carr. 7/6.

RE-ENTRANT LOUD HAILERS (Ex-Govt.) Heavy duty 20 watts all-metal 15 ohms. Diameter 15in., length 15in. (approx.) good condition. **£6/10/-** Carr. 10/- Ditto. Brand new, **£8.** Carr. 10/-.

HEAVY DUTY—ALL STEEL TRIPOD STANDS. Adjustable every 6in. to approx. 9ft. 6in. when fully extended. (Folds up to only 4ft. 6in. for storage). Suitable for outdoor speakers, public address systems, floodlighting, etc., etc. (as illus Dec.). OUR PRICE **£3/10/-**. Carr. 5/-.

VITAVOX PRESSURE UNITS TYPE N Heavy duty. Special quality. 20 watts P.M. Brand new. **80/-**. Ditto but in good order, **40/-**. Carr. 5/- on each.

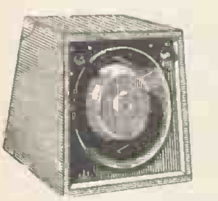

TRUVOX/TANNOY LOUD-HAILERS With 180 ohm line transformer and condenser. Impedante 7½ ohms, handling capacity 8 watts. Complete in slope-front wooden case. In good condition **18/6**. P. & P. 3/6. Brand new **25/-**. P. & P. 3/6.

PRECISION SERIES 834-S (U.S.A.). Multi range tester for A.C./D.C. volts, ohms and milliamps. Basic movement 400 microamps. Housed in wooden box with carrying strap. Overall size 7½ x 7 x 5in. Complete with test prods, batteries, etc. Ready to use, **£4/19/6.** Post 2/6.

ACCUMULATORS **12 v. 25 A.H.** New and unused. Housed in strong wooden case for extra protection, **45/-**. Carr. 7/6. **2 v. 100 A.H.** 75 actual. Ex Govt. New and unused. Complete with carrying handle. Size 6½ x 6½ x 3½in., **15/-** each. Carr. 3/6. 3 sent for **50/-**, or 6 for **£5**, carr. paid. Ditto **16 A.H.**, **5/-**. P. & P. 2/-; 6 for **24/-**. P. & P. 10/-. Ditto **14 A.H.**, less handle, **5/-**. P. & P. 2/-; 6 for **24/-**. P. & P. 10/-

CATHODE RAY TUBES. 2½in. Type VCR139A **25/-**; 3in. Type 3BP1 **30/-**; 5in. Type 5FP7 **35/-**; 5in. Type 5CP1 **35/-**; 6in. Type VCR97 **25/-**. All post free.

ROTARY CONVERTER. 24 v. D.C. to 230 v. A.C. 50 cycles, 150 watts. Brand new and unused. **£8/10/-**. Carr. 7/6. Ditto, 100 watts, **£6/9/6**. Carr. 7/6.

ROTARY CONVERTER. Ex-Govt. 12 v. D.C. input, 230 v. A.C. output, 50 cycles at 135 watts. Complete in carrying case with lid. Voltage control, sliding resistance, mains switch and 0–300 v. A.C. flush meter. In good condition, **£10.** Carr. 10/-.

Motor only, without case, etc. Brand new and unused £8/10/-. Carr. 5/-.

VARIABLE VOLTAGE TRANSFORMER. (BERCO Regulator) Pri. 440 v. 50 cycles, sec. 0–440 v. at 6.5 amps. or can be connected for 230 v. to give 0–230 v. at 12 amps. Brand new and unused £18/10/-. Carr. 10/-.

HEAVY DUTY LT TRANSFORMERS. 230 v. 50 cycles pri. 17 v. sec. at 35 amps., capable of carrying 25% over actual rating. Perfect condition. ONLY **115/-** Carr. 5/-.

6 kV/A. AUTO-TRANSFORMER. 230/110 v. 50 cycles (fully tapped primary and secondary). Capable of 25% over actual rating. Brand new and unused. **£18.** Carr. 20/-. Also **3 kV/A** as above. **£12/10/-**. Carr. 20/-.

20 kV/A AUTO-TRANSFORMER. 230/115 v. 50–60 cycles, by Jefferies Transformer Co., U.S.A. Perfect condition. **£20.** Carr. £1.

CONSTANT VOLTAGE TRANSFORMER. 190–260 v. primary, sec. 115 v. at 1½kV/A (listed at 2 kV/A). Brand new and unused. **£25** or **£45** per pair. Carr. 10/- each.

A.C.-D.C. RECTIFIER POWER SUPPLY UNITS

110–230 v. A.C. 50 cycles input, 100/110 v. D.C. output max. 2½ amp. Brand new and unused. **£4/10/-**. Carr. 7/6.

230 v. A.C. 50 cycles input, 200/220 v. D.C. output at 3/4 amps. approx. Good condition. **£10.** Carr. 10/-.

200/250 v. A.C. 50 cycles input, secondary 24 v. at 26 amps. D.C. Capable of 25% over actual rating. Brand new and unused. **£12/10/-**. Carr. 20/-.

200/250 v. pri., 110 v. sec. at 4 amps. max. Brand new and unused. **£8/10/-**. Carr. 10/-.

AIRBORNE TRANSMITTER RECEIVER. TYPE 1986. A mobile 10-channel crystal controlled V.H.F. Tx/Rx. covering 124.5/156 Mc/s. I.F. band width 23 kc/s. Complete (less external attachments) in metal case, with all valves and 24 v. rotary power unit. Used, but in first-class condition. ONLY **£8/10/-**. Carr. paid. Also, complete with control box and all necessary connecting leads, **£12**, carr. paid.

AIRCRAFT RADIO RECEIVER. (By R.C.A.) Freq. 195 Kc/s to 9050 Kc/s. (33-1500 metres) continuous. For 28v. D.C. input with built-in dynamotor. This 6 valve receiver with 2 R.F. stages and 2 I.F. stages with B.F.O. and C.W. is in our opinion one of the finest sets so far released by the Air Ministry. **£7.10.0.** Carr. 5/-.

TELEPHONE SETS (TELE "F"). Housed in bakelite cases, complete with built-in ringing generators and batteries. Ideal between two or more positions up to practically any distance. Tested before despatched. ONLY **70/-**. P. & P. 3/6. 2 sent for **£6/10/-**. Carr. paid.

TELEPHONE CABLE. Twin one-mile drums (Don 8), **£5.** Carr. 20/-. Single one-mile drums (Don 3). **50/-**. Carr. 7/6.

TELEPHONE DIALS. Standard (G.P.O.) Pattern. 0–9. Brand new. **30/-**. P. & P. 1/-.

C.M.G. 25 PHOTO CELLS (OSRAM). Brand new, **15/-**. P. & P. 1/-.

EVERSHED 12 PEN TIME RECORDER. Portable 12-channel instrument for simultaneous recording of 11 events with time marks provided by the 12th pen. Recording is in the form of "on/off" pulses. Speed 2in. per sec. Price unused (less pens), **£10.** Carr. 10/-.

SELENIUM METAL RECTIFIERS, FULL BRIDGE

6 or 12 v. 1 amp. 7/6;	24 v. 1 amp. 13/6;
12 v. 2 amp. 10/-;	24 v. 2 amp. 20/-;
12 v. 2½ amp. 15/-;	24 v. 2½ amp. 25/-;
12 v. 4 amp. 16/6;	24 v. 4 amp. 30/-;
12 v. 6 amp. 23/6;	24 v. 6 amp. 35/-;
12 v. 10 amp. 40/-;	24 v. 10 amp. 80/-.

BRAND NEW CRYSTAL CALIBRATOR No. 10. (Battery powered 1.4 v. valves.) Complete with full working instructions, circuit diagram, carrying haversack, connecting lead and spare valves. Frequency range: 1.5 to 10 Mc/s. (Nominal) but can actually be used up to 30 Mc/s. Weight 5lb. Size 7in. x 7½in. x 4in. A miniature B.C.221 in every respect. A must for every laboratory, etc. ONLY **£4/19/6.** P. & P. 2/6.

BRIDGE MEGGERS Evershed and Vignoles Series 2 in perfect condition. 250 v. **£22**, carr. paid. Leather case available at 20/- extra.

EVERSHED AND VIGNOLES WEE MEGGERS. 500 v. £12/10/-. Ditto 250 v. £10/10/-. P. & P. 3/- on each.

EVERSHED AND VIGNOLES MEGGER CIRCUIT TESTER (low reading ohm meter). 2 ranges. 0–3, 0–30 ohms. The perfect meter for continuity and polarity testing, complete with test leads and ready to use. Brand new. Only **£4/17/6.** P. & P. 3/-.

MULLARD BRIDGE

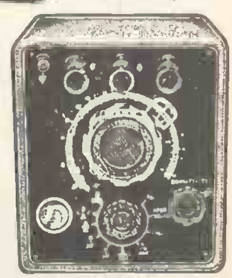

Type GM. 4140/1. Mains operated from 100–250 v. A.C. Will test resistances from 0.1 ohm to 10 megohms and condensers from 10pf. to 10mfd. Good condition and complete with instruction booklet. **£6/19/6.** P. & P. 2/6.

MARCONI SIGNAL GENERATOR. TYPE TF517-F/1. Covering 10–18 Mc/s. 33–58 Mc/s. 150–300 Mc/s. In very good condition. Complete with full technical data and instructions. Unrepeatable at only **£12/10/-**. Carr. 20/-.

ALSO MARCONI SIGNAL GENERATOR. TYPE TF390G for 200–250 v. A.C. mains input. Frequency range 4–16 Mc/s. and 32–100 Mc/s. indirect calibration. Output 1 μV to 100 M/V. 400 c/s internal modulation. In good order. Only **£12/10/-**. Carr. 20/-.

MARCONI VALVE VOLTMETERS TF.428 B/1. 5 ranges A.C. and D.C. 1.5, 5, 15, 50 and 150 v. A.C. mains operation 200/250 v. Supplied in good working order. **£14.** P. & P. 7/6.

AVO VALVE DATA MANUAL. Containing a host of information on hundreds of valves including civilian equivalents of many service types. **21/-**. Post free.

30 WATT AMPLIFIER R.S.C. A.10 ULTRA LINEAR

HIGH FIDELITY PUSH-PULL UNIT EMPLOYING SIX VALVES. EF86, EF86, ECC38, 807, 807, GZ34. Tone Control Pre-Amp. stages are incorporated. Sensitivity is extremely high. Only 12 millivolts minimum input is required for full output. THIS ENSURES THE SUITABILITY OF ANY TYPE OR MAKE OF MICROPHONE OR PICK-UP. Separate Bass and Treble controls give both "lift" and "cut" with ample tone correction for long playing records. An extra input with associated vol. control is provided so that two separate inputs such as "mike" and gram. etc., etc., can be simultaneously applied for mixing purposes. AN OUTPUT SOCKET WITH PLUG IS INCLUDED FOR SUPPLY OF 300 v. 20 mA. and 6.3 v. 1.5 A. FOR A RADIO FEEDER UNIT. Price in kit form with easy-to-follow wiring diagrams.

ONLY **11 Gns.** Or Factory built with 12 months' guarantee £13/19/6. TERMS ON ASSEMBLED UNITS. DEPOSIT 24/9 and 12 monthly payments of 24/9.

Carr. 10/-.

Cover as illustrated 18/9 extra.

Type 807 output valves are used with High Quality Sectionally wound output transformer specially designed for Ultra Linear operation. Negative feedback of 20 D.B. in main loop. CERTIFIED PERFORMANCE FIGURES ARE EQUAL TO MOST EXPENSIVE UNITS AVAILABLE. Frequency response ± 3 D.B. 30-20,000 c/cs. Tone Controls ± 12 D.B. at 50 c/cs. ± 12 D.B. to — 6 D.B. at 12,000 c/cs., hum and noise 70 D.B. down. Good quality reliable components used. Chassis finish blue hammer. Overall size 12 × 9 × 9in. approx. Power consumption 150 watts. For A.C. mains 200-250 v. 50 c/s. Outputs for 3 and 15 ohm speakers. EQUALLY SUITABLE FOR THE CONNOISSEUR OR FOR LARGE HALLS, CLUBS OR OUTSIDE FUNCTIONS, IDEAL FOR USE WITH MUSICAL INSTRUMENTS SUCH AS STRING BASS, ELECTRONIC ORGAN, GUITAR, etc. FOR DANCE BANDS, GARRISON THEATRES, etc., etc. We can supply Microphones, Speakers, etc., at keen cash prices or on terms with amplifiers. EXPORT ENQUIRIES INVITED.

LINEAR "DIATONIC" 10 WATT HIGH FIDELITY AMPLIFIER. A compact attractively finished unit. 12 gns. Cash. Send S.A.E. for leaflet. H.P. Terms. Dep. 22/3 and twelve monthly payments of 22/3.

LINEAR LI/10 10 WATT HIGH FIDELITY AMPLIFIER, with 3 position equalisation switch. 13 Gns.

LINEAR L5/5 HIGH QUALITY STEREO AMPLIFIER. Total output 10 watts. Handsome Perspex Facia Plate. All controls ganged. Only 11 Gns.

LINEAR L45 MINIATURE 4/5 W. QUALITY AMPLIFIER. Suitable for use with any record playing unit and most microphones. Negative feedback 12 D.B. Bass and Treble controls. For A.C. mains input of 200-250 v. 50 c.p.s. Output for 2/3 ohm speaker. Three miniature Mullard valves. Size only 6 × 5 × 5½in. high. Chassis fully isolated from mains. Guaranteed 12 months. Only **£5/19/6** Or Deposit 22/- and 5 monthly payments of 22/-. Send S.A.E. for leaflet.

L63 MINIATURE 3 WATT GRAM AMPLIFIER

For 200-250 v. 50 c.p.s. A.C. mains. Overall size only 6¼ × 4¼ × 2¼in. Fitted Vol. and Tone Control with mains switch. Designed for use with any kind of single player or record changing unit. Output for 2-3 ohm speaker. Guaranteed 12 months. Only 57/9.

R.S.C. A7 3-4 WATT QUALITY AMPLIFIER. Spec. exactly as A5 below with exception of output wattage. Complete kit of parts, diagrams and instructions £3/15/-, carr. 3/6.

R.S.C. A5 4-5 WATT HIGH GAIN AMPLIFIER

A highly sensitive 4-valve quality amplifier for the home, small club, etc. Only 50 millivolts input is required for full output so that it is suitable for use with the latest high-fidelity pick-up heads in addition to all other types of pick-ups and practically all mikes. Separate Bass and Treble controls are provided. These give full long playing record equalisation. Hum-level is negligible being 71 D.B. down. 15 D.B. of negative feedback is used. H.T. of 300 v. 26 mA. and L.T. of 6.3 v. 1.5 a. is available for the supply of a Radio Feeder Unit or Tape Deck pre-amplifier. For A.C. mains input of 200-250 v. 50 c/s. Output for 2-3 ohm speaker. Chassis is not alive. Kit is complete in every detail and includes fully punched chassis (with baseplate) with the blue hammer finish, and point-to-point wiring diagrams and instructions. Exceptional value at only £4/15/- or assembled ready for use 25/- extra, plus 3/6 carriage. Or Deposit 22/- and five monthly payments of 22/- for assembled unit.

P.M. SPEAKERS. 2-3 ohm 2½in. Perdio 21/9. 5in. Goodmans 17/9. 7 × 4in. R.A. Elliptical 19/9. 6½in. Rola 19/9. 8in. Rola 19/9. 8in. Goodmans 21/9. 8 × 6in. Elac with high flux magnet 25/9. 10in. R.A. 28/9. 10 × 6in. Elliptical Goodmans 29/9. 12in. R.A. 29/11. 12in. R.A. 3 or 15 ohms, 10 watts, 12,000 lines, 59/6.

TWEETERS. 4in. Plessey, 3 ohms, 18/9. R.A. 15 ohm 25/9.

COLLARO CONQUEST 4-SPEED AUTO-CHANGERS. With studio pick-up with turnover head. BRAND NEW. Cartoned latest model. For 200-250 v. A.C. mains. £7/19/6. Carr. 4/6.

ACOS Crystal Microphone Inserts. Brand new. Only 5/11 ea. Ex. Equip. 4/11 ea.

ACOS HGP59 Hi-Fi Crystal Cartridges. (Turnover type, with sapphire stylus). Standard replacement for Garrard and Collaro. Only 19/9. B.R.S. Ful-6 19/9. Garrard GC2 19/9.

COSSOR V.H.F. F.M. RADIO RECEIVER KITS. Brand New Boxed with valves, printe circuit and 10 × 6in. Speaker. For 200-250 v. A.C. mains. Pre-aligned I.F.T.s. Normal price 15 Gns. Our price £8/19/6.

HIGH FIDELITY 12-14 WATT AMPLIFIER TYPE A11

PUSH-PULL ULTRA LINEAR OUTPUT "BUILT-IN" TONE CONTROL PRE-AMP STAGES

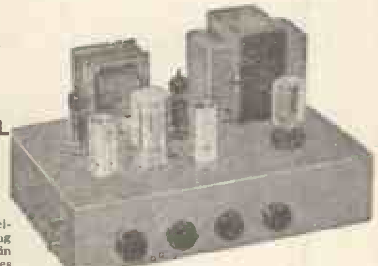

Two input sockets with associated controls allow mixing of "mike" and gram. as in A10. High sensitivity. Includes 5 valves, ECC83, ECC83, EL84, EL84, 5Y3. High Quality sectionally wound output transformer specially designed for Ultra Linear operation, and reliable small condensers of current manufacture. INDIVIDUAL CONTROLS FOR BASS AND TREBLE "Lift" and "Cut." Frequency response ± 3 D.B. 30-30,000 c/cs. Six negative feedback loops. Hum level 60 D.B. down. ONLY 23 millivolts INPUT required for FULL OUTPUT. Suitable for use with all makes and types of pick-ups and microphones. Comparable with the very best designs. For STANDARD or LONG PLAYING RECORDS. For MUSICAL INSTRUMENTS such as STRING BASS, GUITARS, etc. OUTPUT SOCKET with plug provides 300 v. 30 mA. and 6.3 v. 1.5 a. For supply of a RADIO FEEDER UNIT. Size approx. 12-9-7in. For A.C. mains 200-250 v. 60 c/cs. Output for 3 and 15 ohms speakers. Kit is complete to last nut. Chassis is fully punched. Full instructions and point-to-point wiring diagrams supplied. (Or factory built 45/- extra). Only **8 Gns.** Carr. 10/- If required louvred metal cover with 2 carrying handles can be supplied for 18/9. TERMS ON ASSEMBLED UNITS. DEPOSIT 18/9, and 12 monthly payments of 18/9. Send S.A.E. for illustrated leaflet detailing Ready-to-assemble Cabinets, Speakers, Microphones, etc., with cash and credit terms.

R.S.C. PORTABLE GUITAR AMPLIFIERS

JUNIOR 5 WATT. High Quality Output. Separate Bass and Treble "cut" and "boost" controls. Sensitivity 15 mv. High Flux 8in. l/speaker. Input sockets for Radio/Tape or Gram Pick-up and Mike /Instrument Pick-up. Handsome strongly made cabinet (size approx. 14 × 14 × 7in.). Finished in satin walnut and fitted carrying handle. **£8/19/6** Carr. 7/6. Or Deposit £1 and nine monthly payments £1. Send S.A.E for leaflet.

SENIOR 10 WATTS. High Fidelity Push-Pull output. Separate Bass and Treble "cut" and "boost" controls. Twin separately controlled high gain inputs so that two instruments such as Guitar and String Bass can be used at the same time. Two Loudspeakers are incorporated, a 12in. P.M. for Bass notes, and a 7 × 4in. elliptical for Treble. Cabinet is well made and finished satin walnut. Size approx. 18 × 18 × 8in. 15 Gns. Plus 10/- carr. H.P. TERMS. DEPOSIT 26/9. and 12 monthly payments 26/9. Both models for 200-250 v. A.C. mains.

STAAR GALAXY 4-SPEED MIXER AUTO-CHANGERS. Brand New, cartoned. Turnover sapphire styli. Many exclusive features. Unique design motor virtually free from rumble. For 200-250 v. A.C. mains. Limited number tested and guaranteed £5/19/6. Carr. 4/6.

PORTABLE CABINETS

For Record Players or Tape Recorders. Rexine covered. Wide selection of attractive designs and colour combinations. PRICES FROM **15/9**

12in. 10 WATT HIGH QUALITY LOUDSPEAKER IN POLISHED WALNUT FINISHED CABINET

Gauss 12,000 lines. Speech coil 3 ohms or 15 ohms. Only £4/19/6. Carr. 5/-. Terms: Deposit 11/- and 9 monthly payments of 11/-. 12in. 20 WATT 15,000 line l/speakers 15 ohms, in Cabinet finished as above. Size 18 × 18 × 8in. £7/19/6 or Deposit 13/10 and 12 monthly payments 13/10.

PORTABLE CABINETS. Attractive design Two-tone rexine covered. Will take Collaro, B.S.R., Garrard or Staar Auto-Changer, amplifier and 7in. × 4in. or 5in. speaker. Slightly soiled. Only 49/6.

ACOS HIGH FIDELITY PICK-UPS. GP54 with HGP59/52 Cartridge. Turnover sapphire styli, cream finish. Limited number at approx. half-price. Only 29/11.

SPECIAL OFFER

Above cabinet Staar Changer, Gram amplifier, and 5in. or 6in. × 4in. speaker £9/19/6. Carr. 10/-. Or with Collaro Conquest changer in lieu of Staar, 12 Gns. Carr. 10/-.

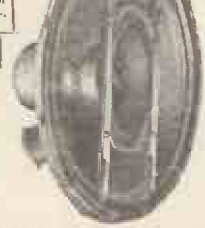

PLESSEY DUAL CONCENTRIC 12in. P.M. SPEAKERS

(15 ohms), consisting of a high quality 12in. speaker of orthodox design supporting a small elliptical speaker ready wired with choke and condensers to act as tweeter. This high fidelity unit is highly recommended for use with our A11 or any similar amplifier. Rating is 10 watts. Gauss 12,000 lines. Price only £5/17/6. Or Deposit 10/6 and 12 monthly payments of 10/6.

R.S.C. (LEEDS) LTD. MANCHESTER, LEEDS & BRADFORD

Open to callers at the following branches :—

5-7 County (Mecca) Arcade, Leeds, 1.
54-56 Morley Street, (above Alhambra), Bradford.
8-10 Brown Street, (Market, St.) Manchester, 2.

TERMS: C.W.O. or C.O.D. No C.O.D. under £1. Postage 1/9 extra on all orders under £2, 2/9 extra under £5 unless carriage stated. Trade supplied. Post orders to Mail Order Dept., 29-31 Moorfield Road, Leeds, 12.

RETURN OF A WINNER!!!

(Exclusive)

We have been fortunate in obtaining further limited supply of this fine and popular cabinet. Instantly recognised as being of leading High Quality manufacturers' stock, this trolley-type cabinet is finished in polished dark walnut. Can easily be adapted to accommodate tape recorder, amplifier, radiogram, etc., etc. External measurements: 24½in. x 16in. x 29in. The whole is mounted upon "easy run" castors. Subject to being unsold. £5/19/6. plus 15/- C. & P.

VERDIK "QUALITY 10." A superb Hi-Fi amp. and pre-amp. with 10 watt push-pull ultra linear output. Beautifully finished in grey-green stove enamel. Controls: Bass, Treble, Volume and input selection for Radio, Mike, Tape, Std. and L.P. Records. Limited stocks at only £14/19/6 plus 7/6 P. & P. (List 20 gns.). Terms available.

EXTRA SPECIAL OFFER!!

A small three-valve **PORTABLE RECORD-PLAYER AMPLIFIER** mounted on baffle 12x7in., with High Flux 6½in. Loudspeaker, Valve line-up ECC83, EL84, EZ80. Incorporates separate bass and treble controls. Max. output 3 watts. Will match all types of high impedance pick-up. Ready to use, £5/12/6 plus 3/6 P. & P.

NEW STYLE CABINET finished in two-tone Leatherette. Will accommodate above Amplifier and Baffle without modification, also most types of Ancillary Equipment. Overall size 18 x 13½ x 8½in. Fitted with carrying handle, £3/9/6 plus 5/- P. & P.

NOTE. If both items purchased together they will be supplied at a special inclusive price of £8/7/6 plus 6/6 P. & P.

OUR PRINTED CIRCUIT F.M. TUNER. This is our printed circuit version of the Osram 912 F.M. Tuner—using T.C.C. printed circuit and condensers, incorporating 5 valves and two germanium diodes. Attractive black and gold dial, with gold escutcheon plate. Dial aperture only 5 x 2in. Osram F.M. booklet plus our additional instructions and individually priced components list—2/6 post free or absolutely complete parcel of components (even the solder!) at £8/8/- plus 2/6 P. & P. Alignment service available if required. We are demonstrating at both branches.

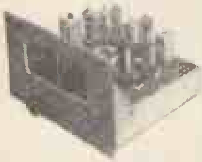

Latest COLLARO STUDIO TAPE TRANSCRIPTOR. 3 motors, 3-speed: 1⅞, 3¾, 7½ i.p.s., takes 7in. spools. Push-button controls. £15/15/- plus 5/- P. & P. Usual H.P. facilities.

"ROLEX" SPECIAL HEAVY DUTY MAINS/BATTERY AMPLIFIER. Very smart unit housed in gred crackle finish case with chrome any cream fittings. For use on A.C. mains 200/250 v. or 6 v. D.C. battery. Valve line-up: 6SK7, 6SN7, 6SL7, 2-6V6, 6X5 and 629C vibrator. 20 watts output to match 4, 8, 16, 250 and 500 ohm speaker systems. Ideal for P.A. work, etc. Size: 13½in. x 8½in. x 7¾in. Mike and gram inputs with separate gain controls, tone control, Brand new, fully guaranteed. **ONLY £15/15/-**, plus 7/6 P. & P.

A SPECIAL HIGH QUALITY PUSH-PULL AMPLIFIER
By famous manufacturer

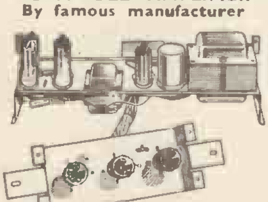

Limited stocks only of this really wonderful quality amplifier employing 4 valves: 2-EL84, ECC83, EZ80. Separate Bass and Treble Controls mounted with Volume Control upon loose panel with flying leads. Excellent quality components employed throughout. Overall dimensions: (Main chassis) 12½in. x 4in. x 5in. high. Control panel: 6in. x 2¾in. Input to match standard high impedance crystal or magnetic pick-up. Output approx. 8 watts max. WHILST STOCKS LAST ONLY £6/19/6, plus 3/6 P. & P.

CABINET SPECIAL!!! JUST ARRIVED!!

Leading manufacturers' special tape equipment cabinet—multi purpose. Will house all your portable tape or record playing equipment, speaker up to 8in. or 10in. x 6in. Size 18in. x 16in. x 14in. Dark green rexine covered, chrome carrying handles and fitted detachable lid with lockable clips. (Keys supplied.) Brand new in original packing. PRICE **ONLY** 75/- plus 5/- part packing and carriage. (Limited quantity). A truly professional job!

RECORD PLAYERS

Full range of changers, single players, transcription units at usual competitive prices. Interesting H.P. facilities.

E.M.I. 4-SPEED STEREO SINGLE RECORD UNIT. Complete with Stereo Head and Sapphire Styli. Brand New and Fully G'teed. **ONLY** £6/19/6 plus 3/6 P. & P. whilst stocks last.

ADVANCE ANNOUNCEMENT!

TWO NEW COMPETITIVELY PRICED TAPE RECORDER KITS NOW READY!

Both 3 watts output, printed circuit construction, valve line-up EF86 EL84, ECC83, EZ80 and EM84 recording indicator. Latest 9" x 4" High Flux Speaker. Complete with Tape and empty Spool, and Acos 39-1 stick mike with stand. Attractive two-tone Cabinet. Supplied with latest COLLARO Studio 3-speed deck. Total price 25 guineas. Supplied with B.S.R. single-speed deck, total 20 guineas.
N.B. These are Kits, amplifier supplied unassembled. Full assembly instructions are included. Please add 7/6 for packing and carriage. All parts available separately. Full details on application.

NEW! FOR THE CONSTRUCTOR

SUPER 1-VALVE SHORT-WAVE RADIO. World-wide coverage at most reasonable cost. Covers 40-100 metres with the coil supplied. Can be extended to cover 10-100 metres. Provision is also made for the addition of two extra valve stages. Employs the famous Acorn-type 954 valve. All necessary components can be supplied complete with full assembly instructions at **ONLY** 35/- plus 2/- P. & P. Send 2/- for point-to-point wiring diagram and price list.

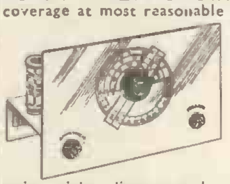

SUPER PERSONAL PORTABLE. A wonderful little set that you can take anywhere. Ideal for camping, picnics, etc. Detachable aerial rod supplied. Covers Medium waveband 200-500 metres. Can be built in approx. 1 hour. All necessary components available at the following SPECIAL INCLUSIVE PRICES: 1-valve version **ONLY** 35/-. Super 2-valve version **ONLY** 41/-. Plus 2/- P. & P. Send for point-to-point wiring diagram and parts price list 2/- post free. Extra for use with the above DLR5 balanced armature headphones, 7/6 pair.

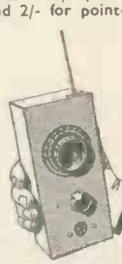

TWO-TRANSISTOR PERSONAL PORTABLE. This is an amazing little receiver with built-in aerial, and small enough to be held in the palm of the hand. Medium wave reception at wonderful volume. Supplied with drilled chassis and colour coded components. Easily assembled with the aid of the easy-to-follow assembly instructions provided. Total cost of all necessary components, including transistors, Deaf-aid type earpiece, wiring wire and even solder. **ONLY** 69/6 or complete with single standard High Resistance earphone at ONLY 62/6. Plus 1/6 P. & P. Parts price list and Easy Lay-out Plans 2/- post free.

SPEAKER BARGAINS

Goodmans 8in. x 2½in., 3 ohms, 25/- plus 1/6 P. & P. 10in. Elac High Flux 3 ohm, 39/6 plus 2/6 P. & P. 8in. Celestion High Flux 3 ohm, 32/6 plus 2/- P. & P. 4in. Plessey Tweeter, 15/- plus 1/6 P. & P. R. & A. Type 9120, Mk. II, 12in., 10-12 watts, 3 ohm, 12,000 gauss, 55/- plus 3/6 P. & P. R. & A. Type 8120, Mk. II, 12in., 10-12 watts, 3 ohm, 10,000 gauss, 39/6 plus 3/6 P. & P. 12in. Bakers Selhurst, 15 ohms, 15 watts, 30-14,000 c.p.s., £4/10/- plus 3/6 P. & P. All the above brand new and fully guaranteed.

SUPER TRANSISTOR/CRYSTAL RECEIVER. Our amazing extra sensitive transistor/crystal receiver for local stations, with built-in ferrite aerial, can be supplied for home contruction at **ONLY** 27/6 for all necessary components inc. pen torch batt. P. & P. 2/- extra. Simple to construct, excellent in performance, most attractive in appearance. Instruction envelope available separately if required at 1/- post free. Suitable Deaf-aid ear piece for above, 12/6.

DECCA PORTABLE AMPLIFIER. As supplied in famous DECCAMATIC III. Complete with small cream knobs. Full range tone and volume controls. Employs ECL82 valve. Size 3 x 3½ x 8¾in. Only 59/6 plus 2/6 P. & P.

SPECIAL CELESTION 8 x 6in. elliptical high flux loudspeaker 30/- plus 1/- P. & P.

VERY ATTRACTIVE PORTABLE CABINET in Red and White polka dot for accommodating the above items and ancillary equipment, 75/- plus 5/- P. & P.

NOTE. Supplied post free if all above items purchased together.

CLYNE RADIO LTD.

RC

162 Holloway Road, London, N.7.
and
18 Tottenham Court Road, London, W.1

SEE OVER FOR MORE BARGAINS

JASON TEST EQUIPMENT

The following equipment of top quality is now available for home construction.

AUDIO GENERATOR AG10. Covers from 10 c/s. to 100 Kc/s. in four ranges. Max. output 10 volts. Min output 100 microvolts. Square wave output with excellent rise time makes this generator very useful for checking all Audio equipment. Housed in attractive metal shelf mounting case measuring 11½in. × 6¼in. × 5¼in. high. All necessary components available, including valves, at a Special Price of £14/5/-, plus 3/6 p. & p.
Fully descriptive booklet with comprehensive assembly instructions available at 2/- post free.

OSCILLOSCOPE OG10. This is a general purpose Oscilloscope based on a "Mullard" circuit employing a DG7-32 3in. cathode-ray tube. A sensitivity of 100 microvolts per c.m. with a band width of 2 c/s. to 2.5 mc/s. makes this a useful unit for T.V. servicing as well as audio amplifier checking. Housed in smart metal case complete with carrying handle. All necessary components available, including valves, at a Special Price of £22/10/- plus 5/- p. and p. Fully descriptive booklet with comprehensive assembly instructions available separately at 3/6 post free.

CLYNE CATHODE RAY OSCILLOSCOPE
for Home Construction

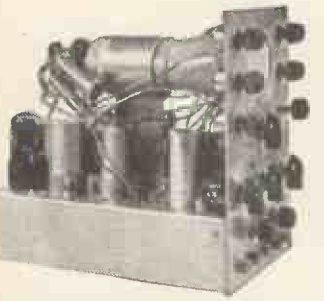

The latest addition to our comprehensive stocks of quality equipment for the constructor. This is an exceptionally sound and robust instrument of the most versatile type, that will be a boon to the seriously minded amateur, serviceman or constructor. Specifications: 8-Range Time Base, switched from 20 c/s. to 160 Kc/s. Y-Plate Amplifier has a sensitivity of 50 mV. and frequency response of 20 c/s to 600 Kc/s with a gain of 150. A calibrating voltage of 6.3 v. 50 c/s is provided. Employs ECR30 2¾in. Cathode Ray Tube and 4 valves: 2/ECF80, 1/EF91, 1/EZ35, 6X5. Controls: X-shift, Y-shift, Focus, Width, Brilliance. ON/OFF. Time Base Frequency (Fine), Time Base Frequency (Course). Sync. Selector. Sync. Amplitude. Y-input Selector. X-input Selector. Amplifier Gain. Operates from 200/250 v. or 110 v. A.C. Mains. All required components for the construction of this wonderful instrument, including comprehensive assembly instructions, available at a SPECIAL INCLUSIVE PRICE OF ONLY £12/19/6 plus 5/- carriage and packing.

A.M. GRAM CHASSIS SPECIAL! (By famous manufacturer)
This special offer chassis is being offered for a limited period only and represents the best possible value for money. Spec.: 3 wavebands, Long, Medium and Short. 5 miniature valves—6C7, 6F15, 6LD20, N108, U107. Attractive vertical glass dial (13in. × 3½in.) in red, green and gold on black background. Two-speed dial drive. Full range tone control. Output approx. 4 watts to match 3 ohm speaker. For A.C. mains 110/250 v. Overall size 13in. × 6¼in. × 6¾in. high. WHILST STOCKS LAST, £7/19/6 ONLY, plus 7/6 P. & P.

VALVES. We have perhaps the most up-to-date valve stocks in the trade. New imported valve types fully guaranteed and P.T. paid and all the usual surplus types at special prices. We also carry a comprehensive stock of all B.V.A. types at current list prices. Send stamp for NEW list now available. Note: Certain American special purpose types can be supplied. Enquiries invited.

RE-GUNNED CATHODE RAY TUBES. (As new.) Guaranteed 12 months. 12in., 14in., and 15in., £5/10/-; 17in., £6; 21in., £7/19/6, plus 10/- c. and p.

★ BARGAIN CORNER ★

12 CHANNEL T.V. TURRET TUNER (By famous manufacturer). Brand new, **NOT** surplus or ex-equipment. 35 Mc/s. **I.F. PCC 84** and **PCF 80** valves. Complete with coils: Band I Channels 1 to 5. Band III Channels 8 to 11. In manufacturers original carton. Fully guaranteed at only 39/6 plus 2/6 P. & P.

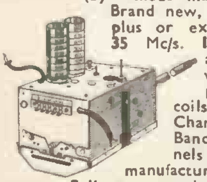

ACOS MIC 39-1. Crystal stick microphone with stand. List price 5gns. Our price 39/6 plus 1/6 P. & P.

DEAF AID TYPE EARPIECES. Standard magnetic type complete with lead and plug. As new. **ONLY 12/6** plus 1/- P. & P.

3-SECTION WHIP AERIALS. Ideal for fishing rods, etc. Each section 4ft. ONLY 7/6 set, plus 2/6 P. & P.

EX-W.D. DON MK. V FIELD TELEPHONE SET. Complete with handset, buzzer, hand generator, morse key. £3 each or £5/10/- pair.
(Both above plus 2/6 P. & P.)

WIRING WIRE. 5 coils 10 yards each in different colours contained in cellophane bag, 5/- plus 9d. postage.

TRANSFORMER SPECIAL. Superior quality half shrouded drop thro' Mains Transformer. Input 200/250 v. Output 350–0–350 v. 80 mA.; 6.3 v. 3 amps. 5 v. 2 amps. Ex-equipment but guaranteed O.K ONLY 9/6 plus 1/- P. & P.

8in. LOUDSPEAKER. Ex-equip. as new. Less transformer 3 ohm speech coil In attractive cloth covered cabinet. Ideal for extension speaker. 22/6 plus 1/6 P. & P.

BARGAIN! REPLACEMENT PICK-UP INSERTS. All brand new and fully guaranteed. Complete with Sapphire Styli. **PHONOFLUID 21/-** each. **B.S.R. TC8** (less bracket) 15/- each. **B.S.R. Hi-G** with bracket, 18/- each. **B.S.R. Hi-G** (less bracket) 15/- each. **E. V. POWER POINT** in Garrard plug-in shell, 18/6 each. **E. V. CARTRIDGE** only 11/6 each. All plus 9d. P. & P.

A COMPACT TEST METER FOR HOME CONSTRUCTION. This is a very sensitive multi-range test meter (500 microamp basic movement) covering the following ranges: A.C./D.C. voltage: 0–10 v., 0–50 v. and 0–500 v. Current: D.C. 0–10 mA., 0–50 mA. and 0–500 mA. Resistance (on internal battery) 2 K.ohm to 100K.ohm. Housed in a smart grey stove enamelled case measuring 3¾in × 7in. × 1¾in. overall. Brand new best quality components and High Stability resistors are used throughout, resulting in a thoroughly reliable, accurate instrument.
NOTE: Meter is supplied with calibrated scale fitted, and all components, including shunt, are prepared for immediate soldering into position. Comprehensive assembly instructions with practical and theoretical diagrams are supplied together with all necessary components at a SPECIAL INCLUSIVE PRICE OF ONLY 59/6 plus 1/6 P. & P. The instruction envelope is available separately if required at 1/6 p. free.

PRECISION TEST METER
(To build yourself)
Nineteen ranges, D.C./A.C. Current and resistance. Designed and produced for us by the famous Pullin Company. All necessary components at Special Inclusive Price of only £5/19/6 plus 2/6 P. & P. Illustrated leaflet with full description available on request.

CABY UNIVERSAL TEST METERS
These pocket-size multi-range test meters are of excellent quality and cover all the most useful ranges (A.C. Volts, D.C. Volts, resistance and current). Supplied complete with test prods, instruction book and batteries.
Model A.10 (2,000 ohms per volt) £4/17/6
Model B.20 (10,000 ohms per volt) £6/10/-.
Plus P. & P. 3/6 on each.
Fully detailed and illustrated leaflet available on request.

ALFA POCKET TESTMETER
A most versatile test meter covering 15 ranges. 3,333 o.p.v. basic movement. Ohms ranges: 0-20K, 0–2 Meg. Volts: A.C. and D.C. 6 v., 12 v., 60 v., 300 v., 1,200 v. Current: D.C. 300 microamps, 30 mA., 300 mA. Size only 3½in. × 5in. × 1¼in. overall. Supplied complete with instructions and test prods. ONLY £5/19/6 plus 2/6 P. & P.

EVERSHED AND VIGNOLES BRIDGE MEGGERS. Series 2. 250 v. Perfect and complete with leather carrying case. **FEW ONLY** at £19/19/-, plus 7/6 P. & P.

DLR5 BALANCED ARMATURE HEADPHONES. Complete with headband and leads, 7/6 pair, plus 1/6 P. & P.

HIGH IMPEDANCE LIGHTWEIGHT HEADPHONES. Brand new imported type 4000 ohms. Complete with leads, 15/- plus 1/6 P. & P.

—TRANSISTORS ! ! !—

SURPLUS—P.N.P.

RED SPOT (Audio/Experimental Application)	5/- ea.
WHITE SPOT, R.F. up to 2.5 Mc/s.	7/6 ea.
STANDARD—	
BRIMAR	
T58	18/6 ea.
MULLARD	
OC16 Power 3 watt	54/- ea.
OC44	18/6 ea.
OC45 R.F. up to 6 Mc/s.	18/6 ea.
OC70	10/- ea.
OC71	10/- ea.
OC72	14/6 ea.
OC/72 matched pair	27/- pr.
OC73	12/6 ea.
OC77	18/6 ea.
NEWMARKET	
V6/2R R.F. up to 4 Mc/s.	19/6 ea.
V6/4R R.F. 4–8 Mc/s.	23/- ea.
V6/8R R.F. up to 8 Mc/s.	26/- ea.
Audio	
V10/15A	12/- ea.
V15/10P (Power)	15/- ea.
MAZDA	
XA104 R.F. up to 6 Mc/s.	18/- ea.
XA103 R.F. up to 4 Mc/s.	15/- ea.
XB104 Audio up to 1 Mc/s.	10/- ea.

Attractive discounts for bulk purchases. Let us have your enquiries.
(ALL POST FREE)

METERS. We carry large stocks of Meters from 25 microamps to 1,500 v. A few of the most popular types are: 25 microamps 2½in. Flush Round, 65/-; 100 microamps 2½in. Flush Round Moving Coil at 45/-; 500 microamps 2in. Flush Round Moving Coil at 18/6; 1 mA. 2in. Flush Square Moving Coil "Elliott" 1954 manf., 25/-; 50 mA. 2in. Flush Square Moving Coil 8/6; 1 mA. 2½in. Flush Round 35/-. Send stamp for complete list. We shall be pleased to quote for special meters to your own specification.

AERIAL TUNING UNIT ZA0841. This well made ex-W.D. unit contains a host of useful components including: 1 mA. 2in. flush round M/C meter, 1 mA. Westinghouse full-wave meter rectifier, 5-pole 5-way heavy-duty silver plated wavechange switch, 3in. dia. silver plated rotary tuning indicator, 350 pF. tuning condenser with insulated coupler and 3½in. calibrated dial (0–180 deg.) etc., etc. Contained in strong metal carrying case 9in × 9in. × 8in. with hinged lid. ONLY 27/6 plus 5/- C. & P.

No. 38 AFV WALKIE-TALKIE. A wonderful offer. This famous trans-receiver unit, with relay operated SEND/RECEIVE switch, covering 7.4–9 Mc/s band, range approx. 5 miles. Good condition. ONLY 22/6 plus 2/6 P. & P. per unit (less accessories). Quantity Export inquiries welcomed.

AMPLIVOX HEADSET SPECIAL. (Not surplus.) As used in up-to-date ships, aircraft etc. Excellent quality super lightweight low impedance magnetic headphones complete with button microphone attached and plastic ear moulds. Absolutely brand new. 45/- pair. Plus 1/6 P. & P.

ALLAN DOUGLAS ELECTRONIC ORGAN
Readers will no doubt be pleased to know that our working model of this amazing organ for home construction, may now be heard and seen, at our Hi-Fi Showroom in Tottenham Court Road, W.1. For the benefit of constructors all components, keyboards, chokes, etc. are available ready made. Full constructional details are available in book form at 15/- plus 1/6 p. and p. We shall be happy to forward a complete price list on receipt of a stamp. Please address all organ enquiries for the attention of Mr. L. Roche.

CLYNE RADIO LTD.
162 Holloway Road, London, N.7
and
18 Tottenham Court Road, London, W.1.

ALSO SEE PAGE 134 135

25,000 OHMS PER VOLT TESTMETER

Made by TRIPLETT of America. Size 7¾ × 6½ × 6⅜in., and incorporates a uniuqe tilting bakelite container size 5¼ × 3½in., which has two meters, a 25,000 ohms per volt moving coil for D.C. measurements, and a first grade moving iron for A.C. Reads Resistance up to 40 Megohms, A.C. & D.C. volts to 1,000, D.C. current to 250 mA., and also has 0-50 Microamps range. Facilities for measuring Condenser Capacity, etc., and Audio Output. Completely portable, with protective face cover. Complete with leads, batteries, and instructions. Fully reconditioned. ONLY £10/10/- (post, etc., 3/6).

UNIVERSAL AVOMETER 34 RANGE MODEL D

Ex-Air Ministry, but thoroughly reconditioned and checked. Supplied with internal batteries and instructions. Covers ranges as follows:

D.C. VOLTS	A.C. VOLTS	D.C. Current	A.C. Current
150 mV.	7.5 v.	15 mA.	75 mA.
300 mV.	15 v.	30 mA.	150 mA.
1.5 v.	75 v.	150 mA.	750 mA.
3 v.	150 v.	300 mA.	1.5 amp.
15 v.	300 v.	1.5 amp.	7.5 amp.
30 v.	600 v.	3 amp.	15 amp.
150 v.	750 v.	15 amp.	
300 v.	1,500 v.	30 amp.	Resistance
750 v.			1,000 Ω
1,500 v.			10,000 Ω

ONLY £8/19/6 (Postage, etc., 3/6).

CANADIAN MOVING COIL PHONES. Low-resistance, fitted noise-excluding chamois ear muffs, and leather covered head-band. Lead terminates to jack plug. BRAND NEW. ONLY 19/6 (Post 1/6).

POWER UNITS TYPE 234

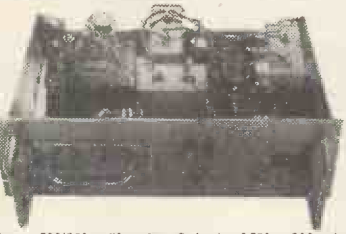

Primary 200/250 v. 50 cycles. Outputs of 250 v. 100 mA., and 6.3 v. 4 amps. Fitted double smoothing. For normal rack mounting (or bench use) having grey front panel size 19in. × 7in. BRAND NEW. ONLY 59/6 (carriage, etc., 7/6).

CRYSTAL CALIBRATOR No. 10

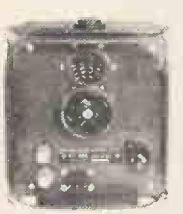

A superb Crystal Controlled Wavemeter just released by the Ministry of Supply. Has directly calibrated dial for nominal coverage of 1.5-10.0 Mc/s. but may actually be used from 500 kc/s. up to 30 Mc/s. Complete with 500 kc/s. Crystal, 2 valves type IT4, 1 or 1R5 and 1 of CV286 (Neon Stabiliser), and Instruction Book. Size 7in. × 7½in. × 4in., weight 5lb. Used but in first class condition. ONLY £2/19/6. Carr. 3/6.

12 VOLTS AMERICAN DYNAMOTOR. Delivers 220 volts at 100 mills. Size 5¼ × 3½in. diameter. Ideal for running Radio and Electric Shaver, etc., from car battery. ONLY 32/6.

EHT TRANSFORMERS. 5.5 kV. (Rect.) with 2 v. 1 a., 79/6. 7 kV. (Rect.) with 2 v. 1a., 89/6. 2.5 kV. (Rect.) with 2-0-2 v. 1.1 a., 2-0-2 v. 2 a. (for VCR 97 tube, etc.), 47/6 (postage 2/- per trans.).

6 v. VIBRATOR PACKS. Output approx. 130 v. at 30 mA., fully filtered and smoothed. Complete, ONLY 12/6. (Post 2/6.)

HIGH FREQUENCY A.C. VOLTMETER

A First Grade Moving Iron Instrument with 6in. Mirror Scale, reading up to 150 volts A.C. at 400 and 1,200-2,400 cycles. In substantial Oak case with removable lid, overall size 8½in × 8½in. × 5½in. Recently made for the Air Ministry, by Everett Edgcumbe, and in perfect order. Brand New & Unused. ONLY £7/10/-. Can also be supplied for 50 cycles, use either 0-150 or 0-300 volts.

TAPPED TRANSFORMER. Normal primary, delivering 30 v. 2 amps., which is tapped to obtain 3 v., 4 v., 5 v., 6 v., 8 v., 9 v., 10 v., 12 v., 15 v., 18 v., 20 v., 24 v. ONLY 20/-. (Post 2/6.)

HETERODYNE FREQUENCY METERS TYPE LM14

Frequency range 125-20,000 kc/s. in 2 bands. This is the United States Navy model of the well-known BC.221 Frequency Meter, but have many additional features which increase their usefulness. Voltage stabilisation circuits and Crystal control ensure extreme accuracy, and in addition they are fitted with an Internal Modulation switch to allow use as a Signal Generator. Size only 8½in. × 8in. × 8½in. Full information on request.

RCA 8in. P.M. SPEAKER

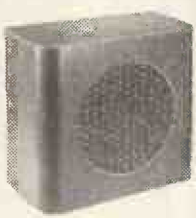

In heavy black crackled metal case, designed for use with AR 88 Receiver, or any set with 3 Ohms Output. BRAND NEW IN MAKERS' CARTONS ONLY 45/- (Post 3/6).

AR88 LF RECEIVERS

Reconditioned as new, and in perfect order. Frequency coverage 75-150 kc/s. and 1.2-30 Mc/s. ONLY £50 (carriage 25/-).

OSCILLOSCOPE No. 11

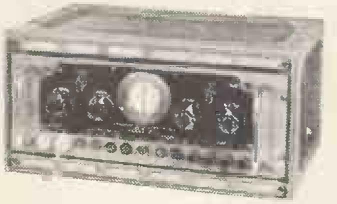

Made by A. C. Cossor. Incorporates Hard Valve Time Base with speeds of 1-5-40 milliseconds, but simply converted to produce 3 cycles per second to 30 kc/s. Controls include Fine and Coarse Gain, Brightness, Focus, X and Y shifts. Has Power Pack for nominal 115 v. and 230 v. A.C., with adequate fuse protection. Employs 2¾in. tube type ACR10. Grey and black engraved front panel, size 19in. × 7in. For standard rack use if required, depth of unit being 12in. In steel transit case as illustrated. Complete with leads and suggested modification data. BRAND NEW. ONLY £12/10/- (carriage 15/-).

CARRYING CASES, solid leather BRAND NEW. Internal dimensions 8½in. H. × 8½in. W. × 4½in. D. Fitted lock and key, and shoulder strap. Ideal for Test Instrument, Camera and accessories, etc. ONLY 35/- (postage 2/-).

AMPLIFIER N24

Utilises 4 valves, 1 each 5Z4G, 6V6G, 6J7G, 6J5G and high quality components such as "C" Core Transformers and Block Paper Smoothing Condensers. A.C. Mains Pack for nominal 110/230 volts. Provision for 600 ohms or High Impedance Input. Output to 600 ohm Line. For normal use only requires changing Output Transformer. Output approximately 4 watts. Designed for Standard Rack Mounting, having grey front panel size 19in. × 7in. All connections to rear panel, front having "On/Off" Switch, Gain Control, Indicator Light, Fuses and Valves Inspection Panel. BRAND NEW IN MAKER'S PACKING. ONLY £4/9/6 (carriage 10/6).

"Q FIVER" COMMAND RECEIVER.

The famous American BC 453 covering 190-550 kc/s. I.Fs being 85 kc/s. Complete with all 6 valves and circuit. Size 11 × 5½ × 5in. BRAND NEW IN MAKER'S CARTONS. ONLY 89/6 (Post 3/6).

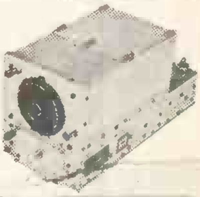

TCS RECEIVERS

The renowned American set designed by Collins for static or mobile use. Coverage 1.5-12.0 Mc/s. in 3 bands. Complete with all 7 valves. Power required 12 v. L.T. and 225 v. H.T. Size 11in. × 13in. × 11in., in black crackled case. IN NEW CONDITION. ONLY £10/10/- (carriage 15/-).

10,000 OHMS PER VOLT TESTMETER

This latest Caby model is a handy pocket sized tester 5⅜in. × 3½in. × 2⅛in. Reads low D.C. voltages at 10,000 ohms per volt, up to 1,000 v. A.C. and D.C. at 4,000 o.p.v. Resistance to 20 megs., D.C. current to 250 milliamps, and also Decibels. Complete with Test Leads, Batteries, and Instruction Book. ONLY £6/10/-.

MAINS ISOLATING TRANSFORMER. Manufactured by Vortexion. Fully shrouded. Will provide true 1:1 Ratio from nominal 230 v. Primary. Rated at 100 watts. BRAND NEW. ONLY 22/6 post 2/6).

Cash with order please, and print name and address clearly

PLEASE ADD POSTAGE OR CARRIAGE COSTS ON *ALL* ITEMS

HARRIS ELECTRONICS
(LONDON) LTD.

Radio Corner, 138 Gray's Inn Road, London, W.C.1. Phone: TERMINUS 7937

Open until 1 p.m. Saturdays. We are 2 mins. from High Holborn (Chancery Lane Station) and 5 mins. by bus from King's Cross

VALVES

Brand new, individually checked and guaranteed

AC/DD	2/6
AC/P	4/6
AC/P1	2/6
AC5PENDD	4/-
AC6/PEN	5/-
AC/SP3	4/6
AL60	6/-
AR6	2/6
AR8	5/-
ARDD5	2/-
ARP3	3/-
ARP4	3/6
ARP12	2/9
ARP21	5/6
ARP24	3/6
ARP34	4/6
ATP4	2/9
ATP7	5/6
AU1	5/-
AU4	5/-
AW3	4/-
BL63	6/-
BT45	40/-
BT9B	40/-
D41	3/3
D42	4/-
D77	4/3
DA30	12/6
DD41	4/6
DET5	15/-
DET18	30/-
DET19	2/6
DET20	2/6
DH76	4/9
E1323	25/-
EA50	1/6
EAC91	4/6
EB34	1/6
EBC33	6/-

EC52	3/-
EC54	3/6
ECC32	4/-
ECC81	6/6
ECC82	6/9
ECC83	7/-
ECC84	7/9
ECC91	4/-
ECL80	9/6
EF22	7/3
EF32	5/-
EF36	3/6
EF39	4/6
EF50	2/6
EF52	5/-
EF54	3/6
EF55	6/-
EF70	4/-
EF80	6/9
EF85	6/10
EF89	8/9
EF91	4/10
EF92	5/-
EL32	3/9
EL35	9/-
EL84	8/3
EL91	7/6
EM4	4/-
EY91	3/6
EZ40	7/-
EZ80	7/6
FW4/500	6/6
H30	5/-
H63	3/6

HP4101	6/-
KBC32	5/-
KF35	5/-
KT2	4/-
KT31	8/-
KT33C	7/-
KT44	9/-
KT241	9/-
KTW63	6/6
L30	4/-
MH4	3/6
ML4	4/-
ML6	6/-
MS/PEN	6/-
MS/PENB	6/-
MS/PEN/T	6/-
N34	8/-
NR15A	3/-
NT37 (4033A)	10/-
OD3	5/-
OZ4	5/-
OZ4A	5/-
P61	2/6
PCC84	8/-
PCC85	8/-
PEN25	4/6
PEN46	5/6
PEN65	6/6
PEN141	4/-
PEN220A	3/-
PEN1340	6/-
PENDD/1360	9/6
PL81	11/-
PL82	8/-

PL83	9/-
PM4DX	3/-
PT25H	7/6
PY82	8/-
QP21	6/-
QP25	5/3
QS75/20	6/9
QS95/10	6/9
QS108/45	6/9
QS150/15	6/9
R10	12/6
REL21	25/-
RG1-240A	17/6
RG3-250	17/6
RG4-1250	9/-
RK34	2/6
RL37	3/6
SP2	4/-
SP4B	7/6
SP13C	4/6
SP41	2/6
SP61	2/6
SP210	4/-
SU2150A	4/9
T41	19/-
TP25	15/-
TT11	3/-
U18	6/-
U19	7/-
U27	8/-
UL84	8/6
UL85	7/-
UU4	4/6
V2D33B	8/-
VP23	3/6
VR78	4/-
VR99	8/-
VR105/30	7/6
VR150/30	7/3
VS110	4/-
VT25	8/6
VU111	3/-
VU120	3/3
VU133A	3/-
W31	7/-
W42	7/-

Y63	5/-
Y66	8/-
Z31	6/-
1A3	3/6
1A5GT	5/-
1C5GT	7/6
1D8GT	6/-
1E7GT	7/6
1L4	3/9
1LDS	3/6
1R5	6/9
1S5	6/-
1T4	4/-
2A3	8/-
2A6	7/-
2C34	2/6
2D4A	4/-
2X2	4/-
3A4	6/-
3B24	3/-
3E29 (829B)	60/-
3Q5GT	9/-
4A1	4/6
4D1	2/6
5U4G	5/-
5V4	7/-
5Y3GT	6/9
5Z3	8/6
5Z4G	8/-
6A6	5/-
6AB7	5/-
6AC7	4/3
6AG5	4/6
6AG7	8/-
6AJ7	4/3
6AK6	7/6
6AK7	8/-
6AM5	5/-
6AM6	6/3
6B4G	4/6
6B8	5/6
6B8G	2/6
6C4	4/-
6C5	6/-
6C6G	4/6

6C8G	5/-
6F5G	5/6
6F6	7/-
6F8G	6/6
6F12	4/6
6G6G	3/-
6H6M	2/-
6H6GT	1/9
6J5	3/6
6J6	4/3
6K6GT	6/6
6K7G	2/3
6K7GT	5/3
6K8G	6/6
6L5G	6/-
6L6	9/-
6L6G	6/6
6L34	4/6
6N7GT	7/-
6Q7G	6/3
6R7G	7/6
6SA7	6/-
6SC7G	5/6
6SC7GT	6/-
6SG7	5/-
6SH7	5/-
6SJ7	6/9
6SJ7G	6/6
6SK7	5/6
6SL7GT	6/9
6SN7GT	4/6
6SQ7	6/6
6SR7	6/6
6SS7	5/-
6V6G	5/6
6V6GT	6/-
6X5GT	6/6
8D2	2/6
9D2	3/-
12A6	5/-
12AH7	7/-
12AT7	6/6
12AU7	6/9
12AX7	7/-
12C8	7/6
12E1	22/6

12H6	2/-
12J5GT	3/6
12SC7	4/6
12SG7	6/6
12SH7	4/9
12SJ7	6/-
12SK7	5/-
12SL7	7/-
12SR7	6/-
15D2	6/-
15E	8/-
15R	7/6
30	5/-
35T	30/-
35Z4GT	7/-
39/44	6/-
53A	3/-
58	6/-
59	6/-
71A	4/6
77	6/-
80	6/3
82	8/-
83	9/6
83V	12/-
84	12/6
89	6/-
210LF	3/-
210VPT	2/6
217C	17/6
220VSG	3/-
446A	14/-
446B	14/-
705A	17/6
715B	97/6
717A	8/6
801	6/-
803	22/6
805	30/-
807 AMER	5/3
807BR	3/9
808	8/-
813	70/-
815	80/-
816	30/-
829A	30/-

833A	£14
843	7/6
866A	10/-
872A	35/-
930	8/-
954	2/-
956	2/-
1619	5/-
1625	6/-
1626	4/6
1629	4/6
4242A	6/-
7193	1/9
7475	5/-
8010AR	22/6
8013A	10/-
8020	6/-
9001	5/-
9003	5/6
9004	4/-
9006	4/-

Cathode Ray Tubes:

3BP1	25/-
5BP1	35/-
5CP1	42/6
5FP7	45/-
PG7/5	15/-
VCR517	10/-
VCRX258 (with scanning coil)	45/-

Special Valves:

2J31	45/-
3A/1481	45/-
3J/170/E	£35
3J192/E	£37/10
723AB	52/6
726A	27/6
ACT25	40/-
CV691	60/-
KR3	45/-
VX7110	15/-
WL417A	15/-

AND MANY OTHERS IN STOCK including Cathode Ray Tubes and Special Valves.

All U.K. orders below 10/- P. & P. 1/-; over 10/-, 1/6; orders over £2 P. & P. free. C.O.D. 2/- extra. Overseas postage extra at cost.

BRAND NEW ORIGINAL SPARE PARTS FOR AR88 RECEIVERS.

TUNING MECHANISM. (Gear) £2/10/- post free.

Please write your other requirements.

TRANSCEIVERS 68T 3-5 mc/s. together with aerial rods, microphones, H.R. headphones, Key in full working order. £6/15/-. P. & P. 5/-.

FAMOUS U.S.A. FIELD TELEPHONES in canvas or leather case, type EE8 £9 per pair post free.

I.F. TRANSFORMERS. 4-5 Mc/s. American made in black crackle finish housing, 6/-. P. & P. 1/-.

HRO MAINS power pack, input 115/250 v. A.C. Output 250 v. 75 mA. and 6.3 v. 3.5 amps. £3, inc. carr.

VARIOMETERS for W/S No. 19. Fully tested and working 12/6. P. & P. 2/6.

COMPLETE V.F.O. UNIT from TX53. Freq. range in 4 switched bands from 1.2-17.5 mc/s. Two V.T. 501s. as oscillator and buffer, 807 as driver, two S130s as voltage stabilizers. Output sufficient to drive two 813s in parallel. Slow motion drive directly calibrated in mc/s. Provision for crystal control, metering of buffer and driver stage. Power requirements 400 v. and 6.3 v. D.C. Can also be used as low power transmitter. In excellent condition with valves and circuit diagram. £5. P. & P. 15/-.

FILAMENT TRANSFORMERS. Primary 0-190-210-230-250 v., 50 c/s. Sec. 1. 2.5 v. C.T. at 10 amps. 2. 2.5 v. CT at 10 amps. 3. 10.5 v. CT at 11 amps., 4,000 v. insulation. Price £2/19/-. P. & P. 5/-. Primary 0-190-210-230-250 v. 50 c/s. Sec. 1. 10 v. CT at 4.5 amps. 2. 10 v. CT at 4.5 amps., 4,000 v. insulation. £1/16/-. P. & P. 5/-. Primary 230 v. 50/60 c/s. 67 v/amps. Sec. 1. 6.3 v 1-6 amps. 2. 6.3 v. CT 3 amps. 3 6.3 v. CT 3 amps. 4. 6.3 v. CT 3 amps. £1/12/-. P. & P. 5/-.

Signal Generator Type TS.14/AP. 3,200-3,370 Mc/s. Fully guaranteed, £85.

Low Resistance Headphones, brand new, type CLR, 5/-; Balanced Armature, 7/6. P. & P. 1/-.

Vacuum Condenser. 32,000 v. 50 pF., 15/-. Post free.

DRIVER TRANSFORMERS. Primary 500 ohms imp. Sec. to match two 805 in push-pull £1/7/6. P. & P. 5/-.

TRANSFORMERS. Relay supply. Primary 230 v. Sec. 0-27/29/31 v. at 0.5 amps., 15/-. P. & P. 5/-.

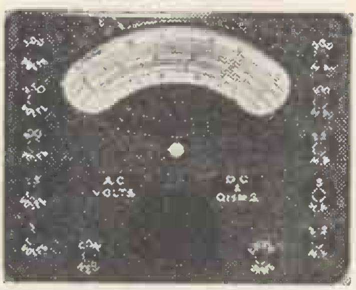

AVOMINORS in leather case with leads. Fully tested and guaranteed, with batteries. AC/DC volt range to 500 v., £3/19/6; as above, 2,000 v. D.C. only £3/19/6. P. & P. 2/6. either.

NON-INDUCTIVE CARBON RESISTANCE. 800 ohms, about 30 watt, 1in. dia., 10in. long, 7/6. P. & P. 1/6.

813 Ceramic Valveholders 3/- each. P. & P. 1/6.

Mains Power Supply Unit for No. 19 wireless set. Made by RCA of Canada. 115 v. A.C. Brand new, £15. P. & P. £1.

ROTARY TRANSFORMERS. 171 watt 12 v. input. 1,600 v. 110 mA. output, 30/-. P. & P. 7/6.

MARCONI SIGNAL GENERATOR. TF144G 85 kc/s., 25 Mc/s. Made up to new standard. £70, delivered free.

COMPLETE SET OF STRONG AERIAL RODS (American). Screw-in type MP49, 50, 51, 52, 53, total length 15ft. 10in., top diameter 0.615in., bottom diameter 0.185in. together with matched aerial base. MP37 with ceramic insulator, ideal for car or roof insulation, £2/10/-, post free.

TELESCOPIC AERIAL MASTS. 7 sections, total 11 yards. Immediate erection £4/10/- each or £8 per pair. Post free.

LIGHT HEADGEAR ASSEMBLY. Ideal for mobile use. Headphone 600 ohms, carbon microphone. 18/-. P. & P. 3/-.

AR88D and I.F. Receivers, completely overhauled and tuned, £60 and £57/10/- respectively. Completely rebuilt with P.V.C. wiring £85.

Modulation Transformers (U.S.A., Collins), primary imp. 6,000 ohms. C.T., secondary 6,000 ohms, 20 W., 9/6 each, post free.

Microphone Transformers. Balance input 30 or 250 ohms. U.S.A. manufacture, 7/6. P. & P. 1/6.

R109 Receiver. Covering 2-8 Mc/s. 6 v. D.C. New and tested, £4/5/-. Carriage paid.

R109A Receiver. Covering 2-12 Mc/s. 6 v. D.C. New and tested £5/5/-. Carriage paid.

SCR 522 TRANSMITTER (BC624) including all valves, 22/6. P. & P. 5/-.

SCR 522 RECEIVERS (BC624), 100-156 Mc/s. including all valves, 25/-. P. & P. 5/-.

VIBRATOR UNIT. 12 v./160 v. 35 mAmps. Exceedingly well filtered and smoothed, excellent for car radios. New, including one 6X5G valve and vibrator. 17/6. P. & P. 5/-.

CARBON INSET MICROPHONE. G.P.O. type 2/6. P & P. 1/-.

P. C. RADIO LTD.

170, GOLDHAWK RD., W.12 SHEpherds Bush 4946

PERSONAL CALLERS WELCOME

MULLARD DESIGNS *Still by far the finest value*

COMPLETE KIT OF PARTS

Designed by MULLARD—presented by STERNS strictly to specification

MULLARD "5-10" MAIN AMPLIFIER

For use with the MULLARD 2 stage preamplifier (described below) with which an undistorted power output of up to 10 Watts is obtained. This combination is throughly recommended for "Hi-Fi" enthusiasts who contemplate a versatile and very high quality home installation. We supply SPECIFIED COMPONENTS AND NEW MULLARD VALVES including PARMEKO MAINS TRANSFORMER (which has extra Power available to drive Radio Tuner) and the choice of the latest Ultra-Linear PARMEKO or the PARTRIDGE Output Transformer.

Price: COMPLETE KIT (Parmeko O/put Trans.) **£10.0.0**

Alternatively we supply ASSEMBLED AND TESTED **£11.10.0**

ABOVE INCORPORATING PARTRIDGE OUTPUT TRANSFORMER £1/6/0 extra

MULLARD'S PRE-AMPLIFIER TONE CONTROL UNIT

Employing two EF86 valves, and designed to operate with the Mullard 3-3 and 5-10 MAIN AMPLIFIERS, but also perfectly suitable for other makes.

Our kit is strictly to MULLARD'S SPECIFICATION and incorporates:

- Equalisation for the latest R.I.A.A. characteristics.
- Input for Crystal Pick-ups, and variable reluctance magnetic types.
- Input. (a) Direct from High Imp. Tape Head. (b) From a Tape Amplifier or Pre-Amplifier.
- Sensitive Microphone Channel.
- Wide range BASS and TREBLE Controls.

Price: COMPLETE KIT OF PARTS **£6.6.0** Alternatively we supply ASSEMBLED AND TESTED **£8.0.0**

(Carriage and Insurance 5/- extra.)

MULLARD 3-3 MAIN AMPLIFIER

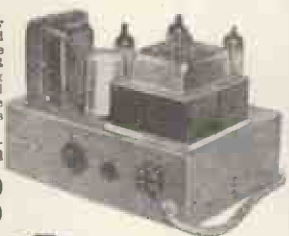

Based entirely on the very popular "3-3" model and designed to operate with the 2-stage PRE-AMPLIFIER (shown here) thus providing all the facilities associated with the more expensive "Hi-Fi" equipment. We recommend it as the IDEAL SMALL HOME INSTALLATION where very high quality is desired at the lower volume level (up to 3 watts).

We supply completely to MULLARD'S SPECIFICATION INCLUDING the latest PARMEKO Output Transformer, specified Valves and Components. Has Power available to drive a Radio Tuning Unit.

Price for COMPLETE KIT OF PARTS **£7.0.0**

Alternatively we supply ASSEMBLED AND TESTED **£8.0.0**

(Carriage and Insurance 5/- extra.)

SPECIAL PRICE REDUCTIONS

(a) The COMPLETE KIT OF PARTS to build both the "3-3" Main Amplifier and the 2-Stage Pre-Amplifier Control Unit **£12.10.0**

(b) The "3-3" and the 2-Stage Pre-Amplifier both Assembled and Tested **£15.0.0**

H.P. TERMS: Deposit £3 and 12 months of £1/2/-.

(c) The COMPLETE KIT OF PARTS to build both the "5-10" Main Amplifier and the 2-Stage Pre-Amplifier Control Unit **£15.15.0**

(d) The "5-10" and the 2-Stage Pre-Amplifier both Assembled and Tested **£18.18.0**

H.P. TERMS: Deposit £3/16/- and 12 months of £1/7/8.

(e) The COMPLETE KIT OF PARTS to build the Dual Channel "3-3" Amplifier and the Dual Channel Pre-Amplifier Control Unit **£21.10.0**

(f) The Dual Channel "3-3" Amplifier and the Dual Channel Pre-Amplifier Control Unit both Assembled and Tested **£25.0.0**

H.P. TERMS: Deposit £5 and 12 months of £1/16/8.

(g) The COMPLETE KIT OF PARTS to build one "5-10" Main Amplifier (Parmeko Transformer) and the Dual Channel Pre-Amplifier Control Unit **£21.10.0**

(h) One "5-10" Amplifier (Parmeko Transformer) and the Dual Channel Pre-Amplifier both Assembled and Tested **£25.0.0**

H.P. TERMS: Deposit £5 and 12 months of £1/16/8.

(i) COMPLETE KIT OF PARTS to build Two "5-10" Main Amplifiers (incorporating Parmeko Output Transformers) and the Dual Channel Pre-Amplifier Control Unit **£31.0.0**

(j) Two "5-10" Amplifiers (Parmeko Output Transformers) and the Dual Channel Pre-Amplifier Control Unit both Assembled and Tested **£36.0.0**

H.P. TERMS: Deposit £7/4/- and 12 months of £2/12/-.

Carriage and insurance 7/6 extra

Prices quoted are subject to £1/6/- extra for Partridge Trans.

COMPLETE MULLARD 5-10 AMPLIFIER

The popular and very successful complete "5-10" incorporating Control Unit providing up to 10 Watts high quality reproduction. Input channels for high output pick-ups and all modern Radio Tuning Units only.

Specified Components and new MULLARD VALVES are supplied including PARMEKO MAINS TRANSFORMERS and choice of the latest PARMEKO or PARTRIDGE ULTRA Linear Output Transformers. Adequate power available to drive Radio Tuner. Price: COMPLETE KIT, Parmeko Transformer **£11.10.0**

Alternatively we supply ASSEMBLED AND TESTED **£13.10.0**

Hire Purchase (Assembled Amp. only). Deposit £2/14/-, 12 months at 19/10.

ABOVE incorporating PARTRIDGE OUTPUT TRANSFORMER £1/6/- extra.

COMPLETE MULLARD 3-3

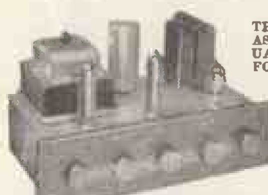

THE COMPLETE ASSEMBLY MANUAL AVAILABLE FOR 1/6.

A VERY HIGH QUALITY AMPLIFIER DEVELOPED FROM THE VERY POPULAR 3-VALVE 3-WATT AMPLIFIER DESIGNED IN THE MULLARD LABORATORIES.

Price for COMPLETE KIT OF PARTS **£7.10.0**

(Plus 6/6 carriage and insurance.)

Alternatively supplied ASSEMBLED AND FULLY TESTED (Plus 6/6 carriage and insurance) **£8.19.6**

H.P. Terms Deposit £2 and 8 monthly payments of £1.

Our kit is complete to the MULLARD specification including supply of specified components, valves and PARMEKO OUTPUT TRANSFORMER. We also include switched inputs for 78 and L.P. records plus a Radio position. Extra power to drive a Radio Tuning Unit is also available.

MULLARD—STERN STEREO DESIGNS

Model 3-3 M/S

DUAL "3-3" MAIN AMPLIFIER

Comprises two "3-3" MAIN AMPLIFIERS (described above) on one chassis and is designed to operate with our DUAL CHANNEL PREAMPLIFIER for both STEROPHONIC or MONAURAL operation.

Price: COMPLETE KIT OF PARTS **£10.0.0**

Alternatively ASSEMBLED AND TESTED **£11.15.0**

H.P. Terms Deposit £2/7/-, 12 months at 17/4.

Its output power is 6 Watts (3 watts per channel) and together with our PREAMPLIFIER provides a very acceptbale STEREO installation.

DUAL CHANNEL PRE-AMPLIFIER

This model incorporates two 2-Valve Pre-Amplifiers (described above) combined into a Single Unit enabling it to be used for both STEREOPHONIC or MONAURAL operation. It is designed primarily to operate with our range of MULLARD MAIN AMPLIFIERS but will also operate equally well with any make of Amplifiers requiring an input of 250 m/v.

Price: COMPLETE KIT OF PARTS ... **£12.10.0** Alternatively ASSEMBLED AND TESTED **£15.0.0**

H.P. Terms £3 Deposit and 12 months of £1/2/-.

Perfectly suitable for MONAURAL only operation, with one "3-3" or one "5-10" MAIN Amplifier to which the second Main Amplifier can at any time be added thus very easily providing for both STEREO or MONAURAL reproduction.

Recommended combination for STEREO operation.

(a) The DUAL CHANNEL PRE-AMPLIFIER together with the Dual "3-3" MAIN AMPLIFIER.

(b) The DUAL CHANNEL PRE-AMPLIFIER together with two "5-10" MAIN AMPLIFIERS. Assembly Manual is available for 3/- or send S.A.E. for Descriptive Leaflet.

When ordering please advise MAKE and MODEL OF AMPLIFIER in use.

COMPLETE STEREO AMPLIFIER

A thoroughly recommended design that very effectively meets the many requests for a low priced but good quality DUAL CHANNEL STEREOPHONIC AMPLIFIER.

Price: COMPLETE KIT OF PARTS **£8.10.0**

Alternatively ASSEMBLED AND TESTED **£10.10.0**

Two Mullard ECL 82 Triode Pentode Valves are incorporated in the design, they form a "CLASS A" single ended output stage in each channel. The input sensitivity is 300 m/volts, therefore when used with most STEREO Crystal Pick-Ups, or Radio Tuning Units, an output of 2 Watts per channel is achieved, or similarly when switched to MONAURAL Pick-up position a combined output of 4 Watts is produced.

Only New HIGH GRADE Specified Components and MULLARD VALVES are supplied in all these models.

Please enclose S.A.E. if ILLUSTRATED and DESCRIPTIVE LEAFLETS are required . . . alternatively the COMPLETE ASSEMBLY MANUALS containing component Price Lists and practical Drawings, etc., are available at 1/6 each.

STERN RADIO LTD. DEPT. W. 109 FLEET ST., LONDON, E.C.4

Telephone: FLEET STREET 5812/3/4

Each Model incorporates the highly successful HF/TR3 Amplifier (described opposite), thus ensuring truly "Hi-Fi" record and playback facilities.

All prices quoted provide for the COMPLETE RECORDER including CRYSTAL MICROPHONE and 1-200ft. Spool of Tape.

There are no "better value for money" Tape Recorders on the market—if you can't call and hear them—send S.A.E. for fully descriptive leaflets.

Stern's "fidelity" TAPE RECORDERS

BEFORE YOU BUY—YOU SHOULD HEAR THESE RECORDERS—THEY ARE COMPARABLE TO THE MUCH HIGHER PRICED MODELS

MODEL CR3/S. Incorporates the New COLLARO "STUDIO" TWIN TRACK 3-speed Deck **£41.0.0**
H.P. Terms: Deposit £8/4/- and 12 months of £3/0/2.

MODEL CR3/T. Incorporates the very popular 3-speed COLLARO Mk. IV "TRANSCRIPTOR" Deck, which has both upper and lower tape tracks **£49.10.0**
H.P. Terms: Deposit £9/18/- and 12 months of £3/12/7.

MODEL TR3/Mk. VI. Incorporates the New TRUVOX Mk. VI TWIN TRACK 2-speed Tape Deck **£49.10.0**
H.P. Terms: Deposit £9/18/- and 12 months of £3/12/7.

! ! RECORD PLAYERS ! !

The LATEST MODELS are in Stock. Many at REDUCED PRICES !!!
Send S.A.E. for ILLUSTRATED LEAFLET

B.S.R. MONARCH UA8 4-spd. Mixer Autochanger with Crystal Pick-up. **£6.12.6**

The COLLARO "CONQUEST" 4-spd. Autochanger, Studio "O" Pick-up. **£7.10.0**

The latest COLLARO "CONTINENTAL" 4-speed MIXER Autochanger, Studio "C" Pick-up.... **£8.10.0**

The NEW COLLARO model RP594, 4-speed Single Record Player, Studio Cartridge **£9.18.9**

The COLLARO model 4 564 4-speed Single Record Player, Studio Pick-up **£6. 6.0**

THE NEW B.S.R. model UA12 is in stock. A 4-"SPEED" MIXER AUTOCHANGER **£8. 7.6**

UA12 is also available incorporating the B.S.R. STEREO Pick-up, plays L.P. and 78 records **£10.10.0**

GARRARD RC121/4 4-speed Autochanger fitted with latest Crystal Pick-up **£10. 0.0**

The latest GARRARD TRANSCRIPTION MOTOR "301" with Stroboscopically marked turntable **£23.18.4**

The new GARRARD Model 4HF High Quality Single Record Player fitted with the latest T.P.A. 12 Pick-up arm and G.C.S. Crystal Cartridge **£18. 7.6**

GARRARD Model TA/MK. II Single Record Player fitted with high output Crystal Pick-up, detachable head **£8.10.0**

HIRE PURCHASE TERMS available on all units £8/19/6 and over. Carriage and insurance on each above 5/- extra.

STERN'S MK. II "*fidelity*" F.M. TUNING UNIT

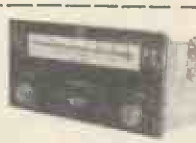

(Plus 5/- carr. and ins.) PRICE **£14.5.0**
HIRE PURCHASE: Deposit £2 and 12 months at £1/0/9. Incorporates the latest MULLARD PERMEABILITY TUNING HEART and the corresponding MULLARD VALVE LINE UP comprising ECC85, 2 type EF85s (or EF89s), EM84, Tuning Indicator, plus 2 type O.A. 79s Germanium Diodes. A really first-class Tuner very attractively presented and comparable to many offered at much higher prices. Power consumption is only 1.5 amps. at 6.3 volts and 25 m.a. at 250 volts.

HOME CONSTRUCTORS !

YOU CAN BUILD THIS TUNING UNIT FOR ONLY **£10.10.0**
(Plus 5/- carr. and ins.)
Please send S.A.E. for fully descriptive leaflet, or the Assembly Manual is available for 1/6.

! ! HOME CONSTRUCTORS ! !

A RANGE OF "EASY TO ASSEMBLE" PREFABRICATED CABINETS
Designed by the W.B. "STENTORIAN" COMPANY for "Hi-Fi" Loudspeaker systems or to accommodate high-quality equipment. The acoustically designed Bass Reflex Cabinets containing the very successful "Stentorian" Speakers give really first-class reproduction and are well recommended. Models are also available to accommodate high-quality Amplifiers, Preamplifiers, Tuning Units, Record Players, etc. All models are very easily assembled, in fact only a screwdriver is required.
Fully illustrated leaflets are available including complete specifications of the various STENTORIAN LOUDSPEAKERS. Please enclose S.A.E.

CAR BATTERY CHARGER

A COMPLETE KIT OF PARTS FOR ONLY **£2.19.6**
Will charge 6 or 12 volt batteries at max. 2½ amps. The design incorporates Reliant Resistor and Fuse and we supply complete with Metal Box container. EASY-TO-FOLLOW ASSEMBLY INSTRUCTIONS ARE INCLUDED.

SPECIAL CASH ONLY BARGAIN

A bulk purchase enables us to offer this very useful INTERCOM SET or BABY ALARM *For only* **£5.5.0**
Consists of MASTER UNIT (illustrated) and one EXTENSION, providing 2-way TALK-LISTEN facility. Complete in polished wood cases, size of each only 7¾ × 4¼ × 6in. high.

! ! RADIOGRAM CHASSIS ! !

ARMSTRONG MODEL A F 208 .... **£23.2.0**
Complete AM/FM chassis producing 5 watts. Separate Bass and Treble controls.

ARMSTRONG "STEREO TWELVE" **£37.16.0**
The most complete A.M./F.M. unit yet produced. For Stereo, giving 6 watts high fidelity push-pull output on each channel, 12 watts for Monaural

ARMSTRONG "JUBILEE" **£29.8.0**
An AM/FM chassis with nine valves and with push-pull output stage providing 6 watts.

ARMSTRONG AM/FM "STEREO 44" **£28.7.0**
Provision is made for Stereo and Monaural playback from pick-up or tape. Outputs provided for Stereo or Monaural tape recording.

RADIO TUNING UNITS

The JASON "MERCURY" Switched F.M. TUNER.
PRICE ASSEMBLED AND TESTED **£13.10.0**
Complete Kit of Parts £9/19/6.

DULCI Model FMT/2 .... **£19.17.6**
A complete self-powered FM Tuner incorporating automatic frequency control.

ARMSTRONG "S.T.3." AM FM Tuning Units **£27.6.0**
A self-powered high fidelity tuner covering full VHF, medium and long wavebands with automatic frequency control on VHF.

DULCI "H4/T" AM FM Tuning Units **£23.15.8**
A 4-waveband self-powered high fidelity tuner covering the VHF/FM transmissions plus the long, medium and short wavebands.

NEW HIRE PURCHASE TERMS are available on all above. Illustrated leaflets available—send S.A.E. (Carr. and Ins. 5/- extra.)

Hi-Fi LOUDSPEAKERS

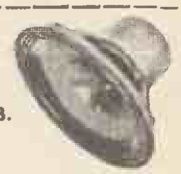

WE HAVE IN STOCK THE COMPLETE RANGE BY GOODMANS-WHARFEDALE-W.B.

And will be pleased to send you Illustrated and Priced Leaflets.

Recommended Types are:

GOODMANS "AXIOM 300." The best 12in. Seller. 15 ohms V/coil, Freq. Resp. 30 c/s., 16,000 c/s. **£11.5.9**

GOODMANS "AXIETTE" 8-inch (as illustrated). 3 or 15 ohms. Freq. Resp. 40-15,000 c/s. **£6.12.0**

W.B. "STENTORIAN" H.F.816, 8in., 3 or 15 ohms. Freq. Resp. 50-15,000 c/s. **£6.10.6**

W.B. "STENTORIAN" H.F.1016, 10in., 3 or 15 ohms. Freq. Resp. 30-15,000 c/s. **£7.12.3**

W.B. "STENTORIAN" H.F.1214, 12in., 15 ohms. Freq. Resp. 25-14,000 c/s. **£9.15.6**

WHARFEDALE "SUPER 8 FS/AL" 8in., 3 or 15 ohms **£6.19.11**

WHARFEDALE "GOLDEN FSB." 10in., 3 or 15 ohms Voice Coil .. **£7.13.3**

WHARFEDALE "W12/FS," 12in., 15 ohms Voice Coil **£10.5.0**

WHARFEDALE "SUPER 12/FS/AL," 12in., 15 ohms Voice Coil .. **£17.10.0**

LOUDSPEAKER ENCLOSURES—TWEETER UNITS—CROSSOVER UNITS *are also available.*

SPECIAL CASH ONLY OFFER !!

This very attractive PORTABLE AMPLIFIER CASE together with a good quality GRAM AMPLIFIER and a matched P.M. SPEAKER. ALL FOR ONLY **£8.7.6** (plus 7/6 carr. and ins.). The Amplifier consists of a 2-stage design incorporating the 3 modern BVA valves and has separate BASS and TREBLE CONTROLS. The Portable Case will also accommodate almost any make of Autochanger and is attractively finished in Grey colour Rexine—WE ALSO SUPPLY SEPARATELY:—

(a) The 2-stage (plus Rectifier) AMPLIFIER £4 2 6
(b) The PORTABLE CARRYING CASE £3 17 6
(c) 12in. P.M. SPEAKER 18 9
(Carriage and insurance 4/- extra)

STERN RADIO LTD. DEPT. W. 109 FLEET ST., LONDON, E.C.4
Telephone: FLEET STREET 5812/3/4

Stern's "fidelity" TAPE EQUIPMENT

A SELECTION OF HIGH FIDELITY PORTABLE TAPE PRE-AMPLIFIERS

Adds "Hi-Fi" Tape Recording to your existing Audio Installation.

IN ALL MODELS WE INCORPORATE THE

TYPE "C" PRE-AMPLIFIER

and offer it complete in portable case with . . .

(a) The new "COLLARO" STUDIO 3 speed Deck. Deposit: £7/6/-. 12 months £2/13/6	£36.10.0
(b) The COLLARO Mk. IV "Transcriptor" 3 Speed Deck. Deposit: £8/6/-. 12 months £3/0/11	£41.10.0
(c) The new TRUVOX Mk. VI Tape Deck. Deposit: £8/14/-. 12 months £3/3/10	£43.10.0
(d) The BRENELL Mk. V 3 Speed Deck. Deposit: £10/6/-. 12 months £3/15/7	£51.10.0
(e) The WEARITE MODEL 4A Tape Deck. Deposit: £12/4/-. 12 months £4/9/5	£61.0.0

STERN'S MULLARD TYPE "C" TAPE PRE-AMPLIFIER—ERASE UNIT

INCORPORATING THE NEW FERROXCUBE POT CORE PUSH-PULL OSCILLATOR and 3 SPEED TREBLE EQUALISATION by means of the latest FERROXCUBE POT CORE INDUCTOR.

PRICES . . . INCLUDING SEPARATE SMALL POWER SUPPLY UNIT

COMPLETE KIT OF PARTS **£14.0.0** ASSEMBLED AND TESTED **£17.0.0**

Deposit £3/8/- and 12 months of £1/4/11. Assembled unit only.

ALSO AVAILABLE EXCLUDING POWER SUPPLY UNIT FOR **£11.15.0** and **£14.10.0** respectively. (Carr. and Ins. 5/- extra)

Send S.A.E. for leaflet or 2/6 for Complete Assembly Manual.

WHEN ORDERING PLEASE STATE MAKE OF TAPE DECK TO BE USED

We present this "Hi-Fi" Pre-amplifier strictly to Mullard's specification etc., incorporating ONLY NEW HIGH GRADE COMPONENTS and the SPECIFIED NEW MULLARD VALVES. It comprises a COMPLETELY SELF-CONTAINED UNIT, all components and valves being contained in a well ventilated Box—Chassis neatly finished in Hammered gold with a very attractively engraved PERSPEX FRONT PANEL.

FOR PERMANENT HIGH QUALITY INSTALLATIONS WE ALSO OFFER (excluding Case) the following

(a) The COLLARO "STUDIO" TAPE DECK and our Mullard Type "C" PRE-AMPLIFIER and Power Unit Assembled and Tested. H.P. Terms: Deposit £6/10/- and 12 months at £2/7/8.	£32.10.0
(b) As above but TYPE "C" PRE-AMPLIFIER supplied as complete Kit of Parts	£29.0.0
(c) The COLLARO Mk. IV TAPE DECK and the MULLARD Type "C" Pre-amplifier and Power Unit assembled, tested. H.P. Deposit £7 and 12 months £2/11/4.	£35.0.0
(d) As in (a) above but the Type "C" supplied as COMPLETE KIT OF PARTS	£32.0.0
(e) The TRUVOX Mk. VI TAPE DECK and the assembled Type "C" Pre-amplifier and Power Unit. H.P. Deposit £8 and 12 months £2/18/8.	£40.0.0
(f) As above but the Type "C" supplied as complete KIT OF PARTS	£36.10.0
(g) The BRENNELL Mk. V Deck and the assembled Type "C" PRE-AMPLIFIER and POWER UNIT	£46.0.0
(h) As above, but the Type "C" supplied as complete KIT OF PARTS	£43.0.0
(i) The WEARITE 4A DECK with Type "C" assembled and tested. H.P. Deposit £11/4/- and 12 months £4/2/1.	£56.0.0

(Carriage and Insurance on above quotes 10/- extra)

STERN RADIO LTD.

DEPT. W 109 FLEET ST., LONDON, E.C.4

Telephone: FLEET STREET 5812/3/4

THE FINEST RANGE OF TAPE EQUIPMENT FOR THE HOME CONSTRUCTOR

YOU CAN BUILD A COMPLETE HIGH QUALITY TAPE RECORDER for £36.0.0

H.P. TERMS . . . Deposit £7/4/-, 12 months £2/12/10.

FOR THIS WE SUPPLY:—
COMPLETE KIT OF PARTS TO BUILD THE HF/TR3 TAPE AMPLIFIER.
THE NEW COLLARO "STUDIO" TAPE DECK.
PORTABLE CARRYING CASE (as illustrated)
ROLA/CELESTION 10in. x 6in. P.M. LOUDSPEAKER.
ACOS CRYSTAL MICROPHONE 1200ft. SPOOL E.M.I. TAPE.

Alternatively for those who prefer another type of TAPE DECK we will supply precisely as above—but IN PLACE of the COLLARO "STUDIO" DECK—WE INCLUDE:—

(a) The Mk. IV COLLARO "TRANSCRIPTOR" DECK... H.P. TERMS . . . Deposit £8, 12 monthly payments of £2/18/2 (£1 extra if we are required to wire up the Transcriptor Switch Banks).	£39.15.0
(b) The new TRUVOX Mk. VI DECK. H.P. TERMS: Deposit £9, 12 months of £3/6/- (Carr. and Ins. on all above is 12/6 extra).	£45.0.0

For constructors with their own Cabinet—WE OFFER:—

(a) COMPLETE KIT to build the HF/TR3 Amplifier, together with the COLLARO "STUDIO" DECK ...	£28.0.0
(b) As above but HF/TR3 ASSEMBLED and TESTED. H.P. TERMS: Deposit £6/6/-, 12 months of £2/6/2.	£31.10.0
(c) COMPLETE KIT to build the HF/TR3 together with the Mk. IV COLLARO "TRANSCRIPTOR" DECK (£1 extra if we are required to wire up Deck Banks)	£30.15.0
(d) As above but HF/TR3 ASSEMBLED and TESTED (£1 extra if we are to wire up Deck Switch Banks)	£34.10.0
(e) COMPLETE KIT to build the HF/TR3 together with the NEW TRUVOX Mk. VI TAPE DECK	£36.0.0
(f) As above but HF/TR3 ASSEMBLED and TESTED. H.P. Terms: Deposit £7/18/-, 12 months of £2/17/11.	£39.10.0
(g) COMPLETE KIT to build the HF/TR3 AMPLIFIER with the BRENELL Mk. V TAPE DECK	£41.10.0
(h) As above but HF/TR3 ASSEMBLED and TESTED. H.P. Terms: Deposit £9, 12 months of £3/6/-.	£45.0.0
(i) THE ASSEMBLED and TESTED HF/TR3 AMPLIFIER with the WEARITE MODEL 4A DECK, incorporates Wearite Head Lift Transformer, etc. H.P. TERMS: Deposit £11, 12 months of £4/0/8.	£55.0.0

(Carriage and Insurance on each above is 10/- extra.)

Attractive PORTABLE CASE is available to accommodate the TRUVOX or COLLARO TAPE DECKS and we offer it together with ROLA/CELESTION 10 x 6in. LOUDSPEAKER—ACOS CRYSTAL MICROPHONE—and 1200ft. SPOOL E.M.I. TAPE—ALL FOR **£9.0.0**
(Carriage and Insurance 5/- extra.)

WE HAVE THE NEW 2-SPEED TWIN TRACK

TRUVOX Mk. VI Tape Deck in stock £26.5.0 Deposit £5/5/-. 12 months £1/18/6

It incorporates PRECISION REV. COUNTER and PAUSE CONTROL and fully maintains the general high standard of all Truvox equipment. The very popular COLLARO Tape Decks and the BRENELL Mk. V Decks are also available.

THE MODEL HF/TR3 TAPE AMPLIFIER

Incorporating *3-SPEED TREBLE EQUALISATION by means of the latest FERROXCUBE POT CORE INDUCTOR.*

PRICE for COMPLETE KIT OF PARTS **£12/15/-**
FULLY ASSEMBLED AND TESTED **£16/10/-**

HIRE PURCHASE: Deposit £3/6/6 and 12 months at £1/4/2. A very high quality amplifier based on the very successful Type "A" design completed in the MULLARD LABORATORIES. ONLY NEW HIGH-GRADE COMPONENTS are incorporated including MULLARD VALVES and a GILSON OUTPUT TRANSFORMER . . . other features are: Magic Eye Recording Head Indicator—Effective Tone Control—Monitoring and Extension Speaker Sockets—has own Power Supply and can be used as independent Amplifier for direct reproduction of Gram. Records or from Radio Tuner. Overall size 11 x 6 x 6in.—Truvox—Collaro—or Brenell—please specify which. Send S.A.E. for leaflet or 2/6 for Assembly Manual.

PLEASE ENCLOSE S.A.E. WITH ALL CORRESPONDENCE

SCOPE FOR A BARGAIN

DOUBLE-BEAM OSCILLOSCOPE TYPE 13A

Made for the Ministry by leading manufacturers (e.g., Erskine & Hartley Electromotives) this fine instrument is suitable for the examination of waveforms from two cycles to ten megacycles. It is extremely well designed and incorporates such desirable features of construction as potted "C" core transformers and paper smoothing capacitors for complete reliability. No electrolytic condensors are used.

TIME BASE	2 cps. to 750 Kcs.
Y PLATE AMPS.	5 Mc/s. bandwidth (3 dB).
CAL. MARKERS	1μ sec. and 10μ sec.
SIZE & WEIGHT	13in. × 10in. × 22in. 58lbs.
EXTERNAL PROBE	For RF measurements
POWER SUPPLIES	Internal (AC mains)

All instruments are in first class condition and are carefully checked and tested before despatch. Mains connector, test leads, probe and circuit diagram are neatly contained in the detachable front cover.

£25 Carr. 30/-

VIDEO OSCILLATOR TF885A

Frequency coverage in two ranges: 25 cps. to 30 Kc/s. and 30 Kc/s. to 5 Mc/s. (sinewave) and 50 cps. to 150 Kc/s. (squarewave). Output 1 watt into 1000Ω sinewave) and 64 volt peak to peak (squarewave). Operates from A.C. mains. MODERN equipment in first class electrical and mechanical condition. £100 carr. paid.

SPECTRUM ANALYSER TF984/1

For viewing the spectra of "S" band transmitters in the range 2,900-3,150 Mc/s. These are in virtually new condition but are NOT tested. Operation is from 180 volts 500 cps. power supplies. £30 carriage paid.

MARCONI VIDEO OSCILLATOR TF410C

An earlier design of video oscillator having the same frequency coverage as the TF 885. The output meter is a circular 3½in. instrument. For AC mains operation. In good condition and working order. £35. Carriage paid.

MARCONI B.F.O. TF602A

Frequency range 10 cps. to 12,000 cps. Operation is from AC mains. Output indication by magic eye. Incorporates 50 cycles check. A reasonably compact instrument useful for general audio testing. Fair condition, tested and working perfectly. £6/19/6. Carriage 10/6.

MARCONI BRIDGE TF868

Measures L. C. & R. each in 7 steps; L. & C. at 1,000 c/s. and R at D.C. L: 1μH to 100H; C: $1\mu\mu$F to 100μF. R: 0.1Ω to 10MΩ. Power factor 0.001 to 0.995. AC mains operation. First class MODERN equipment in virtually new condition. Perfect working order. £65. Carriage paid.

FERRANTI TESTMETER TYPE Q

Volts 0 to 30, 150, 600 A.C./D.C. with additional 0-3 v. D.C. and 0-15 v. A.C. ranges; milliamps 0 to 7.5, 30, 150 and 750 D.C.; ohms 0-25K. Accuracy BSS 1st grade. 500 ohms per volt. With leads, prods, battery and instructions. In velvet lined 4×7×3in. case. Brand new condition, perfect working order 52/6. Post 2/6.

UNIVERSAL IMPEDANCE BRIDGE TF373

An excellent bridge of earlier design having an almost identical specification to the TF868. Those we offer are in very good electrical and mechanical condition and are in perfect working order. £35 carriage paid.

OUTPUT POWER METER TF340

Impedance from 2.5Ω to 20,000Ω in 40 steps. 100 W. to 5 watts. Four ranges 0-5 mW., 0-50 mW., 0-500 mW., and 0-5 Watts. First class condition. Tested. £9/19/6. Carriage 7/6.

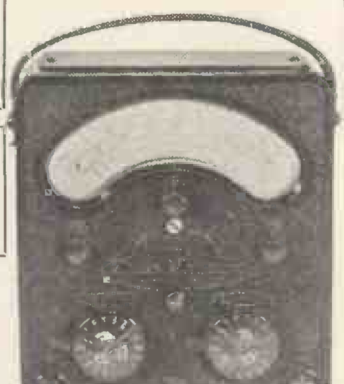

AVOMETER MODEL D.

£8.19.6 (*P. & P. 3/6*)

D.C. Volts	A.C. Volts	D.C. Current	A.C. Current
150 mV.	7.5 V.	15 m/A.	75 m/A.
300 mV.	15 V.	30 m/A.	150 m/A.
1.5 V.	75 V.	150 m/A.	750 m/A.
3 V.	150 V.	300 m/A.	1.5 Amps.
15 V.	300 V.	1.5 Amps.	7.5 Amps.
30 V.	600 V.	3 Amps.	15 Amps.
150 V.	750 V.	15 Amps.	
300 V.	1.5 KV	30 Amps.	Resistance
750 V.			0-1000 ohms.
1.5 KV			0-10 K ohms.

Thoroughly overhauled. Complete with batteries and instructions. An extremely robust meter at a very reasonable price.

G.E.C. SELECTEST DIII

This testmeter has exactly the same ranges as the Avo "D." The scale is even larger. Those we offer are in first class condition. completely overhauled and carefully tested prior to despatch. Complete with battery, test leads and instructions. £7/10/-. P & P. 3/6.

CHARLES BRITAIN (RADIO) LTD.

NEW—The "CONTINENTAL—6"

"For Style, Quality Performance and Value for Money"

COMBINED TRANSISTOR PORTABLE/CAR RADIO SUPERHET

SPECIFICATION

- ★ 195 to 560 metres on medium wave.
- ★ 1,150 and 1,800 metres on long wave.
- ★ 400 mW. push-pull output.
- ★ A.V.C. and Car radio. Standard Fitting.
- ★ Slow motion tuning.
- ★ HI-FI SPEAKER.
- ★ Double tuned IF's.
- ★ 6 months' battery life.
- ★ Resistor and Condenser leads pre-trimmed.
- ★ Printed circuit board marked with component numbers.
- ★ EDISWAN TRANSISTORS.

XA102, 2-XA101, XB103, 2-XC101, 2-DIODES.

TRANSISTOR "8"
STILL AVAILABLE AT £10-19-6 (pp. 2/6)
FREE BOOKLET ON REQUEST

TOTAL COST OF ALL SPECIFIED COMPONENTS INCLUDING CABINET, BATTERY, ETC., ONLY £11/10/-. P.P. 3/6.

All components available separately. Send for descriptive leaflet and prices.

A highly sensitive and selective portable fully tuneable on medium and long waves. Performs equally well as a car radio. Low running costs, good looks and ease of construction combine to produce a radio equal to any commercial receiver in the 20 gn. class.

★ Size 9½ x 7 x 3½.
★ Weight 4lb.

2-WATT POWER STAGE

For use with 'Continental.' Works from 12-volt supply. Overall size 4½ x 3¼ x 2½in. All parts with Power transistor, less speaker, 52/6. P.P. 2/-.

MAJOR—2
(2-Transistor Pocket Radio)

- ★ 4-stage reflex
- ★ Medium wave; tuneable
- ★ Very sensitive
- ★ No aerial or earth
- ★ Complete layout
- ★ Over 6 months on one battery.
- ★ 4½ x 3 x 1¼in.
- ★ Weight only 4 ozs.
- ★ Personal phone

TOTAL **69/6** POST 1/6

NEW BOOKLET FREE: All components sold separately

GOOD RECEPTION ANYWHERE!

MAJOR—3
(3-Transistor Radio)

- ★ 5-stage Reflex Circuit
- ★ No Aerial or Earth.
- ★ Min. Volume Control.
- ★ 3 Ediswan Transistors.
- ★ Medium Wave Tuning.
- ★ Size 4½ x 3 x 1¼in.
- ★ Personal phone.

(See "R.C." Sept., '59) All parts sold separately).

TOTAL **87/6** P.P. 1/6

RESULTS GUARANTEED ANYWHERE
NEW BOOKLET FREE

MINOR—1
(1-Transistor Radio)

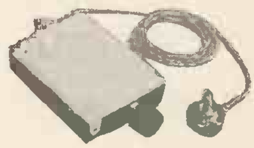

- ★ 3-stage Reflex
- ★ Medium wave
- ★ Ferrite aerial
- ★ Size 3 x 2 x ¾in.
- ★ Includes personal earphone
- ★ Layout diagrams

All components **49/6** P.P. 1/6

Free list on request

THE SMALLEST ON THE MARKET

"SUPER-SIX" Transistor Portable Superhet

- ★ Medium and Long Waves
- ★ 6 Mullard Transistors
- ★ Printed Circuit
- ★ Sensitive and Selective
- ★ Ferrite Rod Aerial
- ★ 3in. 150Ω Speaker
- ★ Full Assembly Instructions
- ★ Size 7in. x 2in. x 1¾in.
- ★ Trimming Tool supplied.

Complete set of parts including attractive cabinet
£9.10.0
P.P. 2/6
All parts sold separately

FREE LEAFLET

High sensitivity and selectivity combine to give excellent reception on both medium and long waves, this set is recommended by us as being one of the easiest-to-build printed circuit transistor sets ever offered. **LIMITED QUANTITY ONLY**

"PRACTICAL TRANSISTOR CIRCUITS"

A booklet produced for the home constructor containing transistor circuit diagrams, practical layouts, data and information. All components used are readily obtainable from us.

(1ST EDITION) **2/-** POST FREE

	ALL TRANSISTOR UNITS DESCRIBED	Total Cost	P.P.
1	Radio Control Receiver (27 Mc s)	50/–	1/–
2	R.F.I.F. Generator (450 kc/s to 3 Mc/s)	25/–	1/–
3	Light Operated Switch	27/6	1/–
4	Square Wave Generator (Audio)	20/–	1/–
5	Signal Tracer (Audio I.F. R.F.)	37/6	1/6
6	Hearing Aid Amplifier	95/–	1/–
7	3-Channel Audio Mixer	42/6	1/–
8	Audio Generator	25/–	1/–
9	Addon Amplifier (250mW power-stage)	59/6	1/6
10	2 Watt Power Stage (for Continental)	52/6	2/–
11	Baby Alarm—100% safe	92/6	2/–
12	Top Band Transmitter (1.8 to 2 Mc/s)	57/6	1/6
13	3 to 12 Mc/s Xtal Osc.	22/6	1/–
14	35-metre C.W. Transmitter	27/6	1/–

TO **HENRY'S RADIO LTD.**

Enclosed please find remittance value 2/- for "Practical Transistor Circuits," Radio Receiver Leaflets and Components Lists.

W.W.
NAME ....
(BLOCK CAPITALS, PLEASE)

ADDRESS ....

....

TRANSISTORS

FROM **5/-** EACH

SHORT-WAVE, R.F. AUDIO AND POWER

SB078	20 Mc/s	6mW	H.F.	10/–
SB305	25 Mc/s	10mW	H.F.	15/–
SB231	30 Mc/s	10mW	H.F.	22/6
SB231R	50 Mc/s	10mW	H.F.	30/–
XB104	1 Mc/s	120mW	Audio	10/–
XA104	6 Mc/s	90mW	Osc/Mix	18/–
XA103	4 Mc/s	90mW	RF, IF	15/–
XC121	—	200mW	Power	17/–
XC131 Matched pairs only		500mW		pr. 34/–
OC44	15 Mc/s	60mW	Osc/Mix.	26/–
OC45	6 Mc/s	60mW	RF, IF	23/–
OC71	600 kc/s	100mW	Audio	14/–
Red Spot	800 kc/s	125mW	Audio	5/–
White Spot	5 Mc/s	125 mW	RF, IF	7/6
Photo Transistor		100mW		10/–
V15/10P 10-watt Power				17/6

FREE DATA & COMPLETE LIST ON REQUEST. ALL GUARANTEED.

CRYSTAL MICROPHONE INSERTS

Acos and other well-known makes. Brand new.

1in. square	7/6
1¼in. square	7/6
1¼in. round	7/6
1½in. round	8/6
1¾in. round	14/–
2in.	12/6
¾in. square, ex-units	3/6

ALL GUARANTEED P.P. 6d. any type.

TRADE ENQUIRIES INVITED ON ALL ITEMS AND DO-IT-YOURSELF UNITS

HENRY'S RADIO LTD.

5, HARROW ROAD, PADDINGTON, W.2
OPEN MON.-SAT. 9-6, THURSDAY 1 O'CLOCK PAD 1008/9

VALVE VOLTMETER

Type 165-A

D.C. ELECTRONIC VOLTMETER.

6-Ranges. 0–3–10–30–100–300 and 1,000 volts. Input res: 11-meg. constant on all ranges. Sensitivity: 3,666,666 ohms per volt on 3 v. scale.

A.C. VOLTMETER.

5-Ranges: 0–10–30–100–300–1,000 volts. Sensitivity: 1,000 ohms per volt.

ELECTRONIC OHMMETER.

6-Ranges, from 0.1 ohms to 1,000 megohms. Movement. 200 microamperes. D.C. accuracy ±2%.

COMPLETE WITH INSTRUCTION BOOK AND TEST PRODS, BRAND NEW.

Input 110-250 volts A.C.

ONLY **£12/10/0** P.P. 3/6

SPECIAL PURCHASE - LIMITED STOCKS

T/X TYPES AND SPECIAL PURPOSE VALVES

EF91	5/–	705A	15/–	807	7/6	1625	5/–	5800	45/–
EF92	5/–	2C43	50/–	872A	15/–	8582	15/–	5829	10/–
813	65/–	725A	35/–	2K25	65/–	1B38	25/–	5839	35/–
832	30/–	726A	15/–	19G3	15/–	1632	6/–	5840A	30/–
832A	35/–	726B	15/–	WL860	30/–	1644	12/6	5852	22/6
829B	40/–	723A/B	55/–	TZ40	35/–	S638	15/–	5932	30/–
QVO4/7	15/–	2J54	35/–	CV129	45/–	5692	30/–	5931	35/–
TT15	45/–	803	22/6	CV2161	25/–	5703	8/6	6004	17/6
446A	12/6	805	35/–	CV100	15/–	5722	17/6	9005	15/–
446B	12/6	35T	15/–	CV85	15/–	5726	8/6	CK5785	8/6

NEW FREE LIST OF OVER 600 TYPES OF VALVES AND TUBES

V.H.F. TRANS/RECEIVER TYPE 1986

10-channel crystal controlled. 124.5 to 156 Mc/s. Nominal coverage 9.72 Mc/s. I.F., 23 kc/s bandwidth. Unit complete with 21 valves, 24 volt power unit, circuit diagrams, etc. £7/19/6, p.p. 10/6. Contained in metal case. New condition

V.H.F. TRANS/RECEIVER TYPE 1986

★ 9.72 MC/S I.F.
★ 23 KC/S BANDWIDTH
★ 10-CHANNEL CRYSTAL CONTROLLED
★ 124.5 to 156 MC/S COVERAGE

Sub-units	Type	With valves	Less valves	P.P.
TRANSMITTER	81	60/–	25/–	2/6
RECEIVER	114	25/–	7/6	2/6
IF Amplifier	476	32/6	12/6	2/6
Modulator	105	20/–	—	2/6
24 v. Rotary unit	3	15/–	—	2/6
10-way Control unit	382	6/–	—	9d.

All the above are in absolute new condition. Full circuits available, 1/9 post free.

MARCONI No. 19 SET CRYSTAL CALIBRATOR

CRYSTAL CONTROLLED OSCILLATORS: 10 Kc/s., 100 Kc/s. and 1 Mc/s. On/Off MODULATOR. With handbook. Unused. ONLY 79/6. P.P. 2/6.

QUARTZ CRYSTALS

FROM 5/- EACH

From 6 Kc/s-47 Mc/s. FT243, FT241, 10XJ and B7G. All types for all purposes. Send for free list.

WALKIE/TALKIE TYPE 38 TRANSMITTER/RECEIVER

Complete with 5 valves. In new condition. These Sets are sold without Guarantee, but are serviceable (7 to 9 Mc/s). 22/6. P.P. 2/6. Headphones 7/6 pair, Junction Box 2/6. Throat Mike 3/6. Canvas Bag 4/-. Aerial Rod 2/6.

R.C.A. SPEAKER

8in. P.M. in black crackle cabinet. For AR88 and all communications receivers. 45/- P.P. 2/6.

TRANSMITTER/RECEIVER

Army Type 17 Mk. II

Complete with Valves, High Resistance Headphones, Handmike and Instruction Book and circuit. Frequency Range 44.0 to 61 Mc/s. Range approximately 3 to 8 miles. Power requirements: Standard 120 v. H.T. and 2 v. L.T. Ideal for Civil Defence and communications.

BRAND NEW

45/- P.P. 5/-.

44-61 Mc/s. Calibrated Wavemeter for same, 10/- extra. P.P. 2/-.

A.C., D.C., R.F. METERS

0–15 v.	2½in.	M.I. (A.C) F.R.	8/6
0–40 v.	2in.	M.C. (DC) F.S.	7/6
0–150 v.	2½in.	M.C. (DC) F.R.	12/6
0–200 v.	2½in.	M.C. (DC) F.R.	12/6
0–600 v.	2½in.	M.C. (DC) F.R.	12/6
0–300 v.	5in.	M.I. (AC) P.	50/–
0–1½ kv.	2½in.	M.C. (DC) P.	15/–
0–2½ kv.	2½in.	M.C. (DC) P.	15/–
0–500 UA	3½in.	M.C. (DC) F.R.	59/6
0–400 UA	3½in.	M.C. (DC) F.R.	59/6
0–1 mA	2½in.	M.C. (DC) F.R.	22/6
2½–0–2½ mA	2½in	M.C. (DC) F.R.	12/6
0–100 mA.	2in.	M.C. (DC) F.S.	10/–
0–150 mA	2in.	M.C. (DC) F.S.	7/6
0–50' mA	2½in.	M.C. (DC) F.R.	12/6
0–750 mA.	2in.	T.C. (RF) P.	6/–
0–500 mA.	2in.	T.C. (RF) P.	6/–
0–1 amp.	2in.	T.C. (RF) P.	6/–
0–3 amp.	2in.	T.C. (RF) F.S.	6/–
0–12 amp	2½in.	T.C. (RF) P.	10/–
0–20 amp.	2in.	M.C. (DC) P.	7/6
0–30 amp.	2in.	M.C. (DC) F.S.	7/6
5–0–5 amp.	2½in.	M.C. (DC) P.	10/–
0–10 amp.	4in.	M.C. (DC) P.	25/–

FREE COMPLETE LIST ON REQUEST

TR 1920 TX/RX

4-channel Xtal controlled. 100 to 120 mc/s. New condition. £6/10/-, p.p. 10/6.

AVO MINOR TESTMETER

AC/DC volts.
0-500 volts.
D.C. mA.
0-500 mA.
RESISTANCE
0-20 K.

COMPLETE WITH LEADS AND LEATHER CASE **79/6** P.P. 2/-.
FULL GUARANTEE.

— PIRANI HIGH VACUUM TEST EQUIPMENT —

PIRANI CONTROL UNIT (1.2mA meter movement). (85/-, p.p. 5/-.)

PIRANI DIFFERENTIAL LEAK DETECTOR. (45/-, p.p. 5/-.)

PYE SCALAMP GALVANOMETER (Type 2000). (£15, p.p. 3/6.)

PIRANI GAUGE HEAD WITH CALIBRATOR

COMPLETE VACUUM TESTING EQUIPMENT (5 ITEMS AS SHOWN) NEW IN ORIGINAL CARTONS.

£25 - 0 - 0 p.p. 10/- *INCLUDING OPERATING INSTRUCTIONS*

(SPARE PIRANI GAUGE HEADS, EDWARDS TYPE M6, LESS CALIBRATOR, 15/- EACH.)

HENRY'S RADIO LTD.

5, HARROW ROAD, PADDINGTON, W.2
(AT JUNCTION OF EDGWARE RD. AND HARROW RD.) PAD 1008/9

HARVERSON SURPLUS CO LTD

Phone : THOrnton Heath 2577 48 BEDDINGTON LANE, CROYDON, SURREY. Phone : THOrnton Heath 2577

The world famous E.M.I. Angel Transcription P.U.

SPECIFICATION

Physical
Length 15⅞ inches (40.32 cms.)
Height 2½ inches (6.41 cms.)
Width 2⅜ inches (6.03 cms.)
Centre of base to stylus tip 12 inches (30.72 cms.). Approx. overall.

Stylus
A diamond stylus is fitted to the 33⅓/45 r.p.m. head supplied.

Head Impedance
1 ohm. (measured at 1,000 c.p.s.).

Frequency Response
For a constant recorded velocity the frequency response is sensibly level within the following limits; with micro-groove stylus. 20—16,500 c.p.s. With standard stylus 20—20,000 c.p.s.

Distortion
Measured at 400 c.p.s., the total harmonic distortion is less than 5% for a recording level of +20 db referred to 1 cm./sec. r.m.s. transverse velocity

Sensitivity
50 mV at secondary of transformer provided from a recording level of +10db referred to 1 cm./sec. r.m.s. velocity

Weight at Stylus Point
Variable from 3—10 grammes as required.

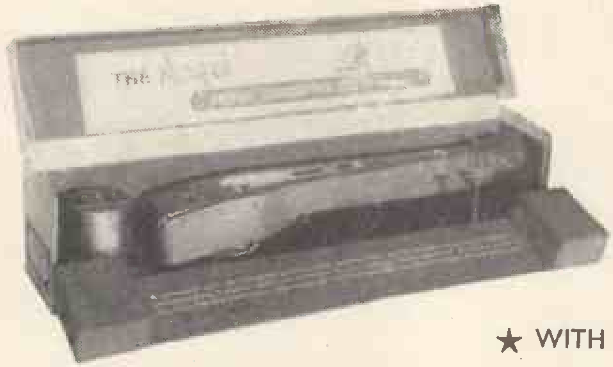

★ (MODEL 17A)

A PICKUP FOR THE CONNOISSEUR ORIGINALLY PRICED AT £17/10/- WE CAN OFFER THE LAST REMAINING FEW AT

£5.10.0

PLUS P. & P. 5/-.

★ WITH DIAMOND STYLUS

500 MICROAMETER

A 4½" Panel mounting 500 Microameter marked in ohms and ideal for building into a multi-range meter.

PRICE **£2.10.0**
Plus P. & P. 3/6.

PLESSEY TWEETER

This well-known Plessey 3 ohm Tweeter at our amazing price of . . .

10/6 TAX PAID
Plus P. & P. 1/6.

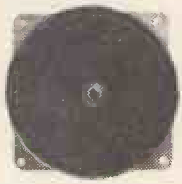

This cabinet as used by a world famous manufacturer. Cost nearly £30 to make. Will accommodate any type of equipment. Can also be used as a cocktail cabinet. Money refunded if not completely satisfied.

Legs for above if desired at per £1 per set.

Dimensions—Length 51½", Height 32½", Depth 17½" without legs—Legs 6".

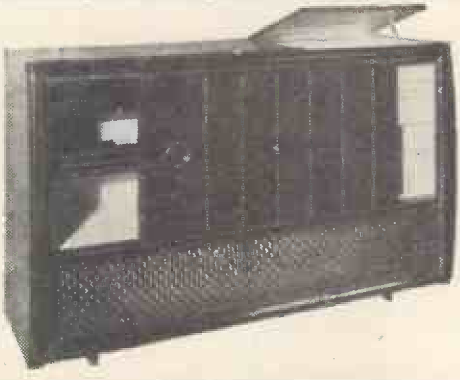

The cream of the Cabinet World

OUR PRICE
£18.10.0
Plus P. & P. 12/6.
Scotland & N. Ireland 25/-

Valve line-up

ECC83, EL84 x EL84, EZ80. Mullard Valves. Bass-Treble-Balance and volume on remote control panel. Fitted with elegant control knobs. Should not be missed.

Stereo Amplifier

This Stereo amplifier as illustrated. Made by a leading manufacturer, it is a robust precision-built job which we offer at the amazing price of . . .

£7.9.6 Plus P. & P. 3/6.

STOP PRESS
TRANSISTOR BY LEADING MANUFACTURER
FIRST GRADE EQUIVALENT OC44
11/6 EACH—60/- FOR 6

SPECIAL OFFER. LIMITED QUANTITY.

GENERAL PURPOSE CATHODE RAY OSCILLOSCOPE

The famous model 160-B C.R. 'Scope, manufactured by R.C.A. of U.S.A. Best general purpose instrument of its kind, complete with 6in. cathode ray tube. Unused, guaranteed perfect. For operation on 110 v. A.C. Price £22/10/-. Carr. 10/-.
Step-down transformer to enable the above to operate on 230 v. Price 19/6.

FRESHLY IMPORTED MINIATURE CONTACT COOLED RECTIFIERS

Half-Wave Type

Max. A.C. in 125 v. D.C. Out. 80 mA.	4/-
Max. A.C. In. 250 v. D.C. Out. 50 mA.	7/-
Max. A.C. In. 250 v. D.C. Out. 85 mA.	8/6

Television Type

Max. A.C. In. 250 v. D.C. Out. 300 mA.	18/6

Full-Wave Bridge Connected

Max. A.C. In. 250 v. D.C. Out. 75 mA.	9/6
Max. A.C. In. 250 v. D.C. Out. 150 mA.	15/-

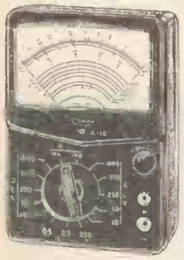

CABY MULTI-RANGE TEST METER. Freshly Imported. Guaranteed Model A-10. A.C./D.C. Voltages, sensitivity 2,000 ohms per volt. Ranges: 10, 50, 250, 500, 1,000 v. Resistance: 10K ohm and 1 megohm. D.C. Current: 0.5 mA. 25 mA., 250 mA. Decibel range. Accuracy: 2 to 3%. Price £4/17/6. P. & P. 1/6. Ask for leaflet fully illustrating and describing this and other models.

LEATHER CARRYING CASES FOR AVO MULTIMINOR WILL ALSO FIT MODEL A-10 ABOVE. NEW. Price 10/6 each. P. & P. 1/-.

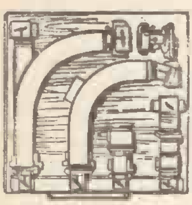

WAVE GUIDE 3 cm. mounted on a carrying board consisting of: (1) directional coupler. (2) 90 degree bend. (3) co-ax to wave guide adaptor type N. (4) British to W.916. (5) Co-ax to wave guide adaptor circular flange. (6) Circular to American adaptor. Complete in carrying case with coaxial cable. Price 60/-. Carr. 10/-.

AERIAL AS ILLUSTRATED. Ideal for Car. Overall length 33in., khaki, with flexible shaft which enables the aerial to be fixed firmly in any position. Price 8/6, plus P. & P. 1/6.

NEW WIRE WOUND RHEOSTAT ON CERAMIC. 58 ohm. 50 watt, complete with instrument knob. Price 8/6. P. & P. 1/6.

W. W. RHEOSTAT. New. 3.5K, 25 watts. Price 7/6. P. & P. 1/6.

W. W. RHEOSTAT. New. 5K, 25 watts. Price 7/6. P. & P. 1/6.

SLIDER RESISTANCE. 44 ohm. 1½ amp. Price 18/6. P. & P. 2/-.

EX P.O. MAGNETIC COUNTER 3 ohms type for 4½/6 volt D.C. operation. Price 6/6 each. P. & P. 1/-.

AS ABOVE 500 ohm for 24/36 volt D.C. operation. Price 6/6 each. P. & P. 1/-.

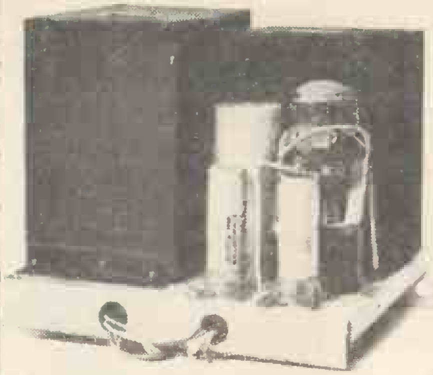

MAINS POWER SUPPLY UNITS, potted and sealed ransformer and choke by famous maker. Mounted on metal chassis 6½ x 7½in., complete with 5Z4 rectifier valve and full smoothing. Input tapped 220-230-240 volts.
Output: 300 V. D.C. at 100 mA.
6.3 V. A.C. at 4.5 amp.
6.3 V. A.C. at 2 amp.
Rectifier supply 5 V. A.C. at 3 amp. Very conservatively rated. Price 42/6 plus P. & P. 6/6.

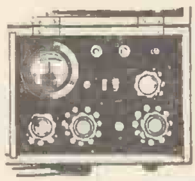

WHEATSTONE BRIDGE UNIT. 4 stud switches 0-10, 0-100 ohms, galvanometer centre zero, F.S.D. 2.5 mA. In oak carrying case 16 x 7½ x 6in., 40/- each. P. & P. 3/6.

EVERSHED & VIGNOLES.

Circuit testing Ohms Meter, pattern "S" complete with testing prods, inst. book etc. Two ranges: 0-3 and 0-30 ohms. Brand new, guaranteed perfect, as illus. Offered at fraction of maker's price £4/17/6 each. P. & P. 2/6.

TRIPLE RANGE VOLTMETER. 0-5 25-250 v. D.C. M/C 3½in. meter 3in. scale, mounted in bakelite carrying case 7½in. x 4½in. x 3in. complete with handle and test leads, 27/6 each. P. & P. 2/-.

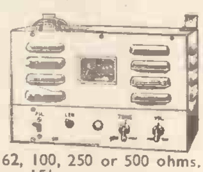

12 v. D.C. AMPLIFIER. as new, for operation on 12 v. car battery, 10 watts undistorted output, with 6L6 valves in push-pull. Mike/Gram input, tapped output 7½, 15, 62, 100, 250 or 500 ohms. £12/10/- each. Carr. 15/-.

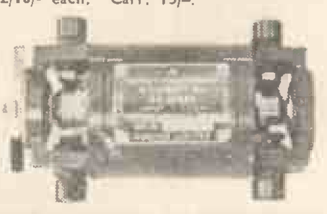

MIDGET ROTARY TRANSFORMERS. 2¼in. dia. x 4½in. Input 11.5 volt. Output 310/365 volts at 30 mA. Brand new. 12/6 each. P. & P. 1/6.

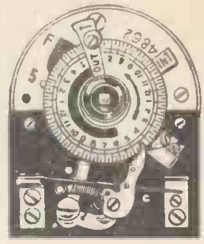

VENNER 8-day clockwork Time Switch. Contacts 1 amp. 230 volt. 24 hour phase, ¼ hour divisions, allows setting for one make and one break to be made every 24 hours, complete with key. Used but guaranteed perfect. Price 27/6 each. P. & P. 1/6.

FRESHLY MANUFACTURED TRANSFORMERS. Ideal for model makers. Input tapped 200/250 volt. Output multi-tapped from 3 to 30 volts at 2 ampere. Price 19/6. P. & P. 2/6.

JACK PLUGS. cylindrical, bakelite, screw on covers, red or black as required, two contacts. Price 2/- each post free. Dozen lots 20/- post free. Three contacts same price.
MERCURY SWITCH, 10 amp. contacts. Single pole, New. Price 3/6. P. & P. 6d.

METERS GUARANTEED PERFECT

Charging Types	
2¼ amp. D.C. M.I. 2in. fl. rnd.	7/6
5 amp. D.C. M.I. 2½in. fl. rnd.	11/6
7½ amp. D.C. M.I. 3½in. proj. rnd.	12/6
9 amp. D.C. Hot Wire 2½in. fl. rnd.	6/6
Voltmeters	
12 v. D.C. M.C. 2½in. proj. rnd.	8/6
20 v. D.C. M.C. 2in. fl. sq.	9/6
25 v. D.C. M.C. 2in. fl. rnd.	7/6
30 v. M.I. 3in. proj. rnd.	10/6
40 v. M.C. 2in. fl. sq.	9/6
150 v. D.C. M.C. fl. rnd. 2½in.	10/6
250 v. A.C. rectified moving coil linear scale 3½in. fl. rnd.	35/-
300 v. A.C. M.I. 2½in. fl. rnd.	22/-
400 v. A.C. M.I. 4½in. fl. rnd.	35/-
Milliammeters	
1 mA. M.C. 2½in. fl. rnd.	25/-
2 mA. M.C. 2½in. fl. rnd.	14/6
5 mA. M.C. 2in. round	12/6
10 mA. M.C. 3½in. fl. rnd.	30/-
30 mA. M.C. 2½in. fl. rnd.	9/6
200 mA. M.C. 2½in. fl. rnd.	9/6
500 mA. M.C. 2½in. fl. rnd.	9/6
Microamp	
50 microamp. scaled 0-100, M.C. 2½in. rnd. fl.	42/6
200 microA. M.C. 2½in. rnd. fl. (calibrated 0-50)	29/6
50 microA. 2½in. square, sidefitting 3 scales	35/-
500 microA. M.C. 2in. rnd.	16/6

Postage on all meters 1/- each

NEW UNCHARGED UNFILLED 12 VOLT ACCUMULATOR 9 ampere in unspillable plastic cases. Comprises 6 x 2 v. separate cells connected by terminal strips. 6 x 5½ x 4½in. over terminals. Price 19/-, plus P. & P. 2/9. Wooden carrying case for same with lid and strap price 3/6.

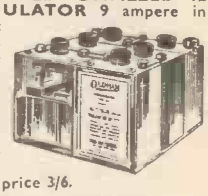

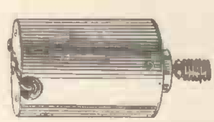

MINIATURE P.M. MOTOR. 12/24 volt, reversible. 1½in. dia. New. Price 9/6 each. P. & P. 1/-.

AIRCRAFT CINE CAMERA G45B Mk. III

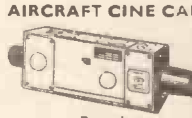

Fully modified, fitted with f/3.5 triple anastigmatic lens, takes 25ft. of 16 mm. film, fitted with 24 v. motor. 16 exposures per sec. Brand new, original packing, £4/10/- each. P. & P. paid.

SERVICE TRADING COMPANY →

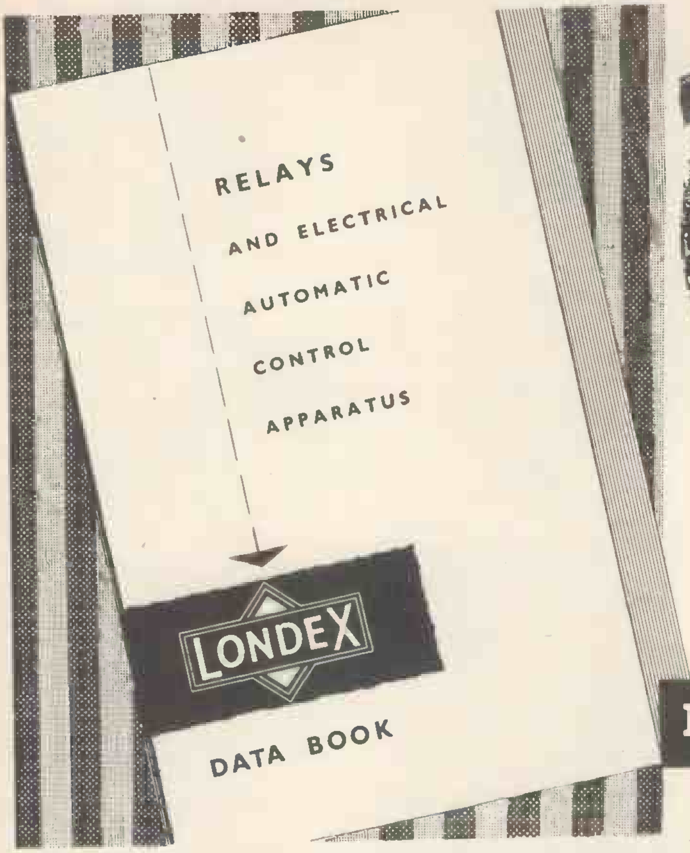

RELAYS
ELECTRONIC CONTROLS
TIMERS
FLUID & GAS CONTROL

The 1960 Edition of our Data Book is now available, it contains 44 pages of illustrated descriptions of our products. If you are interested in Automatic Electrical Control Apparatus a copy No. 144/W.W. will be sent free on request.

LONDEX LTD.

ANERLEY WORKS, LONDON, S.E.20
Telephone: Sydenham 3111

RCA 15 KW TELEGRAPH TRANSMITTER

Type ET-4750-X

Frequency range—2 to 22 megacycles.
Keying Speed—up to 250 words per minute.
Power Supply requirements—230 v. 3 phase 50/60 cycles.

Tube complement: Oscillator—807 (1), Doubler (1st) Amplifier—807 (1), Intermediate Power (2nd) Amplifier—813 (4), Power (3rd) Amplifier—889-R (2), Plate Rectifier—872 A(6), Auxiliary Rectifier—872A (3), Bias Rectifier—872A (2), Keyer—807 (2).

	Length	Height	Depth
Enclosure	11ft.	7ft. 6ins.	4ft. 1in.
Rectifier Unit	4ft. 2ins.	5ft. 3ins.	3ft. 2ins.
Plate Transformer	2ft. 6¾ins.	3ft. 6⅜ins.	1ft. 9½ins.

Weight (Nett)	
Enclosure (including control, R.F. and Output panels)	3,000 lbs.
Rectifier Unit	1,675 lbs.
Plate Transformer 7,000 volts	1,250 lbs.

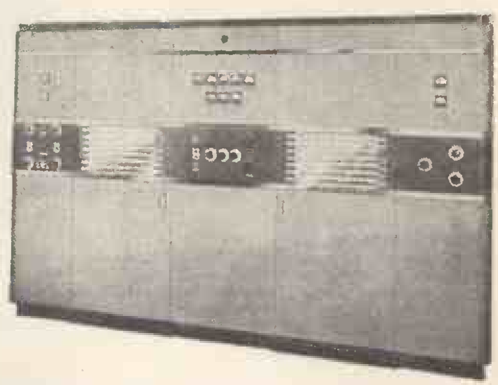

We have a full range of spares for this equipment.

If desired, we can modify this transmitter to work also on the telephone with an output of approximately 5 kW.

P.C.A. RADIO

Offices and Works

BEAVOR LANE, HAMMERSMITH, LONDON, W.6

Telephone: RIV 8006/7

C.R.T. ISOLATION TRANSFORMERS

For Cathode Ray Tubes having Heater/Cathode short circuit and for C.R. Tubes with falling emission. Full instructions supplied.

Type A. Low Leakage windings. Optional Boost 25% and 50%. Tapped mains primaries.

2 volt	12/6 each
4 volt	12/6 each
6.3 volt	12/6 each
10.8 volt	12/6 each
13.3 volt	12/6 each

OUR LATEST SUPERIOR PRODUCT. Type A2. High Quality. Low capacity, 10/15pf. Optional boost 25%, 50%, 75%. **16/6** each

Type B. Mains input. Low capacity. Multi Output 2, 4, 6.3, 7.3, 10 and 13 volts. Optional boost 25% and 50%. Suitable for all Cathode Ray Tubes. 21/-.

RESISTORS. All preferred values. 20% 10 ohms to 10 meg., ⅛ w., 4d.; ¼ w., 4d.; ½ w., 6d.; 1½ w., 8d.; 2 w., 1/-. **HIGH STABILITY.** ½ w., 1%, 2/-. Preferred values 100Ω to 10 meg. Ditto 5%, 9d., 100Ω to 5 meg.

WIRE-WOUND RESISTORS 25 ohms—10,000 ohms: 5 watt 1/3; 10 watt 1/6; 15 watt 2/-. 15,000 ohms—50,000 ohms 5 w., 1/9; 10 w. 2/3

WIRE-WOUND POTS, 3 w. Pre-set Min. T.V. type Knurled Slotted knob. All values 25 ohms to 25K., 3/- ea., 30 K., 50 K., 4/-. Ditto, 1 w. Carbon Track 30 K to 2 Meg., 3/-.

WIRE-WOUND POTS, 4 w. Standard size Pots, long Spindle High Grade. All values 100 ohms to 50 K., 6/6; 100 K., 7/6. **W/W EXT. SPEAKER CONTROL** 10Ω. 3/-.

O/P TRANSFORMERS. Heavy Duty 50 mA., 4/6. Multi-ratio push-pull, 7/6. Miniature 3V4, etc., 4/6. Hygrade Push-pull 10 watts, 15/6. MULLARD "510" 6k or 8k 30/-. **L.F. CHOKES** 15/10H 60/65 mA., 5/-. 10H 85 mA., 10/6. 10H 150 mA., 14/-.

MAINS TRANSFORMERS 200/250 v. A.C.

STANDARD 250-0-250, 80 mA., 6.3 v. 3.5 a. tapped 4 v. 4 a. Rectifier 6.3 v. 1 a., tapped, 5 v. or 4 v. 2 a. Ditto 350-0-350	22/6
MINIATURE 220 v. 20 mA., 6.3 v. 1 a.	10/6
MIDGET, 250 v. 45 mA., 6.3 v. 2 a.	15/6
SMALL, 250-0-250 100 mA., 6.3 v. 3.5 a.	19/6
STANDARD, 250-0-250, 65 mA., 6.3 v. 3.5 a.	17/6
HEATER TRANS., 6.3 v. 1½ a., 7/6, 3 amp.	10/6
GENERAL PURPOSE LOW VOLTAGE. Outputs 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 24 and 30 v. at 2 A.	22/6

ALADDIN FORMERS and cores. ¼in., 8d.; ⅜in., 10d. 0.3in. **FORMERS** 5937 or 8 and Cans TV1 or 2, ½in. sq. × 2¼in. or ⅝in. sq. × 1⅜in., 2/- with cores.
SLOW MOTION DRIVES. Epicyclic ratio 6 : 1, 2/3.
TYANA. Midget Soldering Iron. 230 v. 40 w., 16/9.
REMPLOY INSTRUMENT IRON. 230 v. 25 w., 17/6.
MAINS DROPPERS. 3 × 1½in. Three Adj. Sliders, .3 amp. 750 ohms, 4/3. .2 amps., 1,000 ohms, 4/3.
LINE CORD. .3 amp., 60 ohms per foot, .2 amp., 100 ohms per foot, 2 way, 6d. per foot, 3 way, 7d. per foot.

CRYSTAL MIKE INSERT by Acos 6/6
Precision engineered. Size only 1 × 1 3/16 in.
ACOS CRYSTAL DESK MIKE. Bargain. 35/-.

MIKE TRANSF. 50 : 1, 3/9 ea., 100 : 1 Potted, 10/6.
LOUDSPEAKERS P.M. 3 OHM. 5in. Rola, 17/6. 6in. × 4in. Rola, 18/-. 7in. × 4in. R.A., 21/-. 10in. × 6in. Rola, 27/6. 8in. Plessey, 19/6. 6½in. Rola, 18/6. 8in. Rola, 21/-. 10in. R.A., 30/-.
HI-FI TWEETERS, 4in., 25/-. 12in. Plessey, 30/-.
12in. Baker 15 wt. 3 ohm and 15 ohm models, 105/-.
12in. Baker foam suspension 15 w. 15 ohm, £8.
12in. 15 ohm Plessey 10 wt., 45/-.

I.F. TRANSFORMERS 7/6 pair
465 kc/s. slug tuning miniature can 2⅛ × 1 × 1in. High Q and good bandwidth. By Pye Radio. Data sheet supplied.
Wearite M800 I.F. Miniature 465 kc/s., 12/6 pair.
Wearite 550 I.F. Standard 465 kc/s., 12/6 pair.

CRYSTAL DIODE G.E.C., 2/-. GEX34, 4/-. 40 Circuits, 3/-.
H.R. HEADPHONES, 4,000 ohms, brand new, 16/6 pair.
SWITCH CLEANER Fluid, squirt spout, 4/3 tin.
TWIN GANG CONDENSERS. 365 pf. Miniature, 1⅞in. × 1⅜in. × 1⅞in., 10/-. .0005 Standard with trimmers, 9/-; less trimmers, 8/-. Midget, 7/6; Single 50 pf., 2/6; 100 pf., 150 pf., 7/-. Solid dielectric 100, 300, 500 pf., 3/6.
VALVE HOLDERS. Pax Int. Oct., 4d. EF50, EA50, 6d. B12A, CRT, 1/3. Eng. and Amer. 4, 5, 6, 7 pin, 1/-.
MOULDED Mazda and Int. Oct. 6d., B7G, B8A, B8G, B9A, 9d. B7G with can, 1/6; B12A, 1/3. B9A with can, 1/9.
CERAMIC, EF50, B7G, B9A, Oct., 1/-; B7G, B9A Cans, 1/-.
SPEAKER FRET. Gold Cloth 17in. × 25in., 5/-. 25in. × 35in., 10/-. Tygan 54in. wide, 10/- ft. 27in. wide, 5/- ft. Samples, S.A.E.

WAVECHANGE SWITCHES.

2 p. 2-way, 3 p. 2-way, short spindle	2/6
5 p. 4-way, 2 wafer, long spindle	6/6
2 p 6-way, 4 p. 2-way, 4 p. 3-way, long spindle	3/6
3 p. 4-way, 1 p. 12-way, long spindle	3/6

Wave change "MAKITS" 1 wafer, 8/6; 2 wafer, 12/6; 3 wafer 16/-; 4 wafer 19/6; 5 wafer 23/-; 6 wafer 26/6.
TOGGLE SWITCHES, S.P., 2/-; D.P., 3/6; D.P.D.T., 4/-.
MORSE KEYS, good quality, 2/6.
SUB-MINIATURE ELECTROLYTICS (15 v.), 1, 2, 4, 5, 8, 25, 50 mfd., 100 mfd., 3/- each.

EDISWAN TRANSISTORS JUNCTION TYPE P.N.P.

AUDIO XB102, for amplifiers and output stages up to 250 milliwatts in push-pull. PRICE **10/-**

R.F. XA104 frequency changer up to 4 Mc/s. **18/-**

XA103 IF amp. etc. up to 2 Mc/s. **15/-**

Goltop Power V15/10P, up to 10W with heat sink, 20/-.

1960 RADIOGRAM CHASSIS

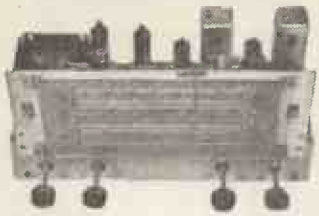

THREE WAVEBANDS
S.W. 16 m.—50 m.
M.W. 200 m.—550 m.
L.W. 800 m.—2,000 m.

FIVE VALVES
LATEST MULLARD
ECH81, EF89, EBC81, EL84, EZ80.

12 month Guarantee. A.C. 200/250 v., 4-way switch. Short-Medium-Long-Gram. A.V.C. and Negative Feedback. 4.2 watts. Chassis 13½in. × 5½in. × 2¼in. Glass Dial Size 10 × 4½in. horizontal or vertical. Two Pilot Lamps. Four Knobs. Walnut or Ivory, aligned and calibrated. Chassis isolated from mains.

BRAND NEW £9. 10. 0. Carr. 4/6.

TERMS: Deposit £5/5/- and 5 monthly payments of £1.
MATCHED SPEAKERS 8in. 17/6; 10in. 25/-; 12in. 30/-.

SUPERIOR FM-AM MODEL

Six Mullard Valves. ECC85, ECH81, EF89, EABC80, EL84, EZ80. V.H.F. 108-87 Mc/s. Med. 190-550 m. Long 1000-1,900 m. Gram input. Ready for use. A.C. Mains 200-250 v. Isolated chassis. Output point for use as Hi-Fi Tuner. 12 month guarantee. Circuit supplied.
Leaflet S.A.E.

£18. 19. 6. Carr. 5/6.

★ GARRARD 4-SPEED RECORD CHANGERS RC121/D MKII MODELS ★

Brand new and fully guaranteed 12 months.

AUDIO PERFECTION

Designed to play 16, 33, 45, 78 r.p.m. Records 7in., 10in., 12in. With plug-in NORMAL HEAD.
OUR PRICE **£10. 10. 0.** STEREO HEAD £2 extra

LATEST COLLARO AUTOCHANGER

£7.19.6

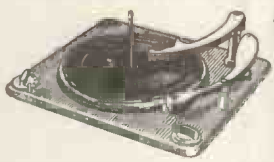

STUDIO 'O' Pick-up
4 Speeds— 10 Records

Or with Portable Cabinet, Amplifier & Speaker
£11.19.6. Carr. 5/6.

B.S.R. MONARCH UA8 4-SPEED AUTOMATIC RECORD CHANGERS

Brand new and fully guaranteed 12 months
OUR PRICE **£6.19.6.** post free
STEREO MODELS UA8, £7/19/6 UA12, £10/10/-

AUTOCHANGER ACCESSORIES

Suitable player cabinets (uncut boards)	49/6
Amplifier player cabinets with cut boards	63/-
2 valve amplifier and 6½in. speaker for above	79/6
3 valve amplifier and 6½in. speaker for above	95/-

Wired and tested ready for use.

★ GARRARD 4-SPEED SINGLE RECORD PLAYER TA MK II ★

£8.10 AUDIO PERFECTION STEREO WIRED

With plug in Normal heads MODEL 4 HF £18 — Stereo Heads £2 extra

BATTERY-MAINS POWER PACK

Same size as batteries B126 and AD35, 90 v. H.T., 1½ v. L.T. 150 mA., only 1/- a year to run on A.C. 200/250 v. Made by COSSOR. List 63/-, our price 39/6.

THE HI-GAIN BAND 3 PRE-AMP

Cascode circuit using Valve ECC84. 17db gain. Kit 29/6 less power; or 49/6 with power pack. Plans only 6d.
Also Band I version same prices.

LATEST "E.M.I." 4 SPEED SINGLE RECORD PLAYER

Acos 73 Hi-Fi Stereo and normal xtal pick-up for 7in., 10in. and 12in. records. Silent motor, heavy turntable. Auto-stop fitted.
Special offer £6/19/6.

VOLUME CONTROLS
Midget size: Long spindle. Guarateed 1 year. All values 5 K. ohms up to 2 Meg.
No switch 3/- D.P.Sw. 4/9
Linear or Log Tracks.

80 ohm Cable Coaxial
Semi-air spaced, ¼in. dia. Ideal Band III **6d.** yd. Losses cut 50%
Post 1d. per yard extra.
FRINGE QUALITY AIRSPACED .... 1/- yd.

COAXIAL PLUGS .... 1/- **LEAD SOCKETS** 2/-
PANEL SOCKETS ... 1/- **OUTLET BOXES**.... 4/6
BALANCED TWIN FEEDER per yd. 6d., 80Ω or 300Ω
TWIN SCREENED BALANCED FEEDER 1/6 yd., 80 ohm.

ALUMINIUM CHASSIS. 18 s.w.g. Plain, undrilled with 4 sides, riveted corners and lattice fixing holes, with 2½in. sides, 7 × 4in., 4/6; 9 × 7in., 5/9; 11 × 7in., 6/9; 13 × 9in., 8/6; 14 × 11in., 10/6; 15 × 14in., 12/6 and 18 × 3in., 16/6.

BLACK CRACKLE PAINT. Air drying, 3/- tin.
P.V.C. CONN. WIRE, 4 colours, single or stranded, 2d. yd.
NEON MAINS TESTER SCREWDRIVERS, 5/-.
CORED SOLDER RADIOGRADE, 4d. yd., ½lb., 2/6.
PAXOLIN 1 × 15in., 8in. × 10in., 1/6. **ION TRAPS** 5/-

"FAMOUS MAKE"
50% Extra Long Play Plastic Tape.
1,700ft. 7in. Reel 35/-. 850ft. 5in. Reel 21/-
SUPERIOR 1,200ft. 7in. Plastic Tape 24/- 600ft. 5in. 15/-. All Spare Reels 3/- each.
LONG PLAY 5¾in. 1,200ft. 28/-. 3in. 225ft. 7/6.
"INSTANT" Bulk Tape Eraser and Head Demagnetiser: 200/250 v. A.C. 27/6.

MAINS TYPE. RM1, 125 v., 60 mA., 5/-; RM2, 100 mA., 6/-; RM2, 120 mA., 8/-; RM4, 250 v. 275 mA., 16/-.
MINIATURE CONTACT COOLED RECTIFIERS. 250 v. 50 mA., 7/6; 60 mA., 8/6; 85 mA., 9/6; 200 mA., 21/-; 300 mA., 27/6; Full Wave 120 mA., 15/-.
COILS. Wearite "P" type, 3/- each. Osmor Midget "Q" type adj. dust core from 4/- each. All ranges.
TELETRON. L. and M. T.R.F. with reaction, 3/6.
FERRITE ROD AERIALS. M.W., 8/9; M. & L., 12/6.
T.R.F. COILS. A HF. 7/- pair. **H.F. CHOKES,** 2/6.

JASON F.M. TUNER COIL SET, 26/-. H.F. coil, aerial coil Oscillator coil, two I.F. transformers 10.7 Mc/s., Detector transformer and heater chokes. Circuit and component book using four 6AM6, 2/6. Complete kit FMT1 with Jason Calibrated dial and 4 valves, £6/15/-. With new Jason Cabinet, FMT2, 20/- extra.

CONDENSERS. New Stock. .001 mfd. 7kV. T.C.C., 5/6. 20kV., 9/6. .1 mfd. 7kV., 9/6. 100pf. to 500 pf. Micas, 6d. Tubular 500 v. .001 to .05 mfd., 9d.; .1, 1/-; .25, 1/6; .5 1/9; .1/350 v., 9d.; .1/1,000 v., 1/9; 0.1 mfd., 2,000 v., 3/6; .001 mfd., 2,000 v., 1/9.
CERAMIC CONDS. 500 v. .3 pf. to .01 mfd., 9d.
SILVER MICA CONDENSERS. 10% 5 pf. to 500 pf., 1/-; 600 pf. to 3,000pf., 1/3.
CLOSE TOLERANCE (±1 pf.) 1.5 pf. to 47 pf., 1/6. **DITTO** 1%, 50 pf. to 815 pf., 1/9; 1,000 pf. to 5,000 pf., 2/-.
TRIMMERS. Ceramic, 30, 50, 70 pf., 9d.; 100 pf., 150 pf., 1/3. 250 pf., 1/6. 600 pf., 750 pf., 1/9. Philips, 1/- ea.

NEW ELECTROLYTICS. FAMOUS MAKES

TUBULAR		TUBULAR		CAN TYPES	
1/350 v.	2/-	64/350 v.	5/6	8/500 v.	3/-
2/450 v.	2/3	100/25 v.	3/-	16/500 v.	4/-
4/450 v.	2/3	250/25 v.	3/-	32/350 v.	4/-
8/450 v.	2/3	500/12 v.	3/-	100/270 v.	5/6
8/500 v.	2/9	8+8/450 v.	4/6	2,500/3 v.	4/-
16/450 v.	3/6	8+8/500 v.	5/-	6,000/6 v.	5/-
16/500 v.	4/-	8+16/450 v.	5/6	8+16/500 v.	7/-
32/450 v.	5/6	8+16/500 v.	5/6	32+32/450 v.	6/6
25/25 v.	1/9	16+16/450 v.	5/6	50+50/350 v.	7/-
50/25 v.	2/-	16+16/500v.	6/-	64+120/350 v.	11/6
50/50 v.	2/-	32+32/350 v.	4/6	100+200/275v.	12/6

FULL WAVE BRIDGE/SELENIUM RECTIFIERS. 2, 6 or 12 v 1½ amp., 8/9; 2 a., 11/3; 4 a., 17/6; 6 a., 22/6.
CHARGER TRANSFORMERS. Tapped input 200/250 v. for charging at 2, 6 or 12 v. 1½ a., 15/6; 2 a., 17/6; 4 a., 22/6. Charger circuit free. **AMPMETERS,** 4 a., and 5 a., 14/6.

NEW and boxed **VALVES** 90-day guarantee

1R5	8/6	6L6G	10/6	EA50	1/6	EY51	12/6
1S5	8/6	6N7M	7/6	EABC80	10/6	EZ81	8/6
1T4	8/6	6Q7G	10/6	EB91	6/6	HABC80	12/6
2X2	2/6	6SA7M	10/6	EBC33	8/6	HVR2A	7/6
3S4	8/6	6SJ7M	10/6	EBC41	10/6	MU14	10/6
3V4	8/6	6SN7	8/6	EBF80	10/6	P61	6/6
5U4	8/6	6V6G	7/6	ECC84	12/6	PCC84	12/6
5Y3	8/6	6X4	7/6	ECF80	11/6	PCF80	11/6
5Z4	10/6	6X5	7/6	ECH42	10/6	PCF82	11/6
6AM6	8/6	12A6	8/6	ECL80	12/6	PCL82	11/6
6BE6	7/6	12AT7	10/6	ECL82	12/6	PEN25	6/6
6BH6	10/6	12AU7	9/6	EF39	7/6	PL82	10/6
6BW6	10/6	12AX7	9/6	EF41	10/6	PY80	8/6
6D6	7/6	12BA6	9/6	EF50	5/6	PY81	10/6
6F6G	7/6	12BE6	9/6	EF80	10/6	PY82	8/6
6H6GT	3/6	12K7	8/6	EF86	14/6	SP61	5/6
6J5M	6/6	12Q7	8/6	EF92	5/6	UBC41	10/6
6J6	7/6	35L6	9/6	EL32	5/6	UCH42	10/6
6J7G	8/6	35Z4	9/6	EL41	10/6	UF41	10/6
6K6GT	6/6	80	10/6	EL84	10/6	UL41	10/6
6K7G	5/6	807	6/6	EZ40	8/6	UY41	8/6
6K8G	8/6	954	1/6	EZ80	8/6	U22	10/6

RADIO COMPONENT SPECIALISTS

OUR ONLY ADDRESS
337 WHITEHORSE RD., WEST CROYDON

POSTAL SERVICE 1/-, OVER £2 FREE. C.O.D. 1/6 (EXPORT C.W.O. POST EXTRA.) Wed. 1 p.m.

THO. 1665. Buses 133 or 68

Special Offer !

. . . to 'Wireless World' readers

TRS

50 only Philips Hi-Fi Speakers

10" Dual Concentric Models, as currently fitted, in quality receivers.

Only 2 gns. each plus 2/6 p. & p.

DON'T BE DISAPPOINTED !

Orders executed in strict rotation.

New additions to GOODMANS speaker range

Latest release of two 10" units

AXIOM 110 - £5.

AXIOM 112 - £8 10s.

also the new Triaxiette Super 8" Unit, £13 10s.

The well known 8" Axiette (£6 12s.) and the 12" Audiom 60 (£9 12s.) as recommended for two speaker systems, are still available, ex stock.

RECORD PLAYER BARGAINS—Latest 4-speed models

NEW RELEASE by E.M.I.—4-speed Single Player Unit fitted with latest stereo and monaural Xtal cartridge and dual sapphire stylii. Auto stop and start. A fidelity unit and bargain buy at only £6/19/6.

SINGLE PLAYERS. BSR (TU9), 90/-; COLLARO (4/564), 6 gns.; GARRARD (4SP £7/10/-. Carr. and ins. 3/6.

AUTOCHANGERS. BSR (UA8), £6/19/6. COLLARO £7/19/6. GARRARD (RC121 4D Mk. II) plug-in head, stereo adapted, 10 gns. Stereo head £2 extra.

RECORD PLAYER CABINETS

Contemporary styled, rexine covered cabinet in two-tone fawn and brown, or mottled red with white polka dot. Size 18½ × 13½ × ht. 8½in., fitted with all accessories, including baffle board and anodised metal fret. Space available for all modern amplifiers and autochangers, etc. Uncut record player mounting board 14 × 13in. supplied.
Cabinet Price £3.3.0. Carr. and Ins. 3/6.

2-VALVE 2-WATT AMPLIFIER

Twin stage ECL82 with vol. and neg. feedback. Tone controls AC. 200/250 v. with double-wound Mains trans. Complete with knobs, etc., ready wired to fit above cabinet.

£2.17.6 P. & P. 1/-.

6-in. Speaker and matching trans., 22/- P. & P. 1/6.

TRANSISTOR 'ONE-WATT' AMPLIFIER
6 v. Battery operated

Latest Push-Pull, 4 Transistor circuit giving full 1 watt Output into standard 3 ohm speaker. Good sensitivity and improved freq. response. Neg. feedback. Var. Tone and Volume Controls. Chassis Size 6½in. × 3½in. × 1½in. Current consumption 10 mA quiescent—250 mA at 1 watt.

2 matched GEC GET15 Transistors .... 42/- pr.
2 GEC GET3 Transistors .... 21/- pr.
Driver Trans. 8/6
Output Trans. (to 3 ohms) 10/6

Complete Kit of Parts incl. circuit etc., less speaker. ONLY 99/6 P. & P. 2/6.

Circuit and instruction booklet 1/6 post free

NOW! The TouRisT Portable

4 valve. Med. & L.W., l'tweight battery Radio. Size only 8in. × 5½in. × 4in. Weight 3½lb. with battery:—

		P. & P.
Complete receiver component kit	57/6	1/6
Set 4 miniature valves (96 series)	35/-	9d.
5in. Speaker & O/put Trans.	21/-	1/6
Cabinet, Dial and Knobs, etc...	22/6	2/-

Latest superhet circuitry, delayed AVC and A.F. Neg. feedback.

Complete kit—BARGAIN—only £6.10.0, post free

*Terrific performance—
Remarkable size—
Staggering Value*

Send for Booklet NOW! 1/6 post free

NEW BOXED VALVES ALL GUARANTEED

1R5,1T4	7/6	EABC80	9/6	EZ81	7/6
1S5	7/6	ECC84	10/6	MU14	9/6
3S4,3V4	8	ECF80	11/6	PCC84	10/6
5Z4	9/6	ECH42	10/6	PCF80	10/6
6K7	5/6	ECL80	10/6	PCL83	12/6
6K8	8/6	EF80	9/6	PL81	12/6
6Q7	8/6	EF86	13/6	PL82	9/6
6V6	7/6	EF91	8/6	PL83	11/6
DAF96	9/-	EL41	10/6	PY80	7/6
DF96	9/-	EL84	9/6	PY81	9/6
DK96	9/-	EY51	10/-	PY82	7/6
DL96	9/-	EY86	10/-	U25	12/6

SPECIAL PRICE PER SET
1R5, 1T4, 1S5, or 3S4 or 3V4, 27/6.
DK96, DF96, DAF96, DL96, 35/-.
6K8, 6K7, 6Q7 6V6, 5Z4 or 6X5, 35/-.

COAX 80 OHM CABLE.

Stand ¼in. diam. Low Loss Semi-Air Spaced Aeraxial.

Special Reduced Prices

20 yds. 12/6, p. & p. 1/6; 60 yds. 32/6 p. & p. 3/-; 40 yds. 22/6, p. & p. 2/6; All other lengths 8d. per yard.
Coax Plugs 1/-. Sockets 1/-. Couplers 1/3. Cable End Sockets 1/6. Outlet Boxes 4/6.

JASON FM TUNER UNITS (87-105 Mc/s)

Designer-approved kits of parts for these quality and highly popular tuners available as follows.

STANDARD MODEL (FMT)—as previously extensively advertised. COMPLETE KIT, 5 gns., post free. Set of 4 spec. valves, 30/-, post free.

LATEST MODEL (FMT2)—attractively presented shelf mounting unit to enclosed Metal Cabinet with Built-in Power Supply. COMPLETE KIT, £7. p. & p. 3/6 Set of 5 spec. valves, 39/6

NEW JASON COMPREHENSIVE F.M HANDBOOK, 2/6 post free. 48hr. Alignment Service. 7/6. p. & p. 3/6.

MULLARD "3-3" AMPLIFIER

Quality built to Mullard's specification, with special sectionalised O/P Trans
Complete kit with front panel only £6/19/6. P. & P. 3/6.

C.R.T. Heater Isolation Transformers

New improved types—mains prim. 200/250 v. tapped

All isolation Transformers now supplied with alternative *no boost, plus* 25% and *plus* 50% boost taps at no extra charge.

2V 2A type ...... 12/6 (P. & P. 1/6)
6.3V. .6A type .. 12/6 (P. & P. 1/6)
10.5V .3A type .. 12/6 (P. & P. 1/6)
13V. .3A type .. 12/6 (P. & P. 1/6)

Small size and tag terminated for easy fitting. Other voltages available.

RE-GUNNED TV TUBES NEW REDUCED PRICES

. . and now 12 months guarantee!

All tubes rebuilt with new heater, cathode and gun assembly—reconditioned virtually as new.

12in. £6, 14in. £7, 17in. £8.10.0, etc.

10/- part exchange allowance on old tube

Carr. and ins. 10/-. Comprehensive stocks—quick delivery.

CONDENSERS—Silver Mica. All pref. values. 2 pf. to 1,000 pf., 6d. each. Ditto. ceramics 9d. each. Tubulars 450 v. T.C.C etc., .001 mfd.-01 and .1/350 v., 9d. each. .02-1/500 v., 1/- each. .25 Hunts 1/6. .5 T.C.C. 1/9. .001 6 kv., 5/6. .001 20 kv., 9/6.

RESISTORS—FULL RANGE 10 ohms—10 megohms 20% ¼ w. and ½ w., 3d., ¾ w., 5d. (Midget type modern rating), 1 w., 6d. 2 w. 9d., 10% Hi-Stab. ¼ w., 5d., ½ w., 7d., 5% ½ w., 9d., 1% HI-STAB. ½ w., 1/6 (10-100 ohms 2/-).

PRE-SET W/W POTS. T/V Type. 25 ohms—50 K ohms. 3/-. 50K—2 Meg. (Carbon. 3/-).

SPEAKER FRET—Expanded Bronze anodised metal 8 × 8in., 2/3; 12 × 8in., 3/-; 12 × 12in., 4/6; 12 × 16in., 6/-; 24 × 12in. 9/-; 36 × 12in., 13/6, etc., etc.

TYGAN FRET (Contemporary pat.), 12 × 12in., 2/-; 12 × 18in., 3/-; 12 × 24in., 4/- etc

LOUDSPEAKERS—P.M. 3 ohms, 2½in. Elac. 17/6. 3½in. Goodmans 18/6; 5in Rola. 17/6. 6in. Elac 18/6; 7 × 4in. Goodmans Elliptical. 18/6; 8in. Rola, 20/-; 10in R. and A., 25/-; 10in. W.B.-HF1012. 99/9; 12in. Plessey 15 ohms with 6/4in. Tweeter and Cross Over Filter, 97/6.

Electrolytics All Types New Stock

TUBULAR		CAN TYPES	
25/25 v. 50/12 v.	1/9	8+8/450 v.	4/6
50/50 v. 100/25 v.	2/-	32+32/275 v.	4/6
8/450 v.	2/3	50+50/350 v.	6/6
16+16/450 v.	5/6	60+250/275v.	12/6
32+32/450 v.	6/6	100+200/275v.	12/6

Comprehensive range in stock

VOLUME CONTROLS—10K—2 Megohms. ALL LONG SPINDLES. MOCCANITE MIDGET TYPE, 1½in. diam. Guar. 1 yr. LOG or LIN Ratios less Sw 3/-. D.P Sw. 4/6. Twin gang controls ¼ Meg. ½ Meg. 1 Meg. less Sw., each 8/9.

7 VALVE AM/FM RADIOGRAM CHASSIS

Valve Line-up: ECC85, ECH81, EF89, EABC80 EL84, EM81, EX80.

Three Waveband and Switched Gram positions. Med. 200-500 m., Long 1,000-2 000 m., VHF/FM 88-95 Mc/s. Philip's Continental Tuning insert with permeability tuning on FM and combined AM/FM IF transformers, 460 Kc/s and 10.7 Mc/s. Dust core tuning all coils. Latest circuitry including AVC and Neg. Feedback. Three watt output. Sensitivity and reproduction of a very high standard. Chassis size 13½ × 6½in. Height 7½in. Edge Illuminated glass dial 11½ × 3½in. Vertical pointer, Horizontal station names. Gold on brown background. A.C. 200/250 v. operation.

Aligned and tested ready for use **£13.10.0** *Carr. & Ins. 5/-*

Complete with 4 Knobs—walnut or ivory to choice.
Three ohm P.M. speaker only required. Recommended quality speakers.
8in. Goodmans special cone 21/6
10in. Rola (Heavy Duty) 30/-
Post & Pkg. 1/6.

We are sorry to cause our customers disappointment, but existing orders have already exhausted present stocks of the above. A new replacement chassis, virtually identical, will be available from early February, price unchanged.

2 WAVEBAND CAR RADIO KIT

12 v. operation Med. & Long Waves

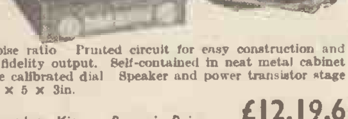

Modern development of the famous Brimar Hybrid vibratorless car radio circuit. Five latest type Brimar low voltage valves and power transistor. R.F. stage and permeability pre-aligned Cyldon Tuner Unit provide extremely good sensitivity and signal/noise ratio Printed circuit for easy construction and 7 × 4in. elliptical speaker for fidelity output. Self-contained in neat metal cabinet 8 × 7 × 2½in. with attractive calibrated dial Speaker and power transistor stage mounted separately approx. 8 × 5 × 3in.

Recommended Buy *Complete Kit Bargain Price* **£12.19.6**

Instruction booklet and parts list available 3/6 post free. P. & P. 3/6.

ONLY A FEW ITEMS ARE LISTED FROM OUR COMPREHENSIVE STOCK. WRITE NOW FOR FULL BARGAIN LISTS, 3d.

Terms: C.W.O. or C.O.D. post and packing up to ½lb. 7d.; 1lb. 1/1; 3lb. 1/6; 5lb. 2/-; 10lb. 2/9.

TRS

RADIO COMPONENT SPECIALISTS

70 BRIGSTOCK RD., THORNTON HEATH, SURREY

Established 1946. Tel: THO 2188 Hours: 9 a.m.—6 p.m. 1 p.m. Wednesday

DEPENDABLE RADIO SUPPLIES LTD.

12a TOTTENHAM STREET, LONDON, W.I.
(2 minutes Goodge Street Station Opp. Heals in Tottenham Court Road)
Phone LANgham 7391/2. *Hours of Business 9-6.*
Callers welcome. *Terms: Cash with order or C.O.D.*

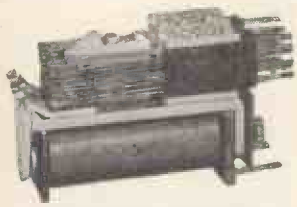

POST OFFICE RELAYS TYPE 3,000

BUILT UP TO YOUR REQUIREMENTS

Type 600 also available

COMPONENT PARTS ALL PLATED

Yokes, 3/- each. Armatures, 9d. each. Adjustable, 1/3 each. Spindles, 1/- each. Top Plates, 3d. each. Bottom Plates, 3d. each. Armatures Screws adjustable, 4d. each. Fixing Screws (with insulators), 2d. each. Buffer Blocks, 6d. each.

BUILD UPS CONTACTS

	Silver	Platinum
1. C/O	1/3	4/-
2. C/O	2/6	8/-
3. C/O	3/6	12/-
4. C/O	4/6	16/-
6. C/O	6/6	24/-
8. C/O	8/6	32/-

Other build ups to order; all tyoes of relays built to your specification.

COIL VALUES

	Single	Twin
Up to 100 Ohms	3/-	5/-
„ „ 500 „	4/-	6/-
„ „ 1,000 „	5/-	7/-
„ „ 5,000 „	6/6	8/6
„ „ 10,000 „	9/-	14/6
„ „ 20,000 „	14/-	17/6
„ „ 40,000 „	16/-	20/-
„ „ 80,000 „	20/-	—

*Slugged coils extra.

SIEMEN'S HIGH SPEED C/O RELAYS

250+250 ohm Twin Coils 6/6
850+850 „ „ „ 8/6
1,000+1,000 ohm Twin Coils 10/6
1,700+1,700 „ „ „ 17/6

G.E.C. MINIATURE SEALED RELAYS

No.	Ohms.	Build Ups	Voltage	Price
Z.530002	180	4C	12	£1 2 6
Z.530005	2	2C	1.3	12 6
Z.530006	40	2C	6	15 0
Z.530008	670	2C	24	19 6
Z.530010	40	2C 2K	6	17 6
Z.530011	180	2C 2K	12	£1 2 6
Z.530014	2	IC	1.3	10 6
Z.530015	40	IC	6	12 6
Z.530016	180	IC	12	19 6
Z.530018	2,500	IC	48	£1 2 6
Z.530019	2	2C 2K	1.3	14 6
Z.530020	2	4C	1.3	16 6
Z.530022	2	M.B.	1.3	12 6
Z.530023	2	2B 2M	1.3	12 6
Z.530024	40	2M	6	12 6
Z.530025	40	M.B.	6	12 6
Z.530027	180	2M	12	17 6
Z.530028	180	M.B.	12	17 6
Z.530031	670	M.B.	24	17 6

S.T.C. MINIATURE SEALED RELAY

4184GD	700	2C	24	19 6

1/6 Post & Packing on all relays. *Send for lists*

ROTARY TRANSFORMERS

Delivery ex stock. Quotations on application.

H.T. 31	H.T. 32
Input 11.5 v. Output 250 v. at 125 mA.	Input 11.5 v. Output 490 v. at 65 mA.

AS SUPPLIED TO GOVERNMENT DEPARTMENTS AND LEADING MANUFACTURERS. NEW AND BOXED.

ROTARY TRANSFORMERS

Made by DELCO
TYPE 1 27/6. P. & P. 3/6.
TYPE 2, 37/6. P. & P. 3/6.
Type 1. Dual voltage 12 or 24 v., input 265 v., 120 mA. output; 500 v., 26 mA. output.
Type 2. 12 v. input 275 v. 110 mA. output; 500 v., 50 mA. output.
Both types dual output.
MADE IN U.S.A.

OTHER DYNAMOTORS IN STOCK, SEND FOR LIST

120 INCHES OF SCALE

The CR50 Bridge covering 10pFd to 100mFd and 1 ohm to 10 Megohms in fourteen ranges has a total length of scale of over 120 inches thereby ensuring easy and accurate readings. A leakage test is incorporated for condensers. Complete with valves, instructions and ready for operation from 200/250 volt A.C. mains. **£8/2/6** plus 4/6 carr./packing.

SC30 OSCILLOSCOPE. A 3in. 'scope for service and design purposes at an extremely low price of **£17/10/-** plus 6/- carr./packing.

VV60 AUDIO VOLTMETER measures 1 milli-volt to 100 volts in five ranges. **£14** plus 4/6 carr./packing.

Further details sent by return of post on receipt of stamped addressed envelope.

TRADE supplied direct. CREDIT TERMS available

GRAYSHAW INSTRUMENTS

126 Sandgate High Street, Folkestone, Kent
Phone: Folkestone 78618

ELECTRICAL & WIRELESS SUPPLY CO.

69, CHURCH ROAD, MOSELEY, BIRMINGHAM 13
Cables: ELEWICO, BIRMINGHAM

Suppliers of American Wireless Communication Equipment for Aircraft such as **BENDIX V.O.R. Type MN-85 VHF 280** crystal-controlled channels radio system incorporating both navigation and communication facilities operating in the frequency range of 108, 0 to 135, 9 mc/s.

RCA Type 710A Signal Generator. Frequency range 370 to 560 mc/s. Direct calibration. Accuracy ½%. Output voltage 1 µV to 90 mV. Output impedance 50 ohms.

TCS Remote Control Units Type 23270A.
TS-98AP Voltage Dividers.

AMERICAN AIRCRAFT CAMERAS FAIRCHILD Types **K24, K22, K20, K19B, K17B, K8A-B** and **GUN CAMERAS** the most recent type **AN/N-9** and **G.S.A.P.**

AMERICAN FLIGHT INSTRUMENTS such as **AIR SPEED, CLIMB, FUEL, TEMPERATURE, PRESSURE, HORIZON, TURN & SLIP** Indicators, **FUEL FLOW AMPLIFIERS, CONTROL DIRECTIONAL GYROS,** etc., etc.

C.C.GOODWIN (SALES) LTD

WORLD WIDE EXPORTERS

AMPLIFIERS · TUNERS · SPEAKERS · MOTORS · PICK-UPS

★ *OVERSEAS ORDERS SENT FREE OF PURCHASE TAX AND SHIPPED PROMPTLY AT MINIMUM COST* ★

U.S.A. & CANADA EXPORT EXAMPLES				PACKED INSURED & CARRIAGE PAID
	Decca Stereo pick-up with arm type ffss	$46.20	(£16/9/6)	
	Garrard 301 transcription motor with Stroboscope.................	$56.00	(£19/19/6)	
	Leak TL12 Plus Amp. with Varislope III	$104.50	(£37/7/6)	

Reduced transit rates for British and Allied Forces Overseas.
Enquiries welcomed.

(Dept. W.5.) 7, THE BROADWAY, WOOD GREEN, LONDON, N.22 **Tel. BOWes Park 0077/8.**

BENSON'S BETTER BARGAINS

POWER UNITS. Input A.C. 115/250 v. Outputs: D.C. 330 v., 120 mA., and 6.3 v. A.C. twice. Potted trans. and LF choke; new (post 3/6), **30/-. Input** 230 v. A.C. Outputs: D.C. 350 v., 80 mA., A.C. 6.3 v. Valves: 807, EA50, EF50, 5Z4G, **25/-.** WAVEMETER **1252:** A.C. Input D.C. 250 v. Output. Valves. EA50, 6J5, 6X5, Y63. 22-34 mcs. 4½in. SM Drive. Copper-lined, hinged case. (Rail 7/6), **35/-. MONITOR 56,** comprising **Indicator 248 and Power Unit 675.** Valves VCR138a, 3/EF50, 2/ECC33, 5/EF55, EF37A, 6V6, 3/EA50 and 2/5U4G, VU120A. Two units each 12×9×18in., black finish. **Panel controls:** Brill., Focus, T.B. Expansion, "Y" shift, "X" shift (two). T.B. 10/20k secs. A.C./D.C. switch, "Y" amp. multiplier/divider. Sig. input, trig., and Y2 input. Voltmeter centre-zero, 5/20/100. "X" Y and G" on "jumpers" at rear. 230 v. A.C. input, with 18-way Cable and mains cable. Cathode probe unit extra, **17/6, £8 10s.** (Rail 20/-). **RELAYS** (Contactors), two heavy-make contacts: 12 v. or 24 v. either **3/6. INDICATORS.** type 277, with 1in. C.R.T., 4/VR91, 2/VR92, **37/6** (p.p. 3/6). Type 101, with VCR530 (6¼in. Blue, magnetic. Octal base), and 2/EB91, 2/EF91, 2/R10, new cond., **30/-** (Post 3/6). Type 1, with VCRX263, 2/EF52, 5/6J6, 1/6V6, 1/EY51, 2/EB91, 3/EF91, RF EHT Generator and 28 kc/s. xtal, **45/-** (Rail 7/6). Type 97 with VCR517, 10 valves, **30/-** (Rail 7/6). **HEADPHONES,** CLR, **7/6.** CR109 Noise Limiter assemblies, with valve, **3/6. NEW M.C. METERS,** 3½in. round flush, 50μA, **70/-;** 100μA., **65/-;** 1 mA., **55/-;** 2 mA. (rectified), **45/-.** 2½in., 1 mA., **22/6;** 2in. 200 mA., 300 mA., each **8/6.** 2½in. 20 v. A.C., **8/6;** 2in. 40v., **8/6;** 300 v. A.C. 2½in., **15/-. VIBRATORS,** Mallory G634C 12 v. 4-pin, **7/6;** 6 v. 5-pin reversible, **7/6. R1155B,** good condition, tested with handbook, **£7/10/-** (Rail 10/-). **SCR522** Modulation or Driver Trans., either **7/6. MORSE TRAINER SET** with buzzer and key wired for 4½ v. battery, **8/6. DRIVES:** slow-motion Admiralty 200:1 ratio, scaled 0-100, **5/6. R1155 S.M.** "N" type, new, **10/6. VIBRAPAK,** 6 v. D.C. to 250 v. 60 mA., smoothed cased, **22/6.** 12 v. to 250 v. 60 mA., **21/-** (p.p. 3/6). **DYNAMOTORS** (post 3/6); 12 v. to 250 v. 60 mA. and 6.3 v. 2.5 A., **11/6;** 6 v. to 250 v. 60mA., **11/6.** Potentiometers, miniature wirewound, 6Ω, 100Ω, 600Ω, 1k and 2k, each **1/-. CHOKES.** LF 10H 200 mA., **8/6;** 9H 100 mA. **5/6;** Potted 10H 100 mA., **7/6;** "C" **5H** 400 mA., **10/6. SWITCHES,** toggle U.S.A., DPDT, **1/6. R.F.27,** good cond., **18/-** (p.p. 3/6). **METAL RECTIFIERS,** 240 v. 100 mA., **4/-;** 240 v. 30 mA.. **3/6;** 600 v. 30 mA., **5/6;** 240 v. 80 mA., **5/6;** 1,000 v. 30 mA., **7/6. Mic inserts,** G.P.O. carbon, **2/6,** bal. armature type, **2/6. CONTROLS** Camera Type 35; a timing device with 24v. minature motor; new, (post 3/6). 10/6. **TRANSFORMERS,** input 230v. Output 6.3v., 1.5A., 6/9; 3A., 8/6; 1A., & 3A., 8/6; 325v., 20mA & 6.3v., 1. A.. 8/6. Multiradio output (40mA), 6/6.

LIST AND ENQUIRIES S.A.E. please. Terms, C.W.O. **Postage extra.** Immediate despatch.

Callers and Post: **W. A. BENSON (WW), 136 Rathbone Road, Liverpool, 15.** *SEF* 6853
Callers: **SUPERADIO (Whitechapel) LTD., 116 Whitechapel, Liverpool, 2.** *ROY* 1130

Smith's of EDGWARE ROAD

ELECTRONIC COMPONENT DISTRIBUTORS FOR OVER 25 YEARS

BLANK CHASSIS

Precision made in our own works from commercial quality half-hard aluminium of 16 s.w.g. (1/16in.) thickness, these chassis go all over the world (they even go off it—in rockets!).
Same day service for ANY SIZE, to nearest 1/16in. and up to 17in. long and 4in. deep, of straightforward two, three or four-sided chassis. Orders for specials dealt with promptly when accompanied by clear instructions or drawings.

SOLDERED CORNERS

While these chassis, owing to their thickness, hardness and efficient folding, will carry components of considerable weight and normally require no corner strengthening, we can do this if required by a special soldering technique at 6d. extra for each corner.

FLANGES

¼in., ⅜in. or ½in. flanges (inside or outside) 6d. extra for each bend.

PRICE GUIDE (normal chassis only)

Work out total area of material required, including waste, and refer to table below:

48 sq. in.	4/-	176 sq. in.	8/-	304 sq. in.	12/-
80 sq. in.	5/-	208 sq. in.	9/-	336 sq. in.	13/-
112 sq. in.	6/-	240 sq. in.	10/-	368 sq. in.	14/-
144 sq. in.	7/-	272 sq. in.	11/-	and pro rata	
Post 1/3		Post 1/6		Post 1/9	

Discount for quantities. Trade enquiries invited.
Spray finishing arranged for quantities of 25 or over.

PANELS

The same material can be supplied for panels, screens, etc. Any size up to 3ft. at 4/6 sq. ft. (sq. in. x ⅜d.) Post, up to 72 sq. in. 9d., 108 sq. in. 1/3, 144 sq. in. 1/6, 432 sq. in. 1/9, 576 sq. in. 2/-.

287/289 EDGWARE ROAD, LONDON, W.2
Telephone: PAD 5891/7595

PROVED

The finest method for cleaning records

Already over 200,000 enthusiastic users

THE "Dust Bug"

AUTOMATIC GRAMOPHONE RECORD CLEANER

PATENT APPLIED FOR

Price reduced to 17/6 (plus 5/10 purchase tax)

from your local dealer or

CECIL E. WATTS LTD.

Consultant and Engineer (Sound Recording and Reproduction)
Darby House, SUNBURY-on-THAMES, MIDDX

THE
BIGGEST and BEST RADIO COMPONENT CATALOGUE

Exclusive to Home Radio, this Catalogue comprises of 128 pages printed on high grade paper listing over 4,000 items with 400 illustrations. Includes full details of EDDYSTONE components and receivers. This Catalogue has been compiled from items actually held in stock. *An essential book for every engineer, constructor, laboratory, workshop, etc.* **Delivery BY RETURN. PRICE 2/- plus 9d. post.** Please mark envelope "Catalogue" in top left hand corner.

HOME RADIO OF MITCHAM

Dept. W, 187 London Road, Mitcham, Surrey. MIT 3282

TELETRON TAPEJAK

The first Transistorized Radio Tuner, specially designed for use with Tape Recorders.
★ High Sensitivity.
★ Twin tuned circuits.
★ Pre-setting for MW. Programmes
★ Fixed tuned for 1500M.

Price...... £5 9 0

THE TELETRON CO., LTD.
112B, Station Rd., London, E.4.
SIL. 0836.

THE ONLY
SUB-MINIATURE "3000 TYPE" RELAY

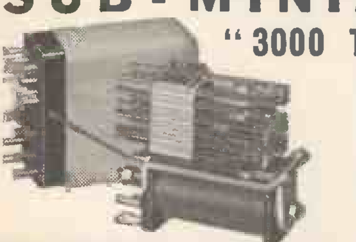

Made in England

Sole Distributors
D. ROBINSON and COMPANY
717 LONDON ROAD, HOUNSLOW, MIDDLESEX.

The Hopwood—Par Type P3 relay, although miniature retains every possible feature of the "3000 Type" plus ceramic insulation and hermetic sealing.

It can have up to 6 poles; twin or HD contacts and tags for PRINTED CIRCUITS.

Telephone:
HOUnslow 6266/7 & 8338

WRITE FOR LIST W.1

LYONS RADIO LTD.

SLYDLOK FUSE HOLDERS. 5 amp. 18/- per doz., 6 for 10/-, 3 for 5/6. 15 amp 19/6 doz., 6 for 11/9, 3 for 6/3, post paid. Reduced prices for larger quantities.
SUPPLY UNITS No. 19. Mk. 2. Rotary transformer units in metal cases 10 × 8 × 6in. Input 12 v. D.C. Output smoothed D.C., 500 v. at 50 mA., and 275 v. at 110 mA. In good condition. PRICE ONLY 45/-, carriage 7/6.
POWER UNITS TYPE SE8. Designed for mains operation of such installations as the SCR522. TR1430 etc. Input 200/250 v. 50 cps. A.C. mains. Output 300 v. at 200 mA. H.T., 150 v. at 20 mA., grid bias, 13 v. at 5 A. L.T., all fully smoothed D.C. Size 20 × 13½ × 11in. In good condition. PRICE ONLY £5/17/6, carriage 18/6.
UNIVERSAL MEASURING BRIDGES. Ex-Govt. by Mullards, measure 0.1 ohm. to 10 megohms, and 10 pfd. to 10 mfd. Can also be used to calculate power factor, with external standards can be used for the measurement of inductance also for percentage tolerance. Operate from 100 v. to 250 v. A.C. mains. Supplied in good condition and working order and operating instructions. PRICE ONLY £7, post 3/6.
INVERTERS. Known as Motor Generator type 7, Air Min. ref. 5U/3238. Input 23/24 v. D.C. Output 80 v. at 1,600 cycles, 240 vA. Carbon pile V/R and filter unit incorporated. In good condition. PRICE ONLY 45/-, carriage 5/-.
METER BARGAINS. Moving coil types, flush panel mtg. 2½in. dia.; 0/500 mA., 0/200mA., 0/100 mA., 0/50 mA., all at 9/6 each. 2in. dia. 0/100 mA., 8/-. Projection mtg. 2½in. dia. 0/1 mA., 17/6. Plug-in type 50/0/50 mA. 2½in. dia., 7/6. Postage 1/-.

3 GOLDHAWK RD., (Dept. M.W.), SHEPHERDS BUSH, LONDON, W.12

Telephone: Shepherd's Bush 1729.

Visit the City's popular accoustically designed

HI-FI Centre

STOCKISTS OF LEADING MAKES OF AMPLIFIERS, TUNERS AND SPEAKER SYSTEMS

AMPLIFIERS, STEREO AND MONAURAL, BY:		V.H.F. TUNERS BY:		HI-FI SPEAKERS BY:	
VERDIK	QUAD	ARMSTRONG	T.S.L.	GOODMANS	W.B.
ARMSTRONG	LEAK	LEAK	DULCI	PLESSEY	T.S.L.
ROGERS	W.B.	QUAD	ROGERS, etc.	WHARFEDALE	G.E.C.
DULCI	etc.			LORENZ	etc.

Another amazing scoop for the Hi-Fi enthusiast

Huge purchase of RCA equipment at enormous reductions

TO ALL CONNOISSEURS OF GOOD AMPLIFIERS, THIS OFFER IN LIMITED QUANTITY IS CAUSING QUITE A STIR.

THE NEW RCA ORTHOPHONIC AMPLIFIER
12–20 watt output; frequency response:—within 0.2 DB 20/25,000 CPS, within 0.5 DB 10/60,000 CPS; noise level:—85 DB below rated output, distortion:—total harmonic less than .01% at 10 watts; valve line up:—two EF86, two KT66, GZ32; dimensions:—16¼ × 8 × 7½in.; weight 32 lb.
Pre-Amp Input Mic., radio/tape high and low level, crystal p/up and magnetic p/up.
Output Tape and record, bass and treble, mixing facilities, low and high pass filter, valve line up:—one EF86, two ECC81. Dimensions:—12⅞ × 6⅛ × 3⅞in.
THE COMPLETE EQUIPMENT AT 29 gns. Carriage extra 15/-.

RCA PANORAMIC MULTIPLE SPEAKER SYSTEM
Beautifully made in walnut finish, using one 15in. Hi-Fi speaker. Response down to 25 c/s, 2—2½ m/coil tweeters. Response up to 20,000 c/s, crossover at 2,000 c/s. Cabinet ported bass reflex and acoustically damped. 25 watt rating. **FEW ONLY—£35.**

THE RCA VARIABLE RELUCTANCE PICK-UP
A new design variable reluctance pick-up. Cartridge completely protected: rom dust, damp and mechanical shock. Embodies an 8-pole balanced design providing the advantages of sensitivity and negligible hum with smooth and extended frequency response. Pick-up arm has simple tracking pressure selector and adjustable pedestal to suit all turntable heights. Fitted with dual sapphire stylus. Tracking pressure: micro-groove 5–7 gms., 78 r.p.m. 9–12 gms. Original price £13/9/6. **OUR PRICE £7/10/-.** Post and pkg. 1/6.

AUTO CHANGERS
Brand new snip in manufacturer's carton. RCA 4-speed auto-changers in maroon finish incorporating auto. and manual control. Complete with Ronette Studio turnover crystal pick-up with sapphire styli for L.P.s and 78 r.p.m. records and including 45 centre post for large hole records. **AT THE AMAZING PRICE OF £7/19/6,** plus 4/6 post and pkg.

TWO SNIPS FOR THE CONSTRUCTOR

THE FAMOUS RCA EQUIPMENT IN LIMITED NUMBERS

(1) Completely assembled with attractive control panel. Just connect units together.
RCA 10 watt p/pull amplifier, less than 1% distortion.
Valve line-up: 6BR7, 12AX7, 6BW6, 6BW6.
Frequency response: 25–20,000 c.p.s., bass, treble and balanced loudness feature.
Ideal for good quality reproducer. **AT THE VERY LOW PRICE OF £7/19/6.**
Post and pkg. 4/6.

(2) The Junior RCA 5–8 watt p/pull amplifier.
Valve line-up: 12AX7, 19AQ5, 19AQ5, 35W4.
Frequency response: 40–20,000 c.p.s. Completely assembled with attractive control panel. Just connect amplifier to power supply. **ONLY £6/19/6.** Post and pkg. 4/6.

THE LAST OF THIS ASTOUNDING OFFER

The VERDIK QUALITY TEN

10 WATT PUSH-PULL ULTRA LINEAR FEEDBACK

Reduced from makers price of 20 gns. Now only

£14.19.6

complete.

Fully guaranteed for valves and service.

Post & Pkg. 7/6.

Fully guaranteed

AMPLIFIER AND PRE-AMPLIFIER

HI-FIDELITY TAPE HEADS
Made by famous manufacturer. Brand new. Upper or lower track, record/play-back, high impedance giving up to 12,000 c.p.s. at 7½ I.P.S. output 5 m/volts at 1 KC at 7½ I.P.S. Erase heads low impedance.
Only 39/6 per pair. Post 1/-. *State upper or lower track.*

SNIPS IN TAPE ACCESSORIES
Brand new E.M.I. 7in. take-up spools in polythene bag, 3/9 each post free, 6 for 20/-. Brand new 5in. Scotch Boy take-up spools 3/3 post free. 6 for 18/-.
1,200ft. P.V.C. tape on plastic spools made by famous manufacturer, 21/- reel. Post & pkg. 1/-. 1,200ft. P.V.C. tape on 5¾ plastic spool, 22/6, plus 1/- post & pkg.
The New American Audio Tape with plastic base. Also supplied in green or blue at no extra cost.

3in. reel 150ft.	6/-
4in. reel 300ft.	10/6
5in. reel 600ft.	18/-

Post and packing 1/- per spool.

THE NEW "INSTANT" BULK TAPE ERASER
Can erase a spool of magnetic tape in a few seconds. Demagnetises oxide deposits on tape heads. Only 27/6 post free.

Electronics (FLEET ST.) Ltd

DEPT. B
152/3 FLEET ST., LONDON, E.C.4
Telephone: FLE 2833
Business hours: Weekdays 9-6. Saturdays 9-1.

Wilkinsons EST. 1921

METERS GUARANTEED

F.S.D.	Size	Type	Price
50 Microamps	2½in.	MC/FR	70/-
100 Microamps	3½in.	MC/FR	70/-
500 Microamps	2in.	MC/FR	25/-
500 Microamps	2½in.	MC/FR	37/6
1 Milliamp	2in.	MC/FS	27/6
1 Milliamp	2½in.	MC/FR	35/-
30 Milliamps	2½in.	MC/FR	12/6
100 Milliamps	2½in.	MC/FR	12/6
200 Milliamps	2½in.	MC/FR	12/6
500 Milliamps	3½in.	MI/FR	30/-
5 Amperes	2in.	MC/FS	27/6
15 Amperes	2in.	MC/FR	10/6
25 Amperes D.C.	2½in.	MI/FR	7/6
50-0-50 Amp.	2in.	MC/FS	12/6
30-0-30 Amp.	2in.	MC/FR	15/6
20 Volts	2in.	MC/FS	10/6
50 Volts	2½in.	MC/FR	25/-
300 Volts	2½in.	MI/FR	25/-

Postage on meters 1/6

CROSS POINTER METERS. 2 separate 100 microamp movements, 22/6.
MICROAMMETER. 250 F.S.D. 3½in. F.R. Sangamo Mod. S37. Scaled for valve voltmeter. Circuit available free. 55/-. Post 1/6.
CATHODE RAY TUBES. 2AP1 25/-, 139A 35/-, 5BP1 55/-. Post 3/-.
TEST PRODS. Retracting points, fused, flex and terminals, 5/6. Post 6d.

RELAYS P.O. TYPE 3000

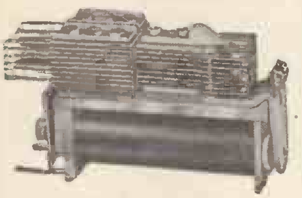

Build to your own specification

Keen Prices

Quick Delivery

Contacts up to 8-Changeover

SPECIAL OFFER. YOKES for Type 3000 Relays 30/- doz. Armatures 9/- doz. Armatures (adjustable) 18/- doz.

MINIATURE RELAYS:

Siemens High Speed Sealed.			S.T.C. and G.E.C. Sealed.			
2.2Ω+2.2Ω	H96A	15/6	2Ω	2 C O	4184GA	18/6
145Ω+145Ω	H96C	19/6	700Ω	2 C O	418GD	19/6
500Ω+500Ω	H96D	22/6	2500Ω	1 make	HD4186EE	22/6
1700Ω+1700Ω	H96E	25/-	2700Ω	2 C O	4184GE	21/6
Siemens High Speed Open.			180Ω	2 m 2 b	M1087	19/6
100Ω+100Ω	H85N	15/-	670Ω	4 C O	M1092	21/6
1000Ω+1000Ω	H95A	17/6	2500Ω	1 C O	M1022	22/6
1700Ω+1700Ω	H85L	17/6	5000Ω	2 C O	M1052	25/-

Comprehensive range available from stock.

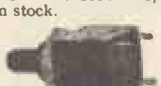

SWITCHES. 1 hole fixing, 3 amp. 250 volt. 1/6 each, 12/- doz.
RACKS—POST OFFICE STANDARD. 6ft. high with U-channel sides drilled for 19in. panels, heavy angle base, 4ft. 10in. in stock.
SOLENOIDS. 12 volt D.C. with 3½in. lever. Ideal for remote control, model railways. 5/- ea., post 1/6. Unit of 26, £4/6/8. Cge. 15/-.
NIFE BATTERY. Nickel cadmium. 6 volts 75 amps., crated and connected. Alkaline filled. Brand new, £7/10/-. Carr. 15/-.
LOUDSPEAKERS. P.M. Elac 5in. round 15/6, post 1/6. Axiom 150 dual cone 12in. 15 watts 15 ohms, fully dustproof, £7/19/6, post 7/6. Pye 10in. portable 3 ohms 50/-, carr. 7/6.

3 IN. ROUND PLESSEY SPEAKER, SEALED TYPE WITH PROTECTIVE GRILLE . . . 19/6, POST 1/6

JACK PLUGS. Cylindrical bakelite screw-on cover, 2 contact 2/6, post 6d.
SOCKETS. One hole fixing for above, 3/6. post 6d.
TELEPHONE PLUGS TYPE 201 with headphone cord, 3/- each, post 1/-. Large quantities available from stock.

TERMINAL BLOCKS. 2-way 4/- doz. or box of 50 for 15/-, 3-way 6/- doz., 50 for 22/6. Post 1/6.
AIR BLOWER. 230 volt A.C. 15in. fan. Volume of free air at max. r.p.m. is 1,250 cu. ft. per min. At maximum efficiency 900 cu. ft. per min. Brand new £25. Carr. 20/-.
XPELAIR EXTRACTION FANS. 7½in. blades, Baffle outlet 190/-. Cge. 5/-.
HEADPHONES. Balanced armature DLR5, 10/6 pr., post 1/6.
HEADPHONES. High resistance 4000Ω CHR, 15/- pr., post 1/6.
HEADPHONES. Balanced armature DHR, 17/6 pr., post 1/6.
LOUDHAILERS RE-ENTRANT TYPE all metal 15in. diameter with mounting bracket £6/10/-, carr. 10/-. Easco 15 ohms 8in. diameter with mounting bracket, £5/10/-, carr. 10/-., 18in. long by 12in. dia. with mounting bracket, £5/10/-, carr. 10/-.
AVO TEST BRIDGES. 220/240 volt A.C. Measure capacities from 5 pf. to 50 mfd. and resistances from 5 ohms to 50 megohms. Valve voltmeter range 0.1 to 15 volts and condenser leakage test. BRAND NEW. Full working instructions supplied with instrument. £9/19/6. Post 3/-.
OSCILLOSCOPE. Type 43. With 3½in. C.R.T. 138A, 4—617, 3—VR54, 5Z4, VU120. Brand New with usual controls, power pack and leads. Suitable for 230 volts, £10/10/-, carr. 12/6.

A LARGE AND COMPREHENSIVE STOCK OF WIRELESS AND ELECTRONIC COMPONENTS

TELEPHONES Easy to Fix Wiring Diagram Free

TELEPHONE SET TYPE "A" Ringing and speaking both ways on a 4-core cable. Very loud and clear over any distance. The handsets are as illustrated and the set is complete except wire. 4-core at 8d. per yard or 2-core at 3d. per yard extra. Price 75/- set, post 3/6.
SET B. Two headphones connected to breast microphones, with leads, plugs and fitted carrying cases. Join instruments together with two wires and 1½ volt battery for a super Intercom., 25/-, post 3/6.
SET "C" Similar to Set "A." Instead of P.O. Type handsets, two P.O. Desk Type Instruments are supplied with usual drawer in base. Complete ready for use. Price 150/-, post 7/-.

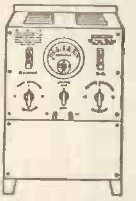

10 AMP BATTERY CHARGER

HERE IS YOUR CHANCE TO PURCHASE A BRAND NEW UNIT WORTH £40! FOR OUR SPECIAL PRICE **£17.10.0**
Carriage 20/-.

Input 200/250 v. A.C. 50 cy. Output 10 amps., 22 volts D.C. Controlled by two 4-position switches for fine and coarse control which enables 6 to 24 volt batts. to be charged. Brand new with 0/12 ammeter. Fused A.C./D.C.

ROTARY CONVERTERS. Input 12 D.C. Output 230 A.C. 50 cy. 135 watts. In fitted case with variable resistance, 0/300 voltmeter. The ideal job for television where A.C. mains are not available. £10. Carr. 15/-. Special connectors, one fitted with 6ft. heavy duty flex and clips for D.C. side. 10/- set, post 1/-. **CONVERTERS ONLY,** 12 volt or 24 volt. £8/10/-. Carr. 7/6.
BATTERIES. Portable Lead Acid type, 6 volts 125 ampere hours. In metal case 16in. × 18in. × 11in. (Two will make an ideal power supply for our 12 volt Rotary Converters). Uncharged £6/10/- each, carriage 15/-. 24 volts 85 ampere, £15 each, carriage 15/-.
UNI-PIVOT GALVANOMETER by Cambridge Instruments, 50-0-50 microamps., dia. 4in. Knife pointer, mirror scale. Complete with leather carrying case. Ideal for laboratory use. £10, carriage 3/-.
FLIGHT TO GROUND SWITCHES. 5C/2828 as used on aircraft. Very robust, will carry a very heavy current 25/- each; or in pairs with auxiliary switch 50/-, post 3/-.
SIGNAL GENERATOR TYPE 52A. Input 230 volt 50 cycles, complete with leads, dummy antenna. Brand new in transit case. 6 to 52 Mc/s. inclusive in 4 bands with calibration charts. Coarse and fine attenuators. Int. and ext. mod. Output 0.5 volt to 100mv., impedance 70 and 100Ω. £10. Carriage 10/-.
MAINS MOTORS. Capacitor 230 v. A.C. 1/40th h.p. 1,400 r.p.m. 55/-, post 3/-.
MAINS TRANSFORMER WITH RECTIFIER mounted on top. Giving a D.C. output of approx. 30 to 40 volts 1 amp. Price 27/6 each, post 2/6.
VARIAC TRANSFORMER. Input 230 ovlts. Output infinitely variable 0-230 volts and 0-270 volts. 9 amp., bench or panel mounting. £15, carr. 12/6.
SELENIUM METAL RECTIFIERS.
Charging Rectifiers. Full Wave Bridge.

12 Volts 1 Amp	8/6 each	24 Volts 1 Amp	13/- each
12 Volts 2 Amps	13/6 each	24 Volts 2 Amps	24/- each
12 Volts 3 Amps	16/6 each	24 Volts 3 Amps	28/- each
12 Volts 4 Amps	20/- each	24 Volts 4 Amps	36/- each

Discounts for quantities of above charging rectifiers.
MAINS TRANSFORMERS to suit above rectifiers.

12 Volts 1 Amp	12/6 each	12 Volts 4 Amps MT5	25/- each
12 Volts 2 Amps	24/- each CT109	12 Volts 4 Amps CT107	29/6 each
12 Volts 2.5 Amps	22/- each MT5B	24 Volts 3 Amps	25/- each

RESISTORS EX STOCK IN QUANTITY WIRE WOUND, HIGH STABILITY CARBON ETC., BEST MAKES AT LOWEST PRICE.

MAGNETIC COUNTERS
Counting to 9999.
2-6 v. D.C., 15/- each, post 1/6.

Type 16A 75/230 v. D.C. 15/- each, post 1/6.

HIGH SPEED TYPE No. 100c, 35/-, post 1/6.

SWISS TYPE COUNTER WITH ZERO RESET, 45/-, post 1/6.

VEEDER-ROOT MAGNETIC COUNTER. General purpose type with zero re-set. 800 counts per minute up to 999,999. 48 volt D.C. 55/-, post 2/6.
THERMOSTAT SATCHWELL, 12in. stem 0/250 volt A.C./D.C. 15 amps A.C. 10 to 90 degrees cent. 25/-, post 2/6.
ROOM THERMOSTAT. Adjustable between 45 and 75 deg. Fahr., 250 v. 10 amp. A.C. Ideal for greenhouses, etc., 35/-, post 2/-.
THERMOSTAT. For frost protection, on at 34 deg. F., off at 40 deg. F., 1½ amps. at 250 volts, adjustable, 4/6, post 1/-.
SIMMERSTAT BY SUNVIC. Plug-in type with knob control, 15 amps 3-pin 200/250 volts, 35/-, post 2/-.
BATTERIES FOR THE MODEL MAKER. MINIATURE—SILVER ZINC. VENNER TYPE H.105. 1.5 Volts 1.5 amp. hour. **Size:** Height 2in., width 1.13in., depth .63in., weight 1.25 oz. PRICE 17/6. Post 1/-.

L. WILKINSON (CROYDON) LTD.
19 LANSDOWNE RD. CROYDON SURREY
Phone: CRO 0839 Grams: WILCO CROYDON

Cooper-Smith

HIGH FIDELITY AMPLIFIERS

REALISTIC SOUND—
REALISTIC PRICES!

SUPPLIED DIRECT TO HI-FI ENTHUSIASTS ALL OVER THE WORLD
GUARANTEED 3 YEARS
LABORATORY BUILT OR IN DO-IT-YOURSELF KIT FORM

STEREO/MONAURAL

MAIN AMPLIFIER

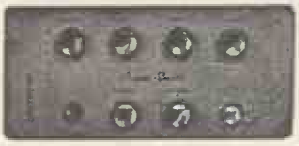

6W. Per Channel Distortion 0.15% Freq. 30-30K c.p.s. Hum and Noise — 80dB. Output Imp. 3 Ω, 8Ω, and 15Ω.
BUILT £15 15 0
KIT.......................... £12 12 0

CONTROL UNIT

Inputs: Gram (3mV.) Radio Tape (100mV.) Hum and Noise —70dB. Also suitable for use with two B.P.I.
BUILT £16 0 0
KIT.......................... £13 13 0

MODEL B.P.I. 10-12 WATT AMPLIFIER
Freq. 30-30K c.p.s. Distortion 0.1%. Hum and Noise —80dB. Output Imp. 3 Ω, 15Ω.
BUILT £14 5 0
KIT.......................... £12 5 0

CONTROL UNIT Mark II
Inputs: Gram (3mV.) Mic. (1.5 mV.) Radio and Tape (100mV.). Hum and Noise—70dB. Switched Filter.
BUILT £10 17 6
KIT.......................... £7 17 6

"BANTAM" 3-4 W. INTEGRATED AMP. & CONTROL UNIT
Bass and Treble Controls. Spare Power: 250V. 40mA. 6.3V. 2A. O.I. 3Ω, 15Ω.
BUILT £8 5 0
KIT.......................... £7 10 0

"PRODIGY" 6-9. W INTEGRATED AMP. & CONTROL UNIT
Distortion 0.15%. Inputs Gram. Radio, Tape, Spare Power 250V. 40mA. 6.3V. 2A. O.I. 3/8/15Ω.
BUILT £15 15 0
KIT.......................... £12 10 0

Full details and stage-by-stage building instructions 2/8 each, post free ("Bantam" 1/8) or free with each unit.

H. L. SMITH & CO. LTD. 287-289 EDGWARE RD., LONDON, W.2. Telephone: PAD 5891-7595

Training in Radio and Television Servicing

The Pembridge College of Electronics provides a full-time One Year course in the basic principles of Radio and Television for prospective servicing engineers. This course is also suitable for those wishing to maintain all types of industrial electronic equipment.

The next course commences on 26th April, 1960. Following course commences on 6th September, 1960.

Home-study courses in Radio and Telecommunications and also kits-of-parts are now available.

For details of these courses, write for prospectus and admission forms to :

The Principal, Dept. P11,
THE PEMBRIDGE COLLEGE OF ELECTRONICS
34a Hereford Road, London, W.2.
Telephone: BAYswater 9117

PC/9

NEW G.E.C., S.T.C. and "WESTALITE" SELENIUM RECTIFIERS. Largest L.T. range in Gt. Britain. ONLY Makers' LATEST GOODS supplied NOT Surplus. S. T. & C. E.H.T., K8/10 4/5; K8/15 5/-; K8/45 9/4; K8/50 9/10; K8/100 16/8; post 4d.

BRIDGE CONNECTED FULLWAVE. 17 v. 1 a. 13/4; 1.5 a. 26/6; 3 a. 30/6; 4 a. 38/-; 5 a. 38/6; 6 a. 48/-; all post 9d. 33 v. 1 a. 22/9 1.5 a. 45/- 3 a. 54/-; 5 a. 68/-; all post 1/6; 54 v. 1 a. 33/-; 1.5 a. 60/-; 2 a. 65/-; 3 a. 74/-; 5 a. 97/-; 72 v. 1 a. 78/-; 3a. 95/-; 5 a. 124/-; 6 a. 155/-; 100 v. 1 a. 61/-; 1.5 a. 112/-; 2 a. 116/-; 3 a. 134/-; 5 a. 180/-; 6 a. 220/-; all post 2/-.

BRIDGE CONNECTED WITH 7¾in. SQUARE COOLING FINS. 17 v. 10 a. 61/-; 12.5 a. 66/-; post 2/6.

BRIDGE CONNECTED HEAVY DUTY FUNNEL COOLED or 7¾in. SQUARE COOLING FINS. Both types, same price. 17 v. 20 a. 120/-; 30 a. 172/-; 50 a. 280/-; 33 v. 6 a. 89/-; 10 a. 102/-; 20 a. 202/6; 54 v. 6 a. 124/- 10 a. 144/- 72 v. 10 a. 186/-; 100 v. 10 a. 270/-; all post 3/-.

"WESTALITE" (BRIDGE) 12-15 v. D.C. 0.6 a. 12/-; 1.2 a. 30/-; 2 a. 32/6; 5 a. 37/6; 10 a. 64/6; 20 a. 117/6; 30 a 171/-; 50 a. 278/-; 24 v. 1.2 a. 30/-; 5 a. 60/-; 10 a. 109/6; 20 a. 208/- ; 36 v. 1.2 a. 47/6; 5 a. 82/6; 10 a. 154/6; 100 v. 1.2 a. 82/6; 2.5 a. 154/6; 5 a. 195/6; 10 a. 391/-; 170 v. 1.25 a. 135/-; 195 v. 1.25 a. 144/6; ½ WAVE RECTS. 150 v. 1 a. 33/-; all post 1/6-3/6 extra, E.H.T. Rects. 14D.134, 25/-; 36 E.H.T. 60 35/10; 1 mA. AC/DC meter rects. 14/6. Post 4d.

"SALFORD" (BRIDGE). 6 and 12 v. D.C. 1 a. 7/6; 1.5-2 a. 8/6; 2.5 a. 11/9; 3 a. 14/9; 4-5 a. 16/6; 6 a. 23/6; 10 a. 34/-; 14 a. 42/-; 24 v. 1 a. 12/6; 1.5 a. 14/3; 2 a. 15/6; 3 a. 26/-; 4.5 a. 29/6; 6 a. 36/6; 10 a. 75/-; other sizes. Post, under £1 add 1/-, over £1 add 1/6.
Suitable Transformers from 14/-. Post 1/6.

Wholesale and Retail

T. W. PEARCE

66 Great Percy St., London W.C1.
Off Pentonville Road,
Between King's Cross and Angel

CLEAN AND SILENT

D.C. to A.C.

UP TO 100 WATTS

WITH THE NEW FELGATE ELECTRONIC INVERTER

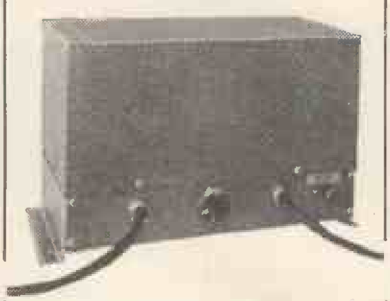

NO MOVING PARTS
FREQUENCY CONTROL

Manufactured by

RADIO MAILING LIMITED
STUDLAND HALL, STUDLAND STREET, LONDON, W.6.

RECO KITS

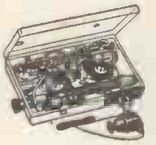

"RECO" MIDDY ONE TRANSISTOR KIT
(M/L or M/S Waves). Size 4⅞in. × 3¼in. × ⅞in. Variable sensitivity control Vari Q ferrite rod aerial. "Sonotone" min. dynamic earpiece with insert. Pencell battery. Complete kit with Ediswan transistor and easy build diagrams, 37/6. P.P. 2/-.

"RECO" PUSH-PULL FIVE KIT
M/L Waves
(Size: 6⅞in. × 4⅜in. × 1⅞in.)
As the Transigen Three but with Push-Pull output stage. Uses EDISWAN Transistors. New improved 3in. speaker. Complete kit £6/7/6. P.P. 2/6. Easy build practical wiring diagrams free with kit.

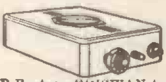

"RECO" TRANSIGEN THREE KIT
(M/L Waves)
Entirely self contained (no external aerial required). R.F. stage EDISWAN transistors. Combined volume and sensitivity control. On test (50 miles from London) tuned in the Home, Light, Third and in the evening Radio Luxembourg. A.F.N. and many others. Attractive pale blue polystyrene case with red grille. Sensitive B.A. Reproducer or "Sonotone" min. earpiece. Complete kit with easy build diagrams and battery, 77/6. P.P. 2/6.

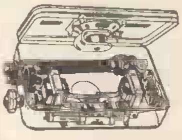

"RECO" PUSH-PULL FOUR KIT
(M/L Waves and 2 S.W.1 coils free.)
Four EDISWAN transistors. Volume control. 3in. speaker. Improved lay-out. Gleaming pale blue polystyrene case with red speaker grille. Complete kit with easy build diagrams and 3-volt battery. £5/3/6. P.P. 2/6.
Parts price list and circuits for the above kits 2/6 set of four.

AFTER SALES SERVICE
RADIO EXCHANGE COMPANY
(Dept. W.W.)
27 Harpur Street, BEDFORD
Closed 1 o'clock Saturdays Telephone Bedford 2367

RADIO CLEARANCE LTD.

TRADE ENQUIRIES INVITED

27 TOTTENHAM COURT RD., LONDON, W.1

The oldest Component Specialists in the trade

Telephone : MUSEUM 9188

EST. 30 YRS

ELECTROLYTIC CONDENSERS—WE HOLD THE LARGEST STOCK OF ELECTROLYTICS IN ENGLAND

ALL CONDENSERS AS ADVERTISED IN THE JANUARY ISSUE, PAGE 152, ARE STILL AVAILABLE

and now . . . RADIO CLEARANCE LTD. *proudly presents the greatest* ALL-TRANSISTOR CIRCUIT *of our time*

BUY AS YOU BUILD the "MIRACLE" Super Six Plus

ANY PART SOLD SEPARATELY

Makes up to a portable transistor superhet embodying all the latest design developments including a self-oscillating mixer, two double-tuned IF stages, audio amplifier and a matched push-pull output stage. Also two germanium diodes are incorporated, additional to the six Mazda transistors, one as detector and the other to assist the AGC as a variable damping element.

12 Good Reasons why the Miracle has no equal

- ★ Printed Board engraved with component locations
- ★ Special provision for use as a CAR RADIO
- ★ Double-tuned IF Transformers.
- ★ 6 First grade Mazda transistors plus 2 Mazda hi-gain diodes
- ★ Hi-flux 5in. (12000 lines) 25-ohm loudspeaker
- ★ Full coverage Medium and Long wavebands
- ★ 3½in. tuning dial with 5:1 slow motion
- ★ Long life dry battery. 150/200 hours
- ★ Internal high-Q Ferrite Aerial
- ★ Push-pull matched output stage 400 Milliwatts
- ★ 3½in. x 7½in. x 10in. two tone vyanide covered case—total weight approx. 4lb
- ★ Comprehensive Manual supplied—so easy to build

Our inclusive price for all components, cabinet and battery, complete in every detail :

£11.10.0

plus 3/6, Regd. p.p.

or any component part supplied separately at the published prices.

INSTRUCTION MANUAL AND CIRCUIT BOOK containing itemised list of all component prices, 3/6 post free. *See and hear a complete working model at our premises.*

MOULDED TROPICAL PAPER CONDENSERS

Small, non-inductive, insulated, high-grade Capacitors 150 v. wkg. .15 Mfd. 5% 10d. .22 Mfd. 10% 9d. 1 Mfd. 10% 1/3. 2 Mfd. 1/9. 2 Mfd. 10% 1/10. 250 v. Wkg., .068 Mfd. 9d. .1 Mfd. 1/1. .22 Mfd. 2% 1/4. 1 Mfd. 10% 1/7. 500 v. Wkg., 680 pF., 1,000 pF., 1,500 pF., 2,200 pF. 7d. each. 3,300 pF. 8d. 5,000 pF., 6,800 pF., .01 Mfd. 9d. each. 8,200 pF. 1/-. .022 Mfd., 03 Mfd. 10d. each. .047 Mfd. 2%, .05 Mfd. 11d. each. .1 Mfd. 11d. & 1/2. .2 Mfd. 5% 1/5. .25 Mfd. 1/6. .5 Mfd. 1/3 & 1/9. 750 v. Wkg., 470 pF. 10%, 820 pF., 1,500 pF., 2,000 pF. 8d. each. 5,000 pF., 6,800 pF. 9d. each. .022 Mfd. 10d. 1,000 v. Wkg., 1,500 pF. 9d. 6,800 pF. 10d. .01 Mfd., 1,500 v. 1/-. .12 Mfd., .15 Mfd. 1/1 each. .3 Mfd. 1/4. .3 Mfd. 10% 1/5.

VALVE HOLDERS

4 pin UX. 7d. 5 pin Brit. Pax. 2d. 7 pin Brit. Pax. 3d. 7 pin Brit. Amp. 4d. Int. Octal Pax. 3d. Mazda Octa Pax. 3d. Loctals Amp. 6d. B7G Pax. 6d. B7G P.T.F.E. 8d. B7G Cer. with saddle and valve retaining spring 1/-. B8A Pax. 4d. B8A Amp. 6d. B8A Cer. 8d. B9A Pax. 6d. B9A Amp. 6d. B8A Cer. 10d. B9A Cer. with saddle and valve retaining spring 1/-. B9A ceramic with skirt 1/-. B9A printed circuit 10d. B7G Valve Cans 6d. EY86 High voltage holders 1/3.

VARIABLE GANG CONDENSERS

Twin Gang 20 pF. Ideal for F.M. 2in. × 1¼in. × 1in. 2/-.
Twin Gang .0005 MFD. 2⅜in. × 2in. × 1⅝in. Spindle 5/16 in. 4/-.
Min. Twin Gang. .0005 MFD. 2½in. × 1⅜in. × 1⅛in. Spindle ¼in. 5/6.
Min. Twin Gang. .0005 MFD. 2½in. × 1⅜in. × 1⅛in. Spindle ¼in. with trimmers 6/6.
Twin Gang .0005 MFD. Geared with S.M. 3/6.
AM FM 2-Gang Condensers, 500 + 20 pF. 3/6.

DISC CERAMIC CONDENSERS 500 v. Wkg.

500 PF. .001 MFD. .0025 MFD., .002 MFD., .003 MFD. .005 MFD. 6d. each. .01 MFD. 9d.

TRANSISTOR COMPONENTS

SUB MINIATURE ELECTROLYTIC CONDENSERS —SLEEVED—All at 2/3 each.

.1 Mfd. 12 v., 2-6-8-10 Mfds. 3 v., 2-6-8-10-12-16-30-50 Mfds. 6 v., 1 Mfd. 10 v., .1, .5/30 Mfds. 12 v., .25 Mfd., 2 Mfds., 8 Mfds. 15 v., 8 Mfds., 16 Mfds. 30 v., 2 Mfds. 70 v.

SUB MINIATURE TRANSISTOR COILS

Set of 3 I.F. Transformers 470 Kc/s plus Oscillator coil.
As specified for Mazda Circuits 23/6 complete.
As specified for Mullard Circuits 23/6 complete.
WTC oscillator Coils for Jackson or Plessey Gang 4/6 each. WTC 470 kc/s. I.F. Transformers 4/- each, 7/6 pair.

SUB MINIATURE CARBON POTS

5K, 50K, 220K, 330K, 1M, 2/- each. 5M with switch, 4/6. 5K, 1/6. 500K preset 1/-. 1M Transistor Pots, 2/-. 5K Transistor Pots, 1/6.

SUB MINIATURE METALLISED PAPER CONDENSERS ¾in. × ½in. 100 v. working.

.005 MFD., .0022 MFD., .002 MFD., .001 MFD., 8d each. .01 MFD., .02 MFD. Price 9d. each.

TRANSISTOR GANG CONDENSERS

With intermediate screen as specified for MULLARD Transistor Circuits 9/6.
As above with switch for L.W. pre-selection 11/-.

MIN. POLYSTYRENE CONDENSERS

10 pF., 100 pF., 500 pF., 1,000 pF. 125 v. wkg. 6d. each.

TV PRESET CONTROLS

Knurled knob and 6BA fixing holes. Diam. 1in. 5K, 25K, 50K, 100K, 250K, 500K, 2M 1/3 each. 25K wirewound 1/6.

SWITCHES ROTARY

Size 1 5/16 in. dia.-2in. spindles. Price 2/11 each.
1 pole 10 way. 1 pole 12 way. 2 pole 2 way. 2 pole 3 way. 2 pole 4 way. 2 pole 5 way. 2 pole 6 way. 3 pole 3 way. 3 pole 4 way. 4 pole 3 way.

POTMETERS CARBON—HI-GRADE

Moulded Tracks. Diam., 1in., 2¼in. spindles. 5K 10K, 25K. Linear only. 50K, 100K, 250K, 500K, 1M, 2M, Log or Linear, less switch, 2/6 each. With switch 4/6.

TRANSFORMERS

Audio Output Types. 6,000Ω to 3Ω 3/6. 10,000Ω to 3Ω 3/9. 13,000Ω to 3Ω 4/-.
Universal CRT Boosters with tapped primaries 2 v. 6.3 v. 13 v., 25% boost all taps, 10/6. Filament transformers, centre tapped, 6.3 v. output, 1.5 amp., 5/9; 3 amps. 9/6.

MODERN TV COMPONENTS

Ferox Line O/P transformers, 16 Kv. U25 19/6. Frame O/P transformers to match 4/6. Scanning Coils to match 15/-. Panel containing 6 preset pots 5/-. Smoothing Chokes: 2 Hy. 250 mA. 3/11. 1.9 Hy. 250 mA. 2/11. 1.3 Hy. 250 mA. 2/6.
G.E.C. Metal Rectifier 250 v. 250 mA. 10/-. 34 Meg. I.F.T. 1/6 ea. 38 Meg. I.F.T. (link) 2/- ea. Masks 14in., 17in. and 21in. 2/6, 3/6, 4/6 (plus 2/6 p.p.).

MISCELLANEOUS

Genuine OC71 Transistors 6/6. Crocodile clips 4d. Coax. Plugs and Sockets 2/2 per pair. Condenser clips 1in. and 1⅜in. 6d. ea. Parmeko Smoothing Choke 8/9 Hy. 100 ma. 6/6. 500 pF. 15 Kv. moulded Condensers 2/6. WX2s Westector 6d. Elliptical Speakers 7in. × 4in. 12/6. 100 assorted first class Erie resistors 12/6. Transistor Twin gang condensers 287 + 166 pF., ex equip. 4/6. Vibrator Has Chokes 1/-. Ext. Loudspeaker panel with switch 1/-.

We have an extensive range of Waxed Paper Condensers (average price 5d. ea.). Metallised Paper Condensers (average price 11d. each) and Wirewound resistors 5/6/7-watt types (average price 1/- ea.).

STAMPED AND ADDRESSED ENVELOPE with any enquiry please. *PLEASE ALLOW FULL POSTAGE AND PACKING CHARGES.*

TERMS OF BUSINESS: CASH WITH ORDER OR C.O.D. ON ORDERS OVER 10/-.

LEWIS have the CABINET for YOU

EXTENSIVE RANGE OF CABINETS FROM £4-7-6

THE GROSVENOR
Price £19.19.0

This elegant cabinet is available in veneered figured walnut and polished to a high glass in a medium shade. Gold embellishments are an attractive feature of the design. 9in. black legs are normally fitted. A three sliding door system reveals ample storage room and space for equipment.

THE BUREAU
Walnut £16.16.0

This popular bureau cabinet is veneered with the finest selected Walnut and beautifully polished in a medium shade. Designed to accommodate almost any of the many units we have available and to give generous storage compartments.

TWO NEW LEWIS CATALOGUES:—

FREE!

The Cabinet Catalogue

The Equipment Comparator Catalogue

(Designed to assist your choice of cabinet and equipment).
Please send me details of your two new catalogues

Name ....

Address ....

....
BLOCK CAPITALS PLEASE WW20

LEWIS radio

120 GREEN LANES, PALMERS GREEN LONDON, N.13 (Near the Cock Tavern).
Telephone: BOWes Park 1155/6

MANY AIRCRAFT FIRMS FIND A.A. BENDERS OF REAL SERVICE.

SO WILL YOU

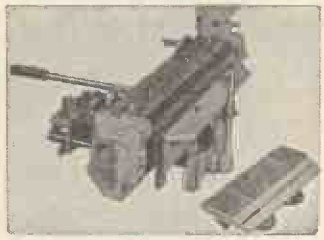

This UNIQUE BENDER

Quickly and Accurately Forms

Angles, Channels, Sections, Boxes, Lids, Trays, Chassis Brackets, Clamps, Clips, Shrouds, etc.

Something quite NEW!

Type RO-20

For private research workers and small units. This is similar in general design and finish to the RX-20 shown above, but is lighter and less expensive.

For 6-page Folder write to:—
A. A. TOOLS (W)
197a Whiteacre Rd., Ashton-u-Lyne

SCOTLAND'S LARGEST STOCKISTS OF GOVERNMENT SURPLUS

RADIO & ELECTRICAL EQUIPMENT

ALL ITEMS NEW AND UNUSED. ALL PRICES INCLUDE POST AND PACKING SCOTLAND AND ENGLAND.

SOLENOID by Westool 250V AC, 2¼ x 2in., 1½in. LEVER 3½lb. Pull., .8 amps. Mounted on brass base, 5½ x 2in. 14/6
MAINS DIMMER. 230 ohms. 1.5/.36 amps. Spiral shaft, knob control 22/6
MUIRHEAD STUD SWITCH. 24 position 7/6
PULLIN GEARED MOTOR. 250 v. A.C./D.C. Series wound, double end drive, 6,000 r.p.m., 200 r.p.m., 1/40 h.p. 37/6
TRANSFORMERS AND CHOKES, PARMEKO, NEPTUNE SERIES, ADMIRALTY RATING.
(1) Primary 112 v. and 230 v., 50 cycles. Output 400-0-400, 400 mA., 50 v. 2 mA. 40/–
(2) Primary 112 v. and 230 v., 50 cycles. Output 350-0-350, 200 mA., 6.4 v. 6 amp., 5 v. 3 amp. 30/–
(3) Primary 115 v., 225 v. and 240 v., 50 cycles. Output 45-0-45, 250 mA., 5 v. 2.8 amps., 5 v. 5.6 amps., 6.3 v. 4.5 amps. 25/–
(4) Choke 10 H. 25 mA. 9/6
Auto-Transformer. 3KVA Air Cooled (100% under-rated). Brand new in case. 230/250 tapped, 12 amps. 105/120 tapped, 28.5 amps. Weight 2 cwt. £15 carriage paid.

Terms C.W.O.

R.M.E. SURPLUS SUPPLIES
143, STOCKWELL STREET, Glasgow, C.1
Telephone: Bell 2634

SOUTH SUPPLIES

(ELECTRICAL) LTD.
95 OLD KENT ROAD, LONDON, S.E.1.
Tel.: BERmondsey 5810
CASH WITH ORDER

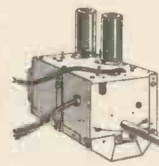

12 - CHANNEL TURRET TUNER

BRAND NEW. Fitted with coils 1 to 5 and 8 to 9. 34/38 Mc/s. Complete with P.C.F. 80 and P.C.C. 84 Valves.
Manufacturer's price £7/7/0.
OUR PRICE **£1.17.6** Plus P & P. 3/6.

ELECTRIC CLOCK, AUTO COOKER TIMER & TIME SWITCH

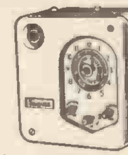

BRAND NEW. Modernise and add pounds to the value of your electric cooker. Ideal for automatic cooking, or any heat or current control. Complete with handsome electric clock. 200/250V. 30 Amp. Full fitting instructions.
OUR PRICE **£3.17.6**
Plus 2/6 P. & P.

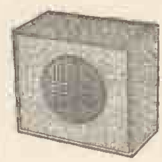

8″ LOUDSPEAKER IN CABINET

Beautifully finished in Leather cloth.
ONLY **22/6**
Plus 2/6 P. & P.

FAN or PROJECTOR MOTOR

220/250 V. BRAND NEW
22/6
Plus 2/6 P. & P.

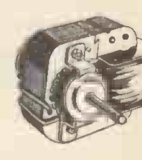

ENCLOSED MAINS FAN MOTOR

200/250 V. A.C. BRAND NEW. **22/6**
Plus 2/6 P. & P.

B.T.H. FAN MOTOR

200/250 V. A.C. Plus 2/6 P. & P. **32/6**

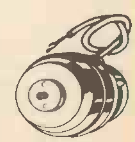

ELECTRIC BLOWER

12 or 24 V. Ideal for Car heaters. Plus 2/6 P. & P. **17/6**

TANK IMMERSION HEATER

Complete with separate Thermostat. 200/250 V. Famous make. Ideal Frost prevention, Photo developing trays etc. List £3/0/0.

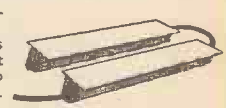

TO CLEAR **22/6** Plus 2/6 P. & P.

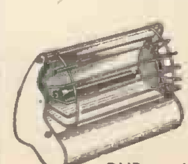

1 KW. ELECTRIC FIRE

Chrome reflector. Fully enclosed back. Made to sell at £2/5/–. BRAND NEW.
OUR PRICE **19/6** Plus 3/– P. & P.

Premier RADIO CO

23 TOTTENHAM COURT RD., LONDON W.1. Tel: MUSeum 3451/2

★ VISIT OUR NEW BRANCH AT **309 EDGEWARE RD., W.2.** TEL.: PADdington 6963

The 'Carol'

TR/1 TAPE RECORDER

INCORPORATING THE NEW B.S.R. TAPE DECK. A Quality Tape Recorder at a price that YOU can afford.

The operation of this Recorder is simplicity itself and the quality in both reproduction and finish, leaves nothing to be desired, the cost being well below present-day prices.

STAR FEATURES:
Deck Controls. Record/Playback Switch and rewind switch with interlocking device to prevent accidental erasure.
Speed. Single 3¾in. per sec.
Playing Time. 5¾in. Standard Tape 1¼ hrs. L.P. Tape 2 hrs. 8 mins.
Inputs. Sockets for Microphone, Radio, Gram, etc., with extension Speaker Socket.
Amplifier Controls. On/off Tone and Volume Controls.
Power Output. 2½ watts.
Valve Line-up. ECC83, ECL82, EZ80.
Overall Size. 13½ × 12 × 8in.
Weight. 20 lb.
Microphone. Acos crystal with stand incorporated and fitted with screened lead and jack plug.

PRICE, including Tape and Spare Spool **Only 19 Gns.** plus 15/- P. & P.

H.P. TERMS: £2 deposit and 12 monthly repayments at £1/12/11.

THE "Petite" PORTABLE

MAY BE BUILT FOR **£7-7-0**

plus 3/- post & Pkg.
Batteries extra.
H.T. 10/- (Type B126) or equivalent.
LT 1/6 (Type AD 35) or equivalent.

★ High Q frame aerials.
★ High sensitivity on both wavebands.
★ Medium and long wave superhet circuit.
★ Instruction book 1/6.
★ Size only 8in. x 8in. x 4½in.
★ Weight including batteries 5½lb.
★ 4 valves of the economy type.

WHY NOT CONVERT YOUR BATTERY PORTABLE TO MAINS OPERATION WITH THE COSSOR MU2 BATTERY ELIMINATOR. SUITABLE FOR PREMIER "PETITE"

This Eliminator is completely assembled and supplied with 4ft. of Mains Lead and Torpedo-type of On/off Switch. It is housed in 2 Metal Containers approximately the same size as the AD35 and B126 Batteries, and suitable for such Receivers as the Cossor 543, 551 and 552 or Receivers operating on 1.4 volt L.T. and 90 volt H.T. for use on 200-250 v. A.C. mains. Size: L.T. unit 3in. × 2⅜in. × 1⅛in., H.T. Unit 4in. × 2⅜in. × 2in. Original Price 3 Gns. OUR PRICE for a limited period only, 37/6 plus 2/- P. & P.

RECORD CHANGERS

B.S.R. Monarch U.A.8 4-speed auto changer	£6 19 6
Collaro Conquest 4-speed auto changer	£7 19 6
Garrard R.C. 120 M.K.2 4-speed auto changer	£8 19 6

Postage and packing on above units 5/- each.

Unrepeatable Bargains ! ! !

THE FAMOUS COSSOR 3 WATT AUDIO AMPLIFIER KIT 562K

ORIGINAL PRICE £9/15/-
OUR PRICE **£5.19.6** P. & P. 2/6

This Kit assembled will provide a compact versatile Amplifier which incorporates the most up-to-date pre-assembled printed circuit and is suitable for operation from Radio, Microphone or Gramophone. The circuit design includes negative feedback, valve line-up 6V4, 6BQ5, EF86. Two Loud-speakers are used, i.e., 10 × 6in. Elliptical and 4in. Treble, ensuring high quality output, suitable for use on 200/250 v. A.C. mains. All items are supplied, including Loudspeakers, Knobs and Escutcheon, with full assembly instructions and in makers' original carton.

SPECIAL OFFER—LIMITED QUANTITY ONLY

A 5-WAVEBAND AM/FM RADIOGRAM CHASSIS
(By Famous Manufacturer)
PRICE **£17.19.6**
plus 5/- P. & P.

A really good quality Chassis with outstanding features: Valve line-up ECC85, ECH81, EF89, EABC80, 2/EL84, ECC83, EZ81; waveband coverage, long, medium, two shorts and F.M. Power Pack and push-pull output stage mounted on separate chassis. Fly-wheel tuning; pickup and extension speaker sockets provided, and edge lit facilities for quality tape recording or playback. Glass Dial supplied suitable for either horizontal or vertical mounting and finished in black with gold lettering. H.P. Terms: Deposit 36/- and 12 monthly repayments at 29/9.

THE "MID-FI"

A NEW DESIGN 4½ WATT AMPLIFIER KIT MAY BE BUILT FOR **95/-**
Plus 3/- P. & P.

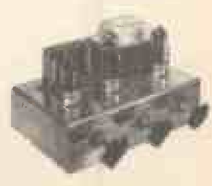

A new circuit for the home constructor requiring a good-quality medium-powered Amplifier for reproduction of Records of F.M. Broadcasts. Technical Specifications: separate bass and treble controls. Valve line-up EF86, EL84, EZ80. Voltage adjustment for A.C. mains from 200/250 volt 3 or 15 ohms impedance. Negative feedback. Size 7 x 5 x 2in., overall height 5in. Silver-hammered finished Chassis.

RCA VICE-PRESIDENT 8-10 WATTS PUSH-PULL AMPLIFIER

A compact versatile Amplifier complete with plug-in Power Pack, valve line-up HY90, 2 - 19AQ5 and 12AX7, separate bass and treble control, suitable for Speakers of 15 ohms impedance and two 3-ohm tappings for Tweeters. For use on A.C. mains, tappings 115-150 and 210-250 can also be supplied with Power Pack suitable for AC/DC mains. PRICE COMPLETE WITH ESCUTCHEON AND KNOBS, £6/19/6, 3/6 p. & p.

RCA PRESIDENT 10-WATT PUSH-PULL AMPLIFIER

A well-designed compact Amplifier with 10 watts push-pull output; specifications: valve line-up 6BR7, 12AX7, 2 - BW6 and Metal Rectifier. Separate Power Pack and separate Control Panel incorporating Volume On/Off, Bass and Treble Controls, suitable for Speakers of 15 ohms impedance with separate tappings for two 3-ohm Tweeters, for use on A.C. mains 110-150 and 200-240. PRICE COMPLETE WITH ESCUTCHEON AND KNOBS. £7/19/6, 3/6 p. & p.

RCA TRANSCRIPTION PICK-UP

A superb transcription Pick-up with variable reluctance cartridge and finger-tip weight adjustment for accurate settings. Suitable for standard and L.P. recordings. PRICE FOR LIMITED PERIOD ONLY, £8/10/- plus 2/6 p. & p.

SOUTHERN RADIO'S SPECIAL BARGAINS

TRANSMITTER - RECEIVER

TYPE 38 MK. II

★ WALKIE-TALKIE ★

Complete in Metal Carrying Case. 9in.× 6¾in.×4in. Weight 6lb. Frequency 7.3 to 9 Mc/s. Five valves, £1/2/6. Post paid.

These TX-Rs are in NEW CONDITION, but owing to demand they are not tested by us and carry no guarantee, but should prove SERVICEABLE.

ATTACHMENTS for Type "38" Transreceivers. ALL BRAND NEW. Headphones 15/6; Throat Microphones 4/6; Junction Boxes 2/6; Aerials, No. 1 2/6; No. 2 5/-; Webbing 4/-; Haversacks 5/-; Valves—A.R.P. 12 4/6; A.T.P.4 3/6; Set of FIVE VALVES 19/- the set.

SPECIAL OFFER No. 2: "38," as above, complete with set of external attachments, 42/6, post paid.

SPECIAL OFFER No. 3: Transmitter-Receiver "38" Mk. II. Brand new with complete set of external attachments including Webbing, Haversacks and Valves. 57/6 post paid. Fully guaranteed.

CONDENSERS. 100 assorted Mica; Tubular, etc., 15/-. NEW.

CONTACTOR TIME SWITCHES. 2 impulses per sec., in case, 11/6.

REMOTE CONTACTOR. For use with above, 7/6.

LUFBRA HOLE CUTTERS. Adjustable ¾in. to 3½in. For Metal, Plastics, etc., 7/-.

MAGNETS. Strong Bar type, 2×½in., 1/6 each.

MORSE TAPPERS. Midget type, 2/9; Standard, 3/6; Heavy type on base, 5/6. ALL BRAND NEW.

MORSE PRACTICE SET. TAPPER with **BUZZER** on base. Complete with battery, 12/6. BRAND NEW.

PACKARD-BELL AMPLIFIERS. Complete. BRAND NEW, with valves, relay, etc., etc., 17/6 each.

QUARTZ CRYSTALS. Types F.T.241 and F.T.243. 2-pin, ½in. spacing. Frequencies between 5,675 kc/s. and 8.650 kc/s. (F.T.243), 20 Mc/s and 38.8 Mc/s (F.T.241, 54th Harmonic), 4/- each. ALL BRAND NEW. TWELVE ASSORTED CRYSTALS, 45/-. Holders for both types, 1/- each. Customers ordering 12 crystals can be supplied with lists of frequencies available for their choice.

RECORDING BLANKS. Brand new. "Emidisc." Ready for cutting. 13in. 6/- each or 15 complete in metal case £4.

RESISTANCES. 100 assorted useful values. New wire end 12/6. NEW.

SPECIAL OFFER. 12 ASSORTED METERS. Slightly damaged. Mainly broken cases (perfect movements). Including 3 BRAND NEW Aircraft Instruments. 12 for 45/-.

STAR IDENTIFIERS. Type I A-N Covers both Hemispheres, 5/6.

T1154 TRANSMITTERS. Complete in transit case. New condition, £2/5/-.

TEST METERS D.C. PORTABLE 0-5,000 ohms 0-6mA 0-1.5v and 3v. In case 3¼in.×3¾in.×2½in. Voltage range can easily be extended by addition of resistances to suit individual requirements. Brand new, 12/6.

ATTACHMENTS for "18" Transreceivers. ALL BRAND NEW. Headphones 15/6; Hand Microphone 12/6; Aerials 5/-; Set of 6 Valves 30/-.

TRANSPARENT MAP CASES. Plastic 14in.×10¾in. Ideal for Maps, Display, etc., 5/6. *Post or carr. extra. Full list Radio Books, etc., 3d.*

SOUTHERN RADIO SUPPLY, LTD.

11, LITTLE NEWPORT STREET, LONDON, W.C.2. GERrard 6653

"BARGAINS WITH PERSONAL SERVICE"

COMMUNICATION RECEIVER R206. 30-0.55 Mc/s. in 6 ranges, separate power pack for 110/230 v. a.c., 12 v. d.c. vibrator pack included, slightly used but in good condition, £19/10/-, carriage 30/- (Mainland). Frequency Adaptor for same with 3 further ranges, 600-50 kc/s., 55/-, carriage 5/- (Mainland). Size 24×13×17in.

COMMUNICATION RECEIVER R107. 9 valve, 3 band, 1.2-17 Mc/s. 18-250 metres. 110/230 v. a.c. and 12 v. d.c., for mobile operation, used but in good condition, from £7/19/6, carriage £1 (Mainland). Size 24×13×17in.

TX/RECEIVER No. 19. 2-8 Mc/s (150-37 metres) in 2 bands, also 230-240 Mc/s V.H.F., 12/24 v. operation. Mk. II model, as new, 70/-; Mk. III, 80/-, carriage on both 12/6 (Mainland). Complete station set, supply unit, variometer, etc., £8/10/-, carriage 25/- (Mainland).

MARCONI TF987/1 NOISE GENERATOR. Range 100 kc/s-200 Mc/s., 230 v. a.c. input, brand new, £21, carriage 10/- (Mainland).

FREQUENCY METER BC221, as new, £32/10/-, carriage 10/-.

SIGNAL GENERATOR, TYPE TS.13/AP. "X" Band. £65, inc. carriage.

AVOMINOR UNIVERSAL TESTMETER. As new, in leather case, 75/-. P.P. 2/6.

ROTARY CONVERTORS. 24 v. d.c. input, 230 v. a.c. 50 c. 100 watts output, brand new, £4/10/-. Ditto, 125 watts, £4/17/6. A few of these models, store soiled, at a reduction of 10/-. Ditto, 150 watts new £5/10/-, with sliding resistor for same £6. Carriage on all the above 7/6 outside mainland extra.

ROTARY CONVERTOR. By Lancashire-Crypto, 24 v. d.c. input, 230 v. a.c. 50 c. 135 watts output in wood carrying case, with 3-pin flush output socket, absolutely brand new and unused in original packing case, £7/19/6, carriage 10/-. A small number left, 24 v. d.c. input, 50 v. a.c. 50 c. 4 amps. output in steel case, £2/10/-. Auto transformer 50/230 v. to suit same, £1/10/-, carriage on each 5/-.

GRIMES (U.S.A.) SEARCHLIGHT SIGNALLING SPOTLIGHT. 12/13 v. approx. 80 watts sealed beam, pistol grip handle incorporating micro switch, separate on/off switch, 20ft. tough rubber flex, size overall 7in. × 7in. × 12in., weight 5lbs. Superb light, just the job for boats etc. BRAND NEW, only 45/-, P. & P. 2/6.

CONTROL JUNCTION BOX. Type 165, Ref. No. 10D 19102, incorporating 2 high speed 670 ohms sealed relays, also 2 Co-Axial relays with miniature Coax. sockets. Brand new, few only, 35/-. P. & P. 2/6.

BATTERY CHARGERS. 230 v. a.c., input, 24 v. d.c. output at 10 amps. with meter, fine and coarse controls enables 6, 12, or 24 v. batteries to be charged, fused with on/off switch, £9/10/-. Carriage £1 mainland.

RECTIFIER SETS. 230 v. 1 ph. input, 24 v. d.c. at 26 amps. output, £12/10/-; 230 v. ditto, 36 v. at 50 amps. output, £17/10/-; 230 v. ditto 3 ph., 36 v. at 50 amps., £20. 380/440 v. 3 ph. input, 36 v. d.c. at 50 amps. output £27/10/-.

NIFE ALKALINE BATTERIES. 25 a.h., 1.2 v. per cell, 10/- ea. P. & P. 1/6.

CONDENSERS. "Pyranol" oil filled 10μF 2 kv. wkg. (part of the Transmitter ET4336) 22/6 ea.; 1 dozen lots at 19/- ea.; 50 to 100, 16/- ea. Packing and carriage at cost.

TELEGRAPH LINEMEN'S SAFETY BELTS. Leather 2in. × ¼in. double buckles, with safety catch, a must for all climbing purposes. Brand new, 17/6. P.P. 2/-.

HAND MICROPHONE. Moving coil No. 13, round 2¼in. diameter, with thumb press switch, brand new, only 12/6. P.P. 1/-. Inserts for same, 4/6. P.P. 6d.

ANTENNA CURRENT INDICATOR. U.S.A. New 2¼in. flush, 8/6. P.P. 6d.

AERIAL VARIOMETERS. Part of 19 set Mk. II. New. 13/6. P.P. 1/6.

373 MINIATURE I.F. STRIP. F.M. conversion, 9.72 Mc/s. complete with 6 valves. Conversion details "P.W." April 1957. Now only 29/6. P.P. 1/6.

CONTROL UNIT, U.S.A. Case 12 × 6 × 3in., hinged lid, with 1 mA. 2¼in. meter flush fitted, 5 micro and 2 toggle switches, relays, condensers and other components, wonderful bargain, 22/6. P.P. 2/6.

Terms. C.W.O. or approved monthly accounts S.A.E. inquiries.

A. J. THOMPSON

"EILING LODGE," CODICOTE, HERTS.

Phone : Codicote 242

ELECTRICAL MEASURING INSTRUMENTS REPAIRED

1. *Considerable reductions in your overheads!*
2. *Prompt Quotations and Service!*
3. *Urgent orders given priority attention!*
4. *Guarantee of satisfaction!*

We specialise in the repair of all types and makes of Voltmeters, Ammeters, Microammeters, Multirange Test Meters, Electrical Thermometers, etc.

As contractors to the Ministry of Supply, General Post Office and other Government Departments, we are the leading Electrical Instrument Repairers in the Industry. No enquiry is too big or too small. For prompt estimate and speedy delivery send defective instrument by registered post, or write to Dept. WW

L. GLASER & CO., LTD.,

96-100 Aldersgate St., London, E.C.1. Tel. MON 6822

BARGAINS FROM PORTLAND ELECTRONICS

POWER PACKS. Input 110-200-220-240 v. 50 cycles or 12 v. D.C. OUTPUT 200 v. 60 ma. and 2, 100 v. 80 ma. one +ive and one −ive to earth. Unit is **BRAND NEW** and contains a wide assortment of useful power components including 4 8 MF 350 v. paper condensers, 2 chokes, 2 100 v. bridge metal rects. and 2 250 v. ½ wave metal rects. Also a 5 pole c/o heavy duty rotary switch with silver contacts, Slydlock fuses and several small components and a potted double screened mains transformer as advertised previously at 12/6. (Output from vibrator winding 24 v. C.T. 3 amps.) Less barreters and vibrator but with full details of input and output corrections, etc. A real snip at 27/6 each.

CONDENSERS. T.C.C. Tubular "METALPACK" 0.1, 500 v. Brand new. 7/6 dozen.

TOROIDAL CHOKES. S.T.C. 1 mH. on a ferrite ring. High Q and ideal for filter applications. 3/- each.

PRECISION POTENTIOMETERS. Colvern 50K. 4in. cam corrected with centre tap. Only slightly used and exceptional value at 15/- each. Ideal for bridges, etc.

SPECIAL OFFER. A few **FURZEHILL B.F.Os.** No. 5 left, reduced to £9/15/- each. Here is a chance to obtain an excellent instrument at a rock-bottom price. Range 0-10 k/cs. 2 watts output. Supplied in excellent condition with 7 valves and in good working order.

MISC. NEW ITEMS. Valves. EF91, 6C4, 3/-. 4313C 3/6. 3A4 4/-. 6SN7 5/-. CRTs, 5CP1, 20/-. 5FP7 15/- each. Wearite I.F.Ts. 6/6 pair. Heinemann circuit breakers 2½ A. 5/6 each. W/W pots 50 ohm 1/3. 5 K. 1/6. 50 K. 1/9. 100 K. log. Carbon 1/3. 230 v. A.C. solenoids, very powerful pull, ⅜in. stroke. 8/6 each.

METERS. 5 ma. F.S.O. Scaled 0-15, 0-75, 0-150. 3in. scale flush round mtg. Brand new by leading U.S.A. manufr. 12/- each.

TRANSMITTER Type 53. Less relays but with 3 807 temp. stabilized V.F.O. and many useful components. Freq. range 2.4-13 Mc/s. 12/6 each.

RECEIVER Type 78. 2.4-13 Mc/s. V.L.U. EF50, ECH35, 6J5, EA50, EF39. Has very accurate tuning dial and temp. stabilized local osc. Complete with 100 Kc/s. calibrator assembly with Xtal and Desynn trimmer. Requires external I.F. and Det. Range 2.4-13 Mc/s. £2 each.

All prices include post and packing. Terms C.W.O.

20 PORTLAND PLACE, STALYBRIDGE, CHESHIRE

R. GILFILLAN & CO. LTD.

National Provincial Bank Chambers, 29 South Street, Worthing, Sussex. Tel.: Worthing 8719 & 30181

VALVES: New, Tested and Guaranteed

Type	Unit Price
1A3	2/6
1A5GT	3/6
1L4	3/-
1L5	5/6
2A3	6/6
2D21	7/6
2X2	1/9
2X2A	1/6
3A4	3/6
5W4GT	10/6
5Z3	7/6
5Z4G	4/-
6A6	5/6
6AB7	12/6
6AC7	5/6
6AG5	3/9
6AM5	7/6
6C6	2/6
6D6	2/6
6F6	3/6
6F7	12/6
6G6G	2/6
6H6GT	1/6
6J5	4/6
6L7	5/9
6N6GT	10/6
6N7GT/G	3/6
6Q7	7/6
6SA7	6/6
6SC7GT	5/6
6SK7GT	2/9
6SS7	4/6
6ST7GT	6/-
6ST7	4/6
6Y6	10/6
9D6	9/6
12AH7GT	6/6
12AU7	6/6
12H6	3/6
12SG7	5/6
12SJ7	6/6
12SR7	6/6
25L6GT	6/6
75	10/6
84	11/6
606	6/6
805	20/-
807 (U.S.A.)	3/6

Type	Unit Price
808	3/6
832A	30/-
837	8/6
953	5/6
955	3/-
956	2/6
9001	4/3
9003	4/3
9006	3/6
2051	10/6
5654 / 16AK5W / CV4010	16/6
ARP9	7/6
ARP12	3/6
ARP35	4/6
AR12	6/6
AU5	8/6
D1	5/6
DDR3	12/6
E1190	8/6
E1323	6/6
EAC91	3/6
ECC31	6/6
ECH35	6/6
EF22	6/6
EF54	4/3
F4A	10/6
GL446B / CV687	10/6
GU21	10/6
KTW62	4/6
ML6	7/6
MS/PEN	5/6
N18	10/6
P41/UR66	4/6
PEN25	2/6
PEN46	4/6
V24	14/6
V2023	6/6
VCR97	15/-
VH54	8/6
VP23	3/6
VR35/QD21	7/6
VR53	4/6
VR54	4/6
VR55	4/6
VR65/65A	2/6

Type	Unit Price
VR66	2/6
VR91	3/6
VR100	5/6
VR108	5/6
VR150/30	4/6
VT52	4/6
VT93	6/6
VT105	5/6
VU120	2/9
VU133A	12/6
X66	8/6
ZD17	10/6

CV

Type	Unit Price
CV44	6/6
CV102	4/6
CV112	6/6
CV118	6/6
CV181	2/-
CV188 Stabilizer	6/6
CV189	8/6
CV201	1/9
CV201 V636 Pentode	4/6
CV246 Crystal	2/6
CV264 Neon Indicator	2/6
CV309 Strobotron	3/6
CV338	5/6
CV388	9/6
CV417	10/6
CV415	4/6
CV749 IN23A	5/6
CV1021 VR21	4/6
CV1179	8/6
CV1137	3/6
CV1188	10/6
CV1576	6/6
CV2829	7/6
CV1052 / KB/A	4/6

U.K. orders below 10/-, postage and packing 1/-; over 10/- postage and packing 1/6. Orders over £2, postage and packing free.

FOR VALVES, TUBES AND COMPONENTS: BY RETURN POST SERVICE

AC6PEN	6/6
ATP4	3/6
AZ1	10/-
AZ31	10/-
AZ41	13/11
B36	10/-
CBL1	26/6
CBL31	23/3
CCH35	23/3
CL4	12/6
CL33	19/3
CY31	16/7
CY1	18/7
CV73	6/-
C36A	6/6
DAF96	8/9
DF96	8/9
DH63	8/-
DK96	8/9
DL96	8/9
DL145	12/-
DN41	16/6
DM70	7/6
EA50	1/6
EABC80	9/-
EAF42	10/6
EB34	2/-
EB41	8/6
EB91	6/6
EBC33	6/9
EBC41	9/6
EBC81	11/4
EBC90	12/7
EBC91	12/7
EBF80	9/9
EBF89	9/6
EBL21	23/3
EBL31	23/3
EC31	7/6
ECC40	23/3
ECC81	8/-
ECC82	7/6
ECC83	9/-
ECC84	10/-
ECC85	9/6
ECF80	12/-
ECF82	13/-
ECH3	26/6
ECH21	23/3
ECH35	23/3
ECH42	9/6
ECH81	9/-
ECH83	13/11
ECL80	10/-
ECL82	12/6
ECL83	19/3
EF9	23/3
EF22	8/6
EF36	5/-
EF37A	15/-
EF39	5/9
EF40	14/6
EF41	9/9
EF42	11/-
EF50	4/-
EF50SYL	7/-
EF54	6/-
EF55	10/-
EF80	7/6
EF85	7/6
EF86	13/-
EF89	8/9
EF91	5/9
EF91 (BVA)	7/-
EF97	13/3
EF98	13/3
EL32	5/6
EL33	14/-
EL34	15/-
EL36	19/11
EL38	26/6
EL41	10/6
EL42	10/6

EL81	16/7
EL83	19/11
EL84	9/-
EL821	26/6
EM34	9/6
EM80	10/-
EM81	10/6
EY51	10/-
EY81	13/3
EY86	10/-
EZ35	16/7
EZ40	7/6
EZ41	7/6
EZ80	7/-
EZ81	7/-
EZ90	7/6
E1148	2/-
FC4	26/6
FC13	6/6
FW4/500	10/-
GT1C	27/6
GZ32	12/-
H30	5/-
H63	10/-
HL23DD	8/6
HL22	6/6
HN309	24/7
K40N	9/-
KF35	8/6
KK32	21/11
KLL32	24/7
KT2	5/-
KT24	5/-
KT33C	8/6
KT36	29/10
KT61	13/6
KT63	7/6
KT66	17/6
KT88	22/6
KTW61	6/6
KTW63	7/6
KTZ41	3/6
MH41	7/9
ML4	8/6
MS4B	5/-
MSP4/5	7/6
MSP4/7	7/6
N37	19/11
N78	19/11
N147	14/-
N339	22/6
NX40	16/-
OZ4	5/6
P61	3/6
PABC80	13/11
PCC84	9/-
PCC85	14/7
PCC88	23/11
PCC89	19/11
PCF80	9/6
PCF82	12/6
PCF84	16/7
PCL82	12/-
PCL83	14/6
PCL84	16/7
PL36	14/6
PL38	17/6
PL81	12/6
PL82	8/6
PL83	11/6
PL84	12/7
PL820	18/7
PX25	12/6
PY31	16/7
PY32	17/11
PY80	7/6
PY81	8/6
PY82	7/-
PY83	8/6
PZ30	19/11
PEN4DD	26/6
PEN4VA	12/6
PEN25	6/-

PEN46	7/-
PEN383	23/3
PEN220A	4/-
PEN45DD	26/6
PENA4	15/-
PM12M	8/-
QP21	5/-
R16	26/6
SP41	3/-
SP61	3/-
SP4/5	10/6
SP4/7	10/6
T41	23/3
TDD13C	7/6
TH233	8/6
TP23	8/-
TP25	10/-
U10	10/6
U14	8/6
U16	12/6
U22	8/-
U25	14/-
U26	12/6
U28	13/6
U37	26/6
U45	15/-
U50	8/-
U76	8/-
U81	10/-
U82	10/-
U84	10/-
U101	10/-
U191	11/6
U339	12/-
U403	16/7
U404	11/4
U801	29/10
UABC80	10/-
UAF42	9/6
UBC41	9/-
UBC81	11/4
UBF80	9/6
UBF89	13/11
UBL21	23/3
UC92	13/3
UCC84	10/11
UCC85	10/6
UCF80	16/7
UCH21	23/3
UCH42	10/6
UCH81	10/6
UCL82	16/7
UCL83	13/6
UF41	9/-
UF42	17/3
UF80	13/11
UF85	9/-
UF86	17/11
UF89	9/-
UL41	10/-
UL44	26/6
UL46	26/6
UL84	9/-
UU6	19/11
UU8	26/6
UY1	12/6
UY41	7/6
UY85	7/-
VP13C	3/6
VP133	15/-
VR22 (PM2A)	3/-
VP23	6/6
VP41	8/6
VR105/30	8/-
VR116	4/-
VR150/30	7/6
VU120A	3/6
VU39 (MU12/14)	8/9
VU111	2/6
W21	6/-
W76	7/6
W77	8/6
W729	10/6
X41	16/-
Y63	9/-
Z309	7/6
Z359	7/6
1A3	3/6
1A7GT	12/6

1C2	11/6
1C5GT	12/6
1D5	12/6
1D6	12/6
1H5GT	9/-
1L4	6/6
1LD5	3/6
1N5	10/6
1R5	7/6
1S4	10/6
1S5	6/6
1T4	6/-
2C26	1/6
2P	26/6
2X2	4/6
3A4	7/-
3A8GT	6/-
3D6	5/-
3Q4	8/-
3Q5GT	9/6
3S4	7/6
3V4	8/6
4D1	3/-
5R4GY	9/6
5U4G	6/6
5V4	11/6
5Y3G	5/-
5Y3GT	8/-
5Z4G	9/-
6A7	10/-
6A8G	9/-
6AC7	5/-
6AG5	5/6
6AK5	6/6
6AL5	4/6
6AM5	12/6
6AM6	4/6
6AQ5	7/6
6AT6	8/6
6AU6	10/6
6B8G	4/-
6BA6	7/6
6BE6	8/-
6BG6G	23/3
6BH6	9/-
6BJ6	9/-
6BR7	12/6
6BW6	9/-
6BW7	8/6
6C4	4/6
6C5GT	6/6
6C6	5/-
6C9	17/3
6C31	7/6
6CD6G	29/10
6D6	5/-
6CH6	10/6
6F6G	7/6
6F6M	7/6
6F1	14/-
6F13	14/-
6F14	26/6
6F15	14/-
6F18	15/3
6F23	18/7
6F33	7/6
6H6	2/6
6H6GT	2/6
6J5GT	5/-
6J5M	6/6
6J6	6/-
6J7G	6/6
6J7M	9/-
6K7G	4/-
6K7M	6/9
6K8G	7/6
6K6GT	7/-
6K7GT	5/9
6K8GT	10/-
6K25	19/11
6L6G	8/-
6L6M	7/6
6L7G	7/6
6L1	23/3
6L18	11/6
6L19	23/3
6LD20	15/11
6M1	17/3
6N7GT	7/6
6P1	19/3
6P26	19/11

6P28	26/6
6Q7G	7/6
6Q7GT	9/6
6SA7GT	8/-
6SG7	7/6
6SH7	6/-
6SJ7	8/6
6SK7	6/-
6SL7GT	8/-
6SN7GT	7/6
6SQ7	9/3
6U4GT	12/-
6U5/6G5	17/3
6U5G	8/6
6U7G	8/6
6V6G	6/-
6V6GT	7/9
6X4	7/6
6X5G	7/-
6X5GT	7/-
6/30L2	12/6
7B6	10/6
7B7	8/6
7B8	6/-
7C5	8/-
7C6	8/-
7D6	13/6
7H7	9/-
7Q7	9/-
7S7	9/6
7Y4	8/6
8D2	2/9
9D2	3/6
10C1	17/3
10C2	17/6
10D2	12/-
10F1	12/6
10F3	23/3
10F9	15/3
10F18	15/3
10L1	15/11
10LD11	12/-
10M2	23/3
10P13	15/-
10P14	19/3
12A6	6/-
12AT6	10/6
12AT7	7/6
12AU6	8/-
12AU7	8/-
12AX7	8/-
12BA6	9/-
12BE6	9/-
12C8	9/-
12E1	35/-
12H6	3/6
12J5GT	3/-
12J7GT	10/6
12K7GT	7/6
12K8GT	13/6
12Q7GT	7/6
12SG7	7/6
12SH7	6/-
12SJ7	6/-
12SK7	6/-
12SL7	8/-
12SN7GT	10/-
12SQ7	8/6
14S7	17/-
15D2	7/9
19AQ5	9/9
19BG6G	23/3
20D1	15/3
20F2	26/6
20L1	26/6
20P1	26/6
20P3	23/3
20P5	23/3
25A6G	10/6
25L6GT	10/-
25Z4	9/6
25Z5	8/-
25Z6	10/-
27SU	19/11
30C1	10/6
30F5	10/6
30FL1	10/6
30L1	11/6
30L15	23/3
30P4	15/-
30P12	12/6

30P16	9/6
30PL1	12/6
30PL13	21/11
35L6GT	10/-
25Y5	9/9
35W4	7/6
35Z4GT	8/-
42	8/-
35Z3	16/7
35Z5GT	9/-

50C5	11/6
50CD6G	29/10
50L6GT	8/6
75	11/6
77	7/6
80	8/6
142BT	3/6
185BT	33/2
210DDT	4/6
210VPT	3/6

83	10/-
301	10/6
302	10/6
304	10/6
305	10/6
306	10/6
807	6/6
954	2/-
955	4/-
956	3/6

5763	9/-
9004	5/6
9006	5/6

DIODES

OA70	4/-
OA79	4/-
OA81	4/-
CG6E	4/-
CG12E	4/-

AUTOMATIC CHANGER UNITS

The latest Collaro Conquest 4-speed auto-changer, in cream with Studio "O" insert. Brand new, fully guaranteed. £7/19/6, plus packing and postage 3/6.

Collaro 4-speed single player unit with automatic stop, cream, turnover crystal cartridge, brand new and guaranteed. £6/19/6.

Garrard Automatic Record Changer, 4 speed, type RC120/D/Mark I. Price £8/17/6, packing and post 3/6.

YAXLEY SWITCHES

4P 3W 3/-. 4P 4W 4/6. 3P 3W 3/-. 3P 4W 3/-. 1P 12W 3/-. 2P 6W 3/-.

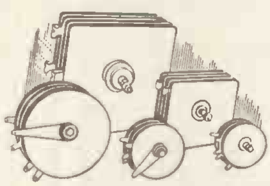

LOUDSPEAKER UNITS

*All brand new. *Note special prices. *All permanent magnet 3 ohms impedance. 5in. units by Plessey Goodmans, Lectrona. 17/6 each.

	Each
2½in. Celestion	19/6
2½in. Rola C25	27/6
3in. Celestion	19/6
5in. Plessey	16/6
6½in. Plessey	18/6
8in. Goodmans	19/6
10in. Elac, Plessey	25/6
6in. x 4in. Plessey	19/6
7in. x 4in. Goodmans	19/6
7in. x 5in. Goodmans	19/6
8in. x 5in. Goodmans	25/6
10in. x 6in. Plessey	25/6
12in. Plessey	29/6

8in. Loudspeaker Units 3 ohms impedance with a matching Output Transformer suitable for 6V6. Brand new but soiled, offered at a Special Price of 11/6 each. Post 2/-.

RECTIFIERS FOR BATTERY CHARGERS

12 v. 1 amp.	4/3
12 v. 2 amp.	7/-
12 v. 3 amp.	10/6
12 v. 4 amp.	12/-
12 v. 5 amp.	14/6

ACOS MICROPHONE

Acos Mic 39/1. Crystal Stick Microphone for use as a hand, desk or floor stand unit, for high quality recording, broadcasting and public address work. List price £5/5/-. OUR PRICE 39/6. With stand 47/6, with floor stand adaptor 52/6, postage 1/6.

TRANSISTORS

Red Spot 5/-. White Spot 7/6. XB102 EDISWAN 10/-. XA104 EDISWAN 18/-.

TELEVISION TUBES

Regunned, 12 months' guarantee. Most types available, E.G., MW.43164, £6. CRM141, £5/10/-. CRM171, £6. Carriage and insurance 10/-.

CRYSTAL TURNOVER CARTRIDGES

Types HGP 37/1. HGP/59/5C GC2. TC8 Power Point, etc., etc. 15/6 each. Acostereo Type 73, 35/- each.

VOLUME CONTROLS

Less switch, 2/10. Single-pole switch, 3/9. Double pole switch, 4/6. All valves. Good selection of "Specials." See our catalogue.

CATALOGUE

Our 1960 catalogue is now available, please send 1/- in stamps for your copy. Trade Catalogues also available, please attach your Business Letter Heading.

ALPHA RADIO SUPPLY CO.

103 LEEDS TERRACE
WINTOUN STREET
LEEDS 7

TERMS: Cash with order or C.O.D. Postage and Packing charges extra, as follows: Orders value 10/- add 1/-; 20/- add 1/6; 40/- add 2/-; £5 add 3/- unless otherwise stated. Minimum C.O.D. fee and postage 3/-.

For full terms of business see inside cover of our catalogue.

Personal shoppers 9 a.m. to 5 p.m. Mon. to Friday. Saturday 10 a.m. to 1 p.m.


18AV56

TECHNICAL TRAINING *in radio television and electronics engineering with*

ICS

The decision is YOURS. To be a success in your chosen career; to qualify for the highest paid job; to control a profitable business of your own. ICS home-study courses put your plans on a practical basis; teach you theory and practice; give you the knowledge and experience to take you, at your own pace, to the top.

Choose the RIGHT *course:*

RADIO AND TELEVISION ENGINEERING
INDUSTRIAL TELEVISION
RADIO AND TELEVISION SERVICING
RADIO SERVICE AND SALES
VHF/FM ENGINEERING ELECTRONICS
COMPUTERS AND PROGRAMMING

A.M.BRIT.,I.R.E.; City and Guilds Telecom. Technicians.
C. & G. Radio Servicing (R.T.E.B.).
C. & G. Radio Amateurs Certificates.

LEARN-AS-YOU-BUILD

Practical Radio Course

Gain a sound knowledge of Radio and T.V. as you build YOUR OWN 4-VALVE T.R.F. and 5-valve superhet radio receiver, Signal Generator and High-quality Multi-tester. At the end of the course you have three pieces of permanent and practical equipment and a fund of personal knowledge and skill . . . ICS Practical Radio courses open a new world to the keen Radio amateur.

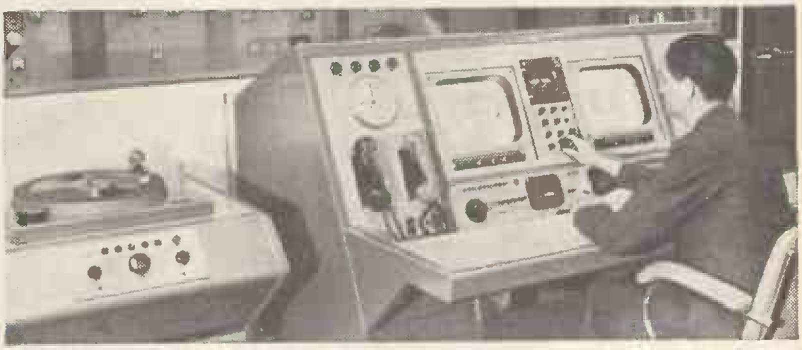

THERE ARE ICS COURSES TO MEET YOUR NEEDS AT EVERY STAGE OF YOUR CAREER

FILL IN AND POST THIS COUPON TODAY

You will receive the FREE 60-page ICS Prospectus listing examinations and ICS technical courses in radio, television and electronics PLUS details of over 150 specialised subjects.

Other ICS courses include:
MECHANICAL, MOTOR, FIRE, CHEMICAL, ELECTRICAL AND CIVIL ENGINEERING . . . SELLING AND MANAGEMENT, ARCHITECTURE, WOODWORKING, FARMING, GARDENING, ART, PHOTOGRAPHY.

PLEASE STATE ON COUPON SUBJECT YOU ARE INTERESTED IN.

INTERNATIONAL CORRESPONDENCE SCHOOLS

DEPT. 221U, INTERTEXT HOUSE, PARKGATE ROAD, LONDON, S.W.11

PLEASE SEND ME FREE BOOK ON ....

NAME .... AGE ....

ADDRESS ....

....

OCCUPATION ....

2.60

TECHNICALLY TRAINED BY

ICS

IN RADIO, TELEVISION AND ELECTRONICS ENGINEERING

Opportunities in Radio Engineering and allied professions await the I C S trained man. I C S Courses open a new world to the keen student. . . .

RADIO AND TELEVISION ENGINEERING; RADIO AND TV SERVICING; ELECTRONICS, COMPUTORS AND DATA PROCESSING, etc.

I C S Courses give very real help to the man setting up his own business or facing a technical career in the radio industry.
Examination Courses for:—British Institution of Radio Engineers, City & Guilds Telecom. Tech., C. & G. Radio Servicing (R.T.E.B.) & C. & G. Radio Amateurs.

LEARN-AS-YOU-BUILD PRACTICAL RADIO COURSE
Build your own 4-valve TRF and 5-valve superhet radio receiver. Signal Generator and High-quality Multi-tester.

FILL IN AND POST THIS I C S COUPON TODAY
It brings the FREE I C S Prospectus containing full particulars of I C S courses in Radio, Television and Electronics.

INTERNATIONAL CORRESPONDENCE SCHOOLS

. . . A WHOLE WORLD OF KNOWLEDGE for the KEEN STUDENT

International Correspondence Schools, (Dept. 222P), Intertext House, Parkgate Road, London, S.W.11.

NAME.............................. AGE.........

ADDRESS ....
Block Capitals Please

....

OCCUPATION ....
2.60

NEWMARKET TRANSISTORS LTD.

ENGINEERS AND PHYSICISTS

FOR EXPANSION SCHEME

Our Production expansion plans coupled with the rapidly increasing utilisation of semiconductor devices has created the following classes of

VACANCIES.

PHYSICISTS
To work on semiconductor material and device problems with an ultimate target of performance improvement and fabrication simplification. Good general academic qualifications essential.

PROCESS CONTROL ENGINEERS
To monitor, maintain and analyse the production of semiconductor devices. Some previous experience in allied field desirable.

PROCESS DESIGN ENGINEERS
To develop and initiate production methods and machines. Some experience of labour saving methods and tooling desirable.

MAINTENANCE ENGINEERS
To maintain chemical and mechanical equipment of specialised nature. A recognised apprenticeship in some branch of production engineering would be an advantage.
Salaries will be paid in accordance with qualifications and experience and ample opportunities exist for promotion.

Apply, giving full details, to:

**PERSONNEL MANAGER,
NEWMARKET TRANSISTORS, LTD.,
EXNING ROAD, NEWMARKET**

RADIO TECHNICIANS IN CIVIL AVIATION

Men aged 19 or over for interesting work providing and maintaining aeronautical telecommunications and electronic navigational aids at aerodromes and radio stations in the U.K. Fundamental knowledge of radio or radar with some practical experience essential; training provided on special types of equipment. Salary according to age and station, approx. £670 at age 25 rising to £795. Prospects of permanent pensionable posts. Good opportunities for those who obtain O.N.C. in Elec. Eng. and certain C. and G. Certificates for promotion to posts with maximum salaries of £875, £1,035 and £1,260. Apply to the Ministry of Aviation (ESB1/RT), Berkeley Square House, London, W.1 or to any Employment Exchange (quoting Order No. Westminster 3552).

MARCONI INSTRUMENTS LIMITED

ST. ALBANS, HERTS.

have vacancies for

SENIOR DRAUGHTSMEN with experience in electronics.

also

DETAIL DRAUGHTSMEN with experience in electronics or otherwise.

Excellent opportunity for experienced men to widen experience with well established and continually expanding company, offering long term progressive employment and good working conditions.

Please write giving full details of experience and qualifications to **Dept. C.P.S., Marconi House, 336/337, Strand, London, W.C.2.** quoting reference WW2970K

VACANCIES FOR
RESEARCH AND DEVELOPMENT CRAFTSMEN IN GOVERNMENT SERVICE AT CHELTENHAM

Experience in one or more of the following:—
(1) Maintenance of radio communication receivers.
(2) Sub-assembly lay out, wiring and testing of radio type chassis.
(3) Cabling, wiring and adjustment of telephone type equipment.
(4) Fault finding in and maintenance of electronic apparatus.
(5) Maintenance of teleprinter or Cypher machines and associated telegraph equipment

Basic Pay £9/9/8 per week plus merit pay, assessed at interview and based on ability and experience as under:—
ORDINARY RATE 10/- to 32/-
SPECIAL RATE 38/- to 70/- per week.

Opportunities for permanent and pensionable posts. Five-day week, good working conditions, single accommodation available.

Apply in writing to: Personnel Officer,
C.G.H.Q., (3/BDC).
53, Clarence Street,
Cheltenham, Glos.

NELSON RESEARCH LABORATORIES
THE ENGLISH ELECTRIC COMPANY LIMITED
STAFFORD
SENIOR & JUNIOR ELECTRONIC and ELECTRICAL ENGINEERS

are required for interesting and varied work in the Nelson Research Laboratories, English Electric Company Limited, Stafford.

Applicants should have sound workshop experience and some knowledge of Drawing Office procedure.

Qualifications up to H.N.C. level are desirable. Duties will include responsibility for the Engineering Design of prototype electronic equipment and electrical control equipment from the rough circuit stage to the issuing of manufacturing information to the Laboratories' Workshops.

These posts offer ample scope for advancement to men with initiative and ability.

Salary according to qualifications and experience. Please write giving full details of salary and qualifications to Dept. C.P.S., Marconi House, 336/7, Strand, London, W.C.2, quoting reference WW 995C.

ARE YOU A SKILLED AND EXPERIENCED ELECTRONICS TECHNICIAN ?

HAVE YOU BEEN A WIRELESS OR RADAR FITTER IN THE ARMED FORCES ?

DO YOU HAVE GOOD TECHNICAL QUALIFICATIONS BUT LACK INDUSTRIAL EXPERIENCE ?

If you can answer "YES" to at least one of these questions then we should like to hear from you.

We need new test and calibration engineers to help us increase the output of our very wide range of telecommunications measuring instruments.

The work requires the understanding of the most modern and varied circuit techniques and embraces all frequencies up to 10,000 Mc/s.

The posts are permanent and pensionable and will prove attractive to men who believe strongly that there is a real career for them in production.

Call and talk it over if you live close to us at St. Albans. Alternatively, write to Dept. C.P.S., Marconi House, 336/7, Strand, London, W.C.2., giving full details of your education and experience and quoting reference W.W.2970J.

**MARCONI INSTRUMENTS LIMITED
LONGACRES, HATFIELD ROAD, ST. ALBANS**

EARN what you're really worth!

You've got ability—everyone has. But are you making the most use of it—to earn what you're really worth? If not, let ICS training develop your ability and help you to a better job, with more security!

Take the right course now . . .

Advertising & Salesmanship
General Advertising
Sales Management
Exams.: Joint Inter., A.A. and I.P.A. Finals, I.S.M.A., U.C.T.A.

Architecture and Building
Clerk of Works
Building Construction
Exams.: R.I.B.A. (Inter.) R.I.C.S., I.Q.S., Inter., Final & Dip. in Working Up, L.I.O.B.

Art
Commercial Illustrating.
Oils and Water-Colours.

Commercial Training
Bookkeeping
Computer Programming
Office Training Bookk'ping
Exams.: I.C.W.A., C.I.S., C.C.S., A.C.C.S., Inst. Bk-keepers.

Draughtsmanship
(State Branch)
Drawing Office Practice
Mechanical Drawing
Maths. & Machine Drawing

Farming and Horticulture
Pig and Poultry Keeping
Flower and Veg. Growing.
Smallholding
Exam.: R.H.S. General

Fire Engineering
Instn. of Fire Engnrs.

General Education
Good English
Exams,: G.C.E. Subjects at Ordinary or Advanced Level

Management.
Industrial Mangmt. Office Mangmt. Personnel Mangmt.
Exams.: Br. Inst. of Mangmt. Inter., Final and Cert. in Foremanship

Mechanical Engineering
Wide range of subjects incl: Workshop Practice, Diesel Engines, Refrigeration & Welding. Engineering Maths., Production Eng.
Exams.: I.Mech.E., Soc. of Engrs., Cert. in Foremanship

Motor Engineering
Motor Mechanics
Running and Maintenance

Photography
The Amateur Photographer
Exam.: P.D.A.

Radio, T.V. and Electronic Engineering
Basic Electronics
Radio Engineering
Indust. Electronics & T.V.
Radio Servicing
T.V. Servicing and Eng.
Practical Radio (with kits)
Electricians
Exams.: Brit.I.R.E., Soc. of Engrs., C. & G. Certs. for Telecom Technicians, Radio Amateurs, Radio Servicing (RTEB)

Writing for Profit
Short Story Writing
Journalism

And Many Other Courses

. . . and fill in this coupon

INTERNATIONAL CORRESPONDENCE SCHOOLS, (Dept. 222Q), Intertext House, Parkgate Rd., London, S.W.11.

Please send FREE book on ....

Name.. Age..............

Address ....

....

Occupation.. 2.60

DIGITAL COMPUTER ENGINEERS

'English Electric' has vacancies for a number of

SITE COMPUTER ENGINEERS

for diagnosis of logic and circuitry faults at operational establishments. Successful applicants will, after an initial training course, be required to take up responsible positions at Computer Installations on customers' premises.

Qualifications required are H.N.C. or equivalent with preferably two years' experience in development or maintenance of Computers or other pulse circuitry. During training, special subsistence allowance will be made for any successful applicants who have to live away from home. Attractive salaries would be offered with these positions which are permanent and enjoy the benefits of the English Electric Staff Pension Scheme and qualify, after initial service, for three weeks' annual holiday.

Applications giving full details of qualifications and experience should be addressed to **Dept. C.P.S., Marconi House, 336/7 Strand, London, W.C.2, quoting reference WW390E.**

NEWMARKET TRANSISTORS

Applications are invited from Senior and Junior Engineers for vacancies in the following departments:—

Applications,
Laboratory Measurements,
Production Testing,
Production Test Equipment.

Salaries will be paid in accordance with qualifications and experience and ample opportunities exist for promotion. All applications will be treated in the strictest confidence.

Apply giving full details to:—

Personnel Manager, Newmarket Transistors Ltd., Exning Road, Newmarket.

A MAST PROBLEM? WRITE TO Skymasts

BEADON GARAGE BEADON ROAD LONDON W6 Telephone RIVerside 1124 and 7878

SENIOR TEST ENGINEER

Required for an expanding organisation producing television and radio transmission equipment. The successful candidate must be capable of formulating test specifications and procedures for a wide variety of equipment, and will be required to train and direct a group of test engineers. Adequate theoretical qualifications and good practical experience are required.

Applications, which will be treated as confidential, should be sent to:

Staff Appointments,
BRITISH RELAY WIRELESS Ltd.
1-7 Croft Street,
LONDON, S.E.8.

TECHNICAL WRITER RADIO & TELEVISION

The preparation of service manuals for our radio and television receivers is undertaken by a small team of people having up to date knowledge of good service practice plus the ability to write effectively and well. We are now able to invite a suitably experienced man to join this team.

Applications including details of age and experience should be sent to the :

Personnel Manager (R.22),
Murphy Radio Limited,
Welwyn Garden City, Herts.

SOLARTRON

A bright future for really good

TECHNICAL WRITERS

We regard technical writers as especially important in our programme of expansion. This programme has already included development of many technically advanced equipments, often in new and exciting fields where previous documentation was sketchy or non-existent.

If *your* technical knowledge and ability to express yourself lucidly, can meet our high standards, you should seriously consider the progressive career prospects and unusual degree of creative satisfaction we can offer.

Opportunities exist in the following fields:—

Computers, character recognition, Industrial controls, X-ray spectrometry.

Please write to the Personnel Officer:

Solartron Electronic Group Limited
Farnborough, Hampshire.

Z. & I. AERO SERVICES LTD.

14 South Wharf Road, London, W.2

Telephone: AMBassador 0151/2 Cables: ZAERO, LONDON

A.R.B. Approved Stockists

RETAIL BRANCH: 85, TOTTENHAM COURT ROAD, LONDON, W.1

AN/AMT-11 RADIO SONDE TRANSMITTERS

Complete transmitter designed to transmit signals in the range of 395-406 mc/s. range audio modulated at 10 tp 200 c/s., modulation frequency depending on the magnitude measured. Measurements range: pressure 1,060 to 5 millibars; Relative Humidity 15 to 90%; Temperature −90 to +50°C. Equipment includes barometric switch and measuring device, humidity and temperature measuring elements, aerial and pressure calibration chart. Transmitter Circuit consists of Double Triode 3A5 with one half acting as modulating oscillator, the other as a buffer, and UHF Triode 5703.

PRICE, brand new £2 10 0
Manual 17 6
One manual supplied free per each six transmitters.
Packing and postage 6 6

UNIVERSAL IMPEDANCE BRIDGE

(Test Set Type 373)

General Purpose Impedance Bridge for 115/230 v. A.C. operation. Measurements ranges: 0.1 to 100,000,000 ohms, 1pF to 1,000mF; 0.1μH. to 100H. Accuracy 1 to 2% (centre of the range) for resistance and capacitance and 10% average for inductance. Operating frequency 1,000 c/s. except higher capacitance ranges where measurements are made at mains frequency. Direct leakage current reading up to 5mA. Polarizing voltage from 0 to 500 volts for reforming electrolytic capacitors. Neon tuning indicator and headsets for balancing. No Zero Indicator provided.

PRICE, unused and guaranteed ...... £30 p.p. £1.

INSULATION TESTERS

EVERSHED SERIES 1 MEGGER INSULATION TESTERS, 500 volts, 40 megohms, secondhand, fully overhauled and guaranteed £25 0 0
Packing and carriage 15 0
EVERSHED SERIES 2 BRIDGE MEGGERS, 500 volts, 100 megohms, with built-in four decade resistance box and ratio arms of .01-.10-1.0-10-100; Selector for Bridge, Megohms and Varley measurements. Unused and fully guaranteed £65 0 0
Packing and carriage £1 0 0
EVERSHED SERIES 2 MEGGER INSULATION TESTERS, 1,000 volts, 200 megohms, in leather cases, brand new £45 0 0
Packing and carriage 15 0
500 volts, 100 megohms in leather case, secondhand. Fully overhauled £17 10 0
Packing and carriage 15 0
EVERSHED SERIES 3 MEGGERS (Wee Meggers).
500 volts, in leather case £13 10 0
250 volts, in leather case £11 10 0
Packing and postage 15 0

TYPE 106 SIGNAL GENERATOR

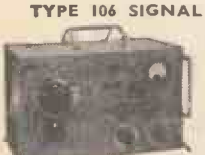

Frequency Range: 5.5 to 52 mc/s. Output 1 microvolt to 100 mV. Output impedance: 70 and 100 ohms. Internal modulation. Provision for External Modulation. Power supplies: 230 v. 50 c/s. or 80 v. 1,000 c/s.

PRICE, unused, complete with calibration charts £12 10 0
Without calibration charts £8 10 0
Packing and carriage 15 0

COMMUNICATION RECEIVERS

ALL AVAILABLE ON H.P. OR CREDIT TERMS, Completely overhauled to "as new" performance and with six months' guarantee.

RCA AR-88LF RECEIVERS £80 0 0
RCA AR-88D RECEIVERS £85 0 0
HALLICRAFTERS S-27 (28-143 mc/s.) £65 0 0
MARCONI CR-100, 60 kc/s.-30 mc/s. .. £42 0 0
BC-342, 1.5-18 mc/s. £42 0 0
Please write for further details.

WESTON MODEL 155 PORTABLE MIRROR SCALE A.C. MOVING IRON AMMETERS

0-150 amps. A.C.

PRICE, new £6 10 0
Post and packing 1 0 0

CATHODE FOLLOWER VALVE VOLTMETER

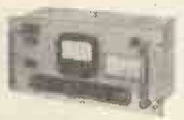

Voltage Range: 100 microvolts to 200 volts in six steps. Frequency Range 300 c/s. to 200 Kc/s. Noise level: 50 microvolts max. Accuracy: better than 3%. Input impedance 100 megohms: 15 pF. The instrument can also be used as an A.C. Amplifier with a maximum output of 10 volts. Power supplies: 200-250 v A.C. Mains.

PRICE £35 0 0
Packing and carriage £1 0 0

TF-582B/1 MARCONI OSCILLATOR-DETECTOR UNIT

Frequency Range 100 kc/s. to 20 mc/s. in six bands. Oscillator output: .3 to 1V; Detector sensitivity at least 10 μV at low frequency end, tailing off to 200 μV at high frequency end; The Unit consists of separate Oscillator and Detector Units mounted in common cabinet. RF output modulated at 1,000 c/s.; Headphone balancing (null indication).

PRICE, fully overhauled and guaranteed £75 0 0
Packing and carriage £1 0 0

B.T.H. "X" BAND PERFORMANCE TESTING RESONATOR (ECHO BOX)

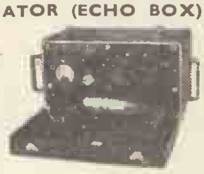

Directly calibrated frequency dial, graduated from 9,170 to 9,470 mc/s. Graduated Attenuator; Microammeter Resistance Indicator; complete with R.F. Cable and Waveguide Adaptor.

PRICE £32 0 0
P. and carr. 15 0

SULLIVAN STANDARD WHEATSTONE BRIDGE

5-decade Wheatstone Bridge. .1-1.0-10-100-1000 absolute ohms; Ratio Arms Ratios: .001-.01-.1-1.0-10-100-1000.

PRICE £85 0 0
CAMBRIDGE SPOT GALVANOMETER, for use with the above: nominal sensitivity 35-0-35 microamps. £12 10 0
Packing and carriage £2 0 0

MARCONI TF-144G SIGNAL GENERATOR

Frequency Range 85 kc/s. to 25 mc/s.; Output 1μV. to 1 volt; 200-250 v. A.C. mains power supply or battery operation. Complete with mains lead and output lead with Dummy Aerial.

PRICE £85 0 0
Packing and carriage £1 0 0

AUDIO OSCILLATORS

HEWLETT PACKARD MODEL 200A, Resistance tuned Oscillator with a frequency range of 35 to 35,000 c/s. in three ranges. Max. output 1 watt into 500 ohms with distortion not exceeding 0.5%. Output is not metered. Power Supplies 115 v. A.C.
PRICE, new, fully guaranteed £28 0 0
Packing and carriage 15 0
HEWLETT PACKARD MODEL 205AG. Resistance Tuned Oscillator with a frequency range of 20 c/s. to 20 kc/s. in three bands. Output 5 watts into 50, 200, 600 and 5,000 ohms with distortion not exceeding 1%. Output Meter, Input Meter; Calibrated Attenuator.
PRICE, fully overhauled and guaranteed £85 0 0
Packing and carriage £1 0 0
LO-50 B.S.R. AUDIO OSCILLATOR, Frequency range 0-16,000 c/s.; Maximum Output 0.5 Watts into 600 ohms. Output Meter, Tuning by means of two dials. Power Supplies 230 v. A.C.
PRICE, fully overhauled and guaranteed £30 0 0
Packing and carriage £1 0 0

SPECIAL UHF AND EHF RECEIVERS

AN/APR-4 Search Receivers. Frequency Range 40 to 2,000 mc/s. Panoramic Adaptors type RDO available.
AN/APR-5 Search Receivers. 1,000-6,000 mc/s.
R-1294 Receivers, 500-3,000 mc/s.
R-1619 Receivers 1,250-5,000 mc/s.
Prices and details on application.

CATHODE RAY TUBES

	V(a1)	V(a2)	V(a3)		
3ACP2	4,000	2,000	550	ES	15/-
3BP1	2,000	—	575	ES	12/6
5CP1	4,000	2.000	575	ES	40/-
7BP7A	7,000	250	—	EM	70/-
VCR-97	2,500	—	—	ES	25/-
VCR-522	1,000	—	—	ES	15/-

Bases for 3ACP2, 3BP1, 5CP1 .... 3/6
Bases for 5FP7 (Int. Octal) 1/-
Packing and carriage 2/6 in £

5SP7 DOUBLE GUN ELECTROSTATIC CATHODE RAY TUBES

Screen coating gives blue-white short persistence and yellow long persistence trace. Average operating conditions: V(a3) 4,000 v., V(a2) 2,000 v., V(a1) 360-700 v. Cut-off voltage 45-75. Sensitivity 80-100 v. D.C. per inch on "Y" and 70-80 v. D.C. per inch for "X" axis. Heater 6.3 v. 0.6 A.

PRICE, new and guaranteed, ONLY £7 0 0
Postage and packing 3 6

SPECIAL TEST EQUIPMENT

TS-3 Wave-Wattmeter 2,700-3,400 Mc/s.
TS-12 S.W.R. Indicator 9,305-9,445 Mc/s.
TS-13 Portable Signal Generator/Wavemeter 9,305-9,445 Mc/s.
TS-14 Signal Generator 3,200-3,370 Mc/s.
TS-34 Portable High Speed Oscilloscope.
TS-35 Portable Signal Generator 8,700-9,500 Mc/s.
TS-36 Power Meter 8,700-9,500 Mc/s.
TS-45 Signal Generator and Wave/Wattmeter, 8,700-9,525 Mc/s.
TS-47 General Purpose Oscillator 40-3,000 Mc/s.
TS-56 Slotted Line, 358 Mc/s.-690 Mc/s.
TS-61 Echo Box 3,140-3,360 Mc/s.
TS-118 R.F Output Power Meter, 20-750 Mc/s.
TS-226 Peak Power Meter 405-425 Mc/s.
Type 57 Standing Wave Indicator, 9,100-9,700 Mc/s.
Details and prices of all the above equipment will be supplied on request.

STANDARD WAVEMETER No. 2

Laboratory Standard Wavemeter covering a range 0.5 kc/s. to 10 mc/s. on fundamentals and up to 300 mc/s. in harmonics. Generation of any frequency from 0.5 kc/s. to 10 mc/s. with accuracy of 1 in $10^6 \pm 10$ c/s.; Generation of any kc/s. from 2 kc/s. to 10 mc/s. with accuracy of 10^6. Output signal amplitude 0.2 to 0.3V. Decade tuning. Mains operation. PRICE £280 0 0
Packing and carriage £5 10 0

KLYSTRONS AND MAGNETRONS

Klystrons:
417A (2K41), 9.1-11.3 centimetres; Output 25 milliwatts £2 0 0
Packing and postage 5 0
723A/B, 8703-9548 mc/s. £3 10 0
Packing and postage 5 0
Magnetrons:
2J36, 9003-9138 mc/s., 14 kW. £8 0 0
Packing and postage 7 6
5J29, 770 mc/s., liquid cooled, 150 watts £3 0 0
Packing and postage 5 0
5J30, 375 mc/s., liquid cooled, 150 watts £2 0 0
Packing and postage 5 0
QK59, QK60, QK61, 10 cm. band £2 0 0
Packing and carriage 5 0

EXPORT ONLY

SCR-522 Transmitter-Receivers and complete installations, for Airborne or Ground Use.
WIRELESS SETS No. 38 Mk. III, incorporating Crystal Calibrators.
BC-950-A four-channel crystal controlled Aircraft Transmitters, 100-124 mc/s., or 100-146 mc/s.
Details and prices on application.

UHF PORTABLE TRANSMITTER-RECEIVERS

RT-159/URC-4.
Pocket Size Handie-Talkies, two crystal channels (125 and 250 mc/s. bands), powered by Mercury batteries.
PRICE, new and complete with Mercury Battery £35 ea.
Packing and carriage 15 0

Wireless World Classified Advertisements

Rate 9/- for 2 lines or less and 4/6 for every additional one or part thereof average lines 6 words. Box Numbers 2 words plus 1/-. (Address replies: Box 0000 c/o "Wireless World" Dorset House, Stamford St., London, S.E.1.). Trade Discount details available on application. Press Day March 1960 issue, Thursday, January 28th. No responsibility accepted for errors.

WARNING

Readers are warned that Government surplus components and valves which may be offered for sale through our displayed or classified columns carry no manufacturers' guarantee: Many of these items will have been designed for special purposes making them unsuitable for civilian use, or many have deteriorated as a result of the conditions under which they have been stored. We cannot undertake to deal with any complaints regarding any such items purchased.

NEW RECEIVERS & AMPLIFIERS

AM/FM stereo chassis, 6w output with 2 speakers; only £20.—Bel Sound Products, Marlborough Yard, N.19. [0182

RECEIVERS AND AMPLIFIERS SURPLUS AND SECONDHAND

HRO Rx's, etc., AR88, CR100, BRT400 G209, S640, etc., etc., in stock.—R. T. & I. Service, Ashville Old Hall, Ashville Rd., London, E.11. Ley. 4986. [0053

LOUDSPEAKERS WANTED

HARTLEY-TURNER speakers, 2 wanted, 4 Ω coils, type 215, in good condition; write stating price for 2 (or 1).—Thomson, 131, High St., Dunfermline. [8882

DYNAMOS, MOTORS, ETC.—SURPLUS AND SECONDHAND

ROTARY transformers D.C. to A.C. 100/110 volt D.C. input, 230 volt 50 cycle single-phase 200-watt output; weight approx. 100lb; ideal all A.C. equipment from a D.C. supply; all brand new but slightly store soiled £10 each, plus 15/- part packing and carriage.—Waltons Wireless Stores, 46-49, Stafford St., Wolverhampton. [0101

TEST EQUIPMENT—SURPLUS AND SECONDHAND

AVO electronic meter, 10Kv multi, and leather case, as new, cost £65; £50 o.n.o. —Mayfield, Rowledge, Surrey. Frensham 396. [8912

MEGGER insulation testers, unused, 500 volt, constant pressure, by Evershed & Vignoles; £30 each.—H. H. Bradford, Ltd., Ramsey, Harwich, Essex. [8892

TELEVET with manual and circuit diagrams, 18 months old, fully guaranteed; for quick sale, £45, o.n.o.—Apply Ambrose, 22, Market St., Pembroke Dock. [8879

SIGNAL generators, oscilloscopes, output meters, wave voltmeters, frequency meters, multi-range meters, etc., etc., in stock.—R. T. & I. Service, Ashville Old Hall, Ashville Rd., London, E.11. Ley. 4986. [0056

FOR sale, 50 Mullard high-speed automatic valve testers, each machine complete with 5 to 600 test cards in series and in metal cabinets; these machines are standard units and have come from a Government factory and were ordered for a discontinued Government job, some are new and some are slightly used; approx. cost from Mullard £120 each, can offer complete with cards and cabinets at £35 each; carriage and packing £3 extra.—Davidson Engineers (M/cr), Ltd., Irkdale St., Smedley Rd., Cheetham Hill, Manchester, 8. Tel. Collyhurst 1610. [8890

NEW COMPONENTS

NEW miniature printed components: Resistors 6d., post 3d.; TV alternators 2/6d.—Ray, 4 Dalton Avenue, Whitefield, Manchester. [0324

200 brand new Wright & Weaire vibrators, type NS/2V., lot at 5/- each.—Taylor Electrical Instruments, Ltd., Montrose Ave., Slough. Tel. 21381. [8910

CRYSTAL microphone inserts with exceptionally high output. (Cosmocord Mic 6.) Guaranteed newly made and boxed, 15/6 post free.—Radio-Aids, Ltd., Dept. W.29, Market Street, Watford, Herts. [0213

TURRET TUNERS, brand new, famous make, 12 channel, coils 1 to 5 and 8/9 fitted, 34/38 m.c.s., complete with P.C.F. 80 and P.C.C. 84, circuit diagram included, £1/17/6 p. & p. 3/6; discounts for quantities; cash with order.—South Supplies (Electrical), Ltd., 95, Old Kent Rd., London, S.E.1. [0827

AMAZING value: Philco Shortwave Car Radio converters, originally £10, to fit any existing car radio and add 6 extra wavebands, 16-19-25-31-49-metre bands, also standard broadcast, 6/12 volts, compact under dash mounting, chromium control panel with 6 press buttons, complete all fittings and instructions, easily fitted; 45/-, post free; each instrument brand new with Mullard valves.—Tomlins, 127, Brockley Rise, Forest Hill, S.E.23. [8878

COMPONENTS—SURPLUS AND SECOND-HAND

VALVES, new and used, from 1/6 each; all guaranteed, all types components cheap, radio, television books; lists free.—Hamilton Radio, 237 Sedlescombe Rd., N., Hastings. [0212

MAGSLIPS at low prices, fully guaranteed, 3 in Receiver No. 5 (AP 10861), 50v. 50c/s, unused, each in tin, 35/-, post 2/1; large stocks of these and other types.—P. B. Crawshay, 94, Pixmore Way, Letchworth, Herts. Tel 1851 [0087

BREAKING hundreds of TVs for spares, all makes; LOPTs from 25/-; scan coils from 17/6; valves from 3/6; tested; also large stocks of new TV components; send requirements for immediate quote and our new lists.—T.C.S., Ltd., 28, Brockley Cross, S.E.4. Tid. 5394. [0334

NEW GRAMOPHONE AND SOUND EQUIPMENT

TAPE recorders, Ferrograph, Vortexion, Brenell, Telefunken, Truvox, Reflectograph, and M.S.S.
TAPE decks: Wearite Brenell, Truvox, Brad-matic, Dulci-Harting, Amplifiers and tuners: Leak, Quad, R.C.A., Dynatron and Dulci; Microphones: Reslo, Lustraphone, Philips, Acos, Grampian, etc. All tape and accessories. Audio service department and recording studio. HIRE purchase facilities available.
LAMBDA Record Company, Ltd., 95, Liverpool Rd., Liverpool, 23, Great Crosby 4012. [8404

CINE-VOX disc recording mechanisms for L.P. or standard operation from 30gns.—56gns.; also complete tape-disc or direct channels from 50gns.-112gns.
DEMONSTRATIONS can be arranged in London.—For full details write to K.T.S., Ltd., "Coplow," Park Rd., Braunton, N. Devon. Callers by appointment only. [0210

GLASGOW.—Recorders bought, sold, exchanged, cameras, etc., exchanged for recorders, or vice versa.—Victor Morris, 406, Argyle St., Glasgow, C.2. [0201

"EROICA" RECORDING STUDIOS (Est. 1949)—For the better class tape recorders for industry, research, music and private use; Ferrograph, Brenell, etc.; complete recording service; music for industry; tape/disc.—31, Peel St., Eccles, Manchester. Eccles 1624. Studio Director, Thurlow Smith, A.R.M.C.M. [0122

GRAMOPHONE AND SOUND EQUIPMENT—SURPLUS AND SECONDHAND

SOUND NEWS will send you the list of demonstration and little used equipment offered for sale in February on receipt of a s.a.e.—See also "Tape Recording," etc., column. [0194

SPECIAL purchase!—1,800ft Agfa-Wolfen L.P. tape on 7in spools, only 32/6; 1,200ft 7in Ferrotape, 26/6; p. & p. 1/6; send for complete list of tape bargains (including American Audio tape, BASF, etc.) and list of new and second-hand tape recorders.—E. C. G. Kingsley & Co., 132, Tottenham Court Rd., London, W.1. Eus. 6500. [0025

TAPE RECORDING, ETC.

RENDEZVOUS RECORDS offer comprehensive 78/LP tape to disc recording facilities. —Leaflet from 19 Blackfriars St., Manchester 3. [8829

SPECIAL offer, Easysplice tape splicer, 3/9, p. & p. 6d.; makes tape splicing easy and accurate.—Easysplice, 30, Lawrence Rd., Ealing. [8893

TAPE to disc recording: Microgroove LP from 27/6, 78 r.p.m. from 11/-, also 45 r.p.m.; 48-hour service; s.a.e. for comprehensive leaflet to.—A. D. Marsh, "Derov" Sound Service, Little Place, Moss Delph Lane, Aughton, Ormskirk, Lancs Aughton Green 3102. [8651

SOUND recording in Leeds! Tape/disc, all speeds; tape recorder hire; studio with full mixing and editing facilities; call or write for further details.—Sound Recording & Equipment Hire, 21, Wade Lane, Leeds 2. Leeds 26192. [8887

TAPE/DISC/TAPE transfer editing, copying; if quality and durability matter (especially with LPs from your precious tapes), consult Britain's oldest transfer service; every new tape recorder is supplied with a 2-year service guarantee; latest American, Belgian, German tapes available at competitive rates.—Sound News Productions, 10, Clifford St., London, W.1. Reg. 2745. [0192

FOR SALE AND WANTED ADVERTISEMENT FORM TURN TO PAGE No. 187

Field [illegible]

GILSON U.L. OUTPUT TRANSFORMERS

WIDE FREQUENCY RANGE—LOW DISTORTION AT ALL POWER LEVELS

— HIGH FIDELITY —

MAXIMUM RELIABILITY · LOW COST

GILSON TRANSFORMERS

are designed, built and tested to the best modern standards with fully paper-interleaved coils and rigid selection ensures that all materials used are compatible with our vacuum varnish impregnation process.

STYLE SIM

WORTH WRITING FOR—
Our new list showing sizes, styles, specifications and prices of a very popular range of output and mains transformers.

R. F. GILSON LTD.

11a ST. GEORGE'S ROAD
WIMBLEDON, S.W.19
Phone : WIM 5695

TRANSFORMERS FOR ENGINEERS TECHNICIANS, SCIENTISTS

TROPICAL LIGHTING, NEON, SPECIAL PURPOSE

SITUATIONS VACANT

LONDON COUNTY COUNCIL.
NORWOOD Technical College, Knights Hill, S.E.27, require (a): 2 Grade B assistants; (b) lecturer; each to conduct classes in one or more of branches covered by department which offers full-time courses in telecommunication and electronics, radio operating and radar, with part-time courses which also include radio and TV servicing, TV technology and other specialist subjects.
FOR Grade B assistants, good qualifications required; appointments temporary in first instance.
BURNHAM F.E. salary scale (men) within the range £738 to £1,486; commencing and final salary depending on age, qualifications and experience.
FOR lecturer, certain administrative responsibilities entailed; appropriate high academic qualifications and/or good specialist experience required. Salary scale (men) £1,370×£35 to £1,550 plus London allowance £38 or £51. Possible entry to scale above minimum for specially approved experience.
APPLICATION forms (foolscap s.a.e.) from Principal at College, to be returned as soon as possible. (2694) [8875

GO Ahead Electronics Engineers.
FRUSTRATED due to lack of scope for their abilities or lack of prospects for future advancement, are invited to discuss the openings which exist for them in the field of technical publications with a national organization. Experience in one or more of the following fields is desirable. Radar systems, Guided Weapons, Microwave techniques, Pulse circuitry, Instrumentation. Preference will be given to those applicants possessing formal qualifications (B.Sc. H.N.C. City and Guilds Telecomms. etc.) A good general standard of education is essential. This is a field in which Ability and Enthusiasm are well Rewarded by a Four Figure Salary. Also required first-class Technical Illustrators. We can only consider the highest calibre candidate who is used to preparing technical illustrations from orthographic prints. Vacancies are available in Manchester, London, Chelmsford and Maidenhead.
YOU are invited to write to Technivision Ltd., Braywick House, Nr Maidenhead, Berkshire. [8900

LOUIS NEWMARK, Ltd., have the following vacancies at their development laboratories at New Addington, Croydon.
AN engineer or assistant engineer with H.N.C. or equivalent, and experience in the light electrical, electronics, electro-mechanical or or aircraft electrical fields to work on the development installation and flight test of automatic pilots for helicopters.
AN engineer or assistant engineer, with a degree or H.N.C. in light electrical or mechanical engineering and relevant experience, for design and development work on small mechanisms and electro-mechanical devices.
PENSION scheme. Apply in writing, giving full particulars to Personnel Officer, Louis Newmark, Ltd., Prefect Works, Purley Way, Croydon, Surrey. [0331

PART-TIME electronic engineers for LP disc cutting, installation work, technical advising, wanted in London.—Box 6677. [0134

HI-FI/COMPONENTS salesmen for West End: top salary for right men; permanency.—Tel. Manager, Pad. 3271. [8911

PART-TIME advertising and office manager required by London hi-fi dealers; age immaterial; experience important.—Box 6676. [0133

SKILLED chassis wirers are required by well known manufacturer of sound amplifying equipment. Good all round knowledge and previous experience essential. Box 6594. [8902

MECHANICAL Draughtsman required for work on designs of commercial radio and TV equipment; write stating qualifications, experience and salary required.—Box 6516. [8888

TELEVISION bench and field engineers required at all times for vacancies in most parts of the British Isles; permanent positions with highest salaries plus bonus for suitable applicants, 5½-day week.—Box 1757. [0251

LEE PRODUCTS (G.B.) Ltd., require a Chief Production Tester who has experience of staff control. This is a progressive position in an expanding organisation.—Apply to Factory, 97, Villiers Road, N.W.2. Willesden 6678. [8898

ELECTRONIC Technician; H.N.C. with Electronics or exceptional practical experience; maintenance and operation magnetic playback systems; geophysical field or playback experience an advantage. Hayes-Orpington area. Box 6028. [8836

DEVELOPMENT engineer.—E. K. Cole, Ltd., Southend-on-Sea, have a vacancy in their development laboratories for an engineer experienced in the development of transistorised radio.—Write, stating age, qualifications and experience, to Personnel Manager. [8915

ERIE RESISTOR, Ltd., require a junior laboratory engineer experienced in prototype manufacture, together with a minimum of G.C.E., O.L., in maths., physics and English.—Write, giving full details, to Personnel Officer, Millora Works, South Denes, Great Yarmouth, Norfolk. [8873

Armstrong

STEREO-TWELVE CHASSIS 36 GNS

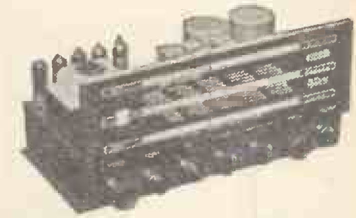

The most complete unit yet produced for stereo giving 6 watts high fidelity push-pull output on each channel, 12 watts total. Full VHF, medium and long wavebands. Stereo and monaural inputs for records, tape and radio and outputs for stereo and monaural tape recording. Comprehensive matching for all types of crystal pick-ups. The perfect basis for a complete monaural reproducing system or for a complete stereophonic system now or later.

STEREO 44 CHASSIS 27 GNS

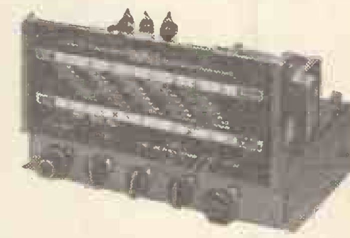

A stereo and monaural chassis providing 8 watts output, 4 watts on each channel, and covering the full VHF and medium wavebands. Stereo and monaural inputs for tape playback and all types of crystal pick-ups and outputs for stereo and monaural tape recording. Separate bass and treble ganged controls together with dual volume control for ease of balancing.

JUBILEE CHASSIS 28 GNS

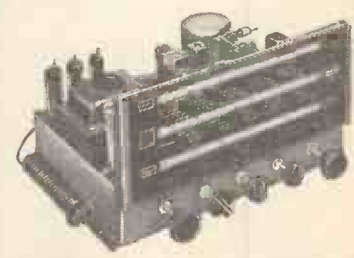

An AM/FM chassis with nine valves and two diodes with push-pull output stage providing 6 watts. Full VHF, medium and long wavebands with automatic frequency control on FM and ferrite aerial on AM. Tape record and playback facilities.

AF208 CHASSIS 22 GNS

See page 60 for details of the new Armstrong Chassis.

Post this coupon or write for descriptive literature or call at our Holloway showroom for full demonstration. Open 9-6 weekdays, 9-5 Sats.

NAME ....

ADDRESS ....

.... WFC

ARMSTRONG WIRELESS & TELEVISION CO. LTD.
Warlters Road, London, N.7
Telephone: NORth 3213

SITUATIONS VACANT

TANNOY PRODUCTS Ltd. Sound Equipment Designers and Engineers, require personnel for their Electrical Test Department. Good all round knowledge and previous experience essential.—Apply Tannoy Products Ltd., Norwood Rd., London, S.E.27. [8901

E. K. COLE, Ltd., Malmesbury, require production testers and inspectors for radar and electronic equipment Ex-service radio and radar fitters suitable. Full canteen & welfare facilities; transport from outlying areas. Applications should be made to Personnel Manager. [0333

ROOTES, Ltd., Birmingham, require experienced radio service engineer with specialised knowledge of Radiomobile, Ecko, etc., to operate Mobile Radio Service; good pay and commissi.n.—Write in first instance to Service Manager, Rootes, Ltd., 90, Charlotte St., Birmingham, 3. [8886

COILWINDING.—Senior engineer required to take charge of design small audio transformers; knowledge of current transistor practice an advantage; applicant would be required to work at Rickmansworth.—Full details to Colne Electric. Ltd., Bury Lane, Rickmansworth. [8909

ENGINEER for audio design work required by small manufacturing Company, West Essex, should have drive and administrative ability; experience in public address field an advantage; ample scope is offered in this appointment.—Write fullest details of experience, salary required, etc., in confidence, Box 6618. [8905

TV/RADIO engineer (fully skilled).—Expanding organisation (Plymouth) has vacancy for above average type; familiar all types, rental business; leadership organising ability essential; opportunity man with ideas, able shoulder responsibility; good wages; superannuation scheme; write stating wages and experience.—Box 6667. [8916

ELECTRONIC engineer required, familiar also with auto-electrical circuits; appointment as development engineer but to be prepared in early stages to assemble and install equipment; keen brain required but very good prospects for the right man.—Phone for appointment Lan. 4746, or write Box W.W. 520, c/o 191, Gresham House, E.C.2. [8883

SKILLED test equipment engineer required to take charge of new section, completely overhaul H.F. and V.H.F. signal generators, audio and R.F. power meters, oscilloscopes, etc., etc.; good pay according to qualifications; Bromley area; write with full details of experience and salary required to—Box No. 6554. [8896

DECCA Navigator Training Department at New Malden require full-time instructor to train senior field engineers in electronic equipment maintenance; excellent prospects for someone combining technical ability with a genuine interest in teaching.—Please apply: Personnel Officer, The Decca Navigator Co., Ltd., 247, Burligton Rd., New Malden, Surrey. [8918

DEVELOPMENT Engineer required by an expanding company, with good practical and theoretical experience of general electronics, also a working knowledge of sheet metal and light engineering practice; staff position; pension scheme and sick club; write giving full details and salary required.—Grundy & Partners, Ltd., 3, The Causeway, Teddington, Middlesex. [8895

RADIO Technicians required by International Aeradio, Ltd., for overseas service. Permanent and pensionable posts. Normally tax-free, inclusive salary in local currency varying with location, and additional marriage and child differentials. U.K. leave, free air passages and insurance. Kit allowance. Qualified candidates to whom replies will be sent write to Personnel Officer, 40, Park St., W.1. [0262

TECHNICAL Sales Engineer is required by the Sales Director of a leading company marketing television and radio receivers and other domestic products; sound technical knowledge preferably coupled with commercial experience are basic requirements together with a pleasing personality and tact in dealing with executives within the organisation and externally.
IN reply, please submit fullest information without which your application may have to be discarded. All applications will be treated with the confidence that such correspondence merits and no references will be taken up without the applicant's permission.—Write Box 6456. [8877

OVERSEAS Oil Exploration Company with world-wide seismic parties offers permanent career to electronic technicians. Work consists in maintaining and operating electronic recording equipment under field conditions. Live generally in camp. Qualification: H.N.C. or equivalent essential, with practical experience in electronics. Home leave every two years.—Box No. 5829. [0331

OXFORD UNIVERSITY COMPUTING LABORATORY has vacancy for electronics engineer, to assist the maintenance of a Ferranti Mercury computer and ancillary equipment; annual stipend £825-£925, according to age and experience, for 40-hour week.—Applications, before 1 Jan., to the Director, University Computing Laboratory, 9, South Parks Rd., Oxford. [8889

EDDY'S (NOTTM) LTD

172 ALFRETON ROAD NOTTINGHAM

GRAM AMPLIFIERS. High sensitivity, 3 watts output, separate volume and tone controls, printed circuit, 59/11. Post and packing 4/- guaranteed. Size 8 x 2¾ x Max. height 5in.

RECTIFIER/STABILISERS for 1.4 v. valves Midget, 3/-. Post 6d.

CONDENSERS, 2000 mfd. 6 v., 1/6. Post 6d.

NIFE ACCUMULATORS. Midget single unit, size 3 x 2¾ 7 amp. hrs., 1/11. Post 1/6.

DYNAMOTORS. 200 v. D.C. to 12 v. D.C. Ideal for train sets on D.C. mains, 19/11. P. 2/6.

CONDENSERS. Tubular wire end (not ex-Govt.), 8 mfd. 450 v., 1/9; 8-8 450 v., 2/6; 16 mf. 450 v., 2/9; 16-8 450 v., 4/-; 16-16 450 v., 3/9; 32 mf. 450 v., 3/9; 32-32 350 v., 4/-. P. 1/-.

VIBRATORS. 12 volt 4 pin, 4/11. Post 1/-.

SPEAKER GOLD GRILL. 6½ x 4, 1/-. P. 6d.

HEADPHONE CORDS. 6ft., 1/11 pr. P. 6d.

JACK PLUGS. Standard Type, 1/11. Post 6d.

MORSE TAPPERS. Plated contacts, adjustable gaps, heavy duty, 3/6. Post 9d.

RELAYS. Siemens high speed, suitable for model controls, 8/11. Post 1/3.

DIMMER SWITCHES. Ideal for train speed regulators, 1/11. Post 9d.

RECTIFIERS. RM1, 4/9; RM2, 6/6; RM3, 7/6; RM4, 15/6; RM5, 19/6. Contact cooled. Miniature 200 v. 60 ma., 7/6. Post 1/-.

GERMANIUM DIODES, 1/- each; 9/6 doz. P. 4d.

CAR RADIO KITS. 7 transistor. Long and Medium waves. 2 watts output, R.F. stage and automatic gain control, 6 or 12 volts. Complete kit with cabinet, 10 gns. Post and packing 5/-.

ALL ABOVE ARE NEW AND GUARANTEED.

1A7GT	12/6	25Z4G	8/-	EF40 ...	13/6
1C5GT	10/6	35A5 ...	12/6	EF41 ...	8/6
1D5 ...	9/6	35W4 ...	6/9	EF42 ...	7/6
1H5GT	9/9	35Z3 ...	13/6	EF50 ...	1/9
1L4 ...	3/9	35Z4 ...	7/6	EF80 ...	6/6
1N5GT	9/9	807(B)	3/9	EF85 ...	7/6
1R5	7/-	954	1/6	EF86 ...	11/-
1S5	6/6	955	3/11	EF91 ...	4/-
1T4	4/9	956	2/11	EL41 ...	9/3
3S4	7/6	9001 ...	4/6	EL42 ...	9/6
5U4G ...	5/9	9004 ...	4/-	EL84 ...	8/3
5Z4G ...	9/-	9006 ...	4/-	EL85 ...	9/6
6AG5 ...	5/-	AZ1	12/6	EY51 ...	9/6
6B8G ...	2/11	AZ31 ...	9/-	EY86 ...	8/6
6BA6 ...	6/6	DAF96	8/3	EZ40 ...	7/-
6BJ6 ...	6/6	DF96 ...	8/6	EZ80 ...	7/-
6C4	3/6	DK92 ...	9/6	GT1C ...	7/6
6F33 ...	5/6	DK96 ...	8/6	L63	3/-
6J5G ...	2/6	DL96 ...	8/6	MU14 ...	8/6
6J5M ...	4/6	DM70 ...	7/6	PCC84	8/6
6J5GT ...	3/6	EABC80	9/-	PCF80	9/-
6K7G ...	2/3	EAF42 ...	8/6	PL81 ...	10/6
6K8G ...	6/6	EB34 ...	1/6	PL82 ...	7/9
6P28 ...	9/-	EB41 ...	7/6	PL83 ...	8/9
6Q7G ...	8/3	EB91 ...	4/6	PY31 ...	8/6
6SA7M	6/-	EBC41 ...	9/-	PY80 ...	7/-
6SG7M	5/-	EBF80 ...	9/-	PY81 ...	8/6
6SN7GT	4/9	ECC81	6/-	PY82 ...	7/-
6V6G ...	5/11	ECC82	7/-	PEN36C	9/6
6V6GT	6/-	ECC83	7/6	U35 ...	8/6
6X4 ...	6/-	ECC84	9/6	UAF42	9/-
6X5GT	6/6	ECC85	8/6	UB41 ...	8/6
7C5	7/6	ECF80	10/6	UBC41	8/6
7C6	7/6	ECH42	9/6	UCH42	9/-
7S7	9/6	ECH81	9/-	UF41 ...	8/9
7Y4	7/6	ECL80	9/6	UF42 ...	8/-
12A6 ...	6/6	ECL82	11/-	UL41 ...	8/6
20D1 ...	9/6	EF36 ...	2/6	UL41 ...	8/6
25L6GT	9/6	EF37 ...	4/-	UY41 ...	7/-

SURPLUS NEW AND GUARANTEED VALVES

Any parcel insured against damage in transit for only 6d. extra per order. All uninsured parcels at customer's risk. Postage and packing 6d. per valve extra. Over £3 free. C.O.D. or C.W.O. only. C.O.D. charge 3/- extra.

S.A.E. WITH ENQUIRIES

SITUATIONS VACANT

AIRCRAFT radio engineers and mechanics required with specific workshop experience of one or more of the following: VHF, HF/MF, ADF, ILS, VOR, X band radar; 44-hr. week. top basic wages—engineers £16 p.w., mechanics £14 p.w.; overtime and bonus system in operation.—Apply in writing, stating experience, to: Managing Director, Air Transport (Charter), (C.I.), Ltd., 7, Willow Rd., Poyle Trading Estate, Colnbrook, Slough, Bucks.

A VACANCY occurs for a first-class R.F. Service Engineer, in the London area; he must have thorough practical and theoretical experience in all aspects of his craft, and preference will be given to applicants also experienced in pneumatics and electronic switchgear; a good salary and excellent prospects are offered; apply, stating age, date available, and giving brief summary of qualifications to —Box 6541. [8891

VACANCIES exist for senior and junior laboratory engineers to work on sound recording and reproducing equipment and kindred projects for T.V., 35 and 16mm films, experience with transistors an asset; salary according to age and experience; pension scheme, staff canteen, 5-day week.—Applications in writing, giving details of education and experience, should be forwarded to: Personnel Officer, Rank Precision Industries, Ltd., Woodger Rd., Shepherds Bush, W.12. [8908

ELECTRONIC authors.—The Company is able to offer positions to electronic authors who should be experienced in the compilation of civil and service publications, and familiar with various types of electronic equipments.—Authors, and also engineers who possess a flair for this work, are invited to write for an interview, stating full relevant details of previous experience, etc., addressed to Personnel Manager, Marshalls' Flying School, Ltd., Airport Works, Cambridge. [8907

INSTITUTE of Cancer Research: Royal Cancer Hospital. Technician to work in Physics Department situated in Royal Marsden Hospital, Fulham Road, S.W.3. Capacity to maintain and service existing electronic equipment and assist with design and construction of new apparatus. Wide range of research and scope offered to enthusiasm and ability. Salary within M.R.C. scale £535—£655. Applications, with names and addresses of three referees, to the Secretary, 33 Sumner Place, S.W.7, quoting Ref. 301/B/20. [8904

B.E.A. require a radio engineer to assist in the development of airborne radio communication and navigation systems, prepare performance specifications and investigate defects; applicants should have City and Guilds Final Certificate in Telecommunications or H.N.C. (Radio) and at least 2 years' experience of radio/radar systems or equivalent experience in other spheres; salary £940-£1,120.—Write to Personnel Manager, Engineering, British European Airways, Engineering Base, London Airport, Hounslow, Middlesex. [8917

ERIE RESISTOR, Ltd., require a young man, aged 21 to 25 years, smart appearance, educated to G.C.E. standard and preferably with O.N.C. or equivalent experience in the radio field, to act as a junior assistant to the quality control engineer; duties will embrace the handling of correspondence on various technical issues concerned with the end usage of radio components manufactured by the company; good salary, superannuation, etc.—All applications will be treated in strict confidence and should be addressed to the Personnel Officer, Millora Works, South Denes, Great Yarmouth, Norfolk. [8874

CIRCUIT Designers and Circuit Laboratory Engineers required for design and testing of automatic telephone exchange systems and other similar projects. Candidates should have had previous experience of this work and preferably have at least an O.N.C. or an intermediate grouped C. & G. certificate. Knowledge of Crossbar Switching or totalisators would be an advantage. Good salary paid to selected applicants. Pension scheme after qualifying period

WRITE giving full details of qualifications and experience to the Personnel Manager, Ericsson Telephones Limited. Beeston, Nottingham quoting Ref. DA/1 [0160

R.E.M.E. Technical Services (Woolwich).—Technical Assistants, Grade III. A first-class opportunity for entry into the Technical Branch of the Civil Service. Suitably qualified men are urgently required for training as Scales Assessors in Scales Branch, Electrical and Guided Weapons Wing, R.E.M.E. Technical Services. The job consists of assessing scales of spare parts needed to maintain and repair guided weapons systems and radar and control equipments, and entails liaison with commercial firms. Experience in repair of Service radar or control equipment at all levels essential. Training in scales work, together with equipment training, will be given.

APPLICANTS must hold a C. & G. Intermediate Certificate in Telecommunications Engineering with Radio II or, O.N.C. in Electrical Engineering, or produce evidence of an equiv. standard of technical education, or have passed a R.E.M.E. Artificer Course. The appointment carries a starting salary of £720 at 26 years rising to £900, with good prospects of promotion, 3½ weeks' leave a year, plus other benefits and privileges. Write, giving age, full details of quals. and exp. to Manager (P.E.2863), Ministry of Labour, Professional and Executive Register, Atlantic House, Farringdon Street, London, E.C.4. [8885

Enclosures, Equipment & Cabinets by STAMFORD

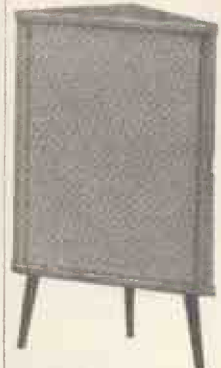

QPS/14
Price £8/19/6

S 27
Price £13/15/-

QPS/14. Size 14½in. side panels, 34in. high, to house any 8in. speaker (state aperture required). Price £8/19/6. or 27/- deposit and 9 monthly payments of 18/2.
S.27. Column enclosure to house any 10in. speaker. Size 12in. × 12in. × 43in. Price £13/15/-, or 41/- deposit and 9 monthly payments of 27/11.

EQUIPMENT	Cash Price £	s	d	Hire Deposit	Purchase 18 Mths.
AMPLIFIERS					
Rogers HG 88	37	10	0	112/6	40/9
Leak TL/12	31	10	0	94/6	34/2
STEREO					
Avantic SPA II	29	8	0	88/6	31/11
Quad 22 Control	25	0	0	75/-	27/2
Leak 20 and Control..	51	9	9	154/6	55/8
TUNERS					
Quad FM	28	17	6	87/-	31/4
Chapman FM85	28	17	6	87/-	30/9
CHASSIS					
Armstrong Jubilee ..	29	8	0	88/-	31/10
Armstrong Stereo 44	28	7	0	85/-	30/10
SPEAKERS					
Axiom 300	11	5	9	33/6	11/5
Golden 10in. FSB ..	8	6	7	25/-	9/-
MOTORS					
Collaro 4T/200	18	12	0	55/6	20/4
Connoisseur Type B ..	27	16	1	82/6	30/3
Garrard 4 HF	18	9	9	55/6	20/1
Garrard 301	22	7	3	67/-	24/3
Lenco GL58/580	25	8	8	78/-	27/8

Write for our New Hi-Fidelity Equipment List and Illustrated list of Complete Systems.

WE SPECIALIZE in supplying and fitting any equipment currently available. NO FITTING CHARGE. DEMONSTRATIONS AT OUR WEYMOUTH TERRACE SHOWROOMS

GP 60 Price £19/19/-

Suitable for housing stereo equipment including two amplifiers, FM and Control Units, Tape Deck and Gram. This model will house the Ferrograph Tape Deck with ease. Price £19/19/-. Or £3 Deposit and 9 payments of 40/7 monthly.

Cabinets veneered in oak, walnut and mahogany, finished in shade required. Delivery England and Wales 12/6. Scotland and Northern Ireland 25/-. Satisfaction Guaranteed or Money Refunded.

Write for our Illustrated catalogue or visit our Hi-Fidelity Showrooms at

84/86/98 Weymouth Terrace, off Hackney Rd. LONDON, E.2 *Telephone: SHO 5003*

Directions: No. 6 bus from Liverpool Street Station to the Odeon, Hackney Road. Walk back two turnings.

A. L. STAMFORD LTD. (Dept V.4)

SOLDERING EQUIPMENT BY

LITESOLD

REGD. TRADE MARK

PRECISION SOLDERING INSTRUMENTS for the ELECTRONICS INDUSTRY

- Comprehensive range
- Robust and Reliable
- Light weight
- Rapid heating
- Bit sizes 3/32in. to 3/8in.
- 'PERMABIT' or Copper bits
- All voltage ranges 6/7v. to 230-250v.
- Prices from 19/6.

Illustrated is the 25w. 3/16in. replaceable bit model with safety shield.

British and Foreign Patents. Registered designs. Suppliers to H.M. and Foreign Governments. Agents throughout the world.

Brochure No. S.5 sent free on request.

Sole proprietors and manufacturers:

LIGHT SOLDERING DEVELOPMENTS LTD.
26 Sydenham Road, Croydon, Surrey

Phone: CROydon 8589 Grams: Litesold Croydon

METER REPAIRS

All makes of Single and Multi-range instruments repaired and recalibrated.

★ *Prompt Service*
★ *All work guaranteed*
★ *Priority for urgent orders.*

Competitive prices for repairs to all types of instruments. Contracts a speciality.

New meters supplied from stock (2" to 6") and complete equipment manufactured to specification.

Call, write or phone for details to:

E.I.R. INSTRUMENTS LIMITED
329 Kilburn Lane, London, W.9 *Tel: LAD 4168*

PARALEX ADJUSTABLE HOLE CUTTER

Morse Taper Shanks

No. 4, 3, 2, 1.

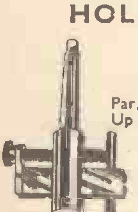

Par. Shanks from ⅜in. to ⅝in. Up to 12½in. dia. Hole capacity.

TEN MODELS

Sold throughout the world

Send for illustrated catalogue to

LUDFRY LTD.
5 Hanway Place, London, W.1
Telephone: MUSeum 7472

SITUATIONS VACANT

MINISTRY of Aviation require electrical engineers (Assistant Signals Officers) for aviation telecommunications and electronic navigational aids. Min. age 23, 1st or 2nd Class degree in physics or engineering, or A.M.I.E.E. or A.F.R.Ae.S. (candidates with Parts I, II & III of A.M.I.E.E. or Parts I and II of A.F.R.Ae. S. or equiv., or of very high professional attainment without these quals. considered). Salary £690 (age 23) to £1,125 (age 34) max. £1,300. Slightly lower outside London and for women. Promotion prospects. Further details and forms from Ministry of Labour, Technical and Scientific Register (K), 26, King Street, London, S.W.1, quoting D.554/9A. [0026

D.S.I.R. requires Assistant Experimental Officer/Experimental Officer at Radio Research Station, Ditton, Datchet, Slough, Bucks, to prepare abstracts of Scientific and Technical articles on radio research and development. Quals.:—G.E.C. "A" level in two science or maths. subjects or equiv. preferably in Physics or Electrical Engineering. Over 22, Pass degree, H.N.C. or equiv. generally expected. Experience in radio research or development, or communications, and ability to read technical French and German an advantage. Salary ranges:— A.E.O. £382 10s.—£830. E.O. £954—£1,166. Forms from Ministry of Labour, Technical and Scientific Register (K), 26, King Street, London, S.W.1. (quote A.340/9A). Closing date 19th February, 1960. [8899

ADMIRALTY require Technical Class Grade III Officers for its Naval Aircraft Repair Organisation. Vacancies exist primarily in the London, Portsmouth, Belfast and Chippenham areas. Candidates must be British Subjects, aged 21 or over. Quals.—a recognised apprenticeship, O.N.C. or equiv. in Electrical Engineering and a good knowledge of electronics as applied to Airborne Radar and Radio equipment and instruments. Service in the Air Electrical Branch of R.N. or R.A.F. would be valuable. Five day week, eighteen days' annual leave, salary in the range £565 (age 21) to £750 on entry, rising to £875 (National rate). The posts are non-pensionable. Applications, with full personal details to Ministry of Labour, Professional and Executive Register, 20 Nelson Street, Bristol, 1, quoting PE 5343. [8903

INSTRUCTOR (Telecommunications) required by Sierra Leone Government Technical Education Department on contract for three tours of 10/12 months each in first instance; salary according to age and experience in scale (including inducement addition) £966, rising to £1,528 a year; gratuity at rate of 15% of total salary drawn; outfit allowance £60; children's allowances £48 to £288 per year; liberal leave on full salary; free passages for officer, wife and 3 children under 18 years; candidates should be between 22 and 45 years of age and must possess C. and G.; Full Technological Certificate in Telecommunications specialising in radio transmission or similar qualifications with at least five years practical experience; experience in Technical Education desirable; write to the—Crown Agents, 4, Millbank, London, S.W.1. State age, name in block letters, full qualifications and experience and quote M2A/50686/WF. [8897

AIR MINISTRY require experimental/assistant experimental officers in (1) Soils Laboratory Cardington, Bedford, Ref. E518/9A. (2) Ruislip, Middlesex, Ref. D641/9A. (1) Duties to take charge of small soil survey teams engaged on foundation investigations for runways, buildings and other civil engineering works at airfields, etc., and to progress and supervise associated laboratory testing. Work requires ability to use Geological Survey maps and publications in interpretation of results of survey. Quals. Higher School Certificate (pref. including geology) or H.N.C. or equiv. quals. and wide experience in responsible capacity in connection with field surveys and associated standard laboratory tests for soils investigations. (2) Duties, experimental work in connection with installation, operation, adaptation and modification of radio equipment and aerials. Quals., H.N.C. Elect. or equiv. quals. and sound general knowledge of principles of radio; practical experience of one or more ground radio systems employed in R.A.F. such as navigational aids, air/ground communications, long range communications or radar an advantage. Salary scales: Cardington E.O. £954-£1,166, A.E.O. £382/10-£830; Ruislip E.O. £1,005-£1,233, A.E.O. £397/10-£880. Forms from Ministry of Labour, Technical and Scientific Register (K), 26, King St., London, S.W.1, quoting appropriate reference. Closing date 12 February, 1960. [8894

SITUATIONS WANTED

ELECTRONIC technician, 29, Portuguese, 7 years' experience in radar, radiation research equipment, etc.—Write to Estradada Portela, 40-3°-D-Lisbon, Portugal [8914

TECHNICAL TRAINING

LEARN Radio and Eectronics the New Practical Way! Very latest system of experimenting with and building radio apparatus—"as you learn"—Free brochure from Dept. W.W.10, Radiostructor, 46, Market Place, Reading, Berks [0241

CITY & GUILDS (electrical, etc.) on "No Pass—No Fee" terms; over 95% successes. —For details of modern courses in all branches of electrical engineering, applied electronics, automation, etc., send for our 148-page Handbook—free and post free.—B.I.E.T. (Dept. 388A), 29, Wright's Lane, London, W.8. [0017

SERVO & ELECTRONIC SALES LTD

COMMUNICATIONS RECEIVERS R107. 1.2-17 Mc/s. in 3 ranges, mains/batty. optn., £9/19/6 (carr. 20/-). **QUARTZ CRYSTALS.** 8 Kc/s. 17/6; 10 Kc/s. 25/-; 200 Kc/s. 20/-; 500 Kc/s. 25/-; 1 Mc/s. 30/-; 2 Mc/s. 25/-; 5 Mc/s. 30/-; 10 Mc/s. 35/- (p.p. 2/-). **CRYSTAL BASES.** ⅜in. pin spacing 2/6; ceramic ½in. and ⅜in. pins 3/9 (p.p. 9d.). **CRT MUMETAL SCREENS.** ET5 22/6; 4EP1 17/6 (p.p. 3/6) **GERMANIUM DIODES** (new and guaranteed not rejects). GEX 34 2/-; GEX 35 2/6; GEX 55/1 5/-. **SILICON DIODES.** GJ6M 10/-; Z810A 12/6; ZR20 15/6 (diode p.p. 1/-). **FERRANTI COLD CATHODE THYRATRON.** GN 10 12/6 (p.p. 1/-). **VALVE SCREENING CANS.** B9A, black oxidised, spring 8d; B7G ditto 6d. (p.p. 4½d.). **ELECTRO-THERMAL VALVE RETAINERS.** VRK8 1/3; VRK73 9d.; VRK75 9d.; VRK157 1/3; VRY4 1/6; VRY15 1/9 (p.p. 6d.), many other types in stock. **B5 VALVEHOLDERS.** E.H.T. 2/- (p.p. 6d.), most other sizes available. **MAINS/BATTERY POWER UNIT.** L332, 12 v. D.C. or 110-250 v. A.C. in., 12.6 v. 2 A. 250 v., 75 mA. D.C. out, 19in. rack mtg., with cct. 37/6 (p.p. 5/-). **E.H.T. TRANSFORMER.** 230 v. A.C. to 9.5 Kv. 3 mA., herm. sealed 55/- (p.p. 3/6). **E.H.T. CAPACITORS.** Visconol, 0.02 μF 11 Kv. 12/6 (p.p. 2/6). 0.1 μF 11 Kv. 17/6 (p.p. 3/6). **COLVERN HELICAL POTENTIOMETERS.** CLR2501, 50 K. 55/- (p.p. 1/6). **HISTAB RESISTORS.** 5% tol. 22/6 per 100 our sel. (p.p. 1/6). **CAPACITANCE /RESISTANCE UNITS,** 2 res. arms 1-4,332 ohms, 2 cap arms 0.001-4.332 μF with data sheet 17/6 (p.p. 3/6). **DRAYTON TYPE RQ GEARED MOTORS.** 37 r.p.m. 230 v. A.C. 75/- (p.p. 4/-). 400, 1,100r and 2,000 c.p.s. **ALTERNATOR SETS** in stock, write fos details. **RECTIFIER UNITS** in 200-250 v. A.C. out 12 plur 12 v. ea. at 3 A. 92/6 (carr. 7/6). **SMOOTHING UNITS** fo. this item 37/6 (carr. 10/-). Both units 19in. rack mounting. **INDICATOR UNIT.** APW 9922A, 1-VCR97, 3-VR91, 2-VR54, 1-CV1285, 1-VT61, numetal shield, focus and brill, controls, 8 pots, ideal for 'scope conversion or C.R.T. display unit. New with circuit 37/6 (carr. 5/-). **TELCON TYPE 53 CHASSIS SOCKETS.** New 10/- doz. (p.p. 2/6); £30 per 1,000 c.p. **NITROGOL CAPACITORS.** 400 v. wkg. 1 μF 2/3 (p.p. 1/-); 2 μF 2/9 (p.p. 1/-). **CAM CORRECTED POTENTIOMETERS.** 10 K., CLR 8302 35/- (p.p. 3/-). **MINIATURE MERCURY SWITCHES** s.p.c.o. 4/- (p.p. 6d.). **CARPENTER POLARIZED RELAYS,** each-side-stable type, operate at 0.25 v. 2.2 mA. 27/6 (p.p. 1/-). **S.T.C. SEALED RELAYS.** 4186ED 17/6 (p.p. 1/-). **BRIDGE MEGGERS.** 500 v. Ser. II, completely reconditioned and guaranteed £21 (carr. 7/6). **DEMONSTRATION GALVO MOVEMENTS.** 250-0-250 microamps., 5in. dia. scale, robustly constructed. not in case. Ideal for schools 20/- each (p.p. 3/6). **MOORE & WRIGHT RATCHET SCREWDRIVERS.** 4in. 6/-, 5in. 6/6, 6in. 7/- (p.p. 1/6). **No. 11 OSCILLOSCOPES.** 3in. C.R.T., mains input, 1-5-40 mS. time base, superb instrument in brand new condtion £11/10/- (carr. 20/-). **RECEIVERS R206.** A few only remaining at £20 Remember the coverage! 10-6,000 metres; (carr. extra). S.A.E. for list.

Post orders to:—
1, Hopton Parade, Streatham High Rd., London, S.W.16.
Callers to: 43, High St., Orpington, Kent.
Tels.: Orpington 31066; Streatham 6165.
Terms: nett c.w.o., monthly, approved acconnts.

Listen round the world with the

EDDYSTONE 840A

Communications Receiver

AC/DC 110/240 volts

Continuous Coverage 30 mc/s (10 metres) to 480 kc/s (610 metres)

PRICE £55

Webb's extended terms, deposit £11.0.0 and 12 payments of £3.17.9 or 18 payments of £2.13.4

WEBB'S RADIO
14 SOHO STREET, LONDON, W.1
Telephone: GERrard 2089/7308

TELEPRINTERS, PERFORATORS, REPERFORATORS, TAPE READERS

Terminals and V.F. Telegraph multi-channel units; Testing Equipment Telephone Carriers and Repeaters; Signalling Rectifiers and Relays, Transformers Transmit and Receive, Filters; Repeating and Retardation Coils; Racks, Relay Bases, Uniselectors, Remote Control Transmitters, British, American, and German Equipment.

BATEY & CO., GAIETY WORKS,
Akeman Street, Tring, Herts.
Tel.: TRING 2183 and 2310

COVENTRY RADIO LTD.

189/191 Dunstable Road, LUTON.
Audio & Component Specialists Est. 1925

If you are unable to visit us at Luton, send for a copy of our

HI-FI CATALOGUE

of 300 items 70 pages.
Price 1/- plus 6d. postage.

Also available now

"THE GRUNDIG BOOK"

12/6 plus 1/- postage.
If you own a tape recorder of any make you will find this book an essential for successful recording.

LUTON'S HI-FI CENTRE

Telephone Luton 7388/9

HIGH GRADE TEST EQUIPMENT

LESLIE DIXON & CO. have pleasure in announcing that they have purchased the complete stock of HIGH GRADE TEST EQUIPMENT from HATFIELD INSTRUMENTS LTD. All items have been rebuilt and calibrated in the Hatfield Laboratories and a selection is offered below :—

EQUIPMENT BY MARCONI INSTRUMENTS LTD.,

Q Meter, Type TF.329G, 50 Kc/s. to 50 Mc/s.
Q Meter, Type TF.866A, 15 Mc/s. to 170 Mc/s.
Output Meter, Type TF.340, 5 mW. to 5 watts.
Signal Generator, Type TF.762B, 300 Mc/s. to 600 Mc/s.
Beat Frequency Oscillator, Type TF.195/4, 50 c/s. to 150 Kc/s. complete with filter, attenuator 1μV to 1 volt. Max. output 2 watts into 50 ohms.
Universal Impedance Bridge Type TF.373D.

Write for complete list, now ready.

Leslie Dixon & Co.
Dept. A. 214 QUEENSTOWN ROAD, LONDON S.W.8.
Telephone: MACaulay 2159

TUITION

ROYAL TECHNICAL COLLEGE, Salford 5, Lancs.
DEPARTMENT of Electrical Engineering.
A COURSE of six evening lectures entitled "PRINCIPLES for the Design of a Computing System."
WILL be given on Tuesdays at 7 p.m., starting on February 23rd, 1960. This course is designed to introduce the logic underlying computer design and its simple applications. The course will be of interest to persons with or without previous knowledge of the subject.
THE fee for the course is £1 11s 6d.
FURTHER details may be obtained from the Head of Department. [8878

FULL-TIME courses for P.M.G. Certificates, C.G.L.I., Telecommunications and Radar Maintenance Certificates.—Information from College of Technology, Hull. [0111

ALL Examinations easier to pass by I.C.S. home study methods. A.M.Brit.I.R.E., C & G. Telecoms, Radio and TV Servicing, etc.—Write for free Prospectus, International Correspondence Schools Ltd., Intertext House, Parkgate Rd. (Dept. 442A), London, S.W.11. [0033

INCORPORATED Practical Radio Engineers home study courses of radio and T.V. engineering are recognised by the trade as outstanding and authoritative; moderate fees to a limited number of students only; syllabus of instructional text is free; the Practical Radio Engineer journal, sample only 2/-; 6,000 alignment peaks for superhets, 5/9; membership and entry conditions booklet 1/- all post free, from the Secretary, I.P.R.E., 20, Fairfield Rd., London N.8 [0088

WIRELESS.—See the World as a radio officer in the Merchant Navy; short training period, low fees, scholarships, etc., available, boarding and day students; stamp for prospectus.—Wireless College, Colwyn Bay. [0018

"HOW and Why" of Radio and Electronics made easy by a new, no-maths, Practical Way. Postal instructions based on hosts of experiments and equipment building carried out at home. New Courses bring enjoyment as well as knowledge of this fascinating subject.—Free brochure from Dept. W.W.12 Radiostructor, 46, Market Place, Reading, Berks. [0240

T.V. and Radio—A.M.Brit.I.R.E., City and Guilds, R.T.E.B. Cert., etc., on "No Pass—No Fee" terms over 95% successes.—For details of exams. and home training courses (including practical apparatus) in all branches of radio, T.V. and electronics, write for 148-page Handbook—free—B.I.E.T. (Dept. 397A), 29, Wright's Lane, London, W.8. [0016

A.M.I.Mech.E., A.M.Brit.I.R.E., City & Guilds, G.C.E., etc., bring high pay and security; "No Pass—No Fee" terms; over 95% successes.—For details of exams. and courses in all branches of engineering, building, electronics, etc., write for 148-page Handbook—free.—B.I.E.T. (Dept. 387B), 29, Wright's Lane, London, W.8. [0118

LEARN-AS-YOU-BUILD course in basic radio, electronic and electrical theory with practical training building a 4-valve TRF and 5-valve superhet radio receiver; Signal Generator and high-quality Multitester.—Write for FREE book. International Correspondence Schools, Intertext House, Parkgate Road (Dept. 442), London, S.W.11. [0358

BOOKS, INSTRUCTIONS, ETC.

"W.W.", Jan., '44, to Dec., '58, unbound; offers.—47, Newstead Ave., Hinckley, Leics. [8913

W.W., 10 vols., 1947-1956, first 5 in easi-bind titled binders, good condition; offers.—Box 6623. [8906

CATALOGUE No 14 Government surplus and model radio control, over 500 illustrated items, 2/- (refunded on purchase), p.p. 6d. —Arthur Sallis Radio Control Ltd., 93 (C), North Rd., Brighton. [0193

BOOKS for C. and G. exams.: Telecom. Principles, A. and B. 9/6; Telecoms. (Principles). 1 and 2. 10/6; Maths. for Tels., 1, 7/-; Maths. for Tel., 2, 5/-; all post free.—Riddiford, 384, Tilehurst Rd., Reading, Berks. [8652

"ABACS or Nomograms" By A. Giet. Translated from the French by H. D. Phippen and J. W. Head. Most engineers have made use of nomograms at some time in their careers, and are fully alive to the fact that they are a very convenient tool when the same formula has to be solved repeatedly for several sets of variables. It is fair to say, however, that only a small proportion of even those who habitually employ nomograms know how to construct them for their own use. Most of the comparatively small literature on the subject is written for mathematicians and is extremely difficult for the practical engineer to comprehend. This book is essentially practical, and not only demonstrates the many and varied applications of the abac or nomogram, but shows how even those without highly specialized mathematical knowledge may construct their own charts. 35/- net. From all booksellers. By post 36/- from Iliffe & Sons Ltd., Dorset House, Stamford St., London, S.E.1.

"INTRODUCTION to Valves." By R. W. Hallows, M.A.Cantab., M.I.E.E., and H. K. Milward, B.Sc.Lond., A.M.I.E.E. Describes the principles, construction, characteristics and uses of most types of radio valves. The approach is simple and, as far as possible, non-mathematical, but the book provides the student with a thorough understanding of valves and how they work. 8/6 net from all booksellers. By post 9/4 from Iliffe & Sons Ltd., Dorset House, Stamford St., London, S.E.1.

THRILLING PERFORMANCE

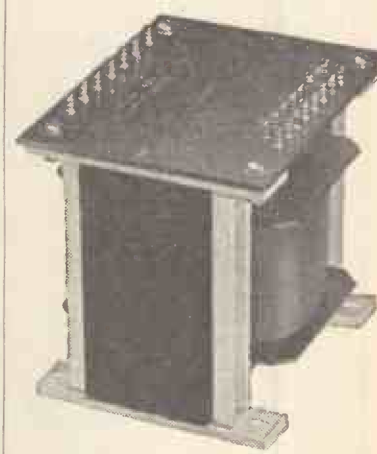

Certain conductors can extract from an orchestra the most thrilling and exciting performances, making others seem lifeless and uninteresting. The same can be said for a Massicore output transformer. With a good amplifier and other equipment it can bring to life such performances that will thrill in a way you may not have experienced before.

MASSICORE SAVAGE

SAVAGE TRANSFORMERS LTD.

NURSTEED ROAD
DEVIZES, WILTSHIRE
Telephone: Devizes 932

BOOKS, INSTRUCTIONS, ETC.

"ADVANCED Theory of Waveguides." By L. Lewin. Sets out various methods of treating problems arising in work on this complex subject. The author has selected for discussion a number of topics as representative of the field in which the centimetre-wave engineer is engaged, many of the examples being concerned with the rectangular waveguides, 30/- net from all booksellers, 31/- by post from Iliffe & Sons Ltd., Dorset House, Stamford St., London, S.E.1.

"TELEVISION Explained." B. W. E. Miller, M.A. (Cantab.), M.Brit.I.R.E. Revised by E. A. W. Spreadbury M.Brit.I.R.E. The sixth edition of a book which assumes a knowledge of the ordinary sound receiver, but no previous knowledge of television circuits. It is non-mathematical, written in simple language and comprehensively illustrated by many diagrams and photographs. It will prove of great assistance to all students of television, to radio service engineers who wish to embark upon television work and want to understand the principles and circuits involved, and to knowledgeable owners of television receivers who would like to understand the working of their set. 12/6 net from all booksellers. By post 13/5 from Iliffe & Sons Ltd., Dorset House, Stamford St., London, S.E.1.

"SECOND Thoughts on Radio Theory." By Cathode Ray of WIRELESS WORLD. Forty-four articles reprinted from popular WIRELESS WORLD series, in which the author examines various aspects of elementary radio science, explains them clearly, and shows that there may be more behind them than is apparent from the usual text-book. This volume deals with basic ideas; circuit elements and techniques; circuit calculations; and some matters in lighter mood. An entertaining and helpful text-book for the student, refresher course for the engineer, and reference book for all combined; 25/- net from all booksellers. By post 26/4 from Iliffe & Sons, Ltd., Dorset House, Stamford Street, S.E.1.

NOW BUILD IT WITH A Jasonkit

Jason offer a number of constructional kit designs to meet requirements in modern test equipment and high-fidelity reproduction. The kits are readily available and embody excellent functional characteristics with clean layout, robust construction and satisfying appearance.

JASON KITS REMAIN AS EVER THE FINEST IN THEIR CLASS. THEY ARE BRITISH DESIGNED TO HIGH TECHNICAL STANDARDS.

Valves extra except where stated.

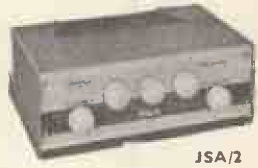
JSA/2


FMT/1

TEST EQUIPMENT

Prices include Valves and CRT.

Oscilloscope OG.10
Ideal for the service engineer and experimenter £22 10 0

Audio Generator AG.10
Range 10 c/s to 100 Kc/s ... £14 5 0

Crystal Controlled Calibrator CC.10
Covering 10 Kc/s to 250 mc/s £16 19 0

Audio Attenuator
Provides 9 stages from 1 to 40 db.......................... £6 0 0

Stabilised Power Packs with Meters
PP20M—300-350v. at 175 mA £22 10 0
PP10M—250-300v. at 85 mA £19 0 0
PP20 (less meter) £16 5 0
PP10 (less meter) £12 15 0

Valve Voltmeter EM10 ... £18 10 0

AUDIO & RADIO

JSA/2
Stereo amp. £13 19 0

JTV/2
Tuner—B.B.C. F.M. and with T.V. sound channels at turn of a switch £12 19 0

FM/1
F.M. Tuner—In chassis form £5 5 0
Power pack for above £2 1 9

Mercury
Switched F.M. Tuner with 2 valves in front end ... £8 13 11

FMT/3
F.M. Tuner—Variable AFC, dual limiters................. £8 5 0

Everest Transistor Portable
7 transistors, R.F. stage, high quality speaker £15 18 9
Six transistor model £13 19 9

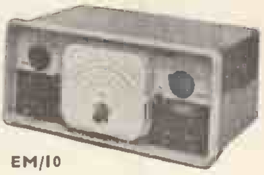
EM/10


FMT/3

Demonstrations
of Jason kits and other Jason equipment daily in our showrooms. 8 p.m. Thursdays.

FULL DESCRIPTIVE LITERATURE SENT ON REQUEST.

THE JASON MOTOR & ELECTRONIC CO., 3-4 (D) GT. CHAPEL ST., OXFORD ST., LONDON, W.1. *GER 0273-4*
(Between Oxford Circus and Tottenham Court Road.)

CLASSIFIED ADVERTISEMENTS

Use this Form for your Sales and Wants

To "Wireless World" Classified Advertisement Dept., Dorset House, Stamford Street, London, S.E.1

PLEASE INSERT THE ADVERTISEMENT INDICATED ON FORM BELOW

- **RATE: 9/- for TWO LINES. 4/6 every Additional Line. Average six words per line.**
- **Name and address to be included in charge if used in advertisement.**
- **Box No. Allow two words, plus 1/-.**
- **Cheques, etc., payable to Iliffe & Sons Ltd., and crossed "& Co."**
- **Press Day, Thursday January 28th for March 1960 issue.**

NAME ....

ADDRESS ....

....

REMITTANCE VALUE............ENCLOSED

Please write in block letters with ball pen or pencil.

NUMBER OF INSERTIONS ....

INDEX TO ADVERTISERS

Printed in Great Britain for the Publishers, ILIFFE & SONS LTD., Dorset House, Stamford St., London, S.E.1, by CORNWALL PRESS LTD., Paris Garden, London, S.E.1. *Wireless World* can be obtained abroad from the following: AUSTRALIA and NEW ZEALAND: Gordon & Gotch, Ltd. INDIA: A. H. Wheeler & Co. CANADA: The Wm. Dawson Subscription Service, Ltd.; Gordon & Gotch, Ltd. SOUTH AFRICA: Central News Agency, Ltd., William Dawson & Sons (S.A.), Ltd. UNITED STATES: Eastern News Co., 306 West 11th Street, New York 14.

Introducing—

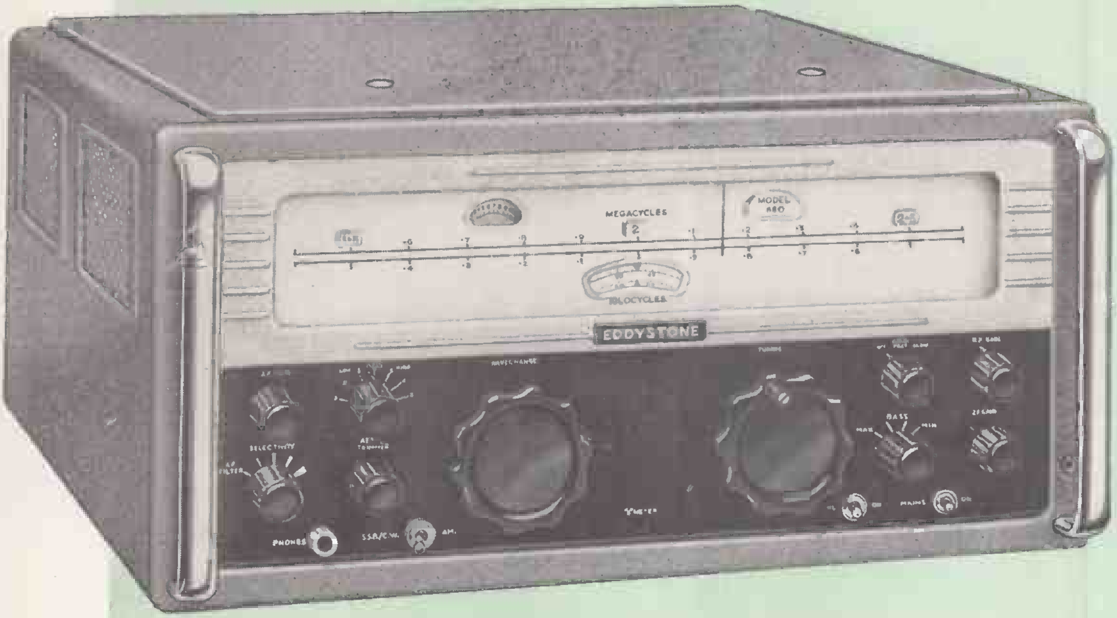

—the EDDYSTONE '880'

High Stability Communications Receiver

The Eddystone " 880 " High Stability Communications Receiver, now in the production stage, reaches high modern standards. It has been designed expressly for use in professional communications systems and, with the many refinements provided, is widely versatile in its applications.

The principle employed results in an exceptionally high degree of frequency stability. Throughout the tuning range of the receiver, which is from 500 kc/s to 30.5 Mc/s, the long term drift does not exceed 50 cycles. Particular care has been taken to reduce spurious responses to an absolute minimum and the figures for such characteristics as cross-modulation, blocking, inter-modulation and image ratio are extremely good. The electrical performance is well maintained in every way and conforms to accepted professional standards.

There are two fully tuned r.f. stages and all tuning is accomplished with a single knob. The tuning rate is linear and the large clear scale shows only the range in use. The frequency can be set to within one kilocycle. Radiation at any frequency has been reduced to a very low figure. Comprehensive information and full specification available on request to commercial and professional concerns.

RADIO PRODUCTS EDDYSTONE TRADE MARK

Manufactured by **STRATTON & CO. LTD.** BIRMINGHAM 31