FEBRUARY 1955

TWO SHILLINGS

Wireless World

Radio · **Electronics** · **Television**

FORTY-FOURTH YEAR OF PUBLICATION

FEBRUARY, 1955

CELLULAR POLYTHENE

in NEW T/V DOWNLEAD developed by

A low-loss downlead will be necessary in many areas for reception on Band III T/V. Using Cellular Polythene as a dielectric, BICC have developed such a downlead having an attenuation approximately 30% less than the present standard service area type with only a small increase in diameter ... one of the many ways in which BICC research and development engineers have helped to supply the needs of the telecommunication industry.

If this development can assist you—or if you are just interested—please write for further information.

BICC

gives

30%

less attenuation with only small increase in size

BRITISH INSULATED CALLENDER'S CABLES LIMITED 21 BLOOMSBURY STREET, LONDON, W.C.1

A81

Wireless World

RADIO, TELEVISION, ELECTRONICS

Managing Editor : HUGH S. POCOCK, M.I.E.E Editor : H. F. SMITH.

FEBRUARY 1955

In This Issue	Editorial Comment	. 51
	Television Society's Exhibition ,	. 52
	Television Standards Conversion. By H. A. Fairhurst	. 53
	Monte Carlo Television Station. By Charles B. Bovill	. 55
	World of Wireless	. 56
	Introduction to Transistor Electronics-1. By H. K. Milward	1 60
		. 65
		. 66
		. 69
		. 71
	Vector Addition and the Slide Rule. By A. G. London	50
	Flux-Cutting or Flux-Linking? By "Cathode Ray"	
	Measurement of Rise-Time. By E. G. Dann	
	Workshop R-C Bridge. By B. T. Gilling	00
	Books Received	
		. 83
	Lacquer Film Capacitors	. 87
		. 88
	Gramophone and Microphone Pre-Amplifier-2.	
		. 91
		. 94
VOLUME 61 NO. 2	Simple Inductance, Capacitance and Resonance Meter. By L. F. Sinfield	. 95
PRICE: TWO SHILLINGS		. 96
		. 97
FORTY-FOURTH YEAR	Random Radiations. By "Diallist "	. 98
OF PUBLICATION		. 100

 PUBLISHED
 MONTHLY
 (4th
 Tuesday
 of
 preceding
 month)
 by
 ILIFFE
 & SONS
 LTD.,
 Dorset
 House,
 Stamford


 Street,
 London,
 S.E.1.
 Telephone:
 Waterloo
 3833
 (60
 lines).
 Telegrams:
 " Ethaworld,
 Sedist,
 London."
 Annual

 Subscription:
 Home and Overseas, £1
 7s.
 0d.
 U.S.A.
 \$4.50.
 Canada
 \$4.00.
 BRANCH
 OFFICES:
 Birmingham:
 King
 Edward

 House,
 New Street,
 2.
 Coventry:
 8-10.
 Corporation
 Street.
 Glasgow:
 26B,
 Renfield
 Street,
 C.2.
 Manchester:
 260,
 Deansgate,
 3.

WIRELESS WORLD

FEBRUARY, 1955

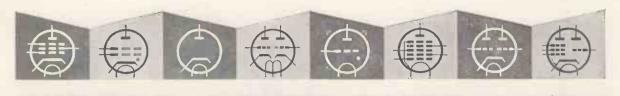

26. Additional Applications of the PCF80

LVES, TUBES E

The Mullard PCF80 was designed primarily as an additive mixer for front end stages in Band I and Band III television receivers and converters in association with the PCC84. This application has been discussed in *Valves*, *Tubes*, and *Circuits* Nos. 15, 16, and 17 (available as reprints with additional notes). The low interelectrode capacitances and short grid base of the valve make it suitable for a number of other applications in which the EF80, ECL80, ECC82, and other valves have hitherto been used.

In television receivers the triode and pentode section of one PCF80 can, with certain limitations, be used to perform separate functions. The performances of the two sections in various audio and video circuits are briefly discussed below. A chart, indicating the permissibility of a large number of combinations of function, will be included in the reprint of this advertisement.

When the triode and pentode of the PCF80 are to be used in different circuits in a television receiver, the advisability of a particular combination is determined by the internal coupling between the sections, especially if the signal levels are widely different, or if the pentode is to be the first valve of a high gain cascade circuit. Use in such a cascade circuit is inadvisable unless the total gain of the stage, or the source impedance, is very low. With a low source impedance, moreover, hum becomes a limiting factor.

The internal coupling has two components: the cross capacitances, and the leakage paths across them. The leakage paths are negligible in all but the most critical combinations of function. The most important capacitive coupling is that between the anode of the triode and the first grid of the pentode. Its maximum value is 0.16pF plus the valveholder capacitance of 0.15 to 0.4pF. The capacitances from the pentode to the triode grid are less than 0.02pF.

The use of the triode in audio applications is restricted by the leakage paths, which will make operation impossible at low audio levels when the pentode is used in a video or timebase circuit. Conversely, the combined effect of the cross capacitances and their shunt resistances prevents the use of the pentode as an audio valve when the triode is used in a video or timebase circuit. The power output of a single triode or even of two in push-pull is insufficient for use in the audio output stage.

With the pentode as a sound or vision i.f. amplifier, the triode may be operated in timebase, video i.f., or audio circuits. It is necessary to minimise hum by effectively earthing the pentode grid or at least by providing the lowest possible impedance to earth. The impedance should not exceed $40k\Omega$ at low frequencies, and it should be still less at higher frequencies. Capacitive decoupling of

the earthy end of the i.f. coil is obtained with 0.1μ F minfor a 50 c/s interfering signal and 0.001μ F min. for 10 kc/s. The most stringent of the combinations in this respect is with the pentode as sound i.f. amplifier and the triode as a timebase or video valve.

CIRCUI

The pentode may be used as a video amplifier in place of the EF80 with a slightly reduced gain but a greater peak-topeak output; or as a synchronising pulse separator with a low screen grid voltage and a high value of anode load to obtain a very short grid base. The triode may be used as a frame pulse clipper or as a conventional frame blocking oscillator. Both sections may be used in a multivibrator circuit to produce a line scanning waveform. A resonant circuit in the triode anode circuit can help to stabilise the natural frequency of the oscillator, if it is locked by a flywheel synchronising system. This can be achieved by returning the control grid of the pentode to a source of controlling bias. In this application no interference is seen if either section of the valve is used for synchronising pulse separation or clipping. But with the pentode in this multivibrator circuit and the triode acting as a frame timebase blocking oscillator, some interaction between line and frame scanning occurs. This combination is not recommended.

In fringe areas, 405-line operation under noisy conditions is considerably improved by flywheel synchronisation. The line timebase coincidence detector which is necessary can incorporate the PCF80 pentode with the two coincident pulses applied to the control and screen grids. The triode can then act as the separate pulse amplifier. In this application the triode or the pentode may be transferred to any of the other scanning applications already discussed without undesirable stray coupling effects.

Circuits for the recommended applications will be published in a future advertisement in this series.



Reprints of this advertisement, with additional notes consisting of a comprehensive application chart, are available without charge from the address below.

MULLARD LTD., Technical Service Department, Century House, Shaftesbury Avenue, W.C.2



FEBRUARY 1955

As She Is Spoke

LVER since wireless telegraphy became practicable, the tongue that Shakespeare spoke has proved short of words for the clear expression of ideas connected with the new method of communication. True, the long-forgotten journalist who wrote, at the turn of the century, about "the message being flashed" was inspired. That phrase, though never quite to the taste of the professional, conveyed to the layman (at least in the days of spark transmitters) a vivid and not inaccurate impression of what really happened. But, after 50 years or more, messages are still being flashed, and the public seems sadly in need of a new phrase.

Of course, it was not until broadcasting came that radio made a big impact on the public at large. We then had an unrivalled opportunity to start off on the right foot. The word "broadcasting" itself was a first-rate example of figurative English, derived in accordance with the best tradition. It is with shame that we admit ignorance of the true paternity of this heaven-sent word. Was it of American origin? Anyway, "broadcasting" was at once adopted by the professional, but, with a queer lack of good taste, the man in the street showed a strange preference for "the wireless" and later for "the radio."

Each new development brought its own inept phraseology. Television was no sooner established than the expression "radio and television" began to trip off the lay tongue (and sometimes, alas, the professional one as well). A nice puzzle it must make for a foreign visitor with a mainly academic knowledge of English, who may reasonably guess that our television is transmitted pneumatically! We were not surprised to see the other day the headline "British Radio and V.H.F." in a lay journal.

The latest innovation in sound reproduction ready-recorded magnetic tapes—might easily become the next victim of our genius for choosing the confusing name. They have been referred to as "prerecorded tapes," which might mean virgin tapes, and "tape recordings," which might mean anything. Fortunately, there is some hope here that a reasonably clear and descriptive name will prevail. E.M.I., the pioneers of these new rivals to disc records, assure us they are to be known as "tape records." The B.B.C. has not, we fear, proved itself a zealous

guardian of the language of its own medium of communication. Some time ago a correspondent drew attention in our columns to the absurdity of that favourite B.B.C. expression "pre-recorded" by enquiring about the meaning of "post-recorded." We believe there is some subtle significance in such variants as "the programme was recorded," "prerecorded" and "from a recording," but nobody seems to know the code. Then there is the most abominable of all B.B.C. words "tele-recording" which seems utterly unnecessary in any imaginable context. Why "tele-," when, in most cases, distance is not an essential factor? Unless the Corporation mends its ways, abominations like "the telly" will soon become respectable and accepted.

Anarchy in the Ether

KECENT newspaper stories about experimental transmissions from the so-called "Europe No. 1" station on the Felsberg make sad reading, and serve to emphasize the chaotic state of congestion on the medium and long-wave broadcasting bands. The station has been transmitting test signals on various frequencies between 238 and 255 kc/s. Naturally enough, as all the channels in that band are already occupied, severe interference has been caused, and protests have been made by the authorities concerned. The Saar has no allocation in the long-wave band, and so it is difficult to see any excuse for these attempts on the part of the station to find a niche for itself.

The Copenhagen Plan is almost a dead letter. For example, under it the two German Republics and Austria are allowed between them 15 medium-wave stations, but have actually 65, plus 37 stations run by the occupying Powers. Clearly, the only solution lies in drastic reduction of the number of medium-wave stations, with supplementary reinforcing services on v.h.f. To evolve a new plan on this basis must be the first task as soon as the international climate is favourable for a conference.

VOL. 61 No. 2

Television Society's Exhibition

N annual event of importance to television enthusiasts, the Television Society's Exhibition, was held this year on January 6th-8th. Marconi's had a camera chain in operation, which provided shots of the exhibition itself, and Belling-Lee arranged the distribution of the signal and also of the B.B.C. programme to exhibitors demonstrating apparatus. Belling-Lee also had a demonstration of the effects of interference suppressors in television reception in Bands I and III. Under the conditions of test a Band I suppressor in the leads to a small motor proved very effective in eliminating interference on Band I, but was quite ineffective on Band III. It was shown that to obtain suppression here a special suppressor had to be mounted inside the motor frame close to the brushes. Dubilier showed inductors and capacitors for suppression, the inductors being miniature dustcore types which it is recommended should be connected in series with the motor field windings close to the brushes.

The effect of the form of modulation upon ignition interference was demonstrated by the G.E.C. A signal with positive or negative modulation was fed, with interference, to a receiver which could be appropriately switched to deal with either type of modulation. The superiority of positive modulation was most evident. Although the black spots of interference with negative modulation were in themselves less evident than the white spots with positive modulation, the synchronizing was so greatly affected that the picture was useless, whereas with positive modulation the synchronizing was hardly affected at all.

Interference is, of course, a matter of major importance in fringe areas, and a scheme which may well reduce it and also permit a useful signal to be obtained in screened locations was shown by J. S. Fielden. This is a three-valve pre-amplifier designed for mounting on an aerial pole and powered by a 50-c/s supply which can be fed to it through the same coaxial cable that is used for the signal. It is intended for use where it is possible to take advantage of neighbouring high ground to erect an effective aerial, perhaps at some distance from the receiver. The repeater 2000/S5 has a bandwidth of 10 Mc/s and can be used with soliddielectric coaxial cable at distances up to 500 yards or with semi-air spaced cable up to 1,000 yards. It operates on Band I. For Band III a convertor unit will be available which will be pre-set to change the frequency of the Band III signal to a Band I channel adjacent to the normal Band I signal, so that the repeater will handle both signals.


Another kind of repeater, intended as a line amplifier for a television relay system, was shown by G.E.C. The interesting thing about this was the use of transistors instead of valves. The advantages of transistors for this type of application are, of course, their small size, robustness and need for only one supply of low-voltage power. The amplifier actually uses experimental point types, and it works at a centre frequency of 5 Mc/s with a bandwidth of 3 Mc/s. A gain of 32 db is obtained and the frequency response is flat to within ± 0.5 db over the 3-Mc/s band.

Test apparatus naturally formed a large section of

the exhibition, and of particular interest was the equipment developed by Bush Radio for the testing and alignment of television sets in production. The heart of the instrument is a swept-frequency oscillator covering about 33–39 Mc/s for i.f. alignment using a cathode-ray display. Spot frequencies are also available for sound-channel rejector adjustment and checking.

The i.f. sweep can be heterodyned to the video range and the resulting video sweep used to modulate r.f. carriers in Bands I and III. Complete television signals, both sound and vision, are provided on three channels in each band, and the vision signal is modulated in alternate "lines" by the video sweep and by a $5-\mu$ sec pulse. The receiver output is displayed on a double time-base tube to show the overall video response and the pulse response. Final alignment and adjustment can then be carried out in an overall test. The outputs are "piped" around the factory to the test positions.

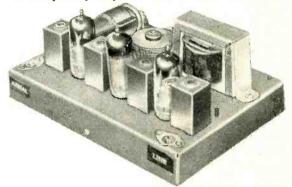A swept-frequency oscillator of the serviceman's



Television pre-amplifier by J. S. Fielden; for a remote aerial.



Band III convertor (below) for the type 1320 Cossor Telecheck swept-frequency oscillator (above).

type was shown by Cossor. This is the 1322 Telecheck which covers Bands I and III and gives a 10-Mc/s sweep on its fundamental and proportionally more on its harmonics. The fundamental range is 10-22 Mc/s. A crystal-controlled marker generator is included. A Band III convertor, model 1321, for the older 1320 Telecheck, which covered Band I only, was shown. It is arranged to screw on to the 1320 instrument.

Amongst an interesting selection of American test gear shown by Livingston Laboratories was an oscilloscope designed for maintenance and adjustment of television transmitter and studio equipment—the Tektronix type 524-D. It can be used for observing the waveforms of complete television frames or single lines or portions of lines. The Y amplifier has a maximum frequency of 10 Mc/s and is flat to 5 Mc/s, while the timebase rate is continuously variable from 0.01 sec per centimetre to 0.1 μ sec per centimetre. Special features include variable sweep delay, sweep expansion (for magnifying detail), an amplitude calibrator and time markers at intervals of 1 μ sec, 0.1 μ sec and 0.05 μ sec.


Radio-Aids showed a small three-stage i.f. amplifier feeding a crystal detector and microammeter. It is available pre-tuned to any Band I channel and calibrated to measure signal inputs up to 1 mV. It is intended for use in aerial and feeder testing and, with a known aerial, for determining the field strength so that a dealer may decide beforehand what sort of aerial it will be necessary to erect.

Apparatus for the measurement of oscillator drift on Band III was shown by Ferguson. A crystal-controlled signal is fed into the receiver under test and the i.f. output is mixed with another crystal-controlled oscillator. The initial adjustment is to zero beat. Oscillator drift then causes the beat frequency to rise and this is recorded by a Servograph.

Printed-circuit technique is developing rapidly and T.C.C. showed many examples. One of considerable importance for the future was the basis of a Band III tuner and well showed the advantage of the technique in securing uniformity of lead length in production. Another example was an aerial filter, intended for receivers using a 34.65 Mc/s i.f., to prevent i.f. break-through. With the circuit of Fig. 1, the coils and capacitors are all printed. The insertion loss is 2 db and at all frequencies below about 41 Mc/s the insertion loss is never less than 20 db and reaches a maximum of 34 db at 38 Mc/s.

There was very little evidence of work on colour television except in the field of cathode-ray tubes. 20th Century Electronics had modified one of their four-gun oscilloscope tubes so that the screen was divided into four quarters, one having an ordinary white phosphor and the others having red, green and blue phosphors respectively. The four electron guns were arranged in a corresponding pattern, with one directed on each phosphor, so that it was possible to display white, red, green and blue television pictures simultaneously. Each gun had its own electrostatic deflection plates and these were fed from the common scanning generators through blocking capacitors so that individual shift voltages could be applied. It was also possible to control the brightness and contrast of each picture separately.

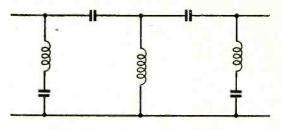On the Mullard stand were some 14-inch experimental c.r. tubes with coloured phosphors, intended for use in colour-picture monitors of the type in which the three coloured images are combined optically by dichroic or half-silvered mirrors. The tubes, which



T.C.C. printed "i.f. breakthrough" filter.

are electrically identical and operate with 12 kV on the final anode, are the types 36CDD12-3, -4 and -5, having blue, green and red phosphors respectively. Another new experimental tube shown by Mullard was the 4MK13 flying-spot scanner, intended for use at the transmitting end for scanning coloured slides and films. To obtain the necessary high level of brightness the anode of the triode gun operates at 25 kV, while the 5-inch screen is claimed to give a substantially panchromatic light output.

Various colour phosphors were demonstrated in Ferranti cathode-ray tubes by the chemical manufacturers Derby & Co., and here the difficulty of producing a good red-emitting phosphor was very evident. Most of the colour television demonstrations so far have, in fact, given rather poor colour rendering in this particular component.

TELEVISION STANDARDS CONVERSION

Possibility of Direct Electronic Method

By H. A. FAIRHURST*

DTANDARDS conversion in television is by no means new, but it is probably not common knowledge that there is a possible alternative to the "brute force" method (of a camera viewing a c.r.t. monitor) used during the "Eurovision" programme exchanges. Whether this alternative could be developed into a system capable of giving acceptable results is not known, but it has a sound theoretical basis and has been proved to work on the bench.

The fundamental principle of the alternative system is that selected lines of picture information at the higher definition are stretched in time until each occupies the line duration of the lower definition system. This is performed by feeding the selected picture line into a delay line of sufficient delay to accommodate the whole slice of information at once, and then switching the characteristics of the delay line while the information is still all inside the line so that when it does emerge it does so at the new desired rate.

Because the higher definition lines occur at a greater rate than those at the lower definition, some of them must be sacrificed, but from the point of view of the lower definition user he will not miss what he has never had, and as the system is theoretically capable

* Murphy Radio.

of giving full horizontal definition his picture should be fully up to standard.

The system works in its simplest form if certain fixed relationships are preserved between the two standards. For example, it is assumed that the frame frequency is the same in the two cases. It is also assumed that the line frequencies are related in some simple manner—2:1, 3:2, 5:3, etc. This can be argued to be a definite disadvantage of the system, for these particular ratios, assuming 405 lines to be the lower definition standard, call for 405 lines, 50 frames, sequentially scanned, $607\frac{1}{2}$ lines interlaced, and 675 lines interlaced, respectively, in the corresponding higher definition systems.

A 405-line non-interlaced system is a case by itself and will not be further considered here, while $607\frac{1}{2}$ and 675-line systems do not appear anywhere as accepted standards. However, of these three, it can be shown that only the 675-line system is an acceptable higher definition to be linked by electronic standards conversion to 405 lines, and this because of the desirability of preserving the interlaced scan.

For the purposes of illustration, the 675-405 line case is shown in Fig. 1, which indicates the sequence of lines chosen from the higher definition (numbered) to make the consecutive lines at the lower definition (broken lines). Three delay lines are required to handle the information without overlap, and the form and timing of the delay line switching pulses are shown. Owing to the need to use three only out of every five high-definition lines, and to the consecutive nature of the lower definition lines, there will be a regular

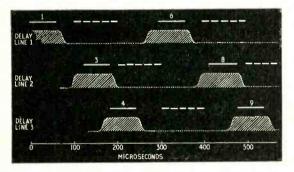


Fig. 1. Showing how the high-definition lines (numbered) are selected and distributed in sequence to the three delay lines, where they are stretched in time to produce the lower-definition lines (broken lines) which follow continuously upon each other. The waveform of the delay-changing current is shown for each delay line.

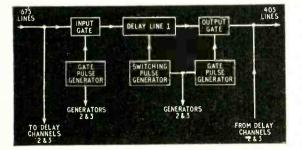


Fig. 2. Simplified block diagram of one of the delay channels. The input gating generators are controlled by the 675-line sync pulses and the output gates from a 5 : 3 count-down circuit operated by these pulses.

slight deformation of the picture in a vertical direction, but this can be shown to be a fixed pattern and normally invisible.

As three delay lines are required to handle the conversion, it is necessary to provide switching and gating circuits to switch the desired picture lines into the correct sections and also to sample the three outputs in turn so as to combine them into the lower definition signal. At the same time means must be provided for switching the constants of the delay lines at the correct times and for the correct durations. Fig. 2 is a simplified block diagram of one of the delay channels.

What of the delay lines themselves? The criterion here is that their constants must be capable of being switched to change the velocity of propagation through them. This could be done by winding the elements of the line on closed ferrite cores which can be saturated magnetically by current flowing through an additional winding. One arrangement successfully tried was to wind each element of the delay line as a toroid on a small ferrite ring and then to string them all on to a copper rod through which was passed the saturating current. Such a coil wound on a grade of ferrite suitable for the frequencies involved has its inductance reduced to nearly one-sixth when the core is saturated, so the smaller change required for the conversion process is easily obtained with quite practicable saturating currents.

Further removed, perhaps, from the bounds of possibility is the number of elements required in each line to obtain the requisite delay. It will obviously be a large number, and will depend a lot on the phase characteristic that can be maintained, but if a cut-off frequency of 20 Mc/s be assumed, with the values of $L=25\mu$ H and $C=10 \,\text{pF}$ the number works out to be over 6,000. This would present a pretty problem for the designer, but it is no doubt not insoluble.

Fig. 2 is very much simplified and gives little hint of the complexity of circuitry which may be involved. It does not indicate, for example, that means must be provided for obtaining an exact timing of the outcoming information and for matching the outputs of the three delay lines. Fortunately the time intervals allow the saturating current pulse to be shifted a few microseconds either way, and this facility could provide a micrometer adjustment on the time the information spends in the line and, therefore, of the instant it begins to emerge. Control of the duration of the outcoming line of information can be achieved by varying the actual amplitude of the saturating current pulse. In this connection it must be noted that the saturating current must have a d.c. component in order to prevent any tendency to saturate the cores in both directions.

Bench experiments with short sections of line have demonstrated the stretching of a pulse and also the various other effects that would be expected on theoretical grounds when the constants of a line carrying a signal are switched. These experiments have shown that to develop such a standards convertor would be a major undertaking, but they have not shown it to be impracticable.

A system of conversion such as this offers one kind of solution to the problem of compatibility in colour television. It would make possible, for example, the transmission on 405 lines of monochrome versions of colour pictures which were being put out on some higher definition system—or, indeed, the transmission of coloured 405-line versions of these higher definition colour pictures. Estimated polar diagram for the transmitter when it is on full power. The datted line shaws the present estimated coverage.

CHARLES B. BOVILL A.M.I.E.E., M.Brit.L.R.E.

By

DIGNE St. SAUVEUR **AVIGNON** IMPERIA, FORCALQUIER ENTON SAN REMO CASTELLANE SALON CANNES Monte Carlo DRAGUIGNAN ANTIBES FREJUS AUBAGNE ARSEIL MILIES 10 20 30 40 TOULON LA SEYNE ILES D'HYERES

MONTE CARLO TELEVISION STATION

W ITH several different standards being used for television in Europe, it was inevitable that eventually the problem of a transmitter located on a "standards frontier" should arise, and it is therefore of interest to examine what has been done in the case of the Monte Carlo television station which was recently put into service.

This station, which is the second commercial television station to be opened in Europe (the other is in the Saar), is situated on Mont Agel, a 3,500-ft mountain overlooking the Principality of Monaco and only some 10 miles from the Franco-Italian frontier.

Since the station is sponsored commercially, and the sponsors are French and handling the publicity for French merchandise, the role of the station is to serve the thickly populated area lying between Menton to the east and Toulon and Marseille to the south west. As Italian television standards differ from the French 819-line system the transmissions would not normally be receivable in Italy. Special receivers will soon be available for this area, however, so that programmes intended for Italian viewers will also be possible.

The design of the station therefore called for the maximum cover towards the south east, and adequate cover for the Principality and French towns extending to the Italian frontier. It will also be appreciated that there is no requirement for any cover over the sea over an arc of about 150 degrees to the south east and south west, nor for cover over the almost uninhabited Alpine region to the north.

The rather special cover requirements have enabled the designers and manufacturers of the station, the Société Radio Industrie, to construct a most economical and effective installation by the use of directional high-gain aerials. The aerials, which are of batwing type, provide a main lobe with a horizontal width of about 45 degrees which provides the main Riviera cover towards Nice, Cannes and Toulon. Very small secondary or side lobes—usually a serious problem to eliminate in directional aerial design—provide, with slight modification to the aerial array, the necessary cover for the nearby towns towards Italy. The aerial

WIRELESS WORLD, FEBRUARY 1955

arrangement incorporates radiators for video and for sound, each having a power gain of about 10, the effective radiation on the video frequency of 199.7 Mc/s being 50 kW and on sound 12.5 kW at a frequency of 188.55 Mc/s. The polarization is horizontal for both video and sound and the French 819-line standard is used, requiring of the aerials a bandwidth in excess of 10 Mc/s. The standard arrangement for France of single sideband transmission is retained.

Next year the power will be increased and the coverage improved as a result.

Preliminary reports of reception indicate very satisfactory results, with clear and steady pictures at St. Tropez, 50 miles from the transmitter. Since the signal travels partly over water to some of the towns to be served by the main lobe, this result is probably to be expected, but it is also reported that good reception is obtained at inland towns such as Draguignan, at which position the signal path is over soil which is notorious for its poor conductivity.

The studios from which the programmes originate are situated in the town of Monte Carlo some 3,000ft below and two miles from the transmitter aerials. In order to avoid the use of buried coaxial cables and their attendant expense for installation and maintenance, and in order to avoid phase distortion in the cables, a duplicated 4-cm radio link conveys the modulations to the transmitters.

The sponsors of the Monte Carlo television station are the "Images and Sound" group, which also operates the Saar television station and which will shortly put into service the extra high-power sound broadcast station for sponsored programmes at Felsberg.

The commercial programme policy of this group is original and differs from that practised in the U.S.A. in several respects. As an example, the group themselves arrange and compose the programmes which are acquired by the publicity organization and the advertising matter is integrated into the programme in a restrained way. Also, the publicity is restricted to one minute every quarter of an hour.

WORLD OF WIRELESS

Colour Prospects + Anglo-French TV Link +

B.B.C. Band II Frequencies + Another "Festival of Sound"

Television News

RECENT pronouncements on the possibilities of the introduction of colour television by the B.B.C. within the next two years have been clarified by E. L. E. Pawley (head of Engineering Services). He points out that the decision has yet to be made by the Government (with the advice of the T.A.C.) whether or not we are to have a compatible system. The B.B.C. Research Station is in fact experimenting with the American N.T.S.C. compatible system adapted to our 405 lines with a 5 Mc/s bandwidth, but is also working on a non-compatible system. This would require a greater bandwidth and, therefore, could not be accommodated in the present channels in Bands I and III. Sir George Barnes, B.B.C. director of television, thinks a decision may be reached by the end of the year. As part of the permanent cross-channel television link

As part of the permanent cross-channel television link to be established by the Post Office a two-way cable link between London and St. Margarets Bay is to be rented permanently by the B.B.C. Presumably the Post Office will be able to provide similar facilities for the I.T.A. should they be required. Until the permanent stations for the cross-channel link are set up in about three years' time the cable will be extended from St. Margarets Bay to Swingate, near Dover (a distance of about two miles), where the B.B.C.'s temporary radio link with Cassel is installed.

Test transmissions from the temporary low-power television transmitter at Tacolneston, 10 miles south west of Norwich, started on January 17th. It is planned to bring the station into regular service on February 1st. Operating in Channel 3 (carriers 56.75 Mc/s vision and 53.25 Mc/s sound, slightly offset) with horizontal polarization, the temporary station will serve an area bounded by Aylsham, East Dereham, Watton, Diss, Beccles and Acle. Vision signals from Alexandra Palace will be picked up near Bury St. Edmunds and relayed by radio to the transmitter site. Sound will be conveyed from Alexandra Palace by line.

For testing Band III aerials and receivers under practical conditions a test-pattern vision signal is to be radiated from a temporary 1-kW transmitter near the site of the I.T.A. South London station. The transmissions, which are due to start on April 1st, are to be conducted by Belling & Lee.

Baird Memorial

AN appeal for funds for a Baird memorial has been launched by the Royal Technical College, Glasgow, where Baird was a student from 1906 to 1910. It is proposed by the governors of the college to establish an annual memorial lecture on developments in television and related fields and to provide a Baird prize in the Department of Electrical Engineering. Donations to the Baird Memorial Fund should be sent to the Secretary/Treasurer, Royal Technical College, George Street, Glasgow, C.1.

V.H.F. Broadcasting

WITH the announcement of the P.M.G.'s approval of an additional v.h.f. station at Wenvoe-making 10 so far approved by the Government—the B.B.C. has made known the frequencies to be used by the 30 transmitters at these stations. The frequencies, together with the e.r.p. for each transmitter, are given in the table below. Incidentally, with the exception of those for Holme Moss and Blaen Plwy, the frequencies conform to the plan for Band II drawn up at Stockholm in 1952. The frequencies given for Wenvoe, however, have yet to be confirmed by the Post Office.

	Home (Mc/s)	Light (Mc/s)	Third (Mc/s)	E.R.P. (kW)
Wrotham (Kent) Pontop Pike (Co.	93.5	89.1	91.3	120
Durham)	92.9	88.5	90.7	60
Divis (N. Ireland) Meldrum (Aber-	9 <mark>4.</mark> 5	90.1	92.3	60
deenshire) N. Hessary Tor (S.	9 <mark>3.</mark> 1	88.7	90.9	60
Devon) Sutton Coldfield	92.5	88.1	90.3	60
(Warwicks.)	92.7	88.3	90.5	120
Norwich Blaen Plwy (Cardi-	94.1	89.7	91.9	120
gan.) Holme Moss	93.1	88.7	90.9	60
(Yorks.)	93.7	89.3	91.5	120
Wenvoe (Glam.)	94.3	89.9	92.1	120

When announcing the inclusion of Wenvoe in the first batch of v.h.f. stations, scheduled to be completed by the end of 1956, the P.M.G. stated that the Television Advisory Committee had recommended the adoption of the B.B.C.'s long-term plans for v.h.f. development. We understand that these provide for a total of 26 stations, at most of which there will be three transmitters or even a fourth where a station serves two regions.

Repeat Performance

AS announced in December, G. A. Briggs, of Wharfedale Wireless, is giving another lecture-demonstration on sound reproduction at the Royal Festival Hall, London, on May 21st. Tickets are priced 5s 6d and 3s 6d. Within a few days of the announcement of prices, all the tickets for the cheaper seats were sold, but as we go to press there are still some 5s 6d tickets available from "hi-fi" dealers in London.

Mr. Briggs is also giving a similar demonstration in St. George's Hall, Bradford, on April 1st, at 7.30. Tickets at 3s 6d and 2s are available from J. Wood & Sons, Sunbridge Road, Bradford.

Valve "Balance of Trade"

WHILE the exports of valves and c.r. tubes continue to decrease imports of these accessories have increased by over 100 per cent during the past year.

Exports of valves during the first eleven months of 1954 (the latest analysed figures available) totalled £1,743,692, and cathode-ray tubes £122,729, whereas the comparative figures for 1953 were £1,867,079 and £147,590. The actual numbers of valves and cathode-ray tubes exported were 4,447,548 compared with 4,643,005 in 1953.

Figures for the first eleven months of 1954 compared with the same period in 1953 show an increase of 131 per cent in the number of valves imported and 66 per cent in the number of c.r. tubes coming into the country. The total value of these imports was £3,075,419 compared with £1,679,352 the previous year.

"Wireless World" Index

THE index to the material published in Wireless World during 1954 is now available from our Publishers, price 1s (postage 2d). It includes both general and classified indexes. Cloth binding cases are also obtainable with index, price 6s 5d by post. The binding of readers' own issues can be undertaken by our Publishers, the cost, including binding case and index, being 17s 6d plus 1s 4d postage on the bound volume.

NEW YEAR HONOURS

Among those receiving decorations in the New Year Honours List are:--

C.M.G.

R. C. McCall, assistant director of television, B.B.C. **O**.B.E.

J. Clarricoats, general scretary, Radio Society of Great Britain. (See "Personalities.")
V. M. Roberts, manager, electronic sales department, B.T-H. (See "Personalities.")

M.B.E.

S. W. Brown, chief radio officer (I.M.R.C.) of s.s. Scythia.

D. Fairweather, chief of crystal production, Marconi's W.T. Company.

H. L. Peddle, signals officer, telecommunications depart-

ment, Ministry of Transport and Civil Aviation. J. Sarche, chief inspector, Ultra Electric, Ltd. (See "Personalities.")

B.E.M.

R. Carter, laboratory mechanic, Royal Navy Signal School.

. W. Jacobs, chargehand (mechanic), Radar Research Establishment, M.o.S.



J. CLARRICOATS, O.B.E.

V. M. ROBERTS, O.B.E.

PERSONALITIES

B. G. H. Rowley, M.A.(Oxon), A.M.I.E.E., Marconi's technical representative in the U.S.A. and Canada since 1950, has been appointed manager of Marconi's Maritime Division in succession to **G. R. Tyler**, who, although having reached retiring age, is continuing with the company as its representative in West Africa. Mr. Rowley was concerned with the development of marine radar at R.N. Signal School at the beginning of the war and was subsequently appointed to the staff of the British Admiralty delegation in Washington. From the end of the war until joining Marconi's he was staff radar officer (Lt. Cdr.) with the Joint Services Mission in America.

Dr. W. J. Thomas, Ph.D., B.Sc., A.M.Brit.I.R.E., has left the Norwood Technical College where he has been since 1947—for the last four years as principal. He has been appointed one of H.M. Inspectors of Schools, the major part of his work being concerned with technical colleges in South Wales. It was largely due to his interest that the Television Society's experimental transmitter was installed in the college, which also houses the of the war Dr. Thomas was education officer at the R.A.F. Radio School, Cranfield, and from 1942 until the end of the war was senior instructor at the Army Radio School, Petersham, Surrey.

John Clarricoats, G6CL, the well-known general secretary of the Radio Society of Great Britain, who is appointed an O.B.E. in the New Year Honours, recently completed 25 years' service with the society. In addition to receiving a gift from the members, mentioned last month he uses also survided the RSC R. Colours Kow month, he was also awarded the R.S.G.B. Calcutta Key "in recognition of his outstanding service to the cause of international friendship through the medium of amateur radio."

Vernon M. Roberts, B.Sc., A.M.I.E.E., appointed an O.B.E. in the New Year Honours, has been with B.T-H. since 1924, when on graduating at the University of Wales he started a three-year student apprenticeship. During the war he was concerned with the development and production of radar equipment. He is now manager of the company's electronic sales department and a director of Multi-Broadcast (Engineering), Ltd. Mr. Roberts has for some years represented B.T-H. on the Radio Communication and Electronic Engineering Association, of which he was chairman in 1950.

J. J. Sarche, who has been appointed an M.B.E., has been with Ultra Electric, Ltd., for 33 years. He is now chief inspector at the company's Western Avenue factory, having previously been assistant chief engineer.

F. E. Debenham, the new manager of the Service Department of Mullard's Valve Division, at Waddon, Surrey, has been with the Mullard group of companies since 1929. For some years during the war he was production manager at the Mullard valve factory at Black-burn. He succeeds E. B. Rogers, who has retired after 28 years with the Service Department.



J. J. SARCHE, M.B.E.



F. E. DEBENHAM

WIRELESS WORLD, FEBRUARY 1955

David L. Davies, B.Sc., Grad.I.E.E., has been appointed chief electronics engineer of Winston Electronics, Ltd., of Hampton Hill, Middlesex. Graduating at University College, Swansea, in 1948, he joined the staff of the Eng.neering Department of Edinburgh University, where he was lecturer in electrical engineering for three years. Immediately prior to joining Winston Electronics last January, at the age of 26, he had been working on guided missiles with English Electric.

E. J. Gargini, author of the article "Piped Scanning Waveforms" in this issue, received his technical training at Southall Technical College. After a short period as a trainee at the E.M.I. and Philco organizations he served in the R.A.F. during the war. He rejoined the E.M.I. Group in 1945, where he has been concerned in the design of cinema sound equipment, multi-channel radiofrequency relay systems, and wired television distribution equipment. He has been recently seconded to the research organization to work on domestic colour television.

Arthur W. Wayne, who describes a simple wave-shaper elsewhere in this issue, is both a professional engineer and a professional musician, a combination which he finds invaluable as a designer of sound-reproducing equipment. He has been a consultant dealing chiefly with acoustics for some years and last year formed Shirley Laboratories, Ltd., of Worthing, for the manufacture of amplifiers, tuners and electronic instruments.

IN BRIEF

The annual I.E.E. Faraday Lecture, which is "designed to appeal to the layman," is this year being given by T. B. D. Terroni, B.Sc., manager and chief engineer of the Transmission Division of the Automatic Telephone and Electric Company. His subject is "Courier to Carrier in Communications." The lecture will be delivered at the Central Hall, Westminster, on January 27th, at 6.0. Tickets must be obtained from the I.E.E., Savoy Place, London, W.C.2.

The demand for admission to the laboratory course in **Pulse Techniques** to be held at the Borough Polytechnic, Borough Road, London, S.E.I, on twelve Wednesday evenings, beginning on February 23rd, has been so great that it is to be repeated. It will be given on Monday afternoons from April 18th and again on Wednesday evenings from April 20th. The fee is 2 guineas.

A Spanish Edition of Scroggie's "Foundations of Wireless" has been published with the title "Fundamentos de Radioelectricidad." It has been produced by Editorial Alhambra, S.A., of Madrid, and costs 195 pesetas.

North America's third distant early warning (DEW) radar chain will be within the Arctic Circle. The first, now almost complete, runs across southern Canada, and the second is on the 55th parallel.


Soviet Colour Television.—Experimental transmissions of field-sequential colour television have recently been radiated from the Moscow television centre. An additional mast has been erected at the centre and a specially equipped studio is to be provided.

CLUB NEWS

Birmingham.—At the meeting of the Slade Radio Society on February 18th at 7.45 at the Church House, High Street, Erdington, R. Rew (G3HAZ) will give a lecture demonstration on "Equipment for Seventy Centimetres."

Cleckheaton.—Two Wireless World contributors will be giving lectures to the Spen Valley and District Radio and Television Society in February. On the 9th at the Temperance Hall, Cleckheaton, Dr. K. A. Exley will speak on audio reproduction, and on the 22nd at the Bradford Technical College, Dr. G. N. Patchett will deal with transistors. Both meetings begin at 7.30.

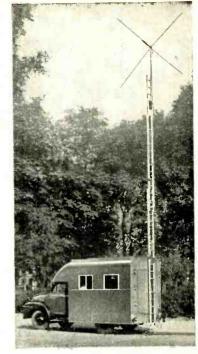MOBILE v.h.f. test unit, with aerial mounted on a 40-ft extensible ladder, has been brought into service by Philips for field - strength measurements. Interchangeable aerials are carried and these are electrically rotated.



N e w a r k.— "Transistor Circuitry" is the subject of the talk to be given by C. L. Wright

(G3CCA) to the Newark and District Amateur Radio Society at 7.0 on February 6th at the Northern Hotel, Newark.

Windsor.—In response to requests from past and present students of the East Berkshire College, a radio society has recently been formed and meets on Thursdays at 7.0 at the Royal Albert Institute, Windsor. Details of the facilities provided by the club, which has its own transmitter, G3KAL, are obtainable from F. H. Rickards, East Berks College, Royal Albert Institute, Windsor.

Leicester.—A member of the Leicester Radio Society will speak on power supplies at the meeting on February 14th. A fortnight later the chairman will deal with griddip oscillators; their construction and application to amateur radio. Meetings are held at 7.30 at the Club Room, Holly Bush Hotel, Belgrave Gate, Leicester.

BUSINESS NOTES

Baird-Ambassador Merger.—Hartley Baird, Ltd. (formerly Baird Television), of 37, Thurloe Street, South Kensington, London, S.W.7, manufacturers of television receivers and tape recorders, has acquired Ambassador Radio, the well-known manufacturers of domestic radio and television sets. R. N. Fitton, managing director of Ambassador, has joined the board of Hartley Baird as director in charge of radio and television. Ambassador will continue to operate as a separate company.

A contract has been awarded to Nash and Thompson, Ltd., Tolworth, Surrey, for the electrical, physical and mechanical testing of electronic components, excluding valves, to the requirements and under the direction of the Radio Components Standardization Committee. Claimed to be the first of its kind to be granted to a commercial undertaking it supplements the testing and proving of newly designed equipment carried out by the Government rescarch establishments.

The "Martinet" automatic steering device for small craft developed by Hartley Electromotives, Ltd., will be produced at their Shrewsbury factory, but the Marconi Marine Company will be the sole concessionaires. The device was shown for the first time on the joint Marconi-Hartley stand at the recent National Boat Show at Olympia. The name of Blick Engineering, Ltd., of Bedesway, Bede Trading Estate, Jarrow, Co. Durham, has been changed to Blickvac Engineering, Ltd. The company, which manufactures high-vacuum impregnators, potting resin impregnating and casting plant and other highvacuum equipment, has a London technical representative at the offices of the associated company, Blick Time Recorders, Ltd., 96-100, Aldersgate Street, London, E.C.1 (Tel. Monarch 6256).

A new prefabricated factory building is being erected at Shepperton for **Winston Electronics**, Ltd., who develop and manufacture electronic equipment for the Services, for many diverse branches of industry and for telecommunications.

The London sales office of **Pye Marine**, Ltd. (formerly Rees Mace Marine) at 11, Hinde Street, W.1, is now closed and the London area sales and service headquarters are at Galleons Works, Yabsley Street, E.14 (Tel. East 4216). The office of R. I. T. Falkner, the sales director, is now 157, Regent Street, London, W.1 (Tel. Regent 2712).

Excel Sound Services, manufacturers of the Celsonic tape recorder, were given the task of recording the Brad-ford Festival Choral Society's recent concert and from the tape produced discs of the programme highlights for members of the society.

Two British aircraft manufacturers—de Havilland and Bristol—are now using miniature Pye Industrial TV cameras for research purposes. In one case the equipment is being used to detect the presence of flame in a new engine being tried out in the bomb bay of a test aircraft. The camera is focused on to the engine (which is in complete darkness) through a heat-resistant glass panel. While the monitor on the pilot's dashboard is blank he knows that all is well.

The reconstructed premises of the G.E.C. in Wellington Street, Leeds, destroyed by fire two years ago, were reopened in December.

FOREIGN TRADE

Each of the 40 Vickers-Armstrong Viscount aircraft ordered by Capital Airlines (U.S.A.) is to be fitted with Marconi automatic direction finders. The standard Marconi radio compass has been modified for operation in North America.

U.S. Import Tariff.—A three-fold increase in the import tariff on radio and electronic equipment is called for by the American Radio-Electronic-Television Manufacturers' Association. The duty was reduced from 35 per cent to 12.5 per cent in 1951. The R.E.T.M.A. states in a report quoted by the *Financial Times* that imports from the U.K. in the first eight months of last year totalled \$607,000, compared with \$463,000 for the whole of 1953. During the same periods imports from Germany were \$295,000 and \$109,000, respectively.

S.T.C. and Marconi's have jointly been awarded a contract for supplying radio-telephony and telegraphy equipment for a new external telecommunications station being built in Addis Ababa, Ethiopia. S.T.C.'s share of the contract includes two 4-kW transmitters; telephone terminal equipment providing two simultaneous telephone channels and voice-frequency telegraph equipment providing two telegraph channels. Marconi's will be responsible for the receiving equipment and aerial installations.

The Near East Arab Broadcasting Station at Limassol, Cyprus, from which commercial programmes are broadcast to the Arabic speaking countries, is being equipped with a 100-kW medium-wave transmitter and a 20-kW short-wave transmitter by Marconi's. Twin 350-foot directional mast radiators have been erected by **B.I. Callenders.** The station operates on 635 kc/s and in the 25, 31 and 49 metre bands.

WIRELESS WORLD, FEBRUARY 1955

PUBLICATION DATE

As already announced Wireless World now appears on the fourth Tuesday of the month preceding that for which it is dated. The March issue will, therefore, be published on February 22nd


.

Radel, Ltd., of Strand Road, Ashar, Basrah, are interested in acting as Iraq Agents for British radio and electronic equipment and are also seeking tenders for the supply of 500 domestic receivers. They require wired chassis with accessories but with a "prefabricated cabinet to be assembled on site." The universal 5-valve receiver must cover two short- and one medium-wave band, operate on 230 V and have Arabic characters on the tuning scale. Interested manufacturers should communicate in the first place with the company's British representative, L. C. Jenkins, 460, Wilbraham Road, Manchester, 21 (Tel. Chorlton 1801).

Cossor's have supplied four medium-power communications installations (No. 53) to the ruler of Kuwait, Persian Gulf. The equipment, which can be operated as a mobile or fixed station, has facilities for c.w., m.c.w. and R/T, and can be remotely controlled.

MERCHANT SHIPPING R/T

UNDER the Merchant Shipping (Radio) Rules, 1952, it is compulsory for all vessels between 500 and 1,600 tons (which class includes small coasters, tramps, tugs and large fishing craft) to carry radio-telephone equipment. These rules came into force on November 19th last year, and the first transmitter-receiver to be granted the G.P.O./M.o.T. Certificate of Approval as meeting the specification laid down in the rules is the Pye Marine "Swordfish." The 50-watt transmitter is crystalcontrolled on eight spot frequencies (between 1,600 and 3,900 kc/s) which are switch selected. The receiver

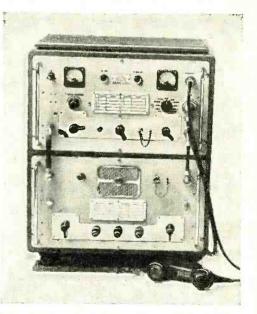

oscillator is also crystal-controlled, and in addition to covering the same frequency range as the transmitter the set provides for reception on 200 kc/s (Droitwich). The combined set measures 24m high \times 20in wide \times 10in deep.

INTRODUCTION

TO

Transistor

I-Physical Basis of Conduction in Semi-Conductors

HE object of this article is to give the reader as clear a working picture of transistor electronics as he has about valve electronics. It is inevitable that such a working picture should be incomplete: in these days theories which deal with all the known facts-where they exist at all-can be expressed only with the aid of mathematics. What is needed, therefore, is a theory which expresses clearly and accurately facts of interest to the engineer rather than those which are needed by the research physicist.

This article is concerned mainly with what happens within the crystal itself and not with transistor circuits. The theory of conduction in semi-conductors (the class in which the germanium crystal falls) is discussed first. This requires an explanation of the structure of these crystals and of the effects due to the presence of certain impurities. These impurities are essential to the production not only of the transistor action but also of the rectifying effects which make the germanium diode possible.

Conduction in Semi-Conductors .- The name semiconductor applies to a group of elements of crystalline structure, which conduct electricity poorly in general, but which may, in association with discontinuities in the material, have different conductivity for currents flowing in opposite directions. The atoms of the group with which we are concerned have four valency bonds and four electrons in their outer orbits. Carbon and silicon are the commonest of these elements; germanium is rather less abundant. Until recently, in fact, germanium was a rather rare chemical curiosity of little importance, which formed a small proportion of the flue dust which collects in chimneys.

Germanium and silicon form symmetrical crystals, the atomic structure of which is represented in Fig. 1. All the valency bonds are used in forming the structure, each bond being an electron pair. In this perfect crystalline structure there are no free electrons and conduction in the ordinary sense, such as in a metal, by free circulation of electrons, is not A crystal of this nature does, however, possible. conduct some current, and for both germanium and silicon, this current is affected by light falling on the crystal and also by its temperature.

Fig. 2 shows a diagram of the four-valency structure, suitably flattened to two dimensions for simplified illustration. All the valency bonds are satisfied and all nuclear charges neutralized. As it stands there is no form of "carrier" for any electric current. But both thermal energy due to temperature and the radiant energy of light (and higher-frequency radiations) disturb this quiescent state. Either may be imagined to shake the structure; and under certain conditions one of the valency electrons may fly off. This, as seen in Fig. 3, leaves an incomplete bond -a resultant positive charge-which is called a "hole."

It is not difficult to see that a number of electrons so shaken off may become an electrical current if a potential difference exists across the crystal; but it is not so easy to picture holes as being very nearly as effective carriers of electric charges. Surprising as it may seem, a hole has very much the same order of mobility as an electron, though it appears to move in the opposite direction. An explanation of the When subject to an process is simple enough. electric field the stress on a neighbouring valency electron causes it to "jump" into the hole, leaving another hole where it came from; this causes the next one to do likewise, and so on. The hole appears then


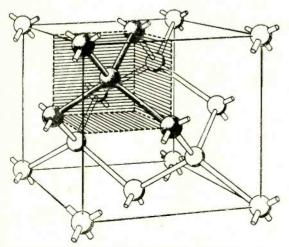


Fig. 1. Atomic structure of a germanium crystal.

Fig. 2. (Right) Representation of valency bonds in silicon or germanium.

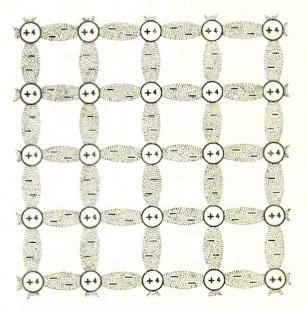

WIRELESS WORLD, FEBRUARY 1955

Electronics

to move from the positive end to the negative. What is most surprising is not that this happens but that it happens so quickly.

One might imagine that electrons moving this way and holes moving that way would frequently "collide" and neutralize cach other. While this happens to some extent it does so in a well-regulated and orderly fashion. Experiments have shown that in general hole-and-electron pairs are generated (and may recombine) only at specific points in the crystalline structure. Irregularities in the crystal structure are an example of such points, though the exact condition necessary for the formation of a generation-and-recombination centre are as yet by no means completely investigated. There would be little point in discussing the present theory here, for it is possible to get a fairly accurate action picture of the transistor from what has been found by experiment. The theory leads straight into quantum mechanics and to realms where simple analogies are quite unusable.

An electron or a hole may be "trapped" in such a centre, where it is held until a hole or an electron comes near enough to be attracted and to combine. Since neither production nor recombination of holeand-electron pairs is entirely indiscriminate, their lifetime is perhaps rather longer than might be expected.

The conductivity of a semi-conductor depends upon the number of free electrons and holes present, and upon their mobility. The number present depends upon equilibrium between the rate of production and the rate of recombination of such pairs. The rate of production is dependent on incident light or ambient temperature and the rate of recombination, being statistically related to the number which arrive at the recombination centres, depends upon the density of the electrons and holes. Any equilibrium state requires the rate of production and recombination to be the same. Thus the conditions which produce a greater rate of production also cause a higher density of carriers, and, therefore, a higher conductivity. An indication of the dependence of the recombination rate on the density has been given by an experiment which measures conductivity in comparison with incident light; this also shows that the die-away of conductivity, after the light has been shut off, is exponential.

When a hole and free electron are formed by thermal or photo action they move in a random way, similar to the motion of a very small particle in a liquid due to Brownian movement. A number of holes and electrons formed or introduced at a point in the crystal structure diffuse throughout at a rate governed by this random movement, which is itself dependent on temperature. The diffusion rate for an electron in germanium is 93 cm²/sec and for a hole 43 cm²/sec. The rate is dependent on temperature and the figures quoted are for 300°K (27°C) and for fairly pure samples of germanium. The most surprising thing is to find that holes and electrons have mobilities which are not very far different.

The conductivity of a semi-conductor is conditioned by temperature and by incident light, but certain impurities in the structure have a much greater effect. For example, "impurity atoms" with five valency electrons fit more or less perfectly in the structure, except that for each impurity atom there is a shortage of one electron. Fig. 4 shows this effect. The atomic nucleus has five units of positive charge and, therefore, is an attracting force for the electron which has been left out of the four-valency structure; but the energy due to temperature is normally enough to cause the electron to diffuse throughout the structure, and not to remain near its parent atom. This is much aided by the reduction of attractive force due to the dielectric constant of the material, which for germanium is 16. Each "spare" electron is, therefore, a potential carrier of electric current. The density of such carriers in a sample is equal to the

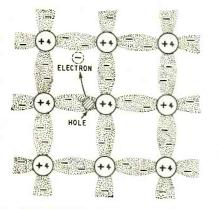


Fig. 3. "Hole" left by electron having "jumped" out of its place, due to thermal or photo effects.

Fig. 4. Illustration of a donor atom in the structure. The effect of the dielectric polarization due to the extra positive charge on the nucleus is shown. The extra electron is assumed to have diffused away from the parent atom and is not shown.

WIRELESS WORLD, FEBRUARY 1955

density of impurity atoms, and the overall conductivity is proportional to the total density of such carriers in the sample.

Such an impurity atom is called a donor. Arsenic and antimony are typical donors for germanium and silicon. A concentration of one donor atom to 10^{4} of pure germanium is sufficient to increase very greatly the conductivity at ordinary temperature; and although hole-and-electron pairs are still formed as in pure germanium, conduction is due mainly to the donated free electrons.

Germanium which has donor impurity atoms is called negative or n-type, because the conduction through it is by means of negative carriers.

There is another sort of impurity which has an equally marked effect on conductivity, and that is the atom with three valency electrons. Examples of this are aluminium, gallium, and boron. These also fit into the crystalline structure without disarranging it,

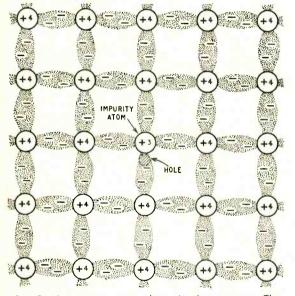


Fig. 5. An acceptor atom shown in the structure. The "hole" diffuses away from the parent atom leaving it with four orbital electrons. In these circumstances, which are normal, the acceptor atoms have a resultant negative charge.

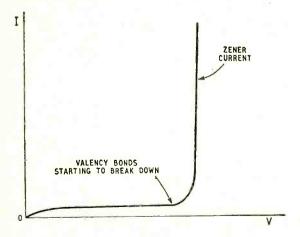


Fig. 6. Zener current in a pure sample of germanium.

but in this case there is an electron missing, instead of one too many. In addition, a nuclear positive charge is missing. The incomplete bond in the structure causes a hole, as seen in Fig. 5. It is perhaps surprising that this sort of hole moves as freely as one caused by light or thermal energy, and diffuses away from the parent atom in a similar way to the donated electron in the previous case. Such an impurity is called an acceptor and the material is then called positive or *p*-type, because the current carriers are holes.

A remarkable effect is shown when the two types of impurity are mixed. The free electrons given by the donor atoms fill the holes from the acceptor atoms, and the balance of holes or electrons remaining carry any current which flows. It is clear, therefore, that if the acceptors and donors are present in equal quantities there are no carriers left, except the hole-and-electron pairs which are generated spontaneously in germanium anyway: the conductivity of the material is then no higher than that of the pure material. Because a small excess of one or other of the impurity atoms causes such a marked change in conductivity the exact proportion to produce this sort of equality is difficult to control in manufacture.


Where both acceptors and donors are present the charge distribution throughout the crystal is uneven when viewed on an "atomic" scale. Each acceptor atom which has had its hole filled represents a resultant negative charge and each donor atom which has lost its fifth electron is a positive charge. There are, therefore, a number of opposite charges fixed in the structure, though the whole is electrically neutral by reason of the mobile charges.

There is one further effect which must be mentioned before the action of the crystal diode and triode can be understood. This is the effect of a large electric field on the production of holes and electrons. When the potential gradient reaches a certain value (the actual value being dependent to some extent on the impurity content of the material) the valency bonds of the structure begin to break up. The effect of such a breaking-up is for a hole to make off towards the negative end and the corresponding electron to the positive end.


All the valency electrons are at more or less the same energy level and in general it would be true to say that a potential gradient sufficient to cause one bond to break up would be sufficient to cause this effect in all other bonds. In practice this is not quite true because of the random thermal energy present, and because the applied potential gradient is modified by the presence of the atoms and electrons. When the potential gradient is not quite high enough to cause spontaneous breaking-up a few bonds will rupture owing to the chance "gift" of some extra thermal energy. The higher the gradient the more likely this is to happen; hence the current due to this effect, known as Zener current, does not start as abruptly as at first it might be imagined. Fig. 6 shows the effect graphically. The bend in the curve is where the first few bonds are torn apart, when the electrical energy plus the thermal energy chance to be sufficient. As the potential gradient is increased more and more valency electrons are able to acquire sufficient energy to break away. The steep part of the curve represents the state in which the electric field supplies nearly all the energy and most of the valency electrons have sufficient energy to break away.

Fig. 7. Presentation of acceptors and donors in the crystalline structure of germanium or silicon.

Fig. 8 (Below). Junction under conditions of thermal equilibrium.

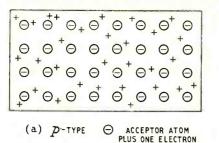

+ MOBILE HOLE

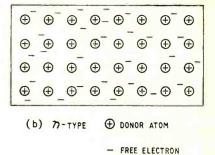


this layer acceptors are in the majority: on the other side donors.

For the purpose of illustration p-type and n-type crystal structure is represented by showing only the acceptor or donor atoms in the structure and the consequent mobile holes or electrons. Fig. 7 (a) shows the p-type material and Fig. 7 (b) the n-type. The acceptor atoms are fixed in the crystalline structure and have the extra valency electrons to which they are not really entitled, hence they have a resultant negative charge. The holes which have wandered away from the parent atoms have an equal positive charge. The material is, therefore, electrically neutral as a whole although throughout the material there are these discrete charges, both fixed and mobile. The donor atoms are similarly fixed but have a positive charge because the fifth electron has wandered away.


When two different materials meet in a junction such as that described above, the holes in the p-type material and the electrons in the n-type material, diffusing in the normal way, cross the boundary into the other sort of material. As we have seen, each side starts electrically neutral, but as holes cross from the p-type to the n-type and electrons go the other way, the n-type material acquires holes and loses electrons, thus becoming positively charged; while the p-type does the opposite and becomes negatively charged. An illustration of the structure is seen in Fig. 8 (a). A standing potential difference is produced between the two materials, and the size of this is regulated by the rate of diffusion across the boundary, the production and recombination rates, and the current of holes or electrons in the reverse direction due to the generation of holes in the *n*-material and electrons in the *p*-material. The potential difference is opposed to the diffusion current and equilibrium is eventually reached when the diffusion current is no larger than the reverse current due to the spontaneous generation.

Fig. 8 (b) shows the distribution of charge over the

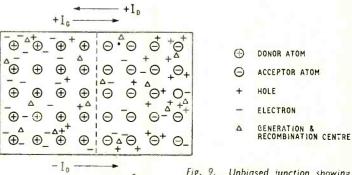

-IG

Fig. 9. Unbiased junction showing diffusion and generation currents.

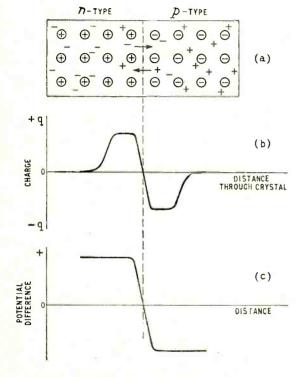

It might at first be supposed that this Zener current would disrupt the crystal structure physically, but this is not so. A current produced in this way is quite stable and the point at which the sharp increase occurs is not particularly temperature-sensitive.


p-n Junctions .- Having seen something of what happens in pure and impure material, it is possible to examine the effects at a junction between p-type and n-type material in a single crystal. A possible method of producing such a junction is easy enough to imagine. Arsenic, for example, will diffuse into a germanium crystal which is made hot enough. If one face of a crystal (having already an acceptor impurity such as aluminium) were exposed to arsenic and heated sufficiently, the arsenic could diffuse into the crystal from one end. We have already seen that the material is p- or n-type according to the majority impurity. In this case the p-type material becomes n-type from one end and a dividing layer must, therefore, exist which is "neutral," having an equal concentration of acceptors and donors. On one side of


WIRELESS WORLD, FEBRUARY 1955

junction when equilibrium has been reached. This is caused by the repulsion of the free electrons in the *n*-type material by the negative potential of the *p*-type, and vice versa. The mobile current carriers are, therefore, repelled from the vicinity of the junction, leaving only the fixed acceptor atoms on one side and donor atoms on the other. This leads to a high resultant concentration of positive charge on the *n*-side of the junction and an equally high negative charge on the *p*-side. Only the fast electrons or holes are able to cross this "barrier."

The reverse current due to spontaneous generation previously referred to arises from the fact that holeand-electron pairs are generated thermally or photoelectrically on both sides of the junction. On the *n*-side the electrons merely add to the free electrons produced by the donors, but the holes, if produced close to the junction, "slide down" the potential gradient to the other side. The equilibrium potential is thus automatically adjusted until the diffusion current exactly equals the generation current. This is true of both holes and electrons. Fig. 9 shows this diagrammatically, with a reminder about the presence of production and recombination centres.

When the junction is biased the effects which produce rectification can be seen. If the junction is forward biased, as shown in Fig. 10, the standing potential difference between the n- and p-materials is reduced. The holes in the *p*-side now find it easier to diffuse to the n-side, so that the diffusion current is increased. The reverse generation current is virtually unaltered, because it is controlled by temperature and incident light only. The two currents are, of course, no longer in equilibrium and the difference flows in the outside circuit. A further increase of bias removes the reverse potential gradient at the junction entirely and the n-side becomes negative in potential while the p-side becomes positive. This means that holes are attracted directly across the junction, as are electrons in the opposite direction. The current is no longer a diffusion current but one in which the carriers

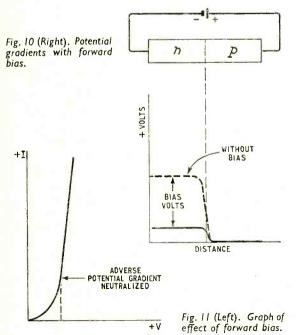

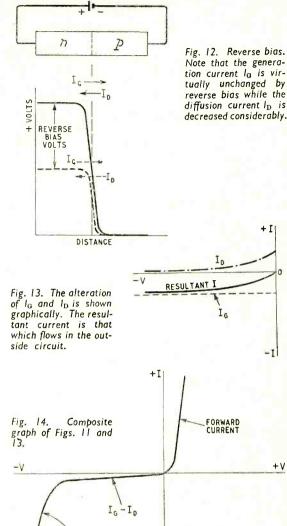

are moving under the direct influence of a potential gradient. As the potential gradient increases from zero the rise of current is very rapid, an effect seen in Fig. 11.

-I

ZENER

CURRENT

Biasing in the opposite direction increases the potential difference between the p- and n-sides. This increase, which is shown in Fig. 12, reduces the diffusion current I_D but has little or no effect on the generation current I_G . Again the equilibrium is disturbed and the *difference* between I_D and I_G flows in the outside circuit. Increasing the voltage has the effect of reducing I_D eventually to zero, but has no effect on I_C , as seen in Fig. 13.

 $I_{\rm G}$, as seen in Fig. 13. If this were all, the characteristic curve would be virtually asymptotic to the graph of $I_{\rm G}$, which is nearly constant. But it will be remembered that when the potential gradient reaches a certain critical value the Zener current starts to flow, that is, holes and electrons are generated spontaneously by the breaking up of valency bonds. At a certain point, therefore, the reverse current curve shows a sudden increase, and

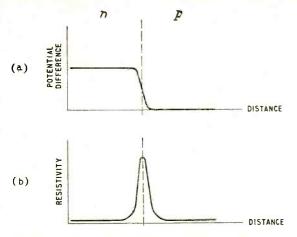


Fig. 15. Graph showing resistivity in different parts of the crystal.

this is shown in the complete characteristic curve at Fig. 14.

It is worth noting that the resistance of the various parts of the crystal may be found very simply by considering the slopes of the curves in Figs. 10 and 12. The graphs show the voltage plotted against distance through the crystal. If we also know the mean current flowing the resistance of any portion of the crystal, or the whole, may be found easily. Again if the cross-sectional area of the crystal is known the resistivity of different portions of the crystal may also be found. Fig. 15 shows clearly that the resistivity is high wherever the potential gradient is steep; in fact, it is proportional to the potential gradient.

The resistance of the junction is, therefore, dependent on the bias and is high when back biased and low when forward biased.

REFERENCES

1. Shockley, W .: "Transistor Electronics." Proc. I.R.E.: Nov., 1952.

I.K.E.: Nov., 1952.
2. Morton, J. A.: "Present Status of Transitor Development." B.S.T.J., May, 1952.
3. Conwell, E. M.: "Properties of Silicon and Germanium." Proc. I.R.E.: Nov., 1952.
4. Roddam, T.: "Transistors." Wireless World, Feb.-

Dec., 1953.

Acknowledgement.-Figs. 1, 2 and 4 are based on Figs. 1, 3 and 12 respectively of reference 1 above. (To be continued)

Historical Valve Collection

ABOUT the year 1920, Robert McVitie Weston, a solicitor with scientific leanings, took to building his own radio receivers and consequently became interested in the various types of valves then available to the amateur constructor-and subsequently in the history of the valve.

His interest spread from current types and soon he was collecting valves of every age and type. A great deal of his time was spent in searching for specimens and many a lunch-hour was devoted to combing junkshops for material. By 1934 he had assembled a collection of several hundred specimens, including one of Fleming's original diodes and a Lee de Forest triode with a descriptive label in Fleming's own handwriting. Housed on the top floor of Mr. Weston's Reigate home, the collection rapidly expanded, following his decision to investigate every possible source of material, both at home and abroad, and by 1938 the exhibits numbered about 2,000.

The war interrupted active collecting, and a change of address necessitated dismantling the museum. After the war, with insufficient time or space to restore it, Mr. Weston felt that the collection was too large and too important for a single person to handle. He therefore decided to hand it over to Standard Telephones and Cables, thereby ensuring not only the preservation of the existing specimens but also the expansion of this unique museum by the addition of new and interesting valves.

This, quite briefly, is the story behind the actual accumulation of the historically priceless selection of valves now assembled in the entrance hall of the Radio Building at the New Southgate works of Standard Telephones and Cables. The company hopes to enrich the McVitie Weston Collection with further examples of really significant valves from every possible source, and to this end welcomes the co-operation of valve manufacturers and others throughout the world in providing suitable items for inclusion. Students of the subject will doubtless appreciate this permanent record of the history of the valve, and it will be possible for them to visit the collection by making application to Standard Telephones and Cables.

A central display cabinet contains only those valves which, for their rarity or other special reasons, are of major and lasting interest. For the rest, it is intended to keep the display flexible and to stage from time to time

special selections illustrating topical aspects of the subject. The main cabinet in the centre of the hall is actually intended to show the general evolution of the valve from the Fleming diode. Outstanding exhibits are two early Fleming diodes; Lee de Forest audions; a Lieben-Reisz gas triode (the only known unused specimen); and diodes used by Marconi at Poldhu.

There are also two corner cabinets, one of which shows the evolution of the water-cooled valve and the other the evolution of forced-air-cooled and radiation-cooled valves. Water-cooled valves include an early example of the Western Electric 220B, the first commercial water-cooled valve and the type with which the 1922 transatlantic radio telephone experiments were carried out. The develop-ment is shown continued through the 1929 Standard Telephones 4030A, an early short-wave valve with integral water-jacket, the Marconi CAT14, the first valve of the very high rating, and includes a modern thoriated tungsten filament valve (S.T.C. 30/260E).

The display of forced-air-cooled valves includes the Marconi ACT (an early type) with various more recent types illustrating the development, and also includes early samples of the silica valve developed by the Admiralty and produced by Mullard.

Another cabinet houses a collection of cathode ray tubes including a very early Braun tube dated 1906; a Western Electric ss4A (a genuine Johnson tube); an S.T.C. 4050AG gas-filled c.r. tube; a gas-focused Von Ardenne tube; an Ediswan projection tube (as exhibited at the Physical Society in 1938); and various modern types.

Trends in the development of valves for v.h.f. and higher frequencies are traced from valves with reduced lead lengths: Marconi Mathieu 1930, 500 Mc/s, 3.5 watts; S.T.C. 4304, 400 Mc/s, 50 watts; S.T.C. 4316, 100 Mc/s; the positive-grid oscillator, S.T.C. 4036A, used in the historic cross-Channel microwave radio link in 1931, 1800 Mc/s; the velocity modulated cavity oscillatorsklystron and coaxial tube; and the cavity magnetron oscillator and travelling-wave amplifier.

The drive to reduction of size is illustrated by a series of valves of old designs through the octal, loctal, bantam and miniature types, finishing with sub-miniatures of contemporary design.

Ionosphere Review, 1954

End of a Sunspot Cycle

T is very interesting at those relatively infrequent epochs which mark the end of a sunspot cycle to look back over the years during which the cycle has run its course and to examine the changes in radio conditions which the varying sunspot activity has occasioned. Or rather (should we say?) to examine the changes in radio wave propagation which have been brought about by the changing *ionospheric* conditions, the latter having been produced by variations in the ionizing radiations falling upon the atmosphere from the sun, in accordance with the variations in the sun's activity, visible evidence of which has been given by the sunspots which appeared upon it.

We may here consider that the end of a sunspot cycle occurs at the epoch of minimum sunspot activity, although this is not strictly true because the old and new cycles overlap each other to some extent around the minimum. But for radio purposes we are justified in assuming that sunspot minimum represents the end of a cycle. Sunspot minimum apparently occurred during 1954, and it is this fact which occasions the above remarks. But we have to add that it is rather too early to be quite certain about the matter yet, and it is never wise to jump to conclusions when one is dealing with sunspot cycles. However, by the end of 1954 there were several good reasons for thinking that the sunspot minimum might he past.

General Effect of the Sunspot Cycle:—Let us now look at Fig. 1, in which the full-line curve is a graph of the twelve-month running average of the monthly values of sunspot number, the latter being the measure in which the degree of sun-spottedness is usually expressed. The monthly value of sunspot

By T. W. BENNINGTON*

number fluctuates rather erratically, but by taking a twelve-month running average we can smooth out the fluctuations and see the general increase and decrease in sunspot activity throughout the cycle. We see that the activity increased from a minimum at the epoch Feb./March, 1944, to a maximum at that of May/June, 1947, and then decreased so as to reach a minimum at some epoch in 1954 which we shall not attempt to indicate precisely, because the last 12 values are, as yet, only provisional. The curve is of a "saw-tooth" shape, there being a relatively rapid increase from minimum to maximum, and a much slower decrease from maximum to minimum. This is a general feature of all cycles which have a high maximum-and the maximum of 1947 was the highest since that of 1778-whereas the cycles with low maxima are more or less symmetrical about the maximum, i.e., their increasing and decreasing phases are of similar duration. In this cycle the increasing phase occupied 39 months and the decreasing phase about 83 months, the total duration of the cycle thus being about 10.2 years, as compared with the mean duration of 11.1 years for the cycles which have occurred since 1755. But it was in no way remarkable in differing from this mean, for the cycles vary from about 9 years to about 13 years in duration. The decreasing phase of the cycle was marked by very large and erratic fluctuations over periods of a few months, so large indeed that they appear as peaks and troughs and ledges even in the smoothed curve of Fig. 1. Towards the minimum of the cycle the curve "flattened-out"—as is usual and the month-by-month variation in the activity was

* British Broadcasting Corporation

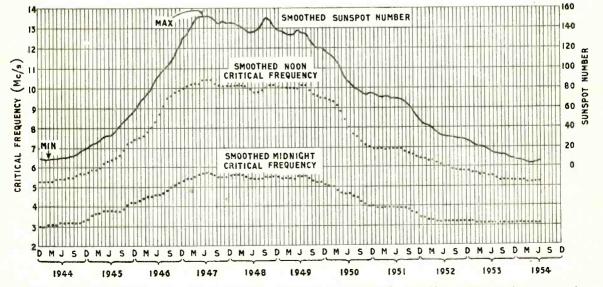


Fig. 1. Twelve-month running average of sunspot numbers and of noon and midnight F2 critical frequencies over the sunspot cycle.

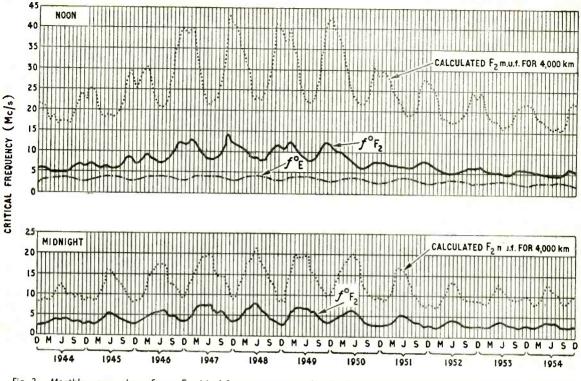


Fig. 2. Monthly mean values of noon E critical frequency, noon and midnight F_2 critical frequencies, and noon and midnight F_2 m.u.f.s over the sunspot cycle.

very small. The value of the 1954 minimum appears to have been lower than that at the 1944 minimum.

The dotted curves of Fig. 1 are from the monthly ionospheric data obtained at the D.S.I.R. ionospheric station at Slough. They are twelve-month running averages of the monthly mean noon and midnight critical frequencies of the F_2 layer, the critical frequency being the highest frequency returned from the layer at vertical incidence. By taking twelve-month running means the large seasonal variations of critical frequency are smoothed out, and the variations due to the changing sunspot activity become more evident.

The object in presenting these curves is to show how the changing sunspot activity affects the frequencies which the ionosphere is capable of reflecting, directly at vertical incidence, and thus by implication, at oblique incidence, as in practical radio communication over a distance. For a variation in the critical frequency at vertical incidence means a corresponding variation in the maximum usable frequency (m.u.f.) for transmission over any given distance.

Both noon and midnight critical frequencies are seen to have followed the variations in the sunspot activity, on this general basis, fairly closely. The noon critical frequency increase with increasing sunspot number was fairly constant until a sunspot number of about 100 was reached, but for higher values of sunspot number the actual frequency increase was less steep, as if a saturation effect in the ionosphere were occurring. It is seen, however, that the general critical frequency variation between sunspot minima and the maximum was of the order of 100% for both noon and midnight, being about 5 Mc/s in the former case and about 3 Mc/s in the latter. The m.u.f.s for short-wave communication would of course undergo corresponding but greater variations than the above, at noon and midnight respectively.

Fig. I does show, therefore, how closely the general ionospheric conditions at Slough followed the general level of solar activity, as indicated by sunspot observations. If we were to look at the ionospheric measurements from other ionospheric stations throughout the world we should see the same trends, though the actual values of critical frequency would be different. We now turn to a more detailed examination of the ionospheric variations, again based on the measurements made at Slough.

Month-by-Month Variations:—In Fig. 2 are plotted, as full lines, the monthly values of the Slough critical frequencies for the F_2 layer ($f^\circ F_2$) for noon and midnight for the whole period covered by the sunspot cycle. The dot-dashed curve shows the monthly values of the critical frequency of the E layer ($f^\circ E$) for noon.

We may dismiss the latter curve at once by saying that the E layer variations over the sunspot cycle, whilst not without significance, are relatively small. The peaks and troughs in the F_2 layer curves are due to the seasonal variations in critical frequency, which, at noon, are such as to produce low values in midsummer and high values around midwinter, and, at midnight, high values at midsummer and low values at midwinter. This type of variation is now well established, being due, of course, to the variations in the relative position of sun and earth with the seasons.

Superimposed on these seasonal variations, how-

WIRELESS WORLD, FEBRUARY 1955

ever, there is an evident long-period variation which is that due to the sunspot cycle, the highest values of both noon and midnight critical frequency occurring near sunspot maximum and the lowest near sunspot minimum. It is regretted that, owing to space considerations, these values have had to be plotted on a rather small scale, so that the variations due to the sunspot cycle are less noticeable than would have been desirable. However, if we examine the dotted curves of Fig. 2 we can see the effect of the cycle upon practical short-wave transmission quite clearly. These dotted curves show the monthly values of F2 layer m.u.f. for 4,000 kms (the maximum possible distance for one hop), as calculated from the Slough monthly critical frequencies, for noon and inidnight respectively. That is to say, they give the monthly values of m.u.f. for a one-hop transmission path, with the F₂ layer over Slough as the apex of the trajectory.

The peculiarities of these curves are rather interesting. At noon in summer the m.u.f. increased between the minima and the maximum from about 16 Mc/s to about 23 Mc/s or by approximately 44%, and in winter from about 22 Mc/s to about 43 Mc/s or approximately 95%. The midnight m.u.f., on the other hand, increased from about 12 Mc/s to 21 Mc/s or 71% in summer, but only from about 8 Mc/s to about 9 Mc/s or 12% in winter. Thus the effect of the sunspot cycle was to increase enormously the m.u.f.s during the winter day, to do so to a lesser extent during the summer night, to an even smaller extent during the summer day and to cause hardly a variation at all during the winter night.

A few words about the reasons for these variations may not be out of place. The sun's effect upon the inosphere at night is an indirect one and thus the variations due to its changing activity would not be so great as during the day. During the deep winter night-when the direct effect of the sun has been removed for so long-they seem almost to disappear altogether, whereas during the summer night-with little darkness—they are still quite apparent. During the day the sun's effect upon the F_2 layer is not a simple one, for its behaviour is anomalous, in that during the summer the increase in the ionizing power of the sun's rays is more than counteracted by an expansion effect, so that the ionization per unit volume actually decreases, and the critical frequency falls, as compared with the winter. Thus the greatest effect of the changing solar activity occurs during the winter day, and is not so apparent in summer.

But we are, perhaps, more interested in the practical effects of these variations upon short-wave communication and it is interesting to note, from the dotted curves, the changing utility of various frequencies throughout the cycle. In doing this we should remember that we are studying curves for the ionosphere above Slough only, and that for practical purposes the usable frequencies will be much modified by conditions in other parts of the world.


Taking the daytime curves first, the most striking feature is the very high frequencies which would seem to have been usable for long-distance communications during the winter months around the maximum. In fact, the curves indicate that frequencies above 30 Mc/s could have been used during 4 winters, though it is doubtful whether such frequencies were, in fact, put to much use for this purpose. A frequency of 28 Mc/s, it is seen, should have been usable during 6 out of the 11 winter periods, whilst a frequency of 21 Mc/s should have been usable winter and summer alike from 1946 to 1950 inclusive, and to have been too high during the summer periods only of the remaining years. A frequency of 15 Mc/s would have been used throughout the year during the years near the sunspot minimum, but would probably have been too low for years around the maximum. Of course, the daily *periods* of usefulness of different frequencies are not apparent from these curves and would vary from year to year.

The midnight curves indicate that 15 Mc/s would have been usable at night during 6 of the summer periods and 11 Mc/s during the remainder. As to the most suitable frequency for winter night-time use the indications are that 7 Mc/s should have been usable throughout the cycle, and would not need alteration from minimum to maximum. Again it is stressed that some modifications to the above conclusions would be necessary when full account is taken of the actual transmission paths, and of other periods of the night. However, the curves do give us a general indication of the utility of different frequencies, both for daytime and night-time use.

The New Cycle:—So much for the old cycle. We learn what we can from the ionospheric measurements taken during its course. But we now desire to know something about the new one, and particularly about how radio conditions are likely to change in the immediate future. Unfortunately, it is here that we are at a loss. For the laws which govern sunspot cycles are not yet known and we are very much in the dark as to how the sunspot activity will vary in the near future. If we only knew that we could well relate our knowledge of radio conditions to it and say how they would most likely change. But we do not know it and so can only speculate, at least for a year or so to come.

For 1955, therefore, it is impossible to forecast what changes may occur. If the new cycle has well begun the sunspot activity may increase somewhat more rapidly than it has been decreasing during the past year. We say this merely because it has usually done so in the year following past minima of which there are records. But it seems unlikely that, by the end of the year, it will have reached a value such as to have produced any large variations in the ionosphere, and to have made any very significant changes to the frequencies at present most useful for shortwave communication.

"I see commercial television is here !"

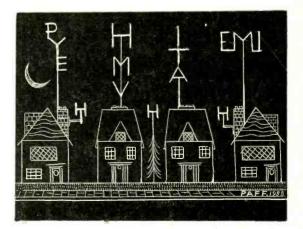

WIRELESS WORLD, FEBRUARY 1955

SIMPLE WAVE-SHAPER

By ARTHUR W. WAYNE*

Giving Square-wave Output from Sine-wave Inputs from 100 to 5,000 c/s

W HILE spot-frequency square-wave generators are useful for general amplifier testing, a continuously variable source is often of value for detailed investigations; for example, of tone control circuits at various settings.

Many types of shaping circuits are available, each with its own particular limitations. The multivibrator is suitable only for spot frequencies, unless accurately matched tandem gain controls are available; and such components are both expensive and difficult to obtain within the required tolerance. Further, the wave shape is unsatisfactory unless passed through a clipper stage, thus adding cost and complication. The transitron circuit is again capable only of spot frequencies, and is apt to be difficult in regard to its power supply. The cathode-coupled clipper is critical of circuit layout, and is better followed by a further clipping stage, while the tetrode limiter needs heavy driving, and does not always produce a satisfactory waveform unless the output be subjected to further clipping.

In fact, all these circuits are at their best only when followed by clippers, and with this in mind, it was decided to make do with a clipper alone, and so arrange the circuit that deficiencies in the clipper could be easily compensated elsewhere. Fortunately, several sine-wave generators were available, so lack of self-contained excitation was not a serious matter. The arrangement finally adopted was that of Fig. 1, and it

* Shirley Laboratories, Ltd.

proved so satisfactory for its purpose that it is now in production for commercial use.

The circuit is almost self-explanatory, but one or two points are perhaps worthy of comment. In order to keep the clipper independent of external conditions, it was necessary to couple it to the output by a cathode follower; and as a position for this stage had to be provided on the chassis, and only double triodes were immediately available, one half of an ECC33 was used for this purpose, and advantage was taken of the other half to provide an input amplifier.

V2a is an overdriven triode, with component values chosen for very sharp clipping. Operated with zero bias and a very low anode load, excessive grid excitation quickly drives the valve into both the anode bend and saturation regions of the characteristic. V2a is directly coupled to V2b, the grid of V2b being held negative to its cathode by the voltage drop across R_7 . C_4 with R_9 form a high-pass filter to help compensate circuit strays and other deficiencies.

Variable Time-Constant

The output from V2b is coupled to VIb via C_s and VR₁, and in operation the full value of VR₁ is used for the lower frequencies, but is reduced from 3,000 c/s upwards, until at 5,000 c/s only about 25,000 ohms are left in circuit. Unless this reduction in time-constant be made, rounding of the corners occurs at the higher frequencies. When a square-wave is passed through a

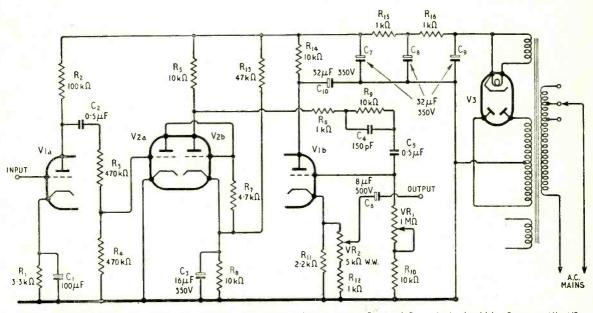


Fig. 1. Circuit diagram of square-wave shaper. All resistors 1-watt except R_{15} and R_{16} which should be 5-watt. VI, V2, ECC33 or ECC82; V3, GZ30 or EZ80.

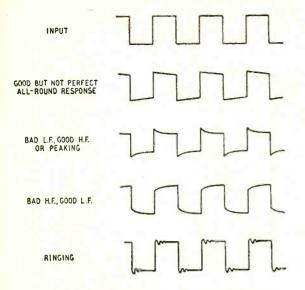


Fig. 2 Typical square-wave distortions and some of the amplifier deficiencies which cause them.

differentiating circuit, as the time-constant is reduced the waveform distorts, the leading edge rising and the trailing edge falling. Advantage is taken of this to compensate for the integrating action of the strays in conjunction with the circuit resistances. While this, admittedly, is a brute-force-and-ignorance method of obtaining results, it does work quite effectively, so *non olet*.

A sine-wave input to the shaper of 4 V r.m.s. is sufficient to ensure satisfactory operation, but some reduction may be necessary from 3,000 c/s upwards. Although a good shape may be obtained from as much as 20 V r.m.s. at 100 c/s, it will be found that between 2 and 6 V r.m.s. is all that can be handled in the higher ranges. In practice, VR₁ is adjusted to give as sharp a leading corner as possible, and the input is then set to give an equal mark-space ratio on the display. It takes less time to set up than to read about.

Constructional Latitude

Circuit layout may be anything the constructor chooses or can achieve, from the worst rat's-nest to a highly finished commercial instrument, and component tolerances do not seem to matter at all. In fact, the shaper appears to be quite unconscious of any deficiencies in either of the foregoing respects,

although it was found that the ECC33 and ECC82 functioned more satisfactorily than their American counterparts. The original unit was made in about 3 hours, including post-constructional alterations, from first commencing the drawings to the finished article : it should not take the most meticulous amateur constructor more than 4 hours or so. And while it is in no way a laboratory instrument, being designed only

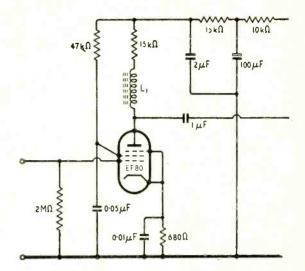


Fig. 3. Wide-band oscilloscope amplifier. A long-wave, dust-cored coil is suitable for L_1 .

for the limited function and coverage described earlier, it does in fact produce a sufficiently satisfactory approximation to a square-wave, from as low as 20 c/s to well above 10,000 c/s.

For the benefit of those who are not accustomed to square-wave testing of amplifiers, a few characteristic displays are given in Fig. 2. Much information can be gained from observing on the oscilloscope screen the effects of deliberately altering the values of circuit components in the amplifier being tested.

Finally, it must be stressed that, when making square-wave tests, the oscilloscope amplifiers must be above suspicion. Not all commercial instruments meet with this requirement, and for those who are doubtful, a circuit for a wide-band amplifier is given in Fig. 3. Power supplies may be taken from the shaper.

> Commercial version of the wave-shaper made by Shirley Laboratories, Ltd., Worthing.

LETTERS TO THE EDITOR

The Editor does not necessarily endorse the opinions expressed by correspondents

Tape Machines

I SUPPORT Harry Crampin's plea (your December, 1954, issue) for higher tape speeds and larger spools. I also agree that the European standard spool (single-cheeked) is preferable to the U.S. and for the following reasons :

One should aim at uniform tape tension on both sides of the gate, because failure to vary the torque with the radius gives an additive error. In other words, without radius compensation on either side, at the time when the tape is being least assisted from the gate by the take-up spool it is also being most heavily impeded on its journey towards the gate by the higher speed at which the reservoir spool has to rotate. As is well known, the simplest and most reliable way of minimizing both these discrepancies is to employ gravity clutches whose slip varies directly with friction and therefore with the loading, but it is perhaps not always realized that unless the "weight ratio" equals the "diameter ratio" compensation is not achieved. A European standard spool weighs 29oz loaded and $8\frac{1}{3}$ oz empty, a ratio of 3.3. Similarly, the effective outer diameter is 11in against the core diameter of $3\frac{1}{3}$ in, again a ratio of 3.3, but on no other design of spool has this been so carefully looked after, certainly not on the U.S. which is also much harder to adapt to the domestic 7in centre and vice versa. The demands for larger spools will not diminish the popularity of smaller ones. A third advantage concerns track discrepancy.

On multi-track machines it is of course possible, with doubleturning the spool over, but unless the machine is in perfect alignment this will result in loss of top. Such a procedure is impossible with single-sided spools, each track always having to be replayed from the head through which it was recorded. Also the European standard spool is much easier to thread, join and edit and there is less chance of noise from the tape catching on the cheek of a spool.

Last but not least, the capacity is larger and in view of these many advantages I deplore the present tendency for the U.S. standard to oust the European. Reverting to Mr. Crampin's preference for Continental designs, 1 would stipulate that in addition to being self-reversing it should be in order to switch off the machine merely by breaking the mains connection. Any form of remote control is out of the question with most British designs as the pressure roller would be left in static contact with the capstan, which the makers strongly deprecate. Could one of the rubber or synthetic rubber manufacturers please state whether too much fuss is not being made over static contacts on pressure rollers, at any rate so far as machines in daily use are concerned?

Cleethorpes, Lincs. R. LEACH.

YOUR correspondent's specification (December, 1954, issue) for an ideal tape recorder reminds me of an R.C.A. wire recorder I had several years ago. This machine was magazine loading like a cine camera, each magazine holding two wires of thr duration each and so arranged that as one was playing the other was rewinding.

The wires were driven at a constant speed by capstans, and a very ingenious spring arrangement between the reels not only kept the wires taut, but also transferred the rotation of the supply reel to the take-up with the necessary compensation for wire build-up. At the end of a reel a notch in a rotating disc (which also served as a footage indicator) tripped over a switch within the machine and reversed the direction of the driving motor and the amplifier connection to the sound heads.

In spite of a bakelite case and 5-in speaker the good design and precision of the mechanism gave a quality and freedom from "wow" seldom obtained with the average popular-priced tape machine. Doncaster. P. STUART.

Variable High-pass Filters

THE use of variable steep-cutting low-pass filters in domestic high-fidelity amplifiers has become almost standard practice. It is therefore surprising that the use of variable steep-cutting high-pass filters (not fixed rumble filters) appears to be relatively rare. Such a filter is of considerable value in minimizing listener fatigue due to distracting effects associated with the low-frequency end of the spectrum, and only too apparent in reproducers having speaker systems capable of extended bass response.

The immediately apparent advantages of a high-pass filter are:

1. Reduction of hum and rumble inherent in many discs, particularly of the 1.p. type. This may readily be verified by playing different discs on a high-quality turntable and noting the disc-to-disc variation in reproduced hum and rumble.

2. Reduction of severe non-linearity distortion due to random "cone flutter" in woofers used with amplifiers having useful response down to 2-5 c/s.

3. Reduction of modulation and other hum sometimes presented free of charge in radiated radio programmes.

The preceding advantages are to some extent obtainable from the usual fixed rumble filter. An advantage peculiar to a variable high-pass filter is that it will, in conjunction with the commoner low-pass filter, provide ready adjustment of "frequency-range balance." It is well known that when for some reason the h.f. response has been sharply curtailed it is often necessary to curtail the l.f. response as well in order to maintain an aesthetic-ally pleasant tonal balance. A suitable product for the l.f. and h.f. cut-off frequencies is generally given as 500,000. On this basis the respective nominal cut-off frequencies for two 5-step filters could, for example, be: (a) Filters out (say 25-20.000 c/s); (b) 40-13,000 c/s; (c) 50-10,000 c/s; (d) 70-7,000 c/s; (e) 100-5,000 c/s. The "straight-line" fanatic will probably pale at or

beyond step (b). Nevertheless, step (e) will allow enjoyment from a treasured acoustically recorded disc.

The high-pass filter can conveniently be of the R-C parallel-T feedback loop type outlined by Thiessen (J. Acous. Soc. Amer., Vol. 16, No. 4, April, 1945). If an existing pre-amplifier cannot painlessly be modified to this extent, reasonable results can be had by using a multi-pole switch and several cascaded elementary R-C filters. The latter alternative may in fact find favour with those who look with suspicion on sharp knees in filter curves.

Pretoria, S.A. M. R. H. MACNAMARA.

Electronics on the Farm

IT seems to me to be about time that the electronics industry and the farm machinery industry got together on the subject of electric fencer units.

The basic electric fencer, by now a hoary old stager, is a six-volt battery (usually an old car accumulator) feeding a balance wheel interrupter and thence a transformer, to inject spurts of negligible power but about 10 kilovolts into a fence wire which is carried on insulators.

Since the power demand is extremely low, the chief disadvantages of the accumulator become very obvious. Accordingly several manufacturers have produced models designed to run off the ubiquitous radio h.t. battery. As far as I know most of these have also been modified in the interrupter mechanism; but if I am any judge of the

contents of a sealed box, and the clicks it produces, the interrupter is still a moving contactor. It is true that the improvements in the interrupter mechanism are probably considerable, for salesmen talk glibly of a five-year guarantee; indeed, I suspect that the timebase is a resistance-capacitor circuit and the contactor a reasonably good magnetic relay. However, I submit that for this purpose a neon tube would be far cheaper and more reliable, and that a wholly electronic unit would be superior to any unit containing mechanism.

I admit that I lack complete technical information. It is possible that I am mistaken in believing that a reasonable neon tube will effectively act as a switch and/or carry the power demand, and I suggest that the matter might well be worth examination.

The advantages which I foresee are cheapness and simplicity in first cost and maintenance, lightness and com-pactness. The neon tube would certainly plug in, presumably the electrolytic capacitor could also be plugged and, although perhaps unusual, the resistor as well. The transformer hardly ever gives any trouble, and therefore maintenance would consist of nothing more than buying a new relatively inexpensive unit and changing it for the old one. It is true that the older farmer might not know which to change, but that idea is becoming out of date.

Another refinement I have yet to meet, except on my own fencers, is a neon earth detector on the h.t. side. I have de-capped miniature Philips neon lamps and connected them across the output terminals $(\frac{1}{2} \text{ megohm in})$ series) so that they flash if the fence wire is *not* earthed. Few stockmen will shock themselves to find out if the fence is in fact working, and I suspect that our cattle would be "out" a good deal more often without this aid.

It appears that present fencers usually have a fre-quency of about two flashes per second. My present balance wheel units suffer far too much from burnt con-tacts, and therefore when I overhauled them this last spring I reduced the frequency to about one per second, thereby in effect doubling the working life. So far I have found no disadvantage.

My units, being expensive of their kind, carry a simple, but not nasty, battery voltage indicator with a push-button switch. It is perhaps because the h.t. battery type is alleged to run for five months on one battery that this refinement is invariably omitted. It is not easy to justify a moderately expensive unit which will not be used above twice a year, but I submit that a push-button, a resistance, and a torch type bulb might serve; with instruc-tions that the bulb should be held on for a few moments and will fade rapidly on a worn-out battery. Hempstead, Essex. H. G. P. TAYLOR.

Mathematics

HAVING been cited in the January issue by F. V. Bale as an example of the type of writer who lowers the tone of *Wireless World* by frightening readers off mathematics, may I be allowed to reply?

If indeed I have been guilty of discouraging anybody from the study of mathematics, then I deserve censure. So far from my intention having been that, however, it has been precisely the opposite; namely, to debunk the supposed esoteric nature of mathematics and to break down the mathematicians' "closed shop." In the very article which Mr. Bale quotes I showed how the basic filter equations could be arrived at by schoolboy algebra, and then, having taken the reader to the desired point by presumably familiar ways, revealed the cosh as nothing to be afraid of but rather as a useful tool-"The practical value of the cosh, then, lies in the fact that it enables one to dodge most of the work by looking up tables.... Any-body can do that."

It surely cannot be denied that there are thousands of potential technicians and engineers who do find hyperbolic functions in the abstract a forbidding and largely meaningless subject, and their relationship to filters far from obvious. The above-quoted article being the example chosen by Mr. Bale to deplore, what alternative treatment does he recommend for these readers?

At the other extreme, my own experience as a wartime radar instructor showed me that graduates in mathematics were not automatically able to apply it to practical uses; most of them had never clearly visualized the physical realities represented by their equations. These, too, surely stand to benefit from an alternative approach.

A crime to which I do quite cheerfully plead guilty is that of lack of respect for the type of author who fills his pages with mathematics and considers it beneath his dignity to explain what it means in words. In this attitude I am glad to be in the company of perhaps the most noted authority on the presentation of technical informa-tion—Prof. R. O. Kapp, whose concluding paragraphs in his paper "The First Draft"* should be taken to heart by the over-mathematical. "CATHODE RAY." by the over-mathematical.

* Obtainable from the Secretary of the P.T.I. Group, University College, London, W.C.1. price 2s.

Viewers' Strike?

LIVING on a main road within a few yards of the junction with another main road and receiving a weak signal from the Brighton booster and a still weaker one from the new Rowridge station, I am finding out some things about ignition interference.

Of all the cars passing my door, 90 per cent are unsuppressed and even some of the new cars have either unsatisfactory suppressors or the suppressors have been removed.

It is time that the P.M.G. made the fitting of sup-pressors to cars compulsory, even if it means supplying the suppressors free. The cost of this could be met from the percentage of broadcast licence fees retained by the G.P.O. If all licence holders got together and refused to renew their licences, I am sure a speedy solution would be found. W. E. NIALL.

Worthing, Sussex.

Tape Terms

A LANGUAGE of magnetic tape recording is evolving and, although standardization is yet a toddler as regards technique, some unhappy selections are emerging in the language and seem to have become accepted as standard terms already.

It helps so much to link meaning with function, rather

than to blind with slick startlers, that one hopes terms such as "azimuth" will not prevail. When technicians use that term, the context usually suggests that they mean "head" tilt relative to tape path. "Azimuth" is an ancient astronomical term of different meaning, shortly put as "an arc of the horizon." This is borne out by its origin: Arabic al (the) sumut (direction). How does it come to be used to suggest a different mean-ing for which a better word exists, namely, "oblique"; Latin *ob* (before) *liquis* (slanting) defined shortly as "to deviate from the perpendicular?" That, surely, is exactly what is meant.

hat is meant. Bristol Magnetic Recorder Company, W. D. ARNOT.

Overseas Buyers

FREQUENTLY an article advertised in Wireless World attracts my attention and I develop an urge to buy it. But I get disturbed about foreign exchange, extra postage for overseas mailing, etc., and I finally decide the product is perhaps not worth all the fuss anyway.

Perhaps this is wrong. Could not your advertisers publish a little bit on how receptive they are to small foreign orders and how to go about it, especially extra payment requirements for overseas mailing? Yonkers, N.Y., U.S.A. MA

MARTIN L. KENELY.

Vector Addition and the Slide Rule

Rapid Method of Calculation

By A. G. LONDON, B.Sc.(Eng.), Graduate I.E.E.

GREAT many calculations in electronics involve working out the value of terms of the form

$$(x^2 + y^2)$$

Two examples which come readily to mind are:

(i) The magnitude of the resultant of two vectors, V_1 and V_2 , at right angles, is given by:

$$\sqrt{(V_1^2 + V_2^2)}$$

(ii) The magnitude of the impedance of a seriestuned circuit is given by:

 $|\mathbf{Z}| = \sqrt{[\mathbf{R}^2 + (\omega \mathbf{L} - 1/\omega \mathbf{C})^2]}$

The usual method of calculating the value of a term of this form is to find the squares separately, add them, and find the root again. This is a rather tedious business, particularly if it has to be repeated a number of times. A much quicker and easier method exists, however, which eliminates those little addition sums, done on odd scraps of paper. The whole process can be carried out on a slide rule without "taking off" any figure except the answer. The slide rule can be of the simplest type, one with only the four main scales.

A reminder of the properties of these scales may not be out of place. They are usually called scales A, B, C and D, from top to bottom, A and D being on the stock; B and C on the slide. They are so arranged that if the cursor is set to a number on scale D the square of that number appears under the cursor on scale A. Square roots are found by the reverse process. Scales C and B, respectively, have similar properties.

Now suppose we wish to find the value of the root $\sqrt{(x^2 + y^2)}$, y being smaller than x, we proceed as follows.

1. Set the slide rule so that y on scale C is opposite x on scale D. (Arrow 1 on Fig. 1.) Then by the ordinary rule for division, x/y will appear on scale D, opposite the end mark on C. (Arrow 2 on Fig. 1.)

2. Set the cursor to the end mark on scale C. Then, as vie have already noted, $(x/y)^2$ will appear under the cur or on scale A. (Arrow 3 on Fig. 1.)

3. To the value of $(x/y)^2$, add 1, and set the cursor to thus new figure, still on scale A. (Arrow 4 on Figs. 1 and 2). The cursor now indicates $(x/y)^2 + 1$ on A; and the square root of this on scale D. (Arrow 5 on Fig. 2.)

WIRELESS WORLD, FEBRUARY 1955

4. Now move the slide until the end mark on scale C is set against the cursor.

5. Read $\sqrt{(x^2 + y^2)}$ on scale D opposite y on scale C. (Arrow 6 on Fig. 2.) In steps 4 and 5 we have used the ordinary multiplication rule to multiply $\sqrt{[(x/y)^2+1]}$ by y, and,

$$y\sqrt{[(x/y)^2 + 1]} = \sqrt{\{y^2[(x^2/y^2) + 1]\}} = \sqrt{(x^2 + y^2)}$$

In the example shown in the figures, x = 4, y = 3. Then the successive steps are:

1. x/y = 1.3334. $\sqrt{[(x/y)^2 + 1]} = 1.667$ 2. $(x/y)^2 = 1.78$ 5. $\sqrt{(x^2 + y^2)} = 5$

3. $(x/y)^2 + 1 = 2.78$

It is important, in step 3, to keep in mind the position of the decimal point in $(x/y)^2$. In the example, the figure 1.78 on scale A actually represents this number, and $(x/y)^2 + 1 = 2.78$. However, according to the relation between x and y, it might represent 1.78 multiplied by any power of 10; e.g., 0.178 or 17.8. Then $(x/y)^2 + 1$ would be 1.178 or 18.8 respectively. Care is therefore necessary at this point in the operation.

The process can very simply be adapted to evaluate a root of the form $\sqrt{(x^2 - y^2)}$. The only change necessary is that, in step 3, 1 is subtracted from $(x/y)^2$, instead of being added, and the cursor is set to this value; i.e., $(x/y)^2 - 1$. The square root is then taken as before, multiplied by y, and the answer read on scale D. The proof is exactly analagous to the case of $\sqrt{(x^2 + y^2)}$. Clearly, this comes in useful, for example, in the series-tuned circuit case mentioned above, if we know the impedance, but the resistance or the reactance is unknown.

Then
$$R = \sqrt{(|Z|^2 - X^2)}$$

While no claim is made that the process described in this article is original, it is a simple and rapid method of solving the particular problem, and deserves to be more widely known. Many readers will, no doubt, be able to find other applications besides those mentioned.

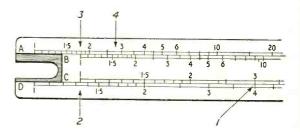


Fig. 1. The first steps in setting the slide rule are shown here, culminating in $1 + (x,y)^2$ at point 4.

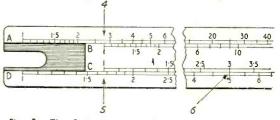


Fig. 2. The final steps are illustrated here, the root appears at point 5 opposite point 4 and multiplying by y gives the answer at point 6.

FLUX-CUTTING or FLUX-LINKING?

NOT very long ago there took place at the I.E.E. a discussion on fundamental electromagnetic theory*. At the end of it the chairman remarked that although it was the normal policy of the I.E.E. to encourage student members to attend its meetings, he was rather glad they hadn't been much in evidence on that particular occasion. Well, certainly, it did seem somewhat unedifying to hear one learned Professor of Electrical Engineering after another disagreeing flatly on the very basic principles of the subject. Quite enough to shake whatever faith students may have in the authorities, and to make one wonder whether there is anything-even Ohm's Law-that can be relied upon to be true.

One of the most discussed things on such occasions is the question of how to reckon induced e.m.f.whether on a basis of "cutting magnetic lines of force" or some other way. Nearly all the electricity used in the world is generated by electromagnetic induction. And the process is fundamental in radio too, for radio waves would be impossible without it, and so would transformers, chokes and tuning coils. If then the most eminent authorities invariably disagree on the principles of the thing, how can anybody be expected to understand it and make the necessary calculations for designing radio and other electrical systems? Disagreement about how wages are calculated can be relied upon to give rise to trouble; how is it that disagreement about how to calculate induced voltage does not? Or does it?

Some while ago† I was rash enough to stick my own neck out into this particular controversy, by advocating the flux-linkage (or flux-threading) idea at the expense of the flux-cutting idea. And now I get a letter from a radio engineer in the Belgian Congo who writes in some concern to report that after gladly accepting my view on this matter, as being in line with that of his one-time professor of electricity, he was dumbfounded on being confronted by a junior colleague with a description of an actual electric generator that by its method of functioning absolutely proved the flux-cutting idea. More shaken faith, presumably! He may be interested to know that at the I.E.E. discussion this particular kind of generator was well in the forefront of the battle, and my shocked ears could hardly believe what they heard when one teacher made the highly immoral suggestion that students should be kept in ignorance of it because it did not square with the official curriculum.


Well, far be it from me to pose as a sort of superauthority to put everyone else right, but it does seem A Controversy on Fundamentals-and a **Practical Solution**

" CATHODE RAY " Bv

to me that at least some of this confusion is capable of being dispelled. First of all, for the sake of any readers who are not yet quite "with us," let me explain what the controversy exactly is. It began explain what the controversy exactly is. with Faraday's famous experiments in 1831. He found that an electric current could be magnetically induced in a circuit in two ways: (1) by moving a magnet near the circuit (or, what comes to the same thing, moving the circuit near a magnet); and (2) by moving neither but varying the strength of the magnetism, say by switching the current on and off in a coil of wire producing it. The first of these processes is applied in every rotary electric generator; the second in every transformer and tuning coil. Faraday visualized the magnetism as lines of force in the space around and within the magnet, and regarded the current in the first class of experiments as being induced by these lines cutting across the circuit (or the circuit cutting the lines). He was inclined to think that the results of the second class of experiments could be regarded in the same way, by supposing the lines of force to spring out of the coil as the current was increased, and so to cut across any coupled circuits.

Before generators and transformers could be designed on a proper engineering basis-and certainly before radio equipment could be designed-it was necessary to be precise about the relationship between movement or variation of magnetic field and the voltage of the e.m.f. generated thereby. The strength of a magnetic field can be reckoned by the force it exerts on a small magnet. It was agreed to suppose that a certain force corresponded to so many lines per square centimetre. The total number of lines over a given cross-section was called the flux. It was found that the e.m.f. generated in a circuit was proportional to the rate at which flux was cut by the circuit, or varied within it. In fact, when the amount of flux corresponding to a "line" had been defined, it turned out that in order to generate an e.m.f. of one volt it

Fig. 1. Here is an idealized example of electromagnetic induction. The dots represent an endon view of 10⁸ magnetic "lines," uniformly distributed. The square circuit is supposed to move steadily from position (a) to position (b) in one second. What will the voltmeter V read during this process? And why?

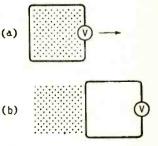

WIRELESS WORLD, FEBRUARY 1955

^{* &}quot;A Short Modern Review of Fundamental Electromagnetic Theory," by P. Hammond, Proc I.E.E. Pt. 1, July, 1954. † Wireless World, June, 1953, p. 285 ("Radio Waves").

was necessary to vary the lines at the rate of $100,000,000 \ (=10^8)$ per second.


Now this is where we get to the controversy. Fig. 1 shows a simple circuit, consisting of a square of wire connected to a voltmeter. So as not to introduce complications caused by the magnetic field due to current in this circuit, let us suppose that the voltmeter has an infinitely high resistance, so that no current flows. The dots are end views of the lines of force produced by a coil not shown, but parallel to the single square turn. To avoid complications again, let us suppose that the return paths of these lines are kept well clear of our picture by means of a high-permeability iron core. Finally let us assume that notwithstanding the fewness of the dots there are actually 10⁸ lines of force enclosed by the circuit, and that they are distributed uniformly over its area. If now the circuit were moved steadily to the right from position (a) to position (b) at such a speed as just to clear all the lines of force in one second, we can safely assume that during this process the instrument would read one volt.

But if you ask a number of engineers to explain this result you will discover two schools of thought. Some will say that three of the four sides of the circuit take no part in the experiment because they cut no lines of force, but that the fourth—the left-hand one was cutting 10⁸ lines per second, and that was why an e.m.f. of 1V was generated. Others will say that at the beginning of the operation 10⁸ lines of force were linked with the circuit, and at the end none were; difference, 10⁸; so magnetic linkages with the circuit were being varied at the rate of 10⁸ per second, and that was why an e.m.f. of 1V was generated.

Divided Counsels

Precisely the same result and explanations are forthcoming if the circuit is kept stationary and the field is moved to the left. And precisely the same result is obtained if both are kept stationary and the current in the unseen magnet coil is reduced at such a rate as to bring the field steadily to zero in one secondbut this time the explanations will vary. The linecutting school of thought splits into two: one group will say that of course this is quite a different effect. so cannot be expected to have the same cause; the others stick faithfully to the cutting idea, and adapt it to cover the changed circumstances by saving that the lines can't just come from nowhere, but that when current in the magnet coil is increased or decreased they spring out or flop back, so cutting the circuit and generating an e.m.f. one way or the other around it. This adaptation of the original line-cutting picture may perhaps be accepted, provided that nothing better can be found and that it is consistent with other known facts. But slightly more elaborate experiments show that an e.m.f. is induced in a circuit by growth or collapse of a magnetic field even when that field is caused by current in that same circuit, and I for one find it a little difficult and unconvincing to visualize a wire being "cut" by lines of force emerging from itself.

When we come to interrogate the linkage school of thought we find them perfectly happy and pleased with themselves, because their account of the previous (Fig. 1) experiment equally well covers the currentvarying or transformer experiment, without involving them in having to explain where the lines come from or where they go. Whether the number of lines Fig. 2. D is an edge view of a metal disk, rotating in the field of a fixed magnet M. Bl and B2 are brushes making electrical contact with axle and edge of disk. Will the voltmeter V give a reading? If so, why?

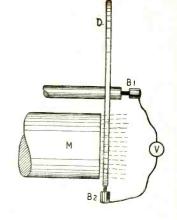

linked with the circuit is made to change by moving the field or circuit or both, or by varying the strength of field in a stationary set-up, makes no difference to the e.m.f. induced; so why, they say, adopt an explanation that has to be forced to fit some of the facts, or alternatively use two explanations to cover facts that are obviously related and can perfectly well be covered by one?

This is the psychological moment, when these linkage people are swelling with self-satisfaction, to perform the experiment known as the Faraday disk or the homopolar generator. One form of it is shown in Fig. 2. D. is an edgewise view of a copper disk which is rotated steadily. B1 is a brush making contact with its axle, and B2 is another making contact at its rim. M is a fixed magnet arranged so that its lines of force pass through the disk, and the whole circuit is arranged so that no lines link with it. Therefore, according to the linkage school of thought, no e.m.f. can possibly be induced by turning the disk. But unfortunately for them the meter shows that it The thing with which my Belgian correspondent is. was confronted, although different in form, was obviously identical in principle, and was no mere theory or experiment but an actual machine used to generate current for actual electro-plating.

If the line-cutting advocates had been called upon to predict the result of the disk experiment, previously unknown to them, there might have been some hesitation and clearing of throats while they tried to decide whether the part of the circuit formed by the disk was or was not cutting the magnetic field. At first sight it might seem not, since no change in the form of the circuit takes place, and the copper in any one part of the disk is as good as in any other. But if members of this group were electron-minded (as the participants in the I.E.E. discussion apparently were not, for the word "electron" was hardly mentioned) they would realize that turning the disk carried the free electrons in the copper around with it, and so causes them to move in a magnetic field, and by using Fleming's right-hand rule (thumb indicating direction of motion and forefinger direction of field, then second finger shows direction of e.m.f.) they would correctly predict an e.m.f. along the radius of the disk crossed by the field.

Having tactfully allowed the linkage people time to think up a way of talking themselves out of the contradiction between their theory and this experiment, we come back to them and invite their comments on it. The I.E.E. discussion showed what at least one of them would say. He would describe the result as an anomaly, and shamelessly advocate keeping it as dark as possible, lest it confuse his students. I hope we all regard this reply as thoroughly unworthy and unsatisfactory and insist on something less ostrich-like. Pressed thus, some might allow it to be brought to the notice of their students, but only as a "special case" or "exception". But if nothing better can be said than this one would, I should think, be obliged to decide in favour of the line-cutting school, even though that meant accepting their curious pictures of lines cutting wires by springing out of them. Another group, represented in subsequent discussion by at least one very eminent authorityt, refuses to be disconcerted by this attack on the linkage position, but shows that the disk experiment is, after all, not an exception to it. They ask one first of all to substitute for the disk a spoked wheel, and then show that the sector-shaped circuits formed by pairs of adjacent spokes and the segments of rim joining them obviously do link with a varying number of magnetic lines as the wheel is rotated, and that a difference of potential is thereby set up between the two brushes. They point out that this state of affairs does not depend on the number of spokes, and that more can be added until finally they are touching one another all the way, and the wheel has become the solid disk of Faraday.

Having re-established the prestige of the linkage

[‡] "Apparent Failures of the Flux-Threading Rule," by C. G. Carrothers and R. O. Kapp, Bulletin of Electrical Engineering Education, June, 1954, pp. 7-12.

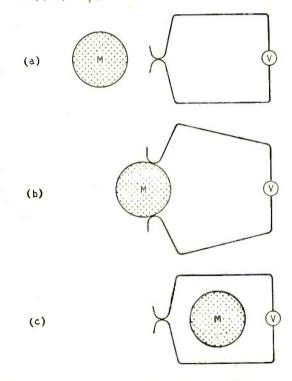


Fig. 3. M is a metal bar magnet which is pushed through the jaws of a spring clip forming a closed circuit. V is a sensitive voltmeter or galvanometer. Does it give any sign while the magnet is being inserted into the circuit? If not, why not? See Fig. 4.

school (and, we hope, expelled those members of it who disgraced it with their treacherous ostrich policy), they go on to conquer other supposedly fatal objections. One of the most interesting of these is Hering's experiment. It is performed with a circuit consisting of a spring clip, normally closed as in Fig. 3(a). The bar magnet M is then forced past the jaws (b) until finally it is inside (c). There is a complete circuit all the time, and clearly a large number of magnetic linkages are introduced into it, yet the most sensitive instrument fails to indicate any e.m.f. This, it is said by some, makes nonsense of the flux linkage idea. It certainly makes nonsense of something, and so it ought, for that something is a misconception of the linkage principle. The fallacy lies in looking at (a) and (c) only, which show an identical circuit with and without a linked field, and forgetting about (b), where the circuit is not identical. As Carrothers and Kapp put it, "the circuit in which one might expect a current to be induced is not there during the time that any inducing could occur."

When Is a Circuit . . .?

This matter of change of circuit needs careful watching, for some changes of circuit during a linking or unlinking process do not necessarily affect the observed e.m.f., and the distinction is sometimes rather a subtle one-as it is in the Hering experiment. For example, altering the shape or extending the length of a flexible lead from a transformer coil to a voltmeter doesn't prevent the ordinary linkage rule from being used to predict the voltage correctly. But the change in circuit during the (b) period in Fig. 3 does upset what might seem to be a valid application of the rule. This can perhaps be more easily seen in Fig. 4. The right-hand part of the double wire square at (a) is not linked with the flux passing through the magnet M. If now the switch is opened (b) the magnet can be moved through into the right-hand square (c) but doing so does not alter the number of lines linked with the circuit that then exists. If now the switch is closed (d) there is a closed circuit the same as in (a), but linking with flux that was not there before. Yet there was no stage at which one would expect V to give a reading.

The fact that in the Hering experiment the switchover is gradual makes no real difference. The process can be more exactly imitated by the arrangement in Fig. 5, in which the slider is moved from the position shown, where the magnet is not embraced by the circuit (the path through the resistance is dead-shorted by the direct path), to the other end, where it is. No one, surely, would expect moving the slider to set up a potential difference between a and b, such as certainly would be set up if a wire between a and b were moved across the pole face of the magnet.

Another demonstration in which the number of circuit linkages is increased by a sort of trick, without generating any e.m.t., is Blondel's experiment, shown in Fig. 6. Wire is wound from a metal cylinder, which acts as a short-circuit, to an insulating cylinder fitted with a metal slip-ring, with which contact is made by a brush B1. This cylinder is placed in an axial magnetic field. By rotating the cylinder, the number of turns linking with the field is made to increase gradually from none at all up to the maximum provided. Yet no e.m.f. is indicated. Nor should one be expected, for it is a sort of continuous Hering experiment.


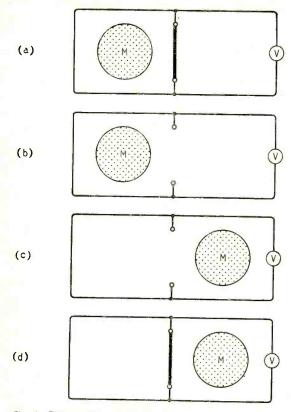


Fig. 4. This variation of the Fig. 3 experiment may make it easier to answer the questions about Fig. 3. If it doesn't, see Fig. 5.

What is the moral of all this? Of the people we questioned, who are right and who are wrong? And what about the people who don't seem to have been represented in our Gallup poll, who refuses to acknowledge the very existence of magnetic fields? Are they like those who hold on to the belief that the earth is flat, regardless of the clear evidence to the contrary? Or are they the only ones who are right?

Before we can answer we shall have to decide what, in this connection, "right" and "wrong" mean. If we think that any rule or theory or idea is-or could be-the right one, we had better think again. In such a question as deciding which of several men in an identification parade stole our wallet last night, it would be possible (whether by luck or good observation) to be right. But in such matters as stating precisely how electromagnetic induction works, nobody can be right, because there are no still more fundamental terms with which to describe the fundamental processes of nature. We can describe the construction and working of a machine, because it is made up of simpler parts that are familiar. But if we press the analysis back to such things as electrons we cannot say what they are made of. If we begin to describe an electron as "a very tiny particle" we are not really describing it, because one should immediately ask "What is a particle?" and the enquiry would never end satisfactorily, because we would be committing the logical sin of defining the obscure in terms of the more obscure. A particle, as commonly understood, is a more complex structure than an electron. If we could start with a knowledge about electrons and such things, then perhaps we could go on to describe

Fig. 5 (right). R is a resistor with a sliding contact which is moved from one end to the other. Do you still feel sure about Fig. 3?

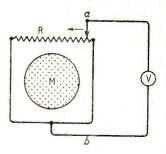

a particle of matter accurately. But even if one day we find that an electron is made of still simpler units, that will only transfer our ignorance from the electron to them.

A Cloak for Ignorance

It is the same with induction. When we talk about lines of force, flux, and even fields, we are using these terms to hide our complete ignorance of what is really happening. All we know is that when certain conditions are provided certain results invariably follow. And what we do in the science of the subject is to state as precisely as possible the relationship between cause and effect. To assist in this it is necessary for most people to use mental pictures or concepts. The test of such a concept is not whether it corresponds accurately with ultimate reality-we wouldn't knowbut whether it is (a) consistent with all observed behaviour, and (b) convenient for its purpose. Of these requirements, (a) might at first sight seem to be essential, but in practice, for the sake of (b), one often uses concepts that only approximately fit the facts, or fit only some of the facts; this apparently unscientific practice is allowable so long as the limitations are clearly understood by all concerned. The position is complicated, however, by (b) being so largely a matter of opinion.

Let's face it—we just don't know how or why it is that pushing a magnet into a coil of wire causes a voltmeter across its terminals to indicate. Probably no one will ever know. But all electrical engineers have to be able to make use of this fact to obtain desired results, such as providing light, heat, and television in our homes. Since it would be difficult to discuss such matters if blanks had to be inserted in place of words wherever our absolute knowledge was lacking, it is necessary to use concepts. To most

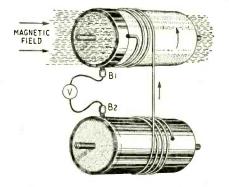


Fig. 6. This is a machine for causing an increasing number of turns to be linked with a magnetic field. Does this process cause V to read? If so, why? people, the concept of a "field"—a sort of sphere of influence—around a magnet renders it easier to discuss induction and to make the necessary calculations. Calling it a field does not in the very least increase our knowledge of it, or prove that it exists. But even if it could be proved that it does not exist, it might still be a good thing to keep it as a concept.

Spectacles for All

The concept of just a field is still too vague and shadowy for most people. So lines of force were invented. Now in so far as anything about a magnetic field can be known, it is known that lines of force do not exist. They are simply a means of showing on diagrams-or visualizing in the mind-the directions in which fields act. They also help to suggest, by their closeness together, the relative strength of the field. As great a mind as Faraday's was not ashamed to use them as a mental aid. In just the same way contour lines on a map help one to visualize the direction and steepness of a slope, but supposing that a magnetic field actually consists of lines is as sensible as supposing that a hillside consists of lines. Yet so firmly does the line idea get one that it is quite difficult not to imagine that if a cylindrical bar magnet were rotated about its axis its lines of force would rotate with it and generate an e.m.f. in a stationary circuit through which they passed. But if we think of the field as we should, as having at any point only magnitude and direction, we realize that turning the magnet does not alter either of these properties anywhere, so is incapable of inducing an e.m.f. in an external circuit (though the stationary field does generate an e.m.f. in the rotating metal of the magnet itself).

Calling the unit of flux a "line," as some people still do, so that magnets are bought and sold on a specification of the number of lines they provide, makes the line idea even more difficult to keep in its proper place. Calling it a maxwell was better, but one couldn't help remembering that 1 maxwell is equal to 1 line. Now that the maxwell has been superseded by the weber, which is equal to 10⁸ maxwells, there may be a better chance of thinking of flux as a continuous magnitude, like length or inductance.


To Clerk Maxwell, Faraday's lines seemed rather quaint; as a mathematician he found a mathematical symbol more appropriate and precise. Mathematical symbols themselves are only concepts, of course, but it must be admitted that they are the most precise and flexible way of stating generalized results of observations. For example, observations on electrons have shown them to have properties that defy any "mechanical model" to imitate, but can be expressed mathematically. Unfortunately only people with exceptionally mathematical minds can get any enlightenment from these expressions. To generalize the observed facts about induction by magnetism, even such a lucid writer as Faraday required a sentence of no fewer than 126 words. Mathematically the same thing can be stated much more precisely thus:

$$\oint \epsilon.dl = -\frac{d}{dt} \iint B.da$$

But there are plenty even of qualified electrical engineers, not to mention elementary students, who fail to appreciate this way of putting it. However, according to the author of the paper discussed at the I.E.E., those who can should escape falling into the silly misunderstandings of those of us who through

mental incapacity are obliged to make do with visual concepts like the cutting or linking of flux lines. He showed that the foregoing equation produces two terms, one corresponding to the transformer or linkage-changing effect, and the other to the motional or cutting effect, and in any particular case one of these effects is often absent. No doubt he always gets the right answers.

But some other mathematician might come along and express what we know about induction in some other way, perhaps without reference at all to magnetic We poor fields, and also get the right answers. morons who haven't a clue to these refined methods, but use either or both of the two flux rules, provided we use them with discretion and beware of trick cases like Hering's, can also get the right answers. Perhaps one day we may meet a Viet Namese refugee who gets the right answers by manipulation of an abacus and a prayer wheel. The point is that as long as each of us understands what we are doing, and can get the right answers by a process that to us makes sense, it is mistaken zeal to insist that everybody must do it in Agreed that it would be convenient if everybody used the same method. Evidently Carrothers and Kapp think so, for they have expressed the view that it would have been better if the flux-cutting rule had never been thought of! Nevertheless, while like them I find flux-linking the most convenient and reliable way to look at induction problems in general, I am not sure that it is invariably simpler and more natural than flux-cutting. All such concepts are spectacles to aid our limited mental vision. I would hesitate to insist that everyone must use a replica of mine.

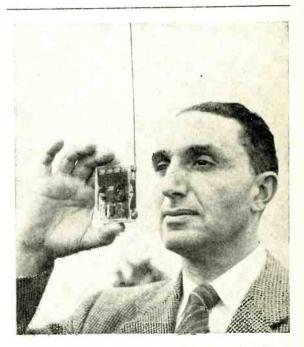

ONE way of solving the battery problem—but perhaps more suitable for nomadic Arabs than for stay-al-home Britons is exemplified by this new transistor transmitter, which is powered entirely by sunlight through the medium of selenium cells. Built by Edward Keonjian (General Electric Company of America), it has a range of about 100ft.

Measurement of Rise-Time

Simple Circuits for Displaying **Pulse** Characteristics

By E. G. DANN

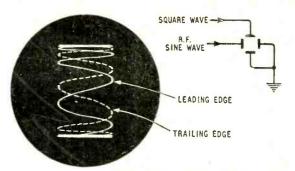


Fig. 2. (Above) Display obtained when a sinusoidal r.f. voltage is applied to the horizontal deflecting plates.

the applied radio frequency, the rise-time may be accurately determined. (See Fig. 2.) For example, if a stationary trace with a convenient number of vertical waves results when the applied frequency is 1.8 Mc/s, the rise time is 1/1.8N microseconds, where N is the number of whole waves displayed.

Bunching of the cycles at the top of the pattern is an indication of slower rate of rise of the upper portion of the leading edge of the square wave.

A simple pattern of the kind shown in Fig. 2 will result only

when there is an integral ratio between the squarewave frequency and the applied radio frequency, as follows from the normal behaviour of Lissajous figures.

The insertion of a filter in the lead to the oscilloscope X plates will improve the purity of the r.f. cycles displayed by elimination of harmonics in the output of the r.f. generator.

Due to the fact that the square wave must necessarily have a negative-going excursion the pattern will ordinarily show a return trace and this will afford observation of the fall-time. If, however, the oscilloscope has provision for blackout of its normal fly-back and remains synchronized with the square wave, the return trace will not normally be displayed.



A PARABOLOID four feet in diameter is mounted on top of this 60-ft mobile extensible mast which the B.B.C. has recently introduced for television outside broadcasts. The aerial, which can be remotely rotated through 360°, can be adjusted to within + I°. When extended the mast is self supporting but provision is made for stay wires if needed.

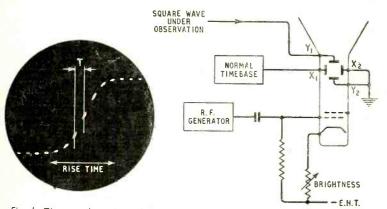


Fig. 1. Time markers derived from the positive half-cycles of a radio-frequency input to the c.r.t. grid.

HE experimenter may on occasions wish to make some observation which is beyond the normal capabilities of his test gear, either as regards the range of measurement or the degree of accuracy available. In these circumstances it is necessary to find some method by which existing equipment may be used to obtain the desired result.

The writer recently needed to make a measurement of the rise-time of the output of a multivibrator, and, while the repetition frequency could be ascertained with a reasonable degree of accuracy, the time-base of the oscilloscope used was insufficiently well calibrated to measure the time of rise of the positive excursion of the square wave.

One well-known method of providing an accurate time scale is to feed a radio frequency to the grid of the cathode-ray tube on which the waveform is displayed. This results in a brightening of the trace over the positive half-cycles of the r.f. wave as shown in Fig. 1. Since the distance between dots corresponds to the periodic time T of the r.f. wave, a fairly good assessment of the rise-time can be made.

Sinusoidal R.F. Time-base

A more accurate method of measuring rise-time devised by the writer is one in which the normal time-base of the oscilloscope is replaced by the output of an r.f. generator. Since the leading edge of the waveform under investigation has some pretensions to linearity the resulting pattern is a series of waves with a vertical time axis. Thus, by observation of the number of cycles displayed and from knowledge of

Workshop R-C Bridge

Incorporating a 1,000-c/s Source and a Protected Sensitive Indicator

By B. T. GILLING

HE instrument to be described was designed by the writer for quick but searching tests of capacitors and resistors in the workshop. It is actually two test instruments in one, namely a resistance-capacitance bridge and a direct-reading leakage indicator for testing electrolytic capacitors at voltages up to 500. As will become apparent, one of its features is its robustness. Although extremely sensitive the instrument is so designed that there is no possibility of damage by overload, even if it is carelessly used.

The full circuit diagram is shown in Fig. 1 and can be divided into five parts as follows: signal source, bridge, bridge indicator, leakage indicator and power supply. These will be dealt with in turn. It will be seen that only one pair of test terminals is used, the required facility being selected by the three-pole switch, S4.


Signal Source.—An alternating-current source is needed, and it is possible to obtain this from a special winding on the mains transformer, but the reactance of capacitors in the picofarad range to 50 c/s is inconveniently large. An R-C oscillator of a very simple design is used in the instrument and the circuit values shown give a frequency of about 1,000 c/s when the voltage at the h.t. decoupling point is 150. The value of the $68-k\Omega$ decoupling resistor may need modification to obtain this voltage.

The output waveform and amplitude are controlled by the cathode resistor, and some slight adjustment of this may be needed. The output transformer T1 is a small 6:1 intervalve type using the high-inductance winding as primary. Any small transformer of about this ratio is suitable provided that the high-resistance winding will carry 5 mA. A Wearite transformer Type 262 is actually used and gives an output of 18 volts peak across the 1,000-ohm ratio arms. A transformer T2 of the same type is used at the output of the indicator.

The Bridge.-The ratio arms consist of a Colvern 1,000-ohm potentiometer Type CLR 7001/15. The standards are selected by switch S3, their tolerance and the number used is limited only by expense, but the six shown give an adequate coverage. Should a standard other than one of those included be needed at any time it is connected to the "Match" terminals. Cracked-carbon close-tolerance resistors are quite cheap, but really accurate capacitors are, unfortunately, costly. A point to remember when buying them is that a capacitor supplied to a definite value is always expensive, but one close to the desired value and very accurately calibrated is less so. For example, it will be less expensive to accept a capacitor from stock calibrated at, say, 0.0988 μ F than to insist on one of 0.1 μ F $\pm \frac{1}{2}$ per cent. Provided the value is low it can always be made up to the desired value with added capacitance.

The 100-ohm variable resistor in series with the $1-\mu F$ standard is to enable a sharp balance to be obtained with capacitors having appreciable losses. If desired this control can be calibrated by the experimenter to give an indication of the relative magnitude of the losses.

A decade resistance box must be considered essential for calibrating the ratio arms and the use of one can usually be obtained at a local technical school, or a suitable "pproach will often get the co-operation of

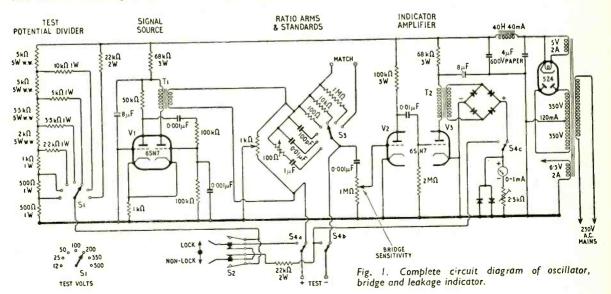

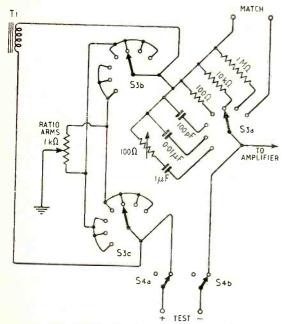


Fig. 2. The addition of two wafers to switch S3 in Fig. 1 permits the use of a single calibration for the ratio-arm scale.

R.E.M.E. or even of a Post Office engineer. At any rate, it is not the insuperable difficulty that it is often made out to be.

The circuit, as set out in Fig. 1, will need two scales on the ratio arms, one the reciprocal of the other, since low resistance and high capacity will be at the same end. Since the resistance element is linear and very evenly wound, the ratio arms can be reversed for capacity measurement and only a single scale will be needed. This is carried into effect as shown in Fig. 2 by using two additional wafers on the standards switch. It is an embellishment well worth incorporating as it simplifies the use of the instrument considerably.

Indicator.—The indicator consists of two parts, the amplifier and the meter. The first comprises two valves operated at zero bias. As the ratio arms move away from the null point the signal to V2 increases and when it exceeds a certain amplitude V2 and V3 act as limiters. The output waveform from the limiters is very distorted but this is of no consequence since the important part of the signal is around the point of balance and then its amplitude is too small to overload the valves.

The output from the amplifier is passed through a step-down transformer, of the same type as that used in the oscillator, to a bridge rectifier and thence by switch S4c. to the meter. This meter movement has a full-scale deflection of 1 mA and has two halfwave metal rectifiers connected back-to-back across These act as a variable shunt. When a low it. voltage is applied to it a metal rectifier has a fairly high resistance, but as the voltage is increased so the resistance decreases shunting a greater proportion of the current away from the meter. The second rectifier section is to protect the meter from any reverse current which may appear in certain conditions when it is being used as a leakage indicator, The 2,500-ohm variable resistor in series with the


meter is to enable its maximum deflection to be adjusted to full scale when setting up the leakage indicator with 25 mA in the shunted circuit.

The rectifiers are both by Westinghouse, Type 4/1A is used as meter rectifier and Type 2/6A, with its outside ends connected together, as the shunt. Alternatively, rectifiers can be made up from an old copper-oxide unit; the bridge consists of one disc per section and the shunt of six per section with one set reversed. No cooling fins are needed.

Fig. 3 illustrates the action of the limiters and rectifier shunt combined. Balance is assumed at the centre of the ratio arms scale and curve A shows the output with no limiting action when care is taken not to overload the meter. The curve is very open and the null point not at all clearly defined. If the balance is to be made sharper a curve such as B is needed which assumes amplification but no limiting. This gives an excellent indication of balance; but when the arms are away from the null point the meter will be hopelessly overloaded and damage will inevitably result. With the limiters in use curve C is obtained, which has the sharpness of B, but which at no time exceeds the full scale deflection of the meter.


In practice the instrument gives a very sharp balance indeed. With the sensitivity control at maximum, as the ratio arm pointer is swung round the dial the meter remains at nearly its full scale deflection until the point of balance is reached. Then the meter moves from full scale to zero and back to full scale again in a matter of five to ten degrees. The sharpness of balance is maintained on all scales, and at the lower end of the 100-pF one it is easily possible to measure to within 0.5 pF. A point to remember when measuring these low capacities is that the residual capacity of the test leads must first be measured and this figure subtracted from the measured value of the component. On all the scales for ease of searching the sensitivity control needs to be set well back and only increased when a really close balance is required.

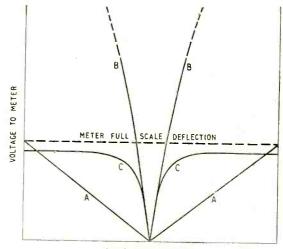The total deflection of the meter in out-of-balance conditions is controlled by the anode voltage of V3,



RATIO ARMS POSITION

Fig. 3. Indicator response, with meter only (A^{\prime}) , with amplification (B), and with amplification and limiting (C).

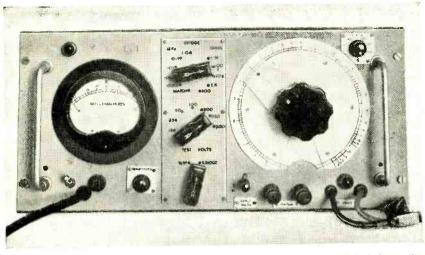

Layout of controls on the front panel. Black and red leads are used to indicate the polarity of the test clips.

and some slight adjustment of the value of the decoupling resistor to this valve may be needed. This should be done after the leakage indicator has been set up.

Leakage Indicator.—Provision is made to test the leakage of capacitors, especially electrolytics at voltages from 12 to 500 and these are selected by switch S1. Potential points are taken from the voltage divider chain across the h.t. supply and series resistors are introduced between these points and the selector switch contacts to limit the current flowing to 25 mA in each range when the test terminals are short circuited. This makes a limiting safeguard without impairing the value of the test, since, although at high current leakages the voltage at the test terminals is reduced greatly, as the leakage current decreases the voltage will rise until at 1 mA and under it reaches the full indicated potential.

The selected test voltage is applied to the capacitor by switch S2. This is a three-position key switch with one non-locking position, allowing the voltage to be applied either momentarily or for "soak" tests and the forming of electrolytics. In the central off position of the switch a $22-\Omega$ resistor is connected across the test terminals to make sure that the capacitor under test is discharged.

Leakage is measured directly on the bridge indicating meter. The shunt rectifier is left in circuit and the meter scale calibrated by hand in milliamps. The scale is roughly logarithmic, 0-1 mA occupying approximately the first third of the scale, 1-10 mA the second third and full scale being set at 25 mA by the $2,500-\Omega$ series resistor. As an alternative to hand calibration, a graph can be made of the new scale against the original linear one.

It will be seen that the instrument when used as a leakage indicator is immune from overload damage irrespective of the test voltage applied.

Power Supply.—A standard 350-0-350 volt, 120 mA transformer is used. At the light total h.t. current of 40 mA a $4-\mu$ F reservoir capacitor gives a smoothed h.t. voltage of 500. At this voltage it is advisable to use paper capacitors in both the reservoir and smoothing positions.

General.-The photograph of the author's instru-

ment shows that it has more standards than are actually necessary, and a 3¹/₂in meter which happened to be available was incorporated although a smaller one would have given perfectly satisfactory results. The "Test" conbrought are nections through the panel and of about four consist inches of flex ending in crocodile clips. This is a much more convenient method than the conven-The tional terminals. method of figuring the dial calibrations can be seen in the photograph. The figure 1 at the middle top of the scale corresponds with the standard in use. No powers of 10 are indicated, each decade starting with 1.

Over a period of years this method of calibration has been found to be far less confusing than the normal method in which a dial of this type would be calibrated 0.01-100. The added ciphers only lead to difficulties of interpretation.

BOOKS RECEIVED

Mathematics of Engineering Systems (Linear and Non-linear) by Derek F. Lawden, M.A. Treatise on differential equations and their solution by classical and modern methods, with examples of their application to problems arising in the design of electrical networks, amplifiers, oscillators and servomechanisms. Pp. 380+viii, Figs. 97, price 30s. Methuen and Company, Ltd., 36, Essex Street, London, W.C.1.

Active Networks by Vincent C. Rideout. Textbook of basic principles and formulae for students of communication engineering, including chapters on negative feedback, transient response of amplifiers, demodulation wave-shaping circuits, noise and information theory. Pp. 485 + xvi; Figs. 364, price 42s. Constable and Company, Ltd., 10-12, Orange Street, London, W.C.2.

Valves for A.F. Amplifiers by E. Rodenhuis. Description of relevant Philips valve types, general hints on amplifier construction and eight complete circuits for amplifiers with outputs from 3 to 100 watts. Pp. 144 + viii; Figs. 97. Price 10s 6d. Cleaver Hume Press, Ltd., 31, Wrights Lane, London, W.8.

The Inventor of the Valve, by J. T. MacGregor-Morris, D.Sc. (Eng.), M.I.E.E. A biography of Sir Ambrose Fleming, published to celebrate the 50th anniversary of his first valve patent. Pp. 124+xviii; Figs. 22. Price 10s. The Television Society, 164, Shaftesbury Avenue, London, W.C.2.

Audio Frequency Power Measurements, No. 8 in the series "Notes on Applied Science" published by the National Physical Laboratory. Discusses the basic principles and describes wattmeters of the electrostatic, thermal and electrodynamic type, their advantages and disadvantages. Pp. 16+iv; Figs. 8. Price 1s. Her Majesty's Stationery Office, York House, Kingsway, London, W.C.2.

Transistors and Crystal Diodes, by B. R. Bettridge. Simple explanation of how they work, and how they can be applied by the experimenter in sound receivers, television sets and amplifiers. Pp. 72; Figs. 47. Price 5s. Norman Price (Publishers), Ltd., 283, City Road, London, E.C.1.

Wireless, by Frederick Roberts. History of the development of communication without wires, written for use in schools. Pp. 98; over 60 illustrations. Price 5s. The Educational Supply Association. Ltd., 181, High Holborn, London, W.C.1.

"Piped" Scanning Waveforms

Unusual Wired Television System Giving Simpler Receivers

By E. J. GARGINI*

HE commercial success of sound broadcast relay companies can be attributed to the simplicity, and hence low initial and maintenance costs, of the terminal equipment. The design of television distribution equipment to the same order of simplicity is clearly desirable so long as the sending equipment and network costs do not become limiting factors. The system described here is based on the principle that terminal equipment should not include circuitry which may be transferred to the sending end, although at the same time this transference should be halted when it comes to power distribution.

Fig. 1 is a circuit of a vision terminal unit which embodies this principle. Two r.f. signals are transmitted over the input cable together with sound signals at service level. A choke assembly separates the sound signals (in a separate control unit) which are then applied to the loudspeakers. The higher frequency r.f. signal is a 5.42-Mc/s carrier wave modulated with picture information only. A vestigial sideband transmission is used, the upper sidebands being suppressed at the sending end. The lower frequency signal is a 1-Mc/s modulated carrier wave, and this effects the double-sideband transmission of a modulated waveform which includes line and frame scanning signals.^{1'2}

By passing the demodulated scanning waveform through a low-pass filter a frame scanning waveform is developed, and by passing the demodulated waveform through a high-pass filter a line scanning waveform is obtained. Input filters at the terminal unit separate the two vision signals. The video carrier modulated signal is amplified in the N309 and then applied via a low-impedance coupling circuit (L, and L.) to the grid of the c.r. tube. Adjustment of the tube bias to the condition that anode current only flows during positive-going carrier pulses results in the display of monochrome pictures at a dot spacing,

* Electric and Musical Industries. This article is based on a lecture which the author gave recently to the Tevision Society. British Patent 704141.

² British Patent Application No. 1658/53.

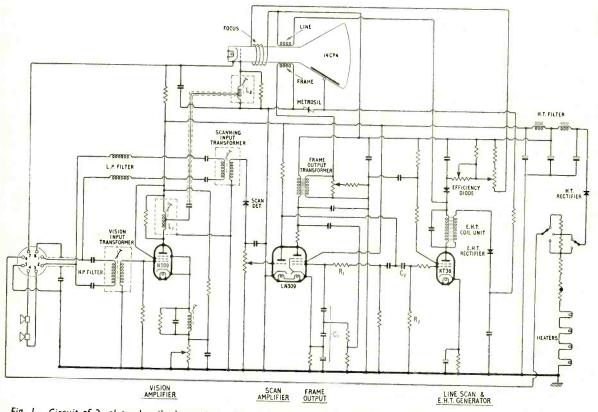


Fig. 1. Circuit of 3-valve subscriber's receiver. The eight contacts of the input plug on the left carry the following: 1 and 2, vision and scanning signals on carriers; 3 and 4, sound at speech-coil level; 5 and 6, mains supply; 7, brightness control voltage: 8, earth connection.

that is, the line is broken up into dots which correspond to the 5.42-Mc/s carrier waves. This tends to render the line structure less prominent.


The scanning signals, after rectification at a XT1 crystal diode and amplification by the triode section of the LN309, are applied to the network R_1 and C_1 . The composite signal is integrated by this RC filter and the resulting frame sawtooth is applied to the pentode frame output stage. The composite scanning signal is differentiated by the high-pass filter C_2 R_2 which results in the production of a line-scanning sawtooth waveform. This is applied to the KT36 line output valve.

This output valve has in its anode circuit directly coupled scanning coils which are shunted by an efficiency diode circuit comprising a diode in series with a resistor shunted by a capacitor. The operation of this circuit is conventional. The diode circuit rectifies the negative overshoot which appears at the valve anode at the termination of the long flank of the sawtooth grid potential. The resulting current produces the first part of the line scanning signal through the coils. The initial positive rise of potential is applied to a section of a low-pass filter which, after rectification, provides e.h.t. for the c.r. tube.

Simple Adjustment

It will be noted that if the unit is constructed for a.c./d.c. mains operation and capacitance-coupled high-impedance frame coils are used, no iron-cored transformers are necessary. Moreover, no synchronizing controls are necessary and the subscriber only has to adjust the focus, contrast and brightness. As the d.c. level is fully maintained and zero carrier can

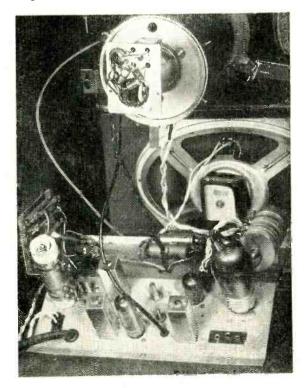Rear view of 14-in cabinet-model subscriber's receiver, showing the 3-valve chassis of which the circuit is given in Fig. 1.



represent black level, the separate brightness control may in certain circumstances be dispensed with.

This simplification has not been obtained without some complication of the sending and network equipment. Fig. 3 is a block diagram of the main waveform generator at the sending end. Fig. 2 (a) illustrates the envelope shape of the carrier wave when the carrier has been modulated by the frame scanning signals of the composite waveform. They are generally of a pulse-like character with interruptions between the pulses, which reduces the envelope amplitude to about 15% of the peak amplitude of the frame scanning signal. These interruptions correspond to the frame return intervals.

The line scanning signals are shown in Fig. 2 (b). These are of constant amplitude and of a sawtooth character. They comprise a linearly rising portion giving way to a ripple of between 50 and 60 kc/s. Interruptions in the waveform correspond to the line return intervals. When the line and frame signals are combined the line frequency components occurring during the frame flyback period are considerably reduced in amplitude. During the curved portion of the frame waveform the line scanning signals modulate the carrier wave to 90% at the beginning of the portion and to 60% at the end.

In Fig. 3 the input signal is the complete video signal obtained from a receiver at the sending installation. A circuit suppresses the video signals, leaving the sync pulses, which are fed in parallel and with negative polarity to two groups of circuits, one for line waveforms (above) and the other for frame waveforms (below). In the line waveform channel pulses are fed to a valve through a differentiating circuit which produces alternative negative and positive spikes at the beginning and end of the sync pulses. The positive spikes are removed by grid current in the valve, leaving only the negative spikes. The positive spikes produced at the anode of this valve are applied to a delay line with a delay of 90 μ sec.

Each positive spike at the anode of the valve is followed 90 μ sec later by a spike of negative polarity. The resultant output waveform at the anode of the valve is applied to the grid of another valve, which removes the positive spikes by grid current limitation and amplifies the negative spikes to produce a positive spike output, 90 µsec delayed with respect to the sync pulses received from the vision suppressor. The effect is that the spikes produced are 10 µsec in advance of the received pulses. This advance is provided because the video signals are relayed as modulation of a carrier wave of higher frequency than the scanning waveform signal carrier. Consequently the scanning signals are liable to be delayed in the transmission system to a greater extent than the video There may also be relative delays in filter signals. circuits at the terminal unit.

The 10-usec advance represents the greatest relative delay likely to be encountered. The advanced pulses are next fed to a phase discriminating circuit included in a flywheel sync circuit which also includes a cathodecoupled sine-wave oscillator. The voltage output of the discriminator circuit controls a reactance valve and thereby the frequency of the oscillator in such a manner as to obtain accurate frequency tracking between the oscillator and the line frequency of the television programme.

Negative pulses set up at the anode of the oscillator valve are applied to a differentiating circuit. The differentiated output of negative and positive spikes


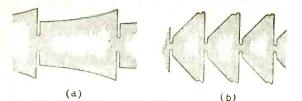


Fig. 2. (a) Envelope shape of the frame scanning signal modulated on its carrier wave, (b) envelope of the line scanning signal on its carrier.

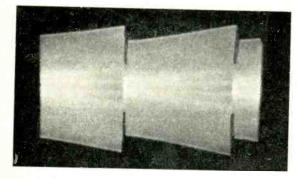

Composite scanning waveform from the sending generator, produced by combining the line and frame waveforms in Fig. 2.

are applied to the grid of a valve forming part of a sawtooth waveform generator. This valve is normally biased off except on the occurrence of positive spikes at its grid. These positive spikes discharge a capacitor in the circuit and generate the short flank of a sawtooth waveform. During conduction of the valve an anode-cathode potential drop produces one of the interruptions in the line scanning signals (Fig. 2 (b)).

The waveform at the anode of the sawtooth oscillator is applied to a shaping circuit which has the effect of providing a relatively sharp transition from the interruption to the linear part. The waveform is then fed through two cathode follower amplifier stages. The output from the first of these is adjustable so that the amplitude of the line scanning signal may be adjusted without introducing waveform distortion. The second cathode follower stage acts as a line and frame combining stage.

Frame Waveform Generator

Returning now to the vision suppressor, the complete sync pulse train from this circuit is also applied to the first valve in the frame waveform section. This only in response to the superimposed pulses. Anode current, therefore, only flows when the frame sync pulse occurs.

The output signal from the limiter is applied to a differentiating circuit and the differentiated pulse is used to fire a blocking oscillator valve. This discharges a capacitor which is charged through a resistor during the interval when the valve is blocked. The capacitor is connected in series with a variable resistor which produces the interruption in the frame scanning signals of Fig. 2 (a). The waveform set up at the anode of the blocking oscillator valve is linearized in a shaping circuit and is finally applied to two cathode follower stages. A common cathode resistor functions as a combining resistor for the cathode follower output stages of the line and frame sections.

A low pass filter connected between the line output stage and the modulator input cuts off in the region of 300 kc/s, and its function is to prevent high harmonics of the line scanning signals from beating with the scanning carrier. A low pass filter following the frame output stage cuts off in the region of 3 kc/s and prevents line signals from passing into the frame circuits.

The combined line and frame scanning signals are now fed to the cathode of an amplifier valve. The output from this stage is connected to the suppressor of a modulator valve which has a carrier oscillation at 984.7 kc/s applied to its grid. This is derived from a conventional crystal oscillator. The scanning signals fed to the suppressor of the modulator valve are of such an amplitude that the anode current is cut off during the interruption in the frame scanning signal. In this way the line scanning signals are suppressed during the flyback time.

The output of modulated carrier frequency signals from the modulator valve is fed by a transformer to an r.f. amplifier stage. The output signal is developed across a tuned circuit which forms part of a wide band filter network A fraction of this output is taken from a tapping point of the circuit and is applied by a capacitor and inductance to the input of a cathode follower and to a diode. These circuits constitute a π -type filter whose output is rectified by the diode. The load circuit of this diode comprises a low pass filter, the output of which is fed to the control grid of the modulator input valve. The signals fed to this valve are modulation frequency components which provide negative feedback, thereby linearizing the modulation process.

A low pass filter prevents feedback of carrier frequency signals and its pass band is approximately that of the modulation frequency band. The filter begins to attenuate at about 50 kc/s, and the reduction of negative feedback at these frequencies gives pre-

has a delay line in its anode circuit which causes the valve to function as a frame pulse The broad separator. pulses which constitute the frame pulse in the broadcast waveform have superimposed on them reflected pulses from the delay line, but the narrow line sync pulses have not. The output from the first stage is fed to a limiter valve which conducts


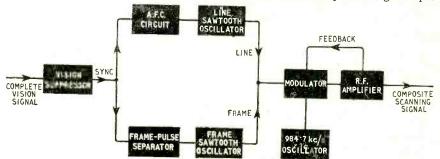


Fig. 3. Simplified block schematic of the waveform generator at the sending installation.

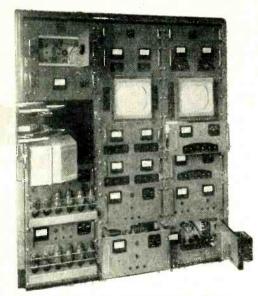

Racks of equipment at the sending installation.

emphasis of the higher frequency components of the line scanning signals. This produces the ripple shown in Fig. 2 (b). A series capacitor reduces the feedback at low frequencies and produces the upward curvature of part of the frame scanning signal in Fig. 2 (a).

The pre-emphasis in the wave shape Fig. 2 (a) of the frame waveform serves to correct for the finite inductance of the practical transformer in the receiver circuit, Fig. 1. The ripple in the line scanning waveform Fig. 2 (b) serves two purposes. It enables more effective use to be made of the scanning carrier and sharpens the cut-off of the KT36 in Fig. 1 produced by the waveform interruption. A sharp cut-off is required to permit the production of high e.h.t.

The ripple in the waveform does not produce "banding" in the picture since it exists only at a time when the KT36 is taking grid current. By virtue of the filters R_1C_1 and R_2C_2 in Fig. 1 the whole of the scanning signal waveform is integrated in the capacitor C_1 (the effective capacitance of all the capacitors in the grid circuit to earth), the line signals having negligible effect on the voltage across it.

The scanning signals from the waveform generator are amplified to a 9-watt level and applied to a low pass filter. Vision signals after demodulation are remodulated on to a 5.42-Mc/s carrier wave; these signals need contain no sync pulses. They are also amplified to a 9-watt level and are fed through a combining filter network which includes a section to which the scanning signals are applied. The composite signal is then combined with sound signals at service level and applied to the line.

Safety Devices

Under fault conditions or at the end of a broadcast a d.c. potential is transmitted from the sending equipment to take out of circuit all repeaters and any subscribers' equipments which may have been left switched on. At the subscriber's premises it operates a small relay in the control box. Another safety device is a resistor connected between the grid of the receiver c.r. tube and true earth which serves to inject a con-


siderable hum into the picture if the subscriber has inserted his mains plug so that the chassis is connected to the live conductor instead of to neutral.

The receiver in Fig. 1 requires at least a 100-mV vision signal and a 200-mV scanning signal. As the sending equipment produces a 30-volt vision signal the total insertion loss must not exceed 50 db. The total effective attenuation of an equalized network using 22 s.w.g. cable is approximately 4 db per 100 yards, which may be taken to include the insertion loss of other subscribers. In the spur cable to the subscriber's down lead transformer, 14 db is the minimum attenuation that can be tolerated without producing a noticeable mismatch. The balance of 36 db may be shared between the transfer loss of the main feeder to spur transformer and the effective cable attenuation. Assuming a transformer loss of 16 db, the remaining 20 db may be accepted as the cable attenuation of a 500-yard cable run and at least six repeaters would be necessary to cover a square mile area

If the terminal unit sensitivity was 10 mV (on vision) the planning loss would be 70 db and the cable run could be extended to 1,000 yards. At least two repeaters would be required to cover a square mile area. The purpose of this calculation is to show that there must be a cost compromise between terminal unit simplification and the number of repeaters required in a given area.

Higher Sensitivity Receivers

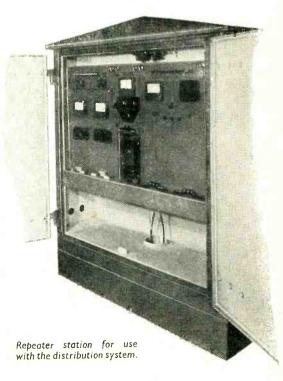The position is further complicated by the fact that if the number of subscribers is low the cost of the repeaters becomes the limiting factor. One solution is to adopt the 70 db planning figure, which entails the use of receivers with 10-mV sensitivity over part of the area, and then use low-sensitivity receivers in



the area close to the repeating equipment. A 5-valve receiver was used in North London in a field test of the system and this had a maximum sensitivity of 5 mV at vision frequencies. A receiver of this sensitivity was chosen because it was most likely to indicate the degree of interference from all sources.

The equipment field tested was primarily designed for single-channel operation. A number of proposals have been made for multi-channel operation. The latest high-grade cables have a cross-talk factor of the order of 50 db at 5.42 Mc/s at the end of a 1,000-yard run and are very similar to existing cables, although manufacturing tolerances have been reduced. A modification of the present system for multi-channel operation uses cables of this type. It employs quadrature transmission of vision and scanning signals in such a way that the resulting cross modulation takes the form of an interfering phase modulation of the desired signal. The effect of this phase modulation is negligible.³

All network transformers and equalizers in the system described cover a band between 0.7 Mc/s and 6.5 Mc/s. It is possible that the vacant band between 1.2 Mc/s, the top end of the scanning signal spectrum, and 2.7 Mc/s, the lower end of the vision signal spectrum, could be used later for colour television.

Finally, I wish to thank the engineers of E.M.I. and B.R.S. whose co-operation has made possible the practical investigation of this type of wired television distribution system.

³ British Patent Application No. 14511/54.

Lacquer Film Capacitors

Development of Sub-Miniature Units for Use with Transistors

EXTREME miniaturization of capacitors for lowvoltage operation for use in equipment employing transistors depends to a large extent on the ability to produce very thin dielectric films which are strong enough to withstand the various processes involved in the manufacture of capacitors.


Ceramics of very high dielectric constants, say of several thousand, offer only a partial solution since there are practical limitations to the extent to which such materials can be reduced in thickness and still be usable in capacitors. Generally speaking the upper capacitance limit is about $0.01 \,\mu\text{F}$ for this type of capacitor, so where larger capacitances are required the wound type, typified by the rolled-paper and metal-foil pattern, offers many advantages.

Recently some work has been done in the Bell Telephone Laboratories in America on the production of extremely thin lacquer films suitable for use in the manufacture of the wound type of capacitor. A paper published in the December, 1954, *Proc.I.R.E.* under the title "Miniature Lacquer Film Capacitors" gives some interesting details of the method employed and of the characteristics of the sub-miniature low-voltage capacitors developed by this means.

The lacquer films are normally too fragile to be self-supporting and to withstand the metallizing, trimming and other processes entailed in the manufacture of the capacitors. The film is therefore formed on a supporting base, or carrier, and remains so supported right up to the final winding process.

The carrier, for which ordinary capacitor paper tissue may be used, is first coated with a "parting layer," the purpose of which is to enable the processed lacquer film to be separated easily from the carrier when the time arrives. If a carrier were used from which the film would naturally strip easily then there would be no need for a "parting layer." When employed, the "parting layer " must consist of a material which is not attacked appreciably by the solvent of the lacquer, or by the lacquer itself.

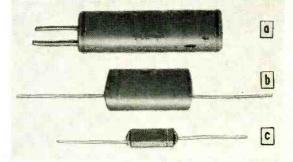After depositing the lacquer film on the prepared carrier, it is metallized and the strip is trimmed and cut to the width required. During the final winding process the processed film is separated from the carrier by winding the film on to the capacitor mandrel



Steps in the miniaturization of capacitors. All units are $2 \mu F$ and (a) is paper and metal foil construction, (b) is metallized paper and (c) is the new metallized lacquer film type. The largest capacitor is $2\frac{1}{2}$ in long.

and the carrier on to another mandrel of the same winding machine.

Assuming a lacquer film 0.1 mil (one tenthousandth of an inch) thick is used, it is said to be possible to produce a metallized lacquer film capacitor for low-voltage operation which is only 1/6 to 1/7 the size of the smallest metallized-paper type of the same capacitance.

The illustration, taken from *Proc.I.R.E.*, shows some recent advances in miniaturization of capacitors. All units are of 2μ F capacitance and (a) is an early style made from two layers of 0.3-mil paper and aluminium foil, (b) is a 0.3-mil metallized paper capacitor and (c) is the 0.1-mil metallized lacquer-film type described here.

Tests over a period of some 2,000 hours are said to show satisfactory stability for this style of construction, while during the tests a counter circuit detected only a small number of punctures, which, incidentally, are self-scaling as with the metallized-paper type of capacitors. This was with a test voltage of 120 V d.c.; with 80 V d.c. all dielectric break-downs were eliminated so that 50 V d.c. would be a conservative rating for this type of capacitor. It will satisfy all or most present requirements of transistor circuitry.

RECORDING TOPICS


Some Factors Influencing the Quality of L.P. Discs


By O. J. RUSSELL, B.Sc., A.Inst.P.

ROM correspondence arising out of my recent comments on recording matters¹, several interesting points have arisen. Accordingly something of a rider to the previous article appears in order, particularly as interesting information has been supplied by a professional recording engineer, who wishes to remain anonymous.

The first happening of interest is that many firms are adopting a standard playback characteristic. This characteristic, which is not very different from the old A.E.S. playback curve previously given, will be variously known as the "new" A.E.S. curve, the NARTB curve and the R.C.A. "Orthophonic" curve. The playback characteristic is shown in Fig. 1(a), and it is very similar to the "old" A.E.S. curve. Suitable compensating circuits are given in Figs. 1(b) and (c).

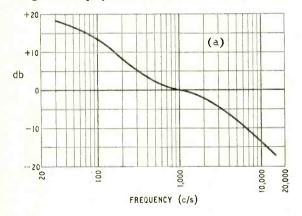
This is a valuable measure of standardization, although not as complete as some might wish. Briefly the curve will apply for all American l.p. and "s.p." (78 r.p.m.) recordings, but the EMI group and the Decca group it is understood will continue to use their present characteristics for 78-r.p.m. recordings while using the new playback curve as a basis for l.p. record-




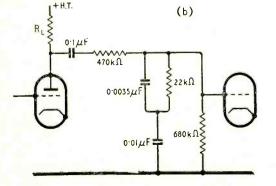

ings. No agreed "zero hour" exists for this changeover, and in fact some firms made the change in December, 1954; during 1955 most of the others will have followed suit. As the new playback characteristic (like the earlier A.E.S. curve) is virtually a "universal" curve, it does in fact compensate satisfactorily for almost all l.p. characteristics previously employed, and also for 78-r.p.m. records employing "top boost," with the possible exception of the Decca "ffrr" 78-r.p.m. characteristic. Thus a single fixed equalizer can be employed in the U.S.A., and with an adjustable tone control would suffice for British records with the exception of some pre-war recordings. However, many virtuoso pre-war recordings have been re-issued in l.p. form, and the recent drastic removal of many noteworthy pre-war recordings from the 78-r.p.m. lists may be an indication that these may be dubbed on to l.p. discs.

Considerable numbers of pre-war recordings have already been dubbed on to l.p. records. The frequent observation that the l.p. dubbing supplies superior quality to the original pressings has been explained by my professional informant. The l.p. discs are frequently made by playing back the actual 78-r.p.m. metallic positives ("mothers") when resurrecting pre-war and pre-tape recordings. Some imperfections of early types of cutting heads may be electrically compensated in the process, and the final l.p. pressing, due to improvements in techniques, may frequently be of superior quality to the original 78-r.p.m. pressings. The very low compliance of the metallic "mothers' increases the frequency of the upper pickup resonance, so that there is presumably less difficulty in extracting high frequencies from the "mother" during the dubbing process. Incidentally, experiments in dubbing from early acoustic "mothers" has shown that frequencies thought to be above the top frequency limit of the acoustic recorders can be recovered. Dubbing has clearly advanced from the days when

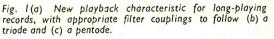

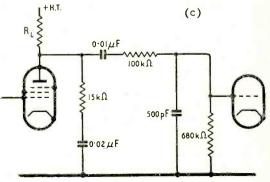

WIRELESS WORLD, FEBRUARY 1955

wax cylinders were duplicated by a pantograph process, although the process described above is basically a mechanical pantograph process electronically refined!

Incidentally, in the past "masters" were burnished, and it has been stated that this burnishing or "polishing" process, while only slightly increasing harmonic distortion, may greatly increase intermodulation distortion.² Considerable success in the restoration of early recordings has been obtained when unpolished masters are available.

In view of the many complex processes intervening between the original tape recording and the finished pressing, it is something of a miracle that modern recordings are generally of such superlative quality. Music in particular is a singularly difficult commodity to "can" to the satisfaction of musicians, technicians and critics simultaneously. The added difficulties of l.p. microgroove techniques have in fact resulted in considerable numbers of recordings suffering from technical blemishes. As might be expected the closer groove spacing renders l.p. discs particularly vulnerable to "pre-echo" due to heavy groove modulation distorting the adjoining outer groove, and thus producing the effect of a "pre-echo" as a faint impression of the sound is heard when the stylus traverses the distorted groove preceding the heavily modulated groove. The longer time delay between grooves due to the slower rotation of l.p. records gives the "pre-echo" a better chance of being heard, as it may coincide with a quiet passage prior to a violent crescendo.

Tape Joins

The impact of technical factors at every point in the overall recording process upon musical quality does not appear to be appreciated in some quarters. However, many technical blemishes in records appear to be directly attributable to the master tape. Tape joins are a particular bête noire of the reviewers. Briefly, they account for abrupt changes in quality, noise level, volume and pitch. While tape is a very suitable medium for long continuous recording, it should be noted that for the master tapes a speed of 30 inches per second is used. Thus a 3,600-ft spool lasts just over twenty minutes, and consequently tape joins are frequently inevitable in practice. Abrupt changes are frequently noticeable at tape joins in the finished l.p. discs. An even more horrifying possibility is the allegation that repeats in classical works are sometimes faked by merely playing the tape through again.3

Even harsher accusations against recording practices have been made4, and it is certainly true that the control engineers play a very important role in the recording process. A simplified diagram of the overall process from studio to the lacquer "cut" is shown in Fig. 2. The acoustic properties of the studio may be adjusted by the use of screens and absorbers, a process in which the recording artists may be expected to have very definite ideas. Pick-up of sound and balancing of orchestral sections may be by the use of several microphones, three to twelve being quite usual. One American recording concern, however, uses only a single microphone for many of its classical recordings. The microphone inputs are individually equalized, mixed and passed through a variable equalizer into a tape recording and playback unit. The microphone outputs are mixed and the variable equalizer adjusted by the engineer until the replay

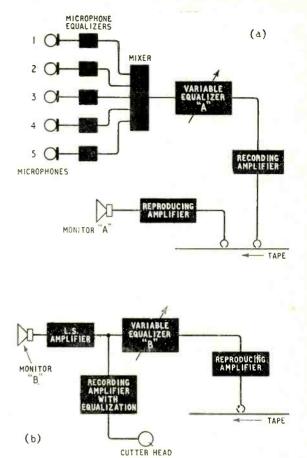


Fig. 2 Stages in the production of a lacquer "cut"; (a) recording the tape master, (b) transcribing from tape to disc.

speaker "A" gives the desired balance in its own particular acoustic environment. While the environment will usually be a familiar one, it may well be a totally unfamiliar one such as the ante-room of a foreign concert hall or theatre. The lacquer "cut" is made by playing back the

The lacquer "cut" is made by playing back the edited tape recording, and generally a different machine and a different monitor speaker "B" in a different acoustic environment will be used. A playback equalizer is used, and generally a disc is cut without need for adjustment of the playback equalizer, although tapes from machines of different characteristics may require equalizing adjustments. When a satisfactory playback is achieved, the lacquer disc is cut via a recording amplifier also incorporating an equalizer. Unfortunately, this equalizer cannot be designated as a "black box" imposing the "recording characteristic," tempting as such a description would be.

Indeterminate Variables

It is clear that so many variables are present, including those variables of the "personal equation" type, that it is pointless to argue over a decibel or two at the extremes of the audio spectrum. This is quite apart from such technical variables as highfrequency playback loss which also enter the picture. Moreover, with the additional technical processes involved in producing the finished pressings, it is clear that perfection in recordings is not easily achieved. Contemplating the overall system from recording studio to the home listener's loudspeaker it is frustrating that overall negative feedback cannot be applied. At present negative feedback is only applied in the broadest cybernetic sense through the activities of critics and the purchasing preferences of the public and the depth of their pockets.

REFERENCES

¹ RUSSELL, O. J., "Stylus in Wonderland." Wireless

World, October, 1954. ² Roys, H. E., "Intermodulation Distortion Analysis as Applied to Disc Recording and Reproducing Equipment."

^a WARRACK, J., "Chamber Music for All." Daily Telegraph, November 8, 1954.

Editorial, The Gramophone, October, 1954.


Recording Tape Splicer

IN theory it is a simple matter to join broken magnetic recording tape, using a pair of scissors or a razor blade and a bit of sticky tape. Those who have tried it will know that in practice it can be very fraying to the temper, and that it is by no means easy to align the ends properly or to produce a joint that will not subsequently hold up in the guides.

The "Bib" tape splicer produced by Multicore Solders, Ltd., Hemel Hempstead, Herts, and used in conjunction with Scotch Boy No. 41 "non-oozing" adhesive tape, produces a perfect joint with the minimum of effort.

The body of the splicer is a brass block grooved to a clearance fit for standard 1-inch tape, with cork pressure pads on hinged arms located to hold the ends firmly in line. A transverse slot at an angle of about 60° is provided to guide the cutter when making the scarfed joint, and parallel slots at the edges of the tape guide ensure that the joint is reduced slightly in width when trimmed-actually by the thickness of the razor blade if it is held vertical. Although not mentioned in the instructions, we found that it was important to make the direction of each trimming cut towards the tapering point on each side, otherwise there was a tendency to pull the extreme point out of the joint slightly. With this precaution

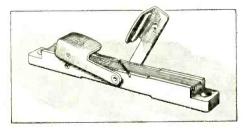a perfect splice was obtained every time. The retail price of the "Bib" splicer is 18s 6d. It is supplied on a flock-sprayed wooden base, but can be removed from this and attached directly to the recorder deck by two screws, if desired. The instruction leaflet contains useful general hints on tape editing.



"Bib" splicer for use with $\frac{1}{4}$ -in standard magnetic recording tape.

Transistorized Telephone

SHOWN in the illustration is a telephone handset fitted with a microphone designed for use in very noisy locations. It responds only to sounds originating close to the mouthpiece; in consequence, the output is much too low for its use in ordinary telephone systems without preamplification.

An amplifier designed around Mullard junction transistors is shown. It comprises two stages for bringing the output of the microphone up to the normal level and a third to give further amplification where a high noise



Noise-cancelling telephone and transistar amplifier.

level prevails at both ends of the line. The amplifiers are operated from hearing-aid type batteries in the plastic tube on the right of the unit.

As transistor equipment can, where necessary, be made very small the amplifier could be incorporated in the handset itself and powered by the low-voltage supply of the normal telephone system.

Commercial Literature

Band III Television Converter with station selector switch, on/off mains switch (which also controls the main receiver) and Band-III station tuning control. May be operated with either a.c. or a.c./d.c. receiver and power consumption is 10 watts. Also a Television Pre-amplifier, a Distribution Unit, and a Multi-outlet Box. Leaflets from Aerialite, Castle Works, Stalybridge, Cheshire.

Oxidation Insulation for closely spaced wire-wound resistors. A new process giving a coating of good insulating properties to the nickel-chromium-iron alloy "Brightray B," described in a leaflet from Henry Wiggin & Company, Wiggin Street, Birmingham, 16.

Capacitance Meter with range of 0-250pF and facilities for measuring stray capacitances in situ. Frequency modulation of a transitron oscillator is changed by capacitance to be measured and the change is detected by a linear discriminator. Also an A.C. Voltage Regulator, an Oscilloscope Camera, a Cathode Follower Unit and various Pressure Transducers. Leaflets from L angham Thompson Rushey Heath Herts Leaflets from J. Langham Thompson, Bushey Heath, Herts.

Arc Soldering Iron with one electrode formed by hollow carbon bit and the other by resin-cored solder fed through the centre of it. Contact with work completes the circuit, forms an arc and melts the solder. Current supplied from 4-V or 6-V battery or transformer. Description on a leaflet from C. J. Casey (London), 49, St. James's Street, London, S.W.1 S.W.1.

Test Gear and Electronic Instruments. Services offered by Livingston Laboratories as agents for a large number of different makes are explained in a booklet "What We Can Do For You," From Livingston Laboratories, Retcar Street, London, N.19.

Gramophone and Concluded from page 14 of January, 1955, issue). Microphone Pre-Amplifier

FROM GRAM

RADIO/TAPE

Constructional Recommendations: Test Procedure

N building the pre-amplifier, there are several practical matters which must receive attention if firstclass results are to be obtained.

To keep the hum level in the input stages as low as possible, the following recommendations should be adopted : -

(a) The wiring, particularly that associated with the grid and cathode circuits, should be arranged so as to

avoid forming loops of large area, since hum voltages of appreciable magnitude can be induced in such loops by stray 50-c/s magnetic fields from nearby mains transformers, etc. A good layout for the microphone and mixer stages is shown in Fig. 8.

(b) The valveholders for the EF86's should be made of high-grade dielectric material, ordinary Bakelite being liable to introduce appreciable coupling between heater and grid pins; the holders made by Ediswan-Clix in p.t.f.e. are suitable. (The advent of all-glass valves such as the EF86, with the grid pin diametrically opposite the heater pins and with internal shielding between them, together with special valveholders, has made it possible to obtain extremely low hum levels even when the grid-circuit impedance is high, so that the advice given by the author in an earlier article,¹⁴ always to use top-grid valves for such applications, may now be regarded as out of date.)

(c) Heater wiring should be twisted and the chassis

Fig. 8. Underside view of part of the chassis, showing a suitable layout for the microphone and mixer stages.

should not be used as a return lead for heater current. Stray capacitance between the heater leads and grid circuit wiring should be kept as small as possible, a good arrangement being to run the heater supply along the top of the chassis, taking each heater feed down through a hole in the chassis near the valveholder but diametrically opposite the grid pin.


By P. J. BAXANDALL, B.Sc.(Eng.)

(d) A common heater supply may be used for all

4 in

MICROPHONE

52

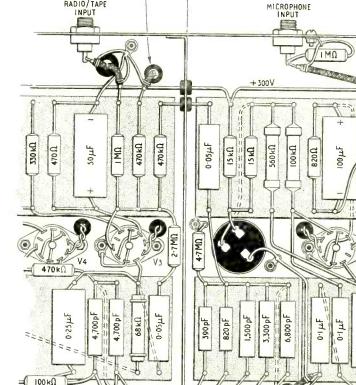

330kQ 5

TREBLE

RASS

100kΩ

8 1/2 in

1775.0

valves, and should have either a fixed centre-tap, connected to chassis, or, alternatively, a "hum-dinger" potentiometer, of value about 100¹², whose slider is connected to chassis. A fixed centre-tap should be quite satisfactory if all other precautions have been taken, but a potentiometer has the advantage of enabling the hum on one particular input stage to be reduced to a specially low value if and when required. (The application of a d.c. bias voltage to the heater supply, as recommended in an earlier article,¹⁴ is unnecessary with moderrn valves such as the EF86, which have been specially designed for input stages.)

(e) The whole pre-amplifier circuit should be electrostatically screened, by mounting in a metal cabinet or by fitting a base-plate to the chassis.

(f) If a microphone input transformer is used, it should be enclosed in a Mumetal screening box. (The "Bi-limboid" series of astatic input transformers, made by Wright and Weaire Ltd., may be recommended; their hum-cancelling properties enable a screening box to be dispensed with under some circumstances, but when used in conjunction with ribbon microphones, it is usually desirable to employ a screening box.)

Some further practical points, relating to matters other than hum, are as follows: --

(g) It is very desirable that when one input stage is faded right down, but is receiving a large input signal, no audible signals from this channel shall get through to the output via unintentional stray couplings. For example, a fraction of a picofarad of stray capacitance between the anode circuit of the input stage in question and the grid circuit of the mixer stage, is sufficient to give very appreciable break-through with the gain control set to zero. Stray capacitance coupling between one input stage and another gives a similar result, except that the volume of the break-through sound is then dependent on the setting of the gain control of the "receiving" stage. In both cases the sound is thin and screechy, due to the greater effectiveness of the stray capacitance coupling at high audio frequencies.

To avoid the above trouble, the components associated with one input stage should be grouped together and a screening partition placed between them and the group of components associated with the next stage. The signal-output lead from each input stage should be screened and taken through to the mixerstage compartment, where the $470\text{-k}\Omega$ mixer-input resistors should be mounted.

(h) A further desirable feature is that no appreciable clicks should be heard on operating the switches associated with the low-pass filter or the microphone bass-cut circuit. In the latter case, it has been found that the main precaution necessary is to mount the bass-cut capacitors on a separate group board, as shown in Fig. 8; if they are mounted on a group board which also contains components having applied d.c. voltages, the slight leakage currents flowing in the group board are sufficient to cause the unused capacitors to become charged, resulting in large clicks when they are switched into circuit.

In the low-pass filter, resistors of $10 M\Omega$ are connected across the switch contacts to ensure that the capacitors are charged to the appropriate voltage before being switched into circuit.

With regard to the general form of construction, the simple scheme depicted in Figs. 8 and 9 is considered to have much in its favour, though the size of the unit could certainly be reduced by adopting a more advanced layout. Due to the use of miniature valves and double electrolytic capacitors, the overall size is, however, small enough for most applications.

For applications where all the facilities given by the circuit of Fig. 1 are not needed, some of the following simplifications may be made, with consequent reduction in cost:—

(a) Adopt triode connections permanently in the microphone input stage; the gain will then be fully sufficient for all normal purposes when a good moving-coil microphone is used, and enough for many purposes using a ribbon microphone. (Connect anode to G_a , G_a to cathode, and make the anode load and cathode bias resistors 100 k^Ω and 1 k^Ω respectively.)

(b) Onit the bass-cut circuit in the microphone stage, or provide a smaller number of positions.

(c) Onit the gramophone input stage, and employ a crystal pickup feeding directly to the mixer stage.

(d) Use the two halves of an ECC81 (12AT7 or CV455 are equivalent) for the mixer and tone-control stages. The anode loads should be 68 k^{Ω} and the cathode-bias resistors 680^{Ω} . Occasional samples of this valve may possibly be too microphonic⁶, but, in view of the reasonably high signal level, little trouble is likely to be experienced.

(c) Omit the master gain control at the output of the pre-amplifier; the facility it provides for fading out two programme sources simultaneously may not be needed.

(f) If the pre-amplifier is to be operated exclusively off a power pack separate from that in the main amplifier, only one stage of decoupling is necessary in the h.t. feed to each input stage. (It is possible, provided suitable precautions are taken with regard to layout and wiring, to obtain a satisfactorily low hum level even if the power pack is built on the same chassis as the pre-amplifier; in particular, the mains transformer should be mounted as far from the input stages as possible and non-magnetic chassis material is desirable. Trouble from hum is, however, much less likely if a power pack well separated from the preamplifier is employed.)

Tests.—The circuits employed in this pre-amplifier are such that no critical adjustments are normally required in order to obtain the desired performance; but, as with any electronic equipment, it is quite possible that—due to faulty components, wiring errors or unsuitable layout—the correct result may not be obtained straightaway.

It is strongly recommended that, no matter what other tests the reader may wish to make, the first test should be to measure various d.c. voltages with a highresistance meter such as an "Avometer" Model 8. If a meter of lower resistance be used, allowance should be made for the reduction in voltage caused by connecting the meter.

The h.t. supply voltage should be within the limits 270 V to 330 V. and anode and cathode voltages should then be within the following limits:—

(a) Cathode to earth, on all valves: 1.2 to 1.8 V.

(b) Anode to earth, on all valves except output valve: 60 to 150 V.

(c) Anode to earth, on output valve: 80 to 170 V. If any of the above voltages are found to be dependent on the settings of one or more of the controls, then wrong connections, faulty components or

self-oscillation should be suspected, in that order. If the pre-amplifier has passed the above d.c. tests, it is reasonably safe to assume that the non-linearity

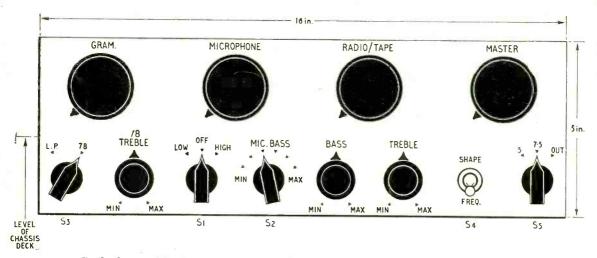


Fig. 9. Suggested front-panel layout corresponding to the under-chassis construction shown in Fig. 8.

distortion will be satisfactorily low and that it will remain low despite normal variations in mains voltage, valve ageing, etc.

Readers possessing, or able to borrow, suitable test gear, will, no doubt, wish to check the frequency response with various control settings. However, the absence of such measuring facilities need not be regarded as an overwhelming handicap. since careful listening tests should be able to indicate whether or not the controls are functioning in approximately the correct ways.

A suitable frequency-response test to start with is to measure the overall response from the microphone-stage input to the final output. The bass and treble tone controls should be set half way between full-lift and full-cut positions, giving a nominally flat response, and the microphone bass-cut and low-pass filter switches should also be set for level response. The effective load on the pre-amplifier output should be 250 k\Omega. The overall response curve should then agree with Fig. 7 within ± 1 db over the frequency range 40 c/s to 15 kc/s. If satisfactory agreement is not obtained, the responses of the various stages should be measured separately, and the origin of the discrepancy discovered. The following points may be helpful:—

(a) If the two 4700-pF capacitors and the two 100-k Ω resistors in the main tone-control network are perfectly matched pairs, the gain from the mixer stage input to the tone-control stage output will normally fall by a fraction of a decibel as the frequency is raised from about 400 c/s to about 4000 c/s. Such a small change in gain is really quite unimportant, but it may be eliminated if the $100-k\Omega$ resistor between the mixer valve anode circuit and the 1 M Ω bass-control potentiometer is reduced in value by an amount equal to the effective output impedance of the mixer stage, this impedance being just under $10 \,\mathrm{k}\Omega$ when two input stages are employed. In practice, due to the effects of component tolerances, the fall in gain between 400 c/s and 4000 c/s may appreciably exceed 1 db, or it might conceivably be a rise rather than a fall; in either case the remedy is to shunt an extra resistor across the appropriate $100-k\Omega$ resistor in the tone-control network.

(b) The frequency response of the mixer stage, when not connected to the tone-control stage, should be flat within a fraction of a decibel up to 15 kc/s. If the response falls off appreciably at the top end, the cause is almost certainly the existence of too much stray capacitance across the $2.7-M\Omega$ feedback resistor; 4 pF would be sufficient to give a loss of 3 db at 15 kc/s. It is not difficult to arrange the wiring so that the stray capacitance across this resistor is kept down to 1 pF, in which case the top loss will be quite negligible. If, due to unsuitable layout, it is found to be impracticable to obtain a low enough stray capacitance, the resultant top loss may be approximately compensated by connecting a small capacitor across each of the mixer input resistors.

(c) Effects of a similar nature to the above can occur in the output stage, and the wiring should be arranged so as to keep the stray capacitance between anode and grid circuits to a minimum.

(d) The frequency response of the output stage in the 30-c/s to 60-c/s region (see Fig. 7) may be adjusted slightly, if necessary, by altering the value of the 8.2-M Ω feedback resistor.

(e) The frequency response of the gramophone input stage, on the "78" setting of S3, may be adjusted, over a region similar to that mentioned in (d), by changing the value of the $6.8-M\Omega$ feedback resistor. In the "LP" (long playing) condition, the response at such low frequencies is determined mainly by the value of the $3.3-M\Omega$ resistor in the network connected to the "LP" contact of S3.

With the pre-amplifier connected to a power amplifier and loudspeaker, and set for a flat frequency response, the Johnson noise at full gain on a microphone channel, with no signal source connected to the input, should be clearly audible all over the room, and should sound louder than the accompanying hum. If the hum level is undesirably high, and if it cannot be satisfactorily minimized with the "hum-dinger" potentiometer, the first thing to do is to find out whether the hum is due to the a.c. heater supply or not; this is easily done by momentarily disconnecting the heater supply—the valves will continue working for a few seconds on their stored heat. No matter what the cause of the hum, a careful consideration of the principles outlined previously should enable it to be cured.

Acknowledgment.—The manuscript of this article has been carefully scrutinized by E. F. Good, who has also done independent calculations to check the mathematical results. This valuable service is hereby gratefully acknowledged.

Apology.—Since the appearance of the negativefeedback tone control article,² in October, 1952, so much correspondence has been received that it has, unfortunately, not been possible to reply to all letters. The writer would like to apologize to the readers concerned and to any others who have been inconvenienced by the fact that, due to unexpected curtailment of spare time, the present article has appeared much later than was originally expected and implied.

REFERENCES

"High-Quality Amplifier Design" by P. J. Baxandall, Wireless World, Jan. 1948. (Also appears in a booklet "High-Quality Audio Amplifiers" available from Wireless World.)

² "Negative-Feedback Tone Control" by P. J. Baxandall, Wireless World, Oct. 1952.

³ "Equipment for Acoustic Measurements—Part 1" by D. E. L. Shorter and D. G. Beadle, *Electronic* Engineering, Sept. 1951.

⁴ "New Equipment for Outside Broadcasts" by A. E. Barrett, C. G. Mayo and H. D. Ellis, World Radio, July 21 and 28, 1939.

"New Equipment for Outside Broadcasts" by S. D. Berry, B.B.C. Quarterly, Summer 1952.

" "Newly Developed Amplifiers for the Sound Programme Chain" by S. D. Berry, B.B.C. Quarterly, Summer 1954.

"Microphones," B.B.C. Engineering Training Manual, page 29, published by Wireless World.

* "Radio Designer's Handbook," page 730, fourth edition, published by Wireless World.

" "High-Quality Amplifier : New Version " by D. T. N. Williamson, Wireless World, Nov. 1949.

¹⁰ "Pickup Input Circuits" by R. L. West and S. Kelly, Wireless World, Nov. 1950. "" "Filters" by "Cathode Ray," Wireless World, Jan. and Feb. 1950.

¹² "The Miller Integrator" by B. H. Briggs, *Electronic Engineering*, Aug., Sept. and Oct. 1948.

¹³ "Design of High-Pass, Low-Pass and Band-Pass Filters Using R-C Networks and D.C. Amplifiers with Feedback" by C. C. Schumard, R.C.A. Review, Dec. 1950.


¹⁴ "Hum in High-Gain Amplifiers" by P. J. Baxandall, Wireless World, Feb., 1947.



AUTOMATIC SWITCHING. Sound broadcast programmes for the B.B.C.'s West Region transmitters are switched to their destinations by a system something like an automatic telephone exchange. It is operated by a single engineer at this control desk, which is the "nerve centre" of a new control room recently installed at the West Region headquarters in Bristol.

SHORT-WAVE CONDITIONS

Predictions for February

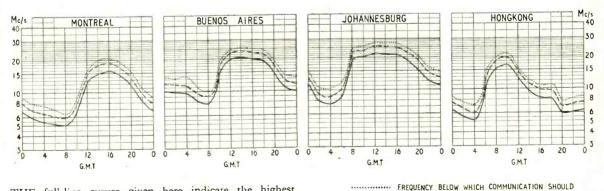

THE full-line curves given here indicate the highest frequencies likely to be usable at any time of the day or night for reliable communications over four long-distance paths from this country during February.

Broken-line curves give the highest frequencies that will sustain a partial service throughout the same period.

4 ----

94

WIRELESS WORLD, FEBRUARY 1955

BE POSSIBLE FOR 25% OF THE TOTAL TIME

- PREDICTED AVERAGE MAXIMUM USABLE FREQUENCY

- FREQUENCY BELOW WHICH COMMUNICATION SHOULD BE POSSIBLE ON ALL UNDISTURBED DAYS

Simple Inductance, Capacitance and **Resonance** Meter

By L. F. SINFIELD

A Useful Adjunct to a Service Signal Generator

HE measurement of small inductors and capacitors for use at radio frequencies is quite a problem, as normally a fairly high degree of accuracy is desired and this entails the use of expensive equipment such as a laboratory universal bridge. Such equipment is certainly not economic if measurements are required only occasionally, as is usually the case.

Although the resonance method does not normally give a direct reading of the inductance it is a simple matter to lay a ruler across a resonance "abac" at capacitance and frequency and read off the induc-tance. A dynatron, transitron or cathode-coupled two terminal oscillator can of course be used, but even if this will oscillate satisfactorily it is rather cumbersome as it requires valves and power supply, and in any case also requires additional apparatus to measure the frequency.

An adaptor was therefore built to work in conjunction with a signal generator so that the generator would resonate coils with a calibrated capacitor and give meter indication of resonance. It was not expected that any very high degree of accuracy would be obtained, but on test inductors of known values have given readings within limits normally required for this range.

Basically the unit consists of a detector and meter to indicate the signal generator output. The tuned circuit is in series with the meter and its high impe-

dance at resonance gives a dip in the meter current. The generator used was a cheaper grade "servicing" type, and was modified so that the output was obtained via a cathode follower to give a lowimpedance output (about 100 ohms) at maximum output through the entire fundamental range of 100 kc/s to 80 Mc/s. Signal generators using a buffer stage, link-coupled output, or both, will be quite suitable and need no modification.

GERMANIUM


A germanium diode (GD5-OA61 or other equivalent) provides rectification for the meter which is of approximately 50 A full-scale deflection. The exact sensitivity and calibration of the meter are unimportant as it merely indicates dip. An ex-Government oil temperature meter was adapted by the author, but a centre-zero movement from a visual indicator unit (see Wireless World, Sept., 1951) could be used. The meter is by-passed by a 0.1µF capacitor and a further 0.001 "F mica type, so that as far as r.f. is concerned the meter and the frame of the $0.0005 \mu F$ tuning capacitor, as well as one side of the inductor, are all earthy.

Actually the meter can be dispensed with entirely and a pair of phones substituted. The signal generator should then be audio-modulated and the tone will be audible in the phones. The unit is then tuned for minimum audio signal. 100-ohm moving-coil and 4,000-ohm moving-iron phones have been tried and both work satisfactorily, but the high-resistance type gives a louder signal. An ideal arrangement would be to fit a closed circuit jack in series with the meter so that high-resistance phones could be inserted in series with the meter to give indications by either method.

Layout and Calibration

Layout is as shown in Fig. 2 and the overall size about $5in \times 4in \times 2\frac{1}{4}in$. A bakelite panel is used and the whole can be put in a wooden or bakelite box. This is a precaution against increasing the minimum capacity of the tuning capacitor. No trouble has been experienced with hand capacity at any frequency.

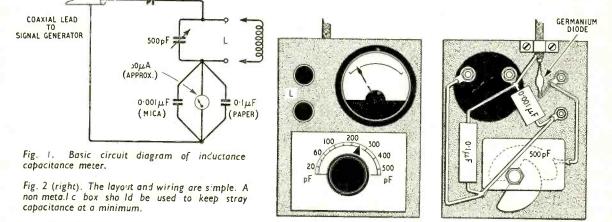Using a known inductance (Wearite PA2-170"H, PA6-37.5, H, PA5-5.5, H) the capacity scale is calibrated. Set the signal input with the generator output control to nearly full scale with the PA2 in place. Set up the following frequencies and calibrate capacitor at each resonant point: 550 kc/s-0.0005µF;



 $610 \text{ kc/s} - 0.0004 \mu \text{F};$ $705 \text{ k/s} - 0.0003 \mu \text{F};$ $865 \text{ kc/s} - 0.0002 \mu \text{F}.$

Below 200pF it is advisable to use a coil having a single layer of spaced turns so that the coil capacity will not appreciably add to the main tuning capacity and cause calibration error. Use now the PA5 type coil and set up as before: 4.8 Mc/s-200pF; 5.5 Mc/s-150pF; 6.75 Mc/s-100pF; 7.5 Mc/s-80pF; 8.7 Mc/s-60pF; 10.7 Mc/s-40pF; 15 Mc/s-20pF.

These are the calibration points used on the original and are satisfactory for most purposes. The lower limit may or may not be obtainable as it will vary within capacitor types.

Order of Accuracy

As a test of inductance measurement accuracy a number of known inductance coils were measured with following results.

Coil	Capacitance	Frequency	Calculated	Actual
	(\mathbf{pF})		L	L
PA3	200	10 Mc/s	$1.23 \ \mu H$	$1.2 \ \mu H$
PO5	200	5.15 Mc/s	4.7 μH	$4.8 \ \mu H$
PA5	200	4.9 Mc/s	5.2 µH	$5.5 \mu H$
PO6	200	2.1 Mc/s	28.0 µH	27.45 µH
PA6	200	1.8 Mc/s	38.5 µH	37.5 μH
PA7	200	630 kc/s	$320 \mu H$	310 µH
R.F. Chok	e 200	225 kc/s	2.5 mH	2.5 mH

The capacitor should preferably be kept at a fairly high value in order to swamp coil self-capacity, provided that adequate dip can be obtained. High values of inductance such as i.f. or long-wave coils, unless pie-wound and of high "Q" may not give a sharpenough dip for good indication. Also, if such inductors are wound in a single pie the high self-capacity may give a false inductance reading.

It is possible to indicate resonance by either setting a given capacity and varying the frequency or vice versa. If the frequency is varied it is necessary to ensure that the dip is actually a resonance and not a comparatively dead spot in the signal generator output. This can be checked by leaving the generator at that frequency and varying the capacitor, when the dip should again be indicated as the capacity goes through the resonant point.

If the signal generator waveform is not pure and is rich in harmonics there is a probability that the tuned circuit will also resonate at harmonics of the input frequency. The correct actual tuning point is therefore the highest frequency setting of the signal generator at which the dip occurs.

Measurement of small capacitors of up to 480pF is carried out by resonating an inductance with the main tuning capacitor, then connecting the unknown capacity in parallel with the coil and retuning back to the dip. The unknown will then be equal to the difference in the main capacitor settings.

It is not considered that the present layout would permit an exact measurement of inductors of less than 1μ H, due to inductance of the internal connections. However, ample dip has been obtained up to the limit of the present set-up (80 Mc/s-20pF-0.2 μ H). This would indicate an inductance of 0.2 μ H, but the actual external inductance will in fact be slightly less than this.

MAGNETIC INDUCTION MEADPHONES


THE method of using a wire loop surrounding a cinema or hospital ward to supply energy to headphones without the inconvenience of connecting leads is by no means new. In general, standard type headphones have been used in conjunction with a small loop to supply them with current by electromagnetic induction.

No electric current is induced in a new type of headphones designed by V. A. Foot, and the forces actuating the diaphragms are purely magnetic. The sketch accompanying the photograph illustrates the principle. Laminated pole pieces of high-permeability material are extended to collect a concentration of flux from the surrounding field, which passes across short air gaps and through a circular armature disc attached to a small conical phosphor bronze diaphragm. As in conventional headphones a polarizing field is necessary, and is supplied by a short permanent magnet which can be rotated to reduce the flux in the air gaps and so to control volume.

The sensitivity is unexpectedly high, and the power required to give good volume in the primary loop surrounding the room is of the order of 10 watts per 1,000 sq ft of floor area.

With no fine wire or wax-impregnated windings to worry about, the phones can be boiled in water or otherwise disinfected, a point which has commended the system to hospital authorities. For hospital use the carpicces are rotatable so that the pole extensions can be kept in line with the vertical magnetic field when the patient is lying down. No volume control is provided in this type.

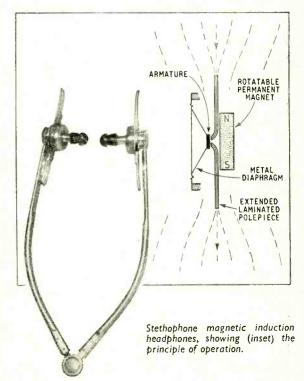The price of both standard and hospital types is $\pounds 2$ 2s per pair and of lorgnette type phones $\pounds 3$ 3s each. A matching transformer suitable for supplying a loop from domestic radio receivers costs 12s 6d. The makers are the Magnetic Broadcasting Co., Ltd., 1, Upper Richmond Road, London, S.W.15.



FEBRUARY

Institution of Electrical Engineers

London.—February 7th. Discussion on "The Problem of Radio Inter-ference" opened by C. W. Sowton at 5.30

February 9th. "A Study of Commer-cial Time Lost on Transatlantic Radio Circuits Due to Disturbed Ionospheric Conditions" by J. K. S. Jowett and G. O. Evans; and "Performance Characteristics of High-Frequency Radio Tele-graph Circuits" by A. M. Humby, C. M. Minnis and R. J. Hitchcock at 5.30.

February 14th. Discussion on "Teaching Faraday's Law of Electro-Magnetic Induction" opened by P. Hammond at 6.0. February 21st. "The Recent Search

February 21st. "The Recent Search for and Salvage of the Comet Aircraft near Elba" by Cdr. C. G. Forsberg, R.N., and G. G. MacNeice at 5.30. All the above meetings will be held at

Savoy Place, W.C.2.

Cambridge Radio Group.—February 15th. "Colour Television" by L. C. Jesty at 8.15 at the Cavendish Laboratory, Cambridge.

North-Eastern Radio & Measurements Group.—February 7th. "Radio Aids to Marine Navigation" by Capt. F. J. Wylie, R.N. (Ret.), at 6.15 at King's College, Newcastle-upon-Tyne.

North-Western Radio Group.—Feb-ruary lóth. "An 8MeV Linear Accel-erator for X-ray Therapy" by C. W. Miller at 6.45 at the Engineers' Club, Albert Square, Manchester.

South Midland Radio Group -Feb ruary 28th. "Thermionic Valves of Industrial Purposes" by E. G. Rowe, P. Welch and W. W. Wright at 6.0 at the James Watt Memorial Institute, Great Charles Street, Birmingham.

North Midland Centre.—February 21st. Faraday lecture "Courier to Carrier in Communications" by T. B. D. Terroni at 7.0 at the Town Hall, Leeds.

North Staffordshire Sub-Centre.— February 14th. "A Transatlantic Tele-phone Cable" by M. J. Kelly, Sir Gor-don Radley, G. W. Gilman and R. J. Halsey at 7.0 at Duncan Hall, Stone.

South-West Scotland Sub-Centre.— February 2nd. "A Study of Some of the Properties and Materials Affecting Valve Reliability" by E. A. O'Donnell Roberts at 7.0 at the Institution of En-gineers & Shipbuilders, 39, Elmbank Crescent, Glasgow, C.2.

Western Centre.-February 8th. Fara-day lecture "Courier to Carrier in Comday lecture "Courier to Carrier in Com-munications" by T. B. D. Terroni, at 6.3J at Brangwyn Hall, Swansea, and on February 10th at 6.45 at Colston Hall, Bristol

British Sound Recording Association

London.—February 18th. "Electro-Acoustics of Microphones" by H. A. M. Clark at 7.0 at the Royal Society of Arts, John Adam Street, W.C.2.

Manchester Centre.—February 14th. "Reproducing Needles" by L. Rollin at 7.30 at the Engineers' Club, Albert Square, Manchester.

Radar Association

London.—February 23rd. "Air-borne Electronic Equipment" by Air Vice-Marshal R. G. Hart at 7.30 in the Anatomy Theatre, University College, Gower Street, W.C.1.

MEETINGS

British Institution of Radio Engineers

London Section.—February 23rd. "A Versatile Electronic Engine Indicator" by R. K. Vinycomb (Southern Instru-ments) at 6.30 at the London School of Unione and Tranical Medicine Kennel Hygiene and Tropical Medicine, Keppel Street, W.C.1.

West Midlands Section.—February 9th. "Electronic Motor Control Sys-tems" by J. C. Rankin (B.T-H.) at 7.15 at the Wolverhampton and Staffs. Technical College, Wulfruna Street, Wolverhampton.

North-Eastern Section .- February 9th. Papers by students at 6.0 at Neville Hall, Westgate Road, Newcastle-upon-Tyne.

Merseyside Section.—February 3rd. "Colour Television—Prospects and Problems in the U.K." by D. W. Heightman (English Electric) at 7.15 at the College of Technology, Byrom Street, Liverpool, 3.

North-Western Section. — February d. "Recent Developments in Test 3rd. Gear in the Radio, Television and Radar Fields" by A. G. Wray (Marconi In-struments) at 7.0 at the Reynolds Hall, College of Technology, Sackville Street, Manchester.

South Wales Section.—February 23rd. "The Training of Radio Engineers" by H. W. French (H.M. Inspector of Tech-nical Colleges) at 6.30 at the Glamorgan Technical College, Treforest.

Scottish Section.—February 10th. "Radio Telephone Systems to the Islands" by T. Moxon (G.P.O.) at 7.0 at the Institution of Engineers and Shipbuilders, 39, Elmbank Crescent, Glas-gow, C.2.

Television Society

London.—February 11th. "Television Coverage of Gt. Britain" by R. A. Row-den (B.B.C.) at 7.0 at the Cinematograph Exhibitors' Association, 164, Shaftesbury Avenue, W.C.2.

February 24th. "Modern Microwave Techniques" by R. L. Corke (P.O. Research) at 7.0 at the C.E.A., 164. Shaftesbury Avenue, W.C.2.

Radio Society of Great Britain

London.—February 25th. "Radio Astronomy and the Radio Amateur" by R. C. Jennison (Jodrell Bank Experi-mental Station) at 6.30 at the I.E.E. Savoy Place, W.C.2. "Radie

Society of Instrument Technology

Chester Section. - February 23rd Chester Section. — reprint 2016 "Some Useful Electronic Circuits for Measuring Purposes" by E. Higham (Lever Bros.) at 7.0 in the Board Room of the Chester & Dist. Hospital Committee, 5, Kings Buildings, King Street, Chester.

Fawley Section.—February 4th. "Elec-tronic Computers" by a member of the staff of Elliott Bros. at 7.0 in Copthorne House, Fawley, Hants.

Incorporated Practical Radio Engineers

East Midlands Section.—February 25th. "Transistors and Their Possible Future Uses" by a member of the staff of the G.E.C. at 7.15 at the Electricity Board Demonstration Theatre, Smithy Row, Nottingham.

Midlands Section.—February 22nd. "Cathode Ray Tubes" by a member of Mullard's staff, at 7.30 at the Connaught Room, Imperial Hotel, Temple Street, Birmingham.



The TRIX range of quality Sound Equipment is the most comprehensive available. There are amplifiers and accessories for all requirements-small, large, indoors or outdoors, permanent or portable. And TRIX workmanship is respected throughout the world. Our catalogue and technical advice are at your disposal.





Enclosed rack type equipment RGA3 633. Combines 30 watt amplifier with pre-set radio, priority microphone control and 3-speed changer.

SERVICE IN SOUND BY



RANDOM RADIATIONS

By "DIALLIST"

Exploring Band III

HIGHLY interesting results should emerge from the Band III reception tests which those enterprising people Belling and Lee are soon to begin. As you probably know, Sutton Coldfield is radiating experimental square-wave transmissions on the 189.75 Mc/s vision carrier frequency which has been allotted to the I.T.A. for its Midland service. The Belling-Lee test unit will first of all balance up the Band I and Band III vision signals from Sutton Coldfield at some convenient spot where both are well received. It will then drive over a large part of the service area and a careful record of the comparative strengths of the two signals will be made. Myself, I believe that in districts which are not of the hilland-valley kind the range of the Band III transmission will turn out to be a good deal greater than many When Wrotham people think. started its sound transmissions in Band II with an output of around 20kW most of us thought that it wouldn't reach out very far; but at 40 odd miles I get a tremendous signal from it with a simple dipole, provided with neither reflector nor director. I'm told, too, that it is received as far away as Shrivenham, Berks (90 miles). If Band II exceeded expectations in the matter of range, I don't see why Band III shouldn't provide surprises as well.

Shadows and "Ghosts"

But Band III is likely to present some pretty problems in hilly country, where wireless shadows may abound. The travelling test unit will have plenty of opportunities of finding out, for there are hills galore around Birmingham. I can testify to that, for I'm writing these notes right up in the Lickey Hills, where I've been staying since Christmas. They're only about 10 miles from the middle of the City. Looking out of the window, I can see the Warwickshire Hills to the south-east; and there'd be another lot in view to the south-west if it wasn't for a belt of trees. My bet, then, is that reception of the Midland Band III transmitter will be rather patchy. "Ghosts" may also be a considerable nuisance. for the shorter the wavelength, the more liable is it to reflection. On the whole, I think that the I.T.A. engineers will have some difficult siting problems; and I doubt whether they'll find the B.B.C.'s aerial masts of much use to them in some places. There'll be some hard thinking, too, for the designers of Band III receiving aerials intended for use in places where "ghosts" abound or the field strength is on the poor side.

North Hessary Tor and Others

THE B.B.C. didn't expect the lowpower temporary transmitter at North Hessary Tor to be of much use to Torquay and parts adjacent. But I've already heard from two friends who live there that it is giving them an excellent signal. In the case of one of them this is a great surprise. His house is towards the Babbacombe end of the town and the ground to north and north-west of it, which lies between it and the transmitter, slopes steeply upward. So steeply, in fact, that you don't have to go far from the back of the house to be on a level with the aerial, which must be a very long way below the line of sight from North Hessary Tor. Rowridge, I.o.W., seems also to be giving a service at a greater distance than was predicted; in some directions, at any rate. There was a storm of indignation, by the way, on the Island when one of the B.B.C. announcers, when giving details of the impending opening of Rowridge, pronounced the first syllable to rhyme with "blow" instead of with "plough." Five new medium-power TV transmitters should be in full operation with their permanent aerial masts before the end of the year. These are Meldrum, Rowridge, Pontop Pike, Divis and North Hessary Tor. The whole of the B.B.C.'s No. 1 programme system should be completed within the following twelve months by the addition of the medium-power Norwich station and the five low-power transmitters planned.*

" Europe No. 1"

THOSE monstrous radio and television stations projected for the Saar and for Monaco are likely to be pretty bad nuisances. So far as this country is concerned, the Saar's 500kW sound transmissions aren't likely to do much harm, for they are on the

* These will be at, or near. Dover, Inverness, Londonderry, Towyn, and Carlisle.

WIRELESS WORLD " PUBLIC	ICATIONS		
TECHNICAL BOOKS	Net Price		
RADIO LABORATORY HANDBOOK. M. G. Scroggie, B.Sc., M.I.E.E. 6th Edition	25/-	26/3	
RADIO VALVE DATA. 4th Edition. Compiled by the Staff of "Wireless World"	3/6	3/10	
SHORT-WAVE RADIO AND THE IONOSPHERE. T. W. Bennington, Engineering Division. B.B.C. Second Edition	10/6	10/10	
SUPERHETERODYNE TELEVISION UNIT. Second Edition	2/6	2/8	
INTRODUCTION TO VALVES. R. W. Hailows, M.A. (Cantab.), M.I.E.E., and H. K. Milward, B.Sc (Lond.), A.M.I.E.E	8/6	8/10	
WIRELESS WORLD TELEVISION RECEIVER MODEL II: Complete constructional details with notes on modernizing the original design	3/6	<mark>3/9</mark>	
RADIO INTERFERENCE SUPPRESSION as Applied to Radio and Television Reception. G. L. Stephens, A.M.I.E.E.	10/6	10/11	
SOUND RECORDING AND REPRODUCTION. A B.B.C. Engineering Training Manual. J. W. Godlrey and S. W. Amos, B.Sc. (Hons.), A.M.I.E.E.	<mark>30/</mark> -	30/8	
ADVANCED THEORY OF WAVEGUIDES L Lewin	30/-	30/7	
FOUNDATIONS OF WIRELESS. M. G. Scroggie, B.Sc., M.I.E.E. 5th Edition	12/6	13/-	
TELEVISION RECEIVING EQUIPMENT. W. T. Cocking, M.I.E.E. 3rd Edition	18/-	18/8	
A complete list of books is availably on application	on.		
Obtairable from all leading booksellers or fro	m		
ILIFFE & SONS LTD. Dorset House, Stamford Street		S.E.1	

long waves and probably won't interfere with Droitwich. But the TV transmissions may cause havoc, particularly when sporadic E is much in evidence. Interference with television reception here was widespread last year at intervals from early June until December. It's a thousand pities that European countries can't get together over the very important question of sound and vision broadcasting channel allocation.* If only we could agree to arm an international body with the powers of the United States Federal Communications Commission!

" Potmeters "

IT'S a queer thing that after all these years we still seem to find it so difficult to make reliable and longlived controls of the potentiometer type. I'm thinking particularly of those used as volume controls and for the contrast control in TV receivers. Far, far too soon do many volume controls become scratchy and scrapy; far, far too soon do those used for the contrast develop such jumps and jerks that it becomes difficult to adjust the gain exactly to your liking. There are, I know, types which don't behave in this exasperating way; and that makes it all the more puzzling that set manufacturers should be content to use any other sort.

Overheating

SUFFICIENT attention isn't always paid by designers to the cooling arrangements in broadcast receivers. Yes, I know that when a set starts dripping blobs of waxy stuff on to the table beneath it the cause may often be that its owner has so placed it that its back is jammed tight against the wall. But it isn't always so. I've seen nasty messes made by sets which were standing well away from the wall. And once that sort of thing starts trouble is on the way. Sometimes the ventilating louvres are in the wrong place; sometimes there aren't enough of them; sometimes they're not long enough. They can't be made wider because they must not allow a "standard finger" to be poked in far enough to touch any live part. Adequate cooling is probably made more difficult by the use of miniature valves; for these run very hot and owing to the smallness of their bulbs there is only a restricted area from which heat can be dissipated.

* Monaco was a signatory to the Stockholm v.h.f. plan under which she is allocated a 50-kW (e.r.p.) television station in each of Bands I and III. The Saar was allocated a 100-kW (e.r.p.) station in Band 1.—Ed.

GLASS-ENCLOSED CARTRIDGE FUSES

FOR MANY USES

All Bulgin Cartridge Fuses are Safe, Certain, and Fireproof. They constitute reliable safeguards against damage to apparatus by overload and are simple and inexpensive to replace. They are uniform and accurate, with highlysilver-plated contact caps. Many sizes and types including models for Automobile and Aircraft use.

ELECTRONICALLY SEALED

Conforming with the latest trends in the manufacture of glass-enclosed cartridge fuses, Bulgin now electronically seal all standard $|\frac{1}{4}$ in fuses. This method of construction gives a stronger and more reliable fuse and ensures that the end caps will not work loose or pull off without fracturing the glass.

The silvered end-caps now present a cleaner exterior surface free from all solder. The fuse element is absolutely protected from ingress of moisture or other injurious matter.

AVOID UNNECESSARY REPLACEMENTS							
	BY	FITTING "PAK" FUSES					
NR1		WHERE surges take place as in the primaries of Mains Trans-					
List No.	Carrying						
PAK.I PAK.2	250 mA. 500 mA.	formers, etc., fuse: may blow unnecessarily. " PAK " types are					
List No.	Carrying	normally delaying and withstand					
PAK.3 PAK.4	750 mA. 1.0 A.	about 75 per cent. overload for					
		approx. 120 secs. Upon the applica-					
List No.	Carrying	1 1 2 2 2 2 2 2 2 2 2 2 2 2 2 2 2 2 2 2					
PAK.5 PAK.6	1.5 A. 2.0 A.	tion of 200 per cent. rating, or more, blowing is instantaneous.					



A. F. BULGIN & CO. LTD., BARKING, ESSEX MANUFACTURERS OF RADIO AND ELECTRONIC COMPONENTS Telephone RIPpleway 3474 (5 times)

UNBIASED

Cuckoo in the Nest

I WAS deeply interested in the Editor's plea in the December and January issues that the control of wireless should be taken out of the hands of the P.M.G. and his allpowerful department. But while desiring to strike the G.P.O. gyves from the wrists of radio he is obviously unable to shake the shackles of editorial caution from himself. In this matter he shows something of a Menshevik mentality rather than the ruthless spirit of the "Old Bolsheviks" which has always characterized his utterances on other matters.

This is clearly shown by the pious hope expressed in the January issue that the Minister who replaces the P.M.G. in assuming parliamentary responsibility for radio will *not* be one who is the head of any of those ministries which are large and greedy users of radio channels. This, surely, is the original argument put forward years ago by the Editor emeritus of W.W. against the P.M.G.'s stewardship. Although that argument still stands, it forms only one count in the case against G.P.O. control.

Radio has grown up since the P.M.G. took it over as a puling infant in 1904, and is more than big enough to justify having a ministry of its own to control its multifarious interests. It is, in fact, fast becoming a cuckoo in the nest, as its rate of growth is so prodigious that in a few years it has already crowded out the G.P.O.'s more legitimate interests, and if handed over to another ministry it would eventually do this cuckoo act in its new nest. Distasteful as the idea may sound to many, what we seem to need is a Ministry of Radio.

Racing by Radio

THERE does not at first sight appear to be much connection between racing and radio, but if certain suspicions of mine are confirmed there will prove to be a very strong connection indeed. As we all know, there are sometimes unexpected results in racing, horses which were considered "dead certs" by the experts being outstripped easily by rank outsiders.

It has been suggested that some of these unexpected results could be accounted for by jockeys receiving pre-race instructions from unscrupulous owners and trainers not to try too hard. The racing correspondent of one national daily writing about this matter at the end of the last "flat" season rather pooh-poohed the

By FREE GRID

idea. He considered that pre-race instructions were greatly over-rated, but added that if it were possible for an unscrupulous interested party to communicate with a jockey during the progress of the race it would then be a matter for serious concern. When reading this my worst suspicions were aroused, for during the past season there seems—judging by the money I have lost—to have been an exceptionally iarge number of these "unexpected results."

It would be a perfectly easy matter to design an ultra-compact lightweight receiver which could be carried about a jockey's person; in fact the thing needn't be concealed, for it could be disguised as a hearing



aid. I find there is nothing in the rules of racing against a jockey wearing an aid to hearing any more than there is against his wearing an aid to clear speech in the form of a wellfitting denture.

At this time of the year jockeys are in normal civilized garb but there is no mistaking one as his small stature and the bowed shape of his legs give him away. Whenever I pass such a figure, as I did the other evening outside a famous club in the Pall Mall, I cannot help regarding him with suspicion although I must confess that so far I have yet to find one wearing a hearing aid.

Euroscopes

EIGHTEEN YEARS ago when the B.B.C. was giving us M & B transmissions from Alexandra Palace on alternate days, television receivers were provided with a switch to change over from the M to the B system and *vice-versa*. As in the case of the famous tablets each of the letters M and B is the initial of a well-known man, and they are used instead of their names, to prevent identification which would result in a free advertisement to their respective firms.

Now, this change-over switch meant quite a lot of complication in the receiver for, not only was the lineage different in the two systems but one used interlacing and the other didn't. But all these problems were solved. I feel, therefore, that it should not be too difficult for some enterprising manufacturer to solve similar problems and produce a set having a change-over switch labelled "British" and "French." This would enable those living in the Cinque Ports section of the south coast to receive French programmes when desired.

I put forward this suggestion as I have a friend living on the White Cliffs of Dover who has a French television set and gets better reception from Lille than he does from A.P. on his British set. He has also been getting a goodly number of viewers to see the French programmes at his house with the result that several French sets have been imported, some by people who do not speak French. Surely this shows that some of the French programmes have a greater eye appeal than anything the B.B.C. radiates. It would seem, therefore, that there might be a market for change-over sets in suitable high-ground localities on the south coast and even a bit inland. The Channel Islands might be another suitable locality for these Anglo-Euroscope receivers.

Tape Recorders

I WAS very interested in a letter published in the December issue in which various shortcomings of tape recorders were pointed out and suggestions made whereby manufacturers could improve them. There was one particular complaint with which I heartily agree and that is the irritating business of loading and threading up. No mention was made, however, of what is, in my opinion, the ideal way of getting rid of this bugbear and that is to follow the technique that has found so much favour with the users of amateur cine cameras.

At one time it was quite a work of art to load an amateur cine camera quickly without getting the film all snarled up. Minor improvements were made but the real thing which put joy into the business was the development of cassette loading. It is the work of a moment to slip into the camera specially designed for it a cassette consisting of a tin box containing both spools, with the film all threaded up ready for use.

threaded up ready for use. It would be necessary to redesign the deck of the tape recorder. But eventually the old separate spool recorders would die a natural death. Dunissa saiose

THE D.C. TO MINOR

unnessall neter

HEAVY DUTY DOMETER

UNIVERSA DAMINOR

DO VALUE CHARACTERISTIC METER

WHILE RANGE SIGNAL GENERATOR recision ELECTRICAL MEASURING INSTRUMENTS

Dependability is an essential quality in any good electrical testing instrument. Absolute dependability is the outcome of good design, suitability for purpose, and a high standard ot good design, suitability for purpose, and a mgu standard of accuracy. in all "Avo" Instruments, which are also noteworthy for their compact portability and robust construction. You can depend on "Avo." When choosing instruments, consult our You can depend on "Avo." When choosing instruments, consult our complete catalogue, a copy o. which may be had iree on application.

THE AUTOMATIC COIL WINDER & ELECTRICAL EQUIPMENT CO. LTD. lelephone: VICioria 3404-9 AVOCET LONDON S.W.I DOUGLAS, STREET WINDER HOUSE

DELECTRONIC TESIMETER

DE ELECTRONIC TEST UNIT

FEBRUARY, 1955

POST THE COUPON TODAY FOR OUR BROCHURE ON THE LATEST METHODS OF HOME TRAINING FOR OVER **150 CAREERS AND HOBBIES**

THE ADVANTAGES OF E.M.I. TRAINING

- * The teaching methods are planned to meet modern industrial requirements.
- * We offer training in all subjects which provide lucrative jobs or interesting hobbies.
- + The student is taken carefully and thoroughly through his chosen subject.
- * A tutor is personally allotted by name to ensure private and individual tuition.
- ★ Free advice covering all aspects of training is given to students before and after enrolment with us.

PRIVATE AND INDIVIDUAL TUITION IN YOUR OWN HOME

Accountancy Advertising Aeronautical Engineering Automobile Engineering Banking Book-keeping Building **Business** Management Carpentry Chemistry **Civil Service Civil Engineering Commercial Subjects Commercial Art &** Drawing

Customs & **Excise Officer** Draughtsmanship Dressmaking Fconomics Electrical Engineering Electronics **Fashion Drawing** Heating & Ventilating Engineering Industrial Administration Journalism Languages Marine Engineering Mathematics

M.C.A. Licences Mechanical Engineering Motor Engineering Photography P.M.G. Licences Police Production Engineering Public Speaking Radar Radio & Television Servicing Radio Engineering Refrigeration Retail Shop Management Salesmanship Sanitation

Secretaryship Shorthand & Typing Sound Recording Structural Engineering Telecommunications Television Time & Motion Study Tracing Welding Writing Workshop Practice Works Management and many others.

Also courses for University Degrees, General Certificate of Education, B.Sc.Eng., A.M.I.Mech.E., L.I.O.B., A.C.C.A., A.C.I.S., A.M.Brit.I.R.E., A.M.I.I.A., City & Guilds Examinations, R.S.A Certificates, etc.

from 15/- per Courses month

THIS COUPON POST TODAY

Please send without obligation your FREE book.

E.M.I. INSTITUTES Dept. 127k.

Grove Park Road, London, W.4.

NAME

ADDRESS

SUBJECT(S) OF INTEREST (We shall not worry you with personal visits)

IC38a

2/55

NEW LEARN THE PRACTICAL WAY - COURSES WITH EOUIPMENT

With many courses we supply actual equipment thus combining theory and practice in the correct educational sequence. The equipment, specially prepared and designed, remains your property. Courses Include: Radio, Television, Electronics, Draughtsmanship, Carpentry, Photography

and Commercial Art, Amateur S.W. Radio. Electricity, Languages, Mechanics, etc.

Equipment supplied upon enrolment and remains your property.



IS PART OF A WORLD-WIDE INDUSTRIAL ORGANISATION



WIRELESS WORLD



Ten features to bear in mind—plus the assurance that these valves are already being widely employed with marked success in both communications and industry. The triodes TY2-125 (CV1924) and TY3-250 are recommended for grounded-grid R.F. amplifiers in communications equipment and as oscillators in compact R.F. heaters. The tetrodes QY3-125 (CV2130) and QY4-250 (CV2131)—included in the Services Preferred Types List—are characterized by high power gain and high efficiencies at V.H.F.

Detailed information on the above range and other V.H.F. valves made by Mullard may be readily obtained from the address below.

MAXIMUM OPERATING CONDITIONS (CLASS C TELEGRAPHY) at 50 Mc/s							Max.		
Valve	Type of Service	Va (V)	Vgl (V)	la (mA)	lgl (mA)	vin(pk) (∀)	P load (W)	η (%)	frequency (Mc/s)
TY2-125 (CV1924)	ampl,	2500	-200	205	40	390	310	76	200
TY3-250	ampl,	3000	-250	365	69	430	670	77	150
QY3-125 (CV2130)	ampl,	3000	-150	167	6.5	300	300	75	200
QY4-250 (CV2131)	ampl.	4000	-225	312	. 9 .	374	800	80	120




MULLARD LTD., COMMUNICATIONS & INDUSTRIAL VALVE DEPT., CENTURY HOUSE, SHAFTESBURY AVENUE, W.C.2

FEBRUARY, 1955

For SPEEDY delivery of precision QUARTZ Crystals

Specialists in the manufacture of Frequency Control Quartz Crystals within the range 2,000 to 20,000 Kc/s

CATHODEON

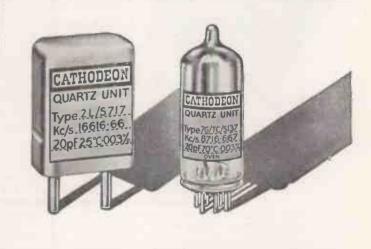




Small urgent orders can now be executed within days, at competitive prices.

Ask for full details.

Tel. LINTON 223



LINTON · CAMBRIDGESHIRE

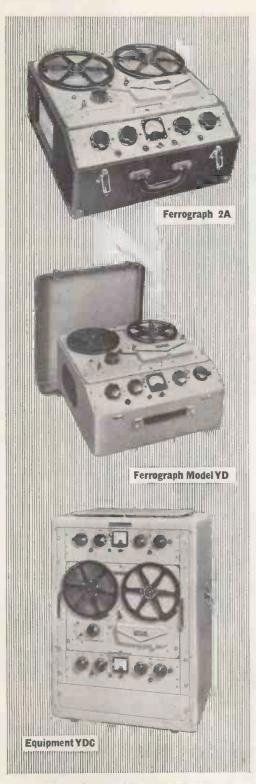

WIRELESS WORLD

A COMMON factor in UNCOMMON PERFORMANCE

WEARITE TAPEDECK

The reputation of the 'Tapedeck' is so well-known and so firmly established as to call for no extravagance in describing its many virtues. Indeed, it forms the basis of the recorder instruments in common use in the Defence Services of the United Kingdom and many other countries, as well as being the choice of broadcasting Authorities throughout the World.

FERROGRAPH 2A A reasonably inexpensive instrument approaching professional standards with a specification commending it to those engaged in educational and cultural pursuits.

FERROGRAPH MODEL YD A triple-speed instrument designed mainly for use in the scientific and industrial fields. Principally intended for operation from and into 600 ohm lines, a high gain stage has been provided, however, to allow for recording direct from normal microphones.

EQUIPMENT YDC A simultaneous dual-channel Recorder-Reproducer offering special facilities for analytical research into medical, aeronautical and scientific problems. Any two activities capable of translation into electrical phenomena within the frequency and phase shift limitations can be recorded and replayed simultaneously.

Originators of Tapedecks WRIGHT & WEAIRE LTD



131 SLOANE ST., LONDON, S.W.1 Phone : SLOane 2214/5 & 1510



Built by Craftsmen Assembly of Scalamp Galvanometers Cat. Nos. W.W. 7901/S-4/S

. The

SCALAMP

Range

You are invited to write for details of the instruments illustrated here.

The Galvanometers and Electrostatic Voltmeters are available in a range of sensitivities—the Fluxmeter has a very high performance and a unique return-to-zero device. Outstanding SCALAMP attributes include a truly functional dustproof case, mains or battery operation, and an easy-to-read hairline spot.



Fluxmeter Cat. No. W.W. 8834



Electrostatic Voltmeter Cat. Nos. W.W. 11308-11310

STANDARD EQUIPMENT IN MANY LEADING LABORATORIES



W. G. PYE & CO. LTD. GRANTA WORKS · CAMBRIDGE · ENGLAND WG.54

42

PROFIT BY EXPERIENCE

There is over 30 years experience behind the Mullard EF 80

The Mullard EF80, high slope R.F. Pentode, is the most widely used valve of its type. This is as much due to its remarkable dependability as to its extremely efficient performance. Designed primarily as an R.F. or I.F. amplifier in television receivers, it is also suitable for use as a video amplifier, mixer or synchronising pulse separator.

The dependability of all Mullard valves is the logical outcome of Mullard advanced quantity production techniques, many of which are unique.

When ordering this type, BE SURE TO SPECIFY MULLARD.



PROFIT BY THE EXPERIENCE OF THIS SERVICE ENGINEER

J. Spivey, Service Manager for Messrs. Vallance & Davison, Leeds, Ltd., says:----

"After all, why take chances? I don't. I use Mullard valves as replacements. Their uniformly high standard takes a great deal of worry off my shoulders—Mullard valves are valves you can trust."

Mullard

THE MASTER VALVE

BLACKBURN • FLEETWOOD • GILLINGHAM • HOVE • LYTHAM-ST. ANNES MITCHAM • PADIHAM • RAWTENSTALL • WADDON • WANDSWORTH • WHYTELEAFE

Mullard MULLARD LTD., CENTURY HOUSE, SHAFTESBURY AVENUE, LONDON, W.C.2

MVEII4C

FEBRUARY, 1955

Paper Capacitors Electrolytic Capacitors Metallised Paper Capacitors Wire-Wound Resistors Composition Resistors Potentiometers

DUBILIER

DUBILIER CONDENSER COMPANY (1925) LIMITED DUCON WORKS, VICTORIA ROAD, NORTH ACTON, LONDON, W.3 Telephone; ACOrn 224! (5 lines) Telegrams: Hivoltcon, Wesphone, London. Marconi International Code. ONDON

Ingland




DOVER

France


Eurovision

The Wayne Kerr Video Oscillator is used by the B.B.C. Engineers to measure the frequency response of the Link over its full bandwidth.

(Photographs by courtesy of the B.B.C.)

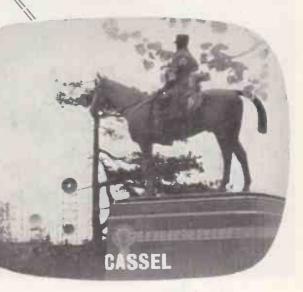

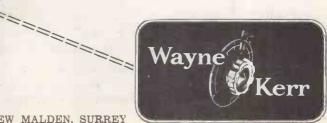
Video Oscillator type 022B + 10 to -50 db on 1 volt peak to peak from 10 kc/s - 10 Mc/s.
Stabilised output. Less than 1% total distortion.
This instrument now includes a 50 c/s square
wave output for examination of the low frequency characteristics of video networks.



9

Full details from: THE WAYNE KERR LABORATORIES LTD., NEW MALDEN, SURREY WIRELESS WORLD

FEBRUARY, 1955

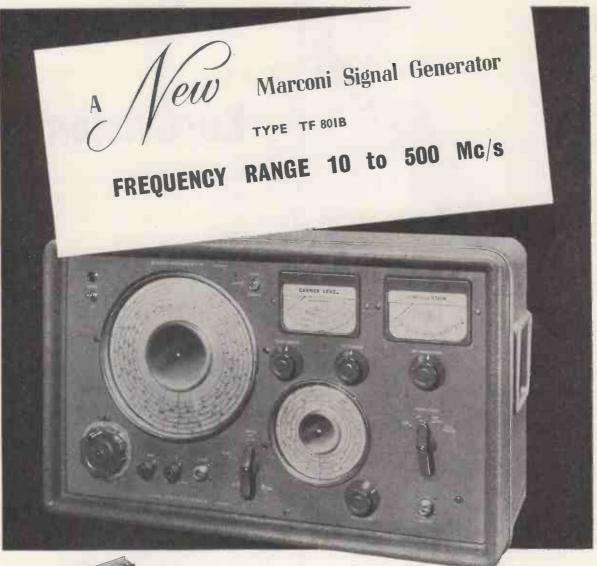



10

This, together with other new designs for 1955, is fully described in the 1955 edition of Marconi Instruments Catalogue.

MARCONI INSTRUMENTS

SIGNAL GENERATORS • BRIDGES • VALVE VOLTMETERS • Q METERS • WAVEMETERS FREQUENCY STANDARDS • WAVE ANALYSERS • BEAT FREQUENCY OSCILLATORS

MARCONI INSTRUMENTS LTD · ST. ALBANS · HERTS · Phone: ST. ALBANS 6160/9 30 Albion Street., Kingston-upon-Hull. Phone: Hull Central 16144. 19 The Parade, Leamington Spa. Phone: 1408 Managing Agents in Export:


MARCONI'S WIRELESS TELEGRAPH CO. LTD · MARCONI HOUSE · STRAND · LONDON, W.C.2

THORN CONTRIBUTIONS TO

space & weight saving

IN EQUIPMENT DESIGN

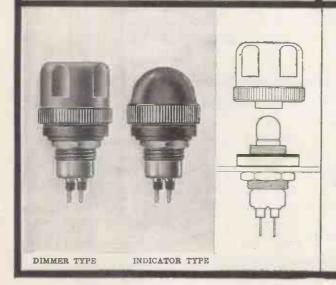ATLAS MIDGET PANEL BULB Overall length: 14.6 mm. Bulb diameter: 6.3 mm. Rating: 28v., 1 watt, 0.04 amp. Also available in 12v., 6v. R.A.E. and S.R.D.E. type approval. Flanged cap and single centre contact for easy replacement.



The need for saving space and weight in modern electronic and panel control equipment is an ever present problem. The Atlas Midget panel bulb was designed with these difficulties particularly in mind. Tiny in size, simply and robustly constructed, its success is confirmed by type approval from the R.A.E., Farnborough, and S.R.D.E., Christchurch.

The development of the Atlas Midget panel bulb made possible the production of the Thorn Miniature Sealed Panel Lampholder, which has been developed specifically for the Armed Services. It is available with dimmer or indicator cap, and will withstand conditions of constant vibration and shock.

Brief details are given below, but further enquiries are invited.

THORN MINIATURE SEALED PANEL LAMP HOLDERS Overall length including

contacts: 1.43 ins. Dia.: .75". Weights: with Indicator Cap 0.276 ozs., with Dimmer Cap 0.644 ozs. Conform to Radio Components Specs. (Prov.) 201, Humidity Class. H.1. Temperature category 40/100 (-40°C. to + 100°C.). Pressure sealed to 20 lbs./square inch.

Completely weatherproof and will withstand conditions of constant vibration and shock. Rotation of the dimmer (cap controls the light output from bright to dim by means of an internal metal shutter. Developed originally for A.F.V.'s, Thorn Miniature Sealed Lampholders have many other obvious applications.

The holders are insulated from the panel which can vary from $\frac{1}{32}$ to $\frac{1}{8}$ thick. Thicker panels may be counterbored. Single hole mounting facilitates fitting. Rotation is prevented by flats on the body. The lamp can be replaced without breaking seals, by unscrewing cap.

THORN ELECTRICAL INDUSTRIES LTD



AIRCRAFT COMPONENTS DIVISION, 105-109 JUDD STREET, LONDON, W.O.1

WIRELESS WORLD

FEBRUARY, 1955

ELAC closed field...

. LOUDSPEAKERS

These loudspeakers have been designed to provide minimum magnetic interference together with high acoustic efficiency. ELAC Elliptical and round loudspeakers are used in most of the leading Television and Radio receivers.

PRICES INCLUDING P.T. FOR LOUDSPEAKERS LESS TRANSFORMER AS FROM NOV. Ist., 1954.

$7'' \times 4''$ Elliptical	Flux 6,500 Gauss	21/10	6 <u>1</u> ″ PM. 6G	Flux 6,500 Gauss	21/10
3 <u>1</u> ″ PM. 3G	Flux 6,500 Gauss	19/10	8″ PM. 8D	Flux 7,500 Gauss	29/1
5″ PM. 5G	Flux 6,500 Gauss	20/6	10" PM. 10D	Flux 7,500 Gauss	34/4



ELECTRO ACOUSTIC INDUSTRIES LTD.

Stamford Works, Broad Lane, Tottenham, N.15

FEBRUARY, 1955



By Appointment to the Professional Engineer



D.C. or A.C. Peak CURRENT CARRYING CAPACITY 5 amps, D.C. or A.C. (RMS) per contact

Although in general the new Painton "Multicon" Series of Plugs and Sockets will be interchangeable with the existing Painton range, the 6-pole Plugs and Sockets have two contacts polarised to eliminate the possibility of 'wrong-way-round' insertion. In the 6-pole size (as on all other "Multicon," sizes when available) there is a complete variety of Plugs and Sockets with alternative mounting arrangements, cable fixings and retaining devices. The "Hammer-finish" silver-grey covers will blend with all equipments.

A low and constant contact resistance is achieved with the heavily silver-plated split contacts.

Any possibility of free moisture remaining between the Plug and Socket face is prevented because spacers keep the mating faces slightly apart, even when the Plugs and Sockets are fully engaged. The patented method of securing both the male and female contacts in the mouldings ensures the satisfactory operation of the Painton "Multicon" range under severe tropical and climatic conditions.



	PLUG		SOCKET			
Cable Cable Entry Entry Top Side		With Mounting Flange	Cable Entry Top	Cable Entry Side	With Mounting Flange	
310009	310018	310007	310008	310029	310006	
FITTED WITH LOCKING CLIP			FITTED WITH LOCKING CLIP			
311291	311292		311294	311295		



310007

500lbs

FEBRUARY, 1955

A headache for

somebody ...

It was a great little portable — but there just wasn't room for the battery. A bitter blow for the designer. Unless specially designed batteries were ordered, he would have to start again. Designers of battery radio sets should note this dilemma. Time, effort (and money) are wasted if you prepare a design and then find you haven't left room for the battery. Ever Ready are always able to make up special units but it's so much simpler to call us in early so that your set is designed, if possible, to take one of our many standard batteries.



DRY BATTERIES FOR RADIOS


If you have a design problem involving dry batteries, get in touch with us at Hercules Place, Holloway, London, N.7 Telephone : ARChway 3030. FEBRUARY, 1955

but for quantity production in electronics..

In the sphere of electronics, whatever you have to produce, whatever its state of development if you want it produced quickly, in quantity, with commensurate quality; if you want it produced economically—it's a job for Plessey!

pairs of trained hands can, if need be, nurse a young idea-develop it-and bring it to full or limited production maturity with a thoroughness that would spell costly delay in any organisation less well equipped. The Division is presently engaged on contracts for for such renowned organisations as B.T.H., Decca, I.A.L., Kelvin Hughes, Marconi's Wireless Telegraph Company Ltd., and Laurence Scott & Electromotors Ltd. If your special interests lie in electronics, serve them well by writing for the Plessey publication which sets out the Division's specialised services.

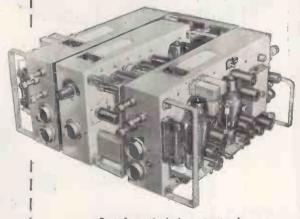At the Electronics Division of Plessey, a thousand



Part of a particularly compact radar installation made for Marconi's Wireless Telegraph Company Ltd.

Plessey

... you should see

ELECTRONICS DIVISION · TELEPHONE VALENTINE 8855 THE PLESSEY COMPANY LIMITED · ILFORD · ESSEX

FEBRUARY, 1955

WIRELESS WORLD

RELAYS=

HERMETICALLY SEALED SERIES 595 H

This is a hermetically sealed version of our series 595 Relay, which is already well known to the aircraft industry.

The armature design reduces the effects of shock, vibration and acceleration; a spring type armature hinge eliminates backlash, friction and risk of displacement.





MAGNE

CES

DE

COIL: In all standard voltages up to 110 V. D.C. Working range between plus 10% and minus 20% of rating.

CONTACT COMBINA-TIONS: up to 2 pole changeover.

BASE: International octal.

WEIGHT: 3¹/₄ ozs.

DIMENSIONS:

Diameter— $1\frac{11}{16}$ " overall. Height — $2\frac{5}{8}$ " overall.

SERIES 595

MD4A

MAGNETIC DEVICES LTD

16

A NEW-PRINCIPLE A-C AUTOMATIC VOLTAGE STABILISER

We have now had released to us by a Government Department the design of our "A.C. Mains Regulator, Automatic, Step, Mark II", and are therefore manufacturing this unit for general sale. It ideally fills the need for a cheap, small and light Stabiliser. Although it measures only $8\frac{1}{2}$ in. x 5 in., weighs as little as 11 lbs., and costs only £24 net, it has a performance fully equal to any similarly rated Automatic Stabiliser of the resonated, saturated core type, without any of the disadvantages.

ASR-1150 has a pure output waveform, is unaffected by changes in mains frequency, and works equally well from no-load to full load, which is 1150 VA. It has a stabilised output at 230V unless otherwise ordered.

Many other Automatic Voltage Stabilisers are now manufactured by us, and all are available for immediate delivery. In some cases the constancy of output is as high as 0.15%. Models are available from 200 VA to 30 kVA, single phase, 3 Phase Stabilisers are also available. Prices are *extremely* competitive.

The NEW "ASR-1150" costs only £24 net

Complete Information is obtainable from: **GLAUDE LYONS LTD.,** STABILISER DIVISION, MEAD OFFICES & WORKS: 16 OLDHALL STREET, LIVERPOOL 3, LANCS SOUTHERN FACTORY: VALLEY WORKS, WARE ROAD, HODDESDON, HERTS: (A10 main London/Cambridge Road, as Junction of A602)

We can supply from stockall types of American tubes, condensers, valves, potentiometers, etc.


MEMO: If you are interested in infinitely-variable Transformers, do not forget the almost indispensable "VARIAC" (Reg'd. Trademark). Models are available from 170VA to 21kVA. Our Catalogue V-549 (3rd Edition) tells the whole story and will gladly be mailed free and post free, on request. **S.E.C**.

GERMANIUM DIODES

GEX 34 in the Ratio Detector

The Ratio Detector has been generally accepted as the most practical form of detector for receivers designed for the new High Quality F. M. Service to be inaugurated next year, since it obviates the need for a separate limiter stage.

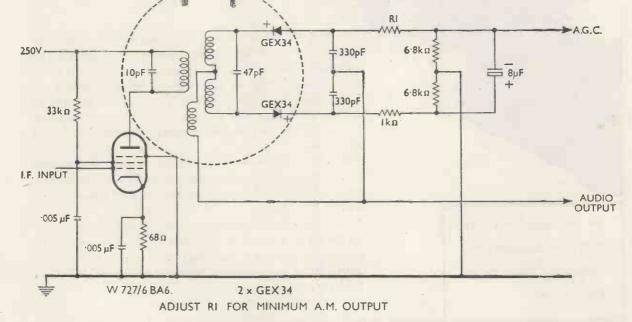The illustration shows the application of two GEX 34 in a typical ratio detector where full advantage has been taken of its small size by enclosing them in the I.F. transformer can. This construction reduces the risk of instability and eliminates the possibility of harmonic feed back via the heater leads.



Transformer Design. Although the circuit shown above is conventional, an I.F. transformer designed for use with thermionic diodes is not necessarily the most suitable for germanium diodes. A suitable design of transformer has been evolved at The G.E.C. Research Laboratories, details of which are available on request.

Write to The Osram Valve and Electronics Department,

THE GENERAL ELECTRIC CO. LTD., MAGNET HOUSE, KINGSWAY, W.C.2.

W 97

W 99

W 61

W 96

W 49

HUNTS METALLISED PAPER

CAPACITORS

TW 54

HUNTS METALLISED PAPER CAPACITORS

Temperature Range

-40°C to + 71°C

-40°C to + 85°C

-40°C to + 85°C

SIZES *A = 1" × it"

-10°C to + 71°C

Working

Voltage

150 D.C.

400 D.C.

600 D.C.

300 A.C.

When it's a question of MINIMUM SIZES ... N 48

MIDGET MOLDSEAL TUBULARS

YPE W99

Heat moulded housing ensuring an adequate seal against moisture. Wire leads soldered directly to capacitor unit in a manner ensuring freedom from intermittent contact (strength of joint exceeds tensile strength of wire lead). leads soldered directly to capacitor unit in a manner ensuring freedom from intermittent contact (strength of joint exceeds tensile strength of wire lead).

Capacitance µ F

0.004 to 0.01 0.02 to 0.04

0.001 to 0.003 0.004 to 0.01

50pf to 0.001 0.002 to 0.004

50pf to 0.001 0.002 to 0.004

B=t"xh

AB

A

B

A

R

AB

TYPE W99 MIDGET MOLDSEAL

TYPE W97 MIDGET THERMETIC -100°C to +120°C

Look to HUNTS!

For maximum reliability. Hunts capacitors for radio and electronic equipment include many types designed to meet the need of designers for decreased dimensions.

Type W99 listed above is just one example taken from Hunts unparalleled range of capacitors for every purpose.

Years of specialisation in nothing but capacitor design and manufacture has enabled us to achieve and maintain that long-lasting reliability, and out-

standing performance which characterises every Hunt product.

Please write for leaflet giving full details of types for all applications.



Capacitance Tolerance: Standard ± 20% (Closer colerance available) Insulation Resistance:

20,000 megoh

working voltage

Power Factor

than 2% at 1.00

per second at 20

A. H. HUNT (Capacitors) LTD., WANDSWORTH, LONDON, S.W.18 BATtersea 1083-7 and in Canada . HUNT CAPACITORS (Canada) LIMITED, AJAX, ONTARIO

High Q inductance coils

wound on Ferroxcube cores

ESIGNERS of compact and efficient tuned circuits and wave filters are making ever-increasing use of Mullard high Q inductance coils.

Based on Ferroxcube, the world's most advanced magnetic core material, these coils combine small size with an inductance of up to 30 henries over a wide frequency range. Furthermore, their convenient shape and self screening properties facilitate either individual mounting or stacking.

Full details of these and other high grade components now available from Mullard will be gladly supplied on request.

Special Features

Small size Low hysteresis loss factor High value of inductance Low self capacitance Controllable air gap facilitating inductance adjustment Self screening **Controlled** temperature coefficient **Operation over a wide frequency** range Easily mounted

'Ticonal' permanent magnets, 'Magnadur' ceramic magnets, Ferroxcube magnetic cores.



LA.I

10

YPICAL

6

LA 3

20

0

600

500

400

300

200

100

0

· LONDON W.C.2 MULLARD LIMITED COMPONENT DIVISION CENTURY HOUSE SHAFTESBURY AVENUE

100

VALUES

1000

New The

& dete "

Super

SUPER OT TWO-SPEED TAPE RECORDER

A truly superb British-made recorder, rich in range and tonal qualities, for home and business recording. Its low price brings high fidelity recording within the reach of all. The "Editor Super" is sufficiently powerful to meet any volume requirement—sensitive encurch to nick up the foliatest whichest enough to pick up the faintest whisper.

> The "Editor Super's" range of tone, from maximum bril-liance to a deep rich bass, IS IDEAL FOR PRE-RECORDED TAPES. It is simple in operation and has an unequalled smooth and reliable control. It is the latest addition to the Editor range of Recorders.



BUY ON THE M.O.S. PERSONAL CREDIT PLAN—10% deposit and balance over 6, 12, 18 or 24 months.

- *
- Recording sense to BSS, therefore suitable for pre-recorded tapes. All leather suitosse with "continental" type of gill locks and fittings. Detachable lid. *

- by Bor Sith Docks and normal. Detectable lid.
 Completely self-contained, portable and compact. Overall size 1611n. x 121n. x 51n.
 Statibility in the self size of the self
 - and flutter.
- TECHNICAL SPECIFICATION
 - Twin track recording GIVING TWO HOURS' PLAYING TIME AT 311n. per
- * *

- AUGAS FLATING THE AI Split. per sec. Single knob control mechanically and electrically interlocked. MIXING AND MONITORING FACILI-TIES for separate Radio/Gram and micro-phone inputs. Tonal balancing control. Amplifier with overall negative feedback uses miniature Mulland valves. May be used independently for P.A. or high fidelity reproduction. Recording level meter by magic eye.

- * Uniform frequency response between 40-10,000 c/s. at 7§in. per sec.
 * Fast forward and fast rewind without unlacing tape, and accidental ersaure made impossible by simple fully automatic control.
- Drop-in Tape loading.
 Positive and instantaneous servo braking on

The "EDITOR" at 45 Gns. is still the lowest priced quality tape recorder. Available on the M.O.S. Personal Credit Plan. as above.

BURGOYNE 2 - SPEED TAPE DECK Here is the heart of your Tape Recorder. If you are building or your Tape modernising your own equipment, you MUST have the latest BUR-GOYNE Tape Deck giving 2 speeds, designed for building into complete recorders.

BRIEF SPECIFICATION ★ 2 HOURS' PLAYING TIME. ★ Automatic speed change. ★ Drop ★ Automatic speed change. ★ Drop in Tape Loading. ★ Instantaneous and positive braking. ★ Minimum wow and flutter. ★ Frequency range 50/10,000 c/s at 7½in./sc. ★ Powered by 3 high-grade motors. ★ Twin-track high impedance heads. ★ Fast forward and rewind without unlacing tape. ★ Overall size 11½in. × 14½in. ★ For 200/250 v. A.C. Mains.

IMMEDIATE DELIVERY FROM STOCK

£13.19.6 (Carr & packing 7/6) BUY ON THE M.O.S. PERSONAL CREDIT PLAN-10% deposit, balance over 6, 12 or 18 months.

ORDER SUPPLY CO. The Radio Centre 33, Tottenham Court Road · London · W.I · Tel. MUS 6667

Brilliant reproduction from 5in. bigh flux P.M. speaker. 4 watts output.
 L.S. Extension sockets and muting switch-

- all functions. For A.C. Mains 200-250 v. 50 c/s.


VISUAL VALVE TESTER

This equipment displays on a cathode-ray tube a family of la/Vg curves for any receiving type thermionic valve. Eleven curves corresponding to eleven different grid voltages are presented simultaneously and a calibrated graticule permits rapid comparison with published data.

Nine standard valve bases are provided, with facilities for connecting others, and the various valve electrodes are connected to the requisite supplies by a multi-button switching board.

This permits any electrode to be connected to any supply without damage and also enables electrodes to be paralleled for test purposes.

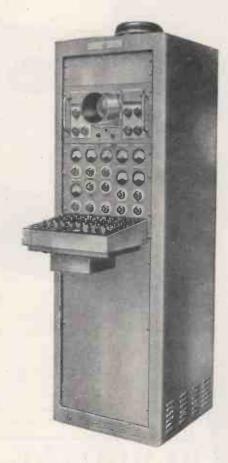All external parameters Va, Vs, Vh, Vg, are continuously variable over a wide range and current and voltage values are metered. Full technical data is available on request.



CINEMA TELEVISION LTD

ARTHUR

RANK

WORSLEY BRIDGE ROAD · LONDON

WITHIN THE J.

COMPANY

LONDON · S.E.26 HITHER GREEN 4600

ORGANISATION

SALES AND SERVICING AGENTS : Hawnt & Co. Ltd., 59 Moor St. Birmingham, 4 Atkins, Robertson & Whiteford Ltd., 100 Torrisdale Street, Glasgow, S.2 F, C. Robinson & Partners Ltd., 122 Seymour Grove, Old Trafford, Manchester, 16



CATHODE RAY TUBES

A wide range of Cathode Ray Tubes and Valves for industrial and domestic use is manufactured by the Electronics Department. 14" and 17" Rectangular Tetrode. Cathode Ray Tubes with Aluminized screens and 6.3 volt, 0.3 amp. heaters are available.

Enquiries to Electronics Dept., Moston, Manchester, 10.





SMALL HERMETICALLY SEALED INSTRUMENTS

Ferranti 2", $2\frac{1}{2}$ " and $3\frac{1}{2}$ " Hermetically Sealed Instruments for Service requirements are available in both moving coil and moving iron types for current and voltage measurement.

Enquiries to Instrument Sales Dept., Moston, Manchester, 10.



FERRANTI LTD · MOSTON · MANCHESTER 10 Head Office and Works : HOLLINWOOD · LANCS London Office : KERN HOUSE, 36 KINGSWAY, W.C.2.

Hifi HIGH FIDELITY AMPLIFIER


The PF91 amplifier, with the PF91A remote control unit, is a versatile and practical combination for those who demand realism in sound reproduction from record players, tape recorders, microphones or radio tuners.

Substantially flat frequency range from 20-20,000 c.p.s., up to 12 watt output.

24

National Physical Laboratory confirms our claims for this amplifier.

SELECTOR

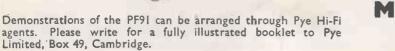

D

TE

MODEL PF91 28 GNS MODEL PF91A 12 GNS

FILTER

TREBLE


BASS

LML

VOLUME

TEST SET R.P. 3110

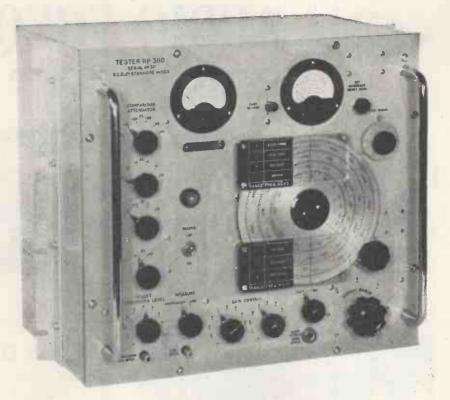A transportable and self contained instrument which provides all the facilities required for measuring the level of a selected signal in the presence of signals of different frequencies.



TECHNICAL DATA

Frequency range: 60 Kc/s to 3,000 Kc/s.

Through or terminated levels, using probe at a point distant from the Tester :--

from +10 db to -61.5 db, reference level 1 mw in 75 ohms.

Terminated levels, signals applied directly to


Tester :---

from +10 db to -81.5 db, reference 1 mw in 75 ohms.

Dimensions: 17'' wide, $15\frac{3''}{4}$ high, 12'' deep. Weight: 75 lbs.

Power supply: 200-250V. A.C. 50 c.p.s. consumption approx. 70 watts.

AVAILABLE FROM STOCK

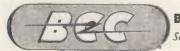

BRITISH COMMUNICATIONS CORPORATION LIMITED

.

Second Way, Exhibition Grounds, Wembley, Middlesex

Telephone: Wembley 1212

FEBRUARY, 1955

AUDIO FREQUENCY EQUIPMENT

POWER OUTPUT METER Type 708

Output powers from 1 milliwatt to 20 watts may be measured by this instrument, in the frequency range 30 c/s to 30 kc/s. No tapped matching transformer is used, and the input impedance remains resistive and constant over the whole frequency range.

Power Range: Frequency Range: 30 c/s-30 kc/s. Input Impedance:

I milliwatt to 20 watts in 4 ranges.

Accuracy:

2, 4, 7, 10, 15, 20, 40, 75, 100, 140, 250, 400, 600, 1,000, 2,000, 3,000, and 5,000 ohms. 10% of full scale power from 30 c/s to 15 kc/s. The meter reading is approximately 1 db low at 30 kc/s.

Price and Delivery: £40 Ex Stock.





L.F. SIGNAL GENERATOR Type 702-

This Signal Generator utilises a resistance-capacitance type of oscillator to provide stable, accurate and easily controlled voltages in the frequency range 30 c/s— 30 kc/s. A screened and balanced output transformer and attenuator enable unbalanced, balanced and floating outputs to be obtained from a source of constant 600 ohm impedance.

Stability:

Frequency Range: 30 c/s-300 c/s, 300 c/s-3 kc/s. 3 kc/s-30 kc/s

±0.05%, ±0.5 c/s. Attenuator:

A 600 ohm constant impedance attenuator provides steps of 20, 40 and 60 db of attenuation under all output conditions.

Price and Delivery: £75 Ex Stock.

FREQUENCY METER Type 726

This instrument indicates directly on a large scale meter, the frequency of any repetitive electrical waveform of amplitude between 0.1 and 20 volts, over the range 20 c/s to 20 kc/s. When used as a tachometer, measurement of speeds of rotary or reci-procating movements may be made up to 1,200,000 r.p.m. without loading the mechanism under test in any way.


 Frequency Range:
 0-200 c/s, 0-2,000 c/s, 0-20,000 c/s,
 0-12,000 r.p.m.

 0-20,000 c/s,
 0-120,000 r.p.m.
 0-1,200,000 r.p.m.
 + 1% of f.s.d. Accuracy: **Power Outputs:** Output Voltages are available for operating Airmec Photocell Equipment. Price and Delivery: £65 Ex Stock.

IMITED

Τ.

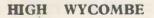Full details of these or any other Airmec instruments will be forwarded gladly upon request.



BUCKINGHAMSHIRE

Telephone: High Wycombe 2060

Cables: Airmec High Wycombe

A PROVED RANGE OF MULTI-WAY PLUGS AND SOCKETS WITH UNUSUALLY LOW INSERTION PRESSURES.

Multi-way Plugs and Sockets with years of experience and application behind them. When specifying these high quality components you will be assured of less insertion pressure per contact than any comparable product can offer, great versatility, and suitability for humid conditions. For rack mounting applications greater latitude in matching up eases the designers problem, and the range of 4, 8, 12, 20 and 28 way units will be found to cover almost every requirement. Widely used by such manufacturers of high quality equipment as:

> Messrs. Marconi's Wireless Telegraph Co. Ltd. Messrs. Standard Telephones & Cables Ltd. The English Electric Co. Ltd.

Full details will be gladly supplied upon request.

POWER CONTROLS

L I M I T E D EXNING RD., NEWMARKET PHONE : NEWMARKET 3181

CONSTANT VOLTAGE TRANSFORMERS IN COLORIMETRY

-but COLOUR MATCHING to-day depends upon CONSTANT VOLTAGE....

In 1955 electronics provides the answer. In colour matching to-day, the precision instruments used must have a reliable and constant voltage supply, and this is one of the many-applications Advance Constant Voltage Transformers fulfil so effectively.

> Full details given in folder W/28 gladly sent on request.

CONSTANT VOLTAGE TRANSFORMERS




28

There are those who consider that there is little to choose in the range of power amplifiers now available—perhaps because the power amplifier is usually considered the "easy" part in the search for audio perfection. Why is it then that leading engineers are so enthusiastic about the QUAD II design?

...on feedbackene lineality

They like the unique integrated feedback to provide complete stability independent of phase changes in the load current . . . the method used for eliminating the loop gain outside the audio range without prejudice to the input signal . . . the way that feedback is again used to provide optimum design stage by stage and to control the effective time constants. They like its use yet again to provide a unique self-balancing phase changer without the usual assymetry to the H.T. line. They like, too, the fact that the specification is fully met with commercially tested valves without matching or alignment of any kind. They extol the conservative ratings and restoration from overload (several nation-wide broadcasting corporations officially uprate the output to 20 watts, since with this degree of overload, distortion is still well within their acceptance figures).

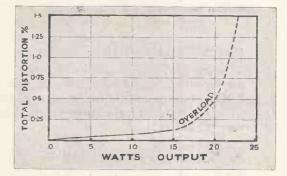Good engineering for the best performance* also results in greater efficiency. Compare the size of the QUAD with any other amplifier of approaching specification. Note the size of the output transformer which results from optimum choice of flux and core material to suit design requirements.



Linearity and overload of the QUAD II amplifier

The QUAD II power amplifier is primarily designed as part of the complete QUAD II amplifier. The power amplifier is also supplied separately as a quality standard when with a suitable input transformer it can be fed direct from a 600 ohm line.

* The unique output stage design principles are discussed in Wireless World, September, 1952.

The QUAD II is available throughout the world. Fully stocked servicing organisations are now operating in Canada, throughout U.S.A., Panama, Canal Zone Trinidad, Jamaica Venezuela, Australia Malaya, Singapore, Japan, Honz Kong, Burma, India, Ceylon, Pakistan, South Africa, Portugal, Italy France Switzerland, Belgium, Norway and Sweden.

CACOUSTICAL ETANUATENDATED

ACOUSTICAL MANUFACTURING CO. LTD., HUNTINGDON, ENGLAND



Now—far ahead of its time—Great new IOKW Short Wave Transmitter!

32 new, special features that won't be matched for years now available in new RCA BHF-10A Broadcast Transmitter!



Front view of BHF-10A transmitter reveals handsome, functional design. Requires only 33 sq. ft. of floor space.

Puts the BROADCASTER far ahead!

The new BHF-10A has sufficient power to cover large service areas; quick frequency change, to increase usefulness; unsurpassed reliability, for unbroken service. The opportunities for commercial stations to increase revenue are *built in!*

Puts the ENGINEER far ahead!

Here are just a few advantages for the *engineer*: easy maintenance, through use of a limited number of high-gain tubes. *Air* cooling. Simplest tuning. Electronically protected circuits – and full power for zonal broadcasting in 90, 75 and 60 metre bands, and international broadcasting over a frequency range of 3.2 - 26.1 mc.

These are just a few of 32 special features of this RCA transmitter that ushers in a new era of radio – proud achievement of RCA's 30 years of broadcast pioneering. Write today for booklet giving complete specifications!

Puts the INVESTOR far ahead!

Years-ahead engineering makes the new RCA 10KW transmitter an exceptionally sound investment. Installation costs are low, for this self-contained transmitter can be installed in existing buildings without alteration. Maintenance has been simplified—and routine operation can be handled by non-technical personnel!



Rear view, power output section showing PA tuning and output coupling unit.



RCA INTERNATIONAL DIVISION RADIO CORPORATION of AMERICA RCA BUILDING

30 ROCKEFELLER PLAZA, NEW YORK, N.Y., U.S.A.

ADVERTISEMENT THE

WE DIDN'T WRITE OURSELVES

The leading experts and users all over the world F. J. CAMM



Editor of 'Practical Wireless' and 'I ractical Television'



IOHN GILBERT of Northern Polytechnic and of B.B.C. Inventors' Club



P. WILSON Technical Editor, The Gramophone'



H.J. BARTON-CHAPPLE Wh.Sch., B.Sc. (Hons.), A.C.G.I., D.I.C., M.I.E.E., Hon. M.Brit. I.R.E.



ORMOND **SPARKES** Radio Consultant and Designer



wrote it for us!

Prov. Patent 10037/53

CAMBRIC CONE Stentorian

UNITS HI-FI

Every claim we have made for these remarkable units has been substantiated by experts and users-they have produced the largest volume of unsolicited testimony ever known in the history of loudspeaker manufacture.

From every part of the world we are told that the quality of reproduction is unrivalled except at many times the price-that these units have enabled everyone to enjoy High Fidelity at realistic cost. We are truly grateful for this amazing response.

Points to note : patented Cambric Cone, high flux density Alcomax magnet, die-cast chassis, Universal impedance speech coil (at 3, 7.5 and 15 ohms) on 8, 9 and 10 inch models. Prices from 37/6 to £9.15.6 (tax paid).

Ready-to-assemble Base Reflex Console Cabinet for 10" or 12" unit £ 10.10.0. Corner Console Cabinet for 8" unit £5.10.0.

Write for descriptive leaflets, or ask your usual dealer to demonstrate. Alternatively, these and other Stentorian speakers may be heard at our London Office (109 Kingsway, W.C.2) any Saturday from 9 a.m. to noon.

WHITELEY ELECTRICAL RADIO CO. LTD NOTTS MANSFIELD



32

Studio microphone

A Ronette "Filtercel" microphone with the fine contours of a studio type utilt, having glogsy black grilles fitted in chrome plated frame. Available with several types of "Filtercel" cartridges. For use with long lines special model with built-in line transformer is obtainable.

Further information regarding these microphones and other Ronette devices will be eladly supplied upon request.

Sole distributors for Gt. Britain: TRIANON ELECTRIC Ltd. LONDON NW10

95, Cobbold Rd., Willesden Telephone Willesden 2116

NEW ARCOLECTRIC SIGNAL LAMPS

For Low Voltage or Mains


Illustrated are a few signal lamps taken from our wide range. The insulation of every Arcolectric signal lamp will resist a flash test of 1,500 volts A.C.

The S.L.90 fillustrated here is a typical Arcolectric fow voltage signal lampholder: "Alt is designed to accept popular M.E.S. butbs. The bulb- is accessible from front or rear of panel. The domed plastic lens surrounded by any polished chrome bezel gives a most or attractive panel appearance. This holder can be fixed in a single 3" hole.

The mains voltage signal lamp S.t. 88/N is supplied complete with an M.E.S. neon tube and a suitable series resistance.

Write for Catalogue No. 128

COLECTRI

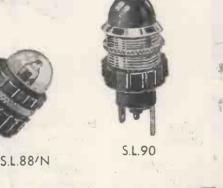



FAMOUS MICROPHONES

S.L.86



5.L.92

S.L.82 S.L.92 S.L.92 CENTRAL AVENUE. WEST MOLESEY, SURREY TELEPHONE: MOLESEY 4336 (3 LINES)

WIRELESS WORLD







33

THE

certone

48 GNS COMPLETE

Abridged Specification

Tape speeds, 71 in. and 31 in./ sec. Fast Forward and Rewind. Self-compensating Servomatic brakes. Single slot loading. Position scales. Inputs Mic., Rad. and Gram. Frequency response 71/in./sec. 50-12,000 cps. within 3db. 33 in./sec. 50-6,000 cps, within 5db, Bias freq., 51 kc/s. Half track recording. Interlocked controls Wow .02% max. Recording to International Standard, Cabinet-Blue and Grey rexine. Storage for Mic. and Mains lead. Detachable lid. Gross weight, 26 lbs. For 210/250 v. A.C. ONLY.

Meticulously recording every tonal facet with complete mastery, the "Concertone" tape recorder will give you the ultimate listening pleasure that comes from superb music faultlessly recorded and reproduced.

MAGNETIC RECORDER

The "Concertone" will re-create, in the home, the true image of the original performance. Whether it be Solo Violin, or Oboe, or a Full Organ with its demanding power and range, the "Concertone" with its wide frequency response, and extended dynamic range, will satisfy the connoisseur of fine music.

Simple, absolutely reliable, rugged, compact, lightweight, and easily portable, the "Concertone" will, wherever there are sounds to be recorded, serve faithfully, earning, justly, unqualified praise for its faultless performance.

Manufactured by the company in its own precision machine shop, the tape mechanism employs three motors and a special design servomatic brake. The brake not only locks the spools securely during transit, but of greater importance, it is completely free from fade, being self-compensating for wear. Unique is the provision of a mechanical interlock which prevents faulty operation.

SEE YOUR DEALER TODAY AND JUDGE THIS FINE MACHINE FOR YOURSELF. IN THE EVENT OF DIFFICULTY SEND DIRECT FOR A COMPREHENSIVE SIX-PAGE LEAFLET (please enclose a s.a.e.).

Trade enquiries cordially invited



FISHER ELECTRONICS COMPANY LTD. 70, BREWER ST., LONDON, W.1. Phone: GER 3376



EXPORT ENQUIRIES TO :- THE BARNETT SHIPPING & EXPORT CO. LTD., 25 MONMOUTH ST., LONDON, E.C.3.

FEBRUARY, 1955

MULTITONE SPECIALIZE

in equipment for the DEAF and for PHYSIOTHERAPY



The ADAPHONE

enables the deaf to hear TV and Radio programmes in comfort and safety and with a clarity unobtainable when using a hearing aid for this purpose. It is also ideal for those with normal hearing who wish to hear the programmes without disturbing others.

The Adaphone has an attractive grey plastic case (3in. x 2in. x 11in.). Weighted straps hold it in position on any chair arm. The input is matched for 2 to 10 ohms connection and the transformer tested to withstand 2,000 volts D.C. The listener can adjust the volume to his individual need without affecting the loudspeaker volume.

Tone control is obtained by alternative output sockets; 'Normal 'and 'High.'

The M3 model has Automatic Volume Compression.

A low-impedance insert-type magnetic miniature receiver of D.C. resistance 30-40 ohms is supplied, but a bone-conduction receiver is available instead, at extra cost, for those who prefer it.

		Complete with					
standard	earm	ould, and leads.			€4	19	0
MODEL	м2	Incomposition	Automatic	Valuma			

Obtainable through all leading Radio Dealers or direct from Multitone Electric Company Limited.

Inquiries should be addressed to **MULTITONE ELECTRIC CO. LTD.** 223-227 St. John Street, London, E.C.I. PIONEERS IN SOUND AMPLIFICATION

MAINS TRANSFORMERS

FULLY INTERLEAVED

SCREENED AND IMPREGNATED. ALL GUARANTEE	υ
ALL PRIMARIES ARE 200/250 v. Half Shrouded.	
HSM63 (Midget). Output 250-0-250 v. 60 m/a., 6.3 v. at 3 amps., 5 v. at 2 amps. [6]	12
HS63. Output 250-0-250 v. 60 m/a., 6.3 v. at 3 amps., 5 v. at	
2 amps	
Output.	·
HS3 350-0-350 v 80 m/a 19/- HS30 300-0-300 v 80 m/a 19	
HS2X. 250-0-250 v. 100 m/a., 21/ HS75. 275-0-275 v. 100 m/a. 21	1-
HS30X. 300-0-300 v. 100 m/a., 21/ HS3X. 350-0-350 v.	
100 m/a 21,	-
Fully Shrouded	
FSM63 (Midget). Output 250-0-250 v. 60 m/a., 6.3 v. at 3 amps.,	
S v. 2 amps	19
FS2. 250-0-250 v. 80 m/a. 21/ FS3. 350-0-350 v. 80 m/a 21 FS30. 300-0-300 v. 80 m/a. 21/ FS3. 350-0-350 v. 80 m/a 21	
F\$30, 300-0-300 v. 80 m/a., 21/-, F\$3, 350-0-350 v. 80 m/a., 21/ F\$2X, 250-0-250 v. 100 m/a., 23/-, F\$75, 275-0-275 v. 100 m/a. 23, F\$30X, 300-0-300 v. 100 m/a., 23/-, F\$3X, 350-0-350 v.	
FS30X. 300-0-300 v. 100 m/a., 23/ FS3X. 350-0-350 v. 100 m/a	1-
All the above have 6.3 4-0 v. at 4 amps., 5-4-0 v. at 2 amps. FS43. Output 425-0-425 v. 200 m/a., 6.3 v. 4 amps., C.T. 6.3 v.	
4 amps., C.T. 5 v. 3 amps. Fully shrouded	/6
FS50. Output 450-0-450 v. 250 m/a., 6.3 v. 2 amps., C.T. 6.3 v. 4 amps., C.T. 5 v. 3 amps. Fully shrouded	6
F35X. Output 350-0-350 v. 250 m/a., 6.3 v. 6 amps., 4 v. 8 amps., 4 v. 3 amps., 0-2-6.3 v. 2 amps. Fully shrouded	_
FS160X. Output 350-0-350 v. 160 m/a., 6.3 v. 6 amps., 6.3 v.	
3'amps., S v. 3 amps. Fully shrouded	
6 amps., 5 v. 3 amps. Fully shrouded	16
3 amps. For receiver R1355. Half shrouded	/6
3 amps. Half shrouded	19
F36. Output 250-0-250 v. 100 m/a., 6.3 v. 6 amps., C.T. 5 v. 3 amps. Fully shrouded	16
FS120. Output 350-0-350 v. 120 m/a., 6.3 v. 2 amps., C.T. 6.3 v. 2 amps., C.T. 5 v. 3 amps. Fully shrouded	
F\$256. Output 250-0-250 v. 80 m/a., 6.3 v. at 6 amps., 5 v. at	
3 amps. Fully shrouded	
FS150. 350-0-350 v. 150 m/a., 6.3-v. 4 amps., 5 v. 3 amps	
C.T. 6.3 v. at 2 amps., C.T. 5 v. at 3 amps. Fully shrouded 31	/6
The above have inputs of 200/250 v.	

OUTPUT TRANSFORMERS

 MIDGET OP.
 5,000Ω to 3Ω
 3/9

 8,000Ω to 3Ω
 3/9

 OPI0.
 10/15 watts output.
 20 ratios on Full and Half Primary...
 17/9

 OP30.
 30 watts output, 20 ratios on Full and Half Primary...
 25/9
 17/9

 OP30.
 30 watts output, 20 ratios on Full and Half Primary...
 25/9
 16/13

 Chokes for Williamson's O.P. Transformer to Author's specification...
 6/4/13/6
 16/6

 10 H. at 150 m/a.
 32/ 32/

FILAMENT TRANSFORMERS

All 200/250 v. Input.

F3. 6.3 v. @ 3 amps.	9/6
F4. 4 v. @ 2 amps., 7/6. F6. 6.3 v. @ 2 amps	7/6
F6X. 6.3 v. @ 0.3 amps., 5/6. F12X. 12 v. @ 1 amp	8/-
FU6. 0-2-4-5-6.3 v. @ 2 amps., 10/ F12. 12.6 v. tapped 6.3 v.	- ,
@ 3 amps.	16/6
F24. 24 v, tapped 12 v. @ 3 amps.	23/6
F29. 0-2-4-5-6.3 v. @ 4 amps., 18/9. FU12. 0-4-6.3 v. @ 3 amps.	17/6
FU24. 0-12-24 v. @ I amp.	17/6
F5. 6.3 v. @ 10 amps. or 5 v. @ 10 amps., or 12.6 v. @ 5 amps.,	
or 10 v. @ 5 amps.	34/-
F6/4. Four windings at 6.3 v. tapped 5 v. @ 5 amps. each, giving	
by suitable series and parallel connections up to 6.3 v. @	
20 amps.	51/6
Quotations, etc. stamped addressed envelope, please.	
desition of the second se	

C.W.O. (add 1/6 in £ for carriage).

Export enquiries invited.

H. ASHWORTH (Dept. W.W), 676, Gt. Horton Road, Bradford 7, Yorks.

35

m-i-n-u-t-e-s into seconds... with the brilliant NEW Superspece soldering iron

ANUFACTURED FOR ENTHOVEN SOLDERS LTD. BY SCOPE LABORATORIES, MELBOURNE, AUSTRALIA

STAR FEATURES

- ★ Heats up from cold in 6 seconds—by a light thumb pressure on the switch ring.
- ★ When not in use, current is automatically switched off—thus greatly reducing wear of copper bit. Electricity consumption is correspondingly reduced.
- **t** It is $10^{"}$ long, weighs $3\frac{1}{2}$ ozs., can be used on 2.5 to 6.3-volt supply. 4-volt transformer normally supplied.
- More powerful than conventional 150-watt irons and equally suitable for light wiring work or heavy soldering on chassis.
- Simple to operate, ideal for precision work. Requires minimum maintenance at negligible cost. Shows lowest operating cost over a period.
- ★ Can be used from a car battery.
- It is by far the most efficient and economical soldering iron ever designed for test bench and maintenance work.

STAR APPLICATIONS

Designed on an entirely new principle, this light-weight, versatile iron is eminently suitable for soldering operations in the RADIO, TELEVISION, ELECTRONIC and TELECOMMUNICATION industries, particularly for all SERVICE work. For general purpose work the Superspeed Iron is the ideal stand-by soldering tool.

The Superspeed soldering iron is available MOM



Write for full particulars, including guarantee terms and free trial facilities, to the sole concessionaires in this country—

ENTHOVEN SOLDERS LIMITED (Industrial Equipment Division), 89 Upper Thames St., London, E.C.4. Telephone: MANsion House 4533

LIST PRICES Subject to trade discou	nts.
Superspeed 3 Soldering Iron	916
Transformer (optional) Replacement Element Replacement Copper Bit	31/6 1/- 10d.

FEBRUARY, 1955

SOUN DTIEUP The Holde A.I.D APPROVED WILLESDEN"TRANSFORMERS ELECTRONIC & TELECOMMUNICATION REQUIREMENTS

WILLESDEN TRANSFORMER CO. LTD., 2a, FRITHVILLE GARDENS, SHEPHERDS BUSH, LONDON, W.12. Telephone: SHE 5819,2714.

T/V TECHNOLOGY RADIO ENGINEERING ELECTRONICS RADIO SERVICING

There's a big future in T/V and Radio. Act now! Increase your knowledge. Back up experience with a sound theoretical background. I.C.S. offer courses of instruction in-

T/Y TECHNOLOGY ADVANCED SHORT-WAVE RADIO & RADIO ENGINEERING & RADIO SERVICE ENGINEERING & RADAR & BASIC ELECTRONICS. FREQUENCY MODULATION.

I.C.S. will also coach you for the following examinations:-B.I.R.E.; P.M.G. Certificate for Wireless Operators; Radio Servicing Certificate (R.T.E.B.); C. & G. Telecommunications, etc., etc.

DON'T DELAY-SEND COUPON TODAY for free descriptive booklet, stating which subject or examination interests you. Fees include all books needed. Examination students coached until successful.

> Reduced terms for H.M. Forces. Dept. 223D, I.C.S., 71 Kingsway, W.C.2.

8.1	
	INTERNATIONAL CORRESPONDENCE SCHOOLS.
	Dept. 223D, International Buildings, Kingoway, London
	W.C.2.
	Please send Booklet on subject
	NameAgeAge

Address

Other People's Amplifiers and Radio Feeder Units

If any reader should have his mind set on a high priced amplifier of another make but would like to save some money if possible, we should like to make the 'following clear-cut offer: if he buys one of our Symphony Amplifiers (Standard or Decca or Studio version) and is not entirely satisfied with it he may return it for full credit against any other amplifier on the market. It should be emphasised at this stage that as Retailers we can supply any amplifier or Radio Tuner advertised in the "Wireless World" or "Gramophone."

GOODMANS CORNER CABINETS (right) for GOODMANS CORNER CABINE IS (right) to the AXIOM I50 Mark 2 manufactured by us to Messrs. Goodmans' measurements. Height, 44In. Price: complete kit in plain board with lin. thick felt, 8 gns Price ready built, 10 gns. Finished in figured walnut, 16 gns. Other veneers to order. Carriage walnut, 16 gns. Other extra according to area.

FREQUENCY MODULATION TUNER UNITS

We have carefully tested the few makes of F.M. Tuners on the market at present and are pleased to be able to recommend and supply the following: **CHAPMAN Model FM81.** Tuneable Model with attractive facia panel and dial. Will provide amazing degree of realism with complete absence of back-ground noise when working with the N.R.S. No. 2 Symphony Amplifier or other high grade amplifier. Price £21. Call for a demonstration or send for leaflet.



TAPE DECKS AND AMPLIFIERS

ELPICO Tape Deck as per "Impresario" Recorder, push-button controls, high-fidelity heads. Price 19 gns. TAPE AMPLIFIER as per "Impresario" Recorder. Separate Treble and Bass controls, neon level indicator. Price 19 gns. TRUVOX Tape Deck Mark III. Price 22 gns.

TAPE AMPLIFIER TYPE C, expressly designed by Truvox to work perfectly with their Deck. 3 valves plus rectifier and Magic Eye level indicator. Price 16 gns.

NORTHERN RADIO SERVICES


Phone: PRImpose 8314 IF KINGS COLLEGE RD, ADELAIDE RD., LONDON, N.W.3 Tubes: Swiss Cottage or Chalk Farm

WIRELESS WORLD

REAL HIGH FIDELITY at modest cost.

•Manufacturer-to-Consumer policy saves you at least one-third cost!

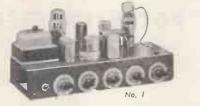We are now specialising in the supply of units for making up high-fidelity Radio and Record-reproducing Equipments for use in the Home small Halls, Schools and Gramophone Societies and single items for replacing in existing equip-ments and radiograms. Our Chief Engineer, who is operating a Technical



No. 1 "SYMPHONY" AMPLIFIER is a 3-channel 5-watt Gram/Radio Amplifier with astonishingly flexible tone control. You can lift the treble, the bass, or—and here is the unique feature—the middle frequencies to suit your own ear characteristics and the record or radio programme being heard. It is thus possible to arrange the frequency-response of the amplifier to a curve equal and opposite to the resultant curve of the other items in the chain so that what finally registers in the brain is as per original. This flexibility of control is far more imporper original. This flexibility of control is far more impor-tant than mere nominal linear response of the amplifier, as the pick-up, speaker, etc., are not linear. Independent Scratch-Cut is also fitted and special negative-feedback circuit employed. The Amplifier can accommodate a wide variety of records from old 78's to new L.P.'s. Input is for all types of pick-up of 0.1 v. output or more and there is full provision (and power) for Radio Tuner. It is available to match 213 or 15 ohms speakers. Price: 10 gns. (carriage 5/-). Fitted in portable Steel Cabinet, 35/- extra.



No. 2 "SYMPHONY " AMPLIFIER as No. 1 but with No.4 "STMPHONT "AMPLIFIER as No. 1 but with 10-watt Push-pull triode output and triodes throughout. Woden mains and output transformers and choke. Full provision and power for Tuner. Output tapped 3, 7,5 and 15 ohms. Competes with the most expensive ampli-fiers on the market yet costs only 15 gns. (carriage 5/-). Fitted in portable Steel Cabinet 2 gns. extra.



"SYMPHONY" AMPLIFIERS with REMOTE CONTROL. Both the above model Amplifiers are available with all controls on a separate Control Panel with up to 4 feet flexible cable which simply plugs into the amplifier. Enables the Amplifier proper to be sat in the bottom of a cabinet whilst the controls are mounted conveniently higher up. Extra cost 2 gns.

"STUDIO SYMPHONY " AMPLIFIERS, Models' "STUDIO SYMPHONY" AMPLIFIERS, Models 1 and 2, new models specially designed to get the maximum out of the revolutionary new Collaro Studio pick-ups and heads type "P" or Transcription. Specification as per our Standard Symphony models but with high-gain, low-noise, built-in Pre-amplifier stage with separate switch correctors for Std. and L.P. Third position on switch provides input matching for Acos and similar output pick-ups. These remarkable new models thus provide all the facilities and matching of our Standard Symphony Amplifiers PLUS the specialised Collaro matchings. Send for copy of "The Gramophone" review of these instru-ments. Price: No. 1, 12 gns; No. 2, 17 gns. Carriage 5/- Guldance Service, is available daily, including Saturdays, from 10 a.m. to 6 p.m., or will deal with enquiries by return of post. Our new illus-trated Catalogue and Supplement will be a great boon to those desiring high quality equipment for modest expenditure. Send two 21d. stamps for your copy now. It may well save you pounds.

CURRENT GARRARD PRODUCTS AVAILABLE FOR IMMEDIATE DELIVERY FROM STOCK AT PRESENT.

MODEL TA 3-speed unit, but with plug-in turnover head Type G.C.2, £10/16/-, or with Acos HGP 33 or 37 heads, £10/14/-, or with two separate high fidelity Acos HGP35 heads, £12/17/-. Unit less heads, £8/11/-, post 2/6. Heads, 42/3 each, post 1/-.

post 2/6. Heads, 42/3 each, post 1/-. **MODEL TB** as above, but with long pickup arm. Less heads, £8/11/-, post 2/6. Heads to fit this unit: Decca XMS, 55/-, Decca Crystal, 35/-, Garrard Standard Magnetic, 25/-, miniature magnetic ow impedance, 25/-, miniature magnetic high impedance, 35/-. Post on heads 1/-. Unit can be supplied with any combination of above heads and is carefully adjusted for stylus pressure on depatch. stylus pressure on despatch.

MODEL RC80M, less heads, £15/5/-, with new turnover head, £17/9/6, with two separate Acos HGP35 heads, £19/9/-, carriage 5/-.

COLLARO PICKUPS AND HEADS. Studio Pickup Arm, 13/10. Studio Pickup head type "O" or "P." (3/0/9. Pickup complete £3/14/7. Studio Transcription Pickup Arm with Studio." P " head, £4/15/9. Ditto with Transcription head, £5/2/5.

TRANSCRIPTION MOTORS IN STOCK. CONNOISSEUR, 3-speed motor, £23/8/11.

SNIP NO. I

SMIP NO. 1 GARRARD LATEST MODEL RC80M AUTO-CHANGER. Fitted with full-length Pick-up Arm to take 3-pin plug-in heads, manufactured end of Oct. 1954. PRICE LESS HEADS, £15/5/-, plus careiage 5/-. These extraordinarily versatile units can be supplied fitted with the following combinations of Pickup Heads with the following receiver. at the following prices

- With two Decca XMS firr Magnetic Heads, £20/15/-With two Decca Crystal Heads, £18/10/-, With Decca Crystal Heads, £18/10/-, With Decca Crystal for L.P. and Garrard Miniature Mag, for Std. Takes miniature fibre or steel needles.
- /ith adaptor and two Acos HGP39-1 Heads, £20/5/-. With
- With adaptor and one Acos HGP39-1 Head for L.P. and Garrard Miniature Mag High Impedance for Std. Takes miniature fibre or steel needles. £19/17/-.

LEV/11/--The above combinations of heads are matched for output and stylus pressure carefully adjusted before despatch. Carriage in each case 5/-. Above mounted in Portable Cabinet 90/- extra

IMMEDIATE DELIVERY FROM STOCK

SNIP NO. 2

SNIP NO. 2 Very latest Model "MONARCH "3 speed AUTO-CHANGER fitted with latest ACOS HGP37 turnover Pickup Head for Std. and L.P. Plays I2in., 10in., and 7in. records mixed in any order. Capacity 10 records. Operates on 100/125 and 200/250 v. A.C. 50 c/s. Unit plate measures 124in. x 104in. Height above plate required 52in.; depth below required 24in. PRICE COMPLETE 613/10/-. Carriage 5/-. IMMEDIATE DELIVERY. Leaflet 24d.

Above mounted in Portable Cabinet, 16 gns., plus carriage 7/6.

"SYMPHONY" BASS REFLEX CABINET KITS. 30in. high, consist of fully-cut ³/₂in. thick, heavy, inert, non-resonant patent acoustic board, deflector plate, felt, all screws, etc., and full instructions, 8in. speaker model, 85/-; 10in. speaker model, 97/6; 12in. speaker model, 45/7/6. The design is the final result of extensive research in our own laboratory and is your safeguard of optimum acoustic results. Carriage 7/6. Ready built, 10/6 extra.

HIRE PURCHASE FACILITIES NOW AVAILABLE on orders of £15 or over. Send one-third deposit with order, balance over 6 or 12 monthly instalments. State which required. 12 monthly instalments.

NORTHERN RADIO SERVICES II. KINGS COLLEGE RD., ADELAIDE RD. LONDON, N.W.3. Phone: PRImrose 8314 Tubes: Swiss Cottage and Chalk Farm. Buses: 2, 13, 31, 113, 187.



"SYMPHONY" BASS REFLEX CABINETS, fully finished in figured walnut, oak or mahogany to our own design and to match our Console Amplifier Cabinet, enabling the housing of a whole enuinment in a two hiere suite: enabling the housing of a whole equipment in a two piece suite; cost: 12in, speaker model, £11/10/-; 10in, £11; 8in, £10/10/-, Carriage according to area. The 10in, model is ideal for the WB HF 1012 (see "The Gramophone" review March) March).



CONSOLE AMPLIFIER CABINETS (above), 33in. high, lift-up lid with piano hinge, take Tape Duck, Gram Unit or Auto-changer, Ampli-fier. Pre-Amplifier, and Radio Feeder Unit, finished medium walnut veneer. De Luxe version, 10 gn. Carriage according to area. Other veneers 10⁴, extra.

38

WIRELESS WORLD

FEBRUARY, 1955

• with concentric

operating spindles

Q.M.B. ACTION

MAINS SWITCH

THOROUGH SCREENING

BETWEEN SECTIONS





POINT-TO-POINT FM V.H.F.

RADIO TELEPHONE LINK



There are many V.H.F. links which require one channel only in the first place but where, after a year or two, an expansion of traffic is anticipated. The Pye F.M. link system with a capacity for up to 7-channels is well suited to meet such a need.

The equipment illustrated comprises a complete radio terminal including Receiver, 10 watt Transmitter and an optional 50 watt Amplifier.



Abbreviated Specification Frequency range 60-216 mc/s Transmitter output Power Io watts, or with Amplifier Unit-50 watts Maximum Deviation 50 kc/s Overall Transmitter-Receiver Performance Frequency Response 300 c/s-6 kc/s±3 db 6 kc/s-36 kc/s±1 db Intermodulation Level At least-55 dbm for 2 tones applied each at 0 dbm Receiver Bandwidth 6 db down + 120 kc/s





Pye New Zealand Ltd. Auckland C.I., New Zealand

Pye Radio & Television (Pty.) Ltd. Johannesburg South Africa

- PYE LIMITED

Pye Canada Ltd. Ajax, Canada Pye Limited Plaza de Necaxa 7 Mexico 5 Pye-Electronic Pty., Ltd. Melbourne, Australia

elbourne, Australia Pye Limited Tucuman 829

Buenos Aires


CAMBRIDGE

Pye Ireland, Ltd. Dublin, Eire

Pye Limited Sth Avenue Building 200, 5th Avenue, New York

ENGLAND

For the LABORATORY and PRODUCTION LINE

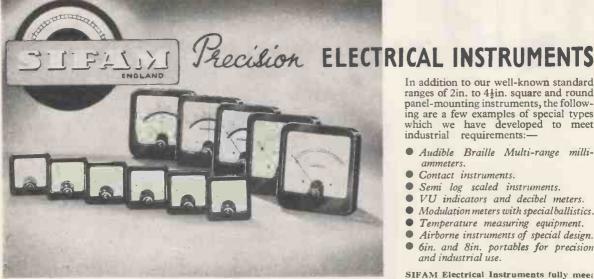

Write for illustrated 'catalogue detailing the wide SIFAM range.

In addition to our well-known standard

ranges of 2in. to 41 in. square and round panel-mounting instruments, the following are a few examples of special types which we have developed to meet industrial requirements:—

- Audible Braille Multi-range milliammeters.
- Contact instruments.
- Semi log scaled instruments.
- VU indicators and decibel meters.
- Modulation meters with special ballistics.
- Temperature measuring equipment.
- Airborne instruments of special design.
- 6in. and 8in. portables for precision and industrial use.

SIFAM Electrical Instruments fully meet the high standards of accuracy and re-liability demanded by modern industrial techniques, production control, laboratory testing, etc.

SIFAM ELECTRICAL INSTRUMENT CO. LTD. Leigh Court, Torquay. Telephone : TORQUAY 4547-8



Lend your skill to Britain, doing - the job you know best



to spend FIFTEEN DAYS IN CAMP earning full pay and allowances plus a total of £9 TAX FREE BOUNTY & EFFICIENCY GRANT.

You can spend fifteen days with your friends, earning full Regular Army pay and allowances. As a member of the Army Emergency Reserve (Cat. IIA) you have no other duties during the year. If a grave national emergency should arise, you may be called up for service in the United Kingdom. You can be called out for overseas service only by Proclamation.

Volunteers are accepted from 18 years of age and engagement is for two, three, or four years. If you have served before in a non-commissioned rank there is every possibility of your filling an existing vacancy or of being promoted as soon as a vacancy occurs.

H.Q., A.E.R., R. Signs., Blacon Camp, Chester.	o O.C.
NAME	
ADDRESS	-
	~D 510


(8)

FLUX DENSITY-GAUSS

WIRELESS WORLD

Standard

magnetic alloys for component designs

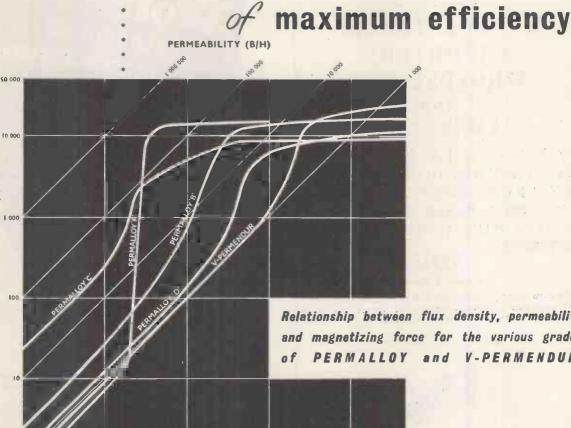

Relationship between flux density, permeability and magnetizing force for the various grades PERMALLOY and V-PERMENDUR.

MAGNETIZING FORCE-OERSTEDS (H)

10

0.1

HIGH quality and consistency, backed by first-class service, are important features in this range of *Standard* magnetic alloys. As large-scale users of Permalloys in communication, electronics and other fields, Standard enjoy the unique advantage of observing these alloys under normal working conditions, a factor which has played an important part in their development.

Please ask for further particulars.



0.01

Standard Telephones and Cables Limited

Registered Office: Connaught House, Aldwych, W.C.2

TELEPHONE LINE DIVISION : North Woolwich, London, E.I6,

42

FEBRUARY, 1955





Obtainable from all leading tool merchants and factors. Fully descriptive Brochure free on request.

WOLF ELECTRIC TOOLS LTD + PIONEER WORKS + NANGER LANE + LONDON + W.S The PERIMALE Self + Branches Birmingham, MANCHESTER, LEEDS, BRISTOL NEWCASTLE, GLASGOW

43



NEW!! JUST RELEASED!!

T.V. SWEEP OSCILLATOR

Model 92A Covering Band III

Frequency modulated oscillator designed for the rapid and accurate alignment of T.V. receivers. Also suitable for checking in band pass amplifier.

Frequency range: Frequency devlation: Output: Amp. Mod.: Sweep: Power Supply: Valves: Weight: Dimensions:

5-250 mc/s. Continuously variable to approx. 15 mc/s. 40 microvolts to 2 millivolts continuously variable. Substantially linear to 6 mc/s sweep width—less than 10% max. sweep. Sweep voltage continuously variable to a max. of 300-v R.M.S. 110/250 v. 4/100 c s, 40 watts approx. ECC91-2 off, 6Z4-1 off, 12AT7-1 off, Z309-1 off. 151b. approx. (6.8 kg). Sin. x 13in. x 9in. (12.7 x 38 x 23 cms).

Cash Price £30.0.0 PROMPT DELIVERY

Write for Illustrated Catalogue and Separate Leaflet

NEW T.V. SIGNAL GENERATOR Model 67A

This reliable Signal Generator is intended for T.V. and Radio Service work. The Colpitt's oscillator circuit used on all ranges gives good frequency stability and waveform.

requency range:	100 Kc/s-240 Mc/s.
Accuracy:	+1%.
Attenuation:	Continuously variable 100 dB.

Gash Price £22.0.0 PROMPT DELIVERY

Write for Illustrated Catalogue and Separate Leaflet


All Taylor Instruments are available on 3 months "No Interest" H.P. terms. Alternative advantageous terms for 10 and 15 months.

 TAYLOR
 ELECTRICAL
 INSTRUMENTS
 LTD.,
 MONTROSE
 AVENUE,
 SLOUGH,
 ENGLAND

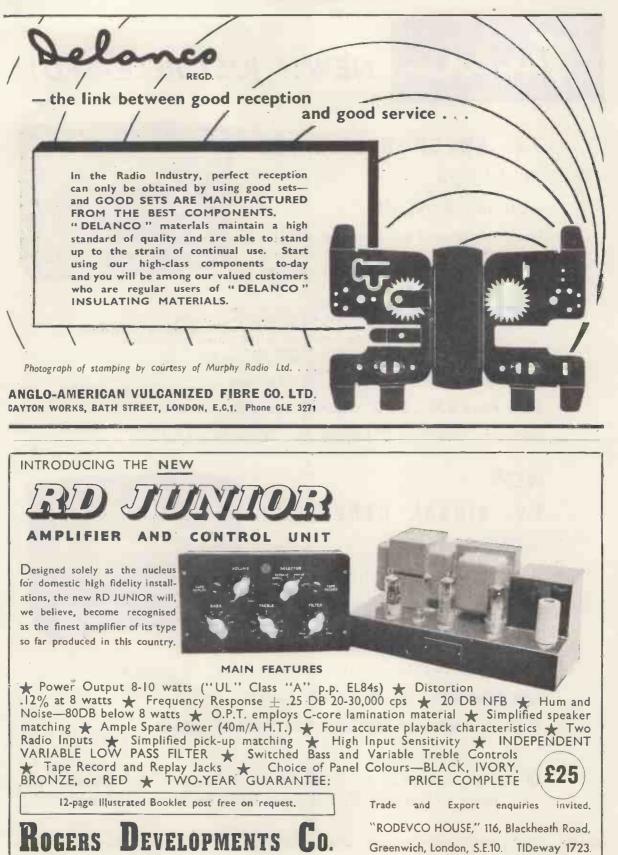 Telephone:
 SLOUGH 21381/3
 Telegrams:
 TAYLINS,
 SLOUGH.








FEBRUARY, 1955

44

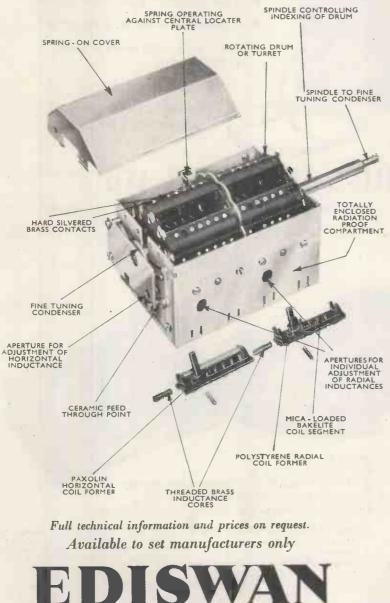Six Advantages of the Clix TELEVISION TURRET TUNER



THE EDISON SWAN ELECTRIC CO. LTD. Member of the A.E.I. Group of Companies

Accurate switching.

The rotating drum of the **Ediswan Clix Television Turret Tuner** indexes accurately to any of twelve positions and re-sets precisely in these positions after switching. No question of mistuning after switching.

All circuits are adjustable with the unit in position in a Television receiver.

Adjustable cores to all inductances are easily accessible with the tuner in position in a Television receiver.

The tuner can, therefore, be set up or re-adjusted in its actual operating position.

Additional tuned circuits may be added at any time without removing the Tuner from the receiver.

The Ediswan Clix tuner is designed so that additional coil segments can be added at any time while the tuner is in position in a receiver.

To tune to another channel the serviceman merely clips into position additional coil segments, carrying correctly wound coils, and trims them by the adjustable cores provided.

There is no need to dismantle the tuner or return it to the Factory for any part of this operation.

Wiring reduced to an absolute minimum thereby eliminating stray capacities.

Stray capacities between wiring can lead to serious mistuning on the very high frequencies of Television Band 3. The Ediswan Clix Tuner is designed so that wiring is reduced to an absolute minimum and materials are specially selected to overcome the problems of drift and instability encountered on these frequencies.



Easily accessible for servicing.

The 'L' section and 'U' section which form the Ediswan Clix tuner are easily parted without removing the drum. This gives easy access to the wiring on the 'L' plate for servicing purposes.

Suitable for mounting in deep or shallow chassis.

Four 4BA tapped holes are provided for mounting the Ediswan Clix Turret Tuner. If required, suitable mounting brackets can be provided for use in shallow chassis.

CR5

155 Charing Cross Road, London, W.C.2. Radio Components Sales Office: 21 Bruton St., London, W.1. Tel: Mayfair 5543

FEBRUARY, 1955

FOR T.V. SERVICE ON BAND II T.V. SERVICE PATTERN GENERATOR TYPE GM 2891 1 I. Covers both Band I and Band III 2 Frequency and Channel indication on dial **3** Video signal both positive and negative 4 Simultaneous sound and video carrier 5 Can be used either locked to mains or free running 6 Choice of four patterns 7 Can be supplied for other T.V. systems than B.B.C. (Made in Holland) LECTRICAL INDUSTRIAL DIVISION CENTURY HOUSE . SHAFTESBURY AVENUE . LONDON W.C.2 ARC AND RESISTANCE WELDING PLANT AND ELECTRODES · HIGH FREQUENCY GENERATORS · ELECTRONIC MEASURING INSTRUMENTS MAGNETIC FILTERS · BATTERY CHARGERS & RECTIFIERS · LAMPS & LIGHTING EQUIPMENT · X-RAY EQUIPMENT MAGNETIC (PM10068)



The AC60 recording amplifier is exactly as used in the new "Impresario" Tape Recorders and is designed primarily for use with the "Elpico" Tape Deck. Together, they provide the finest tape recorder of the age as well as concurrent or independent use as a high fidelity amplification system with a frequency response substantially flat from 48-15,000 cps.



PHILIPS

the short answer

Neither we nor our licensees infringe any competitor's patents.



PHOTO PRINTED CIRCUITS LTD.

GUILDFORD ROAD BISLEY SURREY Telephone: BROOKWOOD 2200

FEBRUARY, 1955

MVM266A

Industry is Solving Valve Testing Problems

WITH THE Mullard HIGH SPEED VALVE TESTER

> Industries which deal extensively with radio and other electronic equipment are finding the Mullard High Speed Electronic Valve Tester ideal for routine checks. This instrument provides the quickest method of checking large quantities of valves, and can be operated if necessary by nontechnical personnel after only a few minutes' instruction.

> Write for full details and a copy of the folder "High Speed Testing in Industry" to Department E.V.D. at the address below.

> > Mullard

Mullard

MULLARD LTD., CENTURY HOUSE, SHAFTESBURY AVENUE, W.C.2

Bullers CERAMICS

High quality material and dimensional precision are attributes of Bullers diepressed products. Prompt delivery at competitive prices.



We specialise in the manufacture of --- PORCELAIN



5300

for general insulation

REFRACTORIES for high-temperature insulation FREQUELEX for high-frequency insulation PERMALEX & TEMPLEX for capacitors





BRITAIN'S MOST POPULAR 15 WATT HIH LOUDSPEAKER

om 150 MARK II

BRIFF SPECIFICATION

Frequency coverage Fundamental resonance 35 c.p.s. Flux density 14,000 gauss. Nett weight

80-15,000 c.p.s. 12 lb. 18 oz.



GOODMANS INDUSTRIES LTD AXIOM WORKS, WEMBLEY, MIDDX .. WEMbley 1200 PRICE £10.5.6 (TAX FREE)

POST THE COUPON BELOW for full details of the Axiom 150 Mark II and our other High Fidelity loudspeakers including crossover systems. bass reflex chambers, etc.

To: GOODMANS INDUSTRIES LTD.
Axiom Works, Wembley, Middlesex.
I am interested in:
Name
Address
WW/2/55 Please write in block capitals

49

meet a nee

Since the Copenhagen Wavelength Convention in 1948 there has been rapid deterioration in the reception on both medium and long wave stations, until we arrive at a position where nearly 800 stations are transmitting on space that can only accommodate 250.

In July of last year the P.M.G. announced the B.B.C.'s scheme for a series of F.M. stations to overcome


Specialists in High Quality Reproduction for

Circuit: A low noise triode R.F.

stage is coupled to a high stability frequency changer. This is frequency changer. This is followed by two I.F. stages and a triple diode triode ratio detector and A.F. stage. Coverage: 85 to 95 mc/s. Output: 3 volts r.m.s.

unnounce

the present chaotic conditions. The B.B.C. are now transmitting F.M. programmes from Wrotham in Kent of unsurpassable quality with un-canny freedom from background canny freedom from Dackground noise. The F.M. service will shortly parts of the be extended to many parts of the country. The listener must now do his share by using equipment capable of doing justice to these high quality transmissions.

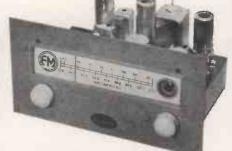

- PERMEABILITY TUN-ING combined with special temperature compensated capacitors in the oscillator circuit ensuring FREEDOM FROM DRIFT.
- MAGIC EYE tuning indi-cator to facilitate accurate . tuning.
- AUTOMATIC LIMITING is achieved by the use of a balanced ratio detector dis-criminator, and an I.F. limiting stage.
- VALVES. The latest type MULLARD ECC85, EF85, EABC80, EM34.



An A.F. attenuator enabling the unit to be used with a high gain amplifier* or a domestic radio receiver such as the ARMSTRONG FC.48.

See page 75 for details of the Arm-strong A.10 High Fidelity Amplifier. * See

enables the unit to be used with any amplifier having auxiliary power supplies of from 250 to 400 volts.

Telephone : NORth 3213.

position input


socket

Visit our Showrooms (address below). Weekdays 9-6 p.m. (Sats. until 5 p.m.). High Fidelity Demonstration on Thurs. at 7 p.m. For further details write to Dept. W.F.

ABMSTRONG WIRELESS & TELEVISION CO. LTD., WARLTERS ROAD, LONDON, N.T.

Image Rejection: 26 db

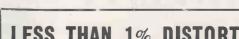max. Image Rejection: 26 db. I.F. Rejection: 60 db. Power supplies required: 30 mA. at 250 volts 6.3 v. 2 amps. Size: Panel 9₹×5{ cut-out required: 9in. ×4[in. Price: £21.0.0 (inc. tax).



Handles with many times the life of wood and blades of Sheffield steel. chromium-plated to prevent rust, combine to make Screwmasters that will last a lifetime. Fully insulated to 5,000 volts



LESS THAN 1% DISTORTION

TAPE RECORDISTS! Are you COMPLETELY satisfied with your recordings? Bad waveform in an oscillator can cause DISTORTION due to intermodulation. NOISY BACKGROUND due to D.C. component in an asymmetrical waveform and INTERFERENCE with radio due to harmonics beating with incoming signal. The fundamental cannot do this!

fundamental cannot do this! The Ordinary Hartley circuit suffers from the disadvantage—that good waveform, large output, and stability do not go together. The new HATFIELD oscillator is GUARANTEED to give at least 4 watts output with less than 1% distortion, and high stability, using only one valve (6V6 or similar). 45 Kc/s to 50 Kc/s. Suitable for high impedance heads, Motek, Lane, Truvox, etc. COIL, complete with circuit, 10/6 post free, Patent app. for.

BIAS REJECTOR COILS Even a small amount of bias frequency getting into the amplifier can cause a lot of trouble, and nearly all tape recorders need a rejector to prevent this. COIL, complete with instructions, 5/6 post paid.

MOTEK TAPE DECKS The famous K6 deck; twin track, two speed, with push buttons and electronic braking, is a beautifully finished job at only £19/19/-. Post free. Or £3 down and 12 monthly payments of £1/10/-

TAPE AMPLIFIERS

The HATFIELD amplifier is complete with oscillator as above, and magic eye, less speaker, at £12/15/-.

COMPLETE RECORDERS

The HERGA recorder incorporates ALL the above items together with a first-class crystal mike and one reel of SCOTCH BOY tape in an attractive two-tone portable cabinet, absolutely complete at 39 gns. Or £5 down and 12 monthly payments of £3/3/4.

Further details and H.P. terms from:



LEXIBLE REMOTE CONTROL OUTFIT

CONTRO

50

NSTRUCT

10

NS



SEL

Our experience in the industrial field has indicated that there is a definite need for this type of outfit offering facilities for making prototype flexible remote controls as required.

The three gauges of Remote Control flexible shafts in these outfits cover the range of torque loadings required for • volume controls • all types of wave change switches • condensers • all controls likely to be met in electronic, radio and television equipment.

These outfits are reasonably priced and comprise:

- 14 H

No. 117 (.117 in. dia.) for remote controls up to 3 in. in length£6.10.0 No. 130 (.130 in. dia.) for remote controls up to 7 in. in length£7. 0.0 No. 150 (.150 in. dia.) for remote controls of a heavier type up to 12 in. in length.......£7.10.0

LTD

BRITAIN

The S. S. White Company will be pleased to advise which Outfit is most suitable for specific applications.

A detailed Parts List is available upon request.

BRITANNIA WORKS, 25-31 ST. PANCRAS WAY. LONDON, N.W.I. Telephone : EUSton 5393

REAT

A /

FEBRUARY, 1955



Williamson Amplifiers (below) Type Illustrated is the GW12 fitted with large 'C' core output transformer. Price GW18 £33:15:0 with 'C' core £38:5:0. GW12 £27:10:0 with 'C' core £32:0:0.



Type PFA Pre-amplifiers (above) The latest PFA unit is built especially for use with our range of Williamson Amplifiers. Separate bass and treble control in equallser section. Low noise—high gain. 5 mv. input. 6 valves. Price £20.

Derronstrations of all these units at B.K. Partners Ltd., 229 Regent St., London, W.I. and Classic Electric Co. Ltd., Croydon.

40 Gardner Street · Brighton 1 · Sussex Tel. : Brighton 26735



have pleasure in introducing the



Corner Horn Assembly

Designed and executed for those who appreciate near perfection in Sound Reproduction.


★ H.P. TERMS AVAILABLE

This and other fine loudspeaker systems are demonstrated daily at our Regent Street Showrooms on audio amplifiers by LEAK, GOODSELL, ACOUSTICAL, ROGERS and ARMSTRONG.

Send for illustrated brochure.



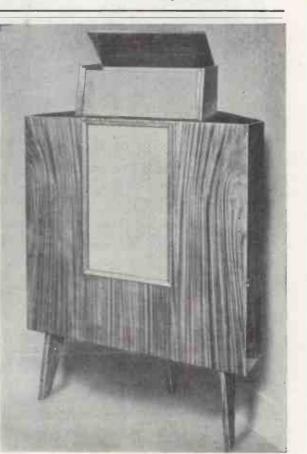229 Regent St., London, W.I. (Entrance Hanover St.) 'Phone: REG 7363



52



The crescendo of an approaching train is one of those complex sounds which are such a test of fidelity in a reproducing system.

How far a Set Designer can go along the line to fidelity is often a question of cost. Presence for price, we believe he should go just as far as Wolverhampton. We would not mention this if it were only our own opinion, but we are proud to say it is also that of many very good engineers who have no axe to grind. Incidentally, the sound of axe grinding is rather a pretty test of fidelity!

REPRODUCERS AND AMPLIFIERS LIMITED . WOLVERHAMPTON . ENGLAND

FEBRUARY, 1955

for unfailing activity

SUB-MINIATURE QUARTZ CRYSTAL UNITS

Type BA, frequency change not exceeding 0.01% from $0^{\circ}C$ to $+70^{\circ}C$ Type DA, frequency change not exceeding 0.01% from $-30^{\circ}C$ to $+45^{\circ}C$ Type EA, frequency change not exceeding 0.002% from $+65^{\circ}C$ to $+80^{\circ}C$

For further details please apply to :-

SALFORD ELECTRICAL INSTRUMENTS LTD PEEL WORKS • SILK STREET • SALFORD 3 • LANCS A Subsidiary of THE GENERAL ELECTRIC CO. LTD. OF ENGLAND

Now! it's easy to edit tapes-economically




USE A PROFESSIONAL TYPE RECORDING TAPE SPLIGER FOR EDITING AND MENDING RECORDING TAPE

The Bib Recording Tape Splicer enables you to edit tapes easily in the same way that cine film enthusiasts edit films.
Tapes can be joined precisely and quickly and, because you can use up all odd lengths of tape, you soon save the cost of the Splicer.

• Sturdily made of nickel-plated brass, the Bib Splicer is mounted on a flock-covered panel. The razor cutter fits neatly under the Splicer. If desired the Splicer can be attached directly to a tape recorder deck. The Bib Splicer is made to an accuracy of plus or minus one thousandth of an inch. It is equally efficient for joining broken recorded tapes without any recorded signals being missed. • Bib Recording Tape Splicer (Prov. Pat. 25520) enables tapes to be accurately positioned, cut and surplus cellulose tape trimmed. Joins are not discernible when these tapes are re-used. 18/6



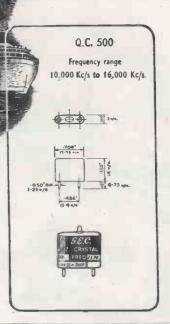Dept. WW2, MULTICORE WORKS, HEMEL HEMPSTEAD, HERTS (BOXMOOR 3636)



SHORTAGE OF RADIO & T/V ENGINEERS

The demand of Industry for our trained students is still greater than we can supply—and is likely to remain so for many years.

We offer

FULL TIME DAY COURSE 1-year course in Principles and Practice of

Radio and Television.

Next course commences April 19th, 1955.

Write for FREE BROCHURES giving details of the above, of our 3-year course (commencing 29th August) and of others.

E.M.I. INSTITUTES—the only college which is part of a great industry.

E.M.I. INSTITUTES (Dept. 127A) 10, PEMBRIDGE SQUARE, LONDON, W.2. Tel. : BAYswater 5131/2.



OSMOR STATION SEPARATOR

Plugs

receiver

into

COMPLETE

The Separator may easily be tuned to eliminate

any one station within the ranges stated and

OSMOR

Aerial

plugs in here



CROYDON, SURREY. Telephone Croydon 5148/9

CHASSIS CUTTER

These really powerful units in compact form give quality and performance right out of proportion to their midget size and modest cost. Osmor "Q" Collpacks have everything that only the highest degree of technical skill can ensure—extra selectivity, super sensitivity, adaptability. Size only 12 x 34 x 34 with variable iron-dust cores and Polystyrene formers. Built-in trimmers. Tropicalised. Prealigned. Receiver-tested and guaranteed. Only 5 connections to make. All types for Mains and Battery superhets, and T.R.F. receivers. Ideal for the reliable construction of new sets, also for conversion of the 21 Receiver, TR.1196, Type 18, Wartime Utility and others. Send to-day for particulars!

T.

2

3

4

5

6

7

SEPARATE COILS 4/-

A full range is available for all popular wavebands and purposes. Fully descriptive leaflets and connection data available. (Optional) new sîmple fixing 2d. extra. Just note these "5 Star" Features. * Only Iin. high. * Packed in damp-proof containers. * Vari-Packed in damp-proof containers.

able iron-dust cores. connection. * Low connection. loss Polystyrene for-T.R.F. REACTION COIL TY TYPE QR A range of coils for F. M. Receivers shortly available. A special design of coils now available for reflex circuits.



Send 5d. (stamps) for fully descriptive literature including "The really efficient 5-valve Superhet Circuit and Practical Drawings," 6-valve ditto, 3-valve (plus rectifier) T.R.F. circuit, Battery portable superhet circuit, Coil and Coilpack eaflets, Chassis Cutter leaflet, and full radio and component lists, and nteresting miniature circuits, etc.

DIALS-VARIOUS DIALS CALIBRATED TO COILS DIALS TRANSIS DIALS CALIBRATED TO COLLS Metal dials, overall size 53in. square. Cream background, 3-colour Type MI, L.M.S. waves. M2, L. & M. waves. M3, M. and 2 S. waves. Price 3/6 each. Pointer 1/6; Drum, Drive, Spring and Cord, 3/2. Cream background, 3-colour

Type A glass dial assembly, measuring 7in. x 7in. (9⁺/₂ x 9⁺/₂ overall). Mounts in any position. Choice of two 3-colour scales, 24/6. P. & P. 1/6.

OUR TECHNICAL DEPT. WILL BE PLEASED TO ANSWER (BY LETTER ONLY) ANY ENQUIRY RELATING TO CIRCUITS IN WHICH OSMOR COILS OR COIL PACKS ARE USED OR ARE INTENDED TO BE USED.

AAAAAA

VE ENDEAVOUR TO KEEP ABREAST OF THE TIMES BY BUILDING THE VARIOUS CIRCUITS PUBLISHED IN WIRELESS WORLD," "PRACTICAL WIRELESS," "RADIO CONSTRUCTOR " ETC. WE KEEP STOCKS OF THE COMPONENTS SPECIFIED. WE

"PRACTICAL WIRELESS "

Coronet Four; Beginners' Superhet; Modern High Power Amplifier 2; Attache Case Portable; R1155 Converter; A.C. Band-Pass 3; Modern I-Valver; 3-speed Autogram, modern reflex, etc.

"WIRELESS WORLD"

"No Compromise" TRF Tuner. "Midget Mains Receiver." Sensitive 2-valve Receiver. Television Converter (special coils in cans available), Midget

sensitive T.R.F., etc.

"RADIO CONSTRUCTOR "


Converting the TRI196 receiver to a general purpose s'het receiver simple crystal diode set. Radio feeder units. Economy 8 W.P.P. Amplifier. Circuit and details available for adding push-pull to the 5/6 valve Osmor superhet.

A LIST OF FIXED CAPACITIES AS REQUIRED FOR SWITCH TUNING AVAILABLE ON APPLICATION

COIL UNITS MAKE EASY SWITCHI

Wavebands may be added or changed in a few minutes. Switching arrangements can be increased as required. Multi waveband Coilpacks may be care as a second sec and Oscillator Coils and Trimmers wired and ready

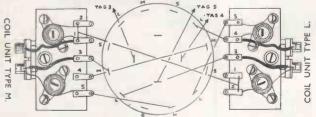THE SIMPLEST AND MOST COMPLETE METHOD OF SET BUILDING SO FAR DEVISED FOR THE AMATEUR.




PER including 4 UNIT foolproof drawings.

NEWCOMERS TO RADIO: WE HAVE A NEW DEPARTMENT READY AND WILLING TO HELP

DESIGNERS ARE ASSURED OF FULL CO-OPERATION Please let us know your requirements — send us your problems.

55

Itd.

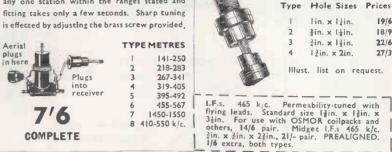

FEBRUARY, 1955



FOR MARINE EQUIPMENT

seagoing Every vessel in this electronic age relies on Marine Communication Equipment.

Our contribution is a specialised range of reliable Headphones which provide ships' operators with the clearest possible reception of all signals-Morse or speech.



with the sensational new UNBREAKABLE CASE

NEW MODEL can now be used ALMOST CONTIN-UOUSLY without overheating. Weighs only 24 oz. Loop for hanging now provided.

The ideal tool for any RADIO - TV - TELEPHONE mechanic or amateur.

Available in 110, 200/220, 220/250 v. for A.C. only. 50/60 Cycles (60 w.).

BALANCED GRIP SOLDERING GUN

Specially designed for soldering on hard-to-reach jobs.

- * INSTANT HEATING -Ready for soldering in 6 seconds.
- * EXCLUSIVE ALLOY TIP-lasts indefinitely under normal use and care. + One year's guarantee.

Sole Distributors :- S. KEMPNER LTD. 29 Paddington St. (off Baker St.), London, W.1.

G. Brown provide Headphones and associated equipment for all known purposes.

56

Brochure "W" sent on request.

irown.L SHAKESPEARE STREET, WATFORD, HERTS.

Telephone: Watford 7241.

22

32 - 1 W.B. HF.810

G E.C. METAL CONE SPEAKER



.....

HF.1012

AMPLIFIERS

OSRAM 912

This renowned amplifier complete—with drilled chassis—front panel. Brand new B.V.A. Valves. All transformers approved by G.E.C. Everything included. Partridge Kit £22/6/3. Wired and Tested £4 extra. Haddon Kit £21/19/3. Tele-Radio Kit £18/18/6.

WILLIAMSON

This amplifier justly celebrated all over the world. Absolutely complete with all parts. Partridge Kit £22/1/-. Wired and Tested £26/15/6.

P.A.1 PRE-AMP FOR WILLIAMSON AMPLIFIER

The P.A.1 pre-amp, especially designed by us—for use with the Williamson, Up to a standard—Down to a special price. Kit $\pounds 6/16/6$. Wired and Tested $\pounds 8/18/6$.

MULLARD 5-10

This clever new amplifier is offered complete to last nut and bolt. Brand new B.V.A. Valves. First quality components throughout. Kit Price £12/10/-.

LEAK

TL.10 £17/17/-. Point 1 Pre Amp. £10/10/-. Vari-Slope Mk. II £16/16/-. TL 12 £28/7/-. TL.25 £34/7/-.

QUAD

Quad II £22/10/-, Quad II Control Unit £19/10/-.


PICK-UPS

ACOS GP.20 Arm ACOS HGP39 Head Std. & L.P	£1 £2 £3 £3 £4 £5 £2	2 17 14 15	0 8 9 5	
DÉCCA XMS Heads Std. or L.P	£2 £6 £9	9	8 5 6 0	
CONNOISSEUR P.U. Heads. Diamond Stylus. Std. or L.P	£7 £11 £7 £1	9 15	11 6 3 0	

GRAM MOTORS

Õ	COLLARO 3/554 3 Speed Motor and Pick up	£8	18	4	
6	COLLARO 2000 3 Speed Transcription Motor	£13	9	6	
0	COLLARO 2010 3 Speed Transcription Motor and "P"				
õ	Pick up	£18	4	9	
0	GARRARD 301 3 Speed Transcription Motor	£25	3	6	
-	GARRARD RC.80M 3 Speed Autochanger with 45				
6	P P M Post	£18	12	9	
6	CONNOISSEUR 3 Speed Transcription Motor	£25	15	5 -	
	Contrological Software Madel				

(Latest Model)

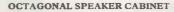

Designed for the G.E.C. Metal Cone Speaker. Price £12 10 0

R.J. SPEAKER CABINET

The sensational new miniature speaker cabinet by Wharfedale. Price £9 10

TUNER UNITS

 CHAPMAN
 S4.
 Four Stage Feeder Unit
 £16
 0
 0
 0
 0
 <

Postage & Packing extra.

ELE-RADIO (1943) L' 189 EDGWARE ROAD, LONDON, W.2.

£3 5

£3 17 6

Phone: PAD 4455/6

Shop hours: Monday-Saturday, 9 a.m. to 6 p.m. Thursday 9 a.m. to 1 p.m.

58

WIRELESS WORLD

FEBRUARY, 1955



When you listen to a Simon Portable you're hearing sound Recording at its lively best. Ask your dealer for a demonstration. Try its simple controls. Hear its faultless reproduction of speech and musicremember that for P.A. or record reproduction you can use the high quality amplifier independently of the recorder.

SIZE :
LOUDSPEAKER :
POWER SUPPLY :
INPUT CHANNELS : High imbedance for microphone: low or high impedance for radio.
POWER CONSUMPTION :
RESPONSE :



RECORDER MODEL SP/1 PORTABLE TAPE 79 Gns.

recording

Ask for illustrated literature. and Information Sheet TI/A

SIMON SOUND SERVICE LTD. (Dept. W.), 48-50 GEORGE ST., LONDON, W.I. Phone : WELbeck 2371 (5 lines) * Monomaster Finger-tip control

- * 2-stage capstan
- * Three motor drive
- * Fast rewind and wind-on



All Brookes Crystals are made to exacting standards and close tolerances. They are available with a variety of bases and in a wide range of frequencies. There is a Brookes Crystal to suit your purpose-let us have your enquiry now.



Brookes Crystals Ltd subpliers to Ministry of Supply, Home Office, B.B.C., etc. 181/3 TRAFALGAR ROAD, LONDON, S.E.10 Phone: GREenwich 1828 Grams: Xtals Green, London

Announcing the new Manning-Carr P.53C Miniature Polarised Relay.

Now in dust-proof heavy gauge anodised aluminium can and miniature S-pin base for plugging in, thus protecting the relay and obviating wiring.

(original version still available).

DATA—A Sensitivity of 25 milli-watts and capable of handling mains voltage on the contacts with alternating currents up to 0.25 amps. Being polarised it has the advan-tage that the Armature contact can be biased

POST OFFICE TYPES 3,000 AND 600 RELAYS

to specification. Tropicalising, impregnating and Services jungle finish if required. Delivery 3-4 weeks.



- * 10 watts push-pull output
- * Simple loading



miniature SOLDERING INSTRUMENTS

the smallest precision soldering instrument you've ever seen

No ceramics or mica are used in ORYX soldering instuments. Nothing to go wrong. Entirely designed and made in England for production line reliability and pin-point precision soldering

Sole Distributors :

ANTEX

The end of a production managers nightmare...

Model	Consumption	Voltage	Bit Diameter	Weight	Length	P	rice	Spare Bits
12	12 watts	6, 12, 24 or 50	3/16" (4.8 mm)	0.5 oz	6.1."	£١	5 0	2/-
-11+	10 watts	6 only	5/32" (4 mm)	0.5 oz.	6″	£1	15 0	7/6
9	8.3 watts	6, 12 & 24	5/32" (4 mm)	0.25 oz.	6"	£١	5 0	1/8
6A	6 watts	6 only	3/32" (2.4 mm)	0.25 oz.	6″	٤I	5 0	1/8
6	6 watts	6 only	1/16" (1.6 mm)†	0.25 oz.	6″	٤I	5 0	

* Special High Temperature Model † Fixed Bit

3 TOWER HILL · LONDON · EC3 Phone: ROYal 4439 Grams: (Overseas) "Antexlim, London" SUPPLIERS TO H.M. AND FOREIGN GOVERNMENTS, LEADING ELECTRONIC, HEARING AID, INSTRUMENT, RADAR, RADIO, T/Y AND ELECTRO MEDICAL MANUFACTURERS, HOSPITALS AND UNIVERSITIES THROUGH-OUT THE WORLD.

Cellular Polythene 75 ohm. T.V. DOWNLEAD CABLE Nominal Attenuation at 50 M'cs:-2.5dB'100ft. P.V.C Sheath.... Plain Copper Wire Braid . . . Cellular Polythene Insulated to 0/129" Diameter. . 1/.029" Annealed Copper Conductor . . . A Glover Product W. T. GLOVER & CO. LTD. Specialists in **Plastic Extrusion** TRAFFORD PARK MANCHESTER 17

COMPOSSENT VARIABLE 3 SPEED GRAMOPHONE MOTOR

We present an entirely new three-speed unit operating at 33¹/₈, 45 and 78 r.p.m. The full 12in. turntable is lathe turned and manufactured of non-ferrous material. The main spindle is precision ground and lapped to mirror finish and runs in phosphor bronze bearings. The synchronous motor is dynamically balanced and resiliently mounted, making it virtually vibrationless, with low noise level and low hum induction.

The speed change is arranged mechanically and gives a 2% variation on all speeds, the synchronous motor running at constant speed at all settings. No braking action is employed 5% 2% to obtain speed change.

It is suitable for playing standard transcription and microgroove recordings. Input voltages 220/250 v. A.C. 50 cycles, or, as specified to order for 200/250 v. A.C. 60 cycles, or 110 v. A.C. 50 or 60 cycles. Mounted on $\frac{1}{2}$ in. die-cast board 15 $\frac{1}{2}$ ×13 $\frac{1}{2}$ in. with 3 $\frac{1}{2}$ in. clearance distance below motorboard. Speed selector turret is fitted at left rear of motorboard. On-off switch at left front also releases pressure on the rubber drive assembly. All motor boards are drilled to take Connoisseur Standard and Super Lightweight Pickups unless otherwise ordered. When used with these pickups mounted in position, $3\frac{1}{2}$ in. clearance above motorboard is recommended.

Price £19.0.0 Plus Purchase Tax £6.15.5. Total £25.15.5

CONNOISSEUR

Super Lightweight 3-head Pickup with Sapphire Stylus

Prices: Complete Pickup with one head (either Standard 78 r.p.m. or Microgroove 331 or 45 r.p.m.), £4/10/- plus P.T. £1/12/1: Total £6/2/1. Each additional head £2/10/- plus P.T. 17/10: Total £3/7/10. Replacement Armature 10/3 plus P.T. 3/8: Total 13/11.

Fitted with Diamond Stylus, complete Pickup with one head $\pounds 7/12/9$ plus P.T. $\pounds 2/14/5$: Total $\pounds 10/7/2$. Each additional head $\pounds 5/12/9$ plus P.T. $\pounds 2/0/2$: Total $\pounds 7/12/11$. Replacement Armature $\pounds 3/13/-$ plus P.T. $\pounds 1/6/-:$ Total $\pounds 4/19/-.$

A. R. SUGDEN & CO. (ENGINEERS) LTD.

WELL GREEN LANE, BRIGHOUSE, YORKSHIRE Telephone : Halifax 69169, Telegrams : "Connoiseur Brighouse"

OVERSEAS AGENTS: S. Africa: W. L. Procter (Pty), Ltd., 63 Strand Street, Cape Town. Australia: J. H. Magrath & Co. Pty, Ltd., 208 Little Lonsdale Street, Melbourne. Canada: The Astral Electric Co. Ltd., 44 Danforth Road, Toronto 13, Ontario. New Zealand: Turnbull & Jones Ltd., Head Office, 12/14 Courtenay Place.Wellington. Hong Kong: The Radio People Ltd., 31 Nathan Road, Hong Kong. Malaya: (Main Distributors) Eastland Trading Co., 1 Prince Street, Singapore. U.S.A. (Main Distributors): Danby Radio Corporation, 2042 Chestnut Street, Philadelphia, 3, Pa. Audio Supply Laboratories, Nickels Arcade Buildings, Ann Arbor., Michigan.



WIRELESS WORLD





FEBRUARY, 1955



Incorporating all the latest developments in tape production

PRE-STRETCHED PVC BROWN OXIDE HIGH OUTPUT LOW BACKGROUND NOISE EASE OF ERASURE HIGH TENSILE STRENGTH NON-CURLING The QUALITY tape at a competitive price... 32/6 per 1200 ft spool On the well-known universal Ferrovoice Spool

600 ft 19/6 300 ft 12/6

The popular FERROVOICE PAPER TAPE is still available

MAGNETIC COATINGS LIMITED 38 GROSVENOR GARDENS LONDON SWI Telephone : SLOANE 9129 WORKS & LABORATORY: 25 DASHWOOD TRADING ESTATE LARCH ROAD - LONDON - SWI2 BALHAM 5579



Completely New & Unique Battery/Spring driven

MINIATURE RECORDER A.C.E. "CONSORT"

47


SIZE : $6\frac{1}{2}^{*} \times 7^{*} \times 12^{*}$. NO LARGER THAN A TELEPHONE I Provides foolproof "ouality" recording anywhere WITHOUT MAINS POWER.



MANY "ALL MAINS" FEATURES INCLUDE : * 2 TRACKS * POWER REWIND * AUTOMATIC ERASE * MONITORING CIRCUIT * 3 SPEEDS * 5in. SPEAKER (Full Trade and Export Terms.)



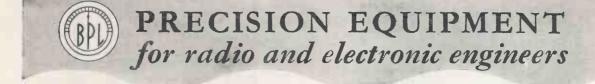CALL FOR DEMONSTRATION OR SEND FOR ILLUSTRATED BROCHURE ASSOCIATED CINE EQUIPMENTS LTD. 353, BEXLEY ROAD, ERITH, KENT. Phone : ERITH 2543





D.C. Milliameter measuring only 5in across, yet retaining a scale length of 9in.



All-purpose test set enabling the simultaneous measurement of current and voltage.


Three-range Probe Millivoltmeter with self-contained stabilised power pack. Automatic overload protection.




Audio-frequency Signal Generator operating from A.C. Mains. Frequency range: 50 cycles to 55,000 cycles.



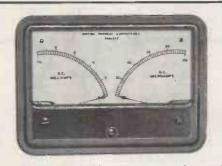Universal Valve Voltmeter with all-range indicator measuring from D.C. to U.H.F.



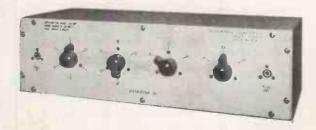High sensitivity double-purpose meter for panel mounting. Movements are independent of each other.



Wide frequency range attenuator with incremental accuracy within 1% up to 70 Mc/s. Backed by N.P.L. certificate.

dmBP31

BRITISH PHYSICAL Radlett, HERTS LABORATORIES





MINNESOTA MINING & MANUFACTURING CO. LTD Arden Rd, Adderley Park, Birmingham 8 167 Strand, London WC2 90 Mitchell St, Glasgow Cl 16 Mosley St, Manchester 2

We are glad to announce

the immediate availability of "Scotch Boy" Magnetic Recording Tape on a new clear plastic 7" reel-more solid, perfectly balanced, with a large centre hub and simplified V slot threading.

Each new reel has its own sturdy handsome hinged box, in our familiar black and plaid, with ample writing space on the underside.

As for the tape, it will "speak for itself." On all types of recorders it will give true, brilliant quality. It is an all-British product of which we are proud.

Daily, professional and home recordists alike are changing to "Scotch Boy."

ELEMENTS OF RADIO SERVICING (2nd Edition) William Marcus and Alex Levy This book gives practical step-by-step procedures for diagnosing troubles in radio receivers and in making the repairs. It presents the information so that the student with a background of simple radio theory can understand it and emphasizes procedures which may be applied to any receiver. All the latest types of receivers are covered including battery and threeway portables. The new edition is greatly enlarged, contains new 8 0000 illustrations, and will be invaluable to service repair men. Approx. 520 pages. 9 x 6 inches. Approx. 40s. Available shortly from your bookseller

McGraw-Hill London

HUNTON will cut your press tool costs for PROTOTYPE and PRE-PRODUCTION RUNS!

THE UNIVERSAL BOLSTER OUTFIT USING STANDARDISED PUNCHES AND DIES FOR SHEET METAL PIERCING AND BLANKING ON FLY PRESSES



THESE ADVANTAGES!

- Specialised range of Chassis Piercing and Forming Tools for the Radio and Electronics Industries.
- To get you started-standardized Punches and Dies in. to 3in. dis. in 1/32in. sizes from stock. At short notice, standardised Tools for square, oblong, and other shapes.
- Adjustable Gauges for exact location of work. Automatic and Positive Stripping of material from Punch. .

If in London and Home Counties, ask for a practical demonstration in your own works. Alternatively, write for illustrated price list to :

HUNTON LIMITED, PHENIX WORKS, 114-116, EUSTON ROAD, LONDON, N.W.I. Tel. : EUSton 1477 (3 lines). Grams: Untonexh, London.

WIRELESS WORLD

KH, I, AYN

AMERICAN RELAYS FOR **OFFSHORE** | ENQUIRIES CONTRACTS

We are already tooled to manufacture many types of these relays, and through our association with the Guardian Electric Manufacturing Company of Chicago, we have access to full information on other types

ARE INVITED

PHONE: NEWMARKET 3181-2-3

TELEGRAMS: MAGNETIC NEWMARKET

M.D.7A

MAGNETIC DEVICES LTD EXNING ROAD, NEWMARKET

ACCLAIMED.

BRITAIN'S FINEST AUDIO REPRODUCER

* Built as a musical instrument, sounds like a musical instrument.

* Entirely new development in electrical-mechanicalacoustical system.

* The most efficient reproducer of audio frequencies in the world with a single drive unit/compound horn housing. * Now used by Television, Broadcasting and Recording Studios throughout the World, as standard monitor.



£9/10/- (plus £3/3/3 P. Tax) Fitted with diamond stylus. Std. or L.P.

 Std. or L.P.
 £9/10/- (plus £3/3/3 P. Tax)

 331/3 and 45 r.p.m. or 78 r.p.m.
 £5/10/- (plus £1/16/7 P. Tax)

 Fitted with sapphire stylus. THE LOWTHER MANUFACTURING COMPANY, LOWTHER HOUSE, ST. MAR: S RD., BROMLEY, KENT, ENGLAND

Type T.P.I £96 as illustrated. or light oak. Ex works.

Valuable Wireless World books

Radio Interference Suppression

As applied to Radio and Television Reception. By G. L. Stephens, A.M.I.E.E. Explains the origins of electrical interference and principles of suppression, then gives practical details of suppression methods for many kinds of industrial, domestic and marine equipment.

8[‡]in. + 5[‡]in. 132 pp. Illustrated. 10s. 6d. net. By post 10s. 11d.

Television in Your Home

Everything the potential viewer needs to know. By W. E. Miller, M.A. (CANTAB.), M.Brit. I.R.E. Provides all the information needed by viewers before and after the purchase of a receiver. Entirely non-technical, the book assumes no previous knowledge whatever of television. Gives invaluable information on buying, installing and using a television set. $7\frac{1}{4}$ in. $4\frac{3}{4}$ in. 64 pp. Illustrated. 2s. net. By post 2s. 2d.

Wireless World Television Receiver Model II

Collected articles describing a complete receiver, using a superheterodyne circuit, which provides a modern standard of performance and is suitable for home construction. Complete constructional details, with all circuits and many photographs.

 $10\frac{1}{10}$ in. $+7\frac{1}{10}$ in. 40 pp. 3s. 6d. net. By post 3s. 9d.

Wireless World Diary 1955


Compiled by the technical staff of "Wireless World," the reference section includes much valuable information of handy formulae, abacs, charts and valve base tables giving connections for over 500 valves. Ample room for notes, one-week-to-an-opening diary.

Rexine (inc. P.T.), 4s. 1d. By post 4s. 3d.

Leather (inc. P.T.), 5s. 10d. By post 6s.

Obtainable from booksellers or direct from :

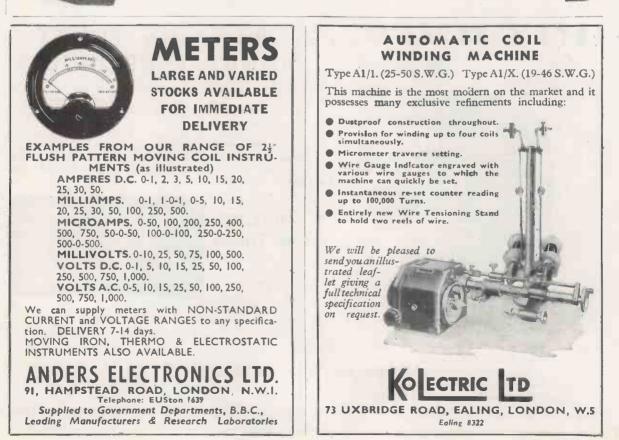lliffe & Sons Limited, Dorset House, Stamford St., London, S.E.I





and Interferences

WIRELESS WORLD

new VALVE VOLTMETERS



E.7555/2

WIDE RANGE

 $0.5\mathrm{V}$ to $15\mathrm{kV}$ F.S.D., peak a.c. or d.c. (an alternative model, **E.7555/3**, with a range of 0.5V to 500V is also available).

by Mullard

BROAD BANDWIDTH

Low level response within 2% from 30 c/s to 100 Mc/s using probe.

EXTREME STABILITY

The high degree of feedback employed minimizes the effects of ageing and supply fluctuations.

"FLOATING" REFERENCE POTENTIAL

Voltages may be measured both positive and negative to earth or other reference potentials.

DIFFERENTIAL MEASUREMENT

Provision is made for differential measurement of direct voltages and, at the same time, for the input resistance to be balanced to earth.

E.7556

SENSITIVE

F.S.D. readings range from 10mV to 300V a.c.

FLAT FREOUENCY RESPONSE

Only 2% (0.2dB) variation between 20 c/s and 1 Mc/s.

ACCURATE

Absolute error is less than 4% over whole range.

NEGATIVE FEEDBACK

As in the E.7555 series the calibration accuracy is precisely maintained.

BUILT-IN CHECK VOLTAGE

A stable 10mV supply provides a quick and easy check of calibration.





Write today for full information on value voltmeters and other instruments in the Mullard range

-

MULLARD LIMITED · EQUIPMENT DIVISION · CENTURY HOUSE · SHAFTESBURY AVENUE · LONDON

WC2 (MI455)



This

ALUMINIZED

Picture tube gives

A^N Ediswan Mazda aluminized picture tube gives a picture 60% brighter and more contrasty than is possible with an ordinary tube.


In addition, Ediswan aluminizing protects the screen from ion burn and, with the new Ediswan ion trap tetrode gun to protect the cathode, tube life is increased.


Ediswan production methods, which include the special in-line vacuumizing system, ensure a higher, more uniform standard of lasting efficiency. For complete satisfaction demonstrate and recommend Ediswan Mazda aluminized picture tubes.



ALUMINIZED CATHODE RAY TUBES

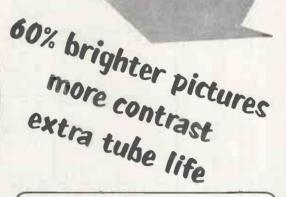
THE EDISON SWAN ELECTRIC COMPANY LIMITED, 155 Charing Cross Road, London, W.C.2 and Branches. Member of the A.E.I. Group of Companies.



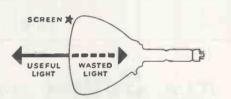

WITHOUT ALUMINIZING

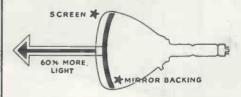Without aluminizing, tubes waste half their light (see diagram above). To counteract this the brilliance must be increased and the tube life is shortened.



WITH EDISWAN ALUMINIZING

Ediswan aluminized tubes have a mirror backing to the screen. All the light is thus thrown forwards giving brighter, clearer pictures and extra life.

NATION WIDE SERVICE

RV9

6 fully equipped cathode ray tube service depots provide better, quicker tube testing should the need arise. Stocks of tubes are available in 26 Ediswan Offices. Only Ediswan give such complete backing to the Trade.

Great Britain's Valve Mail-Order House (2,000) (101) TYP VALVES TROM DEMOBBED RADIO 3 a. VALVES **One Year's Guarantee** SALE L 246 HIGH ST. HARLESDEN 2' IR5 16/5 ECC40 22/1 Giving equivalents of British and American Ser-vice and Cross Reference of Commercial Types with an Appendix of B.V.A. Equiv-alents and Comprehensive Price List. We have still some Valves left at very old 184 14/6 ECC81 22/1 OZ4 954 21-ECC82 ECC83 195 16/5 22/1 OIA 31-41-IT4 22/1 0 14/6 14/6 14/6 18/11 14/6 14/6 14/6 14/6 18/11 116 3/-057 10/-Chassis 31/6 22/8 20/2 20/2 20/2 20/2 23/4 394 ECC91 11726 ECH3 ECH3 ECH35 ECH42 ECH81 BCL80 EF9 EF37A EF39 EF40 EF41 EF42 EF50 ILN5 3V4 IA7GT 71-71-Cutters BRITISH 2A6 1299A 71-10/ with Keys IC5GT IH5GT IN5GT 3A4 3A5 5Y3GT 6A4 6AL5 6AQ5 6AT6 6AU6 6BA6 247 3/-1625 9/6 AMERICAN Post MAX 4/-2**B7** DD207 BATTERY, 1/6 647 11/-EF6 Budget Rates (331%) which are actually sold at the old The easiest and quickest way of cutting holes in sheet metal. The cutter consists of three parts: A die, a punch and an Alten screw. The operation is quite simple. Prices lucl. key: jin. 124/2; kin. 124/3; lin. 134/3; lin. 14in. and 14in., 16/- each; 13in., 19/9; 23pin., 31/9; 21in., 19/9; 13pin., 31/9; 21in., 26/9; lin. square, 24/3-Post 1/-. A.C. 5/-6407 HT.1320 16/5 6E5 MSP41 and 11/price. (1951 rate.) 14/-15/1 11/4 16/5 15/1 22/1 6SF5 **P**2 31-UNIVERSAL 16/5 P215 124 21. PIFCO 21-WONDER" TYPES. 0.000 128F5 RI-33 21-All-in-one Radio-meter 22/ ARP3 13PA 71-5/-EF80 EF91 16/5 20/2 31/6 all f 000 32 34 31-ARP4 5/6 anne HAND TOOL A.C./D.C. Tests every 6BE6 EF93 EK32 16/5 22/8 3/-ARP12 3/-6**J**6 636 31/ 68A7GT 20 68K7GT16 48 41-**CV1124** 5/thingin Radio, Com-6 TOOLS IN EK90 EL3N 20/2 VR18 50¥6 81-5/-11176 ONE 68Q7GT EL.33 16/5 22/1 25/2 714 21-**VR65** 2/plete with Test prods. 29/6. 16/ EL37 884 Post 9d 21/-ROD Antennas. lift. sections interlocking and ex-tending, copper plated steel. BABGAIN. Dozen 2/6 Reduced from 20/-Punches, bends and shears Metal Strip, Rod and Angle. Every 20/-6X4 R1.38 6X4 1 6X5GT 1 12AT7 2 12AU7 2 12AX7 2 128A7GT 13/3 22/1 22/1 22/1 E1.41 16/5 16/5 VALVE THE MONTH METERS R1.42 Post 1/6 16/5 16/5 16/5 American 4 pin U.X. type No. 31. Triode Class A. Amplifier. 2.0 v. .13 amps E1.84 TYANA TRIPLE THREE Small Soldering Iron Latest EL84 EL90 EM1 EM4 EM34 EV51 EZ35 on Handyman needs onei 1.000 usest Uniquel EASY B.T.H. GERMANIUM CRYSTAL DIODE. Complete with Blueprint and operating instructions, 2/-20/2 128K7GT TERMS development. 16/5 16/5 25/2 Complete SALE 128Q7GT ask for with detachable (Full characteristics bench 2'stand, 19/6. Post 1/-. Catalogue 13/3 13/3 13/3 on request.) only 7/6 REDUCED FROM 21/-15. 25L6GT 16 3525GT 13 50L6GT 16 EZ40 EZ41 EZ80 EZ90 GZ34 PL81 FL82 PL83 PY80 PY81 7/6 ELPICO AC36 AMPLIFIER VOLUME CONTROLS 9" TUBE CRT 516 Mag-Pre-heated Electric Soldering Irons. 24 v. 36 Watts. Press button switch fitted. Corroslon-free Bit. Specially designed for fine work. Limited quantity. 3 valves incorporating power ohm. 13/3 5000 Meg netic 4 v. heater, 4 to 5 kV. E.H.T. Int. Octal Base. supply for radio tuner international octal so 10000 AZ1 AZ31 13/3 13/3 13/3 22/1 20/2 30/3 99 ... socket 22/1 16/5 22/1 15/9 18/11 13/3 17/8 15/1 20000 ... Special matching for standard BARGAIN, Carr. & Crate, 4/6, 57'6 25000 AZ50 CBL1 or L.P. records not required. 50000 A.C. only CL4 CY1 100000 £7.19.6 PY82 UAF42 Less switch 4/4. S.P. sw. 6/4. D.P. sw. 7/10. Post 6d. BA50 11/4 INSPECTION LAMP BABCS UBC41 UBL21 BAF42 With stout gal-vanised wire guard. Superior quality. (Less flex and bulb). B B RBC90 UCH21 UCH42 BIB Recording Tape Splicer is a pre-cision-made device combin-ing features of 5 U.S. makes **HEADPHONES** Tape RB41 UF41 UF42 UL41 UL44 UY41 Pos RB91 Lightweight High Resistance RBC33 4000 ohms complete with 16/5 25/2 13/3 9d EBC41 SERVICE SHEETS at fraction of cost. 18/6 The one you require en if available in a dozen as of our best choice, 10/8. 18/11 22/1 PAPE(cord. 16/9 6'6 Post 1/assorted Post 1/-KBL21

WIRELESS WORLD



70

unitelex M.G.4. AMPLIFIER

A low-cost general-purpose amplifier of outstanding performance and distinguished appearance. Output is 5 watts, with matching for 15 ohm and 3 ohm speakers. Input is switched for pickup (90 mV) or microphone (30 mV). In gramophone condition, distortion is 0.8% for 3 watts output at 1 kc, and frequency range is 40/30,000 cycles ± 3 dbs, 20 db of negative feedback being employed. B.V.A. valves used throughout.

Price, in chassis form (Type No. MG4), 8½ guineas; with cover and baseplate (Type No. MG4A), 9½ guineas.

Available from leading stockists, Including the following in the London area: Messrs. Arthurs (Arthur Gray Ltd.); Berry's (Shortwave) Ltd.; City Sale and Exchange Ltd.; Clyne Radio Ltd.; Garland Bros. Ltd.; Mail Order Supply Co.; Nusound Products; Tele-Radio (1943) Ltd.; Webb's Radio.

unitelex (london) ltd. Pagnell St., London S.E.14. TIDeway 5842

TV TRANSFORMER TROUBLES?

"REWIND & REPLACEMENT HANDBOOK"

is now available. An entirely new handbook which every television engineer and dealer should have. It contains exclusive editorial matter on Line Output transformers and many manufacturers' modifications. The most complete catalogue of Manufacturers' Spares in Great Britain.

1/3 (plus 3d, postage)

UNISCAN I Left

The first of a series of universal line output transformers. A complete set of these transformers will cover 80% of British T.V. sets manufactured to date.

NURAY

39/- (plus 2/- post and backing)

Trade Terms upon request.

NURAY Mk. II

The Heater-Booster/Isolator unit that just plugs in. Gives low emission C.R.T. a new ray. Available for 2 volt C.R.T.

27/6 (plus 1/6 post and packing)

With Direct T.V. Replacements you need never be st a loss for a T.V. Transformer. We despatch your order by return. When out of stock we rewind faulty components.





FIRST IN THE QUEUE (if any)

Nowhere can you get the selection of radio and gramophone equipment, nowhere can you get the service that we at Classic can give you. We always carry large stocks of the newest, most up-to-date equipment as soon as it becomes available. Some of the very new equipment is in short supply, but no matter how new or how scarce (or how expensive) it may be, we order it immediately. We don't wait until customers ask us for it. Which means one of two things. Either we have it in stock at once, or, if there is a waiting list, we-and our customers-are at the top of it. And you don't need to call-post enquirers receive the same careful attention as personal shoppers, and very favourable Hire Purchase terms are available to all.

The Classic Service is particularly valuable if you are an overseas customer. You can choose your equipment from our new Special Export Catalogue, which will be sent on receipt of 1/- for postage (airmail extra), and you can be sure that your equipment will arrive at the right time and in the right condition. Here are a few of the newest pieces of equipment available now from Classic

MOTORS
Garrard R.C.90 Auto- changer£22 8 11
Garrard Transcription Model 301/B£25 4 6
Variable Speed Motor £25 15 5
F.M. UNITS
Lowther F.M. Unit £29 6 4
Chapman F.M.81 £21 0 0
Goodsell F.M.T.401 £24 19 6
AMPLIFIERS
Lowther £60 0 0
Williamson (Goodsell) £53 15 0
Leak £40 10 0
Quad£42 0 0
SPEAKERS
Lowther T.P.1 £96 0 0
Wharfedale Speaker Sys-
tem£72 0 0
Pamphonic " Victor " £57 15 0
Acoustical Corner Ribbon £96 0 0
Vitavox Klipshorn£145 0 0
PICK-UPS
Ferranti Ribbon £36 6 8
owther Moving Coil
Diamond Stylus £12 13 3
eak Moving Coil Diamond Stylus £13 4 6
Stytus

This is an extract from our comprehensive 16 page 2 colour Catalogue which is available 6d. post free) from :

GLASSIG ELEGTRIGAL GO LTD 352-364 LOWER ADDISCOMBE ROAD · CROYDON · SURREY TEL · ADDISCOMBE 6061-2

F L

Le

MELLINERS

The McMurdo Valve Retainer secures the valve in the same manner as a screening can, but provides unrestricted ventilation for valve envelope. The retainer is clamped between the chassis and valveholder. It requires no additional fixing.

Retainers are supplied complete with Phosphorbronze Springs.

Retainers may be used with our insulated Top Cap Connector Ref. No. TCI (fits Valve Cap BS448-Type CT1).



WIRELESS WORLD

AIR-DAMPED ANTI-VIBRATION MOUNTS

of exceptional performance: FOR THE PROTECTION OF AIRBORNE EQUIPMENT

- Superior
- vibration isolation. Improved
- shock absorption.
- Low permanent set and drift.
- Operation over
- wide temperature range
- Minimum side sway.
- Wide load range with uniform performance.

Air-damped BARRYMOUNTS have been specially developed to provide assured protection for sensitive equipment against shock and vibration. An outstanding feature is their remarkably uniform performance over the full range of rated load variation.


Over 1,000,000 BARRYMOUNTS go into use every year for the protection of every type of air-borne equipment, from the lightest and most delicate instruments and electronic devices to apparatus up to 140 lbs. weight.

There are also BARRYMOUNTS available for specialised vehicleborne and ship-borne equipment applications.

Made in England under licence from the Barry Corporation of U.S.A.

Write for technical bulletins.

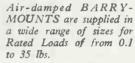CEMENTATION (MUFFELITE) LTD., 39 VICTORIA SF., LONDON, S.W.1 (ABBey 5726)



MINIATURIZED BARRYMOUNTS ARE USED IN THE BRISTOL "BRITANNIA"

BARRYMOUNTS

OSCILLOSCOPE MODEL 2300

This Model meets the need for a compact and robust instrument in which nothing has been sacrificed in order to achieve true portability. It has many of the facilities required in the laboratory as well as ruggedness demanded in the field. Note these features:

● Cathode Ray Tube diameter 2³/₄in. ● Square Wave Response adequate

Direct-coupled X and Y Ampli-

Deflection Sensitivity 50 mV.

fiers.

R.M.S./cm.

- for Television synchronising waveforms
- Hard-valve Time Base-range 7 c.p.s. to 50 Kc/s.
- Trace Expansion control from zero to 15in.
- Frequency Response D.C. to 3 Weight: $6\frac{1}{4}$ lbs. Size: $7\frac{1}{4} \times 4\frac{3}{4} \times \frac{1}{4}$ 7¦in. Mc/s.

Full details of this and other instruments on application to:

INDUSTRIAL ELECTRONICS MAGNET WORKS DERBY ROAD, EAST SHEEN, LONDON, S.W. 14. Phone: PRO 8211



microphones, loudspeakers, borns, pressure units.

> We will gladly send you our catalogue and full information on request

VITAVOX LIMITED, Westmoreland Road, London, N. W. 9. Telephone: COLindale 8671



All ge covers types 41 and 42 (front $|*| \times |1_4"$) 38, 39, and 40 (front $1_3" \times |3_4"$) and power A.C. and D.C. sizes up to 60 inch-lbs. Most sizes available ex-stock and dispatched same day as receipt of order,

6v.-460v. A.C. and D.C. types

WRITE OR PHONE FOR DETAILS PHILLIPS CONTROL (G.B.) LTD. Farnborough, HANTS. Telephone : Farnborough 1120 London Office : 59/61 Union St., London, S.E.I. Tel.: HOP 4567

INSTRUMENT CASES



Sizes up to 17" x 10" x 9". Send for list 32.

CHASSIS

Steel, cadmium plated and passivated. Sizes from 6" x 6" up to $19\frac{1}{4}$ " x 10". Send for list 42.

SUTTON COLDFIELD ELECTRICAL ENGINEERS Clifton Street, Sutton Coldfield. Phone SUT. 5666



THE

HIGH FIDELTY AMPLIFIFR Specialists in High Quality Reproduction for over 20 years CONTROL IINIT AMPLIFIER Anistrony A.10 **Price:** Price: 10 £9.15.0

CONTROLS: 1. Input: (a) Radio 50-100 millivolts. (b) Gram (low impedance) 15-100 m.v. (c) Gram (high impedance) 70-150 m.v. (d) Microphone or Tape Recorder 10-100 m.v. 2. Equaliser: (a) 78¹. (b) 78¹. (c) L.P. (d) American NARTB. 3. Filter: (a) Roll-off 5kcs. (grad). (b) 7 kcs. (c) 9 kcs. (d) 9 kcs. (steep). (e) Level response. (f) Presence lift. 4. Treble: Lift or cut of 15 db. 5. Bass: Lift or cut of 15 db. 6. Volume Control: combined with ON/OFF switch. Power Supply: For radio unit 300 v. 35 m.a. 6.3 v. 2 a. Finisk: Hammered bronze with engraved Florentine bronzed panel.

The A.10 incorporates ALL NECESSARY FILTERS and no additional filter units are required. All components are fully tropicalised.

You can hear this outstanding Amplifier at your local High Fidelity Specialists or at our Showrooms at Holloway, which are open on week-days from 9 a.m. to 6 p.m. (Saturdays until 5 p.m.). You are particularly invited to attend our special High Fidelity Demonstrations on Thursday evenings at 7 p.m. If you would like further particulars please write to us (Dept. W.F.) for descriptive booklet.

ARMSTRONG WIRELESS & TELEVISION CO. LTD., WARLTERS RD., HOLLOWAY, LONDON N.7. Tel; NORth 3213/4 Output: 10-12 watts. Distortion: Less than 0.1% total harmonic at 8 watts. Frequency Response: 10-100,000 cps., within 1 db. 15-30,000 cps. Hum Level: Better than 80 db. down. Damping: Factor: 40. Feed Back: High degree of negative feed back giving outstanding transient performance (special Partridge output transformer with TERTIARY feed back-winding). Input Required: 250 millivolts for 10 watts output. Mains Input: 100-250 v. A.C. 40-60 cycles.

"RECORD NEWS" (November 1954) says:

"Its quality of reproduction is quite excellent, its power output more than adequate for all normal loudspeaker systems, its distortion infinitesimal and its frequency response leaves nothing to be desired. . . . It can only be praised and recommended without reservation."

Interested in F.M.? See page 50.

For Reliable Power **Supplies**

WESTALITE

METAL

RECTIFIERS

Westinghouse metal rectifiers are still leading the field as the most efficient and reliable source of DC power for radio and television. The range of units available embraces all outputs from few to thousands of milliamps at any desired voltage, and those illustrated represent but a few of the many types in common use.

For further details on Metal Rectifiers, write to Dept. W.W.2. WESTINGHOUSE BRAKE & SIGNAL CO. LTD., 82 YORK WAY, KING'S CROSS, LONDON, N.I

£19.15.0





THE COMPLETE TELEVISOR IS SAFE TO HANDLE, BEING COMPLETELY ISOLATED FROM THE MAINS BY A DOUBLE WOUND MAINS TRANSFORMER. ALL PRESET CONTROLS CAN BE ADJUSTED FROM THE FRONT, MAKING SETTING UP VERY SIMPLE.



Brief Technical Datails are as follows:

20 valves (plus tube) Superhet Receiver, tunable trom 40-68 Mc/s without coil or core changing. Wide Angle scanning Flyback EHT giving 14 kV. Duomag Focaliser, permanent magnet focusing with simple picture centring adjustments, suitable for any wide angle Tube, may also be used with a 12in. Tube with very minor modifications.

VISION CIRCUIT. Common RF Amplifier, single value frequency changer, two IF stages, Video Detector and Noise Limiter followed by special type of Video Output Valve. ALL COILS PRE-TUNED ASSURING ACCURATE ALIGNMENT AND EXCELLENT BAND-WIDTH.

SOUND CIRCUIT. Coupling from anode of frequency changer, two IF stages, Double Diode Triode detector and first LF Amplifier, Diode Noise Limiter and Beam type Output Valve, feeding a 10in Speaker. ALL COLLS PRE-TUNED.

TIME BASES. 2 valve sync. Separator, giving very firm lock and excellent interlace.

LINE TIME BASE. Blocking Oscillator using a pentode driving a high efficiency output stage comprising Ferroxcube Cored Output Transformer with Booster Dlode.

FRAME TIME BASE. Blocking Oscillator driving a Beam Output Valve coupled through a Transformer to the high efficiency FERROX-CUBE Cored Scanning Coils. POWER PACK. Double wound Mains Transformer supplying all L.T. and H.T. using two full-wave Rectifiers.

The Televisor may be constructed in 5 easy stages: (1) Vision, (2) Time Base, (3) Sound, (4) Power Pack, (5) Final Assembly. Each stage is fully covered in the Instruction Book, which includes layout, circuit diagrams and point-to-point wiring instructions.

The Instruction Book also includes full details for con-verting existing Premier Magnetic Televisors for use with modern wide angle tubes. All components are individually priced.

Instruction book 3/6, Post Free.

PREMIER TELEVISOR **CONSOLE CABINETS** For 14". 16" and 17" Televisors

A handsome Walnut Cabinet that will be a fitting housing for a first-class Televisor.

Folding doors are fitted to cover the Cathode Ray Tube when not in use. A flap is provided which gives access to the preset controls on the front edge of the Chassis. A baffle board suitable for a 10in, Loudspeaker and all the necessary Tube and Chassis bearers are included. The overall dimensions of the Cabinets are the same : Height $38\frac{1}{2}$ in. Width 19in. Depth Top 19in. Depth Bottom 21in.

TUBE ESCUTCHEONS

17in. White Moulded	21/- (pkg. & post 1/6)
17in. Bronze Moulded, complete with Protective Glass,	
14in. Black Moulded	7/6 (pkg. & post 1/-)
Dark Screen Filter suitable for 14in. Tube	21/- (pig. & post 1/6)
Dark Screen Filter suitable for 16in. and 17in. Tubes	25/- (pkg. & post 1/6)
Polystyrene Mask for E.E.T.901	45/4 (pkg. & post 2/6)
Rubber Bing (anti-Corona) for E.E.T.901	6/8
Polystyrene Shroud for E.E.T.901	6/2

PRICE £13-10-0 PLUS 21/- PKG. & CAR. H.P. TERMS: DEPOSIT \$4,10.0 & 12 MONTHLY PAYMENTS OF 16/11

TERMS OF BUSINESS: Cash with order or C.O.D. over £1. Please add 1/-for Post Orders under 10/-, 1/6 under 40/-, unless otherwise stated.







Pac'ing & Carriage 1 gn.

(Including Reel of Scotch Boy Tape and Microphone)

or Complete Kit including All Parts, Valves, Speaker Cabinet, Tape Unit, Reel of Scotch Boy Tape, Rewind Spool and Microphone at £37.4.0 plus pkg. & carr. 15/-.

SPECIFICATION

TWO SPEEDS 71 in. AND SPEER SECOND.	3§in. ★ 7 VALVE HIGH QUALITY AMPLIFIER.
* THREE SPECIALLY DESI	SIGN. * INDEPENDENT TREBLE AND
ED RECORDING MOTORS	S. BASS CONTROLS.
★ 1,200ft. TAPE REELS P	PRO- * MAGIC EYE RECORD LEVEL
VIDING PLAYING TIMES	S OF INDICATOR.
1 HR. AND 2 HRS.	* AMPLIFIER MAY BE USED
* DROP IN TAPE LOAD	DING. FOR RECORD REPRODUC- TION OF HIGH QUALITY.
* EASY FORWARD OR	RE- * COMPARTMENT FOR HOUS-
WIND WITHOUT REMOV	WING MICROPHONE.
TAPE.	* SPECIALLY DESIGNED MIC-
* ONE KNOB DECK OPE	ERA- ROPHONE BY A LEADING
TION.	MANUFACTURER.

* ONE KNOB DECK OPERA-

£10.4.9 and 12 Deposit monthly payments of £2.17.7 SEPARATE UNITS CAN BE SUPPLIED AS LISTED BELOW :---Amplifier (built, wired and tested with Speaker). £14/15/-, plus postage and carriage 7/6. Hire purchase terms, Deposit £3/13/9 and 12 monthly payments of £10/9.

H.P. TERMS

Amplifier Kit (including Speaker). £11/0/- plus packing and carriage 5/-. Hire purchase terms, Deposit £2/15/- and 12 monthly payments of 15/6.

GP

New Lane 2-speed Tape Unit Mark 6 £18/10/- plus packing and carriage 7/6. Hire purchase terms, Deposit £4/12/6 and 12 monthly payments of £1/6/-.

Portable Cabinet (rexine covered). £4/19/6, plus postage and carriage 5/-. Microphone, £2/15/-, plus postage and carriage 1/-. Reel Scotch Boy Tape MC2-111 (1.200ft.), £1/15/-, plus packing

and carriage 1/-. Instruction Booklet, 2/6. Post free.

FEBRUARY, 1955

= PREMIER RADIO COMPANY = PREMIER MAINS TRANSFORMERS

METERS

Pull Scale Defiection	External Dimensions	Movement
3.5 A.	in. 21 × 21 21 × 21 21 round 21 round 22 round 22 × 21 21 × 21 22 × 22 × 21 22 × 21	$\begin{array}{cccccccccccccccccccccccccccccccccccc$
I mA	21 round	Desk type M/C 25/-

H.T. ELIMINATOR AND

AMSON	AMPLIFIER	KIT	15	gns.
		mlua	710 -	A

H.P. Terms Dep.£5.5.0 & 12m'thly p'ym'ntsof 19/9 This Kit is absolutely comprete and all components are guaranteed exactly to author's specification.

WILLIAMSON OUTPUT TRANSFORMER Author's Specification 3.6 ohms secondaries £4.4.0

MAINS TRANSFORMER SP425A

(Completely Shrouded) This Transformer has an additional 6.3 v. 3A and is capable of supplying an extra 50 mA. for Pre-amp or Feeder unit £2.12.6

WILLIAMSON CH

1.410.	100 1115	P+ 1. (111)	y surouude		* * *	* *	• •	• •	• •	• •	19/6	
30H	20m A.	Fully	shrouded	• • •	• • •	• •	•••	• •	• •	• •	11/9	

WILLIAMSON CHOKES			E CHARGER		
. 150 mA. Fully shrouded	10 01	ll parts to construct 120 volts at 29 mA tor. Uses metal re-	., and 2 volts to ch		
*******			****		•
Build	these	NEW	PRE	YII XI	ß
3-BAND SUPERH	ET	TRF	RECEI	VER	



Plus 2/6 Pk MAY BE BUILT FOR £7.19.6 BUILT FOR **Z1.13.0** & Carr. Latest type Superhet Circuit using 4 valves and metal rectifiers for opera-tion on 200/250 volts A.C. mains. Waveband coverage—short 16-50 metres, medium 180-550 metres, and long 900-2000 metres. Valve line-up 6K8 freq. changer, 6K7, IF, 607 Detector AVC and first AF, 6V6 output. The attractive cabinet to house the Receiver size 12in. long, 64in. high, 54in. deep can be supplied m either WALNUT or IVORY BAKELITE or WOOD. Instruction Book 1/- post free, which includes assembly and wiring diagrams, also a detailed stock list of priced components. & Carr.

DECCA MODEL 33A DUAL SPEED RECORD PLAYER

A 10-1



wn ename! finish 'n good quality for operation on A.C. mains 200/250 v. 50 c.p.s. Supplied complete with single head (either stan-dard or long play-ing). **£4.19.6** Extra Head can be supplied. Plus pkg. and cart. 5/-.

B.S.R. Type GU4A 3-SPEED GRAM UNIT

Fitted with Decca Heads





£5.15.0 FOR

& Carr.

The circuit is the latest type TRF using 3 valves and Metal Rectifiers for operation on 200/250 A.C. mains. Wave band coverage is 180/550 metres on medium wave and 800/2,000 metres on long wave. The dial is illuminated and the Valve line-up is 6K7 H.F. Pentode 6/7 Detector and 6V6—Output. The attractive Cabinets to house the Receiver size 12in. long, 6½in. high, 5½in. deep, can be supplied in either WALNUT or IVORY BAKELITE or WOOD INSTRUCTION BOOK I/- (post free) which includes Assembly and wiring diagrams, also a detailed Stock List of priced components.

MINIATURE TUNING CONDENSERS 2-gang .0005 mfd, with trimmers 6/9

PREMIER VARIABLE IMPEDANCE "MATCHMAKER "M.O.IS OUTPUT TRANSFORMER

Designed to meet the demand for an efficient variable ratio Output Transformer 11 ratios from 13:1 to 80 1 all centre tapped and can be used to match any output valves either aingle or push-puil Class "A" "AB1" "AB2" or "B" to any low impedance speech coll or combination thereot. Primary Inductance 50 henrics 15 watts audio 100 mA. Price 45/-.

LOUDSPEAKERS

ELAC-2}in. dia., Moving Coll, 15 ohm imp. 15/-PLESSEY-Sin. dia., Moving Coil, 3 ohms imp ... 9/11 ELAC-Sin. dia., Moving Collk 3 ohms Imp. ... PLESSEY-Sin., dia., Mains Energised, 3 ohms imp. (600 ohms field) with Pentode Transformer 19/6 22/6

PLESSEY—81n. dia., Mains Energised, 3 ohms imp. (600 ohms field) PLESSEY—10in. dia. Moving Coll, 3 ohms imp... 19/6

23/6 £8/12/6 .. £11/11 ohms. imp.

s. imp. Plus 5/- packing and carriage.

CRYSTAL MICROPHONE INSERTS

Ideal for tape recording and amplifiers. No Matching transformer required, 3/6 post free.

All primarles are tapped for 200-230-250 v. mains 40-100 oycles. All primarles are screened. SP175B, 175-0-175, 50 mA., 4 v. @ 1 a., 4 v. @ 15/-2-3 a. SP350A, 350-0-350, 100 mA., 5 v. @ 2-3 a., 6.3 v. 21/- $\begin{array}{c} @ 2 \cdot 3 \ a. \\ SP351A, 350 - 0 \cdot 350, 150 \ m. A., 4 \ v. \ @ 2 \cdot 8 \ a., 4 \ v. \ @ \\ 3 \cdot 6 \ a., 4 \ v. \ @ 1 \cdot 2 \ a., 4 \ v. \ @ 1 \cdot 2 \ a., \\ SP351A, 350 - 0 \cdot 350, 150 \ m. A., 5 \ v. \ @ 2 \cdot 3 \ a., 6 \cdot 3 \ v. \ @ \\ - 2 \cdot 3 \ a., 6 \cdot 3 \ v. \ @ 2 \cdot 3 \ a., 6 \cdot 3 \ v. \ @ \\ SP501A, 500 - 0 \cdot 500, 150 \ m. A., 5 \ v. \ @ 2 \cdot 3 \ a., 6 \cdot 3 \ v. \ @ \\ SP501A, 500 - 0 \cdot 500, 150 \ m. A., 5 \ v. \ @ 2 \cdot 3 \ a., 6 \cdot 3 \ v. \ @ \\ SP505A, 420 - 0 \cdot 425, 200 \ m. A., 6 \cdot s \ . \ @ 2 \cdot 3 \ a., 6 \cdot 3 \ v. \ @ \\ SP505A, 420 - 0 \cdot 425, 200 \ m. A., 6 \cdot s \ . \ @ 2 \cdot 3 \ a., 6 \cdot 3 \ v. \ @ \\ SP505A, 420 - 0 \cdot 425, 200 \ m. A., 6 \cdot s \ . \ @ \\ SP505A, 420 - 0 \cdot 425, 200 \ m. A., 6 \cdot s \ . \ @ \\ SP505A, 420 - 0 \cdot 425, 200 \ m. A., 6 \cdot s \ . \ @ \\ SP505A, 420 - 0 \cdot 425, 200 \ m. A., 6 \cdot s \ . \ @ \\ SP505A, 420 - 0 \cdot 425, 200 \ m. A., 6 \cdot s \ . \ @ \\ SP505A, 420 - 0 \cdot 425, 200 \ m. A., 6 \cdot s \ . \ @ \\ SP505A, 420 - 0 \cdot 425, 200 \ m. A., 6 \cdot s \ . \ B \cdot S \ . \ SP505A, 420 - 0 \cdot 425, 200 \ m. \ A \cdot S \ . \ SP505A, 420 - 0 \cdot 425, 200 \ m. \ A \cdot S \ . \ B \cdot S \ . \ SP505A, 420 - 0 \cdot 425, 200 \ m. \ A \cdot S \ . \ SP505A, 420 \ . \ B \cdot S \ . \ SP505A, 420 - 0 \cdot 425, 200 \ m. \ A \cdot S \ . \ SP505A, 420 \ . \ SP5$ 30/-30/-40/-52/6 19/6 19/6 17/6

DESIGNS

4-WATT AMPLIFIER

MAY BE Plus 2/6 Pk. BUILT FOR £4.10.0 & Carr.

Valve line-up 6SL7, 6V6 ani 6X5, FOR A.C. MAINS 200/250 VOLTS. The twin triode 68L7 is used for preamplification and also for a com-prehensive tone control direuit, which includes two very wide range and continuously variable tone controls for bass and treble. The output Valve is of the beam type and feeds 4 watts into a specially designed output Transformer which is suitable for either 3 ohm or 15 ohm Speakers. Negative feed-back is applied from the secondary of the output Transformer over the whole Amplifier to the input stage giving an excellent frequency response. Due to the high gain and wide range tone controls any type of pick-up may be used. Overall size 9×7×5in. Frice of Amplifier complete, tested and ready for use, g5/5/- pius 3/6 pigs and carr. INSTRUCTION BOOK 1/- (Post Free) which

INSTRUCTION BOOK, 1/- (Post Free) which acludes Assembly and wiring diagram, also a etailed Stock List of priced components.

ACCUMULATORS

2 volt 10 amp. (by famous maker).... 2 volt 16 amp. ····· 4/11 5/11

MOVING COIL METER A super quality Moving Coll Meter basic movement 2 mA and 4 mA Scale dimensions 24in. Overal dimensions 24in. dia. 14in. deep. Bakelite Case projecting type, At present scaled 1 anno. B.F. By removing thermo compe, reversing scale and recalibrating the meter, a high grade test instrument with any range above the basic F.S.D. may be built up. Frice 2 mA., 5/9, 4 mA., 4/9.

MICROPHONES LUSTRAPHONE: Moving Coli: High Impedance, Stand Type: 25/15/6-Hand Mike 26/6/-. RONETTE-Crystal Mike Incorp. the Filter Cell Insert: High Impd. Ball Type, 22/10/-. CRYSTAL MIGROPHONE-Rothermel 2AD56. Especi-ally recommended. £2.15.0 Table stands for all the above 10/6 and 17/6. ACOS. High Impedance Crystal Microphone, type 36-1, 25/-.

25/-. ACOS. High Impedance Crystal Microphone, type 33-1

22.10/-. 22.10/-. ACOS. "MIO 30" impedance Crystal Microphone 22/10/-. (This Microphone can be used as either Hand or Desk type.)

CRYSTAL MICROPHONE

An entreiv insulated crystal microphone which can be safely used on A.C./D.C. amplifiers. High .mpedance. No background noise, really natural tone. The ideal Mike for tape, wire and sound projectors, price 19/6.

MAINS NOISE ELIMINATOR KIT Two specially designed chokes with three smoothing condensers with circuit diagrams. Cuts out all mains noise. Can be assembled inside existing receiver, 4/11, plus 6d, pigs, and carr.

Germanium Crystal Diodes. G.E.C. wire ended, 2/6.

78

WILLIA







a but of many Mansion Addens

You will find this new and enlarged edition of the Goods GUIDE an invaluable aid in your work. With its help you can speedily find the nearest and quickest means of despatching loads of all sizes and kinds.

"Smalls" or bulk, local or long distance, you will have the information required for moving your goods at your finger tips, with this essential book. Jan.-June issue ready Now.

Jan.-June 1955 and July-Dec. 1955. Half-yearly issues : **3s. 6d. each POST FREE**

ORDER FORM

60035 TRANSFORT

soine

CKHAM

To: Iliffe & Sons, Ltd., Dorset House, Stamford St., London, S.E.1. Please send me *Jan.-June 1955 and July-Dec. 1955 issues of ABC Goods Transport Guide when published. I enclose remittance for *7s./3s. 6d. *Delete where necessary if only one issue required. Name Address.....

STREAMLINED PRODUCING means high quality at low cost

A Monarch Automatic Record Changer is produced every 15 seconds throughout each day. This outstanding production achievement, which will be bettered in the very near future, is the first fruit of an extensive re-equipment programme recently laid down by B.S.R. Here the finest precision machinery, the most modern production methods and raw materials and labour of the highest standard are integrated to produce the world's finest autochanger. Here rigid stage by stage quality and accuracy control, and rigorous final testing determine the reliability and superlative performance the listener has come to expect of the Monarch. B.S.R. are today the tworld's largest producers of autochangers and players outside the U.S.A.





A81

Wireless World

RADIO, TELEVISION, ELECTRONICS

Managing Editor: HUGH S. POCOCK, M.I.E.E Editor: H. F. SMITH.

Edited in C

In This Issue

FEBRUARY 1955

Eultorial Comment .		21
Television Society's Exhibition ,	• •	5 2
Television Standards Conversion. By H. A. Fairhurst	÷ .	53
Monte Carlo Television Station. By Charles B. Bovill		55
World of Wireless		56
Introduction to Transistor Electronics-1. By H. K. Milwa	rd	60
Historic Valve Collection		65
Ionosphere Review, 1954. By T. W. Bennington		66
Simple Wave-Shaper. By Arthur W. Wayne		69
Letters to the Editor		71
Vector Addition and the Slide Rule. By A. G. London		73
Flux-Cutting or Flux-Linking? By "Cathode Ray"		74
Measurement of Rise-Time. By E. G. Dann	• 20	79
Workshop R-C Bridge. By B. T. Gilling	· ·	80
Books Received	• •	82
"Piped " Scanning Waveforms, By E. J. Gargini		83
Lacquer Film Capacitors	• •	87
Recording Topics. By O. J. Russell	s- #	88
Gramophone and Microphone Pre-Amplifier-2.		0.1
By P. J. Baxandall		91
Short-Wave Conditions	• •	94
Simple Inductance, Capacitance and Resonance Meter. By L. F. Sinfield		95
Magnetic Induction Headphones		96
February Meetings		97
Random Radiations. By "Diallist "		98
Unbiased. By "Free Grid "		100

VOLUME 61 NO. 2 PRICE: TWO SHILLINGS

FORTY-FOURTH YEAR OF PUBLICATION

 PUBLISHED
 MONTHLY
 (4th
 Tuesday
 of
 preceding
 month)
 by
 ILIFFE
 & SONS
 LTD.,
 Dorset
 House,
 Stamford

 Street,
 London,
 S.E.1.
 Telephone:
 Waterloo
 3833
 (60
 lines).
 Telegrams:
 "Ethaworld,
 Sedist,
 London."
 Annual

 Subscription:
 Home and Overseas, £1
 7s.
 0d.
 U.S.A.
 \$4.50.
 Canada
 \$4.00.
 BRANCH
 OFFICES:
 Birmingham:
 King
 Edward

 House,
 New Street,
 2.
 Coventry:
 8-10,
 Corporation
 Street.
 Glasgow:
 26B,
 Renfield
 Street,
 C.2.
 Manchester:
 260,
 Deansgate, 3.

FEBRUARY, 1955



ALVES, TUBES & CIRCUI

26. Additional Applications of the PCF80

The Mullard PCF80 was designed primarily as an additive mixer for front end stages in Band I and Band III television receivers and converters in association with the PCC84. This application has been discussed in *Valves*, *Tubes*, and *Circuits* Nos. 15, 16, and 17 (available as reprints with additional notes). The low interelectrode capacitances and short grid base of the valve make it suitable for a number of other applications in which the EF80, ECL80, ECC82, and other valves have hitherto been used.

In television receivers the triode and pentode section of one PCF80 can, with certain limitations, be used to perform separate functions. The performances of the two sections in various audio and video circuits are briefly discussed below. A chart, indicating the permissibility of a large number of combinations of function, will be included in the reprint of this advertisement.

When the triode and pentode of the PCF80 are to be used in different circuits in a television receiver, the advisability of a particular combination is determined by the internal coupling between the sections, especially if the signal levels are widely different, or if the pentode is to be the first valve of a high gain cascade circuit. Use in such a cascade circuit is inadvisable unless the total gain of the stage, or the source impedance, is very low. With a low source impedance, moreover, hum becomes a limiting factor.

The internal coupling has two components: the cross capacitances, and the leakage paths across them. The leakage paths are negligible in all but the most critical combinations of function. The most important capacitive coupling is that between the anode of the triode and the first grid of the pentode. Its maximum value is 0.16pF plus the valveholder capacitance of 0.15 to 0.4pF. The capacitances from the pentode to the triode grid are less than 0.02pF.

The use of the triode in audio applications is restricted by the leakage paths, which will make operation impossible at low audio levels when the pentode is used in a video or timebase circuit. Conversely, the combined effect of the cross capacitances and their shunt resistances prevents the use of the pentode as an audio valve when the triode is used in a video or timebase circuit. The power output of a single triode or even of two in push-pull is insufficient for use in the audio output stage.

With the pentode as a sound or vision i.f. amplifier, the triode may be operated in timebase, video i.f., or audio circuits. It is necessary to minimise hum by effectively earthing the pentode grid or at least by providing the lowest possible impedance to earth. The impedance should not exceed $40k\Omega$ at low frequencies, and it should be still less at higher frequencies. Capacitive decoupling of

the earthy end of the i.f. coil is obtained with 0.1μ F minfor a 50 c/s interfering signal and 0.001μ F min. for 10 kc/s. The most stringent of the combinations in this respect is with the pentode as sound i.f. amplifier and the triode as a timebase or video valve.

The pentode may be used as a video amplifier in place of the EF80 with a slightly reduced gain but a greater peak-topeak output; or as a synchronising pulse separator with a low screen grid voltage and a high value of anode load to obtain a very short grid base. The triode may be used as a frame pulse clipper or as a conventional frame blocking oscillator. Both sections may be used in a multivibrator circuit to produce a line scanning waveform. A resonant circuit in the triode anode circuit can help to stabilise the natural frequency of the oscillator, if it is locked by a flywheel synchronising system. This can be achieved by returning the control grid of the pentode to a source of controlling bias. In this application no interference is seen if either section of the valve is used for synchronising pulse separation or clipping. But with the pentode in this multivibrator circuit and the triode acting as a frame timebase blocking oscillator, some interaction between line and frame scanning occurs. This combination is not recommended.

In fringe areas, 405-line operation under noisy conditions is considerably improved by flywheel synchronisation. The line timebase coincidence detector which is necessary can incorporate the PCF80 pentode with the two coincident pulses applied to the control and screen grids. The triode can then act as the separate pulse amplifier. In this application the triode or the pentode may be transferred to any of the other scanning applications already discussed without undesirable stray coupling effects.

Circuits for the recommended applications will be published in a future advertisement in this series.



Reprints of this advertisement, with additional notes consisting of a comprehensive application chart, are available without charge from the address below.

MULLARD LTD., Technical Service Department, Century House, Shaftesbury Avenue, W.C.2

WIRELESS WORLD



The MAGNAVIEW receiver, incorporating the latest techniques, gives excellent performance and its large-screen, flat-faced, aluminium-backed Brimar Teletube gives extra bright pictures.



and reduces home construction to the simplest possible proportions. Anyone with previous experience in the construction of radio receivers, and an elementary knowledge of the principles of TV circuitry, can build it.

EASY to BUILD

Ask for this booklet

—its popularity has necessitated the issue of a

LANGE NOREEN T.V.

HOME CONSTRUCTOR

THIRD EDITION

A number of circuit modifications have been introduced to give improved per-

formance. The text has been re-written and new drawings and photographs have been prepared. The first step towards building this outstandingly modern TV Receiver is to fill in the application form and post it NOW.

HRIMAH **VALVES** and TELETUBES

Please send me constructional details for the LARGE SCREEN TV. I enclose 6d. Postal Order to cover packing and postage.

NAME ADDRESS

Standard Telephones and Cables Limited FOOTSCRAY, SIDCUP, KENT

Longer Life

for LONG PLAYING RECORDS

Recording techniques have made such strides over the last two years that if you are to get the really superb reproduction made possible by the latest L.P. records you need one of the Acos "Hi-g" Pick-ups. These have been specially designed to meet the very exacting demands of the new records with their shallow groove and microscopic sound "track". This special design is necessary on two scores — firstly to do justice to the brilliant recording, and secondly to ensure the longest possible life from L.P. records. Such records are expensive; even a single playing with an unsuitable pick-up can cause irreparable harm.

If you want the best reproduction and value from your radiogram or record player and L.P. records ask your dealer (or post the coupon below) for details of the "plug-in" ACOS "Hi-g" Pick-ups — specially designed to replace existing pick-ups on most famous makes of record playing equipment. The cost? 32/6d. (plus 10/5d. P.T.)

> ACOS devices are protected by patents, patent applications and registered designs in Great Britain and abroad,

. always well ahead

TO: COSMOCORD LIMITEO, ENFIELD, MIDDLESEX.

Please send me details of ACOS "Hi-g" replacement pick-up heads

NUMBER PLEASE!

THE HURST

The new restricted form of London Telephone Directory no longer includes subscribers, like Cosmocord, in "fringe" areas. Please note therefore that our number is ENFIELD 4022.


ADERESS

NAME.

ww


A UNIVERSAL DOADING PLUG Tip or back solder or erimp-as you please Tip soldered with braid as pigtail through collet and nut

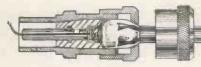Tip soldered with braid bunched up against collet



CLAMPING NUT AND COLLET ONLY REMOVED FROM BODY HOUSING

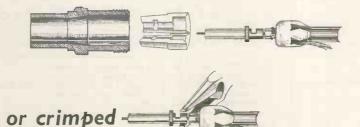Back soldered with braid as pigtail or bunched



• We have now modified out L.1329 coaxial plug to include a hole through the length of the pin so that this can be tip soldered as an alternative to back soldering or crimping. In view of the marked preference for tip soldering, we have also re-instated our all-metal L.734/P coaxial plug.

These two types will now be interchangeable, and by supplying both types we believe we have met most needs that can arise, particularly the requirements both of those who prefer to load the plug without completely dismantling it, and those who dismantle the plug completely before soldering. Both plugs are also suitable for use as a temporary connection, without either crimping or soldering, but this is very bad practice.



"BELLING-LEE" NOTES

These notes have been contributed by our senior research engineer, and introduce a very interesting basis of comparison for aerials, and can, of course, be applied to aerials of any manufacture.

Goodness Factor For Aerials

It has been often stated that aerials for use in fringe areas should have the maximum possible forward gain, thus ensuring that as much signal as possible is available at the receiver. This is undoubtedly the condition required for reception in areas where local interference can be ignored, and where the signal is limited by the noise generated in the receiver itself.

In some areas the picture is marred by local interference, by motor cars, etc., while in others an otherwise perfect picture is spoilt by ghost reflections. In both these cases the directional characteristic of the aerial is important. This is the property of the aerial which enables it to distinguish between the wanted and unwanted signals.

If we now consider the fringe area in which interference is present, we are faced with a problem of how to describe an acrial as neither the forward gain nor the polar diagram give a complete picture of its performance. A Goodness Factor can, however, be defined, but the validity of this Factor can only be tested by practical observation of pictures under a wide range of conditions. We are considering the use of Goodness Factor F, defined by the equation $F = \frac{V}{A}$ where V is the voltage

gain of the aerial relative to a half-wave dipole and A is the total area under the polar diagram, assuming the area under a dipole polar diagram, to be unity, and the amplitude of the diagram in the forward direction to be the same for all areas.

It can now be seen that F includes both the forward gain and the directional characteristics of the aerial and increase in either of these is improved. As an example the Goodness Factor of various "Belling-Lee" aerials is as follows.

BROADSIDE-3	element	array,	5.2
Junior Mult.			3.3
Senior H			2.5
Junior H			2.7
Kayrod			2.3
Dipole			1.0

Advertisement of

BELLING & LEE LTD. -Great Cambridge Rd., Enfield, Middx. Written 14th December 1954

STABILISED POWER SUPPLY UNIT FOR PHOTO-MULTIPLIERS

EDISWAN

Ediswan now have available a new stabilised power supply unit which has been specially designed to feed Photo-Multipliers. It is particularly suitable as a supply unit for Ediswan Mazda Photo-Multipliers type 27.M1, 27.M2 and 27.M3.

	BRIEF	SPECIFICATION	
--	-------	---------------	--

High stability 200-250 v., 40 - 100 c.p.s. High stability D.C. supply w tween 300 and Max. current or neg. may b	ariable be- 1,100 volts. 2 mA. Pos. between 1,	ange in mains ge results in a less than 0.1% 100 volts and utput.	00 ohms. Less than 0.01% R.M.S.

MOUNTING The Unit Is suitable for standard rack mounting or for bench use. Bench Stands are available.



a'new

PRICE - £48

Further information is available on request



RADIO DIVISION • THE EDISON SWAN ELECTRIC COMPANY LIMITED 155 Charing Cross Road, London, W.C.2. Telephone: Gerrard 8660. Telegrams: Ediswan, Westcent, London Member of the A.E.I. Group of Companies

CONVECTION HEATING

FORCED OR NATURAL?

Broadly speaking, there are two types of convection heater: the *natural* convection heater, which depends for its operation solely on the physical difference in the density of warm and cold air, and the *forced* convection heater, in which a fan is used to force warmed air downwards and forwards, away from the heater.

Although natural convectors have their uses—for example in halls, landings or passages, which are not normally occupied for lengthy periods—forced convectors are much more efficient and economical in operation.

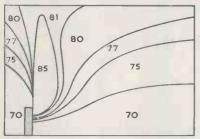


Fig. 1 Diagram showing the heat zones produced by a typical 1 kW natural convection heater. The upwards and outwards path of the warm air is quite clearly indicated. If the power of the heater were increased to 2 kW, temperatures in the particular zones would increase, but the general disposition of the zones would remain the same. The air at floor level would thereforebe noticeably colder. (Temperatures in both illustrations are in degrees Fahrenheit.)

A natural convector warms only the air passing through it and in its immediate vicinity, and this warmed air, being much lighter than the main body of air in the room, rises rapidly towards the ceiling, where most of the heat is dissipated. Although there will be at times a certain amount of mixing of small portions of rising warmed air with the general body of colder air, due to movement of persons in the room, the fact remains that in general the warmest air will be at ceiling level, and the colder air at floor level.

Thus, before the occupants of a room heated by natural convection feel very much benefit, the temperature of the air at ceiling level has to be increased considerably. Obviously, overall room temperature increases very slowly, and power consumption, and therefore costs, are increased.

The steep temperature gradient created by this method of heating often gives the occupants of a room the impression of draughts around the feet and a feeling of "headiness." This arises because, while the human body can withstand a higher temperature around the feet and legs, it cannot, with comfort, tolerate an atmosphere in which there is an upper zone of much warmer air. This warm upper zone, being semi-static in nature, also tends to act as a barrier to rising tobacco smoke and other fumes, thereby worsening the general atmospheric condition. A further disadvantage of natural convection heating is the soiling of the walls and ceiling immediately above the heater caused by the uprising air current becoming dust laden. Much time and effort have been expended on natural convectors in attempts to overcome these disadvantages, all of which arise from the very low velocity of the warmed air emerging from the heater outlet. In spite of these efforts, experiments show that the maximum distance the warmed air can be projected from the outlet of this type of heater is about 6 inches.

With the *forced* air convection heater the effects are the opposite of those occurring with the natural convector. By using a suitable blower system the warmed air is forced, against its natural tendency, downwards and outwards into the room. This stream of warmed air is given sufficient velocity to project it some ten to fourteen feet from the heater.

Unlike the natural convection heater, the forced air convection heater produces the warmer air zone at floor level. The temperature gradient throughout the room is very much less than with a natural convector: the difference in temperature being as little as 5°F between floor level and ceiling.

Thus, with forced convection heating, the warmed air is circulated throughout the entire room and rapidly increases the overall temperature; there is no draughtiness around the occupants' feet, and since the upper air is at a slightly lower temperature than the air at floor level, there is no feeling of "headiness." Other advantages of the forced convector lie in better physical design. In order to get maximum air velocity natural convection heaters are usually tall in relation to their width and depth: not always an ideal shape from the points of view of stability and convenience in placing in a room. Forced convectors can be designed to much more stable dimensions, and can be made compact enough to fit unobtrusively into any convenient position. Furthermore, forced convectors will

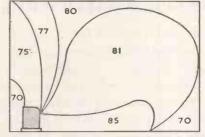


Fig. 2 Heat zones produced by a forced convection heater, the "H.M.V." 2 kW Cavendish Heater. Note the even temperature gradient throughout the entire room, with the warmer air zone at floor level. These figures were plotted from actual tests taken in a room measuring $14' \times 11'3' \times 8'$ high (1,265 cu. ft.), with a semi-circular bay containing 5 windows.

operate with unimpaired efficiency even when sited below a window. Cold air currents in the vicinity of the window gravitate towards the floor, where instead of creating a draught as they would normally do, they are warmed by the heater and circulated into the room. Similarly, cool fresh air entering the room through the window will be warmed by the heater and will help to keep the air within the room fresh and clean.



FEBRUARY, 1955

BORDELI FOR RESEARCH		EQUIPMENT ENT and TESTING
T.V. TRANSMITTERS-		BEE
RADAR		0
NUCLEONICS	- 80	20 //
INDUSTRIAL ELECTRONIC	S	

PORTABLE OSCILLOSCOPE TYPE WM.3.B.

A compact general purpose D.C. Coupled portable Oscilloscope with facilities for rapid precision time and voltage measurements. Volts and time meter presentation — no calibration markers required. Displayed waveform measured by voltmeter bridge system (visual null balance). 9 range voltmeter gives high accuracy readings unaffected by amplifier gain or linearity. Dual 'Y' input paths with attenuators afford signal comparison and mixing facilities. Floating circuit enables AC/DC signals to be measured with respect to D.C. potentials within ± 500 V.

DISTRIBUTED AMPLIFIER TYPE 2B 50 c/s - 100 Mc/s

A unit designed for use with high speed Oscilloscopes to provide amplification over a very wide frequency spectrum at high output voltage levels.

The amplifier is extensively used in the study of high speed waveforms having rise times in the milli-microsecond range. It is being widely used with scintillation and coincidence counters, high speed scalers, and signal generators.

SPECIFICATION

Input Impedance, 75 ohms. Output Impedance, 200 ohms nominal. Max. Output, 150 Vpp. Phase Response, Substantially linear over pass band. Bandwidth, 50 c/s-100 Mc/s. Gain, x 12.

For further details write to :

SPECIFICATION

C.R.T. E.H.T. 0.8 & 1.2 kV.

'Y' Amplifier D.C. - 6 Mc/s.

MAX. SENSITIVITY 350 mm/V (at reduced bandwidth)

VOLTAGE MEASUREMENT \pm 10 mV to \pm 500 V AC/DC ± 21/2% F.S.D.

TIME MEASUREMENT 0.25 microseconds - 40 milliseconds

SWEEP DRIVE Triggered or recurrent, phase and frequency selected

WRITING SPEED 6 milli-seconds/cm - 0.5 microsecond/cm



E.M.I. FACTORIES LTD. HAYES, MIDDLESEX. Phone: Southall 2468 Ext: 857 & 655





COSSOR **Telecheck and Marker Generator** Model 1322 for Bands I and III

Model 1322 — used in conjunction with a cathode ray oscillograph - provides equipment for the display, measurement and correct adjustment of RF and IF response curves of television receivers. This entirely new instrument comprises a swept oscillator covering the Television BANDS I and III (5-75 Mc/s. and 155-255 Mc/s.) and a frequency marker oscillator so that precise calibration of the oscillograph display may be made; accuracy of the frequency of the marker pips being verified by reference to an internal crystal. The

alignment oscillator is set to the video carrier to which the receiver is tuned and the sweep (either I Mc/s. or IO Mc/s.) is automatically derived from the time base voltage of the display oscillograph. The response of the "strip" under test to the frequency band applied is then presented on the screen of the cathode ray tube. The RF output of Model 1322 is available at 75 ohms and is adjustable from a maximum of 40 millivolts to a minimum of 10 microvolts through a coarse and fine attenuator.

TELECHECK CONVERTER FOR BAND 111 Model 1321

COSSOR

This adaptor provides owners of Model 1320 "Telecheck" with an extension of the frequency range of the original instrument into the BAND III television channel. Thus, alignment procedures adopted for BAND I RF/IF "strips" are available also for BAND III receivers. A selection of the desired BAND is made by means of a switch. Pattern generator facilities for picture time base linearity checks have been retained. Model 1321 Adaptor is designed for permanent attachment to the standard "Telecheck" providing a neat, light and compact unit. Mounting is effected by four screws and the inter-connecting wiring is carried in a single insulating sleeve.



ELECTRONIC INS

Write for illustrated leaflets about both these instruments : OL60 A. C. COSSOR LTD · INSTRUMENT DIVISION (Dept. I) HIGHBURY GROVE · LONDON · N.5 Cables: Cossor, London Telephone: CANonbury 1234 (33 lines) Telegrams: Cossor, Norphone, London

F

FEBRUARY, 1955

-

6668

177

Marconi VHF Multi-Channel Equipment

TYPE HM 181

90

Multi-channel radio links are not only recognised economic alternatives to line and cable routes wherever the latter are costly because of intensive urban development or the wild nature of the terrain; they are frequently preferable in their own right. The type HM 181 equipment has been designed for comparatively simple schemes using two terminals working point-to-point or with a limited number of repeaters. It operates in the frequency range 150-200 M/cs, employs frequency modulation and gives high performance with low distortion.

It provides the following facilities:----

- 8, 16 or 24 channels
- Repeaters with easy channel dropping facilities
- Unattended operation
- Engineers' order wire
- Ease of access for maintenance

Over 80 countries now have Marconi equipped telegraph and communication systems. Many of these are still giving trouble free service after more than twenty years in operation



Lifeline of communication MARCONI

COMPLETE COMMUNICATION SYSTEMS

Surveyed, planned, installed, maintained

MARCONI'S WIRELESS TELEGRAPH CO., LTD., CHELMSFORD, ESSEX Partners in progress with The 'ENGLISH ELECTRIC' Company Ltd.

LEARN THE

PRACTICAL

EWI INSTITUTES

EXPERIMENTAL OUTFIT

NEWI EXPERIMENTAL KITS in Radio, T.V. etc.



SenTerCel H.T. rectifiers from 125V 30mA to 250V 300mA

Specially designed for use in domestic Radio & Television receivers, these miniature rectifier stacks have an established position with manufacturers to whom reliability, small dimensions and low costs are important.

FEATURES

SELENIUM

RECTIFI

- Instant starting no warmingup period
- Unlimited instantaneous overload
- No limit to size of reservoir capacitor
- Simple mounting-no valve holder

RM

RM4

RM3

- Withstand overloads such as charging current of de-formed electrolytic capacitors
- Low heat dissipation
- Practically indestructible in service
- Simple wiring—two connectors only
- Small size . . . low weight
- B LOW COSt

Standard Telephones and Cables Limited Registered Office: Connaught House, Aldwych, London, W.C.2

RECTIFIER DIVISION : Edinburgh Way, Harlow, Essex.

RMI


RMO

TYPE

Telephone : Harlow 26811

el

VORTEXION

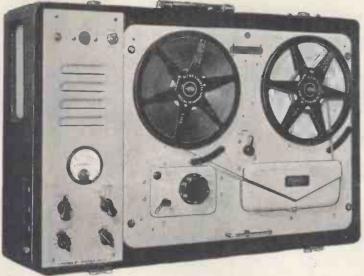

The amplifier, speaker and case, with detachable lid, measures $8\frac{1}{2}$ in. x $22\frac{1}{2}$ in. x $15\frac{3}{2}$ in. and weighs 30 lb.

PRICE, complete with WEARITE TAPE

POWER SUPPLY UNIT to work from 12 volt Battery with an output of 230 v., 120 watts, 50 cycles within 1%. Suppressed for use with Tape Recorder. PRICE £18 0 0.

TAPE RECORDER

* The noise level is extremely low and audibly the hum level and Johnson noise of the amplifier and deck are approximately equal. Only 25% of this small amount of hum is given by the amplifier alone.

★ Extremely low distortion and back-ground noise, with a frequency response of 50 c/s.—10 Kc/s., plus or minus 1.5 db. A meter is fitted for the measurement of signal level and bias level.

* Sufficient power is available for recording on disc, elther direct or from the tape, without additional amplifiers.

* A heavy mu-metal shielded microphone transformer is built in for 15-30 ohms balanced and screened line, and requires only 7 micro-volts approximately to fully load.

★ The .5 megohm input is fully loaded by 18 millivolts and is suitable for crystal P.U.s, microphone or radio inputs.

A power plug is provided for a radio feeder unit, etc. Variable bass and treble controls are fitted for control of the play back signal.

+ The power output is 3.5 watts heavily damped by negative feedback and an oval internal speaker is built in for monitoring purposes.

* Facilities are provided for using the amplifier alone and using power output or headphones while recording or to drive additional amplifiers.

★ The unit may be left running on record or play back even with 1.750 ft. reels with the lid closed.

FOUR CHANNEL ELECTRONIC MIXER

is almost essential for the professional or semi-professional where a number of different items have to be mixed on one tape recording.

It is recommended by a number of tape recorder manufacturers for this purpose.


Any normal input impedance can be supplied to order, balanced or unbalanced, the standard being 15-30 ohms balanced.

The normal output is 0.5 volt on 20,000 ohms or less, but 600 ohms is available as an alternative.

The steel stove enamelled case is polished and fitted with an engraved white panel suitable for making temporary pencil notes.

An internal screened power pack and selenium rectifier feed the five low noise non-microphonic valves.

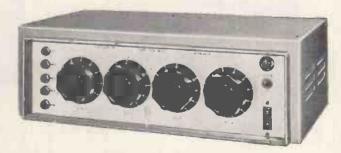Used in many, hundreds of large public address installations and recording studios throughout the world.



PRICE £36 15 0.

Manufactured by

VORTEXION LIMITED, 257-263, The Broadway, Wimbledon, London, S.W.19

Telephones: LIBerty 2814 and 6242-3

Telegrams: "Vortexion. Wimble, London."

04

FEBRUARY, 1955



YOUR LOCAL DEALER

MODERN TECHNIQUES

138-144 Petherton Road, London, N.5

Tel. : Canonbury 5896

E.M.I. INSTITUTES—the only college which is part of a great industry.

E.M.I. INSTITUTES DEPT. 12. E, 10. PEMBRIDGE SQUARE, LONDON, W.2 TEL.: BAYSWATER 5131/2 Associated with "H.M.V." MARCONIPHONE COLUMBIA ETC.

WIRELESS WORLD

AT .

with this increased demand.

REAK

nd this

From long experience and by extreme attention to design details during development work on the pre-production models, we enable our labour force to achieve a high output per man-hour. The labour costs thus saved offset the increased costs incurred for high-grade materials, components and finishes, and this together with quantity production (made possible only by a world-wide market) explains how quality products may be sold at reasonable prices. The results obtainable with the new Leak TL/10 and "Point One" are indistinguishable from those obtained with the TL/12 model—a fact easily proved by an instantaneous changeover test. The new TL/10 has been used since its introduction for all our public demonstrations, including those at the New York Audio Fair. These are some of the reasons why sales of the TL/10 and "Point One," since their introduction in April last year, are three times as great as for the famous TL/12 in the corresponding months of 1953—and why the size of our factory has been more than doubled to cope with this increased demand.

Sales up 300%!

with the NEW





GNS COMPLETE A price made possible only by WORLD-WIDE SALES

* Make this THE HEART of your HI-FI EQUIPMENT

TL/10 POWER AMPLIFIER

This 10 watt amplifier maintains, in every respect, the world renowned Leak reputation for precision engineering, fine appearance and fastidious wiring.

SPECIFICATION

Circuitry

A triple loop feedback circuit based on the famous TL/12. The output transformer is the same size as in the TL/12.

Maximum power output: 10 watts.

Frequency Response: ± I db 20 c/s to 20,000 c/s.

Harmonic Distortion: 0.1%, 1,000 c/s. 7.5 watts output.

Feedback Magnitude: 26 db, main loop.

Damping Factor: 25.

Hum: - 80 db referred to 10 watts.

Loudspeaker Impedances: 16 ohms, 8 ohms, and 4 ohms.

+ Distortion Of the order of 0.1%. ★ Write for leaflet W ★

Hum Negligible, due to the use of recently developed valves and special techniques. * Input selector Radio, tape, records; any and all records

can be accurately equalised.
 ★ Treble
 Continuously variable, + 9 db to - 15 db at 10,000 c/s.

★ Bass Continuously variable, + 12 db to - 13 db

at 40 cls.

at 40 c/s. ★ Volume Control and Switch The switch controls the power supply to the TL/10 power amplifier. ★ Tape Recording Jacks An exclusive feature. Readily accessible jacks are provided on the front panel for instantaneous use with Tape Recorders which have built-in (low level) amplifiers.

H. J. LEAK & CO. LTD., BRUNEL ROAD, WESTWAY FACTORY ESTATE, ACTON, W.3 Phone: SHEpherds Bush 1173/4/5

Radio The radio input sockets at the rear permit the connection of the LEAK V.S. tuner unit. An input attenuator is fitted. H.T.

"POINT ONE" PRE-AMPLIFIER

The handsome gold escutcheon plate contributes to the elegant appearance, and blends with all woods.

Pickup The pre-amplifier will operate 'Am any pickup generally available in the world. A continuously variable input attenuator at the rear of the pre-amplifier permits

the instantaneous use of crystal, moving-iron and moving-coil pickups.

and filament supplies are available from the pre-amplifier.

Telegrams: Sinusoidal, Ealux, London

Cables : Sinusoidal, London

· FEBRUARY, 1955

GENUINE HALF-PRICE OFFER.

> COILS-T.R.F. AND SUPERHET T.R.F. long and medium wave with circuit diagram, 5/6. Superhet long, m and short wave, aerial and oscillator colls, e.g., set of six colls with circuit, 10/6.



96

ł

CHASSIS ASSEMBLY

GHASSIS ASSEMBLY S colour, S waveband scale covering standard, Long, Medium, and Short wave-bands, scale pan, chassis punched for standard 5-valve superhet, pulley driving head, springs, ctc., to suit. Scale size 14jin x 3jin. Chassis size 16in. x 3hu. 21n. deep. Price 15., plus 1/6 post Note.-This is the one that fits our 39/6 table schutet.

RADIO SCALES. 4/- DOZEN



An exceptional bargain this month is our assorted parcel of radio scales. A most useful collection for all who make up experimental or other radios. We offer tweive assorted scales mostly in two or three colours for 4/-, plus 94, post and packing. Linker quantity only. RESISTORS

1

50 assorted 1 and 1 watt resistors. Rang-ing between 10 ohm. and 10 megohm. (Our selection.) Price 5/- pkt. Ditto, 1 watt, 7/6.



EX-ROYAL NAVY SOUND POWERED TELEPHONE

POWERED TELEPHONE These require no batteries, and will go for long periods without stiention. Complete with generator and sounder which gives a high pitched note, easily heard above any other noise. Also fitted with an indicator lamp which in quite sticutions can be used instead of the sounder, or where several are used together will indicate which one is being called. Size 71in. x 91in. x 71in., wall mounting, designed for ships' use, but very suitable for home, office, warehouse, factory, garage, etc. Price 57/6 each, plus 4/6 carriage.

INSTANT HEAT CONVECTOR INSIANI HEAT CONVECTOR The heater with the lowest possible thermal capacity, 4% long; made from heavy gauge sheet steel (galvanied), 1 kW., suitable A.C. or D.C. Price only 22, or with thermostat §3/15/-, Note.— The thermostat mounts separately and will control up to three heaters.

CLEVELAND CAR BATTERY CHARGER



Gives 1; amp. charge-uses ever-lasting metal recti-

AIGROMETER Exceptional purchase en-ables us to offer a lin. procision micrometer at the very low price of 10%. A micrometer is an essential part of an engineer's equipment. You will have found the need for one on many occasions in the past for measuring wire gauge. etc. Price 10%, post free. Note.-We now have a waiting list for this, orders in rotation. RAM 912 OSRAM 912

The constructional dat: for this Hi-Fi amplifier is available, price 3/6. which amount will be credited to you if you buy the components later. One "912 Shopping List" will be included with the booklet.



GRAMOPHONE AUTO-CHANGER

Latest type by all famous makers are in variably in stock at competitive prices.

 $\langle \cdot \rangle$ THE "WINDSOR 5"

THE "WINDSOR 5" This is a 5-valve A.C. superhet covering the usual long, medium and short wave-bands. It has a particularly fine clear dial with an extra long pointer travel. The latest type loctal valves are used and the chassis is complete and ready to operate. Chassis size I510. x 61n. x 61n. Price £9/19/6 complete with 81n. speaker. Carriage and Insurance 10/-H.P. terms if required.

TABLE RADIO CABINET

. TABLE KADIO GABINE! Due to a special purchase, we are able to offer this very fine cabinet, size approx. $15\times14\times61$. Walnut vencered and satin finished, 39/6, carriage and packing 3/6. Note.—This cabinet is the correct one for the Windsor chassis above with 61in sneuker.

TERRIFIC NEW CIRCUIT

CCASIONAL 55 - we have evolved a new T.B.F. circuit and have had really amazing results, equal in fact to many superhets. You really should try this circuit. All parts including valves (6X7, 6376, 6and 6X5) and Bakelite case with back cost only §5/10/-, plus 2/6 post and insurance. Data included with the parts is also available semarately wrice 24-.

TRANSFORMER 100 WATTS

TRANSFORMER 100 WATIS These are transformers with a wound primary tapped 200, 220, 240, but no secondary There is ample window space, however, for the hand winding of second-ary to suit your own requirements. Approximately two turns per volt are required. The amps taken out will depend upon volts, e.g., 10 amps, at 10 volts, 50 amps, at 2 volts, etc. etc. Price 10/-, post and packing 2/-

separately price 2/-.

64in. sp

REFTHOVEN CHASSIS Extremely well built on chassis size approx. $9\frac{1}{2} \times 7\frac{1}{2} \times 8\frac{1}{2}$, using only first-class components, fully aligned and tested, 110-240-volt A.C. mains operation. Three wave bands covering medium and two shorts. Complete with five valves, frequency changer, double diode triode, pende output and full wave restifier. Special cash-with-order price this month, $\frac{4}{5}/19/6$, carriage and insurance 7/6.

BARGAIN FOR CONSTRUCTORS

Modern style cabinet in contrasting veneers, with metal chassis, three knobe, coloured scale, and pointer. Price 29.6. post, etc., 2/-. All other components to build 2-waveband superhet. Price 25. Data, 1/6 (free with components.)

HEATING TRANSFORMER

2] volts at 400 amps. Continuous rating: suitable for unfreezing water pipes sting of resins during casting, setting of glues during cabinet making, edge veneer-ing, etc., etc. Compite in metal case with carrying handle, price £12, carriage and packing 6/-.

LIGHTWEIGHT REFLECTORS

Ideally suitable for all purposes where the in-tensification of electric illumina-tion or Infra Red is required. The material nsed is lightweight alu-minium highly

minlum, highly polished, All are pierced for Standard Lamp-

STAR. 7 in. dia. by 6in. deep. Price 7/6 each. Post, etc., 1/3.

SENIOR. 111in. dia. by 4in. deep. Price 13 6 each. Post, etc., 1/9.

JUNIOR. 61 in. dia. by 31 in. deep. Price 7/3 each. Post, etc.,

BIJOU, 5Hn. dia by 2in. deep. For 40-60 watt

lamps. Price 6 each. Post. etc Price 6/8

BELL. 5in. dla. 5in. deep. Price 6/3 each. Post. etc., 1/3.

1/3.

holders

medium,

BARGAINS TO CLEAR

2-VOLT ACCUMULATORS

Made for the Porces by one of the most famous firms in the world. 15 amp.-hour, elze approx. 6×1 fin. square in chomte case, pre-charged, only need filling with acid, 2/9 each, plus 1/- post and in-surance.

PORTABLE CABINET



handle. We can supply, where re-quired, the metal chassia, all other parts necessary to make a Mains or Battery portable. Note: All of these cabinets have slight imperfections; these are hardly notice-able however, and will not impair the performance or safety of the set. Price 7/6 each, post and insurance 3/6.

REMOTE CONTROL



5-AMP. SURFACE SWITCHES

HICRAFT

Obiong Brown 1-way 1- each. Ob-long White 1-way 1/- each. Obiong Brown 2-way 1/3 each. Obiong White 2-way 1/3 each. Round White 1-way 10d. each. Round Brown 2-way 1/- each. 2-way 1/- each.



WAVE-CHANGE SWITCHES

One dozen assorted wave-change switches, ideal for experimen-ters. Note, these are un-used and not removed from equipment. Our assortment. Price 5/-, post and packing 1/-



110-VOLT 21-AMP. RECTIFIER

This is an excellent unit suitable for driving 110 v. D.C. equipment from 230 v. A.C. mains or for charging bat-teries for stand-by lighting, ctc. Made for the Government-mew and unused, with switchgear. Price £17/10/- each.

NAIL INSULATORS Suitable for electric fences. indoor aerials, etc., 3/- per dozen, post and packing 1/-.

WESTINGHOUSE RECTIFIER Full wave-suitable for up to 80 volts at 15 milliamps. Ideal for relays, meters, etc. Price 2/6, post 6d.



DECCA CRYSTAL PICK-UP

A snip for the connoisseur-turnover he suitable all records-limited quant 29/6, plus 2/- post and packing.

This fine speaker is coming to the front rapidly—price $\pounds 8/15/-$. Octagonal cabinet made to maker's specification, $\pounds 11/10/-$, walnut or oak.

HIRE PURCHASE TERMS.—Any goods costing £5 or more may be purchased by extended payments—deposit 10% (or more)—balance purchased by extended payments-spread over 12 months.



quantity

G.E.O. METAL CONE SPEAKER

MAKE A CONVECTOR



Almost any metal case can be con-verted into a useful convector type elec-tric heater if you tric heater if you use our porcelain mounted element 250 watts small size. 250 watts small size Price 2/6, post 6d

STARTER/CHARGER CAR KIT All parts to build 6 and 12-voit charger which can be connected to a 'flat'' battery and will enable the car to be started instantly. Kit comprising the following:---

Mains transformer	19/6
6-amp. rectifier	22/6
Regulator Stud Switch	3/6
Resistance Wire	21-
Resistance Former	2/6
Mains on/off Switch	1/-
0-5-amp. Moving Coll Meter	9/6
Constructional Data	1/6
or if bought all together price is	59/6.
plus 2/- post and packing.	
	_



THE TWIN 20

This is a complete fluorescent lighting fitting. It has built-in ballast and starters -stove enamelled white and ready to work. It is an ideal unit for the kitchen, over the work-bench, and in similar locations. It uses two 20-wast lamps. Price, complete less tubes, 28/6, or with two tubes, 39/6. Post and insurance, 2/6. Extra 20-wast tubes 7/6 each. THE F.M. FEEDER UNIT



All the parts necessary to make the Denco P.M. Unit are now available. The unit gives an A.F. output suitable for feeding in at the plekup sockets of any standard broadcasting receiver and superior results. can be expected. The full constructional details as prepared by the Denco tech-nicians are available—price 1/8 post free, Alternatively, they will be given free to those ordering all the parts which come to $\pm 0.8/7/6$, plus 2/8 post and packing. Note: Four valves and everything in-cluding a prepared metal chassis is sup-plied. Approximate chassis measurements plied. Approximate chassis measurements x6x1; Demonstrations at our branch

ALL MAINS THREE



A handy mld-get A.C./D.C. 3-valve mains receiver giving powerful recep-tion over long and medium waves. All

waves. All component parts, includ-ing valves, colls, resis-tors, etc., but not loudspeaker and cab-inet (you may already have these) will cost you only 19/6 plus 1/6 post-data available separately 2/- post free.

PLUGS FOR MODERN VALVE HOLDERS Each is fitted casen 18 fitted with a rubber shroud. For B7G button base and type 2 for B8A. Price 1/4 each, discounts for quantities.

-0





LAST CHANC Readers will remember that this fine receiver was offered last month at the silly price of \$25 and they have been going out very quickly. If you send immediately however, you will probably be just in time to secure one. The set, a product of one of our famous manufacturers, has H.F. stage, tuning indicator, and all modern refinements, covers 5 wavebands including short including short waves to 11 metres. Offered less valves and power - pack, otherwise complete and unused--price carriage 7/6 s octal range 7/6 £5. (uses valves).



COMPLETE TOOL KITS-THE ELECTRICIAN'S

THE ELECTRICIAN'S This is as illustrated and contains 55 fine tools arranged on 8 trays in an automatic steel tool-box. The box opena under slight that a practical electrician needs, including tenon naw, ratchet brace, hack-saw, chieles for wood, brick and steel, pliers, side coun-ters, hammers, spanners, socket wrenches, pad-saw, et. Price El5/10/*, or H.P. if required. RADIO ENGINEER'S

RADIO ENGINEER'S This again is fitted into an automatic tool-box and contains 50 tools including pliers, side counters, screwdrivers, side and straight snips, hammers, spanners, and socket wrenches, hand-drill, B.A. taps, drills, etc. Price £11/10/-. H.P. terms if required.

THIS MONTH'S SNIP

ATTACHE CASE. Complete with leather handle and clasps--uitable for almost any portable instrument. Limited quantity--price 23/6. Carriage and packing 2/6. A similar model but slightly smaller and m one colour 19/6, plus 2/6 carriage.



THE CLEVELAND

"ORGANTONE"

The Cleveland "ORGANTONE" is a Svaire 3-ware band superhele covering to a very stringent specification. Orram miniature valves are employed and low loss iron cored coils account for an excellent signal to noise ratio for a recellent signal to noise ratio for the user taken to ensure freedom from frequency drift. The output stage utilises variable negative feedback for tone control, and, but for stand-ard pentode correction, no cut in the ordinary sense is applied. A gram, position is provided and reproduction of records is particularly good. An anyly proportioned power transformer with a primary tapped for 110-280 volts gives complete isolation from the mains.

provided and represent a primary tapped for the second power transformer with a primary tapped for the size is 10 in. x 44 in. from the mains. Chassis size is 12 in. x 7in. x 7in.—Scale size is 104 in. x 44 in. This receiver has been tested in particularly difficult areas and its stability and noise rejection have produced exceptional results. Price 2117(10/- or 2115/0 deposit—carriage, etc., 7/6. A circuit diagram and photograph available price 2/- post free. A circuit diagram and photograph available price 2/- post free. If has a 7-valve

ANOTHER GLEVELARID GRASSIS-THE THEMEDO The first Circeiand chassis was good, but this one is really superb. It has a 7-valve circuit with 6 watts output, fitted with independent hass and treble controls. It is really an efficient 8.P. circuit coupled to a high-fidelity amplifier. The chassis size is the same as the Organtone, namely 12x7x7 with the $10\,kx4$ multi-coloured scale, and it is built to the same exacting specification as the Organtone. Price $\pm 14/10/r$, carriage and packing, 7/6. H.P. terms if required.





Aut aut

BUREAU CABINET

This is a really beautiful abinet degantly veneered in walmat and finely polished, The control board, revealed when the front is dropped down is ample for the larger than average radio chassis or amplifier and slongside there is a space for a tape recorder or atto record changer mechanism. Both the radio board and the control board are left uncut to suit your own equipment. Sits a approximately 30in. high, 33in. wide, and 16in. deep Price 16 guineas. carriage 12/6. carriage 12/6.

SEE OVER

LTD.

97



WIRELESS WORLD

LAST CHANCE TO SECURE THIS BARGAIN

ADDITIONAL STOCK ITEMS

98

r

1

10 Π

lo

POTTED TRANSFORMERS

POTTED TRANSFORMERS These are of really auperior construction fitted in cast metal cases and compound filled. Terminuis come to chonite bass-bassic structure of the second structure of the 200/230 normal 50 evole mains input and fully screened primary. Type 5F1. 055-0-265 at 300 m.a.; 6.3 v. at 7 amp; 4.4 v. at 2.5 amp; Price 35/-plus 3/6 carriage. Type 5F2. 365-0-365 at 100 m.a.; 4 v. at 2.5 a.; 6.9 v. at 4.2 a Price 32/6, carriage and packing 3/6. Type 5F3. 1540 v. 2 v. at 2 a.; 4 v. at 1 a.; This is an ideal transformer for televisors and scopes using V.C.B. 97, etc. Price Science 2/6. BOTTED CHARKES

POTTED CHOKES

POTTED CHOKES These chokes are in similar type cases and therefore match the above transformers. Type 5F4. 5 H. at 300 m.a. Price 10/-, carriage and packing 2/6. Type 5F5. 10 H. at 150 m.a. Price 12/6, post and packing 2/6.

HIGH POWER TRANSFORMERS

High POwer IKANSTOKIICS, For R.F. Heaters, transmitters, etc., etc. These are open wound type for maximum cooling and have the normal 200-230 primary fully screened. Type 5P6, 1,000 v. at 4 amp, e.g., 15 K.V.A. Price £8/10/-, carriage and packing 5te.

K.V.A. Price £8/10/-, carriage and packing 5/-. Type 5F7. 1,500 v. at 1 amp. e.g., 1.5 K.V.A. Price £15, carriage and packing

AUTOMATIC MOTOR STARTER

For remote con-trol of D.C. motor between 1 and 3 kw., adjustment for 100 v. or 230v., Unused and in first-class condi-tion, compiete with metal and wired glass cover. Frice £10, car-riage 5/-.



"SNIPERSCOPE "

"SNIPERSCOPE " Fanous wattime " cate eye". used for seeing in the dark. This is an infra-red image converter cell with a silver casedum screen which lights up (like a cathode ray tube) when the electrone released by the infra-red strike it. It follows that as light form an ordinary lamp is rich in infra-red these cells will work: burgiar alarma, counting elevaties, which electors and the hundred and one other devices as will the simpler type of photo cell. Here then is a golden opportunity for some interesting experiments, price 5/- each. Data will be supplied with cells if requested.

1 9 RELAYS -0 Extra light weight. extra sensitive for high speed or radio control work, weight only 11 oz., closes ou 2 mA., solid platinum changeover contacts, adjustable pressure.

0 TELEPHONE JACK PLUGS



As illustrated 7d. each, Sockets i suit, 10d. each


Price 12/6.

TRANSMITTER VALVE 100 T H

Unused and fully guaranteed. £4/10/-each, post and insurance 2/6.

HEADPHONES

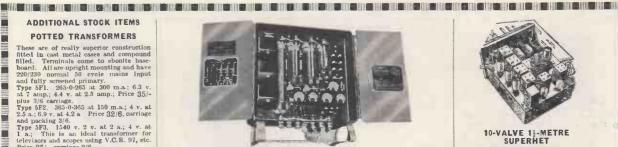American ear insert type (HS/30), 29/6; British moving coll type, 9/6; High resistance, diaphram type, 15/-.



CHARGING SWITCHBOARD

Feed this Switchboard through a Mains Transformer and Rectifier giving 24 volt D.C. up to 50 anns. and you have an excellent multi-circuit charger for almultaneously charging several batterles at different currents. This is an ex. Government switchboard tacta at 550 watta 18 volts fitted into ateel cases with doors. It contains three reverse current relays, one voltmeter, one main ammeter, two secondary ammeters and three variable resistors for controlling circuits. These are brand new, in original cases. Price £4/10/-, carriage 10/2.

AMERICAN RADAR

We have brand new, still in original unopened packing cases as shipped from America, three items of equipment which form the major parts of the radar system not only to control the Tower but also to follow it. Item 3 is known as Control Unit BC-1268-A, incorporates a cathode ray tube as well as a control equipment.

YOURS FOR

RC-184. Item 1 known as Tower TR24a is in fact the aerial base and motor driven gear box which rotates the antenna. Item 2 known as the Indicator I-221-A incorporates a magsiip device and appears

POWER FOR TR1154/55

We can offer brand-new, and unused, the two rectifier units for mains operating the transmitter TR1154 and its associated receiver R1155. Both rectifier units are completely enclosed in metal cases and operate directly from normal 50 cycle A.C. mains. Price £17/10/- the pair, carriage and packing 10/- extra.

TRANSMITTER 1131

This is a high powered transmitter for operating over the same frequency range average the same frequency range the first over 1132, i.e., 70-130 mega-operation of the same frequency range orobably contains around 2500 there are equipment. As far as we know these have rever been used hut of course have been in store for a long time and therefore they will need attention before being put into operation. We offer these less valves 237/10⁻⁷. Buyer collects. We also have a quantity already stripped so if you are edding sparse for this transmitter please get in touch with us now.

We shall be glad to negotiate with in-tended purchasers of this equipment and would also like to hear from any reader able to give any more information about it.

£1 ONLY COMMUNICATION RECEIVER R1155. This set, as most will know, is considered to be one of the finest com-

MAINS POWER PACK FOR R.1155

With Pentode output stage. Plugs into socket on receiver so no internal modification⁸ are required. Price 25/10/- complete with 5in. speaker ready to work, carriage 3/6- If bought with receiver deposit is 30/-.

MAGNETRONS

Precision made for RADAR type Nos. CV.186 and CV.64. Unused, guaranteed. Any not functioning correctly will be replaced. Price £2/10/-. Post and insurance 10/-.

R1132

NIL22 We have a small quantity of these receivers less valves still available. Their condition unfortunately is not good but they appear to be repairable, and, of course, contain a multitude of spare parts. At 30/- each they represent a real bargain. If not collecting, please include 5/- for packing and carriage.

RECEIVER TRANSMITTER 38

This is the British equivalent of the valkie-talkie. It operates on the fre-quency range 7.49 mc/s. It has many novelty applications in the home and can eventually be turned into a useful fittle portable receiver. Complete and with valves unused but not guaranteed, price 2% over 306 extra. valves unused hut 37/6, post 2/6 extra

STABILAVOLT

This is a valve designed and constructed to facilitate the taking off of several voltages, each of which will be stabilized These are brand new and unused. Price 10/6 each, post 1/- extra.

IMPORTANT NOTE

Owing to the bulkiness of many of the items listed on this page it may not be possible to keep stocks at all branches, therefore please telephone confirmation that the item is actually at the branch before journeying specially to see it.



10-VALVE 13-METRE SUPERHET

Ideal for Commercial T.V. These contain 6 valves type 8P61, and one each RL7, RL16, and RA50. 81x IF transformers 12 Mc/s. band, and hundreds of other useful components. Price 39/6, plus cariage and packing 7/6. These receivers are unused

BLOCK CONDENSERS



New and unused. .5 mfd. at 2.500 v. 3/6; 4 mfd. at 750 v., 3/6; 8 mfd. at 500/ 600 v. 5/-.

BREAKDOWN PARCEL

Unit for breaking down-offered at only a little over the price of the Aladdin Coll Formers it contains. Note. All parts can easily be removed as they are all bolted together. The unit contains:-6 Aladdin §in. Coll Formers with dust cores. cores.

6 metal cans for above coil formers.

a t-position 12-pole switch.
14-position 12-pole switch.
6 miniature R.F. chokes.
2 25-mid. 25-v. electrolytics.
30 paper tabular condensers. .002 to .1 mostly for 450 v. 56 carbon resistors, values from 1 watt to

26 carbon resistors, values from 4 watt to 2 watt. 2 medium-size R.F. chokes. 7 moulded octal valve-holders. 1 moulded diode valve-holder. 20 mica condensers (moulded, silver and

ceramic). 7 insulated top caps for valves. 4 components strips (one 40-way, one 11-way, one 5-way, and one 3-way). 1 very useful chassis, size $18 \times 5 \times 3$ [in Plus dozen of nuts, botts, servew, washers, and other useful items such as §in. spindle evidenders with the strip of the strip of the strip washers.

extenders, etc. Price only 7/6, post and packing 2/6.

GREATLY REDUCED. CATHODE RAY TUBES





Diaphragm driven, extremely sensitive, highly suitable for recorder work, No matching needed. 3/6 each.

VACUUM PUMP

Type B3 new in makers cartons-many applications in home or factory-22/6 post 1/-.



carriage 10/-. We can supply a 12 volt, 50 amp Mains Transformer at £4/5/-, plus 5/- carriage.

WIRELESS WORLD

20

1

Ĩ

ē

SERVICE DATA

SERVICE DATA 100 service: sheets, covering British freeeivers which have been sold in big quantities, and which every service entineer is ultimately bound to meet. The following makes are included: Aerodyne, Alba, Bush, Cossor, Ekco, Ever-Ready, Perguson, Ferranti, G.E.C., H.M.V., Koister-Brandes, Lissen, McMichael, Mar-ord, Mullard, Murphy, Philo, Philipe, Pye, Uitra, Undoubtedly a mine of information invaluable to all who earn their living from radio servicing. Price \$1 for the complete folder. Our Folder No. 2 consists of 100 data sheets covering motor of the popular American T.B.F. and hyper-bet recivers "all dry" etc., which have been imported Into this country. Names include Sparton, Emmerson Adminal, Crossley, R.C.A., Victor, etc. Sach sheet gives circuit diagrams and optonent values, alignment procedure, is \$1. Post free. is \$1. Post free.



INSTANT HEAT CONVECTOR

The heater with the lowest possible thermal capacity, 4ft. long; made from heavy gauge sheet steel (gaivanised), 1kw., suitable A.C. or D.C. Price only 22 or with thermostat 23/15/-. Note: The thermostat 25/15/-. Note: The thermostat point separately and w1b1 control up to three heaters.



METER KIT The Multi-meter Hustrated meas-rest CC DC. volte-and D.C. mianipe and D.C. mianipe oper volt and is equally suitable for the keen experimenter, service engineer or student. All the essential justiable for the keen experimenter, selected resistors, wire for shunts. 8-point range selector, cali-brated scale, stick-on range indicator and full instructions for making are available as a kit, price 19/8 plus 8d. post and packing. as a kit packing.



BLANK CHASSIS

Kilburn.

(Now Open.)





We confidently believe we carry the best stock of cabinets in London. The one illustrated is The Bureau, a really beautiful uablet elegantly wenered in walud and finely polished. The control board is revealed when the front is dropped. Both radio board and motor board are left uncut to suit your own equipment. Price is 16 guiness, carriage 12/5. We have many other types In stock. Pay us a visit, or send for Cabinet List

BATTERY 3-VALVER 19/6

This employs a modern circuit which ensure-good reception on both medium and long waves—all the parts including values, resistors, tuning condensers, in fact everything except loudspeaker, cabinet, and metai chassis (you may already have something suitable, from an old receiver for instance), will cost you only 19/6. Data available separately price 1/6.

ALL-DRY BATTERY BARGAIN 90 volt 3-pin plug type layer built battery by famous maker-recent manufacture-approximate dimensions 24in. x 21n. x 34in.-prot 5/r. eg.. approximately haif list-post and packing 9d.



THIS CABINET FREE

This month we are giving free a very tine modern portable cabinet to all purchasers who buy both the Truvox Tape Deck and the Cleveland Wide Band Amplifier. These three items will all fit together and make an extremely good tape recorder. Prices are as follows:-Truvox Tape Deck Mark IIIU, the very latest model, price £23.2/-. Cleveland Wide Band Amplifier, designed in onjunction with Truvox engineers to get conjunction with Iravox engineers to get the very best results from their fine deck, price £15, or £38 the two. Hire Purchase terms, send deposit of £4 or over, balance will be spread over tweive months--carriage, packing, and insurance 12/6 on the two



SENT FOR 15'- ONLY This cabinet is offered below cost. It is suitable for

This cabinet is offered below cost. It is suitable for a televisor using tube sizes varying from 121n. to 171n., its overall dimensions being 3ft. 5ln. high, 1ft 4in. deep, 1ft. 101n. wide. It is complete with plywood back and "Bowler Hat." Originally made for a very expensive televisor and really good quality. Unrepeatable. Offered at 27.5/r, carriage, packing, etc., 12/6. Note: These are cut for 121n. tubes, but the holes for the controls are not drilled.

PRICE CORRECTION

We regret that an error occurred in our January advertisement—the Elpreq Tape Recorder was incorrectly priced, it should read 39 guineas, not 35 guineas, not

NEW YEAR BARGAIN

MINI-MAINS FOUR

User a 4-vaive circuit with high-efficiency coils-covers long and medium wave bands and fits into the neat white or brown Bakelite cabinet-limited quantity only. All the parts, including cabinet, valves, in fact, everything, £3/19/6 plus 2/- post. Constructional data free with the parts, or available separately 1/6.




CABINETS 19/6

You can make an excellent bass reflex cab-inet with this well made veneered and polished walnut cabinet. Limi-ted quantity





NOBLEMAN GRAM A 70 Gn. RADIOGRAM direct from makers for only 40 Gns. Or £4 deposit. A beautiful piece of farmiture yet a most up-to-date radiogram-figured walnut lined sycamore-radio raised to com-fortable level-compartment for records-beaute A.C. mains superhet, covers long, medium and short waves-all latest re-finements, negative feed-back tone control, etc.-large multi-coloured edglet dial-istest Collaro three-speed auto-changer with the famous "Studio" pick-up-plays all types of records perfectly. Free Delivery in London Ares. Else-where £2.

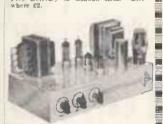

MULLARD AMPLIFIER "510"

MULLARD AMPLIFIER "510". A High Quality Amplifier designed by Mullard engineers Robust high fidelity, with a power output exceeding 10 watts and a harmonic distortion less than 4% asstremely wide and president and the from 10 to 20,000 C.P.S.--three controls are provided and the whole unit is very autable for use with the Collano Studio and most other good pickups. The price of the unit £12/10/- or 25/- deposit, plus 10/- carriage and Insurance. Alternatively, if you wish to make up the unit yourself we shall be glad to supply the components separately. . Send for the Mullard amplifier shopping list. shopping list.

NEW 5 AMP. THERMOSTAT (MINIATURE)




 $\label{eq:second} \begin{array}{l} u_{3} \times 1^{-} \times 1^{+} \ \mathrm{nign}, \\ u_{3} & \mathrm{ext} \ \mathrm{is} \ \mathrm{ext} \$



ELECTRONIC PRECISION EQUIPMENT LTD. 152-153, Fleet Street, E.C.4. 249, Kilburn High Road, | 42-46, Windmill Hill, Ruislip, | 129, Stroud Green Road, Finsbury Park, N.4. Phone: ARCHWAY 1049 Half-day Thursday. Middlesex. Phone: RUISLIP 5780 Half-day Wednesday. Phone: CENTRAL 2833 Half-day Saturday. Post orders should be marked "Dept. 2" and addressed to our Ruislip dept.

FEBRUARY, 1955

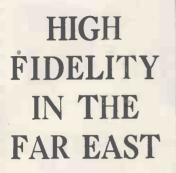Photograph kindly supplied by The Radio People Ltd., Hong Kong.





OMNI-DIRECTIONAL 3-Speaker System W15/CS SUPER 8/CS SUPER 5 Treble Units Facing Upwards—Crossover Frequencies 800 and 5000 c/s.

This superb speaker, used here for a record recital at King's College, Hong Kong, has the W15/CS as bass speaker with fundamental resonance below 30 C/S; the Super 8/CS as middle speaker; and the Super 5 as third speaker with response well maintained to 16,000 C/S. The middle and top speakers,

fitted with a volume control, face upwards to avoid undue directional effects. PRICES (Tax free)

W15/CS sand-filled enclosure £47; Treble Assembly £18; HS/CR3 Crossover with V.C.s £8/10/-. Total price £73/10/-.

Whartedale WIRELESS WORKS LTD., IDLE, BRADFORD, YORKS. Phone : Idle 1235/6 (2 lines) Grams : Wharfdel, Idle, Bradford





THE 'GATLEY' Electronic Timer

> An Electronic Time Delay invaluable in many fields of Electronics and electrical engineering, e.g., process control, photographic exposure timing, etc. Time intervals range from 1/5th sec. to 1 min. In die-cast case suitable for wall mounting.



Holley's

First Again with SOMETHING NEW in HIGH-FIDELITY

Bearing In mind that room acoustics also are an important factor when perfection in Sound Reproduction is required, we are now in a position to demonstrate *IN YOUR OWN* **HOME** the latest High-fidelity equipment by the following makers.

ACOUSTICAL, LEAK, PAMPHONIC, SOUND SALES, GOODMANS, WHARFE-DALE, CHAPMAN, TANNOY, ROGERS, GARRARD, W.B., GRUNDIG, BARKER, LOWTHER, CONNOISSEUR, ARM-STRONG.

Phone, call or write stating type and makes of equipment you are interested in.


This offer only applies at present to the greater London area but is shortly being extended to the provinces, also we still hold SIDE BY SIDE DEMONSTRATIONS of the above makers' products at

HOLLEY'S RADIO 285, CAMBERWELL ROAD, LONDON, S.E.S. Telephone : RODNEY 4988. HIRE PURCHASE TERMS. AFTER SALES SERVICE.

WIRELESS WORLD



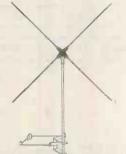THE ANTIFERENCE RANGE COVERS ALL TYPES OF INSTALLATION AT PRICES YOUR CUSTOMERS CAN AFFORD TO PAY




X4L Chimney lashing 6ft. mast for vertical mounting 75]-. Wall mounting Model X4W 66[6. 10[ft. mast chimney lashing Model X4M 115]-. Mast head mounting Model X4P 40]-.



LD7R 1 wave spacing; 6ft. mast 79/6. 1 wave spacing; 10ft. mast Model LP7M 124/6. 1 wave spacing; 12ft. mast double lashing Model PD7RM 168/-.



for chimney lashing. Complete with 12ft. mast and double lashing equipment type LSG 210|-. As FD73 but less mast and lashing equipment Model FDH73 91/6.

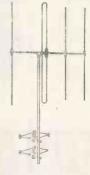

FD74 Four element array complete with 12ft. mast and double lashing equipment type LSG 231/-. As FD74 but less mast and lashing equipment Model FDH74 112/6.



LD7 Single Dipole with 3ft. swan neck mast and chimney lashing equipment 48/-.


As LD7 but with wall mounting bracket Model WD7 39/6. **SDU7** Single Dipole with ample stand-off Arm and Universal Bracket for surface mounting in a horizontal or vertical position 32/6.



U2RC A tunable "De Luxe" Room Aerial with patented insulator; cream plastic sleeved rods complete with 15ft. cream coaxial cable 21/-. Model U2R (as U2RC but less cable) 15/-.



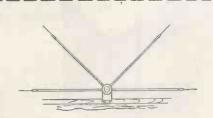U2W For mounting as shown in lofts or sheltered external positions. Complete with patented insulator, two tunable rods. mounting brackets and fixing screws 16/6.



UV4 The most powerful loft aerial obtainable. Complete with patented insulator, four tunable rods. mounting brackets and fixing screws 2216. Available 'or HORI-ZONTAL mounting as an X array 251-.

Sales Division: Bicester Road, Aylesbury, Bucks. Tel. Aylesbury 1467/8 DHB/A/L^s

FEBRUARY, 1955

GRUNDIG TK 819 THE PORTABLE TAPE RECORDER WITH 40 c.p.s. to 14,000 c.p.s. FREQUENCY RANGE

SUPERBLY designed and engineered by Tape Recorder speciallsts. Two tape speeds $(3\frac{3}{4}in./sec. and 7\frac{1}{2}in./sec.)$ for 2 hours' speech or one hour's music recording per spool of tape. Automatic stop at end of spool. Fast forward or rewind time (2 minutes per full tape of 1,200ft.). Built-in precision place indicator, recording level meter by magic eye. Built-in pockets for 2 spare spools and microphone. Most Radio and Photographic Dealers stock Grundig. Ask for a demonstration or write for folder with full specification—Grundig (Gt. Britain) Ltd., Kidbrooke Park Road, London, S.E.3. (Electronics Division, Gas Purification & Chemical Co. Limited.)

95 GNS

(less microphone). Wide-range Grundlg Ribbon Microphone 12 gns. Grundig Moving Coil Microphone 6 gns. Attractive Hire Purchase Terms.

GRUNDIG

An audio frequency triumph!

> THE WORLD'S FINEST portable TAPE RECORDERS



U.K. Agents : The SOLARTRON ELECTRONIC GROUP LTD. THAMES DITTON, Surrey. MEIRIX-

The entire range of electronic and electrical test apparatus manufactured by the Internationally famous Companie Générale de Métrologie of Annecy, France can now be obtained from the exclusive U.K. Agents, The Solartron Electronic Group Ltd., of Thames Ditton, Surrey.

SOLARTRON-

A NEW TECHNIQUE IN HIGH SPEED WAVEFORM MONITORING

BANDWIDTH : 10 kc/s to 300 mc/s

INPUT IMPEDANCE OF EACH PROBE : Approx. 1 pf (input element of variable capacity divider)

MAXIMUM SENSITIVITY : Full Scale Deflection for 1 Volt input

TIME SCALE : Variable from .05 microsecs to 5 microsecs.

RECURRENCE RATE OF MONITORED WAVEFORM : 100 c/s to 10 kc/s

CALIBRATION :

Provision is made for accurate measurement of time and voltage scales of a waveform

PREVENTION OF JITTER : A circuit is incorporated for providing a stable display when a monitored waveform is jittering with respect to its driving pulse.

HIGH SPEED RECURRENT WAVEFORM MONITOR TYPE \$00

The wide bandwidth and high sensitivity of the instrument as well as the very high input impedance result from the use of a sampling technique. During each recurrence a measurement is made of the instantaneous amplitude of one point in the waveform. This measurement is amplified and applied to the cathode ray tube as one co-ordinate of a graph of the waveform. During subsequent recurrences, instantaneous measurements are made of different points, resulting, after about 100 recurrences, in a complete graph.

Please write for further information.

METROPOLITAN - VICKERS ELECTRICAL CO LTD - TRAFFORD PARK - MANCHESTER, 17


Member of the AEI group of companies

Leading Electrical Progress

FEBRUARY, 1955



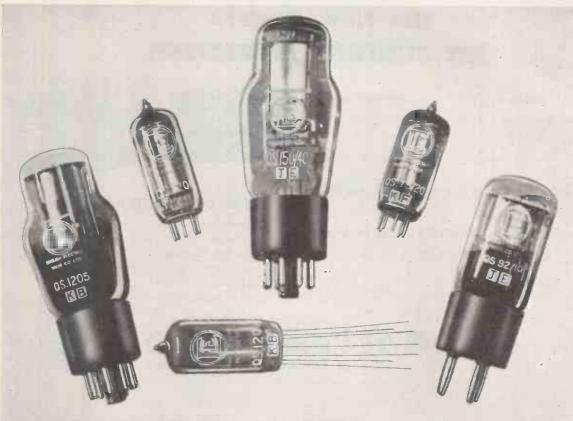ENGLISH ELECTRIC WIRELESS WORLD COMPANY LIMITED



Voltage Stabilisers

- **ENGLISH ELECTRIC VALVE COMPANY** make the largest range of gas filled voltage stabilisers in this country.
- **ENGLISH ELECTRIC VALVE COMPANY** possess wide experience in production to fine limits which is your assurance of high quality products.
- **ENGLISH ELECTRIC VALVE COMPANY** voltage stabilisers satisfy all requirements for reliability, and British Service types are fully approved.

Whether your needs are for General, Rugged or High Stability type valves, make sure before completing your specifications that you have full details of all English Electric Valve Company products.

Write to :

ENGLISH ELECTRIC VALVE COMPANY LIMITED

WATERHOUSE LANE . CHELMSFORD . ESSEX

In stock at Webb's Radio the NEW Rogers "RD JUNIOR" AMPLIFIER

This 1955 design offers unapproachable value, the specification rivals amplifiers costing double its price of **£25**

★ OR ON WEBB'S EXTENDED PAYMENTS DEPOSIT £5, FOLLOWED BY 12 MONTHLY PAYMENTS OF £1 : 16 : 8 OR 18 MONTHLY PAYMENTS OF £1 : 5 : 7.

> A 12-page descriptive booklet is yours for the asking from

HERE ARE SOME OF ITS MANY FEATURES :

Two radio inputs, selected on control panel. Pre-set volume control on pick-up input. Low pass filter adjustable from 5 to 9 kc/s and OFF. 8-10 watts output. 0.12% distortion at 8 watts: Frequency response 0.25 d.b., 20-30,000 c/s. Ample spare power for feeder units.



WIRELESS WORLD

14 SOHO STREET, OXFORD STREET, LONDON, W.1 Tele: GERrard 2089. Shop Hours: 9 a.m.—5.30 p.m. Sats. 9 a.m.—1 p.m.





"TL/10" AMPLIFIER and "POINT ONE" PRE-AMPLIFIER SENT FOR This 10-watt amplifier maintains, in every respect, the world-renowned LEAK reputation for precision engineering, fine appearance, and fastidious wiring. The Pre-amplifier will operate from any well-known pick-up, whether DEPOSIT crystal, moving iron or moving coil. Provision is made for Tape Recorder and Play back and, as an exclusive feature, readily accessible jacks are provided on the front panel for instantaneous use. See maker's advt. p. 95 for full technical specification. The total Cash Price for these Two Units is £28.7.0. Our NEW EASY TERMS are £3 Deposit with order and 14 monthly instalments of 40/- (carriage and crate free).

L-R-S

The amazing New

for the Connoisseur

If you require FINEST QUALITY REPRODUCTION together with WORKMANSHIP of the HIGHEST ORDER your choice



THE VERY LATEST

LEAK DYNAMIC PICK-UP complete with two detachable diamond heads and transformer is now available from stock. Cash price £20.19.9, or sent for £3 deposit and 10 monthly Payments of 40/-. Post paid

1925

TERMS

MUREX 'SINCOMAX' MAGNETS




ARE USED IN E.I.C. INSTRUMENTS

The high magnetic stability and strength of 'Sincomax' magnets makes a robust job even of a sensitive Microammeter. In this application as in many others Murex Sintered Magnets continue to give accurate and reliable service.

Photograph by courtesy of E.I.C. (Hillington) Ltd., Glasgow

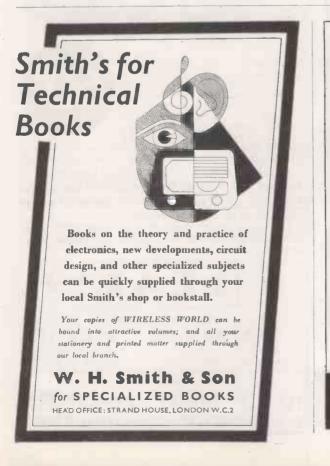MUREX LIMITED (Powder Metallurgy Division) RAINHAM • ESSEX • Rainham, Essex 3322 London Sales Office: Central House, Upper Woburn Place, W.C.I. Euston 8265





A.D. S. RELAYS LTD. Dept.W.W. 12, STORE STREET, LONDON, W.C.I. Tel.: MUSeum 2453



HARTLEY-TURNER Sound Equipment

We should like, once again, to draw attention to the Hartley-Turner Super Control Preamplifier.

This is designed to feed the output from Tape Recorders, Crystal and Magnetic Pick-ups and Radio Tuning Units to the main amplifier.

Employing sub-miniature valves and highest quality components throughout, this unit combines efficiency with simplicity of operation, reliability and compactness.



Brief Specification :

4 switched input channels. Input sensitivity: 1V positions 1 and 2; 25 mV positions 3 and 4, for 1V R.M.S. output. Cathode follower output stage. Separate continuously variable Bass and Treble controls: Bass variable 0db to +25db at 40 c/s: Treble variable -10db to +10db at 10 Kc/s.

Power required: 250V DC 3mA 6.3V 0.9A

Whole unit completely screened and enclosed in case $10\frac{5}{8} \times 3\frac{1}{8} \times 3\frac{1}{8}$ in.

PRICE: £8.18.6

Full particulars sent free and post free on application to:

H. A. HARTLEY CO. LTD., 152, HAMMERSMITH ROAD, HAMMERSMITH, LONDON, W.6.

Telephone : RIVerside 7387

	1		
		er.	00
RAD	10		/
KAD	EPI	10	VE
TE		1	46
	SYS	J I'	75

The Hudson range of highly efficient and economically operated two-way communication systems comprises equipment a pplicable to various requirements in all countries.

OF LONDON

LIST OF MODELS
AM/250/M 6 watt Vehicle Station, 60 to 100 Mc/s.
AM/150/M 5 watt Vehicle Station, 100 to 185 Mc/s. Single or up to 5 channels.
AM/250/F 6 watt Fixed Station, 60 to 100 Mc/s.
AM/150/F 6 watt Fixed Station, 100 to 185 Mc/s. Single or up to 10 channels.
FM.102 10 watt FM Vehicle Station, 60 to 185 Mc/s. Single or up to 4 channels via remote control.
FM.101 10 watt FM Fixed Station, 60 to 185 Mc/s. Single or up to 10 channels.
HED.113 50 watt AM or FM Fixed Station. 60 to 185 Mc/s. Up to 4 channels via remote control.
Supplied to the G.P.O. and Home Office.
THERE ON ELECTRONIC

Consult

HUDSON ELECTRONIC DEVICES, LTD. APPACH ROAD, LONDON, S.W.2 Telephone: TULse Hill 4861

Cables : HUDELECT, LONDON

FEBRUARY, 1955



RO

RADIO EXPORT

TUBES

1,000 types of Receiving and Transmitting Radio Tubes available ex stock.

HALL ELECTRIC LTD Haltron House, 49-55 Lisson Grove, London, N.W.1.

Tel.: Ambassador 1041 (5 lines) Cables: Hallectric, London

SOMERFORD TRANSFORMERS AND CHOKES



MODERN ELECTRICS LTD Tel.: TEMple Bar 7587.

164 Charing Cross Road London WC2

104 Charing Ch	ross Rodd, London, w.C.Z.	Cables: Modcharex, London.
Export enquiries welcomed.	Immediate delivery from stock.	Prompt attention to post orders.
TAPE RECORDERS	RECORD REPRODUCING TEST EQUIPMENT	MICROPHONES
GRUNDIG 819	Model 2000	ACOS Mic 22 (Crystal)
WEARITE TAPE DECKS Type A and B RECORDING TAPES	RCBOM A.C. £19 6 7 Valve Characteristic RCBOM A.C./D.C. £28 0 6 Meter (New Type) £60 0 301 Transcrip	0 LUSTRAPHONE M/C with T/F C51 £5 15 6 Table base for above £1 1 0
GRUNDIG L.G.S. 1,200ft £2 0 0 850ft £1 14 0		RESLOM/C (Low Imp.) 20 0
600/t £1 5 0 FERROVOICE 1,200/t. £1 2 6	3-spd	0 FILM INDUSTRIES 0 Ribbon £10 0 0 0 MICROPHONE STANDS
Spare Spools 4 E.M.I. type 88, 1,200ft. £1 E.M.I. type 88, 600ft £1	W.B. STENTORIAN COSSOR HF.610 £2 10 6 HF.810 £3 0 6 Oscilloscope 1035 £104 0 MF.912 £3 7 0	Floor, 3 extensions £3 12 6 0 Table Stand £1 5 0
GEVAERT 1,200fc £1 15 0 SCOTCH BOY	HF.912	0 LEAK AMPLIFIERS TL.10 complete
1,200ft. £1 15 0 600ft. £1 1 0 Spare Spools, 1,200ft. 4 6 Spare Spools, 600ft 3 6	Axiom IS0 Mk. II £10 5 6 PICK-UPS Axiom I02 £9 18 2 ACOS H G 20	SOLON. New instru-
FERROGRAPH 42 5 0 1,200fc. 43 3 0 1,750ft. 43 3 0 8‡in. Spools 9 6	WHARFEDALE X.M.S. Magnetic	5 ment Iron 200-250 v. 25 w
AGFA 1,200ft	Bronze 10in £4 12 9 Type O or P £3 14 Bronze 8in £3 4 0 LEAK	⁸ HEADS, SAPPHIRE and DIAMOND STYLI for the above HEADS NOW

Transformers

Transformers

Transformers

OUALITY-RELIABILITY

For the Mullard Amplifier. For the Osram 912 Amplifier. For the Williamson Amplifier. C. R. Tube Isolation Transformers. Instrument Transformers. and all popular types.

FROM



-SUPERIOR RADIO SUPPLIES-**!!!CONSTRUCTORS!!! OBTAIN "SUPERIOR RESULTS"** WITH THESE RECEIVERS

THE SUPERIOR T.R.F. RECEIVER (BUILDING COST 27/5/-). Suitable for A.C. Mains 220/240 volts. Mcdlum and Long Wavebands. Very attractive valuat venered cabinet finished in two contrasting colours. All brand new components, available individually for the construction of this fine receiver. Valve line-up: 68G7, 68G7, 64W64, 65G2. Complete construction bookket for the SUPERIOR T.R.F. RECEIVER with theoretical and practical diagrams, also price list of recommended parts. Price 1/8 post free. THE SUPEREX "ATTAGER" ALL DRY PORTABLE (BUILDING COST 27/15/-). A really superb 4 VALVE SUPERHET receiver, giving first-class results on both Long and Mcdium Wavebands. The cabinet is very compact (Size 11)in. X §in. Source 10 box 10 colours of high quality leatherete. Weight of complete receiver less batteries 81bs. All component used are of the highest grade. 08M0R HIGH Q COLES and FRAME-AEELAL, Plessey Amplion Midget I.F.T.s. Provision is also made for 71n. X 4in. X TACHE " BOOKLET giving fall building details and practical wiring dia-grams. Price 1/8 post free.

Frame Price 1/6 post free. **THE SUPEREX UPRICHT PORTABLE (BUILDING COST \pm 7/15/-3).** Chassis assembly and components almost identical to attache model with the exception of the cabinet. This is of the upright model with large speaker aperture in the front, with dial and controls under 110-tup lid in the top of cabinet. Also covered in twin colours of leatherette. Cabinet atz: 101µ. x ± 11 µ. X ± 11 µ. See More SUPER-EX "UPRIGHT" BOOKLET, price 1/6 post free.


EA OFRIGHT BOULDEL, price [J6] post tree. Designed on

We have a large range of Badlo and Television components and special purpose valves at very competitive prices. TERMS: Cash with order or C.O.D. Extra charge for G.O.D. please add postage. (U.K. and N. Ireland only.) OPEN: 9 a.m. to 6 p.m. Monday to Saturday, 1 p.m! Thursday. PERSONAL CALLERS WELCOMED.

SUPERIOR RADIO SUPPLIES

37, Hillside, Stonebridge, London, N.W.IO. Phone: ELGar 3644.


WIRELESS WORLD

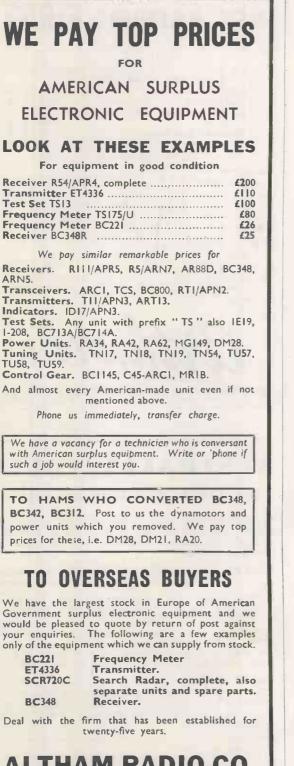





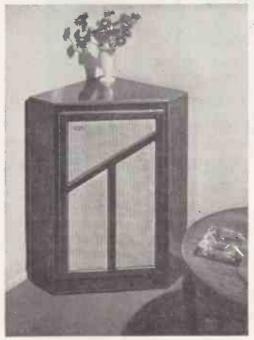Introduce A NEW HIGH FIDELITY CORNER DIFFUSION SPEAKER



Designed for small and medium sized halls and for use in homes where quality is a vital factor.

The lower registers are reproduced with exceptional smoothness assisted by the bass reflex action of the corner cabinet. The high notes are brought out with brilliant clarity from the specially designed acoustic system.

The overall effect of this construction is to give life and extra-ordinary depth to the sound which thereby approaches a three dimensional quality and truly justifies the term "high fidelity." The technical excellence of this instrument is matched by its artistic conception as a piece of stylish furniture finished in walnut veneers.

Maximum handling capacity	12 watts
Speaker flux density	10,000 line
Impedance	15 ohms
Height	32 inches
Maximum width	27 inches
Maximum depth	18 inches
Net weight	54 Ibs.

PRICE:

CABINET Only (Pats, applied for)...... £26 8 6 SPECIAL SPEAKER TO MATCH £3 0 0 Plus Purchase Tax on Speaker..... £1 0 6 TRUVOX LIMITED HARROW MIDDLESEX




A

-

FEBRUARY, 1955

LOCKWOOD Standard Loudspeaker Cabinet

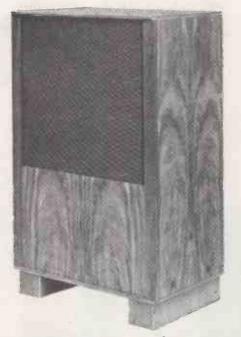

This new 'LOCKWOOD' model has been manufactured to meet the demand for a cabinet of high quality, and in conjunction with various loudspeaker units and high fidelity apparatus is capable of giving reproduction of a very high order.

*A vented design developed from the Monitoring Loudspeaker Cabinet used by The British Broadcasting Corporation (BBC. PAT. 696,671), this enclosure is, we believe, the sensible approach to the problem of providing good quality in the home at a reasonable price.

The combination of good materials and first-class workmanship is incorporated in a functional design, and this cabinet is acceptable in most furnishing schemes. It can be manufactured in exotic vencers additional to the almost traditional Oak, Mahogany or Walnut, or alternatively in coloured finishes, suitable for Broadcasting and Television Studios.



A brochure, free on request, fully explains these new models and why they are supplied ready to assemble.

EXPORT & TROPICAL MODELS AVAILABLE.

Trade enquiries invited.

DEMONSTRATIONS BY APPOINTMENT ONLY.

* "Wireless World," November & December, 1950.



Acoustically Designed Cabinets

LOCKWOOD & Co = LOWLANDS ROAD HARROW = MIDDLESEX

A	
	IURS FIRST
ASK AKIT	IUKS FINJI
NEW VALVES	and your enquiries for all Radio and Electrical ods, especially those in short supply.
	he largest variety of valves in
	know your requirements.
AVO METERS IN	STOCK
	£19 10 0
Avo Model 8 Signal Generator, M	Lains and Battery
Models	
Electronic Test Meter	£40 0 0
Valve Characteristics	Meter £60 0 0
Also full range TAYLO	R METERS. List on request.
A A A A A A A A A A A A A A A A A A A	Leak TL/10 Amplifier and
VALVE MANUALS	"Point One "Preampli-
5 0 1	fier complete
Osram 5 0	Leak Tuning Unit 635 6 3
Brimar No. 5 5 0	Grundig Tape Re-
Mazda, Part 2 2 0 Mullard Valve	corder £68 5 0
Replacement 2 6	Grundig Microphone £6 6 0
Cuide	Recording Tapes:
Art and Science in Sound Reproduc-	All makes in stock.
	Terms: C.O.D. or Cash with order.
tion by Brittain, D.F.H 2 6	Goods offered subject to being unsold
Postage 6d. each extra.	and to price alteration.

Cathard EST.

GRAY HOUSE, 150-152 CHARING CROSS ROAD, LONDON, W.C.2 TEMple Bar 5833/4 and 4765. Cables : TELEGRAY, LONDON

AUSTRALIA CALLS

TELECOMMUNICATION ENGINEERS

Rapidly developing, Australia urgently needs professionally qualified Engineers to assist in the expansion and maintenance of its national telephone, telegraph, radio and television services.

SALARY: From £890(A) to £1,262(A) per annum, depending on qualifications and experience.

CONDITIONS OF APPOINTMENT: Permanent appointment to the Postmaster-General's Department. Free passages for appointee and dependents. Initial accommodation provided. In approved circumstances, special settling-in allowances. Full salary from date of embarkation. Superannuation, generous annual and sick leave conditions. Good opportunity for advancement.

FOR FURTHER DETAILS: Engineers qualified or about to qualify electrical, mechanical and other sections enquire or forward the following coupon to the Australian Post Office Representative, Australia House, Strand, London, W.C.2.

Dear Sir, Please send full details of the opportunity for Telecommunication Engineers in the Australian Post Office.
Name
Address

HE SCIEN BRITISH	MADE	A NEW directly radio	, ho	ateo	l va	ives	10		
TYPE DESCRIP	TION U.S. EQUIV-	FILAMENT Volts Ma	Anode Volts	Screen Volts	Grid Volts	Anode Ma	Screen Ma	Mutual Conductance	Fower Output

			Volts	Ma.			Voits	1-14	1-12		Output
XFRI*	R.F. Amplifier	IAD4*	1.25	100	45	45	0	3.0	0.9	2 mA/V	
XFR2*	R.F. Amplifier	5678*	1.25	50	67.5	67.5	0	1.8	0.5	I.I mA/V	
XFR3	H.F. Triode	5676	1.25	120	135		— 5	4.0		1.65 mA/V	
XFY14	Output Pentode	5672	1.25	50	67.5	67.5	- 6.5	3.1	0.95	0.65 mA/V	50 m₩†

* Fully screened with metallized coating. \dagger With input signal 4.55 V. A.C. and anode load 20 k Ω .



STONEFIELD WAY, VICTORIA ROAD, RUISLIP, MIDDLESEX

Telephone: Ruislip 3366

10

You can count on these for a reliable performance

STAND-OFF INSULA-TORS, Working voltage 1,500/5,000. Very high insulating resistance. Ceramic non-tracking. Silicone treated to repel moisture (ideal for tropics). Tag or spill end. We have a full range to cover most needs.

S.L.8 SPIN WHEEL DRIVE. A precision slide rule drive complete with 3 band glass scale. The spin wheel drive gives perfect control through ratio 24 : 1. Fitted with constant velocity coupling, eliminating strain on condenser and providing mechanical and electrical isolation from vibration and noise.

M.G. GANG CON-DENSER. Available as 1. 2 or 3 gang, 490 p.F. nominal capacity matched and standardised to close limite. Codmium closed and standardised to close limits. Cadmium plated steel frame. Aluminium Vanes. Low loss non-hygroscopic insulation. Length excluding spindle: 1 gang-1 fsin. to 3 gang -3 kin. Price 1 gang, 9/3. 2 gang, 14/- 3 gang, 18/3.

Write for full details of the complete range of precisionbuilt components for Radio and Television industry.

JACKSON BROS. (London) LTD., KINGSWAY · WADDON · SURREY Telephone : CROydon 2754-5. Telegrams : WALFILCO, SOUPHONE, LONDON.


FEBRUARY, 1955



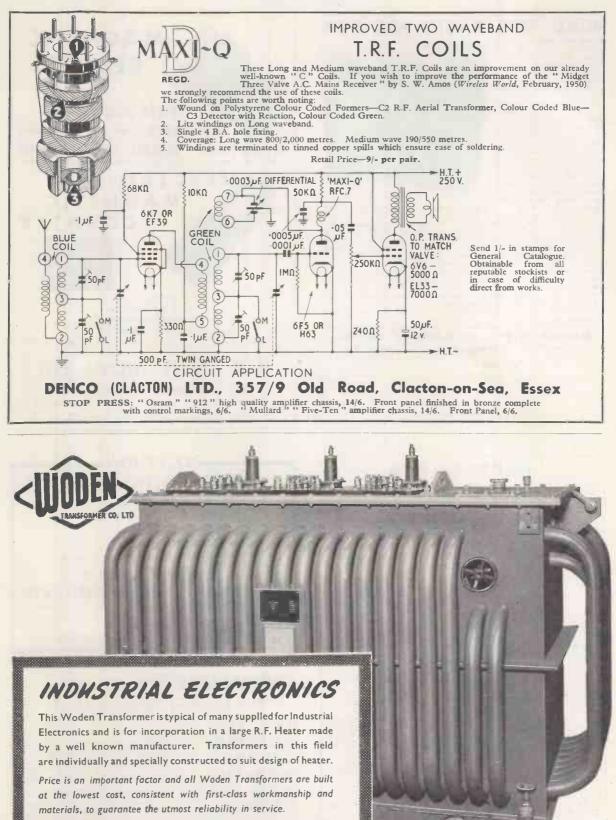A. B. PARKER WHEATCBOFT WOBKS, WELLINGTON STREET, BATLEY, YORKSHIRE. Tel.: Bailey 426







WODEN TRANSFORMER CO. LTD.

MOXLEY RD., BILSTON, STAFFS. Bilston 41959

118

FEBRUARY, 1955



WIRELESS WORLD



120

WIRELESS WORLD

FEBRUARY, 1955



SPECIAL OFFER :

200 kc. DT cut, zero temperature co-efficient over the range-30° centigrade to $\pm 55^\circ$ centigrade. Frequency adjustment .005% or better. Mode: Face shear. Sliver-plated electrodes, wire mounted. Basing in. pin spaced. Other bases to order, £1 each.

GOODS OF QUALITY PROMPT DESPATCH

WIRFIESS WORLD



WAX TUBULAR CONDENSERS WITH WIRE ENDS .001 mfd. 350 v. 5d. each or 4/6 doz. .002 mfd. 400 v. 5d. each or 4/6 doz. .002 mfd. 1,000 v. 9d, each. 002 mfd. 1,000 v. 9d. each. 005 mfd. 600 v. 9d. each. 01 mfd. 500 v. 5d. each. 02 mfd. 1,000 v. 7d. each. 035 mfd. 500 v. 5d. each or 4/6 doz. 05 mfd. 350 v. 9d. each. 1 mfd. 500 v. 6d. each. 1 mfd. 500 v. 6d. each. 3 mfd. 500 v. 5d. each or 4/6 doz. VARIABLE CONDENSERS ang Midget with dust cover .00035 mid, with trimmers . . 8/6 ca. 2 TINNED COPPER WIRE-All 4 oz.
 Reel%.

 16 8. W.G.

 18 8. W.G.

 20 8. W.G.

 22 8. W.G.

 22 8. W.G.

 24 8. W.G.

 26 8. W.G.
 2/8 2/10 ENAMELLED COPPER WIRE-All Reels Price 8.W.G. 8.W.G. Price 30 32 34 36 38.... 3/1 3/3 3/5 3/7 3/1 16 18 20 22 24 3/11 4/2 40 **CHASSIS** Aluminium Undrilled with Reinforced Corners. Available in the following sizes.
 Sizes.
 Sizes.

 Øin.x4in.x2in.
 4/6 ea.

 8in.x7in.x2in.
 6/3 ea.

 10in.x7in.x2in.
 7/3 ea.

 12in.x8in.x2in.
 8/6 ea.

 14in.x8in.x2in.
 9/6 ea.

 16in.x7in.x2in.
 12/9 ea.

 16in.x9in.x2in.
 12/9 ea.

 16in.x9in.x2in.
 12/9 ea.

 All are four sided—Ideal for rudio receivers—amplifiers—powerpacks etc.
 12/9 ea.
 PERSPEX IMPLOSION GUARDS Incorporating escutcheon and filter. 12in. type 11/6 ca. 16in. type 14/6 ca. POCKET TEST METER Ex. Govt. volt meter, two ranges 0-15 v.; 0-250 v. D.C. complete in case 17/6 each. NYLON CORD 25 yd. reels Nylon drive cord on wooden reel 2/9 each. WE INVITE YOU TO BUILD THIS PORTABLE FOR ONLY THIS PORTABLE FOR ONLY Gł gns. Full details, circuit diagram, point to point wiring instructions, and compited list of components. Avail-able 2/- ea. Case can be supplied separately. Available in the following attractive colours: • Lizard Grey; • Blue; • Marcon; • Brown. Dial, 1/3 each. Chassis, 3/-.

2X2

5Z3

6B4

6ST7



VIBRATORS ETC. Vibrator unit for 6 v. operation 14/6 ea. Post 1/6. 6 v. and 12 v. Vibrators, 4 pin UX types, 6/6 each.

TERMS : Cash with order or C.O.D. Postage to

SPECIAL PURPOSE ALPHA VALVES VR65 VR65A VR66 IASGT ... 5-6 807 716 956 3/6 CV173..... 10/-CV286..... 7/6 3/6 9001 56 6/9 9002 EI148 8/6 9003 5/6 21 VR9I 5Z3 6B4 6G6G VR53 VR54 VR55 6/6 VR9I(SYL) 9004 5/6 6/-6/6 7/6 9006 954 6/--2/-7/6 VR92 VR105/30 VR55 VR56 VR137 (139) VRII9 954 VRI36 4/--71-**VR116** VR119 ... VT52 ... VU111 ... VR150/30 6/--TTU VUI20A 916 31. 8/6 **VU64** Full List Avail-8/-955 4/9 8/-866A 77 8/--65A7 10/-able. LOUDSPEAKER UNITS HEADPHONES-MICROPHONES, Etc. $\label{eq:constraints} \begin{array}{c} \textbf{LOUDSPEAKER UNITS}\\ Rola 50 in speaker with trans... 16/-ea.\\ Plessey 6j h. lightweight unit 16/6 ea.\\ Rola 6j in. standard type... 17/6 ea.\\ Rola 6j in. with trans... 18/-ea.\\ Truvox 6j in. with trans... 18/-ea.\\ Plessey 8in. Rightweight unit... 17/6 ea.\\ R. & A. Sin. standard type... 17 6 ea.\\ Plessey 10 in. unit ... 19.6 ea.\\ Elas 10 in. unit ... 22/6 ea.\\ Goodmans 10 in. unit ... 12/6 ea.\\ Elliptical 4in. × 71n. unit ... 18/6 ea.\\ Mains Energised 8in. unit ... 10/6 ea.\\ Rod mains 20/6 ea.\\ Mains Energised 8in. unit ... 10/6 ea.\\ Rod mains Energised 8in. unit ... 10/6 ea.\\ Rod mains Energised 8in. unit ... 10/6 ea.\\ Rod Mains Energised 8in. 0.000 0.\\ Rod Mai$ American phones by Trimm Mfg. Co. of Chicago, U.S.A., 1,200 ohms, each 13/9 pr. earpiece Headbands, wide type Throat microphones, American surplus, 1/9 ea.

 Throat microphones, American surplus, Complete with strap, lead and plug type T308
 4/- set

 "Regent" Hand Microphone. Crystal insert, nickel chrome plated head, complete with lead and jack plug, listed at 2 Gns. Our price
 4/- set

 Throat Microphones, type Za.21095.
 21/- ea.

 2 units per box
 1/8 per box

 600 Q HEATER TRANSFORMERS 230 v. Input 2 volt .5 amp. 230 v. Input 2 volt 3.0 amp. 4/6 7/9 5/-10/-Morphy Richards replacement 230 v. Input 4 volt 1.5 amp. 230 v. Input 4 volt 3.0 amp. 230 v. Input 5 volt 2.0 amp. 10/-PLIERS With side cutters 230 v. Input 6.3 volt .5 amp. 230 v. Input 6.3 volt .5 amp. 230 v. Input 6.3 volt 1.5 amp. 230 v. Input 6.3 volt 3.0 amp. 230 v. Input 12 volt .75 amp. 51-91-PRESET CONTROLS (CARBON)

 1 pole 9 way

 4 pole 2 way

 4 pole 3 way

 3 pole 3 way

 3 pole 3 way

 50 K Ω ; $\frac{1}{2}$ meg Ω ; 1 meg Ω ; 2 meg Ω ; 1/9 each. HUNTS CONDENSERS (Screened) . RESISTORS 2 WATT NITROGOL CONDENSERS OSMOR COIL PACKS SPRAGUE CONDENSERS **RESISTORS**—Brand new. A good selection from 10Ω to 15 meg. Ω . All popular sizes. 20/-MAINS TRANSFORMERS Input 200/250 volts. Output 325-0-325 v. 20 mA 6.3 v. 3a. 12/- ea. 20 amp 2 pole Diamond switch, 4/6. WIRE WOUND RESISTORS

WIRELESS WORLD

. 17/6 ca CRYSTAL DIODES CONDENSERS Waxed cartons with flying leads, 4 mfd. 500 V. 1/8 ea. 4×4 mfd. 500 V. 3/4 each. Plastic case, wire ends, 2 for 2/1. 3/4 each. IRON ELEMENTS Standard adaptable type 230 V. 1/8 ea. AF 4/3 pr. DOUBLE TRIMMERS 250/250 pf.; 100/100; 100/50. All 6d. ea. Ĩ. YAXLEY SWITCHES 1/6 ea. 1/9 ea. 2/6 ea. 1/6 ea. OCTAL PLUG AND SOCKET ·· 1/- es. HIGH VOLTAGE HIGH VOLTAGE E.H.T. CONDENSERS .002 mfd. 18 kV. .001 mfd. 6 kV. 500 pf. 10 kV. 7/6 ca. 5/- ca. 5/- ca. CONNOISSEUR PICK-UP BEEE Standard model, magnetic typ complete with matching transform Listed at £4/10/5. Our P.ice 29/6. type. Box of 4 BA. nuts and shakeproof washers and bolts mixed, countersunk and round head, over 100 items, 1/- box. and round head, over 100 items, $|I_{-}$ box. 2 meg. Amplion vol. controls, double pole switch, 2/6 each. 100 K $\Omega_{1}^{*} \pm meg \Omega_{1}^{*} \pm meg \Omega_{2}^{*}$ single pole switch 2/e cach. RECORDING TAPE 1,200 feet tape on Cyldon reel. (Brown plastic type.) 18/6 reel. INTERNATIONAL OCTAL VALVE HOLDERS Paxolin 4d. each. Amphenol 6d. each. Ceramic 1/- each. WIRE WOUND RESISTORS Available in the following values:--25Ω, 50Ω, 100Ω, 150Ω, 200Ω, 250Ω, 350Ω, 500Ω, 1,000Ω, 1,50Ω, 2,003Ω, 2,501Ω, 3,500Ω, 5,000Ω, 6,680Ω, 10,000Ω. Tolerance plus or minus 10 per cent. Ratings 5 wait, 1/e ea; 10 wait, 1/3 ea; 15 wait, 1/9 ea. FILAMENT TRANSFORMERS Primary 200/250 v. Secondary 6.3 v. 1.5 amps, tapped at 4 v. and 2 v., 7/6

Mallory .1 mfd. 600 v. condensors, 1/-

Pentode Output Transformer, 2/9 ea

FEBRUARY, 1955

PORTABLE RECORDING OR PROJECTOR CASES Revine covered. (Ready for carry) 15in. z 94in. x 13in.). Internal dim sions, 14in. long, 11in. deep. 64 front. height, 9jin. rear height. Weig 8jib. Price 13 6 cach. Postage and Facking 2/icep, Dynamics, Weight

3/9

3/6 3/9

6/-8/-2/-

41-

6

Fostage and Fashing 2/-. MAINS DROPPERS Dubilier type HY71223, 1,350 Ω with 5 taps, 2/6 ea. 945 Ω Dropper with 5 taps, 2/6 ea. Vibrator elips, 4d, ea.

POCKET TEST METER. Ex-Govt. volt meter, two ranges, 0.15 volts, 0-250 volts, D.C., 17/6 cach.

volts, D.C., 17/6 each. TELEVISION PEE-AMPLIFIER, by Plessey, complete with valve (EF42), as small compact modern unit for London frequency. Price 13/6. " COMPACT "TELEVISION AERIAL for indoor use London frequency, sup-plied complete with universal mounting backplate in neutral brown finish. Complete with full instructions. Cat. No. CD4. Original price, 50/-. Our price 12/6 ea. No. CD4. O price 12/6 ea.

METAL RECTIFIERS FOR CHARGERS 12 v. i a. 1/6; 12 v. 1 a. 4/9; 2 v. 1 a., 3/3; 12 v. 2 a., 10/6; 12 v. 3 a., 13/3; 12 v. 5 a., 18/6.

MOULDED MIGA CONDENSERS All wire ends. .0001, .0003, 0004. .0005, .01, .001, .005, .00027, .0008, .00005, .003, 4/6 doz.

BULGIN PORCELAIN STAND-OFF INSULATOR

3-hole fixing, wingnut type, 1/- each. 3-noie nxing, wingnut type, 1/2 excit. METAL CASE-AMPLIFIER OR BATTERY CHARGER CABINET. Fin-ished brown crackle. Removable base or chassis. Vent holes. Supplied with bakelite side panel. Size 9½in.x 6½in.x 7½in. Price 8/6 ca.

	_	-	_	_
CONDI		PS		
he following is			01 1	111
ne tonowing is	ifactu	rors'	UTD	1118
ocks of many	well k	nown I	nake	18
LUMINIUM CA	LN 1	ALES	, UI	11
IXING			A.F.	
× 8 mid. 480 v			4/- 4/-	00
$\begin{array}{c} \times 8 \text{ mfd. } 450 \text{ v.} \\ \times 16 \text{ mfd. } 450 \text{ v.} \\ \times 24 \text{ mfd. } 350 \text{ v.} \\ \times 32 \text{ mfd. } 475 \text{ v.} \\ 2 \times 4 \text{ mfd. } 450 \text{ v.} \\ 6 \text{ mfd. } 450 \text{ v.} \end{array}$			3/-	0.0
× 29 mfd 475 v			3/9	63.
2 x 4 mfd 450 v.				
6 mfd. 450 v.			3/-	ea.
6×8 mfd. 350 v.			4/-	ea.
6 × 16 m(d. 350 v			3/3	ea.
8×16×8 mfd. 33	50 v.		3/6	ea.
0 x 20 mfd. 500 v			4'9	ea.
4 mfd. 450 v			2/9	ea.
4 x 16 m/d. 350 v			3/6	ea.
2 mfd. 450 v			3/-	ea.
2 x 8 mfd. 350 v.			3/6	ea.
2 × 16 mfd, 350 v	• • •		4/6	ea.
2×4 mfd. 450 v. 6 mfd. 450 v. 8 $\times 16$ mfd. 350 v. 8 $\times 16$ mfd. 350 v. 8 $\times 16 \times 8$ mfd. 350 v. 9 $\times 16 \times 8$ mfd. 350 v. 4 $\times 16$ mfd. 360 v. 2 mfd. 450 v. 2 $\times 16$ mfd. 350 v. 2 $\times 16$ mfd. 350 v. 2 $\times 216$ mfd. 350 v. 2 $\times 32$ mfd. 450 v. 2 $\times 32 \times 8$ mfd. 350 v. 3 $\times 32 \times 8 \times 8$ mfd. 350 v. 3 $\times 32 \times 8 \times 8$ mfd. 350 v. 3 $\times 32 \times 8 \times 8$ mfd. 350 v. 3 $\times 32 \times 8 \times 8$ mfd. 350 v. 3 $\times 32 \times 8 \times 8$ mfd. 350 v. 3 $\times 32 \times 8 \times 8$ mfd. 350 v. 3 $\times 32 \times 8 \times 8 \times 8$ mfd. 350 v. 3 $\times 32 \times 8 \times $		6	111	ea.
2 X 52 X 8 Inid. 3	- 95	nofd.	010	ca.
95 W	1. 20	mau.	5/9	
2 × 32 × 8 mfd. 3. 2 × 32 mfd. 350 v 25 v. 0 mfd. 450 v. 4 mfd. 350 v.			2/9	
4 mfd. 350 v			21-	ea.
			~1	
R. RANGE	00 -		0/0	07
10. R. 690, 8 mld. 6	500 %.		2/9	02
LR 2050 20 ml	4 500	¥	3/3 3'6	0.0.
 K.KANGE R.A50, 8 mfd. 2 R.1650, 16 mfd. R.2050, 20 mfd. R.2050, 20 mfd. S.R.501 50 mfd. 6 × 16 mfd. 500 v. 6 × 8 mfd. 500 v. 	4 000	*	41.	P.B.
R.501 50 mfd.	12 7		4'- 1/9 5/- 4/9	(23.
6×16 mfd. 500	V.		5/-	ea.
6 x 8 mfd. 500 v			4/9	ea.
	TALE	5	1/0	0.0
mid, 350 V		****	1/9	Cil.
× 8 mfd 250 -			3/-	08.
×8 mfd 450 v.			1/1 3/- 4/-	28.
6 mfd. 350 v			2/9	ea.
6×8 mfd. 450 v.			4/-	ea.
6 × 16 mfd. 450 v	7		4/6	ea.]
6×24 mfd. 350 v	<i>.</i>		4.9	ea.
4 mfd. 350 v.			2/9	ca.
2 mfd. 350 v.			19	ea.
2 × 32 mfd. 350	· · ·		4/9	ea.
50 mfd. 12 v.			1/9	68.
VIRE ENDED T	PES			
8 mfd. 450 v. covered 10 mfd. 450 v.	cardl	board		
covered		1	/11	ea.
10 mfd, 450 v.			3/9	ea.
BIAS CONDENSE	De		5,0	-
Internet and an and				
2 mid 50 v	ypes		1/-	63
25 mfd 25 s			1/3	P3.
i0 mfd. 12 v.			1/-	ea.
i0 m(d. 50 v.			1/-2/8	63.
00 mfd. 12 y			1/9	ea.
12 mid. 50 v. 12 mid. 25 v. 50 mid. 25 v. 50 mid. 12 v. 50 mid. 12 v. 100 mid. 12 v. 100 mid. 25 v.			1/9	ea.
VIRE ENDED T	DEC	ARD		
OVERED	res	UNEDI	DUA	RD.
5 mid 01 m			1/9	0.0
0 mid 19 v			1/9	ca.
5 mfd. 23 v 0 mfd. 12 v 0 mfd. 50 v.			2/3	P.S.
······································			010	
	_	-	-	-

2.2 K Ω ; 470 Ω ; 7.5 K Ω ; 22 Ω ; 150 Ω ; 5.6 Ω K; 390 Ω ; 150 K Ω ; $\frac{1}{2}$ meg Ω ; 39 Ω ; 1.5 meg Ω ; 56 K Ω ; all 4d. each. BAKELITE CASED CONDENSERS .1 mfd. 1000 V.; .03 mfd. 4 kV.; .01 mfd. 4 kV.; .03 mfd. 500 V.; .001 mfd. 4 kV. All I/6 each. 12 mfd. 350 V. 5/6 ea. Type H.O. 48/- each. Type LM 40/- each. Type T.B. 50/- each. Type TRF 40/- each.

-05 mfd. 500 V.; .01 mfd. 1000 V.; .1 mfd. 350 V.; -02 mfd. 750 V. All 9/- doz.

per 100.

be added to orders as follows : 9d. up to 10/-; 1/up to 20/-; 1/6 up to 40/-; 2/- up to £5. MAIL ORDER ONLY. Send 6d. in stamps for illustrated Catalogue.



WIRELESS WORLD



Phone: CENtral 5812-3-4

109 and 115 FLEET STREET, LONDON, E.C.4



WIRELESS WORLD



FEBRUARY, 1955







11 in. × 4 in. × 3 in. A design of a complete S-VALVE SUPPRHET RECRIVER em-ploying an R.F. Stage, and incorporating a separate VIBRATOR PACK size 4 x 2 i incorporating a separate VIBRATOR PACK size 4 x 2 i K 6 in. for use on 5 or 12 volt D.C. supplies. We can supply all components to build this complete Receiver and Vibrator Pack We can supply all components to build this complete Receiver and Vibrator Pack We can supply all components to build this complete Receiver and Vibrator Pack (Carr. and In. s 5 is extra.) Or the Receiver Components for £9/19/6 and the Vibrator

Components for EX10.7. Or the accerter components for 2x/18/6 and the violation Components for EX10.7. Receiver, it is a new design employing new Components. Send 2/8 for the compiler set of ASEMBLY INSTRUCTIONS, CIRCUITS and PRACTICAL LAYOUTS, including a complete individual Component Price List.

A BULK PURCHASE ENABLES THIS SPECIAL PRICE REDUCTION OF THE FAMOUS SHAFTESBURY PORTABLE AMPLIFIER

TESBUR


Suitable for home use and small Halls. Has matched inputs for both Record Players and Microphone. Also provides for the "mixing" and "fading " of both Gram. and speech as requested.

COMPRISING

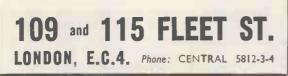- (a) A 4-Yalve High Gain Amplifier for use on A.C. or D.C. mains 200-250 volts with 5 wats output. Incorporating independent Volume Controls for Mike and Gram, either of which can be faded at will, a variable Tone Control and independent input sockets for Mike and Gram.
 (b) A Transverse Carbon microphone which obtains its polarizing current from the amplifier-mo batteries are necessary.
 (c) An Sin. Goodmans P.M. Speaker with the "Ticonal" magnet for first-class reproduction.
- reproduction

THE COMPLETE EQUIPMENT is all contained in the PORTABLE CARRYING CASE £18'0

Having been reduced from £30/9/-. HIRE PURCHASE TERMS. DEPOSIT £4/10/-and 12 monthly payments of £1/5/4 • Light in weight • Easy to OARRY • GENU-INELY PORTABLE. An illustrated leaffet containing free data is available on receipt of 8.A.E.





THE "MINI TWO-THREE"


An "Alldry" Battery Portable of midget size, 64in.×44in.×34in. designed to cover medium wave-band 190-559 metres, with use of short trailer aerial.

The simple design of this Receiver is so arranged that either a 3-valve set or a 2-valve (afterwards easily converted to the 3-valve) can be ade

made. Consists of a T.R.F. circuit using a regenerative detector with H.F. stage and a high gain output pentode. Valve line up IT4-

! CONSTRUCTORS!! A NEW SUPERHET TRANSPORTABLE THE "SUPER THREE"

For use on A.C. Mains 200-2500 volts.
This set includes a Mains Transformer and Chassis is NOT live to mains former and Chassis is NOT live to mains former and consequently the Receiver can safely be used in the Kitchen, etc.
Valve line up 6K8--6J7--KT61, plus Metal Rectifier.
The I.F. Transformer is supplied " pre-aligned ": and thereby ensures extreme simplicity of Tuning-In fact, more simple than most T.R.F. Receivers.
Compact and easy to build simple " point to point " practical diagrams are supplied with a completely drilled chasis.
The omplete Receiver Chassis can be built to cover the Medium Waveband only for
Set to the state the two additional matrix is a state of the state of th

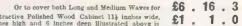

The attractive Pollshed Wood Cabinet 114 inches wide, **£1 . 1 . 0** 84 inches high and 6 inches deep illustrated above is **£1 . 1 . 0** The CONSTRUCTOR'S MANUAL is available ior 1/-, this shows the component prices, which are all available for separate purchase.

A DUAL-CHANNEL PRE-AMPLIFIER and TONE CONTROL UNIT

Attractively finished in "Old Gold" and providing full control of BASS and TREBLE in conjunction with a main volume control. It can be used with any amplifier and with any plok-up, the range of frequency control provided by the unit affording ample compensation for all types of plok-ups and all natures of recordings, i.e., English, American and long-playing. without recourse to plok-up correction. The extreme flexibility of the bass and threble control is such that the level of bass and fibble can be set to suit any conditions irrespective of the volume output of the measurement of the bass and are given in maintee and prover supply and can be accommodated either on of away from the scham lastined power supply and can be of a cabine or any other position. Frie including drilled chasts, values (68NT and US), g3/16/9. Complete assembly data are available separately for L. Completely assembled and ready for use, g5/5/-





A design of a simple 1-valve 2-stage Battery Receiver, giving excellent results on medium and long wavebands and having exceptionally low battery consumption. Drilled chassis and practical diagrams make it the ideal set for the beginner to build.

The complete chasis, including valve, can be built for 37/6, plus 8/11 P/Tax, the attractive plastic case is 9/6, and suitable headphones, 14/9. The complete assembly instructions, I ayout an '! a com-ponent price list are available for 1/6.





128



MAINS DROPPERS. 3in. × 14in. Adl. 314ders. .3 amp. 750 ohm:, 4/9. .2 amp., 1,000 ohms, 4/3.

WIRELESS WORLD

FEBRUARY, 1955

ELECTROLYTH	CS ALL	TYPES NEW STOC	K.
Tubular Wire ends		50/25 v.	1/9
8+16/500 v.	5/6	50/50 v.	2/-
16+16/500 v.	6/-	Can Types, Clips,	
1/275 v.	21-	32+32/350 v.	4/6
2/450 v.	2/3	32+32/275 v.	4/6
4/350 v.	1/6	16/450 v.	3/6
4/500 v.	2/-	32/350 v.	4/-
8/450 v.	2/3	60/350 v.	6/6
8/500 v.			8/6
	2/9	250/350 v.	
10/500 v.	2/6	8+16/450 ▼ .	5/-
16/500 v.	4/-	8+16/500 v.	5/6
8+8/500 v.	4/8	16+16/450 v.	5/6
32/350 v.	4/-	16+16/500 v.	6/-
32/500 v.	5/-	16 + 32/350 v.	4/6
			6/6
32+32/350 v.	5/6	32+32/450 v.	
32+32/500 v.	7/8	60+100/350 v.	11/6
25/25 v.	1/9	100+200/275 v.	12/6

POINTER KNOBS .- Brown with white marking line, small 9d., large 1/-.

PEN TORCHES.—Drydex, chromlum plated with vest pocket ellp. Complete. New battery and bulb. Listed 3/4. Our Price 2/6. HANDLITE.—Drydex, pocket or handbag fiashlight. Complete. Battery and lens bulb. Listed 3/5. Our

ALUMINIUM GHASSIS.—18 s.w.g. Plain, undrilled, folded 4 sides and riveled corners lattice fixing holes. Strong and soundly constructed with 2410, sides, 71n. × 4in., 4/6; 11in. × 71n., 6/9; 13in. × 9in., 8/6; 14in. × 11in., 10/6; sund 18in. × 18in., 16/6.

ACID HYDROMETER.-New ex-Govt. Unbreakable. Packed in metal case, 7in. x 14in. dla., 4/6.

TWIN GANG TUNING CONDENSERS....0003 mfd. midget with trimmers, 8/6; 375 pf. midget less trimmers, 6/6; .0005 Standard size with trimmers and feet, 9/-; less trimmers, 8/-; ditto, solled, 2/6.

LOUDSPEAKERS P.M. 3 OHM. 3in. Plessey, 12/6. Good mans 4in. square, 15/6. 5in. 14/6. 6in., 16/-. 7in. Elliptical 18/6. 8in. & A. 17/6. 10in. B. & A., 25/-. 6in. Plessey with trans., 7,000 ohms to 3, 19/6.

I.F. TRANSFORMERS

465 Ke/s Sing tuning Minlature Circular Can, 2jin. by 1jin. diam. Fits octal V-holder cut out. High Q and good bandwidth. By Pye Radio, Two mounting feet. BRAND NEW, 6/9 PAIR

307 WHITEHORSE RD., WEST CROYDON

OPEN ALL DAY SATURDAY.

P. & P., 6d. El orders post free. ALL MAINS TRANS.-U- extra postage. Lists 3d.

V'HOLDERS.-Pax: Int. Oct., 4d.; EF50, EA50, 6d.; B12A CBT, 1/3. Monlded: Int. Oct. 6d.; B7G, 9d.; with screening can. 1/6; B8A, B8G, B9A, 1/-; VCR97, 2/6. Ceramic: EF50, B7G, 1/-, ENG, and AMER, 5., 7. and 9-pin. etc., 1/-.

HIGH VOLTAGE VALVE CAPS. 1. Oct., 1/-,

SLOW MOTION DRIVES .- Epicyclic ratio 4:1, 2/3

EXT. L.S.-Switched Socket, on-off and paralle switching, complete with plug, 2/-.

MORE MONEY-SAVING



WIRELESS WORLD

POST

FREE

EVERY COMPONENT CAN BE SUPPLIED

SEPARATELY.

diagrams and circuits.

PRICE 6/-

FEBRUARY, 1955



ANOTHER BIG BARGAIN RADIOGRAM CHASSIS

5-valve superhet, 3 wavebands-long, medium, short. Latest type miniature valves, gram. switch, ext. speaker socket. Large full vision dial. Size $12 \times 7 \times 8in$.

LASKY'S £10.5.0

WE CAN SAVE YOU MONEY Packing and Insurance 10/- extra. -----MAGNIFICENTLY YOUR TV IN HOUSE

THE DE-LUXE

THE DE-LUXE Complete with mask, glass, castors, shelf, bearers, C.R.T. neck end protector, back, speaker fret and baffle board. Finished in beautiful figured medium, light or dark walnut veneer, with high polish. Suitable for most home constructor T.V. receivers, including the "Viewmaster," "Practical Television," "Tele-King," "Magniview," "Wireless World," etc. Can be supplied with cut-out for 14in., 16in. and 17in. C.R. tubes at no extra cost.

An allowance of 4/6 will be made if the

Inside Dimensions: Depth 164in.; width 172in; height 28in. and width 184in.

WHY NOT CONVERT YOUR TABLE RECEIVER TO A CONSOLE MODEL? Adaptor frames for fitting 9in. or 10in. C.R. tubes available if required. LASKY'S PRICE Carriage 12/6 extra.

MANUFACTURERS'

SURPLUS TV

H.P.Terms.Deposit£2/17/plus carriage. Balance plus charges spread over 12 mths.

BARGAINS

COMPONENT



MAINS TRANSFORMERS All 200-250 v. 50 c.p.s. primary. Finest quality, fully guaranteed.

MBA/3. 350-0-350 v. 80 mA. 6.3 v. 4 a., 5 v. 2 a. Both fila-ments tapped at 4 volts. An ideal replacement trans. 18/-.

MBA/6. 325-0-325 v. 100 mA. 6.3 v. 3 a., 5 v. 2 a. tapping board. Price 22/6.

MBA/7. 250-0-250 v. 80 mA. 6.3 v. 3 a., 5 v. 2 a. Both fia-ments tapped at 4 volts. 18/-.

 MBA/8.
 SPECIAL OFFER.

 Drop through type.
 235-0-235 v.

 60 mA. 6.3 v. 3 a.
 12/6.

MBA/9. 400-0-400 v. 60 mA. 6.3 v. 1 a., 4 v. 2.5 a. Price 12/6.


AT/3. Auto transformer. 0-10-120, 200-230-240 volts 100 watts. Price 17/6.


..........

OF THESE **SUPERB** CABINETS! ONE THE ROTHESAY

The last word in outstanding contemporary The last word in outstanding contemporary design. Absolutely rigid construction throughout with the finest laminated woods, veneered in walnut, polished light, medium or dark shade. Fitted with gold anodised speaker grille. The C.R.T. aperture frame is detachable, supplied to suit any size tube to order. Full length doors if required can be speplied with the cabinet. Veneered both sides, polished to march the cabinet and moured with full match the cabinet, and mounted with full length piano hinges.

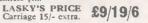NOTE THESE GENEROUS SIZES. Notice dim. 344 in. high, 21 in. wide, 214 in. deep. Inside dim. 188 in. wide, 194 in. deep. Size of top 224 in. × 21 in. Thickness in.



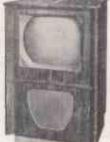

Carriage 15/- extra. (3/10/- plus H.P. TERMS. Deposit £3/10/- plus carriage charge. Balance plus charges The Rothesay cabinet with doors. Price £14/9/6. MOVING COIL MICROPHONES LESS THAN A MAR HALE USUAL PRICES

MANUFACIURERS SURPLUS	IV CUMPUNENI BARGAINS	HOME HIGH	THOMES LESS THAN
MANUFACIURERS SURPLUS WIDE ANGLE 38 mm. Line E.H.T. trans., ferrox- cube core. 9-16 kV. 25/- Scanning Coils, low imp. line and frame 25/- Frame Output Transformer 10/6 Scanning Coils low imp. line and frame 17/6 Frame blocking osc. trans- former caslam cored 4/6 Focus Magnets Ferrox Lure 25/-	IV CUMPUNENT BARBAINS STANDARD 35 mm. Line Output Transformers No. E.H.T. 12/6 Line Output Trans- formers 6-9 kV. E.H.T. and 6.3 v. winding. Ferrox-cube 19/6 Scanning coils. Low imp. line and frame, by Igranic 12/6 Scanning Coils. Low imp. line and frame, by Igranic 14/6 Line blocking oscillator trans- former 4/6 Frame blocking oscillator transformer 4/6	ELECTROLYTIC CONDENSERS ALL BRAND NEW	HALF USUAL PRICE! By well-known manufacturer. Moving coil. Switch incorporated. Low impedance. Listed at £6/6/- LASKY'S 59/6 MIKE TRANSFORMERS, 100-1 Each 1/11. C.R.T. Neck Protectors 2/6.
P.M. Focus Magnets. Iron Cored 19/6	Frame output transformer 7/6 Focus Magnets:	8 mfd. 450 v.w. 1/9 16 mfd. 350 v.w. 2/6	SPECIAL T.V. CONDENSERS
Duomag Focalisers 29/6 300 mA. Smoothing chokes 15/- Electromagnetic focus coil, with combined scan coils 25/-	Without Vernier 12/6 With Vernier 17/6 Focus Coils. Electromagnetic 12/6 200 mA. Smoothing chokes 10/6	16 mfd. 500 v.w. 3/6 20 mfd. 500 v.w. 3/6 30 mfd. 500 v.w. 3/3 60 mfd. 350 v.w. 3/3	64 mfd. 450 v.w. 3/11 100 mfd. 450 v.w. 4/11 32 + 100 mfd. 450 v.w. 7/6 100 + 200 mfd. 350 v.w. 5/11
ION TRAPS. All types, 3/ ENERGISED SPEAKERS 8in. with O/T 600 ohm field, 15/6. 8in. less O/T 600 ohm field, 12/6.	CLOSED FIELD SPEAKERS 6½in. 18/6 8in. round and 6½in. Elliptical 19/11.	64 mfd. 450 v.w. 3/11 150 mfd. 350 v.w. 3/1 150 mfd. 350 v.w. 3/6 400 mfd. 150 v.w. 3/6 8 + 8 mfd. 450 v.w. 3/6 8 + 16 mfd. 450 v.w. 3/6	DENCO F.M. FEEDER UNIT All components and valves in stock Uses 6AM6, 12AH8, EB91, and two 6AB6. THE COMPLETE
8in. less O/T 1,200 ohm field, 12/6. 61 in. with O/T 600 ohm field, 14/	P.M. LOUDSPEAKERS 23in., 16/ 5in., 18/6. 61in., 16/6.	$12 + 12 \text{ mfd. } 350 \text{ v.w.} \qquad 2/6$ $16 + 16 \text{ mfd. } 350 \text{ v.w.} \qquad 3/6$	PARCEL £6/7/6. Post extra. All components available separately.
Special Purchase!	3in., 12/6. 8in., 18/6. 10in., 19/11. Super Bargain in	$\begin{array}{rrrrrrrrrrrrrrrrrrrrrrrrrrrrrrrrrrrr$	VALVES & C.R. TUBES. Over 25,000 in stock. Mullard, Brimar, Osram, G.E.C., Ferranti, etc.
a share of the state	SPEAKER	MANY OTHER SINGLE AND MULTIPLE CONDENSERS	METROSILS, 10 Kv. 5/-
	CABINETS	HIGH VOLTAGE E.H.T. CONDENSERS	BRIMISTORS. CZ.1 1/6 each. CZ.3 6d. each.
	Attractive design finished in figured walnut veneer. Size 123 × 8 × 43 in. Will take 63 in. speaker. LASKY'S 17/11	.1 + .1 mfd. 3.5 Kv. 5/11 .1 mfd. 7 Kv. 15/- .001 mfd. 12.5 Kv. 7/6 .001 mfd. 15 Kv. 10/- .0005 mfd. 10 Kv. 3/6 .0005 mfd. 15 Kv. 6/6	OUTPUT TRANSFORMERS Midget Pentode 3/6 Miniature Personal, 3S4, etc. 3/6 3/11 Standurd pentode 3/11 Push-Pull, 6V6. 9/6 Multi Ratio, P.P. 12/6
	Post and packing 2/6 extra.	.04 mfd. 12.5 Kv 5/-	Heavy Duty, P.P 14/11

130



MORE MONEY-SAVING LASKY BARGAINS NEXT PAGE ON

WIRELESS WORLD





132

WIRELESS WORLD

SELENIUM RECTIFIERS	R.S.C. TRAN	SEORMERS
L.T. Types H.T. Type H.W. 2/6 v. ½ a.h.w 1/9 120 v. 40 mA 3/11		
6/12 v. 1 a.h.w. 2/9 250 v. 50 mA 5/9 F.W. Bridge Types 20 v. 50 mA 5/9	FULLY GUARANTEED, INTERI	
6/12 v. 1 a 4/11 250 v. 80 mA 7/9 6/12 v. 1.5 a 7/9 250 v. 150 mA. 9/9	MAINS TRANSFORMERS Primaries 200-230-250 v. 50 c/s.	FILAMENT TRANSFORMERS Primaries 200-250 v. 50 c/s.
6/12 v. 2 a 9/9 RM4 250 v. 250	FULLY SHROUDED UPRIGHT MOUNTING	6.3 v. 1.5 a 5/9 0-4-6.3 v. 2 a 7/9 6.3 v. 3 a 8/11 0.9 6 17/6
6/12 v. 4 a 14/9 200 v. 275 mA 12/11	250-0-250 v. 60 mA. 6.3 v. 2 a., 5 v. 2 a., Midget type, 21-3-3in	12 v. 1 a 7/9 0.3 v. 0 a 17/0
6/12 v. 10 a 29/9 F.W. (Bridge Type)	350-0-350 v. 70 mA., 6.3 v. 2 a. 5 v. 2 a 18/9 250-0-250 v. 100 mA., 6.3 v. 4 v. 4 a., c.t.,	0-2-4-5-6.3 v. 4 a. 16/9 12 v. 3 a. or 24 v. 6.3 v. 2 a 7/6 1.5 a 17/6
24 v. 10 a 57/6 250 v. 80 mA 11/9	0-4-5 v. 3 a	CHARGER TRANSFORMERS
CO-AXIAL CABLE. 75 ohms 1 in., 7d yard. Twin screened feeder, 9d yd.	250-0-250 v. 100 m.A., 6.3 v. 6 a., 5 v. 3 a.,	All with 200-230-250 v. 50 c/s Primaries: 0-9-15 v.
SILVER MICA CONDENSERS. 5, 10, 15, 20, 25,	300-0-300 v, 100 mA., 6.3 v, 4 a., 5 v, 3 a 22/9	11 a., 11/9; 0-9-15 v. 3 a., 16/9; 0-9-15 v. 4 a., 18/9; 0-9-15 v. 6 a., 22/9; 0-9-15 v. 15 a., 45/
30, 35, 50, 100, 120, 150, 180, 200, 230, 300, 330, 400, 470, 500, 1,000 pfd. (.001µF), .002 mfd.	300-0-300 v. 100 mA., 6.3 v4 v. 4 a. c.t., 0-4-5 v. 3 a	
(2,000 pfd.). All at 5d. each. 3/9 dozen one type. DIAL BULBS, M.E.S., 8 v. 0.15 a., 6/9 doz.,	350-0-350 v. 100 mA., 6.3 v. 4 a., 5 v. 3 a. 22/9 350-0-350 v. 100 mA., 6.3 v. 4 v., 4 a. c.t.,	ELIMINATOR TRANSFORMERS Primaries 200-250 v. 50 c/s. 120 v. 40 mA. 7/11
8.5 v. 0.15 a., 6/9 doz.; 4.5 v. 0.3 a., 6/9 doz.		120 v. 40·mA., 5-0-5 v. 1 a 14/9
ELECTROLYTICS (Current production) NOT ex Govt.	350-0-350 v. 150 mA., 6.3 v. 2 a., 6.3 v. 2 a., 5 v. 3 a	OUTPUT TRANSFORMERS Midget Battery Pentode 68:1 for 3S4, etc. 3/6
Tubular Types Can Types 8#F 450 v 1/11	425-0-425 v. 200 mA., 6.3 v. 4 a., c.t., 6.3 v.	Small Pentode, 5,000 Ω to 3Ω
8 mfd. 500 v 2/6 10 mfd. 350 v 1/11	4 a., c.t., 5 v. 3 a., suitable Williamson Amplifier, etc	Standard Pentode, $5,000\Omega$ to 3Ω . $4/9$ Standard Pentode, $8,000\Omega$ to 3Ω . $4/9$
$\begin{array}{cccccccccccccccccccccccccccccccccccc$	Amplifier, etc	Standard Pentode, 10,000 ohms to 3 ohms 4/9 Multi-ratio 40 mA. 30:1, 45:1 60:1, 90:1.
$\begin{array}{cccccccccccccccccccccccccccccccccccc$	TOP SHROUDED DROP THROUGH TYPE 250-0-250 v. 70 mA., 6.3 v. 2.5 a	Class B Push-Pull
$32\mu F 250 v 3/9$ 32 mfd, 500 v 5/9 64 mfd, 450 v 4/9	260-0-260 v. 70 mA., 6.3 v. 2 a., 5 v. 2 a 15/9	Push-Pull 10-12 Watts 6V6 to 3Ω or 15Ω 15/9 Push-Pull 10-12 Watts to match 6V6 to
$\begin{array}{cccccccccccccccccccccccccccccccccccc$	350-0-350 v. 80 mA., 6.3 v. 2 a., 5 v. 2 a 17/6 275-0-275 v. 80 mA., 6.3 v. 3 a., 4 v. 2.5 a. 14/11	3-5-8 or 15Ω 16/9
50µF 12 v 1/3 8-8 mfd, 500 v 4/9	250-0-250 v. 100 mA, 6.3 v. 4 a., 5 v. 5 a. 21/5	Push-Pull 20 Watts high-quality sectionally wound 6L6, KT66, etc., to 3 or 15Ω 47/9
50μF 50 v 2/3 8-16μF 450 v 2/11 16-16μF 450 v 4/11	0-4-5 v. 3 a	SMOOTHING CHOKES
Can Types 8 mfd. 250 v 1/3 16-32µF 350 v 4/9	3 a 21/9 350-0-350 v. 150 mA., 6.3 v. 2 a., 6.3 v. 2 a., 5 v. 3 a 29/11	250 mA., 3 H., 50 ohms 11/9
8 mfd, 450 v $2/3$ $32-32\mu$ F 350 v $4/9$ 8 mfd, 500 v $2/9$ $32-32\mu$ F 450 v $5/11$	5 v. 3 a	150 mA., 7-10 H. 250 ohms
AMPLIFIER OR CHARGER CASES. Size 143×	E.H.T. TRANSFORMERS. 2,500 v. 5 mA.,	80 mA., 10 H. 350 ohms. 5/6 60 mA., 10 H. 400 ohms. 4/11 50 mA., 40 H. 1,000 ohms. 10/9
5§×71 in. high. Strongly made in perforated steel. Grey enamel finish. Onty 9/6,	2-0-2 v. 1.1 a., 2-0-2 v. 1.1 a., for VCR97, VCR517	20 mA., 30 H., 1,000 ohms. Potted 10/9 20 mA., 30 H., 1,000 ohms
VOLUME CONTROLS with long spindles, all values, less switch, 2/9; with S.P.	THE SKY CHIEF T.R.F. RECEIVER	EX-GOVT. MAINS TRANSFORMERS All 230 v. 50 c/s. input
switch, 3/9.		8.8 v. 4 a
WIRE WOUND POTS: 20 ohms, 500 ohms, 5K, 20K, 50K, 100K (medium length spindles), 2/9. 220 ohms, 2K,		0-11-22 v. 15 a
length spindles), 2/9, 220 ohms, 2K.		
10K, 20K, Preset type, 1/9 each.		16-18-20 v. 35 a 79/6
10K, 20K, Preset type, 1/9 each.		16-18-20 v. 35 a
10k, 20k, Preset type, 1/9 each. AMMETERS. Moving coil. 0-5 amps., 2in. scale, 11/9.		16-18-20 v. 35 a. 79'6 7.7 v. C.T. 7 amps 4 times. 25'9 460 v. 200 mA., 6.3 v. 5 a. 27'9 305-0-365 v. 150 mA. 8/9 3000-0-300 v. 80 mA. 5 v. 3 a. 8/1
10K, 20K, Preset type, 1/9 each. AMMETERS. Moving coil. 0-5 amps., 2in. scale, 11/9. EX-GOVT. E.H.T. S25 mfd, 4,000 v. Blocks. 4/9	A design of a 4-stage, 3-valve 200-250 v. A.C.	16-18-20 v. 35 a. 79/6 7. v. C. T. 7 amps 4 times. 25/9 460 v. 200 mA., 6.3 v. 5 a. 27/9 365-0-365 v. 150 mA. 8/9 300-0-300 v. 80 mA. 5 v. 3 a. 8/11 278-0-278 v. 100 mA. 8/9 300-0-300 v. 150 mA. 8/9
10K, 20K, Preset type, 1/9 each. AMMETERS. Moving coil. 0-5 amps., 2in. scale, 11/9. EX-GOVT. E.H.T. Smfd., 4,000 v. Blocks. 4/9 5 mfd., 2,500 v. Blocks. 3/9 5 mfd., 3,500 v. Cans. 3/1	A design of a 4-stage, 3-valve 200-250 v. A.C. Mains receiver with selenium rectifier. For inclusion in either of cabinets illustrated above. It	16-18-20 v. 35 a. 79'6 7. v. C. T. 7 amps 4 times. 25'9 460 v. 200 mA., 6.3 v. 5 a. 27'9 365-0-365 v. 150 mA. 8'9 300-0-300 v. 80 mA. 5 v. 3 a. 8/1 278-0-278 v. 100 mA. 8/9 300-0-300 v. 150 mA. 8/9 40 v. C. T. 150 mA. 8/9 300-0-300 v. 150 mA. 29'9
10K, 20K, Preset type, 1/9 each. AMMETERS. Moving coil. 0-5 amps., 2in. scale, 11/9. EX-GOVT. E.H.T. Smfd., 4,000 v. Blocks. 3/9 5 mfd., 3,500 v. 5 mfd., 3,600 v. Cass. 3/3 1 mfd. 9lus 1 mfd. 8(00 v., large blocks	A design of a 4-stage, 3-valve 200-250 v. A.C. Mains receiver with selenium rectifier. For inclusion in either of cabinets illustrated above. It consists of a variable Mu high gain H.F. stage followed by a low distortion grid detector triode.	16-18-20 v. 35 a
10K, 20K, Preset type, 1/9 each. AMMETERS. Moving coil. 0-5 amps., 2in. scale, 11/9. EX-GOVT. E.H.T. SmdOTHING CONDENSERS 25 mfd., 4,000 v. Blocks. 5 mfd., 3,500 v. 3/9 5 mfd., 9lus 1 mfd. 8,000 v., large blocks 3/3	A design of a 4-stage, 3-valve 200-250 v. A.C. Mains receiver with selenium rectifier. For inclusion in either of cabinets illustrated above. It consists of a variable Mu high gain H.F. stage followed by a low distortion grid detector triode. The next stage is a further triode amplifier with tone correction by negative feedback Finally	16-18-20 v. 35 a
10K, 20K, Preset type, 1/9 each. AMMETERS. Moving coil. 0-5 amps., 2in. scale, 11/9. EX-GOVT. E.H.T. SMOOTHING CONDENSERS 25 mfd., 4,000 v. Blocks. 4/9 5 mfd., 4,000 v. Blocks. 3/9 5 mfd., 3,500 v. Cans. 3/3 1 mfd. plus 1 mfd. 8,000 v., large blocks 9/6	A design of a 4-stage, 3-valve 200-250 v. A.C. Mains receiver with selenium rectifier. For inclusion in either of cabinets illustrated above. It consists of a variable Mu high gain H.F. stage followed by a low distortion grid detector triode. The next stage is a further triode amplifier with tone correction by negative feedback. Finally commes the output stage consisting of a parallel connected double triode giving ample output at an	16-18-20 v. 35 a. 79'6 7.7 v. C.T. 7 amps 4 times. 25/9 460 v. 200 mA, 6.3 v. 5 a. 27/9 305-0-365 v. 150 mA. 8/9 300-0-300 v. 80 mA. 5 v. 3 a. 8/11 278-0-278 v. 100 mA. 8/9 300-0-300 v. 150 mA. 8/9 300-0-300 v. 150 mA. 29/9 40 v. C.T. 150 mA. 4 v. 6 a., 6.3 v. 6 a., 6.3 v. 0 6 a., 4 v. 3 a., 4 v. 3 a., 40 v. C.T. 150 mA. 4 v. 6 a., 4 v. 3 a., 4 v. 3 a., 4v. 3 a., 5 v. 2 a. 22/9 EX-GOVT AUTO. TRANSFORMERS 15-10-5-0-195-215-235 v. 500 watts.
10k, 20k, Preset type, 1/9 each. AMMETERS. Moving coil. 0-5 amps., 2in. scale, 11/9. EX-GOVT. E.H.T. Smfd., 4,000 v. Blocks. 25 mfd., 2,500 v. Blocks. 3/3 mfd. plus 1 mfd. 8,000 v., large blocks (common negative isolated). 9/6 1.5 mfd., 4,000 v. Blocks. 5/9 Ex-GOVT. ACCUMULATORS with non-spill vents Umused and guaranteed. 2 v. 16 A.H., 5/9 each EX-GOVT. BLOCK FX-GOVT. BLOCK	A design of a 4-stage, 3-valve 200-250 v. A.C. Mains receiver with selenium rectifier. For inclusion in either of cabinets illustrated above. It consists of a variable Mu high gain H.F. stage followed by a low distortion grid detector triode. The next stage is a further triode amplifier with tone correction by negative feedback. Finally commes the output stage consisting of a parallel connected double triode giving ample output at an extraordinary low level of distortion. Point-to- point-wiring diagrams instructione and parts	16-18-20 v. 35 a. 79'6 7.7 v. C. T. 7 amps 4 times. 25'9 460 v. 200 mA., 6.3 v. 5 a. 27/9 305-0-365 v. 150 mA. 8/9 300-0-300 v. 80 mA. 5 v. 3 a. 8/11 278-0-278 v. 100 mA. 8/9 300-0-300 v. 150 mA. 8/9 300-0-300 v. 150 mA. 8/9 300-0-300 v. 150 mA. 29/9 40 v. C.T. 150 mA. 4 v. 6 a., 6.3 v. 6 a., 6.3 v. 06 a., 4 v. 3 a., 4 v. 3 a., 4v. 3 a., 5 v. 2 a. 22/9 EX-GOVT AUTO. TRANSFORMERS 15-10-5-0195-215-235 v. 500 watts. 15-10-5-3-315 v. 1,000 watts. 27/9
10k, 20k, Preset type, 1/9 each. AMMETERS. Moving coil. 0-5 amps., 2in. scale, 11/9. EX-GOVT. E.H.T. S5 mfd., 4,000 v. Blocks. 4/9 5 mfd., 2,500 v. 5 mfd., 2,500 v. Blocks. 3/3 1 mfd. plus 1 mfd. 8,000 v., large blocks (common negative isolated). 9/6 1.5 mfd., 4,000 v. Blocks. 5 mfd., 4,000 v. Blocks. (common negative isolated). 9/6 1.5 mfd., 4,000 v. Blocks. 5 mfd., 4,000 v. Y/9 EX-GOVT. ALCUMULATORS with non-spill vents. Unused and guaranteed. 2 v. 16 A.H., 5/9 each EX-GOVT. BLOCK PAPER CONDENSERS 2 mfd. 800 v. 1/9 4 mfd. 2,000 v. 6/9 4 mfd. 2000 v. 2/9 6 - 6mfd.450 v. 5/9	A design of a 4-stage, 3-valve 200-250 v. A.C. Mains receiver with selenium rectifier. For inclusion in either of cabinets illustrated above. It consists of a variable Mu high gain H.F. stage followed by a low distortion grid detector triode. The next stage is a further triode amplifier with tone correction by negative feedback. Finally comes the output stage consisting of a parallel connected double triode giving ample output at an extraordinary low level of distortion. Point-to- point-wiring diagrams, instructions, and parts list, 2/6. This receiver can be built for a maximum	16-18-20 v. 35 a. 79'6 7.7 v. C. T. 7 amps 4 times. 25'9 460 v. 200 mA., 6.3 v. 5 a. 27'9 305-0-365 v. 150 mA. 8'9 300-0-300 v. 80 mA. 5 v. 3 a. 8/11 278-0-278 v. 100 mA. 8/9 300-0-300 v. 150 mA. 8/9 300-0-300 v. 150 mA. 8/9 300-0-300 v. 150 mA. 8/9 40 v. C.T. 150 mA. 8/9 40 v. C.T. 150 mA. 29'9 40 v. C.T. 150 mA. 4. v. 6 a., 4. v. 3 a., 4. v. 3 a., 4. v. 3 a., 4. v. 3 a., 5 v. 2 a. 27/9 20/9 EX-GOVT AUTO. TRANSFORMERS 15-10-5-0-195-215-235 v. 500 vatts. 15-10-5-0-195-215-235 v. 500 vatts. 27/9 Double wound 10-0-200-220-240 v. to 10-0- 276-25-315 v. 1,000 watts. 69/6 Double wound 0-230 v. to 0-230 v. to 10-0- 216-25-515 v. 50 V. X0 (21 amps). 8/15/-
10K, 20K, Preset type, 1/9 each. AMMETERS. Moving coil. 0.5 amps., 2in. scale, 11/9. EX-GOVT. E.H.T. Smfd., 4,000 v. Blocks. 4/9 5 mfd., 2,500 v. Blocks. 3/3 1 mfd. plus 1 mfd. 8,000 v., large blocks (common negative isolated). 9/6 1.5 mfd., 4,000 v. Blocks. (common negative isolated). 9/6 1.5 mfd., 4,000 v. Blocks. (common negative isolated). 9/6 1.5 mfd., 4,000 v. Blocks. Y/9 Common negative isolated). 9/6 1.5 mfd., 4,000 v. Blocks. 5/9 EX-GOVT. ACCUMULATORS with non-spill vents Unused and guaranteed. 2 v. 16 A.H., 5/9 each EX-GOVT. BLOCK PAPER CONDENSERS 2 mfd. 500 v. 5/9 4 mfd. 500 v. 2/9 6-6 mfd. 450 v. 5/9 4 mfd. 500 v. 2/9 6-6 mfd. 450 v. 5/9	A design of a 4-stage, 3-valve 200-250 v. A.C. Mains receiver with selenium rectifier. For inclusion in either of cabinets illustrated above. It consists of a variable Mu high gain H.F. stage followed by a low distortion grid detector triode. The next stage is a further triode amplifier with tone correction by negative feedback. Finally comes the output stage consisting of a parallel connected double triode giving ample output at an extraordinary low level of distortion. Point-to- point-wiring diagrams, instructions, and parts list, 2/6. This receiver can be built for a maximum of £4/19/6 including cabinet. P.M. SPEAKERS. All 2-3 ohms film Plessev	16-18-20 v. 35 a. 79'6 7. v. C. T. 7 amps 4 times. 25'9 460 v. 200 mA., 6.3 v. 5 a. 27'9 305-0-365 v. 150 mA. 8'9 300-0-300 v. 80 mA. 5 v. 3 a. 8'11 278-0-278 v. 100 mA. 8'9 300-0-300 v. 80 mA. 5 v. 3 a. 8'14 278-0-278 v. 100 mA. 8'9 300-0-300 v. 150 mA. 29'9 40 v. C.T. 150 mA. 4 v. 6 a., 6.3 v. 6 a., 6.3 v. 6 a., 4 v. 3 a., 4 v. 3 a., 5 v. 2 a. 22'9 EX-GOVT AUTO. TRANSFORMERS 15-10-5-0-195-215-23 5 v. 500 watts. 27'9 Double wound 10-0-200-220-240 v. to 10-0 27'5-205-315 v. 1,000 watts. 69'6 Double wound 0-230 v. to 0-230 v. in steps of 11 volts from 37.5 5 KVA (21 amps). £6'15/- Double wound 0-170 v. 1,500 watts. 69'6
10k, 20k, Preset type, 1/9 each. AMMETERS. Moving coil. 0.5 amps., 2in. scale, 11/9. EX-GOVT. E.H.T. Smfd., 4,000 v. Blocks. 4/9 5 mfd., 2,500 v. Blocks. 3/3 Imfd. plus 1 mfd. 8,000 v., large blocks (common negative isolated). 9/6 1.5 mfd., 4,000 v. Blocks. (common negative isolated). 9/6 1.5 mfd., 4,000 v. Blocks. (common negative isolated). 9/6 1.5 mfd., 4,000 v. Blocks. Yet Blocks. Yet System 10. Yet Blocks. Yet System 10.	A design of a 4-stage, 3-valve 200-250 v. A.C. Mains receiver with selenium rectifier. For inclusion in either of cabinets illustrated above. It consists of a variable Mu high gain H.F. stage followed by a low distortion grid detector triode. The next stage is a further triode amplifier with tone correction by negative feedback. Finally comes the output stage consisting of a parallel connected double triode giving ample output at an extraordinary low level of distortion, Point-to- point-wiring diagrams, instructions, and parts list, 2/6. This receiver can be built for a maximum of £4/19/6 including cabinet. P.M. SPEAKERS. All 2-3 ohms. 64 in. Plessey, 16/9. 8 in. Plessey, 15/9. 10in RA 26/9 10in	16-18-20 v. 35 a
10k, 20k, Preset type, 1/9 each. AMMETERS. Moving coil. 0.5 amps., 2in. scale, 11/9. EX-GOVT. E.H.T. Smfd., 4,000 v. Blocks. 4/9 5 mfd., 2,500 v. Blocks. 3/3 1 mfd. plus 1 mfd. 8,000 v., large blocks (common negative isolated). 9.5 mfd., 4,000 v. Blocks. 5/9 1 mfd. plus 1 mfd. 8,000 v., large blocks (common negative isolated). 9.6 1.5 mfd., 4,000 v. Blocks. 5/9 EX-GOVT. ACCUMULATORS with non-spill vents Unused and guaranteed. 2 v. 16 A.H., 5/9 each EX-GOVT. BLOCK PAPER CONDENSERS 2 mfd. 300 v. 1/9 4 mfd. 730 v. 3/9 4 mfd. 730 v. 4/9 4 mfd. 500 v. 5/9 4 mfd. 730 v. 3/9 4 mfd. 730 v. 4/9 4 mfd. 400 v. plus 2 mfd. 250 v. 5/9 4 mfd. 400 v. 15 mfd. 500 v. 4 mfd. 400 v. 15 mfd. 500 v. 4 mfd. 400 v. 15 mfd. 500 v. 5 mfd. 500 v. 7/9 4 mfd. 400 v. 15 mfd. 500 v. 5 mfd. 500 v. 7/9 5 mfd. 500 v.	 A design of a 4-stage, 3-valve 200-250 v. A.C. Mains receiver with selenium rectifier. For inclusion in either of cabinets illustrated above. It consists of a variable Mu high gain H.F. stage followed by a low distortion grid detector triode. The next stage is a further triode amplifier with tone correction by negative feedback. Finally comes the output stage consisting of a parallel connected double triode giving ample output at an extraordinary low level of distortion. Point-to- point-wiring diagrams, instructions, and parts list, 2/6. This receiver can be built for a maximum of £4/19/6 including cabinet. P.M. SPEAKERS. All 2-3 ohms. 64in. Plessey, 16/9. 8in. Plessey, 15/9. 10in. RA., 26/9. 10in. Plessey, 18/6. 10in. Rola with Trans., 29/6. R.S.C. BATTERY CHARGER KITS. For mains input 900, 250 u; 50 of c. To schward. 	16-18-20 v. 35 a
10k, 20k, Preset type, 1/9 each. AMMETERS. Moving coil. 0.5 amps., 2in. scale, 11/9. EX-GOVT. E.H.T. Smfd., 4,000 v. Blocks. 4/9 5 mfd., 2,500 v. Blocks. 3/9 5 mfd., 3,500 v. Cass. 3/3 1 mfd. plus 1 mfd. 8,000 v., large blocks (common negative isolated). 9 (common negative isolated). 9/6 1.5 mfd., 4,000 v. Blocks. 5/9 EX-GOVT. ACCUMULATORS with non-spill vents Unused and guaranteed. 2 v. 16 A.H., 5/9 each EX-GOVT. BLOCK PAPER CONDENSERS 2 mfd. 300 v. 2/9 4 mfd. 730 v. 3/9 4 mfd. 730 v. 4/9 4 mfd. 730 v. 4/9 4 mfd. 400 v. plus 2 mfd. 250 v. 5/9 4 mfd. 1,000 v. 4/9 4 mfd. 400 v. plus 2 mfd. 250 v. 5/9 4 mfd. 400 v. 15 mfd. 500 v. 4 mfd. 400 v. plus 2 mfd. 250 v., 1/11. 7/9 EX-GOVT. BLOCK ELECTROLYTICS. Small size 2,000 mfd. 12 v. for L.T. smoothing, 1/11 ea	 A design of a 4-stage, 3-valve 200-250 v. A.C. Mains receiver with selenium rectifier. For inclusion in either of cabinets illustrated above. It consists of a variable Mu high gain H.F. stage followed by a low distortion grid detector triode. The next stage is a further triode amplifier with tone correction by negative feedback. Finally comes the output stage consisting of a parallel connected double triode giving ample output at an extraordinary low level of distortion. Point-to- point-wiring diagrams, instructions, and parts list, 2/6. This receiver can be built for a maximum of £4/19/6 including cabinet. P.M. SPEAKERS. All 2-3 ohms. 64in. Plessey, 16/9. 8in. Plessey, 15/9. 10in. R.A., 26/9. 10in. Plessey, 18/6. 10in. Rola with Trans., 29/6. R.S.C. BATTERY CHARGER KITS. For mains input 200-250 v. 50 c/s. To charge 6 v. accumu- lator at 2 amps, 25/9. 	16-18-20 v. 35 a
10k, 20k, Preset type, 1/9 each. AMMETERS. Moving coil. 0.5 amps., 2in. scale, 11/9. EX-GOVT. E.H.T. Smfd., 4,000 v. Blocks. 25 mfd., 2,500 v. Blocks. 3/9 5 mfd., 3,600 v. 5 mfd., 3,600 v. Cass. 1 mfd. plus 1 mfd. 8,000 v., large blocks 3/9 (common negative isolated). 9/6 1.5 mfd., 4,000 v. Blocks. (common negative isolated). 9/6 1.5 mfd., 4,000 v. Blocks. (common negative isolated). 9/6 1.5 mfd., 4,000 v. Blocks. (common negative isolated). 9/6 EX-GOVT. ACCUMULATORS with non-spill vents Unused and guaranteed. 2 v. 16 A.H., 5/9 each EX-GOVT. BLOCK PAPER CONDENSERS 2 mfd. 1000 v	A design of a 4-stage, 3-valve 200-250 v. A.C. Mains receiver with selenium rectifier. For inclusion in either of cabinets illustrated above. It consists of a variable Mu high gain H.F. stage followed by a low distortion grid detector triode. The next stage is a further triode amplifier with tone correction by negative feedback. Finally connected double triode giving ample output at an extraordinary low level of distortion. Point-to- point-wiring diagrams, instructions, and parts list 2/6. This receiver can be built for a maximum of £4/19/6 including cabinet. P.M. SPEAKERS. All 2-3 ohms. 64 in. Plessey, 16/9. 8in. Plessey, 15/9. 10 in. R.A., 26/9. 10 in. Plessey, 18/6. 10 in. Rola with Trans., 29/6. R.S.C. BATTERY CHARGER KITS. For mains input 200-250 v. 50 c/s. To charge 6 v. accumu- lator at 2 amps., 25/9. To charge 6 v. or 12 v. battery at 2 a., 31/6.	16-18-20 v. 35 a
10K, 20K, Preset type, 1/9 each. AMMETERS. Moving coil. G.S. amps., 2in. scale, 11/9. EX-GOVT. E.H.T. Smfd., 4,000 v. Blocks	 A design of a 4-stage, 3-valve 200-250 v. A.C. Mains receiver with selenium rectifier. For inclusion in either of cabinets illustrated above. It consists of a variable Mu high gain H.F. stage followed by a low distortion grid detector triode. The next stage is a further triode amplifier with tone correction by negative feedback. Finally comes the output stage consisting of a parallel connected double triode giving ample output at an extraordinary low level of distortion, Point-topoint-wiring diagrams, instructions, and parts list, 2/6. This receiver can be built for a maximum of £4/19/6 including cabinet. P.M. SPEAKERS. All 2-3 ohms. 64in. Plessey, 18/6. 10in. Rola with Trans., 22/6. R.S.C. BATTERY CHARGER KITS. For mains input 200-250 v. 50 c/s. To charge 6 v. or 12 v. battery at 2 a., 31/6. To charge 6 v. or 12 v. battery at 4 a., 49/9. 	16-18-20 v. 35 a. 79'6 7.7 v. C. T. 7 amps 4 times. 25'9 363-0-365 v. 150 mA. 8/9 300-0-300 v. 80 mA. 5 v. 3 a. 8/11 278-0-278 v. 100 mA. 8/9 300-0-300 v. 150 mA. 29/9 40 v. C.T. 150 mA. 4 v. 6 a., 0.3 v. 6 a., (-3, v. 0-8 a., 4 v. 3 a., 4 v. 3 a., 4 v. 3 a., 4 v. 3 a., 5 v. 2 a. 22/9 EX-GOVT AUTO. TRANSFORMERS 15-10-5-0-195-215-235 v. 500 watts. 27/9 Double wound 10-0-200-220-240 v. to 10-0- 275-205-315 v. 1,000 watts. 69/6 Double wound 0-10-240 v. to 0-130-140- 150-160-170 v. 1,500 watts. 69/6 Carriage on any of above 5/- extra. 69/6 Ex-GOVT. SMOOTHING CHOKES 250 mA., 10 H. 50 ohms. 14/9 250 mA. 10 H. 50 ohms. 14/9 250 mA. 10 H. 50 ohms. 16/11 100 mA. 5 H. 100 ohms, Tropicalised. 6/9 100 mA. 10 H. 50 ohms. 6/9
10K, 20K, Preset type, 1/9 each. AMMETERS. Moving coil. 0.5 amps., 2in. scale, 11/9. EX-GOVT. E.H.T. Smfd., 4,000 v. Blocks. 25 mfd., 2,500 v. Blocks. 3/9 5 mfd., 3,600 v. 5 mfd., 3,600 v. Cass. 1 mfd. plus 1 mfd. 8,000 v., large blocks 3/9 (common negative isolated). 9/6 1.5 mfd., 4,000 v. Blocks. (common negative isolated). 9/6 1.5 mfd., 4,000 v. Blocks. (common negative isolated). 9/6 1.5 mfd., 4,000 v. Blocks. (common negative isolated). 9/6 EX-GOVT. ACCUMULATORS with non-spill vents Unused and guaranteed. 2 v. 16 A.H., 5/9 each EX-GOVT. BLOCK PAPER CONDENSERS 2 mfd. 1000 v	A design of a 4-stage, 3-valve 200-250 v. A.C. Mains receiver with selenium rectifier. For inclusion in either of cabinets illustrated above. It consists of a variable Mu high gain H.F. stage followed by a low distortion grid detector triode. The next stage is a further triode amplifier with tone correction by negative feedback. Finally connected double triode giving ample output at an extraordinary low level of distortion. Point-to- point-wiring diagrams, instructions, and parts list, 2/6. This receiver can be built for a maximum of £4/19/6 including cabinet. P.M. SPEAKERS. All 2-3 ohms. 64 in. Plessey, 16/9. 8 in. Plessey, 15/9. 10 in. R.A., 26/9. 10 in. Plessey, 18/6. 10 in. Rola with Trans., 29/6. R.S.C. BATTERY CHARGER KITS. For mains input 200-250 v. 50 c/s. To charge 6 v. or 12 v. battery at 2 a., 31/6. To charge 6 v. or 12 v. battery at 2 a., 34/6. FO ACHARGE KITS CONSIST OF BLACK CRACKLE	16-18-20 v. 35 a. 79'6 7. v. C. T. 7 amps 4 times. 25'9 460 v. 200 mA., 6.3 v. 5 a. 27'9 305-0-365 v. 150 mA. 8'9 300-300 v. 80 mA. 5 v. 3 a. 8/11 278-0-278 v. 100 mA. 8'9 300300 v. 150 mA. 8'9 300300 v. 150 mA. 8'9 300300 v. 150 mA. 29'9 40 v. C.T. 150 mA. 4 v. 6 a., 6.3 v. 6 a., 29'9 40 v. C.T. 150 mA. 4 v. 6 a., 4 v. 3 a., 4 v. 3 a., 4 v. 3 a., 5 v. 2 a. 22/9 EX-GOVT AUTO. TRANSFORMERS 15-10-5-0-195-215-235 v. 500 vatts. 150-105-0-195-215-235 v. 500 vatts. 27'9 Double wound 10-200-220-240 v. to 10-0- 275-205-315 v. 1,000 watts. 69'6 Double wound 0-230 v. to 0-230 v. in steps of 11 volts from 57.5 5 KVA (21 amps)
10K, 20K, Preset type, 1/9 each. AMMETERS. Moving coil. G.5 amps., 2in. scale, 11/9. EX.GOVT. E.H.T. SMOOTHING CONDENSERS. 25 mfd, 2,500 v. Blocks. 3/3 5 mfd, 3,500 v. Cans. 3/1 mfd. plus 1 mfd. 8,000 v., large blocks (common negative isolated). 9/6 1.5 mfd., 4,000 v. Blocks. (common negative isolated). 9/6 1.5 mfd., 4,000 v. Blocks. (common negative isolated). 9/6 1.5 mfd., 4,000 v. Blocks. 1.5 mfd., 4,000 v. 1.5 mfd., 4,000 v. 1.5 mfd., 4,000 v. 1.5 mfd., 4,000 v. 1.5 mfd. 800 v. 1.7 9 4 mfd. 300 v. 2 mfd. 800 v. 2 mfd. 800 v. 2 mfd. 100 v. 4 mfd. 1000 v. 4 mfd. 100 v. 4 mfd. 100 v. 5 mfd. 100 v. <	A design of a 4-stage, 3-valve 200-250 v. A.C. Mains receiver with selenium rectifier. For inclusion in either of cabinets illustrated above. It consists of a variable Mu high gain H.F. stage followed by a low distortion grid detector triode. The next stage is a further triode amplifier with tone correction by negative feedback. Finally connected double triode giving ample output at an extraordinary low level of distortion. Point-to- point-wiring diagrams, instructions, and parts list, 2/6. This receiver can be built for a maximum of £4/19/6 including cabinet. P.M. SPEAKERS. All 2-3 ohms. 64in. Plessey, 16/9. 8in. Plessey, 15/9. 10in. R.A., 26/9. 10in. Plessey, 18/6. 10in. Rola with Trans., 29/6. R.S.C. BATTERY CHARGER KITS. For mains input 200-250 v. 50 c/s. To charge 6 v. or 12 v. To charge 6 v. or 12 v. battery at 2 a., 31/6. TO charge 4 a., 49/9. ABOVE KITS CONSIST OF BLACK CRACKLE LOUVRED STEEL CASE, MAINS TRANS.	16-18-20 v. 35 a
10K, 20K, Preset type, 1/9 each. AMMETERS. Moving coil. G.5 amps., 2in. scale, 11/9. EX-GOYT. E.H.T. SMOOTHING CONDENSERS. 25 mfd., 2,500 v. Blocks. 3/3 5 mfd., 2,500 v. Blocks. 3/4 5 mfd., 3,500 v. Cans. 3/3 1 mfd. plus 1 mfd. 8,000 v., large blocks (common negative isolated). 9/6 1.5 mfd., 4,000 v. Blocks. 5/9 EX-GOVT. ACCUMULATORS with non-spill vents Unused and guaranteed. 2 v. 16 A.H., 5/9 each ex-GOVT. BLOCK PAPER CONDENSERS 2 mfd. 800 v. 1/9 4 mfd. 730 v. 3/9 4 mfd. 1,000 v 4/9 15 mfd. 500 v 5/9 4 mfd. 1,000 v 4/3 8-8 mfd. 500 v 5/9 4 mfd. 1,000 v 4/3 8-8 mfd. 500 v 5/9 4 mfd. 1,000 v 4/3 8-8 mfd. 500 v 5/9 4 mfd. 1,000 v 4/3 8-8 mfd. 500 v 5/9 4 mfd. 1,000 v 4/3 8-8 mfd. 500 v 5/9 4 mfd. 1,000 v 4/3 8-8 mfd. 500 v	A design of a 4-stage, 3-valve 200-250 v. A.C. Mains receiver with selenium rectifier. For inclusion in either of cabinets illustrated above. It consists of a variable Mu high gain H.F. stage followed by a low distortion grid detector triode. The next stage is a further triode amplifier with tone correction by negative feedback. Finally connected double triode giving ample output at an extraordinary low level of distortion. Point-to- point-wiring diagrams, instructions, and parts list, 2/6. This receiver can be built for a maximum of £4/19/6 including cabinet. P.M. SPEAKERS. All 2-3 ohms. 64in. Plessey, 16/9. 8in. Plessey, 15/9. 10in. R.A., 26/9. 10in. Plessey, 18/6. 10in. Rola with Trans., 29/6. R.S.C. BATTERY CHARGER KITS. For mains input 200-250 v. 50 c/s. To charge 6 v. accumu- lator at 2 amps, 25/9. To charge 6 v. or 12 v. battery at 4 a, 49/9. ABOVE KITS CONSIST OF BLACK CRACKLE LOUVRED STEEL CASE, MAINS TRANS- FORMER, FULL WAVE METAL RECTIFIER, FUSES. FUSE-HOLDERS AND CIRCUIT	16-18-20 v. 35 a
10k, 20k, Preset type, 1/9 each. AMMETERS. Moving coil. G. Samps., 2in. scale, 11/9. EX-GOVT. E.H.T. Smfd, 4,000 v. Blocks	A design of a 4-stage, 3-valve 200-250 v. A.C. Mains receiver with selenium rectifier. For inclusion in either of cabinets illustrated above. It consists of a variable Mu high gain H.F. stage followed by a low distortion grid detector triode. The next stage is a further triode amplifier with tone correction by negative feedback. Finally connected double triode giving ample output at an extraordinary low level of distortion. Point-to- point-wiring diagrams, instructions, and parts list, 2/6. This receiver can be built for a maximum of £4/19/6 including cabinet. P.M. SPEAKERS. All 2-3 ohms. 64in. Plessey, 16/9. 8in. Plessey, 15/9. 10in. R.A., 26/9. 10in. Plessey, 18/6. 10in. Rola with Trans., 29/6. R.S.C. BATTERY CHARGER KITS. For mains input 200-250 v. 50 c/s. To charge 6 v. accumu- tator at 2 amps, 25/9. To charge 6 v. or 12 v. battery at 2 a., 31/6. To charge 6 v. or 12 v. battery at 4 a., 49/9. ABOVE KITS CONSIST OF BLACK CRACKLT DOVER S. FUSL-HOLDERS AND CIRCUIT. Any type assembled and tested for 6/9 extra.	16-18-20 v. 35 a
10k, 20k, Preset type, 1/9 each. AMMETERS. Moving coil. 0.5 amps., 2in. scale, 11/9. EX-GOVT. E.H.T. Smfd., 4,000 v. Blocks. 4/9 5 mfd., 2,500 v. Blocks. 3/3 1 mfd. plus 1 mfd. 8,000 v., large blocks (common negative isolated). 9/6 6.5 mfd., 4,000 v. Blocks. 3/3 1 mfd. plus 1 mfd. 8,000 v., large blocks (common negative isolated). 9/6 1.5 mfd., 4,000 v. Blocks. 5/9 EX-GOVT. ACCUMULATORS with non-spill vents Unused and guaranteed. 2 v. 16 A.H., 5/9 each EX-GOVT. BLOCK PAPER CONDENSERS 2 mfd. 300 v. 1/9 6-6 mfd. 450 v. 5/9 4 mfd. 1,000 v. 4/3 8-8 mfd. 500 v. 5/9 4 mfd. 1,000 v. 4/3 8-8 mfd. 500 v. 5/9 4 mfd. 1,000 v. 4/3 8-8 mfd. 500 v. 5/9 4 mfd. 1,000 v. 4/3 8-8 mfd. 500 v. 5/9 4 mfd. 1,000 v. 4/3 8-8 mfd. 500 v. 5/9 4 mfd. 1,000 v. 4/3 8-8 mfd. 500 v. 5/9 5 mfd. 400 v. plus 2 mfd. 250 v., 1/11. 5.0 v. 5.0 v. 5/9	A design of a 4-stage, 3-valve 200-250 v. A.C. Mains receiver with selenium rectifier. For inclusion in either of cabinets illustrated above. It consists of a variable Mu high gain H.F. stage followed by a low distortion grid detector triode. The next stage is a further triode amplifier with tone correction by negative feedback. Finally connected double triode giving ample output at an extraordinary low level of distortion. Point-to- point-wiring diagrams, instructions, and parts list, 2/6. This receiver can be built for a maximum of £4/19/6 including cabinet. P.M. SPEAKERS. All 2-3 ohms. 64in. Plessey, 16/9. 8in. Plessey, 15/9. 10in. R.A., 26/9. 10in. Plessey, 18/6. 10in. Rola with Trans., 29/6. R.S.C. BATTERY CHARGER KITS. For mains input 200-250 v. 50 c/s. To charge 6 v. accumu- lator at 2 amps, 25/9. To charge 6 v. or 12 v. Battery at 4 a., 49/9. AbO'E KITS CONSIST OF BLACK CRACKLE LOUVRED STEEL CASE, MAINS TRANS- FORMER, FULL WAVE METAL RECTIFIER, FUSES, FUSE-HOLDERS AND CIRCUIT. Any type assembled and tested for 6/9 extra.	16-18-20 v. 35 a
10k, 20k, Preset type, 1/9 each. AMMETERS. Moving coil. 0.5 amps., 2in. scale, 11/9. EX-GOVT. E.H.T. Smfd., 4,000 v. Blocks. 4/9 5 mfd., 2,500 v. Blocks. 3/3 1 mfd. plus 1 mfd. 8,000 v., large blocks (common negative isolated). 9/6 6.5 mfd., 4,000 v. Blocks. 3/3 1 mfd. plus 1 mfd. 8,000 v., large blocks (common negative isolated). 9/6 1.5 mfd., 4,000 v. Blocks. 5/9 EX-GOVT. ACCUMULATORS with non-spill vents Unused and guaranteed. 2 v. 16 A.H., 5/9 each EX-GOVT. BLOCK PAPER CONDENSERS 2 mfd. 300 v. 1/9 6-6 mfd. 450 v. 5/9 4 mfd. 1,000 v. 4/3 8-8 mfd. 500 v. 5/9 4 mfd. 1,000 v. 4/3 8-8 mfd. 500 v. 5/9 4 mfd. 1,000 v. 4/3 8-8 mfd. 500 v. 5/9 4 mfd. 1,000 v. 4/3 8-8 mfd. 500 v. 5/9 4 mfd. 1,000 v. 4/3 8-8 mfd. 500 v. 5/9 4 mfd. 1,000 v. 4/3 8-8 mfd. 500 v. 5/9 5 mfd. 400 v. plus 2 mfd. 250 v., 1/11. 5.0 v. 5.0 v. 5/9	A design of a 4-stage, 3-valve 200-250 v. A.C. Mains receiver with selenium rectifier. For inclusion in either of cabinets illustrated above. It consists of a variable Mu high gain H.F. stage followed by a low distortion grid detector triode. The next stage is a further triode amplifier with tone correction by negative feedback. Finally connected double triode giving ample output at an extraordinary low level of distortion. Point-to- point-wiring diagrams, instructions, and parts list, 2/6. This receiver can be built for a maximum of £4/19/6 including cabinet. P.M. SPEAKERS. All 2-3 ohms. 64in. Plessey, 16/9. 8in. Plessey, 15/9. 10in. R.A., 26/9. 10in. Plessey, 18/6. 10in. Rola with Trans., 29/6. R.S.C. BATTERY CHARGER KITS. For mains input 200-250 v. 50 c/s. To charge 6 v. accumu- lator at 2 amps, 25/9. To charge 6 v. or 12 v. Battery at 4 a., 49/9. AbO'E KITS CONSIST OF BLACK CRACKLE LOUVRED STEEL CASE, MAINS TRANS- FORMER, FULL WAVE METAL RECTIFIER, FUSES, FUSE-HOLDERS AND CIRCUIT. Any type assembled and tested for 6/9 extra.	16-18-20 v. 35 a
10k, 20k, Preset type, 1/9 each. AMMETERS. Moving coil. 0.5 amps., 2in. scale, 11/9. EX-GOVT. E.H.T. Smfd., 4,000 v. Blocks. 4/9 5 mfd., 2,500 v. Blocks. 3/3 1 mfd. plus 1 mfd. 8,000 v., large blocks (common negative isolated). 9/6 6.5 mfd., 4,000 v. Blocks. 3/3 1 mfd. plus 1 mfd. 8,000 v., large blocks (common negative isolated). 9/6 1.5 mfd., 4,000 v. Blocks. 5/9 EX-GOVT. ACCUMULATORS with non-spill vents Unused and guaranteed. 2 v. 16 A.H., 5/9 each EX-GOVT. BLOCK PAPER CONDENSERS 2 mfd. 300 v. 1/9 6-6 mfd. 450 v. 5/9 4 mfd. 1,000 v. 4/3 8-8 mfd. 500 v. 5/9 4 mfd. 1,000 v. 4/3 8-8 mfd. 500 v. 5/9 4 mfd. 1,000 v. 4/3 8-8 mfd. 500 v. 5/9 4 mfd. 1,000 v. 4/3 8-8 mfd. 500 v. 5/9 4 mfd. 1,000 v. 4/3 8-8 mfd. 500 v. 5/9 4 mfd. 1,000 v. 4/3 8-8 mfd. 500 v. 5/9 5 mfd. 400 v. plus 2 mfd. 250 v., 1/11. 5.0 v. 5.0 v. 5/9	A design of a 4-stage, 3-valve 200-250 v. A.C. Mains receiver with selenium rectifier. For inclusion in either of cabinets illustrated above. It consists of a variable Mu high gain H.F. stage followed by a low distortion grid detector triode. The next stage is a further triode amplifier with tone correction by negative feedback. Finally connected double triode giving ample output at an extraordinary low level of distortion. Point-to- point-wiring diagrams, instructions, and parts list, 2/6. This receiver can be built for a maximum of £4/19/6 including cabinet. P.M. SPEAKERS. All 2-3 ohms. 64in. Plessey, 16/9. 8in. Plessey, 15/9. 10in. R.A., 26/9. 10in. Plessey, 18/6. 10in. Rola with Trans., 29/6. R.S.C. BATTERY CHARGER KITS. For mains input 200-250 v. 50 c/s. To charge 6 v. or 12 v. Dattery at 2 a., 31/6. To charge 6 v. or 12 v. BATTERY CHARGER For normal A.C. mains input 200-230 v. 50 v., 50 c/s. Selector panel for 6 v. or 12 v. Charger (CHARGER For somal A.C. mains input 200-230 v. 50 v., 50 c/s. Selector panel for 6 v. or 12 v. Charger (CHARGER For somal A.C. mains input 200-230-250 v. 50 c/s. Selector panel for 6 v. or 12 v. Charger (CHARGER For somal A.C. mains input 200-230-250 v. 50 c/s. Selector panel for	16-18-20 v. 35 a
 10K, 20K, Preset type, 1/9 each. AMMETERS. Moving coil. G.E.C. 0-5 amps., 2in. scale, 11/9. EX-GOVT. E.H.T. SMOOTHING CONDENSERS 25 mfd, 4,000 v. Blocks	A design of a 4-stage, 3-valve 200-250 v. A.C. Mains receiver with selenium rectifier. For inclusion in either of cabinets illustrated above. It consists of a variable Mu high gain H.F. stage followed by a low distortion grid detector triode. The next stage is a further triode amplifier with tone correction by negative feedback. Finally connected double triode giving ample output at an extraordinary low level of distortion. Point-to- point-wiring diagrams, instructions, and parts list, 2/6. This receiver can be built for a maximum of £4/19/6 including cabinet. P.M. SPEAKERS. All 2-3 ohms. 64in. Plessey, 16/9. 8in. Plessey, 15/9. 10in. R.A., 26/9. 10in. Plessey, 18/6. 10in. Rola with Trans., 29/6. R.S.C. BATTERY CHARGER KITS. For mains input 200-250 v. 50 c/s. To charge 6 v. accumu- lator at 2 amps, 25/9. To charge 6 v. or 12 v. battery at 4 a, 49/9. ABOVE KITS CONSIST OF BLACK CRACKLE LOUVRED STEEL CARGE, FULL WAVE METAL RECTIFIER, FUSES, FUSE-HOLDERS AND CIRCUIT. Any type assembled and tested for 6/9 extra. R.S.C. 6 v. or 12 v. BATTERY CHARGER For normal A.C. mains input 200-230-250 v., 50 c/s. Selector panel for 6 v. or 12 v. charging. Variable charge rate of up to 4 AMP8. Fused.	16-18-20 v. 35 a. 79'6 460 v. 200 mA., 6.3 v. 5 a. 25'9 365-0-365 v. 150 mA. 8/9 300-0-300 v. 80 mA. 5 v. 3 a. 8/11 278-0-278 v. 100 mA. 8/9 300-0-300 v. 150 mA. 8/9 300-0-300 v. 150 mA. 8/9 300-0-300 v. 150 mA. 29'9 40 v. C.T. 150 mA. 4 v. 6 a., 6.3 v. 6 a., 6.3 v. 6 a., 4 v. 3 a., 4 v. 3 a., 5 v. 2 a. 22'9 EX-GOVT AUTO. TRANSFORMERS 15-10-5-0-195-215-235 v. 500 watts. 27'9 Double wound 0-200-220-240 v. to 10-0- 276-205-315 v. 1,000 watts. 69'6 Double wound 0-230 v. to 0-230 v. in steps 61'10 v. 1500 watts. 69'6 Carriage on any of above 5/- extra. 69'6 250 mA. 10 H. 100 ohms. 14'9 250 mA. 10 H. 100 ohms. 14'9 250 mA. 10 H. 100 ohms. Poticalised. 3/11 50 mA. 50 H. 1,000 ohms. Poticalised. 3/11 50 mA. 51 H. 100 ohms. Poticalised. 3/11 50 mA. 510 H. 2/9 LT. type 1 amp. 2/9 16 s.w.g. aluminium, receiver type. 4/9 18 s.w.g. undrilled aluminium anuplifier type 12in. × 8in. × 24in. 5/3 18in. × 8in. × 24in. 5/3 18
 10K, 20K, Preset type, 1/9 each. AMMETERS. Moving coil. G.E.C. 0-5 amps., 2in. scale, 11/9. EX-GOVT. E.H.T. SMOOTHING CONDENSERS 25 mfd, 4,000 v. Blocks. 4/9 5 mfd, 2,500 v. Blocks. 3/3 1 mfd, plus 1 mfd 8,000 v., large blocks (common negative isolated). 9/6 1.5 mfd. 4,000 v. Blocks. 5/9 EX-GOVT. ACCUMULATORS with non-spill vents Unused and guaranteed. 2 v. 16 A.H., 5/9 each EX-GOVT. BLOCK PAPER CONDENSERS 2 mfd. 300 v. 1/9 4 mfd. 2,000 v. 6/9 4 mfd. 500 v. 2/9 6-6 mfd. 450 v. 5/9 4 mfd. 1,000 v 4/3 8-8 mfd. 500 v 7/9 4 mfd. 1,000 v 4/3 8-8 mfd. 500 v 7/9 4 mfd. 1,000 v 4/3 8-8 mfd. 500 v 7/9 4 mfd. 1,000 v 4/3 15 mfd. 500 v 7/9 4 mfd. 1,000 v 4/3 8-8 mfd. 500 v 7/9 4 mfd. 1,000 v 4/3 8-8 mfd. 500 v 7/9 4 mfd. 1,000 v 4/3 8-8 mfd. 500 v 7/9 4 mfd. 1,000 v 4/3 8-8 mfd. 500 v 5/9 4 mfd. 1,000 v 4/3 8-8 mfd. 500 v 5/9 4 mfd. 1,000 v 4/3 8-8 mfd. 500 v 5/9 4 mfd. 1,000 v 4/3 8-8 mfd. 500 v 5/9 4 mfd. 1,000 v 4/3 8-8 mfd. 500 v 5/9 4 mfd. 1,000 v 4/3 8-8 mfd. 500 v 5/9 4 mfd. 1,000 v 4/3 8-8 mfd. 500 v 5/9 4 mfd. 1,000 v 4/3 8-8 mfd. 500 v 5/9 4 mfd. 1,000 v 4/3 8-8 mfd. 500 v 5/9 4 mfd. 1,000 v 4/3 8-8 mfd. 500 v 5/9 4 mfd. 1,000 v 4/3 8-8 mfd. 500 v 5/9 4 mfd. 1,000 v 4/3 8-8 mfd. 500 v 5/9 4 mfd. 1,000 v 4/3 8-8 mfd. 500 v 5/9 4 mfd. 1,000 v 4/3 8-8 mfd. 500 v 5/9 4 mfd. 1,000 v 4/3 8-8 mfd. 500 v 7/9 5 mfd. 1,000 ohms, 23/9. SPECIAL 0FFER. Mains Trans. 200-250 v. 50 c/s. Primary. Secs. 300-0-300 v. 150 mA. 63. v. 4 a. 5 v. 3 a. half shrouded drop through, 21/9. HEAVY DUTY BATTERY CHARGER For normal 200/250 v. A.C. mains. Muaranteed 12 mont	A design of a 4-stage, 3-valve 200-250 v. A.C. Mains receiver with selenium rectifier. For inclusion in either of cabinets illustrated above. It consists of a variable Mu high gain H.F. stage followed by a low distortion grid detector triode. The next stage is a further triode amplifier with tone correction by negative feedback. Finally connected double triode giving ample output at an extraordinary low level of distortion. Point-to- point-wiring diagrams, instructions, and parts list, 2/6. This receiver can be built for a maximum of £4/19/6 including cabinet. P.M. SPEAKERS. All 2-3 ohms. 64in. Plessey, 16/9. 8in. Plessey, 15/9. 10in. R.A. 26/9. 10in. Plessey, 18/6. 10in. Rola with Trans., 29/6. R.S.C. BATTERY CHARGER KITS. For mains input 200-250 v. 50 c/s. To charge 6 v. accumu- lator at 2 amps, 25/9. To charge 6 v. or 12 v. battery at 4 a., 49/9. ABOVE KITS CONSIST OF BLACK CRACKLE LOUVRED STELE LOUVRED STELE CASE, MAINS TRANS- FORMER, FULL WAVE METAL RECTIFIER, FUSES, FUSE-HOLDERS AND CIRCUIT. Any type assembled and tested for 6/9 extra. R.S.C. 6 v. or 12 v. BATTERY CHARGER For normal A.C. mains input 200-230-250 v. 50 c/s. Selector panel for 6 v. or 12 v. charging. Variable charge rate of up to 4 AMP8. Fused, and with 5 amp meter. Well ventilated metal case	16-18-20 v. 35 a. 79'6 460 v. 200 mA., 6.3 v. 5 a. 25'9 365-0-365 v. 150 mA. 8/9 300-0-300 v. 80 mA. 5 v. 3 a. 8/11 278-0-278 v. 100 mA. 8/9 300-0-300 v. 150 mA. 8/9 300-0-300 v. 150 mA. 8/9 300-0-300 v. 150 mA. 29'9 40 v. C.T. 150 mA. 4 v. 6 a., 6.3 v. 6 a., 6.3 v. 6 a., 4 v. 3 a., 4 v. 3 a., 5 v. 2 a. 22'9 EX-GOVT AUTO. TRANSFORMERS 15-10-5-0-195-215-235 v. 500 watts. 27'9 Double wound 0-200-220-240 v. to 10-0- 276-205-315 v. 1,000 watts. 69'6 Double wound 0-230 v. to 0-230 v. in steps 61'10 v. 1500 watts. 69'6 Carriage on any of above 5/- extra. 69'6 250 mA. 10 H. 100 ohms. 14'9 250 mA. 10 H. 100 ohms. 14'9 250 mA. 10 H. 100 ohms. Poticalised. 3/11 50 mA. 50 H. 1,000 ohms. Poticalised. 3/11 50 mA. 51 H. 100 ohms. Poticalised. 3/11 50 mA. 510 H. 2/9 LT. type 1 amp. 2/9 16 s.w.g. aluminium, receiver type. 4/9 18 s.w.g. undrilled aluminium anuplifier type 12in. × 8in. × 24in. 5/3 18in. × 8in. × 24in. 5/3 18
 10K, 20K, Preset type, 1/9 each. AMMETERS. Moving coil. G.E.C. 0-5 amps., 2in. scale, 11/9. EX-GOVT. E.H.T. SMOOTHING CONDENSERS 25 mfd, 4,000 v. Blocks. 4/9 5 mfd, 2,500 v. Blocks. 3/3 1 mfd, plus 1 mfd 8,000 v., large blocks (common negative isolated). 9/6 1.5 mfd. 4,000 v. Blocks. 5/9 EX-GOVT. ACCUMULATORS with non-spill vents Unused and guaranteed. 2 v. 16 A.H., 5/9 each EX-GOVT. BLOCK PAPER CONDENSERS 2 mfd. 300 v. 1/9 4 mfd. 2,000 v. 6/9 4 mfd. 500 v. 2/9 6-6 mfd. 450 v. 5/9 4 mfd. 1,000 v 4/3 8-8 mfd. 500 v 7/9 4 mfd. 1,000 v 4/3 8-8 mfd. 500 v 7/9 4 mfd. 1,000 v 4/3 8-8 mfd. 500 v 7/9 4 mfd. 1,000 v 4/3 15 mfd. 500 v 7/9 4 mfd. 1,000 v 4/3 8-8 mfd. 500 v 7/9 4 mfd. 1,000 v 4/3 8-8 mfd. 500 v 7/9 4 mfd. 1,000 v 4/3 8-8 mfd. 500 v 7/9 4 mfd. 1,000 v 4/3 8-8 mfd. 500 v 5/9 4 mfd. 1,000 v 4/3 8-8 mfd. 500 v 5/9 4 mfd. 1,000 v 4/3 8-8 mfd. 500 v 5/9 4 mfd. 1,000 v 4/3 8-8 mfd. 500 v 5/9 4 mfd. 1,000 v 4/3 8-8 mfd. 500 v 5/9 4 mfd. 1,000 v 4/3 8-8 mfd. 500 v 5/9 4 mfd. 1,000 v 4/3 8-8 mfd. 500 v 5/9 4 mfd. 1,000 v 4/3 8-8 mfd. 500 v 5/9 4 mfd. 1,000 v 4/3 8-8 mfd. 500 v 5/9 4 mfd. 1,000 v 4/3 8-8 mfd. 500 v 5/9 4 mfd. 1,000 v 4/3 8-8 mfd. 500 v 5/9 4 mfd. 1,000 v 4/3 8-8 mfd. 500 v 5/9 4 mfd. 1,000 v 4/3 8-8 mfd. 500 v 5/9 4 mfd. 1,000 v 4/3 8-8 mfd. 500 v 5/9 4 mfd. 1,000 v 4/3 8-8 mfd. 500 v 7/9 5 mfd. 1,000 ohms, 23/9. SPECIAL 0FFER. Mains Trans. 200-250 v. 50 c/s. Primary. Secs. 300-0-300 v. 150 mA. 63. v. 4 a. 5 v. 3 a. half shrouded drop through, 21/9. HEAVY DUTY BATTERY CHARGER For normal 200/250 v. A.C. mains. Muaranteed 12 mont	A design of a 4-stage, 3-valve 200-250 v. A.C. Mains receiver with selenium rectifier. For inclusion in either of cabinets illustrated above. It consists of a variable Mu high gain H.F. stage followed by a low distortion grid detector triode. The next stage is a further triode amplifier with tone correction by negative feedback. Finally connected double triode giving ample output at an extraordinary low level of distortion. Point-to- point-wiring diagrams, instructions, and parts list, 2/6. This receiver can be built for a maximum of £4/19/6 including cabinet. P.M. SPEAKERS. All 2-3 ohms. 64in. Plessey, 16/9. 8in. Plessey, 15/9. 10in. R.A. 26/9. 10in. Plessey, 18/6. 10in. Rola with Trans., 29/6. R.S.C. BATTERY CHARGER KITS. For mains input 200-250 v. 50 c/s. To charge 6 v. accumu- lator at 2 amps, 25/9. To charge 6 v. or 12 v. battery at 4 a., 49/9. ABOVE KITS CONSIST OF BLACK CRACKLE LOUVRED STELE LOUVRED STELE CASE, MAINS TRANS- FORMER, FULL WAVE METAL RECTIFIER, FUSES, FUSE-HOLDERS AND CIRCUIT. Any type assembled and tested for 6/9 extra. R.S.C. 6 v. or 12 v. BATTERY CHARGER For normal A.C. mains input 200-230-250 v. 50 c/s. Selector panel for 6 v. or 12 v. charging. Variable charge rate of up to 4 AMP8. Fused, and with 5 amp meter. Well ventilated metal case	16-18-20 v. 35 a. 79'6 460 v. 200 mA., 6.3 v. 5 a. 25'9 365-0-365 v. 150 mA. 8/9 300-0-300 v. 80 mA. 5 v. 3 a. 8/11 278-0-278 v. 100 mA. 8/9 300-0-300 v. 150 mA. 8/9 300-0-300 v. 150 mA. 8/9 300-0-300 v. 150 mA. 29'9 40 v. C.T. 150 mA. 4 v. 6 a., 6.3 v. 6 a., 6.3 v. 6 a., 4 v. 3 a., 4 v. 3 a., 5 v. 2 a. 22'9 EX-GOVT AUTO. TRANSFORMERS 15-10-5-0-195-215-235 v. 500 watts. 27'9 Double wound 0-200-220-240 v. to 10-0- 276-205-315 v. 1,000 watts. 69'6 Double wound 0-230 v. to 0-230 v. in steps 61'10 v. 1500 watts. 69'6 Carriage on any of above 5/- extra. 69'6 250 mA. 10 H. 100 ohms. 14'9 250 mA. 10 H. 100 ohms. 14'9 250 mA. 10 H. 100 ohms. Poticalised. 3/11 50 mA. 50 H. 1,000 ohms. Poticalised. 3/11 50 mA. 51 H. 100 ohms. Poticalised. 3/11 50 mA. 510 H. 2/9 LT. type 1 amp. 2/9 16 s.w.g. aluminium, receiver type. 4/9 18 s.w.g. undrilled aluminium anuplifier type 12in. × 8in. × 24in. 5/3 18in. × 8in. × 24in. 5/3 18
 10K, 20K, Preset type, 1/9 each. AMMETERS. Moving coil. G.E.C. 0-5 amps., 2in. scale, 11/9. EX-GOVT. E.H.T. SMOOTHING CONDENSERS 25 mfd, 4,000 v. Blocks	A design of a 4-stage, 3-valve 200-250 v. A.C. Mains receiver with selenium rectifier. For inclusion in either of cabinets illustrated above. It consists of a variable Mu high gain H.F. stage followed by a low distortion grid detector triode. The next stage is a further triode amplifier with tone correction by negative feedback. Finally connected double triode giving ample output at an extraordinary low level of distortion. Point-to- point-wiring diagrams, instructions, and parts list, 2/6. This receiver can be built for a maximum of £4/19/6 including cabinet. P.M. SPEAKERS. All 2-3 ohms. 64in. Plessey, 16/9. 8in. Plessey, 15/9. 10in. R.A. 26/9. 10in. Plessey, 18/6. 10in. Rola with Trans., 29/6. R.S.C. BATTERY CHARGER KITS. For mains input 200-250 v. 50 c/s. To charge 6 v. accumu- lator at 2 amps, 25/9. To charge 6 v. or 12 v. battery at 4 a., 49/9. ABOVE KITS CONSIST OF BLACK CRACKLE LOUVRED STELE LOUVRED STELE CASE, MAINS TRANS- FORMER, FULL WAVE METAL RECTIFIER, FUSES, FUSE-HOLDERS AND CIRCUIT. Any type assembled and tested for 6/9 extra. R.S.C. 6 v. or 12 v. BATTERY CHARGER For normal A.C. mains input 200-230-250 v. 50 c/s. Selector panel for 6 v. or 12 v. charging. Variable charge rate of up to 4 AMP8. Fused, and with 5 amp meter. Well ventilated metal case	$ \begin{array}{c c c c c c c c c c c c c c c c c c c $

R.S.C. HIGH FIDELITY watt AMPLIFIER 25 Hum level 66 D.B. down. Certified

A NEW DESIGN FOR 1955 HIGH GAIN "PUSH PULL OUT-PUT." BUILT-IN PRE-AMP. TONE CONTROL STAGES. INCLUDES valves, sectionally wound output 7 valves, sectionally would output transformer, block paper reservoir condenser, and reliable small com-ponents. AN INPUT OF ONLY 20 millivolts IS REQUIRED FOR FULL OUTPUT. THIS MEANS THAT ANY TYPE OF MICRO-PUONE OF DECK UP DE CUITA DE PHONE OR PICK-UP IS SUITABLE. Two separate inputs controlled by separate volume controls allow simul-taneous use of "Mike" and Gram., or Tape and Radio, etc., etc. Individual controls for Bass and Treble "lift" and "cut." Six

negative feedback loops giving total of 24 D.B. Frequency response ± 3 D.B. 30-20,000 c/s. H.P. Terms now available on request. Cover as illustrated if required, price 17/6 extra.

W.B. "STENTORIAN" High fidelity P.M. Bpeaker, HF1012, 10 watts, 15 ohm (or 3 ohm) speech coll. Where a really good quality speaker at a low price is required we highly recommend this unit with an amazing performance. highly res £3/13/6

MICROPHONES. Crystal, hand or Desk type, good quality Acce, 50/-. Stand type with base and adjustable stand, £8/19/6. Both suitable for use with our amplifiers.


F SEGSET 3-SFEED MIXER AUTOCHANGERS with high impedance magnetic pick-up with due point alloy stylus for long playing or standard records. (Will piga 2,000 records before replacement stylus required.) Brand new, cartoned, guaranteed. Limited stocks at only 10 gns, plus 5/- carr. PLESSEY 3-SPEED MIXER AUTOCHANGERS with

H.M.V. LONG PLAYING RECORD TURNTABLE COMPLETE WITH CRYSTAL PICK-UP (SAP-PHIRESTYLUS). Speed 33 r.p.m. BRAND NEW, CARTONED. Only £3/19/6 (approx. half price). Carr. 5/- (For 200-250 v. A.C. Maina).

R.S.C. 4-5 WATT HIGH GAIN AMPLIFIER TYPE A5



A highly sensitive 4-valve quality amplifier for the home, small club, etc. Only 50 millivoits input is required for full unput to that it is suitable for use with the latest high-radiativy pick-up heads, in addition to all other types of pick-ups and practically all miles. Separate Bass and Troble controls are provided. These give full long playing record equalisation. Hum level is negligible being 71 D.B. down. 15 D.B. of negative feedback is used. H.T. of $300 \cdot v.25$ m.A. and L.T. of 6.3 v. 1.5 a. Is available for the supply of a Badio Peeder Unit, or Tape Deck preamplifier. For A.C. mains input of 200-230-250 v. 50 of. Chassis is not alive. Kit is complete in every detail and includes fully punched chassis (with basepilate), with green cracket finish, and point-to-point wiring diagrams and instructions. Exceptional value at only $g_{\rm M}(15)^{c}$, or assembled ready for use 25/- extra, plus 3/6 car.

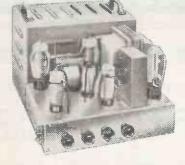

to-point wiring diagrams, are supplied. EXTRA HIGH SENSITIVITY, HIGHEST QUALITY for **9 Cms**. plus carr. 7/6.

total

R.S.C. A3 10 WATT "PUSH PULL" HIGH FIDELITY AMPLIFIER.

harmonic distortion

OR LARGE HALLS,

GARDEN PARTIES,

complete in every detail.

0.35% measured at 10 watts. Com-

parable with the very best designs. SUITABLE FOR SMALL HOMES

HALLS, etc., etc. For ELECTRONIC ORGAN OR GUITAR. For STANDARD OR LONG PLAYING RECORDS. Size approx. 12in. × 10in. × 9in. Weight 20 lb. Power

consumption 175 watts. Outputs for 3 and 15 ohms speakers. The kit is complete in every detail. Chassis is

For mains input 200-250 v, 50 c/s. Complete kit of parts including point-to-point wiring diagrams and instructions. Amplifier can be used with any type of feeder unit or pick up. This is not A.G.(D.C. with "'live" chassis but A.C. only with 400-400 v. Trans. Output is for 2-3 ohm speaker. (We can supply a very suitable 10m, unit by Roin at 27/b). The amplifier can be supplied ready for use for 25/- extra. Full descriptive leaftet, 6d. With Self Contained Pre-amplifier and Tone Control.



A PUSH PULL 3-4 WATT HIGH-GAIN AMPLIFIER FOR £2/19/6

R.S.C. MASTER INTERCOMM. UNIT, with provision for up to 4" Listen Talk Back Units" individually switched. A high gain amplifier enables speech and other sounds comanating from the rooms containing remote control units to be heard at the master control. The unit is in kit form and point-to-point wirting diagrams are supplied. A walnut veneered wood or Brown Bakelite cabinet is included. Mains input is 200-250 v. 50 c/s. H.T. line 300 v. CHASHS IS NOT "ALIVE." Ideal for use as "Baby Alarm" "Sound amplification 4 wats. Price only £5/19/6. "Listen — Talk Back Unit" in bakelite or walnut veneered cabinet. on be supplied at 35/- each. Full descriptive leasist 9d The Master Unit can be supplied assembled and tested for 30/- extra.

PERSONAL SET BATTERY SUPERSEDER KIT.



Battery Ellininator. Com-plete with case. For 4 valve receivers requiring 90 v. 10 mA. and 1.4 v. 250 mA. Fully smoothed. Outputs from normal. 200-250 v. 50 c/s mains. Price with circuit, 35/9. Or ready for use, 42/6. Size of units 51-4-14in.

All parts for an " All Dry "

BATTERY SET CONVERTER KIT. All parts for con verting any type of battery receiver to all mains AC. 200-250 v. 50 e/s. Kit will supply fully smoothed H.T. of 120 v. 90 v. or 60 v. at up to 40 mA., and tuly smoothed L.T. of 2 v. at 0.4 a. to 1 a. Price complete with circuit and instruc-tions only 428/9. Supplied ready for use for 8/9 extra.

H.T. ELIMINATOR AND TRICKLE CHARGER KIT with case, Mains input 200-250 v. Output 120 v. 40 mA, and 2 v. h a. Price with circuit, 29/6. Or in working order, 37/6.



This amplifier, whist having sufficient output to fill a small, and, is the ideal amplifier for the quality enthusiast who now so that though the average isteing level is less than one wast it is necessary, for the very highest quality, to bave an output of at least ten times this figure in order to obtain completely distortionless reproduction of sudden load sounds. The layout of the components has been planned to give the very maximum of performance with the minimum of constructional effort. Large safety factors in every com-ponent, A.C. and H.T. fuses, punched chassis with baseplate, screened input plugs, valves, and with casy-to-follow polat-to-point wiring diagrams. The only things necessary to build this superb instrument are a soldering iron, serve-driver and pliers, everything else is supplied down to the hast nut and bolt. Two independent volume controls so that programmes can be mixed together if desired, such as microphone announce-ments superimposed on a musical programme, or two independently controlled microphones, or even just gramo-phone/raili, facility evit broken so that hyper resort equalisa-tion for uncorrected pick-ups. They are also provided so that be user can atter the tonal values to suit his personal taste and surroundings. Because of the large negative eetback employed the output transformer can be so designed that it provides all the specified power even with targe variations of loudspeaker impedance. Terminals are provided for 3 ohm and 15 ohm loudspeakers.

H.T. and L.T. available for the supply of a Radio Feeder Unit.

nt. Six Negative Feedback Loops. Maximum input for full output 130 millivolts. Frequency response ± 3 DB 50-20,000 cycles. Negligible hum and distortion. For A.C. mains input 200/230/250 v. 50 c/s.

COMPLETE Kit of Parts, £7/19/8 (carriage 5/-..

Supplied assembled and tested for 45/- extra.

H.P. TERMS AVAILABLE ON ASSEMBLED UNITS

FOUR STAGE RADIO FEEDER UNIT. Design of a H16H FIDELITY, L. and M. wave T.R.F. Unit with self-contained heater supply and thorough H.T. decoupling. Only 200-400 v. 16-20 m.A. H.T. required from main amplifier. Three valves and Low Distortion Germanium Diede Detector. Flat toppel response char-acteristic. Loaded H.F. colis. Two variable Mu controlled H.F. stages. 3 gang condenser tuning. Cathode follower output stage. Switch position for Gram. and Gram. input and output sockets. Performance comparable with the best in Feeder Units. For A.C. mains '00-220-230 v. operation, Size 11-6-7, int. Illustration, full set of easy-to-follow wiring diagrams and instructions and individually priced parts list 2/6. This unit can be built for only £3/15/-including Dial and Drive Knobs and every item required.

of only

CLUBS.

DANCE

WIRELESS WORLD

FEBRUARY, 1955

A newly

7/6 9/6 1/3

11/3 15/-23/6



TAPE RECORDING EQUIPMENT. We can offer a well constructed cabinet hand-somely finished in grey or brown restme made specifically to take Truvox and Wearite Tape Decks. Measures 221a, x 14ia. x 94in. deep. Completely portable, shows attractive speaker grilleat one end, to take 6in. apeaker. This cabinet is especially made to take in addition to the above decks, the very latest ELIFOC tape amplifier (Mk. V) at £16/16/-. Price of cabinet 79/6, plus P. and P. £16/16/-. P. and P.

N.B.—We can supply from stock the latest Truvox and Wearite Tape Decks at 22 gainess and ± 235 respectively. Reduction of 20/- on cabine if purchased at the same time as either of these tape decks! same time as either of these tape decks!) N.B.—We can also supply from stock the astounding Truvox Radio Jack. Overall length 4 jin. \times 2 jin. \times 2 jin. Just plug into your tape recorder or any suitable amplifier to receive direct reception from any two local stations, or to make recordings (in the case of tape recorder) of any of the programmes radiated by the selected stations. Price only 23/8/4 tax paid, or send stamp for Illustrated lealet.

We also have in stock Elpico new tape dek at £19/19/-. Truvox Tape Amplifier type "C" at £16/16/- especially for use with Truvox Deck. Truvox Telephone adaptor at £2/2/-; also Dictation Attachment at £4/4/-.

x4/4/-SPECIAL PURCHASE. We can offer strictly limited supply of "Limpet" telephone tape recorder attachments. Simply stick rubber santion pad to base of telephone and plug into Input-jack on your tape recorder. This automatically records incoming telephone conversation. Our price absolutely complete conversation. Our price absolutely complete with lead and jack plug. 17/8 only, port free

Menufacturer's surplus high-quality crystal microphone for hand or stand use. A few only at 50/-, post free. We also have a limited number of Ronatte Type ZA crystal microphone inserts at 23/6.

ROTHERMEL DA1 Crystal Microphone Inserts. Brand new, 7/6 each, plus 9d. Inserts. P. & P.

P. & P. MISTER SPECIALI We have a limited quantity of alteraif electrical thermometers brand new, by Weston. 21n. moving coll meter, flush square fitting. These meters have a luminous scale graduated 40-140 degrees centigrade, but the full scale deflec-tion is approximately 150 microampsi Price 12/6 each only, plus 1/- F. & P. VIER ATOR PACK. Brand new, he Mallory.


VIBRATOR PACK. Brand new, by Mallory. 12 volt input, 150 v. 40 mA. output. Com-plete with synchronous vibrator 27/6. plete with synchronous vibrator 27(8, R1155A RECEIVERS guaranteed service-able in original packing cases. 27(19/6, Fully assembled Power Pack and output stage, to jug straight into B1155 for A.O. 200/250 volts at 79/6. We have a few brand new R1155A at 51(17(16/6, also in original packing cases—Deduct 10/- if purchasing either receiver together with power pack. Plus 10/- packing and carriage.

Flus 10/- packing and carriage. **B1124 RECEIVER UNIT.** Coverage 30-40 Mc/s. Including 6 valves—3 type 9D2, 1 each, 8D2, 15D2 and 4D1—Six valve-screening cans, 24 ceramic triumers, 6 ceramic valve holders, resistors, condensers, 1.F.T.'s coils, etc. In very good condition, a bargain at 16/6 each only, plus 3/6 packing and package. netage

BECEIVER TYPE 25/73. section of TR1196). St (The receiver **BECEIVER TYPE** 25/73. (The receiver section of TR1196). Supplied complete with full data for conversion to 3-wave-superhet receiver. Unit is complete with 6 valves 2-EF39, 2-EF36, FK32 and EBC33, also standard 1.F.T.*3 463 Kc/s. Price 27/6 plus 2/6 P. & P. **TR1196** TRANSMITTER PORTION. We

TR1196 TRANSMITTER PORTION. We can also supply the transmitter portion of the above reseiver incorporating valves, EL32, EF50, CV501. Type 600 relay, transformer, colls, switches, etc. Limited quantity at 12/6 only, plus 2/6 P. & P. 24 VOLT ROTARY CONVERTER. Input 24 v. D.C. Output 200/250 v. A.C. 100 watte. Complete in black steel box 18jin. x 11jin. x 6jin. Weight approx. 30 lb. Completely smoothed, incorporates Sodium Lamp transformer. Brand new, 92/6.

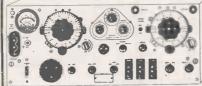SPECIAL PURCHASE OF EX-NEW ZEALAND ARMY TRANSMITTER/RECEIVERS.



ranges up to 35 miles on morse and 30 miles speech, iu average country. Considerably greater ranges may be obtained by the use of horizontai aerials. H.T. is supplied by a built-in vibrator pack, requiring 12 volk input. Valve line-up, 24%601, 74076, 6X60 and 6Q7GT, 465 Kc/s. L.F.T.'s. Bet weighs 384 lb. Measurements 22 lin. × 10 lin. × 10 lin. These units are brand new, and price is 26/1396 only, plus 10/6 packing and carriage. This price includes fully illustrated 60 page instruction booklet including full circuit dia-grame, suggested aerials, fault-finding etc. An unrepeatable bargain 1

REMOTE CONTROL UNITS

These units originally intended for use with the above transmitter/receiver, when Inter-connected can be used as ordinary telephones or for practice more-working one-to-ones. Complete in handsome steel case, can be operated by ordinary torch battery. Has built-in more key and buzzer unit. Frice for each is 15/-. Suitable headphones can be supplied at 7(6 plus 5/- for carbon hand microphone. The whole plus 2/6 P. & P. Each unit includes full operating instructions—and is brand new.

N.B. Certain other spares are available and your specific enquiries will receive our very prompt attention.

			METERS	
F.S.D.	Size	Type	Fitting	Price
50 mlcroamp	D.C. 2in.	M.C.	R.P.	50/-
100 microamp	D.C. 24in.	M.C.	F.B	45/-
500 microamp	D.C. 2in.	M.C.	R.P.	13/6
500 microamp	D.C. 2in.	M.C.	F.R	18/6
1 mA.	D.C. 21a.	M.C.	F. 8q.	17/6
1 mA.	D.C. 2in.	M.C	F. Sq. (scale calib. 1.5 kV.)	15/-
1 mA.	D.C. 24in.	M.C.	F.R	22 6
1 mA.	D.C. 211n.	M.C.	Desk Type	276
5 mA.	D.C. 2in.	M.C.	F. 8q.	76
10 mA.	D.C. 21in.	M.C.	R.P	81-
10 mA.	D.C. 241n.	M.C.	F.R	10/-
15 mA.	D.C. 2in.	M.C.	F.R	7/8
20 mA.	D.C. 2in.	M.C.	F.R	7/8
50 mA.	D.C. 2in.	M.C.	F. Sq	8/6
150 mA.	D.C. 21n.	M.C.	F. 8q.	78
200 mA.	D.C. 21in.	M.C.	R.P	10/-
1 amp.	R.F. 24in.	Thermo	R.P.	10/-
3 amp.	R.F. 2in.	Thermo	F. Bq	6/-
6 amp.	R.F. 24in.	Thermo	F.B	7/6
20 amp.	D.C. 2in.		R.P. (with shunt)	10/6
25 amp.	D.C. 21in.	M.I.	F.R.	6/6
30 amp.	D.C. 21in.	M.I.	F.R	12/6
15 volt	A.C. 2)in.	M.O.	F.R	10/-
20 volt amp.	D.C. 21n.	M.C.	F. Sq	7/6
15-0-15 volt	D.C. 211n.	M.C.	F.R	17/6
150 volt	D.C. 2in.	M.C.	F.R	15/-
			ving Coll. Thermo = Thermo-couple.	
F. Sq. = Flush	Square. F.R.	 Fiush 	Round. M.I Moving Iron.	
METER RECTI	FIERS. 1 mA	. by G.E.	C., at 8/6, also 5 mA. by Westinghouse at 8/6	3.

EX-W.D. GATHODE RAY TUBES. Guaranteed full picture. VCR97 at 40/-. VCR517C at 35/-. Also VCR139A--Ideal for oscilloscope 21in. screen at 35/-. We also have VCR97 with slight cut-off, very suitable for oscilloscope, testing purposes, etc., at 15/- only. All these tubes are brand new, in original packing, and tested before despatch. Please add 2/6 packing and carriage for any of the above tubes.

216 packing and carriage for any of the acove dues. AMERICAN TRIPLET MULTI-RANGE TESTMETER. Housed in strong wooden case with carrying handle. Case size 10in. × 8jin. × 6in. deep. Meter 4in. rectangular type, with 50 microamp basic movement. Knife-edge needle. Incorporating the following ranges, 0-6000 volt D.C. 7 ranges, 20,000 ohms per volt. 0-6000 volt D.G. 7 ranges 1000 ohms per volt 0-6000 valts A.C. 7 ranges, -100 ohms per volt. 0-12 amps. D.C. 7 ranges. 0-60 megohm resistance, 3 ranges. -12 to -7 decides, 7 ranges. 0-600 volt und meter. 7 ranges, 1000 ohms per volt. Exch instrument is in nearly new condition, has been thoroughly overhauled, and is supplied ready working, complete with battery and test prods. Price £11/19/6 plus 3/6 p. & p. H.P. Terms available.

TRIPLETT RECTANGULAR METER. 4in. scale. Knik-edge needle. Basic movement 0-100 micro-amps. At present graduated for multi-range meter. Brand new in scaled cartons, 90/- plus 2/- p. & p.

STOP PRESS ! 1 ! 21" BOUND FLUSH MOUNTING METER by WESTON, blank scale ready for re-engraving, FSD 650 micro-amps, brand new 27/6 only.

TYPE 201 MK. II.— Built into substantial steel cabinet mounted on casily removable resiltent mountings. The instrument is fully trop-icalised. Two wave-bands. 2-4 Mc/s. (75-150 metres) 4-8 Mc/s. (75

41

1 10 666. STEEL INSTRUMENT BOXES 111 Crackle finished in Brown or Black. Com-plete with chassis and insulated front panel. Measures 0 jin.x7jin.x6jin. at 7/6, plus 2/6 P. & P. BRAND NEW C.R. TUBES. By leading manufacturer. 14KP4A. Latest type 14in. rectangular 6.3 v. heater. 12-14 BAAAD NEW C.R. TUBES, ---By leading manufacturer, 14KP4A, Lakest type 14in. rectangular 6.3 v. heater, 12-14 Kv. in original sealed cartons. Limited quantity only at £13(19)6. SORE VI PERSONAL CALLERS ONLY!!!

 CHARGER TRANSFORMERS. Input 230 v.

 6/12 v. 1 a.
 9/9

 6/12 v. 2 a.
 11/9

 6/12 v. 4 a.
 17/6

 6/12 v. 6 a.
 25/

AMERICAN INDICATOR UNIT TYPE BC529A. Brand new incorporating 3in. tube 3BP1; with mu-incetashield, 2-68N7G7, 2-6B6G7, 6X5G, 2X2, 6G6G, 9 potentio-maters 24 v. aerial switch motor, trans-former, and a host of small components. The whole unit which measures only \$din. x \$Jin. x 13jin.is brand new, enclosed in black teackie box, and can be supplied at 65/-plus 5/-p. & p. 6-volt VIBRATOR PACK. Ex-W.D. 6-volt liput, output 140 v. 30 mA. Fully smoothed and rectified, incorporating Wearite 6 volt 4 plu vibrator type NSB6. Unit size ouly 6jin. x 5in. x 2jin. Price 16/- plus 1/6 P. & P. New condition. FOWEE BACK TYPE 301. For 200/230 v. AMERICAN INDICATOR UNIT

1/6 P. & P. New condition.
POWEE PACK TYPE 301. For 200/250 v.
A.C. 50 cycle. Black case size 84m. x 64m. smp. (for 650, 31 v. at .3 amps. Could be adapted for R1155, etc. Price, complete, 27/6 only plus 2/6
P. Wireg. All near-additional statements of the statement of the

etc. Price, complete, 27/6 only plus 2/6 P. & P. A Barxain.
R. F. ONTES. All new condition and complete Case size 9/1n. X 7/1n. X 51n.
Type 25.--0-30 Mc/s, 15/-Switched Tuning.
Type 25.--0-50 Mc/s, 19/6. Switched Tuning.
Type 27.--05-56 Mc/s, 45/-. Variable Tuolng. Type 27.--05-56 Mc/s, Variable Tuolng.
Type 28.--05-56 Mc/s, 45/-. Variable Tuolng.
Type 28.--05-56 Mc/s. Variable Tuolng.
Type 28.--05-56 Mc/s.
Variable Tuolng.
Type 28.--05-56 Mc/s.
Variable Tuolng.
Type 28.--05-56 Mc/s.
Variable Tuolng.
Type 28.--05-56 Mc/s.
Variable Tuolng.
Type 28.--05-56 Mc/s.
Variable
Tuols.
Tuols.
The wood of the second se


carriage and packing. BATTERY CHARGER 6/12 v. 4 A. Attrac-tive grey and red metal case. Fused in and out. Full charge or half charge. Complete with heavy duty crocodile clips. Not Ex-Gort. Full guaranteed. £4/19/6.

BEADFHORES. Brand new, ex-Gort., by BEADFHORES. Brand new, ex-Gort., by 8. G. Brown. Type CLR. Low resistance, 7/8 per pair. Type CHR high resistance, 12/6 per pair. We can also supply very special brand new American ex-Gort. light-weight high resistance phones by Trimm as 15/- per pair.

CO-AXIAL CABLE. Standard 80 ohms brown, stranded centre, conductor, 6d. per yard only! Not Govt. surplus. Min. 12 yds " VOLTALYTE " 2 volt 60 amp. ACCUMU-LATORS MULTI-PLATE Type in celluloid containers. Size 3in. x 3in. x 4 \$\frac{1}{2}\$ high at 9/6 each plus 2/- P. & P. Or 3 for 28/6, post

BRANDENBURG E.H.T. UNITS. 6-9 kV., 6 gns.; 13-16 kV., 9 gns.; 6-9 kV. coll, 39/-; 10-15 kV. coll, 55/-. Wiring diagram supniled

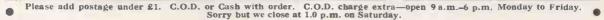No. 38 TRANSMITTER/RECEIVER. WALKIE-TALKIE. Range approx. 5 miles. Coverage 7.4-9 mc/s. The set only, complete with valves at 30/-, in very good condition.



134



musical in-struments. in-Maximum output I watts. Nega 5

Current of the second tax paid.

HIRE PURCHASE We are pleased to announce advan-tageous hire purchase facilities on any single item over £5. Ask for details, mentioning what you are interested in.

LATEST 3-SPEED AUTO-CHANGER, long arm model complete with C. and D. high fidelity heads. Limited quantity at £17/10/-plus 5/- P. & P. H.P. terms available.

plus 5)- P. & P. H.P. terms available. ANOTHER GRAM UNIT BARGAIN 1 Collaro RC/531-8 record auto-changer for 78 r.p.m. Brand new complete with separate plug-in magnetic head. Our price £3/8/- only, plus 6/- p. & p. Collaro AC/514-Single record playing units for 78 r.p.m. Brand new in sealed cartons, with separate plug-in magnetic head. Our price £4/12/6 plus 3/- p. & p.



"CONTEMPORARY." A well-made Cabinet In light wood, made especially to blend with this type of furniture. The motor board is uncut, and will accommodate most Radio Chassis and Auto-chance units. Ryle: 301n. x 151n. x 291n. high. Price £8/15/-, plus 10/- post and packing. DECCA LIGHTWIENCE

DECCA LIGHTWEIGHT PICKUPS. Com-plete with either standard or L.P. Crystal Cartridge lasts. Complete with Rest and Tracking instructions, 32/8 plus 1/8 P. & P. Also their very itatest type, as above, but with tura-over head 47/6 only 1 Plus 1/8 P. & P.



Carrying cases in black leatherette finish Carrying cases in black leatherette finish. An extremely well-made case with chrome locks and corner places for extra strength. This cabinet will house any 12in. Hi-FI speaker, but can be put to a number of uses. Front panel and 11d are removable, and the cabinet is packed in a strong cardboard container for carrying purposes. Bize: 184:n. X. 104:n. X. 164:n. high, 55/-, plus 5/- post and packing.





THE "SUPERIOR" FOUR KIT. Our new four-vaive receiver. A.C. maine, 200/250 v. M. and Long Waves. As with our very successful "Economy Four" all required components are supplied. Walveline-up: 26807, 6X60T and 6V60T. Chassis ready drilled. Cabinst size, 10jin. × 10jn. wide. Maximum depth at base, jin., tapering to 3jin at top. Sloping front. Very attractively finished in light walnut and peach. Each component brand new and tested prior to packing. Complete instruction booklet with practical and theoretical diagrams is provided. Booklet available at 1/6, post trike or complete kit, 26(9/6)/11 Please add 2/ packing and carriage. If preferred me-orisingpicable and brandet wavechange witch, dial, pointer, dram pulley, drive spinale, drive spring and knobs, at 45/-, pins 2/6 packing and carriage. M.B.--Our Kits are even supplied with sufficient solder for the job.

THE "SUPERIOR " FOUR KIT. Our

N.B.-.OUT Kits are even emplied with sufficient solder for the job. THE R.C. GRAM REPLACEMENT CHASSIS HIT To meet the very great demand for this type of receiver, we have produced this unit. For Long, Medium, and Short Waves. Valve line-up: 6KS Prequency changer, 6K7 LF. Amplifer, 6Q7 List Audio, Detector and AV.C. 6V Output, 6X5 Pull-wave recti-ther. For A.C. main 200/250 volts. 4 watts provision for gram. Attractive liltuninsked black, red, green and gold dial for hori-zontal tuning. Four controls are: Tuning, (M/M/8/Gram. Vol./on/61, Tone (veriable); Chassis size: 13Ha, × 6Hm, × 24Im. Dial tize: 10hn, × 6Hm, As 24Im. Dial tize: 10hr, velia, ascimative the simplified by the use of a SG/8. LF. Coll prox., and high-grade drop-through half-shrouded Mains Transformer, with voltage adjuster panel. This chassis, can easily be assembled in one verning. Illustrated pamphit with full assembly instructions, practical and theoreti-cal witing diagrams and itemised price list. 1/6, post free. The main litems for this receiver can be supplied separately, as under. Prilde chassis, complete with valve-holders, A/E panel, FU panel, tuning condenser and, 38/6, tax paid. Pair of 465 Kc/8. LF. Transformers, 9/8 pair. Half shrouded drop through Mains Transformer, 22/6. LF to total cost of ALL litems purchased separately, assembled dial and thrive at 39/6. 3 waveband coil pack with gram position, 38/6 (as x paid. Pair of 465 Kc/8. LF. Transformers, 9/8 pair. Half shrouded drop through Mains Transformer, 22/8. LF to total cost of ALL litem purchased separately is nearly 10, but we shall be pleased to supply all the required components right down to the sheat nut and bolt, at a special inclusive price of 32/8/3, plus 2/8 packing and postage. A set of four small brown and cream engraved knobs to sult is savaltable at 1/2 each knob. This chassis is a professional job in every respecial and sub seemaled, in very limited quantities at 28/11/6, plus 6/- cariage and packing.

THE "ECONOMY FOUR " T.R.F. KIT

THE "ECONOMY FOUR "T.R.F. KIT A three valve plus metal rectifier rectirer. A.C. mains 200/280 v. Medlum and Long waves. We can supply all requirer components in R.K. We wave as apply all requirer components in R.K. We by G. Chasterady driller - Cushues size 12 in. long five Grant seady driller - Cushues size 12 in. long five first seady driller - Cushues size 12 in. long five first seady driller - Cushues size 12 in. long five first seady driller - Cushues size 12 in. long five first seady driller - Cushues size 12 in. long for the seady driller - Cushues size 12 in. long for the seady driller - Cushues size 12 in. long for the seady driller - Cushues size 12 in. long for the seady driller - Cushues size 12 in. long state 1 at our abop premises 1. We proudly claim that our fully illustrated instruction booklet is the most comprehensive available for this type of receiver—Booklet available at 1/8 post free. The is allowed if kit is purchased later—Please, 2/8 packing and carriage for complete kit.



DULCI RADIO/RADIOGRAM CHASSIS

DULCI RADIO/RADIOGRAM CHASSIS This very popular range of superior chassis can be supplied from stock. We will gladly demonstrate any to personal callers. All incorporate latest type valves 6B26, 6BA6, etc. Plywheel tuning, negative feedback over entire audio section. Engraved knobs-stone position for Radio and Gram. All are built on chassis sele lijin. x 7 shin. high. All A.C. 100/110 and 200/220 v.-Dial size Shin. x 4jin. for horizontal tuning. Attractive appearance: Model B.3. Long, Medium, Short Waves (5 valves). Cash Price £12/12/-, H.P. Terms, £314/- deposit, 12 months at 12/82. Model B.3. Double Feature Fush Pull and R.F. Stage (7 valves). Cash Price £18/18/-Model B.4. (Mcdium, Long and Pour Short Waveshads). Cash Price £18/18/-Bridel B.5, plus Pms Hull Stage (6 valves). Cash Price £18/18/-Model B.6., (Mcdium, Long and Pour Short Waveshads). Cash Price £18/18/-Bridel B.6, plus Pms Hull Stage (6 valves). Cash Price £19/18/-. H.F. Terms £3/13/- deposit, 12 months at £19/21. Model B.6. plus Pms Hull Stage (6 valves). Cash Price £19/18/-. H.F. Terms £3/13/- deposit, 12 months at £19/21. Model B.6. plus Pms Hull Stage (6 valves). Cash Price £19/18/-. H.F. Terms £3/19/-deposit, 12 months at £19/22. Model B.6. plus Pms Hull Stage (6 valves). Cash Price £19/18/-. H.F. Terms £4/13/- deposit, 12 months at £19/21. Model B.6. Punple Feature Punch Pull Punc B F. Stage (7) Model B.6. Punple Seature Punch Pull Punch B F. Stage (7) Model B.6. Punple Seature Punch Pull Punch B F. Stage (7) Model B.6. Punple Seature Punch Pull Punch B F. Stage (7) Model B.6. Punple Seature Punch Pull Punch B F. Stage (7) Model B.6. Punple Seature Punch Pull Punch B F. Stage (7) Model B.6. Punple Seature Punch Pull Punch B F. Stage (7) Model B.6. Punple Seature Punch Pull Punch B F. Stage (7) Model B.6. Punple Seature Punch Pull Punch B F. Stage (7) Model B.6. Punple Seature Punch Pull Punch B F. Stage (7) Model B.6. Punple Seature Punch Punch

£18/18/-. £1/6/9. Model R.s.

 $\underline{21}(6)6$. Model B.6, Double Festure Push Pull Plus R.F. Stage (7 valves). Cash Price 22 gns. H.P. Terms $\underline{25}/15/6$ deposit, 12 months at $\underline{21}/12/6$. All chassis fully guaranteed 12 months. Please include 7/6 packing, carriage and insurance. Illustrated leaftet available. Suitable speakers available. Ask for speaker list.



RAMBLER MAINS UNIT I--At last we are able to oner our special mains units kit for uning our popular all-dry "Rambler" on A.C. Mains. Complete, kit, which when assembled fits snugly into battery compartment, can be sop-plied at 47/6, plus 1/6 packing and postage. Frice Includes all required components, and full assembly in-structions. structions.

THE R.E.P. ONE-VALVE BATTERY RECEIVER EIT. Simple one-valve all-dry battery receiver for headphones, easily built in one evening. All required components built in one evening. All required components Including headphones. can be supplied at inclusive cost of 42/- plus 2/- p. & Oper-ated by Ever-Ready Bild type battery available at 7/9. Full assembly details the NEW R.C. HIGH-FIDELITY AM-PLIFIER. P.P. 6V6 output. Freq. 25-tion. Provision for Freeder Unit Max. UNDISTORTED OUTPUT 64 watch. Frie 14 gras, subs 7/6. NOW AVAILABLE --Kit of Parts, complete with fully illus 20-carriage. Illusfrated booklet available separately at 1/6. Attractive metai cover, now available, with built-in carrying hamile

carriage. Illustrated booklet available separately at 1/6. Attractive metal cover, now available, with built-in carrying hamile STUFCA SINGLE SPEED RECORD FLAT-STUFCA SINGLE SPEED RECORD FLAT-Hig DESKS 32A. Easily converted to either the DESKS 32A. Easily converted to either relation of L.P. Price with one crystal cartridge of either type, 24/19/6; or with both cartridges, 55/19/6. Plus 57-P. & P. C.I. 10 WATT AMPLUTIERS. Measure 12in. x 6in. x 6in. Vaire line up-6AM6. 6AM6, 65N7, 524, 6768 Puah Pull. Separ-ate Bass and Treble controls, multi-rablo output transformer for 3 ohm or 15 johm speakers. Fully guaranteed11 £10/15/-plus 5/-P.P. We also have in stock-Connolsseur, 3-speed motors, pick-ups. Pick-ups and heads by Garrard, Decca, Collaro, 26:5-MPLIFIER BARGAIN. "THE EMPRESS" Super quality push-pull 4 valve 4 walt amplifier. Ideal for record or mulo tuner reproduction. Measures only 71in. x 71in. x 31in. Vaire line-up EL42, EL42, E244, CO3, for use with one or two 3-olum speakers. Price £7/7/- plus 3/-P. & Por PORTABLE GABINETS, Manufarturer surplus. Well made brown regine_covered, will take any standard single player will bottom clearance of 31n. The size closed 15in. x 13in. x 5jin. Total aize closed 15in. x 13in. x 5jin. X 5jin. X 5jin. X 5jin.



136

WIRELESS WORLD

FEBRUARY, 1955



R.F. UNIT(Ex-BC800). 800.) Can be con-verted for use on 2 metres or 70 cm. Con-tains (3) 956 valves, etc. Brand new in tropical packed cartons.

PRICE 17/6

Post Paid

RECEIVER UNIT Ex-TRI143A. Suitable for conversion to 2 metres and F.M. Wrotham. Circuit diagram free. Price, less valves, 9/-, post

paid. TRANSMITTER UNIT Ex-TRI143A. Suitable for conversion to 2 metres. Circuit diagram and coil conversion details supplied free.

Price, less valves, 5/-, post paid. AMPLIFIER UNIT Ex-TRI143A. A 3-stage transformer coupled amplifier. Push-pull VT52's output to modulate push-pull VT501's. Circuit diagram free, 4/6, post paid. INSPECTION LAMP. 2 pole S.B.C. Holder with 6ft. spring loaded lead in case 3in. × 3in. × 4in. with on-off switch on front panel. Price 6/- post paid.

6/-, post paid. TOGGLE SWITCHES. 5 amp. 1-way recessed panel type, 1/-, post

paid. **SLOW MOTION DRIVE.** Reduction 40-1. Excellent for S.W. operation, Price 3/6, post paid. **INDICATORS.** Aircraft undercarriage type with 4 miniature E.S. holders in bakelite case. Price 1/6, post paid. **CRYSTALS** by R.C.A. 100 kc/s. 3-pin mounting. Price 12/6,

post paid. POINTER KNOBS. In. radius, fitting in. spindle. Black bakelite;

3 for 2/6, post paid. BLOCK CONDENSERS. 8 mfd. 600 v. W. tropical. 750 v. w., normal. Price 5/-, post 1/-. 23-WAY SWITCH. Make before break. Incorporating a single pole 3-way Yaxley type switch. Price 3/6, post paid. HEATER TRANSFORMERS. 6.3 v., 1.5 A. output, 230 v. input.

TANNOY P.A. SPEAKERS. 8 watt, 6in. diam. P.M. with re-entrant baffle mounted in wooden cabinet with line OP trans. Military surplus Cat. No. ZB11565. Price 20/-, post paid. Enquiries invited for quantities. HEADBAND TORCHES.

for quantities. HEADBAND TORCHES. (Leave both hands free for awkward jobs). M.E.S. holder, bulb and reflector, headband with rubber pad, battery box with 4ft. cable; all wired ready for use. PRICE 4/-, post 1/-. Needs 4½ v. battery Vidor VOO17 or similar standard battery. VALVES. 6SN7gt 6/9. (Ex.new surplus units) 807 (American) 8/6. Disc-Sealed Triode (Lighthouse tube GL446A (19E4) Boxed, New, 25/-, All post paid. ALL RADIO MINDED AMATEURS should send for full details of the "Medresco" Deaf-Aids which can be converted into many interesting devices including: 1. A Crystal Receiver incorporating a Germanium Diode. Circuit requires no alteration to present wiring. 2. An O-V-2 (detector with two stages of amplification) receiver. (Circuits for these two supplied free.) "Medresco" Units, all in perfect working order (checked by experts), complete with Crystal Microphone and incorpora-ting three miniature valves, are a wonderful bargain at only 27/6 each. Postage 1/-. See our full-page advertisement in "Wireless World," January issue (Page 126). We have a well organised Post Order Dept. giving brombt service.

We have a well organised Post Order Dept. giving prompt service. OTE:-Orders and Enquiries to Dept. 'W.' PROOPS BROS. LTD., 52, Tottenham Court Road, W.I. NOTE :

Shop hours : 9 a.m. to 6 p.m. Thursday : 9 a.m. ta 1 p.m. OPEN ALL DAY SATURDAY.

LANgham 0141.




23, HIGH STREET, ACTON, W.3 (Opposite Granada Cinema)



COMPLETELY BUILT SIGNAL GENERATOR

Coverage 120 Kc/s-320 Kc/s., 300 Kc/s-900 Kc/s., 900 Kc/s., 2.75 Mc/s., 2.75 Mc/s.-8.5 Mc/s., 8.5 Mc/s.-25 Mc/s., 17 Mc/s.-50 Mc/s., 25.5 Mc/s.-75 Mc/s. Metal case 10 x 62 x 44in. Size of scale 64 x 34in., 2 valves and rectifier. A.C mains 230-250 v. Internal modulation of 400 c.p.s. to a depth of 30 per cent., modulated or unmodulated, R.F. output continuously variable 100 milli volts. C.W. and mod. switch, variable A.F. output and moving coil output meter. Black crackle finished case and white panel. Accuracy plus or minus 2%. £4/19/6, or 34/- deposit and 3 monthly payments 25/-. P. & P. 4/- extra.

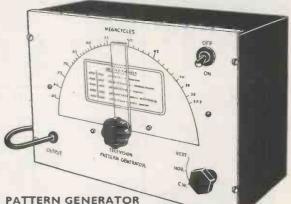

40-70 Mc/s. direct calibration, checks frame

and line time base, frequency and linearity,

vision channel alignment, sound channel and sound rejection circuits and vision channel band width. Silver plated coils, black crackle finished case 10 x 67 x 47 in, and white front panel. A.C. mains 200/250 volts. This instrument will align any T.V. receiver, accuracy plus or minus 1%. Cash price £3/19/6 or 29/- deposit and 3 monthly payments of £1. P. & P. 4/extra

EXPORT & TRADE ENOURIES INVITED

(N.B. Post and packing charges stated apply to British Isles only.)

 \star

Both generators guaranteed for 12 months ÷

MAINS TRANSFORMER3 Primary, 200-250 v. P. & P. 2/-. 300-0-300, 100 mA., 6 v. 3 amp., 5 v. 2 amp., 22/6

Drop thro' 350-0-350 v. 70 mA., 6 v. 2.5 amp., 5 v. 2 amp., 14/6.

Drop thro' 250-0-250 v. 80 mA., 6 v. 3 amp., 5 v. 2 amp., 14/6.

280-0-280, drop through, 80 mA., 6 v. 3 amp., 5 v. 2 amp., 14/6.

250-0-250 80 mA., 6 v. 4 amp., 14/-.

Drop thro' 270-0-270, 80 mA., 6 v. 3 amp., 4 v. 1.5 amp., 13/6.

Drop thro' 270-0-270 60 mA., 6 v. 3 amp., 11/6.

250 v. 350 mA., 6.3 v. 4 a., twice 2 v. 2 a. 19/6

Auto-trans. Qnput 200/250, H.T. 500 v. 250 mA., 6 v 4 a., twice, 2 v. 2 a., 19/6.

250-0-250, 60 mA., 6.3 v. 1.5 a. 0-5-6.3 v. 1.5 a., 10/6.

Auto Trans. Input 200/250. H.T. 350 v. 350 mA. Separate L.T. 6.3 v. 7 a., 6.3 v. 1¹/₄ amp., 5 v. 3 amp., 25/-. P. & P. 3/-.

Heater Transformer. Pri. 230/250 v. 6 v. 1; amp., 6/-: 2 v. 2; amp., 5/-. Pri. 200/250. Secondary 9 v. 3.5 amp., 6.3 v. 3 amp., 12/8.

Pri 200 v. Sec. 500-0-500 and 500-0-500 250 mA. both windings. 4 v. 3 amp. 4 v. 3 amp., 39/6. P. & P. 5/-.

Mains Transformer, fully impregnated, input 210, 220, 230 and 240. Sec. 600-6500, 275 mA., and 290 v. at 30 mA., complete with separate heater transformer. Input 216, 220, 230, 240. Sec. 6.3 v. 2 amp. three times, 0, 4. 6.3 v. at 3 amp. and 5 v. 3 amp., 45/-p, & P. δf -

Mains Trausformer, fully impregnated. Input 210, 220, 230, 240. Sec. 350-0-350 100 mA., with separate heater trans-former. Pri. 210, 220, 230, 240. Sec. 6.3 v. 2 amp., 6.3 v. 3 amp., 4 v. 6 amp., and 5 v. 2 amp., 30/~. P. & P. 5/-.

MAINS TRANSFORMERS. chassis mounting, feet and voltage panel. Primaries 200/250.

350-0-350 75 mA. 6.3 v. 3 a. tap 4 v. 6.3 v. 1 a., 13/6.

500-0-500 125 mA. 4 v: C.T. 4 a., 4 v. C.T. 4 a., 4 v. C.T. 2.5 a., 27/6.

500-0-500 250 mA. 4 v. C.T. 5 a. 4 v. C.T. 5 a. 4 v. C.T. 4 a., 39/6.

9in. T.V. Cabinet, front in contrasting walnut vencers, size 16iln. long. 11jin. high. by 18jin. wide. Complete with two pieces expanded aluminium in gold, 12×9in. and 5in. speaker battle and chassis, 20/-, post paid.

61in. M.E. Speaker, 1,000 ohm field.

R. & A. T.V. energised 6 in. speak with O.P. traus., field coil 175 ohn 9/6. P. & P. 2/6.

R. & A. 61in. M.E. speaker with O.P. trans., field 440 ohms 10/6. P. & P. 2/6.

Volume Controls. Long spindle less switch, 50K, 500K, 1 meg., 2/6 each. P. & P. 3d. each.

Volume Controls. Long spindle and switch, $\frac{1}{2}$, $\frac{1}{2}$, 1 and 2 meg., $\frac{4}{4}$ each; 10K and 50K, $\frac{3}{3}$ (8 each. $\frac{1}{2}$ and 1 meg., long spindle double pole switch, minia-ture, $\frac{5}{2}$. P. & P. 3d. each.

Trimmers. 5-40 pf., 5d. 10-110, 10-250, 10-450 pf., 10d.

Twin-Gang .0005 Tuning Condenser, 5/-. With trimmers, 7/6.

Twin Gang, .0005, with feet, size 31×3×111., 6/6.

3-gang .0005, with feet, size 42×3× 1\$in., 7/6.

T.V Coils, moulded former, iron-cored wound for re-winding purposes only. Ali-can 1]×13in., 1/- each, 2 iron-core Ali-can 2]×3in., 1/6 each.

Tred Metal Rectifier 250 v. 150 mA. 6/6

Metal Rectifier 230 v. 45 mA., 6/-. Metal Rectifier. RM2, 125 v., 100 mA. 3/6

Mains Droppers. 0.3 amp., 460 ohms, tapped 280 and 410, 1/6; 0.2 amp., 717 ohms, tapped at 100 ohms, vitreous, 1/6; 0.3 amps, 950 ohms, tapped 700 and 825, 2/6; 0.2 amp., 1,000 ohms vitreous, tapped 2/6; vitreous, 0.3 amp., 700 tapped 680, 640, 600, 3/6. P. & P. on each 34.



23 HIGH STREET (Uxbridge Road) ACTON, W.3. Telephone : ACOrn 5901.

Hours of Business :

Wednesday 9-1 p.m. Other days 9-4.30 p.m. Saturday 9-5 p.m.

T.V. CONVERTER for the new commercial stations complete with 2 valves. Frequency:-can be set to any channel within the 186-196 Mc/s. band. I.F.:-will work into any existing T.V. receiver designed to work between 42-68 Mc/s. Sensitivity:-10 Mu/v with any normal T.V. set. Input:-arranged for 300 ohm feeder. 80 ohm feeder can be used with slight reduction in R.F. gain. Circuit EF80 as local oscillator. ECC8I as R.F. amplifier and mixer. The gain of the first stage, grounded grid R.F. AMPLIFIER 10 db. Required power supply of 200 v. D.C. at 25 mA. 6.3 v. A.C. at 0.6 amp. Input filter ensuring complete freedom from unwanted signals. 2 simple adjustments only. £2/10/-, P. & P. 2/6.

USED 12in. TUBE: aluminized, heater cathode-short, 10KV max. 2 v. heater complete with line and E.H.T. transformer 9 KV with ferrocart core, line and width control, EY51 rec. winding frame O.P. scan coils and 12in. perspect secutcheon. $g\beta(17)6.$ P. & P. 76.

GENERAL PURPOSE 3-IN-1 MAINS TRANSFORMER. Input 200/250. Sec. 250 v. 350 mA., 6.3 v. 4 amp. twice, 2 v. 2 amp. 500 v., 350 mA., 6.3 v. 4 amp. twice, 2 v. 2 amp. Auto-transformer, 110,250 v., 250 w.tt, 19/6. F. & F. 3/6.

HIGE-IMPEDANCE PLASTIC RECORDING TAPE, by famous manufacturer. 600ft. on aluminium spool, 8/-, 1,200ft. on aluminium spool, 17/6, post paid.



kit, 4/-;

Cyldon 5 channel T.V. Tuner, uses EF80 and 12AT7 less valves, 12/6, post paid. Radiogram Chassis, 6 valve A.C./D.C. 3 wave-band superhet 195-255 v., 19-49, 200-550 and 1,000-2,000 metres, I.F. 470 Kc. size of chassis $13 \times 6 \mid \times 2 \mid n$, size of scale $7 \nmid \times 3 \mid n$ valve line-up 10C1, 10F9, 10L011, U404 and 10P14. Twin mains filter input, 2 dial lights and 8 ln. P.M., 28/17/6. F. & P. 5/-.

CR100 Coil packs in first-class condition less oscillator section, complete with 4-gang tuning condenser. 19/6. P. & P. 3/6. CR100 465 Kc. I.F.s, types 3, 4 and 5 and F.B.O., new condition, 7/6 each. 465 Kc. Xtal for CR100, 12/6. 4-gang tuning condenser for CR100, 9/6.

CONSTRUCTOR'S PARCEL, medium and long wave A.C. mains 230/250 2-valve plus metal rectifier, comprising chassis $10_1 \times 4_2 \times 1_1$ in., 2 wave-band scale, tuning condenser, wave-change switch, volume control, heater trans., metal rectifier, 2 valves and wholders, smoothing and blas condensers, resistors and small condensers, and medium and long wave coil, litz wound, 22/6. P. & P. 2/6 extra. Circuit and point-to-point, 1/3.

CONSTRUCTOR'S PARCEL comprising chassis $12\frac{1}{4} \times 8 \times 2\frac{1}{4}$ in , cad. plated, 16 gauge, yh., LF. and trans. cut-outs, back-plate, 2 supporting brack-ets, 3 wave-band scale, new wavelength stations names. Size of scale 11 $\frac{1}{4} \times 4\frac{1}{4}$ in, drive sp., drum, 2 pulleys, par. for 465 LF.s., tvin gang, 16 × 16 mid. 350 wkg., mains pars of 465 LF.s., tvin gang, 16 × 16 mid. 350 wkg., mains pars, 5 × 2 amp, 5 × 2 amp, 5 × 2 amp, 5 × 2 amp, 5 × 2 amp. 39/6.



Battery charger, input 230/250 v. output 6 and 12 volt 1 amp. Black crackle finished case size 10 x 6 x 4in. Incorporating metal rectifier, mains on-off switch, and output switch. 21/-, P. & P. 3/-.

OUTPUT TRANSFORMERS. Standard type 5,000 ohms imp., 4/9; 42-1 with extra feed-back windings, 4/3. Miniature 42-1, 3/3. Multi-matio 3,500, 7,000 and 14,000. 5/8. 10-watt push-pull, 6V6 matching, 7/-, 90-1 3 ohm speech coll, 6/6. PUSH-BACK CONNECTING WIRE. Doz. yds., 1/6. Post paid.

STANDARD WAVE-CHANGE SWITCHES 4-pole 3-way, 1/9; 5-pole 3-way, 1/9; 3-pole 3-way 1/9; 9-pole 3-way, 3/6; Miniature type, long spindle 3-pole 4-way, 4-pole 3-way and 4-pole 2-way, 2/6 each. 2- pole 11-way twin water 5/-; 1-pole 12-way single water 5/-. P. & P. 3d.

POTATO AND VEGETABLE PEELER

By famous manufacturer. To suit models A200 and A700, Capacity $4\frac{1}{2}$ by, complete with water pump. All aluminium construction, white stove-enamelled finish. Originally intended for adaption on an electric food-mixer, can be easily converted for hand operation. 39(6. P. & P. 3)-.

PERSONAL SHOPPERS ONLY. Enlarger, 17/6; 12in., 27/6. Sin Germanium Crystal Diode, 1/6, post

Used 9in. Tube, with ion burn, 17/6. post paid

Line O.P. Transformer in aluminium can mounted in rubber, 12/6.

Crystal Set, medium and long wave, in plastic cabinet, 16/-.

Headphones, per pair 8/-.

21-.

Speaker Matching Unit on aluminium chassis, 3-15 ohms reversible, 12/6. Line and E.H.T. Transformer, 14 Kv., using ferrocart core, complete with line aud width control, and corona shields U37 rectifier winding, 35/-.

Line and E.H.T. Transformer, 9 Kv. using ferrocart core, complete with built-in line and width control. Mounted on small all-chassis. Overall size 44×14in. EV51 rec. winding, 27/6. Scan Colls, low line low impedance frame, complete with frame trans-former, to match above, 27/6. P. & P.

Line and E.H.T. Transformer, 9 Kv., ferrocart core, EY51 heater winding, complete with scan coils and frame output transformer, and line and width control, £2/5/-. P. & P. 3/-.

As above, but complete with line and frame blocking transformers, 5 Henry 260 mA. choke, 100 mfd. and 160 mfd. 350 wkg. 380 mA. A.C. ripple. £2/19/6 P. & P. 3/-.

Valve Holders, moulded octal Mazda and laoctal, 7d. each. Paxolin, octal Mazda and loctal, 4d. each. Moulded B7G, B8A and B9A, 7d. each. B7G moulded and B9A with screening can each.

22 mfd., 350 wkg	2/- 4/- 1/3 3/6 4/6 5/9 3/9
32 x 32 mfd., 350 wkg	4/-
	6/6 11d.
250 mfd., 12 v. wkg	1/-
6 mfd., 500 wkg., wire ends 8 mfd., 500 v. wkg., wire ends 8 mfd., 350 v. wkg., tag ends 9 mfd., 25 v. wkg., wire ends	3/3 2/6 1/6 1/9
100 mfd., 350 wkg	4/-
100 mfd., 450 v. wkg., 280 mA.,	
	3/11
160 mfd., 350 v. wkg., 280 m.A. A.C. ripple. del + 16 mfd., 350 wkg. i 64 + 16 mfd., 350 wkg. 50 mfd., 180 wkg. i mfd., 180 wkg. j mfd., 150 wkg. 04 + 100 mfd., 280 wkg. 04 + 100 mfd., 280 wkg. 26 + 32 mfd. min. 275 wkg. 00 mfd., 50 wkg.	4/6 9/6 3/3 1/9 1/6 1/6 7/6 114 4/- 1/9

Miniature wire ends moulded, 100 pf., 500 pf., and .001, ea... 7d.

T.V. Filter in lightly tinted Perspex slze 131 × 11 × 3/16in. 4/6.

Combined 12in, mask and escutcheon in lightly tinted Persper. New aspect, edged in brown. Fits on front of cabinet, 12/6. As above for 15in. tube, 17/6.

Frame Oscillator Blocking Trans.,4/6. Line Osc. Blocking Trans., 4/6.

Tube Mounting Bracket, size 9} x 45in 12in. tube clamps, 2/-.

Int. tube Change, g/*. CHOKES: 2-20 Hen. 150 mA., 15/-. P. & P. 3/-. 6 Hen., 275 mA., 15/-. P. & P. 3/-. 100 Hen., 40 mA., 15/-. P. & P. 3/-. 2 henry 150 mA. 3/8; 250 mA. 10 heary 10/6; 5 henry 250 mA. 60 ohma., 8/8.

P.M. Foons Unit for any 9 or 12in. tube except Mazda 12in., with Vernier adjustment, 15/~.

P.M. Focus Unit for Mazda, 12in., with Vernier adjustment, 17/6.

Wide Angle P.M. Focus Units, Vernier adj. state tube, 25/-.

Energised Focus Coil, low resistance mounting bracket, 17/6. Ion Traps for Mullard or English Electric

Ion Traps for Mullard or English Electric tubes, 5/., post paid. Standard 465 Kc. Iron-cored I.F.s. 4×14×11m., per pr., 7/6. Wearite standard, iron-cored, 465 Kc. I.F.s 3×14×11m., per pr., 9/6. Iron-Cored 465 Kc. Whistle Fliter, 2/6. 465 KG, MIDGET I.F.s. Q.120 size 1/in.long, iln. wide, fin. deep by very famous manufacterer. Pre-aligned adjustable iron-dust cores, per pair 12/6.

WIRELESS WORLD



GEE RADIO

TYPE) ELENIUM METAL RECTIFIERS specification from milliamps to a All:work fully guaranteed. Very vited for large or small quantites. from milliamps to amps., H/W., F/B., or three-phase. ly guaranteed. Very good delivery. Your enquiries in-

RECTIFIERS, PENCIL TYPES, S.T.C. K/3 SERIES. I milliamp for H.T. and E.H.T. APPLICATION. EX-STOCK.

Volts	Туре	Price	Volts	Туре	Price	Ve	lts	Туре	Price
248	K3/10	3/10	1000	K3/40	7/6	25	50	K3/100	14/8
:375	K3/15	4/5	1140.	K3/45	8/2	30	80	K3/120	16/8
500	K3/20	5/1	1260	K3/50	8/8	36	00	K3/140	19/3
. 655 -	K3/25	.5/8	1500	K3/60	9/8	41	00	K3/160	21/6
	K3/30	6/	1780	K3/70	11/-	46	60	K3/180	24/3
885	K3/35	6/10	2030	K3/80	12/4	51	50	K3/200	26/-

885 K3/35 6/10 2030 K3/80 12/4 5150 K3/200 26/-RECTIFIERS FOR LT. APPLICATION--F/B. S.T.C. TYPE: 12 v. D.C. at 1 amp., 6/6; 12 v. D.C. at 2 amp., 10/6, p.p. 94. 12 v. D.C. at 3 amp., 15/-, p.p. 1/-; 21 v. D.C. at 4 amp., 17/6, p.p. 91, 12 v. D.C. at 6 amp., 25/-, p.p. 2/-; 12 v. D.C. at 1 amp., 40/-, p.p. 2/6; 24 v. D.C. at 1 amp., 12/6; 24 v. D.C. at 2 amp., 21/-, p.p. 1/-; 24 v. D.C. at 4 amp., 30/-, p.p. 2/-; 24 v. D.C. at 2 amp., 21/-, p.p. 1/-; 24 v. D.C. at 4 amp., 30/-, p.p. 2/-; 24 v. D.C. at 6 amp., 35/-, p.p. 2/6. VALVE: TESTER, TYPE 4. 200/230 v. A.C. input. Ex-Govt., in good condition, with descriptive book containing circuit diagram of instrument and how to test valves from 1.4 v. to 40 v. With valve-holders for, Brit., 4, 5, 7 pin and Octal, U.S., 5 and 7 v., With valve-stantial wooden case. Price £7/19/6, carriage 10/- extra. WESTON ALL-PURPOSE A.C./D.C. TEST METER, MODEL

stantial wooden case. Price £7/19/6, carriage 10/- extra. WESTON ALL-PURPOSE A.C./D.C. TEST METER, MODEL E.865. 1,000 ohms per volt. New and unused, complete with leads and batteries. £8 each only, pp. 3/6. WESTON BATTERY OSCILLATOR, MODEL E.692. TYPE 2. Also new and unused. Coverage 100 kc/s-26 Mc/s. Audio output approx. 400 c/s. Available at the ridiculously low price of only £5/19/6, p.p. 4/6. (Oscillator complete with instruction booklet.)

p.p. 4.6. (Oscillator complete with instruction booklet.) TELE-THONE L/SPEAKER No. 2 (By Vitavoz). This is H/Duty 6jn. P.M. 15 ohm S/C. with 600 ohm built-in Link Transformer, housed in strong wooden case. £1/8/-, carriage 5/-. VITAVOX PRESSURE UNITS. Heavy duty, P.M. 20 watts. Brand new. £4/9/6, carriage 5/-.

TRUVOX I2in. 3 OHMS P.M. SPEAKERS. Brand new and boxed, 39/6, post paid.

ROTARY CONVERTERS. 12 v. D.C. input 230 v. A.C. output, at 100 watts. Brand new. £4/17/6. Ditto, 24 v., same price, carriage 7/6.

100 watts. Brand new. £4/17/6. Ditto, 24 v., same price, carriage 7/6. ÁN/APA-L CATHODE RAY INDICATOR AMPLIFIER UNIT. Complete, comprising OF. 3BPI C.R.T., 7-6SN7GT, 1-6H6, 1-6G6, 1-2X2, 1-6X5, valves. Bargain value, £4/19/6, plus 10/- carriage. TUNING UNITS (EX-U.S.A.). Types available, T.U.6B., T.U.9B. T.U.26B. Good condition, soiled cases, 19/6 each, p.p. 3/-. AC/DC SUPPLY UNIT. (S.T.C. SELENIUM RECTIFIER). Complete with Mains Isolation transformer, fixed and housed in strong metal cabinet. 250 v. A.C. to 200-220 v. D.C. @ 3-4 amps. Ready to use for £6/10/- only, carriage 10/-.

CAR RADIO TRANSFORMERS. 12 v. ex-Philco, 300 v. H.T. at 90 mA. Brand new and unused. Only 12/6, p.p. 2/-. 12 v. Oak Vibrators, 4-pin U.X. base, new and unused, 7/6 each., p.p. 9d.

TRANSFORMERS PUSH-PULL OUTPUT (BY PARMEKO) 25 watts for 6L6 valves. To match, 3, 8 and 15 ohms. New and unused. 29/6, p.p. 2/6.

R.1155 COMMUNICATION RECEIVERS. Individually tested and despatched in good working order. Cases slightly soiled. £8/19/6, carriage 10/-

RECEIVER TYPE 109 in good condition. Freq. range 15-68 metres continuous, designed to operate on 6 v. battery. Limited quantity only £417/6, plus 10/- carriage.

 EA(7)0, plus 10/2 carriage.
 N.D. 38 WALKIE-TALKIE TRANS-RECEIVER, in good condition (ress) external accessories), 35/-, p.p. 2/6.
 HALF MILE OF TWIN DON "8" TELEPHONE WIRE, Brand new, on wooden drums, £2/12/6 per drum, carriage 10/-, England only.

HIGH-VOLTAGE TRANSMITTING CONDENSERS. Hank Pot Type (25 pf. 8, kV.) (40 pf. 9,6 kV.) (500 pf. 15 kV.) (600 pf. 9,6 kV.) (750 pf. 15 kV.). Any type, 3/6 each, p.p. 1/-. TELESCOPIC AERIALS. Min. length 12in. Max. length 48in. Suitable for car radio aerials. 8/6 each, p.p. 9d.

CATHODE RAY TUBES.

CATHODE RAY TUBES. Type 38P1, 3in., new and unused, with base and screen, 42/6, p.p. 2/-. Type VCR 138 (ECR35). 34in. With screen and base, in new and unused condition, 42/6, p.p. 2/-. Type VCR97, 6in., ex-equip.. in good order, 20/-, p.p. 3/6. VCRX131, Iin. C.R.T., new and in perfect condition. Miniscope re-placement tube, etc., 35/-, p.p. 1/-. Type CV 1526, 24in., 4 v. filament, 3,000 v. anode, complete with base and mu-metal screen, 20/-, p.p. 2/6.

PHOTO ELECTRIC MULTIPLIER CELLS. TYPE 931A. 62/10/-, p.p. 1/-. Also 931A complete on chassis with multiplier network and two 932 valve-holders, etc., 63/10/-, p.p. 2/-. 4 CORE 3/036 "METAFLEX." V.I.R. in flexible tubing, 1§th dia. overall, 2/6 per yard., p.p. 2/6.

SIEMENS HIGH SPEED RELAYS. Twin 1,000 ohm coils, perfect

condition, 15/-, p.p. 6d. 2,000 OHMS H/R. EAR PIECES, 3/6 each, p.p. 9d.

BATTERIES M.T./L.T. Heavy duty layer type. 150 v. tapped at 87 v. H.T. L.T. 41 v. Perfect condition. Size 91 n. x 41 n. x 41 n. 87 v. H.T. L. 4/6, p.p. 2/6.

15 LITTLE NEWPORT ST., LONDON, W.C.2. _GERrard 6794/1453_

125 Tottenham Court Road, W.I. Tel.: EUS 4982

All orders and enquiries to our Edgware Road branch, please. This is open all day Satu-day

WIRELESS WORLD



AMERICAN "WESTON" OSCILLA-TOR TYPE 776. 50 Kc/s-30 Mc/s. Modulated or unmodulated R.F. output. 400 cycle audio output. Max. output voltage 100 m/volts. 110 volt A.C. operation, £12/10/- each.

METERS. All brand new and boxed, 0-1 mla., desk type, fitted with 2¼in. scale. Res. 100 ohms, 25/-; 0-1 m/a., 2¼in. round, F/M., M/coil, 7/6; 0-10 m/a., 2¼in. round, F/M., M/coil, 10/-; 0-100 m/a., 2¼in. round, F/M., M/coil, 10/-; 0-100 m/a., 2¼in. round, F/M., M/coil, 10/-; 0-100 m/a., 2¼in. round, F/M., M/coil, 10/-; 0-200 m/a., 2¼in. round, F/M., M/coil, 10/-; 0-200 m/a., 2¼in. square, F/M., M/coil, 7/6; 0-200 m/a., 2¼in. round, F/M., M/coil, 10/-; 0-200 volts, 2½in. square, F/M., M/coil, 7/6.

AMMETERS. 0-1 amp., 2½in., projecting, R.F., 7/6 each; 0-5 amp., 2½in. round F/M., R.F., 7/6; 20/20 amp., 2in. round F/M., 0-30 amp., 2in. square, F/M., M/coil, 7/6.

A.C. VOLTMETERS 50 CYCLE. 0-15 volts, 2½in. round, F/M., M/I., 8/6; 0-20 volts, 2½in. round F/M., M/I., 10/=; 0-300 volts, 2½in. round, F/M., M/I., 25/=; 0-300 volts, 3½in. M/I., housed in wooden case complete with two test leads, 39/6 each.

MICROAMP METERS. 0/100 24 in. flush panel mounting, scaled 0-1,500 yards, first-grade instruments, brand new and boxed, 42/6; ditto, scaled 0/50 microamp., 62/6.

CERAMIC TRANSMITTER SWITCHES. Extra heavy-duty silver contacts, 3in. dia., I pole, 6 way, 3 bank, 9/6 each; I pole, 6 way, 2 bank, 6/6 each; I pole, 4 way, I bank, 5/6 each



TYPE 4 WAVE METERS. Cavit tuned absorption wavemeter covering 200-220 megacycles, brand new and boxed, supplied VU39, SP61. with EA50 and CV51 magic eye tuner, 29/6 each.

MAINS TRANSFORMERS. All 230 volt 50 cycle input. 250 x 250 volt 150 m/a., 4 volt 3 amp., 9/6 each; 500 x 500 170 m/a., 4 volt C.T. 4 amp., 3,000 volt insulation. 22/6 each; 670 x 670 volt 200 m/a., 6.3 volts 4 amp., 5 volts 3 amp., 49/6 each; 1,500 volts 330 m/a., 52/6 each; 2,000 volt 5 m/a., 15/6 each; 4 volt 14 amp., 6.3 volt 1⁴ amp., 10/6 each. METER RECTIFIERS. Full bridge 2 m/a., S,T.C., brand new, 5/6 each. UNISELECTOR SWITCHES. 4 bank double wipers, 25 position, 32/6. Ditto 8 bank, 45/-.

METER SWITCHES. Standard Yaxley type, 8 bank, single pole, 9, 11 or 12 way, 7/6 each.

H.R.O. 6 VOLT VIBRATOR POWER SUPPLY UNITS. Output 165 volt 80 m/a., 6.3 volts 3 amp. 6 x 5 rectifier, choke and condenser smoothed, cabinet size 7 in. x 7 in. x 6 in. Supplied with clips and leads, new down 20 6 networks 7in. x 6in. Supplied brand new, 29/6 each.

POWER PACKS. Input 200/250 volts Output 175 volts 60 m/a., 12 volts 2.5 Fully smoothed, 5Z4 rectifier, 32/6 each. P.40 A.C. amp.

BATTERY CHARGERS. 200/250 volts A.C. input, 24 volts 10 amps. output, perfect working condition, £12/10/- each.

TELEPHONE HANDSETS. Ex-American, standard P.O. type, 12/6 each.

AMERICAN POWER RHEOSTATS. 8 ohm, 3:3 amp., 8/6 each; 8 ohm, 2:5 amp., 7/6 each; 60 ohm, 1:3 amp., 7/6 each; 90 ohm, 0:7 amp., 5/6 each. 1deal for train, model or charging control.



BRAND NEW in origina transit case £11/19/6 each

BRAND NEW but shop soiled £9/19/6 ea. USED MODELS but in perfect working £7/19/6 each order

A combined power pack and audio output stage for A.C. mains, can be supplied with a receiver for an extra cost of 79/6 each.

CHROMIUM PLATED TELESCOPIC AERIALS. Min. length 12in, extends to 48in. Ideal for car radios, etc., 7/3 each.

SOUND POWERED MICROPHONES AND RECEIVERS. No batteries required. Just connect wires to speak or listen, 3/6 each.

HEADPHONES. Brand new, Canadian "Northern Electric," finest ever produced, 50 ohm coils, complete with P.I. Jack Plug, 10/6 pair.

RELAYS. Polarised, twin 600 ohm coils, 8/6 each. We stock all types of relays, 600 and 3,000 types, heavy and light contacts including platinum. Send us your enquiries, we are the cheapest in the trade.

SIX FOOT P.O. RACKS. 19in. "U" Channel, 79/6 each.



CHOKES. 20 henry 300 m/a., 13/6; 15 henry 275 m/a., 10/6; 20 henry 120/180 m/a., 10/6; 9 henry 100/150 m/a., 7/6.

TEST SETS TYPE 109. Brand new and boxed, fitted with 2in, 0-5 m/a., M/C., meter, also 0-40 volt 2in. M/C., meter, with mains plugs and leads and many other useful parts, 12/6 each.

FREQUENCY SCRAMBLERS. 6AC, YBO2700. For secret telep missions, complete with all valve Type No. FREQUENCT SCRAMBLERS. Type No. 6AC, YBO2700. For secret telephone trans-missions, complete with all valves, £5 each. P.O. KEY SWITCHES. Double pole change-over. Complete with knob, brand new, 2/9.



A MPLI-RECORD FIERS. A quality push-pull 6V6 amplifier, 8 watts output. Will match any type speaker, tone and vol-ume controls. Housed in attractive cream

desk type cabinet. Will match any type of gram input. For operation on 200/250 volts A.C. £6/10- complete.

A.C. $\pounds 6/10/$ - complete. This amplifier can be supplied in kit form with cabinet, complete to the last nut and bolt with easy to build point to point wiring diagram for $\pounds 5/10/2$. Suggested speakers for use with the above equipment, a quality 10in, 3 ohm speaker, 22/6 or an extra special quality 12in. 15 ohm speaker, $\pounds 4/19/6$.

RECEIVERS AND TEST GEAR MIDGET REVERSIBLE MOTORS. For

operation on 4, 6, 12 or 24 volt D.C. Size 2in. x 1 $\frac{1}{2}$ In., spindle length $\frac{1}{2}$ in. x $\frac{1}{6}$ in. Ideal for model makers, 10/6 each.

MUIRHEAD PRECISION BUILT KEY SWITCHES with heavy contacts. 8 pole SWITCHES with heavy contacts. 2 way, brand new, 4/6 each.

MULTIWAY TOGGLE SWITCH BOXES. Fitted with 16 toggle type switches. Ideal for train or model control. Brand new and boxed, 9/6 each.

TEST SET TYPE 28. Complete with 50 microamp meter, housed in instrument case with many other useful components, supplied with leads and wooden transit case, 65/- each.

CERAMIC SWITCHES. 3 pole, 4 way, 4 bank, 10/6 each; 4 pole, 3 way, 3 bank, 6/6 each; 7 pole, 2 way, 3 bank, 5/6 each.

ADMIRALTY POWER PACK TYPE FHB. 200/250 volt A.C. input. Output 2,500 volts 10 m/a., stabilised 350 volts 200 m/a., stabilised 110 volts negative 200 m/a., 6.3 volts 10 amp., also containing a complete 6V6 audio output stage and 6in. P.M. Loud-speaker, £5/10/- each.

EX-W.D. POWER PACKS. 230 volt A.C. input. Output 150 volts 60 m/a., 6.3 volts 1½ amps. Fully smoothed, twin metal rectifiers, 29/6 each.



5 way, 3/6 each.

DESK TYPE TELEPHONES. Standard Post Office type, complete with handset and con-nection block. Circuit and simple instructions available for installation. 42/6 each.

285 POWER PACKS. 230 volt A.C. input, output 2,500 volts 5 m/a., 350 volt 200 m/a., L.T. 6.3 volts. Double choke and paper condenser smoothed. 5U4G and VUI20 rectifiers. deal as a television power pack. Special price, 69/6 each.

WIRE WOUND POTENTIOMETERS. Midget type, 20 ohm, 750 ohm, 1,200 ohm and 5K. ohm, 2/- each. 3 watts size, 5K. ohm, 10K. ohm, 15K. ohm, 20K. ohm, 3/6 each. size, 400 ohm, 10K. ohm, 2/6 each. 10 watt size, 50K. ohm, and 100K. ohm, 7/6 each.

T.R.1196 RECEIVERS. Complete with 6 valves, 2 of EF39, 2 of EF36, 1 EK32, 1 EBC33. I.F. frequency 465 Kc/s. Simple conversion for complete superhet receiver, 27/6 each. T.R.I.96 RECEIVERS.

S.441B POWER PACKS. 200/250 volt input. Output 300 volts 200 m/a. 12 volts 3 amp., fully smoothed, 5U4G rectifier, 62/6 each


R.F.26 UNITS. Brand new. 50/65 mega-cycles. 2 of EF54 valves, I EC52 valve, Muircycles. 2 of EF54 valves, 1 EC52 head slow motion dial, 29/6 each.

600-900 MEGACYCLE R.F. UNITS. of three types, R.F.116, 118, and 119. £4/10/-complete set. Brand new.

HEAYBERD AUTO TRANSFORMERS. Brand new, housed in metal case with carry-ing handle. 200/250 volts input, 100 volts output, 750 watts, £4/10/- each.

HOURS OF BUSINESS: 9 am., to 6 p.m., Thursday I p.m. Open all day Saturday. PLEASE PRINT YOUR NAME AND ADDRESS CLEARLY ALSO INCLUDE POSTAGE OR CARRIAGE ON ALL ITEMS.

140

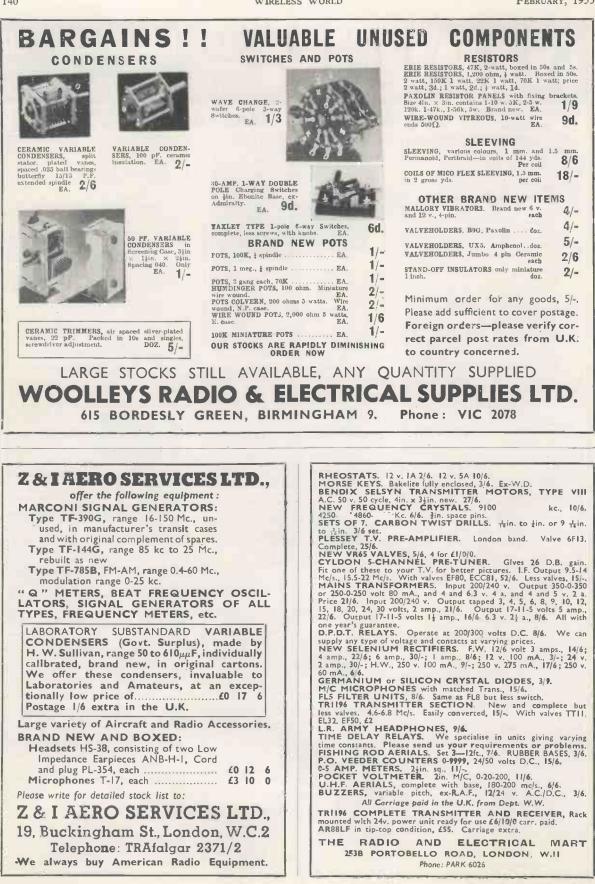

CONSTRUCTOR'S BARGAINS!

RF UNITS TYPE 26 and 27. RF UNITS TYPE 26 and 27. For use with the R.1355 or any receiver with a 6.3 v, supply. These are the variable tuning units which use 2 valves EF54 and 1 of EC52. Type 26 covers 65-50 Mc/s (3.5-5.0 metres), covers 85-65 Mc/s (3.5-5.0 metres), Complete with valves, and BRAND NEW IN MAKER'S CARTONS. ONLY 35/- each.

"PYE " 45 MC/S I.F. STRIP. Ready made for London Vision Channel, this made for London Vision Channel, this 5-stage strip contains 6 valves EFSO and I EASO. Supplied with circuit and details of very slight mods. required. BRAND NEW, ONLY 70,⁶ or less valves 50/-.

I.F. STRIP 194. An easily modified strip recommended for T.V. con-structors who want good results at moderate cost, or for those who have built televisors but are having trouble built televisors out are naving trouble in the sound or vision receivers. Size 18in. x 5in. x 5in. it is complete with6 valves VR53, 1 of VR92, and 1 of VR56or VR53. Mod. data supplied. ONLY45/- (postage, etc., 2/6). Less valves,19/6 (post, etc., 2/6).

TELESCOPIC AERIAL. Pulls out of metal tube 15in. long to extend to 73in. BRAND NEW, ONLY 7/6 (postage 10d.)

AMPLIFIER 208. Ideal for conversion into a high gain TV pre-amp. Complete with 2 valves EF50. ONLY 15/- (postage, etc., 1/6).

INDICATOR TYPE 95 Built on two-deck chassis, this contains VCR97 tube with mu-metal screen, 16 valves SP61, 4 of EA50, and 2 of EB34 and also shoals of components. ONLY 59/6 (carriage, etc., 7/6).

INDICATOR UNITS, TYPE 6. Contain VCR97 Tube with mu-metal screen, 4 valves EF50 and 2 of EB34. NEW CONDITION. ONLY 59/6 (carriage, etc., 7/6).

INDICATOR 233 CHASSIS. Similar to the type 6 Indicator Unit. This contains VCR97 CRT holder, 11 valve holders, resistors and condensers, etc. In excellent condition. ONLY 10/-(carriage, etc., 5/-).

AMERICAN 12 v. DYNAMOTORS. Output 255 v. 60 mA. Ideal for car radio or running electric shaver from car battery. ONLY 22/6.

V. BLOWER MOTORS. ONLY 12/6.

6 v. VIBRATOR UNITS. Made by the National Co. of America for use with H.R.O. Communications Re-ceivers, supplying 165 v. at 85 mA. fully smoothed D.C. Complete with vibrator and 6X5 rectifier in black crackle cabinet size 7in. x 7jin. x 6in., only 29/6 (postage, etc., 2/6).

CRYSTALS. British Standard 2-pin 500 kc/s., 15/-. Miniature 200 kc/s. and 465 kc/s., 10/- each.

SPEAKERS. P.M., 6±in., less trans 19/6; 8in. less trans. 19/6; 10in. with trans. 27/6 (postage 2/- ea.)

CHOKES. 10H 60 m/a., 4/-, 5H 200 m/a. 7/6, 20H 120 m/a., 10/6 (post 1/- ea.)

COMMUNICATIONS RECEIVER R.1155

The famous ex-Bomber Command Receiver known the world The tamous ex-Bomber Command Receiver known the world over to be supreme in its class. Covers 5 wave ranges: 18.5-7.5 Mc/s., 7.5-3.0 Mc/s., 1,500-600 kc/s., 500-200 kc/s., 200-75 kc/s, and is easily and simply adapted for normal mains use, full details being supplied. Aerial tested before despatch. BRAND NEW AND UNUSED IN MAKER'S TRANSIT CASES, ONLY & CU/19/6

BRAND NEW AND UNUSED IN TRACE ONLY £11/19/6. SLIGHTLY USED RECEIVERS, Grade 1, also tested working before despatch, £9/19/6. SECONDHAND, good condition, aerial tested before despatch,

A.C. MAINS POWER PACK OUTPUT STAGE, in black metal case, enabling the receiver to be operated immediately, by just plugging in, without any modification. Can be supplied as follows, WITH built-in $6\frac{1}{2}$ in. P.M. Speaker, £5/10/-, LESS

speaker, £4/10/-. DEDUCT 10/- IF PURCHASING RECEIVER AND POWER PACK TOGETHER.

Please add carriage cost of 10/6 for receiver and 5/- for Power Pack

POWER UNIT TYPE 3

Made for use with the R.1132A, this is a standard rack mounting job to match the receiver, and is for 200/250 v. 50-cycle mains with outputs of 250 v. D.C. 100 mA., and 6.3 v. 4 amps. Fitted with H.T. current meter and voltmeter, this is a first-class unit, and can be used for a variety of receivers. Used, but tested working before despatch. ONLY 90- (carriage, etc., 5/-). Connecting Cable with Jones Plugs for receiver and power unit, 10/-.

AMERICAN LORAN INDICATOR UNIT APN.4. AMERICAN LORAN INDICATOR UNIT APN.4. The unit recommended as a basis for the "WIRELESS WORLD" TELEVISION OSCILLOSCOPE, copy of which is supplied, contains 5CPI CRT and screen. 14 valves 65N7, 3 of 65L7, 8 of 6H6, 1 of 65J7, 100 kc/s. crystal, and hundreds of condensers, resistors, etc. BRAND NEW IN MAKER'S TRANSIT CASES. ONLY £6/19/6 (carr., etc., 15/6).

METERS	
F.S.D. SIZE AND TYPE	PRICE
I milliamp. D.C. 21in, Flush circular	
1 ,, D.C. 21/2 in. Desk type	. 25/-
5 " D.C. 2in. Flush square	. 7/6
100 ,, D.C. 21/2 in. Flush circular	
150 " D.C. 2in. Flush square	. 7/6
500 "thermo 2in. Flush square	. 5/-
500 thermo 2in. Proj. circular	. 5/-
20 amps. D.C. 2in. Proj. circular	. 7/6
40 amps. D.C. 2in. Proj. circular	. 7/6
30-0-30 amps. D.C. Car type moving iron	
15 volts A.C. 24in. Flush, circ., mov. iron	. 8/6
All meters Brand New in Maker's Cartons.	

100 MICROAMPS METERS

24in. circular flush mounting. Widely calibrated scale of 15 divisions marked "yards" which can be rewritten to suit requirements. These movements are almost unobtain-able today and being BRAND NEW IN MAKER'S CARTONS are a snip at ONLY 42/6.

HOUR METERS. For checking running time of equipment. Operates from normal 50 cycles mains. BRAND NEW IN MAKER'S CARTONS. ONLY 39/6.

MODEL MAKER'S MOTOR. Reversible poles. Only 2in. long and 14in. diameter, with 4in. long spindle. Will operate on 4, 6, 12 or 24 volts D.C. ONLY 10/6.

TRII96 TRANSMITYER SECTION. valves. In perfect condition, less ONLY 7/6 (postage, etc., 2/6) 229

159 RECEIVER UNIT. Contains 1 each valve, types EF50, EA50, SP61, RL37 and 24 v. selector switch. ONLY 12/6.

VACUUM PUMPS. For Handymen and Model Makers, Ex-R.A.F. Type B3. BRAND NEW IN MAKER'S CARTONS. ONLY 22/6 (post 2/-).

TRANSFORMERS. Manufactured to our specification and fully guaranteed. Upright mounting, fully shrouded, normal primaries. 425 v.-0-425 v. 250 mA., 6.3 v. 4 a., 6.3 v. 4 a., 5 v. 3 a., 50/-. 350 v.-0-350 v. 160 mA., 6.3 v. 6 a., 6.3 v. 3 a., 5 v. 3 a., 42/6. 350 v.-0-350 v. 150 mA., 6.3 v. 5 a., 0-4-5 v. 3 a., 32/6. 250 v.-0-250 v. 100 mA., 6.3 v. 6 a., 5 v. 3 a., 32/6. 250 v.-0-250 v. 60 mA., 6.3 v. 3 a., 5 v. 2 a., 21/-. Please add 2/- per transformed

Please add 2/+ per transformer postage.

TRANSFORMERS. FILAMENT.

6.3 v. 2 a., 7/6 (postage 1/-). TRANSFORMERS, EHT. Upright

mounting. EHT for VCR97 Tube 2,500 v. 5 mA. EHT for VCR9/ 1006 2,500 v. 5 mA. 2 v.-0-2 v. 1.1 a., 2 v.-0-2 v. 2 a., 37/6. EHT 5,500 v. 5 mA., 2 v. 1 a., 72/6. EHT 7,000 v. 5 mA., 2 v. 1 a., 82/6. Please add 2/- per transformer postage.

MODULATOR TYPE 67. Contains FUEDULATOR TTPE 67. Contains fully smoothed normal A.C. Mains Power Pack, transformer being 345 v. -0.345 v. at 200 mA., 6.3 v. 5 a., 6.3 v. 250 mA., 5 v. 2 a., 6 valves SP61, 3 of EA50, 2 of EB34, and 1 of 5Z4. BRAND NEW IN MAKER'S CASES. ONLY ATM (creating 7/4) 67/6 (carriage 7/6).

MU-METAL SCREEN FOR VCR97 TUBE, etc., ONLY 8/6.

CABLE. CLEARANCE OFFER of 23/36 twin polythene. Weatherproof, and suitable for outdoor use, 39/6 per 100 yard coil (carriage, etc., 3/6). S.A.E. for sample, trade enquiries invited.

SPECIAL OFFER. Ex-**Ex-Admiralty** L.T. Normal L.T. TRANSFORMER. Normal mains input, output 4 v. 20 amps. C.T. New and unused, these have become damaged, but are still usable, the damage being confined to broken fixing lugs, and/or broken bakelite terminal panels. Formerly sold at 30/-, now offered at 17/6 (post, etc., 2/6).

ROTARY POWER UNIT, Type 87. Ex-RA.F. Input 24 v. Output 230 v. 65 mA., and 6.3 v. 2 amps. Fully filtered, smoothed, and noise sup-pressed. Ideal for running radio on boats or other 24 v. D.C. source. BRAND NEW. ONLY 15/- (postage, etc., 2/6).

INTERNATIONAL OCTAL PLUG Fits into 1.O valveholder 2/- (post 3d.).

GANGED POTENTIOMETERS. Double 50K and double I meg., 7/6 each. 2-WAY CERAMIC 3-BANK SWITCHES, 7/6 each.

Cash with order please, and print name and address clearly



Radio Corner, 138, Gray's Inn Road, London, W.C.I. 'Phone: TERMINUS 7937

141

(Open until 1 p.m. Saturdays. We are 2 mins. from High Holborn (Chancery Lane Station) and 5 mins. by bus from King's Cross)

WIRELESS WORLD invaluable reference odition of an

RADIO LABORATORY HANDBOOK

M. G. Scroggie, B.Sc., M.I.E.E.

6th Edition

25s. net BY POST 26s. 3d.

This well-known practical work describing laboratory equipment and methods of operation has now been entirely re-written and greatly enlarged. Among the subjects considered are layout and furnishing of premises, methods of measurement, sources of power and signals, indicators and other instruments and circuit and signal measurements. There is a comprehensive references section, and the text is supplemented by many photographs, diagrams, graphs and tables.

8³in. × 5¹/₈in. 460 pp.

Available from booksellers or direct from :-

lliffe & Sons Limited, Dorset House, Stamford Street London S.E.1

MIDLAND INSTRUMENT CO.-

POWER SUPPLY UNITS No. 5, complete except for the 6-v. accumulator, consists of the 6-v. 5-amp. hand generator, with cut-out, 6-v. input vibrator pack, provides all L.T. and H.T. outputs for the 18 and 38 sets, space Maliory vibrator, bakelle accumu-lator box, etc., etc., in metal back carrying case, complete with beit and shoulder webbing, new in scaled carloss, 40/c, carrings 6/r, Sect. 7(6); N.I. 10/-

CHARGING KITS, consists of a G.E.C. 1]-map. full-wave rectifier, and a Douglas 200/250-v. A.C. Input transformer, specially wound for this rectifier, with requisite voltages to charge a 2, 6 or 12-v. battery at 1]-amps. 2 high grade components, complete with circuit diagrams and instructions, brand new, 25/, post 1/8.

G.E.C. MINIATURE RELAYS, all contacts are platinum, and relays are brand new boxed, 5,000-ohms, 2-pole change-over, hermetically sealed, 10/-, post 6d. Ditto, 5,000-ohms, 2-pole change-over and 2-pole make before break, hermetically sealed, 12/6, post 6d. Ditto, 40-ohms, 4-pole change-over, open type, 8/-, post 6d.

G.E.C. TYPE 600 BELAYS, brand new and boxed, 75-bram, 2-bole heavy-duty make an 1-pole change-over, 5/-, post 6d. Ditto, 130-bhms, 2-pole heavy-duty make, 5/-, post 6d Ditto, 5,000-bhms, 1-pole make, 6/-, post 6d.

U.S. RELAYS, Leach pattern, 200-ohm, 2-pole changeover, 1/6, post 4d., 15/- doz., post 1/8, ditto 3-pole changeover, 1/9, post 4d., 18/- doz., post 2/-.

BUZZERS, 3-6-v. high note, platinum contacts, variable note control knob, high grade type, worth 40/-, our price, new unused, 5/-, post 1/-.

ELECTROLYTIC CONDENSERS, 32-mfd. 450-v. D.C., by Zenith, Micamold, etc. new and guaranteed, cartons of 12 condensers, 10/-, post paid.

PROJECTION UNITS, consists of an optical mount, fitted with a bloomed f/2.2 Achro-matic iens, 3iin. focal length, at one end, also a convex/concave ground glass at the other, attached to an enclosed lamphouse, fitted with a 24-v. 15-watt lamp, and pollshed reflector, fraction of original cost, 10/w, post 1/-.

VARIABLE RHEOSTATS, wire-wound on ceramic, 50-ohns at 1-amp., laminated wiper arm, Bakelite knob control, in diecase cases size 51in. x 41in. x 21in., fitted on/off toggle switch and 2 cannon plugs, new, boxed, 7/8, post 1/8.

SELSYN Towner aan 2 cannon pugs, new, ooken, 715, pos 176. SELSYN TANNMITTERS (Magsile), 3in. type, pure synchro x-y-1-2-3, suitable as master or slave, 50-r, 50-cycle single phase A.C. operated. When two or more of these are wired up, the rotation by hand (or other means) of one, will result in a 100 per cent. follow in the other(s), both clockwise or anti-clockwise, supplied brand new with test report, in tropicalised scaled cartons. Yalue, 28 each, our price 25/-post 21-2 for 50/-, post paid with wiring diagram, SIEMEN'S HIGH SPEED RELAYS coll res. 145 ohms, single-pole changeover plainum contacts, adjustable armature tension and contact gap, well worth 35/-, our price, new, unused, 5/-, post 64., 50/-doz. post 24. doz., post 2/-

TELEPHONE SETS, consists of 2 combined receivers and microphones, connected by 20tf. twin fiexible, provides perfect 2-way communication (up to 1 mile with extra flex), self-energiesd, no battery required, complete ready for use, new, howed, 12(6, post 1/-


CEYSTAL SET COLLS, high-gain dual range med. and low, complete with crystal set circuit, 2/8, post 4d.; Variable conds. .0005 mfd.; Bakellte dielectric, complete with pointer knob, 3/8, post 4d.; Germanium detector, latest wire-ended type, 2/s, post 4d.; Warechange switches, 6d., post 3d.; (Dix plugs with sockets, 4 sets 2/s, post 4d. All items to construct a crystal set, 10/s, post paid.

Many other bargains; send 3d, with S.A.E. for current lists.

MIDLAND INSTRUMENT CO., MOORPOOL CIRCLE, BIRMINGHAM, 17 Tel. : HAR 1308


BC610 TRANSMITTERS with speech amplifier, aerial tuning unit, etc. Brand new RCA TRANSMITTERS Type ET-4336. Complete with original speech amplifier, crystal multiplier and VFO units. Unused and re-conditioned. Can be supplied with very large quantity of spares. RCA TRANSMITTERS. Type ET-4332 modified by R.A.F for use on crystal or master oscillator. Complete with speech amplifier. MULTI CHANNEL TRANSMITTER T-4/FRC, with modu-lators MD-1/FRC, 2 Mc/s to 18 Mc/s. Each channel 400 w. output, W.S. No. 19 & 20 both complete with installation kit-Tropicalised. New. MAGNETO IO LINE U.C. TELEPHONE SWITCH-BOARDS (complete). MARCONI SIGNAL GENERATORS Type T.F. 144G. As new, checked. A.R.88D's, A.R.77's, S27's, HRO, BC.312, BC.342, R.109 and others METAL RECTIFIERS Type IB, D.C. output 10 amps at 22 v, input 220/250 v., 50 c/s. All above items in excellent working condition Working demonstration upon request. A large selection available for SCR399 (BC610), ET4336, SCR610, EE8 Telephones, and Tele-SPARES printers type 7B. TX VALVES 805, 807, 813, 861, 66A, 100TH, 250TH, and many others. Large stock of Tx condensers, crystals and other components. Alignment and repair of communication receivers and all other short-wave equipment undertaken. New Address, Offices and Works BEAVOR LANE, HAMMERSMITH, LONDON, W.6 Telephone: RIV 8006,7

nen

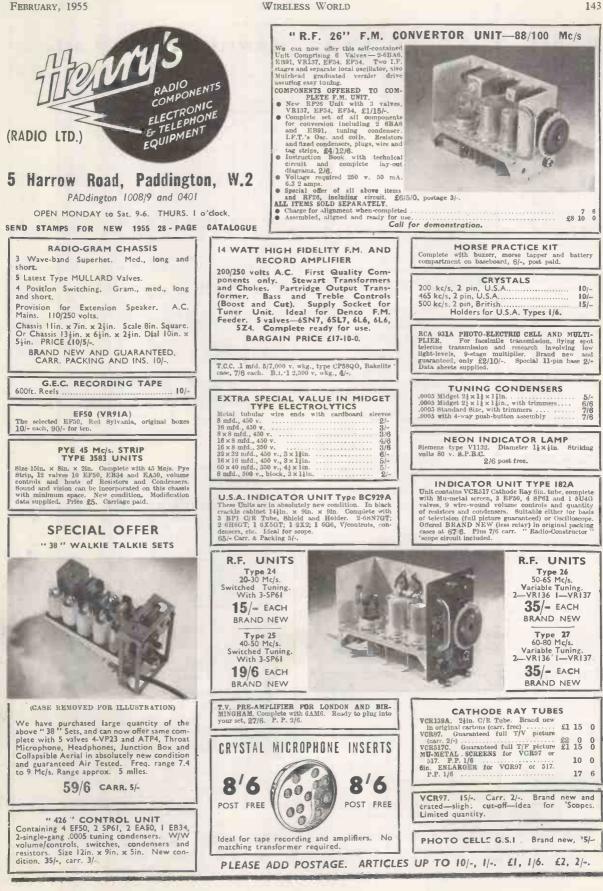

WIRELESS WORLD

144

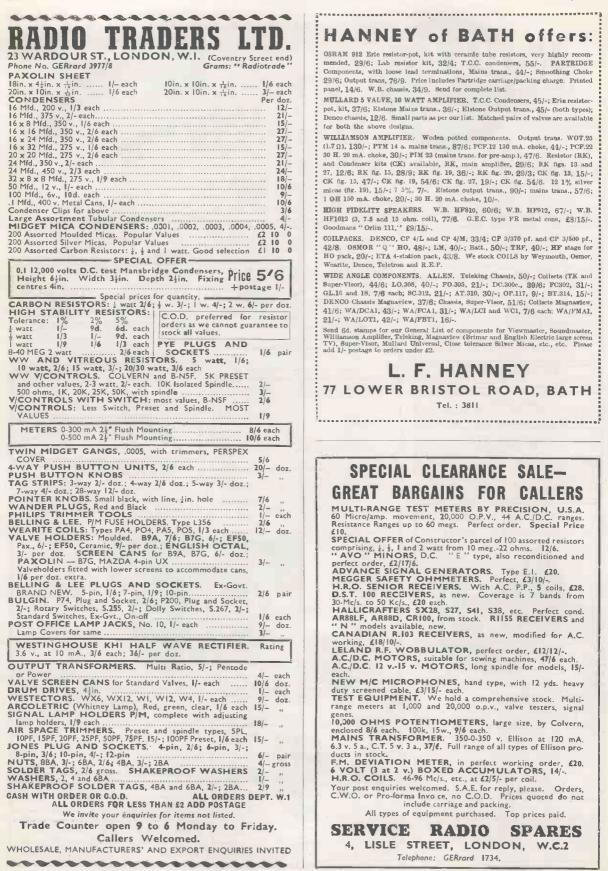

WIRELESS WORLD

Best Buy at Britain's TEST SET TYPE 87. Ex- R.A.F. corresponds to

TEST SET TYPE 87. Ex- R.A.F. corresponds to TF796. Incorporates a signal generator covering 150 to 300 Mc/s. Also pulse generator. Operates from standard A.C. mains. Contained in hand-some grey instrument case size 23in. x 10in. x 84in. Basis of the audio signal generator described in ''W.W.'' Aug./Sept. 1949. Complete with all valves and in brand new condition. Price £4/19/6.

U.H.F. SIGNAL GENERATORS by R.C.A. TYPE 710A. Covers 370 to 560 Mc/s. Large directly calibrated dial. Carrier level and 400 c/s. modulation monitored by large 200 micro-amp. meter. Precision piston attenuator. For A.C. mains operation 117 volts 50/60 c/s. Complete with instruction manual. BRAND NEW. £35.

3 CENTIMETRE TEST SET. Type 205A In brand new condition, £17/10/-.

HOUR-METERS. Indicate the time any given A.C. mains operated apparatus has been in use. Ideal for life testing, process timing, etc. BRAND NEW and BOXED. 39/6 each

E.M.I. OUTPUT METER. Desk type incor-porating a 2½in. I mA. meter together with instrument rectifier, etc. 2 ranges 0.500 milli-watts and 0.55 watts and decibel scale. Brand new in original manufacturers' boxes with Instructions. Price 35/-, post 1/6.

METER BARGAINS, ALL BRAND NEW 15 v. (50~) mov. iron 24in. pnl. mtg.... 8/6 20 volt moving coil 2in. sq. pnl. mtg.... 7/6 3,500 volts moving coil 34in. projection 10/-

METER RECTIFIERS. 1 mA. Salford Instruments, 8/9. 5 mA. Salford Instruments, 6/9. 2mA., S.T.C. as used in E.M.I. Output Meter, 5/6. All are full wave bridge and brand new.

METAL RECTIFIERS. Heavy duty Selenium METAL RECIFIERS. Heavy duty setenium 10 jin. long with 3 jin. square plates. Two are required for a full wave bridge giving 48 volts at 10 amps. Brand new and ridiculously cheap at only 57/6 per pair plus 2/6 post. R.M.4 250 volts 250 mA. Only 12/6. R.M.2, 4/3 each or 2 for 8/-, Selenium 300 volts 100 mA. Brand new, 8/-. Selenium 300 ex-W.D., 6/9 each.

X'TALS

X'TALS 465 kc/s S.T.C. tin. pins suitable for crystal, gates, IF checking, etc. Brand new, boxed 10/- each. 200 kc/s American G.E.C. tin. pins suitable for crystal calibrators, etc. Brand new, boxed, 10/- each. 100 kc/s tin. pin spacing. British, ex new units, 15/- each.

ROTARY POWER UNIT TYPE 104. Input 12 v., Output 230 volt 60 mA. and 6.3 v. at 2.5 amp. Fully filtered and smoothed and noise suppressed. Ideal for car radio, etc. Only 15/- each.

POWER UNIT TYPE 285. A.C. mains input 230 v. 50 cps. Outputs E.H.T. 2 kV. @ 5 mA. H.T. 450 volts @ 200 mA. L.T. 6.3 v. @ 17 amps., fully smoothed, 2 chokes, paper condensers, etc., complete with valves 5UdG, VU 120 and Ef 50. This was the ground power unit for the "Gee" equipment and should be very useful for T.V., etc. A REAL BARGAIN AT ONLY 69/6.

RACKS. 6ft. "U" channel P.O. type for 19in. panels, heavy angle base. Price 79/6, plus carriage at cost.

MODULATOR TYPE 67. This unit is a pulse modulator with pulse width of 1,2 and 5 micro-seconds. The pulse amplitude is also variable. It is a particularly useful instrument variable. It is a particularly useful instrument as it contains a heavy duty power pack suitable for 230 volt 50 cps. mains supply. The mains transformer outputs are 6.3 volts twice, 5 volts for the rectifier and the H.T. winding is 345-0-345 volts. Also included are 5 SP61, one VR116,2 EB34, and 3 EA50. Size of case 18 \times 9 \times 7 inches. These units are brand new in original packing cases. Price 67/6 plus 7/6 carriage 7/6 carriage.

COMMUNICATIONS RECEIVER ADMIRALTY TYPE B.28 (MARCONI CR.100). Valve line up 2 RF, F.C. separate local Osc., 3 I.F.'s, and Det., Output, B.F.O. an rectifier. Self contained power supply 200/250 volts A.C. 50 c/s. Variable Selectivity (crystal filter). 6,000, 3,000, 1,200, 300 and 100 cycles. Frequency coverage 60 kc/s to 30 Mc/s in six ranges, continuous except for gap between 420 to 500 kc/s. Size 16in. x 134in. x 12in. Weight 82lb. The set for the serious operator. Thoroughly overhauled 134m, X 12in. Weight 82lb. The set for the serious operator. Thoroughly overhauled and in good condition, complete with new valves and air tested prior to despatch. A real bargain at only £27/10/- plus £1 carriage.

VALVE VOLTMETERS. Ex-R.A.F. VALVE VOLTMETERS. Ex-R.A.F. Operates from standard A.C. mains. stabilised H.T. supply. Three ranges:—50/200/500 volts D.C. Meter employed 2¼in. 1 mA. F.S.D. Contained in handsome wooden instrument case size 14in, x 8¼in. X 9in. Complete with all valves and tested prior to despatch. In brand new condition and a real bargain at only 79/6 plus 5/6 carriage. Operates

COMMUNICATIONS RECEIVER R.1155 World-wide reception is ensured by the R.F. and 2 1.F. stages. Five wavebands, 2 L.W., M.W. and 2 S.W. Magic-eye, large dial and vernier make tuning simple. Contained in attractive black crackled cabinet, its handsome appearance does insting to its superb actractive black crackled cabinet, its handsome appearance does justice to its superb per-formance. Supplied with FREE BOOKLET giving circuit data and details of the power pack required for A.C. mains operation. Fully aerial-tested before despatch. Gladly demonstrated to callers.

Fully aerial-tested before despatch. Gladly demonstrated to callers. BRAND NEW. "MINT" condition, in ORIGINAL MAKER'S TRANSIT CASES, fill/19/6. Shop soiled models, as new, £9/19/6. A few only used models, £7/19/6, 10/6 carriage on each. Send S.A.E. for full details of power packs and receivers, or 1/3 for booklet. "N MODELS. Cover Trawler and shipping hards. EvenIper, condition. 617(19/6, nur.

¹ N ODELS. Cover Trawler and shipping bands. Excellent condition, £17/19/6, plus 10/6 carriage. D.F. Loops and Visual indicator Metters available. A.C. MAINS POWER PACKS AND OUTPUT STAGE. Enable the R.1155 to be used to operate speaker from 200/250 volts A.C. without ANY MODIFICATION WHAT-EVER. All our power packs have heavy duty transformers, are complete with leads and Jones plugs and are guaranteed for 6 months. Type A. In smart black metal case, size

Jones plugs and are guaranteed for 6 months. Type A. In smart black metal case, size 8½ in. \times 4½ in. \times 6½ in., less speaker, price £4/10/- plus 3/6 carriage. Type B. With built in 5 in. speaker in black metal case size 13½ in. \times 5½ in. \times 7½ in. Price £5/5/- plus 3/6 carriage. Type C. With an 8in. speaker in specially designed beautiful black crackle cabinet speaker to match receiver, size 11½ in. \times 10½ in. \times 6in. A de Luxe job. Price £6/10/- plus 3/6 carriage.

carriage. NOTE: 10/- REDUCTION WHEN PUR-CHASING ANY OF THE ABOVE POWER PACKS WITH RECEIVER.

TRANSFORMER BARGAINS. Brand new ex-manufacturer's surplus drop through. Primary 200/250 volts 50 cps. Secondary 310-0-310 v. 70 mA, 6.3 v. @ 3 a., 4 v. @ 2 a. Can be used with either 4 v. or 6.3 v. rectifier. Only 9/6 plus 1/6 post. A similar type transformer, 325-0-325 100 mA, 6.3v. 4 a., etc., can be supplied to callers only a 2/6.

Filament transformer, standard tapped primary, $12 v. 1\frac{1}{2}$ a. and 6 v. $1\frac{1}{2}$ a. secondary. Only 7/6.

HEAVY DUTY SLIDING RESISTORS, 250 watts rated to carry 25 amps., resistance 0.4 ohms, suitable for physics labs., charging board, etc. Laboratory type with worm drive, on metal stand, size 9in. x 4in. x 6in. high. Price 7/6 each. BRAND NEW.





INDICATOR TYPE 182A Indicator contains 3 EF50, 1 5U4G, 4 SP61 and a 64 in. C.R.T. Type VCR 517, complete with Mu Metal-screen, 9 wire wound pots, with large assort-ment of resistors and condensers. Can be con-verted to Oscilloscope (as described in "Radio Constructor."). Circuit supplied. Tubes have Constructor."). Circuit supplied. Tubes have no "Cut Off " and can be domonstrated to callers, BRAND NEW (less relays). In original transit case, 67/6 plus 7/6 carriage.

INDICATOR UNIT TYPE 95. Exactly the same as the 62 indicator unit but is 50 cycle ver-sion. Double decker chassis, containing loads of components, 16 SP61, 2 EB34, 4 EA50, ecc., etc. Brand new condition (less VCR97). Only 45/- plus 7/6 coreires 7/6 carriage.

45 Mc/s PYE STRIPS. Vision unit for London frequency. Complete with 6 EF50 and EA50. Circuit provided. Brand new. £3/10/- each.

E.H.T. TRANSFORMER. For VCR97, etc. Mains input, output 2,500 volts, 4 volts at 2 amps, and 2-0-2 volts at 2 amps. Fully guaranteed at 35/- plus 1/- post.

VALVE BARGAINS New and in original boxes. 6AG5, VR53 (EF39), VR56 (EF36), 6K7G, 6C5Met, 6SH7-Met., VT501 (TT11), all at 6/6. RK34, E1148, 954, 2X2, VU120A, all at 2/6. Replacement bargain EL50, 5/-. Dargain CL30, 3/-. New, ex units, 6AK5, VR91 (EF50), Sylvania, VT52 (EL32), 807, 7/6. VR65 (SP61), 3/6. VT501 (TT11), 3/6. CV6, VR78. VR92 (EA50), 1/6 each, 15/- dozen.

U.S.A. BLOWER MOTOR for 105 volts A.C. operation. Outlet 24in. diameter, extremely powerful. Snip for only 22/6 plus 2/- post.

CABLE. Heavy duty twin polythene weather-proof, suitable for extension mains, lead, etc. SPECIAL CLEARANCE OFFER, 39/6 per 100 yd. coil, plus 3/6 carriage. S.A.E. for sample.

NITROGOL CONDENSERS. With cera-mic insulating terminals. 8 mfd. 2 kV. wkg. size Sin. x 3 jin. x 4 jin. at 12/6 each. 4 mf. 2 kV. wkg. size 3 jin. x 2 jin. x 4 jin. at 7/6 each. 4 mf. 1.25 kV. wkg. size 3 jin. x 2 jin. x 41 in. at 5/6 each. BLOCK CONDENSERS. 40 mfd. 450 v.

COMMAND RECEIVERS. BC455. Covers 6-9 Mc/s (33-50 Metres), 125K7, 12K8, 125K7, 125K7, 125K7, 12A6. Brand new. Black crackled, 69/6 plus 2/6 post.

BARGAINS, BARGAINS, BARGAINS, HUGE STOCKS OF COMPONENTS, RECEIVERS, VALVES, AT SPECIAL REDUCED PRICES FOR CALLERS.

LANE

146

WIRELESS WORLD

FEBRUARY, 1955

146	WIRELESS WORLD	FEBRUARY, 1955
<section-header></section-header>	22.00 CIRCUITS for 2/6 dourses for 2/6 dourses Endand against Antional properties of the form of	The set of
MAGNETIC RELAYS BUILT TO SPECIFICATION. Coil Winding and Tropical Spring Sets and Coils supplied separa Send for Price List or quota KAYE ELECTRICAL MANUFAC Havelock Works, Havelo Harrow, Middleset HAR. 1432.	FLASHER U contacts. Wil The whole moo and 600. Ilizing. Attely if required. Attion. CTURING CO. AMPLIOYN CCURING CO.	CRNMENT SURPLUS NITS. Containing 2600 slug type relays, each 8 platinum give approx. ; second pulses from 12 to 24 volts supply. unted in metal dis-cast box 44 x 34 x 34 in. high. Suitable dicator lights on cars, etc. Price 17/6, post 2/ TTYPE 46, for 230 v. A.C. supplies. Output 6.3 v. ind 220 v. at 110 ma. D.C. Contained in a ventilated case in deep. Weight approximately 1 cvt. Price 55/10/ This is the power supply unit for 1155 Receiver LT and T. PACKS. 24 volt input, 110 volt D.C. about 40 ma bete with 12 v. vibrator, stabiliser VS/110/A. Complete New and boxed, 15,6 each, post 2,6. MOTOR GENERATORS. Ref. SAM3INJIBA. at 44 amps, output 60 volts at 8.8 amps 530 watts. Brand 's crate, 50/-, carriage 6/6. CTHUR T. SALLIS (V.W.) bad, Brighton, Sussex. Tel. Brighton 25806 ONS RADIO Ltd.
CABINETS MADE TO ANY SIZE OR FINIS CALL OR SEND DRAWINGS FOR	DORDER SH QUOTATION DEPT. E.) DEPT. E.) DORD. E.C.1 POWER UNITS 2,000 v. D.C. 5 to 2,000	TYPE 285 Input: 230 v. 50 cps. A.C. mains. Outputs: E.H.T. AA, 350 v. D.C. 150 mA, 6.3 v. A.C. 5 A. and 6.3 v. A.C. 10 A, ted units originally designed for operating "GEE" ground ted with metal cased, paper condensers (not electrolytics), valves and WR91, etc. Housed in metal cases 18 x12 x91m, with input/ te holders and on/off switch mounted on front panel. In good pilled with circuit diagram. A REAL SNIP AT ONLY 65/6. S. Type 607, as new, in original cartons, American made. SPECIAL 6 each. VU306 half wave directly heated rectifier. V. htt. 4 v. te 2,760 v. D.C. output I. 125 mA. Max. Pk. inverse 5,000 v. Pk. (EE 10/- CV173 (EF55), 12/6. S66A, 12/6. VR91s, dirty and y but all tested and guaranteed electrically good. PRICE ONLY 19/6: 12 ico 35/ DENSEE UNITS. These contain 5 metal cased condensers with optimary or 35.

RECEIVERS

EDDYSTONE 640. 1.2-30 Mc/s. £22 10 0; 740. 550 kc/s.-30 Mc/s. £35; 750. £45; 670. £35. HALLICRAFTERS SX28 550 kc/s.-32 Mc/s. £45; SX24 £35; S20R £28; 1953 Portable model £50. SX71. AS NEW. NATIONAL HRO receiver complete with all coils, etc., from £28; MARCONI CR100 £30. Set of three dials for AR88D per set £1 10.

MANUALS

For £1 7 6

BRITISH TEST EQUIPMENT

AVO Voltage Multipliers 1,200 v., 4,800 v., can be used with Model 40 Brand new. Carriage paid, each 5/6; Test Meter type 7 £15; AC/DC Minor £6; Roller panel valve tester. AS NEW £10; Valve Characteristic Meter. AS NEW £45. TAYLOR TV Wobbulator. 260A. AS NEW £28. EVERSHED Wee Meggers 500 v. £11 10 0; 500 v. Bridge types, etc. MARCONI Signal Generators, Type TF517, 150-300 Mc/s. £45; TF390G £45. COSSOR Double Beam scopes types 339A and 339 from £35.

SERVICE AND REALIGNMENT of all British and U.S.A. types **COMMUNICATIONS RECEIVERS** to makers' specifications AT LOW COST.

BENDIX BC221 Frequency Meters 125 kc/s.-20 Mc/s. available from stock

Large range of VHF receivers and Microwave test equipment. Kindly write for details or requirements.







PLEASE NOTE. Carriage and Postal charges refer to the U.K. only. Overseas freight, etc., extra.

ELECTRONIC IGNITION TESTER. Type V.E.D. Patt. 563562 by English Electric in original V.E.D. Part. 363562 by English Electric in original wood case. A Cathode Ray rester for checking ignition of internal combustion engine while engine is operating, will operate from 6, 12, or 24 volts D.C. or 230 volts A.C. Built into black crackle case with hinged front and carrying handle. Dim.: 15¹/₂in. x 8¹/₂in. x 11¹/₄in. No leads or instruc-tion book available.

£15 each CARRIAGE ASK FOR X/H535 10/- EXTRA INDICATOR UNIT TYPE 6H. With VCR.97 tube and valves, 4-VR91 (EF50), 3 VR54 (EF31). Dim.: 18in. x 84in. x 74in. Weight 271b. In orleinal word case. C' RRIAGE ASK FOR X/E777 59/6d. each 5/- EXTRA $\begin{array}{c} \text{INDICATOR UNIT TYPE 6. With VCR-97}\\ \text{tube and valves, 4-VR91 (EF50), VR54 (EB34),}\\ \text{3-VR92 (EA50), VR78 (D1), etc. Dim.: I8in. x 84in. x 74in. Weight 2' lb, In original woo' care. ASK FOR ASK FOR X, H524 45/= each 5/- EXTRA$ R.F. UNIT TYPE 24. In orieinal Carton. With valves 3-VR65 (SP61), etc. Range 20-30 Mc/s., switching tuning. Dim.: 9½in. x 7½in. x 4½in. Weight 7 lb. ASK FOR X/H850 10/- each EXTRA 10/- each R.F. UNIT TYPE 25. In Original Carton. 40-50 McS., orherwise as R.F. 24. ASK FOR 12/6d. each POST 1/6 X/H347 R.F. UNIT TYPE 27. With Broken Dial, Ranze 65-85 Mc/s. Valves 2-VR135 (EF54), VR137 (EC52), etc. Variable tuning. Dim.: and weight as R.F. 24. ASK FOR POST 1/6 29/6d. each EXTRA X/E771

DISTRIBUTION BOARDS. 250 volts 15 amp. DISTRIBUTION BOARDS. 200 voits to amp. 3 way. A "Simplex" iron-clad 14 amp. distri-burion board with 6 rewirable fuses, highly efficient fuse unit, mounted on hinged batterns bu'ion board with 6 rewirable fuses, highly efficient fuse unit, mounted on hinged batterns and fireproof fillet between poles. Size Bin. L. x 64In. B. x 34in. D. Weight B Ib. Ask for X/H949. "Sandali'e Duplex." similar but with no fillet. Overall size Bin. L., 84in. B., 4in. D. Weight I3 Ib. Ask for X/H950. "M.E.M. Kantark," similar, but with no fillet. Overall size: Bin. L., 7in., B., 34in. D. Weight B Ib. Ask for X/H951. All unused but slichtly marked extractable due to All unused but slightly marked externally due to being stacked. POST 6/6d. each PAID SPECIAL QUOTATION FOR QUANTITIES.

BRASS GLANDS. 3in. diam. In three lengths, 1. 3/16, 1in., 11in. Bore 1in. Price 1/3 each. Post Paid.

ROTARY CONVERTER TYPE 195. Input 24 V. D.C. 5 a. Output 230 V. A.C. 50 c/s. 100 w. Complete in metal case. Dim.: 13in. x Ilin. x Pin. with carrying strap. ASK FOR £5.19.6d. each CARRIAGE X/H914 CARRIAGE PAID

CARRIAGE SUPPRESSOR UNIT SC/870. Contains 4 H.F. chokes and 4 tubular condensers 0.1 mfd. 250 V. D.C., carrying 5 amps. (2 sets on each lead) each choke and condenser separately screened in compartments of aluminium alloy box 4‡in. x ASK FOR 2/6d. each POST 1/-EXTRA

CLYDESDALE

Order direc from :---




2, BRIDGE STREET, GLASGOW, C.5

SUPPLY CO. LTD.

SPECTRUM ANALYSER TYPE TSX-4SE (3 centimeter)

The TSX-4SE Spectrum Analy147

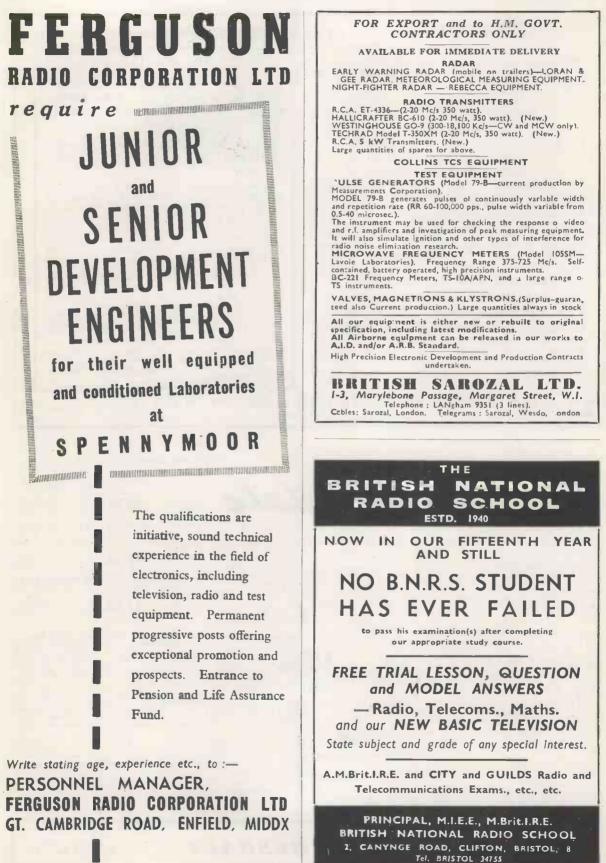

Wireless World Classified Advertisements

Rate 7/- for 2 lines or less and 3/6 for every additional line or part thereof, average lines 6 words. Eax Numbers 2 words plus 1/-. (Address replice: Box OOOC /o "Wireless World" Dorest House, Stammoord St., London, S.E.I.) Trade discount details available on application. Press Day: March 1955 issue, Thursdar, January 27th. No re-sponsibility accepted for errors.

WARNING

Readers are warned that Government surplus components and valves which may be offersd for sale through our columns carry no manu-facturers' guarantee : Many of these items will have been designed for special purposes making them unsuitable for civilian use, or may have deteriorated as a result of the conditions under which they have been stored. We cannot undertake to deal with any complaints regarding any such items purchased.

NEW RECEIVERS AND AMPLIFIERS

OUR new Mullard amplifier-MW/VHF re-ceiver-transistor receiver, can all be heard at-Mariborough Yard, N.19, 8 mins. Archway Station, 25 mins. West End. Ring Arc. 5078, Bel Sound Products Co.

SHIRLEY LABORATORIES, Ltd., 125. Tar-ring Rd., Worthing, Sussex, announce the superb pre-amplifier incorporated on same chassis, 15 watts output, response 15 c/s to 60,000 c/s extending to 130,000 c/s; bass lift 18 db, cut 18 db, treble lift 14 db, cut 20 db, hum and distoriton almost immeasurable: 230V @ 20 ma, 6.5v @ 2 amps at octal socket; beautifully constructed to instrument stand-ards, B.V.A. valves; price complete with en-graved panel, £18/18. Also the "Mullard" 10-watt amplifier with tone-control system, 18/57, and the E.S.2 square-wave generating unit for converting your sine-waves to square-waves, 28,-Write for full details. Tels, 513, 3571. [3579]

3571. [3579
 RECEIVERS. AMPLIFIERS—SURPLUS AND SECONDHAND
 NEW ZEALAND TX-RX NO. ZC.1 inter-communication sets for mobile work, built in Vibrator Packs for 12 volt operation.
 TWO types available:—
 MK. 1: 13 Valve TX-RX 2.2 to 6.5 MCS in one band. Power output approx 2 watts. CW or phone. Break in operation, built in aerial tuner or all types of aerial. Size 22X10X12. Weight approx, 501b. Waterproof cover.
 MK. II. As above except covers 2 wavebands 1.85-4 Mcs and 4-8 Mcs and 11 valves with syncronous vibrator.
 THESE sets are absolutely brand new, they have never been In service. The outer cases are slightly solled due to storage, but the sets have been hermicially sealed.
 Each set is supplied complete with instruc-tions manual, 1 pair moving headphones. 1 moving coll, hand microphone, key. set of heavy battery leads, and set of resilient mount-ings.

HRO Rx's and colls in stock, also AR88, BC348R, CR100, etc.—Requirements please to R. T. & I Service, 254, Grove Green Rd.. London, E.11. Ley. 4986 [0053]


R.F. units types 26 at 27/6. 25 at 15/-. 24 at 11/-, brand new in original cartons. with valves: postage 2/6.-E.W.S. Co., 69, Church Rd., Moseley, Birmingham. [3393

AMPLIFIER, 2 speakers, turntable mike, setc., new condition, 40 watts; proceeds of sale for Group Captain Cheshire, V.C.-Write to Warden Le Court, Liss Hants. [3982

WIRELESS WORLD 2 R.F. 3-valve quality tuner, M.W. and L.W., unused, ideal for use with all high fidelity amplifiers; £6/10. Including valves, limited number; bargain.— Box 0892. [4035

NEW LOUDSPEAKERS

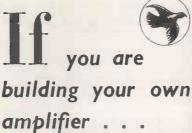
GOODMANS loudspeakers, also supplied in polished cabinets, write for list, easy pay-ments.—Stamford (Dept. D.21), 20, College Parade, Salusbury Rd., London, N.W.6. [3997



or any other audio equipment calling for high quality transformers you should complete and post the coupon below immediately. This will ensure that you receive the following:---

- An article on High Fidelity and the output transformer by J. C. G. Gilbert, F.R.S.A., Assoc.I.E.E., M.Brit.I.R.E., etc. (reprinted from "Music Trades Review").
- An illustrated brochure giving full details of the Partridge components specified for the Osram 912 and Mullard 510 amplifiers.
- 3. Technical data sheets and all available literature on the Partridge range of transformers and chokes.

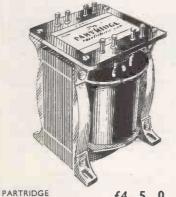This material is free. Post the coupon now.



TYPE P3591A

£4.5.0

1

(Push-pull output) Specified in the Osram 912 circuit. If performance down to 30 c/s is required it is essential to employ a transformer of this calibre.

OVER 100 STANDARD TYPES

are available in the Partridge Range. Our Catalogue gives full technical details frequency response curves, etc.

Post this coupon now!

To PARTRIDGE TRANSFORMERS Ltd. Roebuck Road, Tolworth, Surrey.

Send me :

Ł

Ē

I

I

. I

- (1) The article on High Fidelity.
- (2) Illustrated brochure for amplifier components.
- (3) Technical data sheets. (Cross out which not required.)

NAME..... ADDRESS W.W.255 Please use Block letters.

LOUDSPEAKERS-SURPLUS AND SECONDMAND HARTLEY TURNER 215 speaker, condition as new; offers.-Emmott, The Porch, Ports-mouth Rd., Esher, Surrey.

GOODMAN'S Axiom 150 Mk. 2 speaker in 11-ply corner cabinet, Goodman's specifica-tion as new; £12.-Whittle, 99, Market St., Hindley, Laurs [4060]

Hindley, Lanes 14060 TEST EQUIPMENT-SURPLUS AND SIGNAL generators, oscilloscopes, output meters, valve voltmeters, frequency meters, multi-ranse meters in stock; your enguirles are invited.-Requirmements to R.T. & I. Service, 254, Grove Green Rd, London, E.H. Ley. 4986, UNIVERSAL meter Taylor model 90A BS 89 Afrst-grade accuracy, IOO o.p.v. AC/DC, E8/IO only; also valve tester 45A/S with adap-tors measuring mutual conductance of almost all modern valves, £14; both in perfect condi-tion, practically new.-Write: Strauss, 5, Gloucester Ave., Slough, Bucks. [3697]

all modern valves, 214; both in perfect condi-tion, practically new.-Write: Strass. 5; Gloucester Ave., Slough. Bucks. [3897] FreeQUENCY stabilizing sets by G.E.C., com-prising one multivibrator unit 100kc/s to 1kc/s. one ditto 1k/s to 50c/s, and one 3-phase amplifier unit for 50c/s stabilized output; all three units fitted power pack for 200-250 vs single phase a.c. mains. mounted in standard rack 56in high complete with 100kc/s crystal. 27 valves and circuit diagrams, new; 239. BRIDGE-MEG testing sets by Evershed & Vig-noles, 250v self-contained type in alloy case, rang: 0.010 to 50MQ, leather case, used. accuracy tested, £12/15; ditto, 1.000V, 0.010 to 200M(h as new. 25; MICROAMMETERS 24/in M.C., flush, round, centre zero, Sangamo-Weston, 250-0-250 micro-amps, new, 22/6 p.f. CAMBRIDGE Unipivot meter, 100 microamps f.s.d., 5in mirror scale calibrated 0-120, in hardwood case 9 Jin/9 Jin, with Cambridge Yach-Junction 0.5nia, 20mc/s max., as new; EREQUENCY Paic. READENCY 245; ditto, 1.600x, 4Xin dia., 180y, 210-455v £9; all p.f. ELECTRICAL tachometers, calibrated 40-60c/s, 4Xin dia., proj., 230v, £8; 71m dia., proj., 210-455v £9; all p.f. ELECTRICAL tachometers, calibrated 40-60c/s, 4Xin dia., flush, 12/18V a.c., rect./M.C., com-piete with separate a.c. tacho-generator, reads 50c/s at T-G speed, 3.000rpm, new; 37/6 p.f. TONG-TEST ammeters. Crompton-Parkinson 2-tange, 0-100 and 0-400amps, leather case; 57/6 p.f. VARIAC transformers, all 230v input type 200CUC 0-270V, 2 amps, £6; type 100L, 0-230V, 8amps, £14; type 50B, 0-270V, 20-31amps, £35. CONSTANT voltage transformers, input 180-260V, output 230V, 630VA; 1-kva. £12; carr. extra except where stated., P. B. Crawshay, 94, Pixmore Way, Letchworth, Herts, Tel. 1631. [3945]

NEW DYNAMOS, MOTORS, ETC. WARD rotary converters for radio, tele-vision amplifiers, etc. ALSO, rotary transformers, alternators, DC generators etc. SPECIAL ofter.-Revolving armature alterna-tors, 2 pole, ball bearing, 3,000 r.p.m., with direct coupled 24-30v exciter, and voltage control components; output 230v, 50 cycles, 3.25 k.v.a. 8 power factor; price with Vee rope pulley, £42 each, nett, ex-works. WARD, 75. South St., Bishops Stortford, Herts, Tel. 1694. [0039

SPECIAL television rotary converters, guaran-teed interference free, fitted radio and tele-vision filters, wt. 60b, d.c. input 12v 200va, out. 24v. 32v, 50v, 110v, 230v d.o., to 230v out, 250va, £28/10 del., also converters for radio-gram and general use, inputs, outputs and prices as above; the above also supplied without smoothing, £25 del. immediate despatch; trade supplied.

mothing, £25 del. immediate despatch; trade supplied. AT a purchaser's home 60 mls. S.W. of Sutton Coldfield a 24y TELEVISION converter was tested on Ekco tele-vision, 12in tube, stated consumption 135 watts d.c. current from battery only 9½ amps, picture and sound were perfect and completely free of interference or flutter. THE above is the latest product of British manufacture and is guaranteed for one year. J.A.P. No. 2A 1.2hp petrol engine, alr-cooled. 4-stroke, starting rope, tools; £17/10 delivered. (near Angel).



150



-THE MODERN BOOK CO.-BRITAIN'S LARGEST STOCKISTS **OF BRITISH and AMER!CAN**

TECHNICAL BOOKS

Radio and Television Engineers' Refer-ence Book edited by E. Molloy. 70s. 0d. Postage 1s.

Prostage Is. Basic_Television by B. Grob: NEW EDITION. 485. 0d. Postage Is. Practical TV Aerial Manual for Bands and III by R. Laidlaw. 4s. 6d. Postage 3d.

130 Frinciples of Transistor Circuits edited by R.F. Shea, 885.0d. Postage Is. Telecommunications by A. T. Starr, 355.0d. Postage 9d. Electronic Organs by R. L. Eby. 40s.0d. Portrage 9d.

Postage 9d. Principles and Practice of Radar by H. E. Penrose and R. S. H. Boulding. 50s. 0d.

Pöstage Is.

¹¹Postage Is. Magnetic-Amplifier Circuits by W. A. Geyger, 42s. 6d. Postage 9d. Television Engineers' Pocket Book edited by E. Molloy & J. P. Hawker. 10s. 6d. Postage 6d. Telévision Receiver Servicing: Vol. I-Time-Base Circuits by E. A. W. Spread-bury. 21s. 0d. Postage 9d. The Oscilloscope at Work by A. Hass & R. W. Hallows. 15s. 0d. Postage 9d. Brimar Radio Valve and Teletube Manual: No. 5. So. 0d. Postage 9d. Radio Valve Data compiled by "Wireless World." 3s. 6d. Postage 3d.

Please write or call for our catalogue.

19-23 PRAED STREET (Dept. W.2)

> LONDON, W.2 Phone: PADdington 4185 Open all day Saturday



AERIAL-MASTS. American Yagi 5 element ATray AS-66/APG. 30ft, one piece 4in, dia. hollow wood masts. 36ft. 3 section 2in, dia. tubular stee, masts. 45ft, 9 section 1/2 in, dia. tubular stee, masts. 45ft, 9 section 1/2 in, dia. American steel masts. MS-44. Soft. Bendix plywood masts MT-7A. 70ft. American ply-mold masts. 200 m/cs "H" dipoles. 20ft. American tripod base aluminium masts. AS/TPX. 9ft. one piece American police whips. 18ft. BC-610 6 section whips. TELEPHONE AND TELEGRAPH APPARATUS. 1+1 terminals and by-pass filters; 1+3 terminals: 1+4 terminals AFFARATOS. 1+1 terminals and by-pass filters; 1+3 terminals; 1+4 terminals and repeaters; S and SX, S and DX, filter : power bays; repeaters; V.F. ringers; perfor-ators: Wheatstone equipment; teleprinters; undulators; switchboards; rectifiers: EE-65, TG-10, etc., etc.

ADDO EQUIPMENT. R.C.A. squadron announcers (12-25 watt speakers), R.C.A. 25 watt high power speakers. Portable megaphones PA-4. SCR 625 MINE DE-TECTORS.

CONTROL UNITS. RM-6, 7, 12, 13, 21 25. 29. 42

AMERICAN TRANSMITTING TRANS-FORMERS AND CHOKES. A large variety by Amortran, Kenyon, R.C.A., Thordason, etc., etc.

TRIPLE DIVERSITY RECEIVERS. 1.5 to 30 mtcs. Self contained on rack with all refinements. Full details available. 100 WATT BROADCASTING TRANS-MITTERS by Woden. Self contained in 4(t. 6in, cabinet 622/10)- with valves.

RACKS, de luxe, 19 inches wide channel iron sides, 3 x 2, 3ft. 6in. high, 40/-; both carr. 10/-.

Many other items too numerous to mention. Send your requirements. Lists available. All packing and shipping facilities. Lists available.

P. HARRIS ORGANFORD DORSET Telephone : Lychett Minster 212.

DYNAMOS. MCTORS. ETC.-SURPLUS AND SECONDHAND 2.000c/s motor-alternator sets. input 220v 500VA. comp.ete with starter, fuses. control panel and voltmeter, all mounted in ventiated steel cabinet 14in.26in.X49in high, new in original cas.s; £16. carr. extra. P. B. CRAWSHAY. 94. Pixmore Way. Letch-worth. Herts. Tel. 1851. [3943

NEW GRAMOPHONE AND SOUND EQUIPMENT FERROGRAPH magnetic tape recorder

FERCOGRAPH magnetic term 76gns. * BARITE tape decks and component parts. DISC recording machines and blank discs. LEAK amplifiers, 10w £17/17; preamp £40/10. GOODSELL, 5w £13/10, preamp £40/10. GOODSELL, 5w £13/10, preamp £40/10. GOODSELL 5w £13/10, preamp £40/10. EVERYTHING for the professional recording studio and quality dealers. SOUND DISCS (SUPPLIES), Ltd., 178 Bis-pham Rd. Southport, Lancs, Tel. 8d153. 13169

Lane Decks.

\$24

T./R. amplifiers for Truvox, Lai etc.; 5 watt £14, 10 watt 19gns. F.M. tuners, Denco £8, ready built. U./L. 14 watt amps, with pre-amp, HARDING ELECTRONICS, 120a, 1 London, N.W.2. Mora Rd., 10032

London, N.W.2. [0032 **FERROGRAPH** tape recorders for high grade sound: H.M.V. 2300 Disc Recorder, com-plete (1 only); Emidiscs and Emitape 88: "EQOIGA" RECORDING SERVICES. [Gas "Miscellaneous," page 153.) [0122 **T**APE recorders for sale, exchange, or nire in Greater London, good quality tape re-corders wanted for cash, all types of repairs, mechanical and electronic, caried out by specialists, all accessories available, we deal exclusively in magnetic recording equipment. THE MAGNEGRAPH RECORDING Co., Ltd. I. Hanway Place, London, W.I. Tel, Langham 2156.

2156. ISON CINE-VOX disc recording equipments. type CJJ for high-quality recordings from exist-ing microphone equipment; price from 28gns; also available as a complete channel inclusive of mic. amplifier and playback equipment, at 70gns; type C7, for highest quality professional requirements--recorder mechanism at 48gns, or complete channe, at 110gns; demonstrations arranged in London. PLEASE write for details to K.T.S., Ltd.. "Coplow," Park Rd., Braunton, N. Devon. Tel. Braunton 224. Callers by appointment only. 10209

GRAMOPHONE AND SDUND EQUIPMENT —SURPLUS AND SECONDHAND C.J.R. tape recorder monitor and mixing facilities, studio quality; £70.—Box 0947. [4054]

GARRARD RC75/AC automatic record changer, high fidelity heads mounted, as new; £12.—Emberbrook 4278. [3970]

MSS type PM/1 tape recorder, little used. ribbon mic., 5 rolls tape; can be seen Central London; offers around £55; cost £135. -Box 0713.

CRAMOPHONE AND SOUND WANTED.-Garrard R.C.30 record changer. mechanism only.-Offers to Lovegrove. Neal's Farm, Wytold, Checkendon, Oxon. [4052

NEW COMPONENTS

WHY not ask us to give you a quote? WE manufacture high-qua ity transformers to suit your requirements at very competitive prices: out delivery is good, and all our work carries a 12 months' guarantee WOODROW TRAN.FORMERS, Ltd., 7. Dud-den Hill Lane Willesden, N.W.10. Tel. Wil. 1347. [3946]

COMPONENTS-SURPLUS AND SFCONDHAND GERMANIUM Giddes, 1/- each; quantities don N.8. Jone J. Green Lanes, Lon-don N.8. [3649

SOUTHERN RADIO SUPPLY, Ltd., 11, Little Newport Street, London, W.C.2. See our displayed advertisement, page 161. [0016

WESTINGHOUSE "Stabilistor." constant voltage stabiliser, input 190/260, output 230 volts, 600va, believed inuesd, £10/10; rec-tifier units 230, input 110 volts D.C. out 2.5 amps £6/10,--Hutchings, 1, Kinloch St., N.7, [4051]

50.000 meta-giass seals, single way her-metically sealed terminals for soldered con-nections and fixing, mostly lky and 2kv sizes, new, 65/- per 1,000 assorted.-P. B. Crawshay, 94, Pixmore Way, Letchworth, Herts. Tel. [394]

VALVES. new and guaranteed surplus: all boxed. CV131. 5/6: CV133. 7/6: CV136. 6/6 CV133. 6/6: CV140. 6/-: CV216. 8/6: CV345. 30/-: CV416. 9/6: CV417. CV491. 9/-: CV492. 8/-: CV455. 7/-: CV491. 9/-: CV492. 7/-: CV493. 7/6: CV566. 9/-: CV758. 8/6: CV797. 8/6: CV550. 7/6: CV2129. 9/-: CV1758. 6/-: CV2127. 6/6: CV2129. 9/-: CV1759. 10/6: CV2209. 9/6: post 6d each: 500 other types stocked: s.a.e. for full list: 24-hour service. cash with order or C.O.D.-Bentley. Ltd. Radio House. Chalcoc Rd., London, N.W.1. Primrose 9090. [3905]



Illustration (abbrox.) actual size



Type approved Cat.A No. 464

12 Vane type 500 Volts Width 16.5mm Length 22mm Height 19mm Insulation 10,000 megs. Power Factor less than .001 Temp. Coeff. 50 parts/million/°C





We can supply

any Cabinet to YOUR OWN SPECIFICATION. The one illustrated can be obtained in Walnut, Oak or Mahogany for £19/15/0 or as a COM-PLETE RADIOGRAM incorporating:

5 Valve Superhet Auto-	C40/17/A
5 Valve Superhet Auto- changer and 10in. Speaker for	140' 11' 4
8 Valve Armstrong F C 48 Auto-	000/41/1
8 Valve Armstrong F.C.48 Auto- changer and 10in. Speaker for	+67/14/4
changer and rom speaker for	202 IT T
10 Valve Armstrong R.F.41 Auto-	070/10/0
10 Valve Armstrong R.F.41 Auto- changer and 10in. Speaker for	1/0'10'0
14 Valve Armstrong 125/C Auto- changer and 10in. Speaker for	000/0/4
changerand LOin Speakerfor	388/6/4
changer and roin. speaker for	200 0 1

(H.P. terms can be arranged) Send I/- for complete Catalogue of Cabinets, Chassis, Autochangers and Speakers (refunded on receipt of order).

LEWIS RADIO CO. 120, GREEN LANES, PALMERS GREEN, LONDON, N.13. BOWes Park 6064

DUODE 12cSUPREMELY NATURAL SOUND



INSIST ON HEARING A DUODE

Whatever your amplifier Whatever your cabinet Whatever your pickup Whatever your receiver Whatever your radiogram It must end in a Duode

The greatest care taken in choosing any or all of these primary stages of a good quality installation is wasted unless the same care is given to the choice of the most important, most critical final stage of all-the recreator of sound itself.

That choice has to be lived with for some time. A hasty decision and failure to hear a Duode may condemn the really critical ear to a long sentence. So, before you plunge

INSIST ON HEARING A DUODE

The Duode 12c is a 12in. unit with the famous dual drive, built-in crossover and feedback, giving a range from below 25 to over 16,000 c.p.s., PLUS absolute smoothness and a grip of transients and bass which is unequalled. Definition throughout the range is superb. NATURALNESS, freedom from boom or harshness and continuing pleasure are the fruits of DUODE ownership. The 12c at £20 is the finest high-quality sound unit available today. The 12b at £14 and 12a at £10 are also the best in their categories. The Duode 12c is a 12in. unit with the famous

Any recognised music or radio dealer can, if he any recognised music or radio dealer can, if he wishes, buy Duode Units from us for his stock and demonstration. If yours will not do this for you, we will help by offering you the facility of trying a Duode at home under ver/ fair and reasonabls conditions.

Write for details today Barker Sound Reproducers 3 Newman Yd., London, W.1 COMPONENTS-SURPLUS AND SECONDHAND SUPREME RADIO. 746B. Romford Rd., Manor Park. London. E.12. TEL. 11f. 1260. Est. 19 years. 1955 RADIO and television component part Dargains at the right pr.ce. ELECTRCLYTIC cond.. 8mid 450v working. seeved tuouar w/end our price; 1/11 ea.; 32mid 350v tag end. aiumit.um can, smail 1/9 ea.; 16+8mid 450v all. can or sleeved w/end. 4/9 ea. 4MFD 150v Dubiller Drylytic w/e card. cond., 10d ca.

10d (a. 25MFD 25v Micropack tag end metal bias cond.,

1 4 ea. METALPACK 0.1mfd 350v condensers, 8d ea.

or //6 doz. SPRAGUE 0.1mfd 350v w/end cond., 6d ea. or 5/6 doz. INT/OCTAL v/holders. Amphinol type, 6d ea.

INT/OCTAL v/holders, Ampliant type, at the or 5/6 doz. E.P.50 valves, Red Sylvania, 10/6 ea. ALL parts an stock for "Denco" F.M. unit; this will be the future rad.o. DENCO F.M. Technical Bulletin "DTB8" for Jounding P.M. feeuer an.t, 1/6. CO-AXIAL cable, 800hm, brown or black, 8/-doz vnc.

Goz. $v_{0.5}$, stands, costing, form to block, of STEEL chassis, ready punched for s/het lay-out. 14,n×6,n×3,n, 2/6 ea HEATER trans. 0-250v sec 6.3v at 1.5amp, oarga.n pr.ce, 5/9 ea. TAPPED heater trans. 0-210v-230v-250v, sec., 0/2v, 4v-6.5v at 1.5amp, really a bargain at


STEEL CHASSS, TEAC, Putter, N. 2011, 2011, 2011, 2011, 2011, 2011, 2012, 2014,

04410 MAINS trans., 250-0-250v, 80ma 6.3v, 2.5A, 6.3v, 0.6A, Pri. 0-210-530-250v 12/- post paid RADIO CLEARANCE, Ltd., 27, Tottenham Court Rd., London, W.1. Tel. Museum 9188 [0015

WANTED. EXCHANGE, ETC. VHF test equipment.

TS47AP, TS174, TS175/U, TS148 or TSX-4SE; analysers; BC221 freq meters. TS69, and any U.S.A. test gear; Klystrons type 723/AB, 2K33 2K39 2K41; receiver. APR4 and units TN16 17-18-19; RCA AR88D, S27 and SX28s and S27CA; microwave equipment; highest offers given by return.—Ger. 8410. Universal Elec-tronics, 27. Lisle St. Leicester Square, Lon-don, W.C.2. [0229]

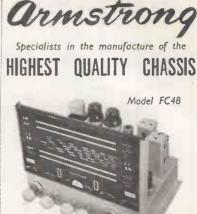don, W.C.2. [0229] WANTED, receivers A.P.R.4, also T.N.16. 17, I.8, 19, etc., and any radio test gear. LESLIE DIXON & Co., 214, Queenstown Rd., Battersea, S.W.8. Macaulay 2159. [0176] WANTED, HRO coils, Rxs. etc., A.R.88s, B5348s, S27s, etc.—Details to R.T. & I. Ley, 4986. [0163]



Price : £23.18.0

FC 48 RADIOGRAM CHASSIS with provision for F.M. Tuner.

- 8 Valves including 2 double triodes.
- .
- 8 Watts output free Push-pull Tetrodes. Independent Bass and Treble lift and cut. Magic Eye tuning indicator. Coverage 16-50, 49-120, 190-550, 900-2000 .
- metres .
- Large four colour illuminated dial. Overall size: $12\frac{1}{2}$ " x 9" x 9 $\frac{1}{2}$ " high. Supply : 200-250 volts A.C. mains.
- .



TWIN Radiogram 57 Price Gns. (Inc. Tax).

RADIOGRAMS We now have a fine range of High Fidelity Radiograms which are much in demand. The Twin model incorporates the magnificent FC.48 chassis, the new latest 3-speed inter-mixing record changer, and high flux 10in. Joudspeaker. The cabinet is finished with a beautiful walnut veneer.

TELEVISION The TV.5 Range is avail-incorporates all the most up-to-date improve-ments such as 5-channel selector switching and aluminised flat faced tube and tinted filter.

★ PROVISION IS MADE FOR AN ADAPTOR WHICH WILL ENABLE YOU TO RECEIVE ALL 13 CHANNELS, WHICH WILL BE AVAILABLE AT A NOMINAL CHARGE WHEN REQUIRED the TRUE

The TV.5 Range really give th BLACK AND WHITE PICTURE

TV.5 14in. Chassis, £54/0/3 (inc. P.T.). TV.5 14in. Console, £72/9/0 (inc. P.T.). TV.5 17in. Chassis, £64/15/11 (inc. P.T.). TV.5 17in. Console, £82/19/- (inc. P.T.).

Our Showroom at the address shown below is open daily from 9 a.m. to 6 p.m. (Saturdays 5 p.m.) and we are always delighted to demonstrate any of our Models or supply any information regarding them. If unable to visit us please send for the specifications you may require to Dept. WF.

ARMSTRONG WIRELESS & CO. LTD. WARLTERS ROAD, HOLLOWAY, LONDON, N.7 -Telephone : NORth 3213/4-



WEST END RADIO

13. Jotally enclosed in neavy steel case, new in maker's carton. Our Price 68.15.0 carr. free. Trade Terms for quantities. R.109 RECEIVERS. Complete 79/6. P.& P. 10/-. BATTERY CHARGERS, 6 or 12v. 4 amp. 79/6. P.& P. 4/6.

ACCUMULATORS. Celluloid 2v. 7 amp. New 7/6. P. & P. 1/6. SWITCH BOARDS with 16 Toggles, new

2 P 12V. 4A. SELENIUM RECTIFIERS. 14/3.

& P. 1/6. P. & P. 1/-.

CANADIAN MARCONI No. 9 RE-CEIVERS. 2 Channel 1.9-5 Mc/s. 10 valves. B.F.O. BRAND NEW, 95/-. P. & P. 15/-.

1,000 Bargains for callers!

WEST END RADIO LTD. 14, LISLE STREET, LEICESTER SQUARE, LONDON, W.C.2. Phone: GER 7341 OPEN ALL DAY SATURDAY!

WANTED, EXCHANCE. ETC. -WANTED, tuning units, TN17, TN18, TN19, for R54/APR4; £50 each offered. -Box [0261 WANTED, Aerial tuning units B.C. 939a. P.C.A. Radio, Beavor Lane, Hammer-smith, W.6.

A BOUT 50 infra-red receivers. Type No. 5c/2246 or similar equipment; also separate converter cells, perfect condition only.—Box 0817.

WANTED, set manufacturers' or ex-Govern-ment radio equipment, large or small quantities of valves, electrolytics, speakers, neters, also components, LOWE BROS., 9a, Diana Place, Euston Rd., N.W.I. Eus. 1636/7.

WANTED, BC 610 halicrafters. ET 4336 ceivers and spare parts for above. also BC 221 frequency meters; best prices.—P.C.A. Radio Beavor Lane, Hammersmith, W.6.

A LWAYS buying scrap mercury, contacts, points, all kinds of scrap, high-grade and non-ferreous scrap metals and scrap precious metals, any form, top prices.—Belgrave Buyers (W) 5. Belgrave Gardens, London, N. 99, Mal. 7513.

Mai. 7515. WANTED, signal generators types TF146, TF390C, TF762A, frequency meters BC221, TS174, T5175; also receivers types AR86, etc., APR4 or similar.—Send price and details to Hatfield Instruments, Ltd., 175. Uxbridge Rd... Hanwell, W.7. Tel. Ealing 0779/9857. [0037

Hanwell, W.1. 181. Earny VALVES WANTED ALL types of valves required for cash; state quantity and condition.—Radio Facilities, Ltd., 38. Chalcot Rd., N.W.1. Primrose 9090, [3906]

CABINETS LEWIS RADIO have the best selection and finest finish.—See page 150. [0224

CABINETS made to order; Bass reflex speaker cabinets, all types and finishes.— See display advertisement, page 156. A. DAVIES & Co. (Cabinet Makers), 3, Park-hill Place, off Parkhill Rd., Hampstead, N.W.3, Guillver 5775

Guiliver 5775 WALNUT radiogram and 'clevision cabinets, soundly constructed; stamp for details.-R. Shaw, 69. Fairlop Rd., Leytonstone, E.11. [3193]

METERS WANTED We urgently require meters of all types, any quantity, large or small; prompt cash. ANDERS FLECTRONICS, Ltd., 91, Hampstead Rd., London, N.W.1. Euston 1639. [3738]

REPAIRS AND SERVICE MAINS transformers rewound, new trans-formers to any specifications. MOTOR rewinds and complete overhauls; first-class workmanship; fully guaranteed. F.M. ELECTRIC Co., Ltd., Potters Bldgs., Warser Gate, Nottingham. Est. 1917. Tel. 47698.

47898. [0113

LOUDSPEAKERS repaired promptly.-Model Loudspeaker Service, Bullingdon Rd., Oxford. (3690

MAINS transformers, E.H.T.s. chokes, field wound or manufactured to any specification. LADBROKE REWIND SERVICE, LTD., 8208, Harrow Rd., London, N.W.IO.

Harrow Rd., London, N.W.10. [ULL TRANSFORMER rewind service. mains, E.H.T. transformers and chokes, prompt delivery, range of replacement types ex-stock or manufactured to your specification. METROPOLITAN RADIO SERVICE Co., 75, Kilburn Lane, London, W.10. Ladbroke 2296. [0200

24-HOUR service, 6 months' guarantee, any transformer; rewind, mains outputs and i.f.s., etc.; all types of new trans., etc., sup-plied to specification; business heading or ser-vice card for trade prices.—Majestic Winding Co., 180, Windham Rd., Bournemouth. [2526

Co., 180, Windham Rd., Bournemouth. 12526 ELECTRICAL test instruments repaired and recalibrated, all makes, ammeters, volt-meters, multi-range test meters; meters sup-plied or converted to any range.—Electrical Instrument Repair Service, 329, Kilburn Lane, W.9. Ladbroke 4168. D.C. BOULTON for repairs to any loud-speaker; specialists on heavy and P.A. types; cone assemblies, field colls, repair acces-sories, pressure units, microphones; trans-formers rewound and to specification; motor rewinds.—Lumby St., Manchester Rd., Brad-ford. Tel. 22838.

AS professional sound recordists and mem-bers of the Association of Professional Recording Studios, we are particularly well qualified to give and service on all aspects of sound recording and reproduction; circuits designed, prototypes built, repairs and modifications carried out quickly and

modifications carried out quickly and thoroughy CALLERS by appointment only. please. ARIEL SOURD 5.7. Lancaster Mews, London, W.2. Tel. Paddington 5092. [0026 A RMATURE rewinding service to the trade, vacuums, drilks, grinders, hood dryers, dental motors, vacuum cleaner armatures re-placed from stock; 24 hours's service; every job guaranteed; we also specialize in complete over-nauls and rebuilds of vacuum cleaners; all vacuum cleaner parts, hoses, bearings, fans, brushes for any make in stock.-Regam Elec-tric, 95. Park Lane, Leeds, 1. [0028]



Trade enquiries to sole distributor. SAM MOZER

Edm. 7707

95, Kendal Avenue, N.18.

The Mullard 5 Valve 10 Watt HIGH QUALITY AMPLIFIER as demonstrated at the Radio Show

can now be heard at




Component Specialists since Broadcasting started who can supply all the parts for under £8 (less valves)

Priced parts list available

Full details are contained in a booklet by Mullard technical experts, price 2/6 from:

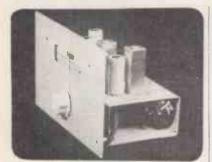H. L. SMITH & CO. LTD. 287/289 EDGWARE ROAD, LONDON, W.2 Telephone : Paddington 5891 Hours 9 till 6 (Thursday I o'clock)

Near Edgware Rd. Stations, Metropolitan & Bakerloo



F · M · TUNERS

Basic Model " A," is thoroughly proven in sensitivity, stability and reliability. Early deliveries are being

aintained.	These a	re m	use	rom	BOGDOF	10	191
Incorpo	rating cle	ctrica	l and	mech	nanical	ban	d-
	unique						
	stabilit						
	Closely						
	Addition						
	rontplate,	. " 3-	D ''	scale	, and	late	st
magic e	ye.						

The kit version uses the same new miniature VHF type components. Fully worked chassis is stove

The kit version uses the same new miniature VHF type components. Fully worked chasals is stove enamelied, and wound tested coils are included, it is complete with valves, even nuts and bolts. F.M. with really sensitive Medium Wave reception is possible with the CB4 double superhet. Incorporates variable de-emphasis, variable matching, ferramic rod serial, mains power supply. Single or push-pull output can be added. Ar hand built "BEL product.

	Model " A "	£11	17	6	
	"A "tuning scale, magic eye	£2	0	0	
	Standard power unit Aerials, 5/- and		10		
	CB4, less output stage, mains				
	"B" local station receiver	£21	0	0	
	all these, our new Mullard				
ur	transistor receiver		mer	unu	00

He

BEL SOUND PRODUCTS CO. MARLBOROUGH YARD N.19. Short walk Archway stn. 25 mins from West End. Ring ARC 5078.



General Wireless Courses. We definitely Guarantee

"NO PASS-NO FEE"

If you're earning less than £15 a week this enlightening book is for you. Write for your copy today. It will be sent FREE and without belieview copy today. It without obligation.



REPAIRS AND SERVICE SERVICE sheets for hire or sale over 2,000 models, radio and television; list 1/-; s.a.c enquiries.-W. Gilbert, 24, Frithville Gardens. London, W.12. Tel. She, 3052. [3315

R EWINDS, mains transformers, chokes, REWINDS, mains transformers, chokes, Solenoids, R.F., E.H.T. colls, etc.; new types including "C" cores, designed or to specifica-tion; you: enquiries will receive prompt atten-tion.—Melton Metallurgical Laboratories, Ltd., Transformer Section, 387-9, Ashley Rd., Park-stone, Poole, Dorset. I3998

PAINTS, CELLULOSE. ETC. PAINT spraying handbook, 3/6 post free, cellulose and synthetic paints and all spray-ing reoutistes cuppied; catalogues free.—Leo-nard Brooks, 53. Harold Wood, Romford. [0207

WORK WANTED A.I.D. approved Govt. contractors seek work. Bel, London, N.19. Arc. 5078. [0183]

ELECTRONIC equipment made to order; wiring assembly contractors, prototypes developed.-R.A.E. Mfg. Co., 135a, Kentish Town Rd., N.W.I. Gul. 7011. [0219

CAPACITY AVAILABLE VACUUM impregnation capacity available, Hadfields Solventiess to RCS214 Specifica-tion — Enquiries to, Avis & Baggs, Ltd., Gos-brook Rd., Caversham, Reading. Tel. 71753 [0094

HIGH fidelity L.P.s from your own tapes. HIGH fidelity L.P.s from your own tapes. "EROIGA" Recording Services (Regd. 1949). 31 Peel St. Eccles, Manchester. ECCLES 1624. Director: Thurlow Smith. A.R.M.C.M.

METALWORK, all types cabinets, chassis, racks, etc., to your own specification; capacity available for small milling and cap-stan work up to lin bar. PHILPOTT'S METAL WORKS, Ltd. (GAB1), Chapman St., Loughborough. [0208

FRAMES D. & P. 10 wire Mk. 3 sets, ref. no. YA.6562; quantity available: accept 10/- per set for minimum quantity of 50.-Box 0740.

DAVENSET HT3 high voltage battery charger, 3 independently controlled circuits suitable AC240, recent complete maker's overhault; £20 o.n.o.-Waterloo Garage, 5-7, Coral St., S.E.1.

YOUR own tape recording transferred to disc.—Write, call or 'phone Queensway Private Recording Studios, 123, Queensway, W.2. Tel. Bay, 4992. Studio recordings, tape recording service.

BUILD your own TV and learn about its operation, maintenance and servicing; jualified engineer-tutor available whilst you are learning and building.—Free brochure from E.M.I. Institutes, Dept, WW.58, London, W.4. (Associated with H.M.V.)

COPPER wires enamelied, tinned, Litz, cotton, Csilk covered, all gauges; B.A. screws, nuts. Vashers, soldering fass, evelets, ebonite and laminated bakelite panels, tubes, coll formers; Tufnol rod. headphones, flexes, etc.; latest radio publications, full range available; list, s.a.e.; trade supplied —Post Radio Supplies, 33, Bourne Gardens, London, E.4. [0138

BRITISH SOUND RECORDING ASSOCIA-TION. Details of membership, open to the professional sound recording high quality reproduction and other branches of audio engineering, together with details of the Lon-regimeering, the second second second second Portsmouth and Cardin Contres, may be ob-tained from the Hon. Membership Secretary, H. J. Houlgate, A.M.I.E.E., 12, Strongbow Rd, 10031 f0031

PATENTS [0031] THE proprietor of British Patent No. 573313 enilded "Multiple section electronic tube and method of making it," offers same for icence or otherwise to ensure practical work-ing in Great Britain—Inquiries to Singer. Stern & Carlberg, 14E, Jackson Blvd., Chicago 4, Illinois, U.S.A. [3926]

1 IIII0015. U.S.A. [3926] SITUATIONS VACANT The engagement of persons answering these advertisements must be made through the local office of the Ministry of Labour and National Vervice, etc., if the applicant is a man aged 18-64 or a woman aged 18-59 inclusive, unless he or she or the employer is excepted from the provisions of The Notification of Vacancies Order, 1952.

DVERTISEMENT for Δ

A DUERTISEMENT for RADIO and Television Repairer Instructor. RADIO and Television Repairer Instructor. Letchworth Government Training Centre. Un-established post. Should possess thorough knowledge of basic radio and television theory combined with considerable practical experience of fault-finding, alignment, adjustment and servicing of commercial radio and television re-ceivers. Able to instruct from first principles and to demonstrate use of bench tools and re-path of combined sets for ratio and set and a result of the first principles and to demonstrate use of bench tools and re-path of configuration of 5640 p.a. 18 days' annual eave with pay.—Apply Ministry of Labour and National Service. Employment Exchange. Letch-worth. [3977]



12

AT

Bouquets praising the occellence of Savage Transformers continue to reach us from enthusiastic users all over the world.

"Thank you for making the transformer on order 7/1384 so quickly. The transformer has been tried out and is working satisfactorily." B. E. A. Southgate.

"After getting home the first thing I did was to install the transformer and I must say that it is more than satisfactory." R. A. K. Johannesburg.

" In April 1251 you supplied me with a 2B36B output transformer which has given me every satisfaction on my Williamson amplifier." G. T. R. Leeds.


"The writer purchased one of your mains transformers in 1930 when your premises were somewhere around Clerkenwell. It has been in continual service since that date and when last seen was still functioning perfectly at Lancing. G. E. Southampton.

"Your unit arrived in good condition and caused a minor sensation when unpacked. The audio chap there said 'That is the kind of service vou dream about but seldom get."

D. M Toronto.



WIRELESS WORLD

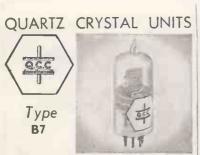

The type B7 unit is mounted in the standard B7G valve envelope and is hermetically sealed an fully evacuated.

Available for the 'requency ranges from 100 kc/s Available for the requency ranges from two kcjs to 500 kcjs, and from 3 Mcjs. to 16 Mcjs. Gold electrodes applied by cathodic sputtering give permanence of calibration. Normal adjustment accuracy 0.01% Max, adjustment accuracy 0.003%

Early delivery can be given of some frequen-cies, and we will be pleased to quote for your specific requirements.

THE QUARTZ CRYSTAL Co. Ltd 63-71 Kingston Road, NEW MALDEN, SURREY

Telephone

MALden 0334

Coules, etc.. OUARTZCO NEWMALDEN

THE OSRAM NINE-ONE-TWO AMPLIFIER INSTRUCTION BOOK and HIGHEST QUALITY COMPONENTS Available from **COVENTRY RADIO** 189. DUNSTABLE ROAD, LUTON. 'Phone : 2677. Price 3/6, plus 3d. postage also Our 1954-5 Component Catalogue at 1/-

Good Investments

SEWING MACHINE MOTORS. New and guaranteed, radio suppressed, 230 volts A.C./D.C., with fixing bracket, foot control and needls light, £6/10/-. Carr. 2/6.

BATTERY CHARGERS. The Lesdix "NITN-DAY " Battery Charger keeps your accumulator in good order during the winter months. Double wound transformer, metal rectifier wired in vent, metal case with Ammeter and terminals; for use on 230 volt A.C. 50 cycle supply, output 12 volts 4 amps., 85/-, carr. 3/6, or 6 volts 3 amps., 75/-, carr. 3/6.

FLEXIBLE DRIVES for small motors, 7ft. long, 5/6, post 1/-.

TERRY ANGLEPOISE LAMPS for drawing boards or Workshop wall or machine fixing. Wil. stay in any position; new, with \$.[.C. Lampholder, flex and shade, 35/-, post 2/6.

REPAIRS to Variable Slider Resistances and Motor Starters; best quality resistance wires used, prices moderate.

Leslie Dixon & Co. Dept. A, 214 Queenstowa Road, London, S.W.8

Telephone: MACaulay 2159

ULTRA ELECTRIC, Ltd.,

WESTERN Ave., Acton, London, W.3. RADIO & television development engineers. (a) APPLICATIONS are invited f.om senior development engineers with experience and academic qualifications for important work on new development projects. THE posts are permanent and pensionable and offer scope for the right men to work in ideal conditions in modern, well-equipped labora tories.

conditions in inverse. As a set of the per-tories. PLEASE write in strict confidence to the Per-sonnel Manager for an interview appointment. (b) JUNIOR engineers (aged 21/29) are also required, and app.cants for these posts should have some technical training and preferaoly previous experience. Please write as above. [3572]

TLTRA ELECTRIC, Ltd.,

WESTERN Ale., Acton, London, W.3. ELECTRONIC development engineers are required in all grades for work on: (a) sub-milaturisation of WEP, radio and audio circuitry; (b) transistor applications; (c) VHF communication; (a) pulse techniques; (e) radar and radio navigation. APPLICATIONS are invited from:— (a) SENIOR development engineers with degree or equivalent qualifications, and more than five years' experience in one or mole of the above fields.

tields

helds. (b) JUNIOR engineers with degree or HNC with or without experience for work in the acove fields. (c) TEST equipment development engineers with experience of design of test equipment to meet production requirements. THE posts are permanent and pensionable, and offer scope for the right men to work in ideal condition, in modern, well-equipped labora-tories.

tories. PLEASE write, in strict confidence, to the Per-sonnel Manager for an interview appointment. [3573

. V. ROE & Co., Ltd.,

A WOODFORD Aerodrome, Cheshire. HAVE vacancies in their newly formed WEAPONS Research Division. AERODIVNAMICISTS. WITH Honours Degree in Physics, Mathematics or Engineering and at least two years experi-ence are required to work on an aerodynamics group on aerodynamic theory and analysis of new weapon projects. Candidates should be familiar with supersonics. MATHEMATICIANS. WITH Honours degree to work on flight


familiar with supersonics. MATHEMATICIANS. WITH Honours degree to work on flight dynamics and studies of control systems, a cnowledge of numerical mathematics would be an advantage. ELECTRONIC Encineer. A graduate with research and development ex-perience in electronics or with electro-mechani-sal devices. BOOD salaries and prospects ENSION and life assurance scheme. APPLY giving full particulars of academi-training and experience to:--A. V. ROC & CO., Ed., WEAPONS Research Division, WOODFORD. Cheshire. ELECTRONIC Technicians.

L APPLICATIONS are invited for radar and electronic technicians for appointments as civilian technical assistants Grade III, tele-communication mechanics or electricians with R.E.M.E. in Anti-Aircraft Command in the

communication mechanics or electricitans with R.E.M.E. in Anti-Alteratt Command in the Newark area. (a) TEOHAL assistants should hold Ordinary National Cartificate in Electrical Engineering ordination and the R.E.M.E. foreman or sig-ransament artificer R.E.M.E. foreman or sig-nals. Royal Signals C.P.O., Royal Navy or senior N.C.O. R.A.F., with service radar or electronic qualifications; starting salary at 23 is approx. (b) TELECOMMUNICATION mechanics and electricians should have had several years' ex-perince in the repair of wireless and line rodiciency pay of up to 30/- per week. ALL applications should be submitted to A.D.M.E H.Q. 5 A.A. Group. "Cloverlands," new digate Lane, Kimberley, Nottingham, star-ing age, qualifications and experience. [3593 ARAWING office training.

DRAWING office training.

ARVING office training. ARCONI'S WIRELESS TELEGRAPH Co., School as from February 1955 onwards. A six an this course with fixed salary at the Drawing Office School, course with fixed salary at the Drawing Office School, course with fixed salary at the Drawing Office School, course with fixed salary at the Drawing Office School, course with a second salary at the Drawing Office School, course with the Company's Design will be available at Acton, London, A few posts workshop experience. Must produce evidence of drawing ability. Preferably have O.N.C. Mech. or E.ee. A limited number of posts will be available. A limited number of posts will be available. A limited number of posts will be available. The preferably have O.N.C. Mech. or E.ee. Five: DAY week. Pension and Life Assurance Scheme. Social and Athetic C'ub APPLY (in writhing) giving full details of education, training, experience, etc. (including HM. Forces). to The Secretary. Marcon's Wireless Telegraph Co., Ltd., New St., Chelms-ford, Essex. [4056]

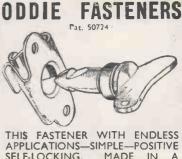

MADE IN SELF-LOCKING. VARIETY OF TYPES AND SIZES. SPECIAL FASTENERS TO SUIT CUSTOMERS' REQUIREMENTS. WIDELY USED IN THE RADIO INDUSTRY.

Illustrated brochure and other Information will br gladly sent on request. DEPT "W.W."

3ddie, Bradbury & Cull Ltd., Southampton Tel.: 55'83 Cables: Fasteners, Southampton



courses in all branches of Englasering— Mechanical, Electrical, Civil, Auto. Aero., Radio, etc., Building etc. If you're earning lesathan£15a week, tell us what interests vo and writefor your copy of "ENGINEERING OPPORTUNITIES oday-FREE B.I.E.T.


.87 College Louse, 29-31. wright's Lane, fondon, W.8.

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY



CONVERTOR TYPE 26. For conversion from channel 3 to channel I, complete with self contained power supply unit and totally enclosed in a handsome well finished steel case. Price complete, £11/17/-. Also available in chassis form less HT supply but including mains operated heater supply for inclusion in receivers. Price complete, £8 CONVERTOR TYPE AC/4. For weak signal areas. Price complete, £15/15/-. (Leaflets on request.)



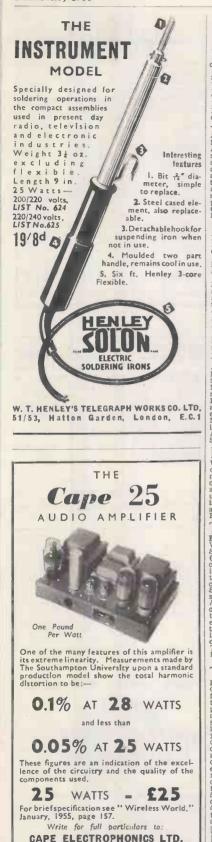

43-45 SHIRLEY HIGH ST., SOUTHAMPTON Telephone: Southampton 74251

SITUATIONS VACANT

ELECTRONICS Engineers. VACANCIES exist in the expanding electronics division of Saunders-Roe. Ltd. The range of work is unusually wide and interesting, covering design and development of analogue and digital computers, electro-mechanisms, measuring appa-ratus, strain gauging equipment and tech-niques, etc. Salarles offered are commensurate with qualifications and experience. Assistance with gualifications and experience. Assistance will be given with accommodation. WRITE stating age, experience, etc., or send P.C. for application form to the PERSONNEL Department (Ret. WW/17), Saun-ders-Roe, Ltd., East Cowes, I.o.W. [3929]

LONDON COUNTY COUNCIL.

LONDON COUNTY COUNCIL. NORWOOD Technical College, April, 1955; Assistant Grade B to teach telecommunications subjects to C. & G. Full Tech. Cert. standard; additional television advantage; must have degree or equivalent, together with teaching and/or industrial experience; salary within the scale £585×£25-£964 plus London allow-ance £36 or £48; commencing and maximum salary according to age, qualifications and ex-perience.-Application forms from Secretary at College, Kn.gats Hill, S.E.27, returnable by February 12 (1655). [4018 MURPHY RADIO require:--

MURPHY RADIO require:--1. SENIOR Radio Receiver Designer. 2. INDUSTRIAL Chemist with previous experi-ence of plating and finishing processes; the applicant will be in charge of the chemistry laboratory and should be able to deal with all chemical problems arising out of radio and television design and productions. 3. VERSATILE Engineer with sound knowledge and application and well verred in quality con-trol and life test methods; thorough knowledge of plastic materials and good theoretical back-ground an advantage. APPLICATIONS staling which vacancy referred to and giving details of age, experience, quali-fications and salary should be addressed to-personnel Department (A.L.), Murphy Radio, Ltd., Welwyn Garden City. [4003 RAUGHTSMEN end designers.

DRAUGHTSMEN and designers.

DRAUGHTSMEN and designers. E. K. COLE, Ltd., Ekco Works, Southend-on-Sea, have the following vacancies:--MOULD designers and jig and tool draughts-men for the plastics division. ELECTRONE, radio and theirision designers and gaugatimeters MECHANICAL draughtsman for plant layout in the production engineering department. APPLICATIONS to the Personnel Manager, Southend-on-Sea 49491. [4028 MCTHADDS development section of Pye, Limited, has VACANCIES for senior and junior television entruity engineers with drive and initiative; salaries dependent on qualifications and experience.--Apply to Chief Television Engineer, Pye, Ltd., Cambridge. [599 TECHNICAL Instructors (telecoms) for work Notal. SIGNALS (Civilian Establishment).

TECHNICAL Instructors (telecoms) for work with ROYAL SIGNALS (Civilian Establishment), Vacancies exist ur 1 Training Regiment Royal Signals for unestablished Grade III instructors (with prospect of eventual establishment). Suc-cessful applicants fill be required to undertake interesting and varied instructional duties in the fields of electronics and the basic prin-ciples of radio and/or line communications. Salary socording to age. Liberal leave. APPLICANTS should have a sound knowledge of radio and/or VF telegraphy and carrier telephony. Academic qualifications are not essential, but O.N.C. or City and Guids Cer-tificates would be an advantage. Training in instructional techniques would be given to suc-cessful applicants. Apply to: THE Chief Instructor, 1 Training Regiment. Royal Signals Catterick Camp, Yorkshire. THOMENTS (MARCE) (HF and VHF radio)

Royal Signals Catterick Camp, Yorkshire. [4032] TECHNICAL Instructor (HF and VHF radio) required for POSTS and Telegraphs Dept..Nigerian Federal Govt., for one tour of 12 to 24 months in the first instance. Appointment either (a) on con-tract with salary scale (including expatriation pay) £807 rising to £1.269 a year with gratulty at rate of £100/£150 a year, or (b) with pro-spect of permanency with salary scale (includ-ing expatriation pay) £750 rising to £1.175 a year. Outfit allowance £60. Free passages for officer and wife Assistance towards cost of children's passages or grant up to £150 annu-ally for maintenance in U.K. Liberal leave on full salary. Candidates must have extensive experience in G.P.O. or with firm of electrical manufacturers in installation and maintenance of HF and VHF radio telephone links...Write to the State sale name in Dock letters. full Quality for and dates at present employed by the General Post Office sould submit their applications through their Establishment Divi-sion. [4035] E

sion. 14033 E LECTRONIC development engineers required for work on industrial electronic, nucleonics. X-ray and electro-medical apparatus. Good con-ditions and pension scheme operating. APPLY to: General Radiological, Limited, Chief Engineer, 15. Clipstone St., W1. 14036




Excellent reproduction with absence of background noise provides an amazing degree of realism when used with Wide Range reproduction equipment. of

The FM81 uses the latest valves and tech-niques; Tuned R.F. stage; Frequency Changer; 2 I.F. stages; Ratio Discrimin-ator; A.V.C.

Tunable between 87.5 Mc/s.-100 Mc/s., the FM81 will receive the proposed National B.B.C. frequency modulated V.H.F. trans-missions as and when installed within approx-imately 60 miles from the transmitter. £21 tax paid.

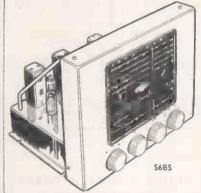Type F.M.82 similar to above, but with preset station selection, separate trimmer for each position. Range of each position 87 Mc/s.-100 Mc/s. Output 2 volts approx Self powered 200/250 v. £24 tax paid.



- SGBS 9 Band (6 Electrical band spread) with SGBS R.F. F.C 2 1.F. Delayed Amplified A.V.C. Variable Selectivity. Fly Wheel Tuning. Tropicalised. Suitable for use with any High Quality Amplifier. £44. Tax paid.
 - A new model similar to the well-known S6BS but only 3 Wave Bands; 16m-50m, 195m-550m, 800m-2,000m. £30. Tax paid.
- As S6 but 4 Wave Bands; 12.5m-37m, 35m-100m, 90m-250m, 190m-550m. £30. SGE Tax paid.
 - 3 Wave Bands. 16m-2,000m, R.F. pre-Amplifier, variable selectivity I.F. Delayed Amplified A.V.C. very low distortion. £21/6/8. Tax paid.
- S5E As 55 but 12.5m-550m. £21/6/8. Tax paid.

The Standard high-quality Feeder Unit Specification as S5 but without R.F. amplifier. £16. Tax paid. **S4**

A modified version of all models is available for use with Leak, Acoustical and other High Quality Amplifiers.

C. T. CHAPMAN (Reproducers) LTD. RILEY WKS., RILEY ST., CHELSEA, S.W.IO FLAxman 4577/8

Export Enguiries Invited

156



17 Victoria Gardens, London, W.11. Park 6636



You can see your cabinet being made in our cabinet-making workshop.

Oak, 30

£9.10.0 £9. 0.0

Cabinets made to order. Armstrong Chassis and Amplifiers. The Leak TL/10 Amplifier. LOUDSPEAKERS.

Open till 5.30 Saturdays A. DAVIES & Co. (Cabinet Makers) 3 Parkhill Place, off Parkhill Road, London, N.W.3. GULLIVER 5775.

WIRELESS WORLD

SITUATIONS VACANT WIRELESS station superintendents required

SITUATIONS VACANT WIRELESS station superintendents required NIGERIA Posts and Telegraphs Department for one tour of 18 to 24 months in the first instance. Option of appointment (a) on tem-porary terms with salary scale (including expatriation pay) E664 rising to £1,392 a year. Gratuity at the rate of £100/£150 a year, or (b) with prospect of pensionable employment with salary scale (including expatriation pay) £750 rising to 1,175 a year. Outfit allowance £60. Free passages for officer and wife. Assistance towards cost of children's passages or grant up to £150 annually for maintenance in U.K. Liberal leave on full salary. Candi-dates must have had wide practical experience of modern redio technique and equipment, in particular V.H.F. Equipment, and equipment. WRITE to the Crown Agents, 4. Millbank, London, S.W.I. State age, name in block letters, full qualifications and experience. and quote M2C/30086/WF. [4037]

letters, full qualifications and experience, and quote M2C/30086/WF. [4037] BURNDEPT, Ltd. have vacancies, due to ex-pansion, for: I. Telecommunications Development and Re-search Engineers. Qualified to operate as Pro-lect Leaders under uptopriedary designs. Ex-perience medic be within one or more of the full dama drouge station designs, with special emphasis on U.H.F. techniques within this field. (b) F.M. Single- and multi-channel equipment development in both V.H.F. and U.H.F. bands. (c) Development of subminiaturisation tech-niques and special components. 2. Telecommunications Laboratory Instrument Mechanics and Wiremen. MUST be fully conversant with modern minia-ture and subminiaturisation techniques, and be able to wire from circuit diagrams on own initiative. Those capable of converting experi-mentally wired models to final stage by own initiative will receive special consideration. Ex-cellent working and model shop facilities. APPLICATIONS giving full particulars, includ-ing present salary, should be sent in confidence to Personnel Manager, Burdept, Ltd., Erith. Kent. [590]

SHORT BROTHERS & HARLAND, Ltd., Bel-for their research department. THE position involves responsibility for pro-viding equipment, supplies and services in the laboratories; also control of laboratory per-ronnel.

CANDIDATES, also control of labora-connel. CANDIDATES should possess organizing ability, and be familiar with the running of a labora-tory or workshop. EXPERIENCE in light electrical equipment or precision instruments essential. CONSIDERABLE tenacity and drive necessary to co-ordinate and sustain action with external official bodies. THIS appointment is suitable for a retired forcer of one of the technical branches of the

THIS appointment is suitable for a retired officer of one of the technical branches of the Services ASSISTANCE with housing, and with removal

expenses. SEND full details of age, qualifications and ex-perience, quoting Ref. 613/St. App., to Staff Appointments Officer, Short Bros. & Harland, Ltd., P.O., Box No. 241, Belfast. [3344

PERSONNEL required for employment by Canadian electronics company in Canada,

L'Canadian electronics company in Canadian as follows:--TECHNICIANS.--Qualifications: Higher National Certificate in electrical engineering or City and Guilds Certificates in Radio Engineering, plus 5 years' experience in radar production, instal-lation and esvicing. ENGINEERS.--B.Sc. or A.M.I.R.E., plus 5 years' practical experience in radar, preferably radar fire control. APPLICANTS should be natural born British subjects.--Write, stating age, experience, full qualifications, to Box 07(41).

RADAR and Electronics.—Senior, Intermediate and junior development engineers required. Salaries according to experience and ability. ALL-POWER TRANSFORMERS, Ltd., Chertsey Rd., Byfleet, Surrey. [3973

Ma., Bytheet, Surrey. [3973
 A. V. ROE & Company Limited have the following vacancies for electronic and mechanical engineers in their Weapons Research Division at Woodford:
 (a) SENIOR Engineer with Honours Degree and considerable experience of development of electronic computors or simulators to take charge of a group developing guided weapon simulators.
 (b) SENIOR Engineer with Honours Degree and considerable development experience to take charge of a group developing hydraulic and pneumatic servo and precision mechanical devices.

pheumatic servo and precision international devices. (c) A number of engineers with either Honours Degree in Physics or Engineering or appro-priate research or development experience to work on guided weapon computing navigation and control systems. SALARIES will be commensurate with ability and experience. Applications, giving full par-ticulars of age, qualifications and experience. etc., should be addressed to: The Chief Designer, Weapons Research Division, A. V. Roc & Com-pany Limited, Woodford, Cheshire. [3792

R ADIO/TV service engineers for inside and outside work; attractive salaries and excel-lent prospects for right men; West-End and N.W. areas of London.—Apply Broadmead Wire-less Co., 123, The Broadway, S.W.19. [4049 Wire-



VOLTMETERS. Moving coll 0-12 and 0-120. Panel mounting with resistance complete 2jin. overall mounting with resistance diameter, carr. paid, 5/-.

diameter, carr. paid, 5/-. CHARGING BOARDS. Control Panel Only. 24 v., 1,260 watts. Includes five lin. moving coll ammeters (1, 0-40 a., 4, 0-15 a.). One moving coll volumeter 0-40 v. Five heavy duty sliding resistances, etc., complete in metal case as shown with fold-back doors. Size, 18 × 17 × Sjin. Onered at less than half the component value. Price, carriage extra. \$24/18/6.

component value. Price, carriage extra, §4/19/6. PHILCO RADIO SETS. 3-wave 5-valve. Fully re-conditioned and tested. Incorporating 2 speed tuning. In wainut cabinet. A.C. or Universal Mains. Approx. size: 18 x 14 x 59, 55/10/.- Carr. paid. 4-VALVE (Used) SUPERHET OTILITY RECEIVERS Fully reconditioned. Medlum waveband only. 6[Jin. P.M. speaker. Complete in pinewood cabinet. fize 13] x 12 x 46, 200-250 A.C. mains, §3/18/6. Carr. paid.

CAMBRIDGE UNIPIVOT METERS. Range 0-60 microamperes. High grade laboratory instrument. Cu. Res. 12.4 ohms at 20°C. For Callers only, 27/10/-. TRANS-RECEIVER TYPE 18. Mk. 3. H. T. 120 volt. L.T. 3 volt. Frequency 8-9 mcs. Complete in case with aerials, etc. Less mike and phones. £3/15/- carr. paid. N.B.-Carriage charges relate to British Isles only

23 LISLE ST. (GER. 2969) LONDON, W.C.2 Closed Thursday 1 p.m. Open all day Saturday

MORSE **CODE** Training



COURSES for BEGINNERS and OPERATORS, also a

SPECIAL COURSE for passing the G.P.O. Morse Test for securing an AMATEUR'S TRANSMITTING LICENCE. Send for the Candler BOOK OF FACTS

It gives details of all Courses Fees are reasonable

Terms: Cash or Monthly Payments

THE CANDLER SYSTEM CO (55W) 52b ABINGDON ROAD., LONDON, W.8 Candler System Co., Denver, Colorado, U.S.A



METER DAMAGED YOUR



Leading Electrical Instrument Repairers to the Industry

Contractors to the Ministry of Supply and General Post Office epairs by skilled craftamen of all makes and types of Voltmaters, Aumeters, Multramage Test meters, Electrical Thermometers, Recording Instruments, etc. Quick deliveries-from speedy estimate send defective instruments by registered post to:---L. CLASER & CO. Electrical Instrument Repairers 96-100 ALDERSGATE STREET, E.C.I (Tel. : MONarch 6822)





"LAFCO" EASY PAYMENT GUIDE LOOK FOR US EVERY MONTH HERE

VILLIERS ROAD, LONDON, N.W.2.

DEALERS' ENQUIRIES INVITED.

Telephone

METRIX TEST METERS (see their illustration-"Wireless World" November Issue, page 114), Model 410, 19 ranges, £9/2/11 or 22/4 deposit and 8 × 22/4. Model 460, 28 ranges, £14/6/4 or 35/- deposit and 8 × 35/-.

35/- deposit and 8×35/-. SOLDER THE "PRIMAX" WAY FOR 8/7 SOLDER THE "PRIMAX" WAY FOR 8/7. (Cast Price 70/-. (Cast Price 70/-. da weights only 23 oz. OTHER 90LDERING EQUIPMENT AS FOLLOWS:

FOLLOWS:

HERLEY SOLON TYPE 625, 19/8 CASH OR 2/6 deposit and 8 monthly payments of 2/6, 65 WATT TYPES, OVAL BITS, 23/8 CASH (OVAL BITS) 40/4 or 4/11 and 8×4/11. 240 WATT TYPES (OVAL BITS ONLY) 66/-or 8/1 and 8×8/1.

or 8/1 and 8×8/1. SOLO SOLDER TOOL ready to be run off a 8-volt battery (car or m/cycle battery) 37/6 CABH or 4/7 deposit and 8×4/7. The transformer is available to enable the tool to be run off 220-230 v. A.C. mains at an additional 28/3 or 3/6 and 8× 3/6. A combined De Luxe unit consisting of the Tool and Transformer permanently mounted and wired, in handsomely finished cartons, 85/- or 10/5 and 8×10/5. (s.a.e.for Leafet.) ADCUA & SUM 6 2000 deposit and 8 monthly ADCOLA. 25/6 or 3/2 deposit and 8 monthly payments of 3/2.

payments of 3/2. Also Handyman's tools as follows: B, & D. Hu. Electric Drill 13/11 (deposit and 8 monthly payments of 13/11 (25/13/6 CASH). Hu. Electric Drill Kit 27/11 (and 8 × 12/3 (25/5/). Gin. Sander Polisher Kit 23/- and 8 × 23/-(25/17/6). (This list is not complete.)

Desk 117, LAFCO COMPOUNDS LTD. 3, CORBETTS PASSAGE, ROTHERHITHE NEW RD., S.E.16. BER 4341 (Ext. 1)

appliances. (c) V.H.F. mechanisms or U.H.F. circuits and tuning

(c) V.H.F. of U.H.F. circuits and tuning mechanisms. (d) RELAYS and vibrators. (e) LOUDSFEAKERS and acoustics. A good salary and a progressive future are offered to men who can design components suitable for high production rates, while maintaining standards of quality and performance. There are also vacancies for qualified engineers and draughtsmen with less experience who will be able to undertake responsible design work after a period in the laboratory. All posts are permanent and pensionable and a modern indovatory provides efficient and agreeable working conditions. Send particulars of qualifications, experience who will be able to the personnel Manager. The Pessey Company, Limited, liferd, ESSEY. (4058)

Limited, Ilford, Essex. [4009] NATIONAL COLLEGE OF RUBBER TECH-NOLOGY, Northern Polytechnic, Holloway, London, N.7. SENIOR laboratory technician with knowledge of electrical circuits and some experience with electronics required for duties mainly in Physics Laboratory. Department contains X-ray dif-fraction equipment, radio frequency dielectric heating appartus and electron microscope. Salary scale £401X£25—£503 with possibility of proceeding to maximum of £590. APPLY in writing giving full details of age, qualifications, experience, etc., to the Secretary. [3040]

SERVICE engineers; all-round experienced and improvers required.—Radio Centre, 33. Tottenham Court Rd., London, W.1. (4022 A PPLICATIONS are invited for trainees as studio installation and maintenance engin-eers for home and overseas service with well-known television company.—Apply Box 0483.

TELEVISION Service Engineers required for Inside and outside servicing for Central Sotland, must be fully experienced; first-class wages.—Box 0666. [3979

TESTERS required for television and radio manufacturers; good rates for experienced men, N.W. London area. - Write for full parti-culars to Boz 7628. [0032

ExpERIENCED TV engineers reqd; must salaries.-Apply Ernest Coyne, 120/122, Lad-broke Grove, W.10. Bay, 1947. [C4013

SERVICE engineers with knowledge of tape recorders required; permanent position; ex-cellent salary.--Radio Centre, 33, Tottenham Court Rd., London, W.1. [4021

A n expanding instrument firm pioneering new developments in the field of radiation physics has vacancies on its research staff for Electronic Engineers or Physicists with an elec-

APPLICANTS should have a sound theoretical training and considerable practical experience. The posts would be of particular interest to those who wish to obtain experience in new fields of electronic technology. THE laboratory is pleasantly situated in Surrey and a Pension Scheme exists.—Box 0635. [7969]

TECHNICAL salesman required for West End showroom, specialising in HIF1 and tape recorders; knowledge of domestic radio and television also required.—Radio Centre, 33, Tottenham Court Rd., London, W.1. [4020

ENGINEERS required for installation and cperation of television transmission equip-ment, --Apoly in first instance by letter, to Engineer-in-Charge, Pye, Ltd., 11, Hinde St., London, W.1. [3885]

BUYER required for radio manufacturer senior level in similar capacity cssential; four figure salary.—Apply, giving full details of past experience and stating salary required, to Box 0994. expe 0894

14031 TECHNICAL Engineer required by redo and television component manufacturers in Reading area: \$750 per annum.—Apply Gillone Electric. Ltd., Rockstone Works, Rosemary Lane, Blackwater, near Camberley, Surrey, Tel. Camberley 2350.

Camberley 2360. [4053] MCMICHAEL RADIO, Ltd., Slough, Bucks, have vacancies from time to time for electronic engineers to be engaged on Govern-ment projects; those wishing to be considered are invited to write fully to the Chief Engineer. Equipment Division. [0198]


Equipment Division. [0198 Equipment Division. [0198] ExPERIENCED radio testers and inspectors required for production of communication and radio apparatus, also instrument makers, wirers and assemblers, for factory test appara-tus.—Apply Personnel Manager. E. K. Cole. Ltd., Ekco Works Malmesbury, Wilts. [0238 ELECTRONIC Development Engineers, Senior and Junior, with a leaning towards tech-nical writing, to undertake the preparation of instruction manuals. specifications, etc., for guided weapons and like projects. A working knowledge of pulse circuitry and microwave techniques essential. APPLY, giving full details of experience, age etc., to the Personnel Manager, The General Electric Co., Ltd., Brown's Lane. Allesley, Coventry. [3873]



3 MONTHS' GUARANTEE. (On emis-sion). Not Ex-W.D. Had some hours' use. Various types and makes. Picture shown to callers. Carriage and insurance 15/6 extra. Please quote make and type required when ordering. C.W.O.

T.V. 12in. CHASSIS-97/6.

Complete chassis by famous manufacturer, easily adapted to Channel 3. R.F. E.H.T. unit included. Drawing FREE. Easily fitted to Table or Consul model. Owing to this chassis being in three separate units (Power-Sound and Vision-Timbebase inter-con-nected) THIS CHASSIS IS LESS VALVES AND TUBE, but see our catalogue for cheap valves. Our £5 Tube fits this Chassis. List of valves by request. Carr. 5/-.

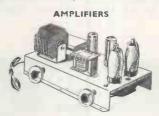

Push-Pull, 77/6. 7 watts output A.C. or Universal. 4 valves and 1 rec. Ideal for Pick-up or Mike. Post 2/6, ready to plug in.

AMPLIFIERS. 57/6. 4 watts output, 3 valves. A.C. or A.C./D.C. Ideal for Pick-up or Mike. Post 2/6, ready to plug in.

SPOTLIGHTS. 8/9. Butlers, new but ex-**SPOTLIGHTS.** 8/9. Butlers, new but ex-W.D. 74 in. dia. 64 in. deep. These lights are similar to those sold for £3-£5, but finished black. This light is easily fitted to dumb irons of bumper. Bulbs now available 6 v. 36 or 48 watt. 12 v. 30 or 48 watt. 4/6 each.

CAR RADIO TRANSFORMERS. 5/9. 6 volt. New. Post I/-.

LADIES ONLY! Treat the lady and your-self to a heated blanket for the home, 37/6 brings a complete heater kit that a lady can fit by herself unoided—with free drawings.

FIRESIDE " RIPPINGILLS " HEATER. TRESIDE "RIPPINGILLS" HEATER. 71/6. For the home, works or office. Although these are used ex-W.D. they have all been overhauled and work perfectly (paraffin). Carriage 2/6.

EXTENSION SPEAKERS



Brand new P.M. speaker (low impedance). Mntd. on polished and veneered baffle stand. 5ft. lead ready connected. ONLY 19/9. Post 1/9.

H.T. BATTERIES. 3/9. 60 volt, 60 + 11 volt (personal portable type), 67 ± 10^{-1} volt (layer type), all Ex-W.D. but fully tested O.K., post 1/-. $87 + 64\frac{1}{2} + 4\frac{1}{2}$ Ex-W.D., only 3/9. Post 1/9.

RECTIFIERS 8/9. T.V. Type. Salvage, guaranteed, 250 volts at 200 mA. Post I/-Salvage,

BEDSIDE T.R.F. RADIOS. 4 valve L. & M. wavebands. Walnut, White or Pale Green Plastic Cabinets. Complete £6/9/6, plus 3/6 p. & p.

Send 24d, for catalogue.

157



LIGHT SOLDERING DEVELOPMENTS LTD... 106, GEORGE STREET, CROYDON, SURREY. Tel. CROvdon 8589



TAPE RECORDERS ONLY

Consult

The Northern Specialists for your

GRUNDIC, PRIMA, WYNDSOR, PLAYTIME & STENORETTE.

etc., etc.

Advice & Repairs.

DIXON'S ELECTRONIC SALES & SERVICE 229 OXFORD RD., MANCHESTER 13 (Nr. University). Telephone : ARD. 4269

TAPE PRE-AMPLIFIER TYPE 4/WRB/2

is of new design, and has been developed specifically for the user with professional requirements, to go with a 3-HEAD TAPE DECK. Comprises separate recording and replay channels with correct equalization characteristics for $7\frac{1}{2}$ and $3\frac{2}{2}$ i.p.s. tape, peak-programme-type meter and circuit, bias and erase supply, DIRECT/REPLAY monitor com-parison switching, cathode-follower output to monitor amplifier. Designed primarily for the WEARITE TYPE 2B TAPE DECK, but suitable for any other good 3-head deck. Deliveries commencing middle January, Please write for full specification, which will be sent as soon as released. sent as soon as released.

ARIEL SOUND 57, LANCASTERMEWS, LONDON, W.2 Telephone: PADdington 5092

WIRELESS WORLD

SITUATIONS VACANT TELEVISION Demonstrations.—Applications are invited for the following appointments: (a) SENIOR Maintenance Technicians.—Appli-cants must have experience of television equip-ments and be capable of accepting technical responsibility for the efficient maintenance of a studio

Interest and be to the efficient maintenance of a studio.
(b) CAMERA Control Technician/Operators.— Previous experience of TV cameras and associated equipment an advantage.
(c) TELECINE Technician/Operators.—Previous experience of slim projection an advantage bus applicants must also have a good technical experience to enable them to maintain this type of equipment. Technician/Operators.—Previous experience of audio amplifiers, microphones, etc., of tage or public addres work an identifier projection and the stratege of audio amplifiers, microphones, etc., of tage good technical between a distance.
THESE posts are suitable for an advantage transfer the seasing a good technical between and anot applicants posteriate in the superiment of a suitable for any program of the superiment and pension-able, successing applicants will normally be assed in London but may be required to travel overseas; please write, giving full details of usperime and quifications to—Box 0775. 1399
N even superior of the English Electric Co.*s

An expansion of the English Electric Co.'s Guided Weapons Division at Luton has created further vacancles for all grades of Senior and Junior Staff for the Electronics Department, particularly the following:-SENIOR Engineer with experience of produc-tion engineering of prototype electronic equip-ment coupled with a working knowledge of electronic circuitry. SENIOR Engineer to lead a large group of engineers and junior engineers in the develop-ment of specialized electronic test gear for factory and field use. SENIOR Engineer with sound fundamental knowledge of electronics coupled with an ability to apply it to general circuit develop-ment.

ability to apply it to general circuit develop-ment. SENIOR Instrumentation Engineers with either a degree or H.N.C. together with experience of the design of transducers for use with electronic or bridge measuring systems. SENIOR Engineer to lead a small group con-cerned with the development and field trials of ground radar equipment. Applicants should have had considerable previous experience of similar wor! SENIOR Engineer for Radar experiments and maintenance. Applicants should have a wide experience of Services radar equipments. SENIOR Engineer for missile telemetry instal-tation planning. Applicants must be familiar with existing blemetry systems and measuring techniques. Although no trials work is in-volved this post would suit a man with trials envertence.

experience. JUNIOR Engineers and Laboratory Assistants are also required to assist in the above work. HOUSING assistance will be given in some

ALL of the above posts are permanent and progressive and attractive salaries are offered to the successful applicants A STAFF Pension Scheme is in operation.— Applications to Dept. C.P.S., 336-7. Strand. W.C.2, quoting Ref. S.A.38B. [4012

W.C.2, quoting Ref. S.A.36B. [4012 **A**PPLICATIONS are invited for posts in a development laboratory located in North-amptonshire; minimum qualification required is a degree in physics or the equivalent; ex-perfence in microwave work would be advan-tageous.-Box 0842. [4014 **S**CANNER mechanics wanted, must be able to dismantle and repair mechanical details of radar gear, ex-service radar mechanical trades-men with suitable experience will be considered. - Write, stating experience and wages required. to Box 0738. [3986]

TECHNICAL Assistants. A small number of opportunities exist to enter the factory laboratory of a leading radio and television receiver manufacturer for young men of H.N.C. and O.N.C. standards. These positions provide interesting work in the pre-production stages of large scale manufacture. COMMENCING salarles will be in accordance with age, experience and qualifications.—Please apply in writing to the Personnel Officer, Mitcham Works, Ltd. New Road, Mitcham, Junction, Surrey, quoting reference G.I. [4043 TXYPERIENCED technical executive required Junction, Surrey, quoting reference Gir, resource EXPERIENCED technical executive regulred by successful public television and radio company to supervise national organization for development, manufacture and service; opportunity of directorship for right man; pen-sion.—Full details in strict confidence to Box 0168. [3525]

EXPERIENCED Fault-Finders wanted by Mid-equipment: permanent post located in the Midlands are offered to men with excerience of radar, radio control, V.H.F. equipment.—Write, stating fully experience and salary required, to the Personnel Manager, Box 0394. [3875

Manager, Box 0393. [3876 SENIOR transformer designer required with experience of all types of transformers up to 3,000 kVA; excellent prospects for ar emergetic man capable of supervising juntor engineers, excellent working conditions, pension scheme, canteen, etc.; West London area.-Applications to Box 8135. [3565 E NGINEER, aged 25 to 35, preferably having Higher National Certificate required for the maintenance of electronic equipment and the testing and alignment of new instruments used for quality control and automatic testing of all types of telecommunication cables.-Apply, giving full particulars, to Box 652. [3769

WAFER SWITCHES TO SPECIFICATION

One or more type "H" switches having any desired contact arrangement or water spacing made from parts supplied by A.B. Metal Products Ltd.

Most types despatched within 48 hours

Send for Price List of 82 "standard " arrangements and switch design chart

Orders and enquiries by post only:

SPECIALIST SWITCHES 24 CRANBOURN STREET. LONDON, W.C.2



Kit of parts for the simple construction of a first class Tape Deck

Comprising complete set of accurately machined components with every nut and bolt and full instructions for building a high-quality 2-speed Tape Deck. Very compact, lin, x 74in., taking 600ft. reels. Twin track recording with the very latest type High Fidelity Ferroxcube heads (30-12,000 C/S at 74in.). High-speed capstan, precision balanced flywheel, ball bearing pressure roller giving remarkable freedom from "wow." Fitted with the latest Collaro con-stant speed motor. stant speed motor.

Price £7 10 0 E. W. A. 266, WARBRECK DRIVE, BLACKPOOL



"AUTOMAT" HOME CHARGERS AND KITS

SELENIUM L.T. RECTIFIERS. S.T.C., Westalite, G.E.C., etc., 40 m.a. to 10 amps All new goods with full guarantee.



S.T.C., Westalite, G.E.C., etc., 40 m.a. to 10 amps All new goods with full guarantee. FOOLPROOF CHARGER KITS, Genuinely trouble three and ultra reliable. As solid for 11 years through "W.W." with full data sheet and instructions. No. 1 Samp, rectifier, 65 watt tange, 1 mpregnate of the solution of the solution of the solution and the solution of the solution of the solution of the solution and the solution of the solution of the solution of the solution and the solution of the solution of the solution of the solution and the solution of the s

CHAMPION PRODUCTS

43 Uplanes Way, LONDON, N.21. Phone LAB. 4457.

SITUATIONS VACANT TRANSFORMER Designer regulard for de-velopment projects involving audio-tre-guency power transformers, pulse transformers, oll-filled units, etc.-Apply stating are, guali-fications and experience, to The Personnel Manager (Ref. R.G.), The General Electric Co., Ltd., Brown's Lane, Allesley, Coventry, 10260

ELECTRONIC Engineer required by company in East Anglia to take charge of small but expanding department wiring and testing elec-tronic units for precision instruments; practical production experience essential; pension scheme. —Details of age, experience and salary required to Box 0684. [3976]

JUNIOR designers required to deal with small transformers power, audio, pulse, etc.; specialised training will be given to engineers with suitable basic training and experience — Applications to Technical Director, Gresham Transformers, Ltd., Twickenham Rd., Han-worth, Middx. [3569]

TECHNICAL Corespondence Clerk. A vacancy exists for a radio and television corres-pondence clerk at the new factory of Bush Radio, Ltd., Kew.-Applications should be for-warded with full details of past experience, etc., to the Personnel Manager, Bush Radio, Ltd., Power Rd., Chiswick, W.4. [3983

Power Rd., Chiswick, W.4. 13983
 RADIO and radar testers. First-class men required for work on V.H.F. communication gear and Government contracts for radio and radar equipment by Midiand manufacturers; men with wide experience of fault finding in any of the fields mentioned should write, giving full details, to Box 0393. [3874]
 DECCA RADAR, Ltd., require testers for fault finding and alignment on radar equipment; applicants with experience in radio to television testing considered; good prospects in an expanding department for suitable appli-cants.-Personnel Officer, Decca Radar, Ltd.. 2, Tolworth Rise, Surbiton, Surrey. [4017]

2. JOINTHE RUSE, SUITDION, SUITEY. 14017 ENGINEER with sound basic knowledge of light electrical and A.F. engineering for sound recording equipment department; pen-sion scheme.-Apply, stating experience, qualifications, age and salary required, to the Personnel Manager, B.A.F., Ltd., Woodger Rd., London, W.12. [4010

alifications, age and salary required, to the free sconnel Manager, B.A.F., Lid., Woodger Fersonnel Manager, B.A.F., Lid., Woodger Rd., London, W.I.2.
 LECTRONIC Engineers.—If you are seeking a permanent position in a Company specialising in control equipment for the industrial field, your attention is drawn to the fact that Messrs. Lancashire Dynamo Electronic Products, Lid., have, as a result of further expansion, a number of vacancies for technical and administrative staff.
 THE vacancies are as follows:—
 A. Application Engineers with electrical engineering background and some knowledge of industrial electronic equipment, capable of discussing and interpreting the requirements of the customer and formulating complete schemes involving electronic equipment. Application for the substrate of the customer and formulating complete schemes involving electrical machines, contactor gear and electronic equipment. Application for the substrate of the customer and formulating complete schemes involving electronic equipment. Applications and conducting correspondence with the customer in relation to such producing complete instruction manuals from basic circuit details.
 C. Design Engineers with electronic and/or existing circuit techniques, and passing detailed circuit information to the Drawing Office, specifying component requirements. Supervising mechanical design and preparing test specifications. In terms of electronic equipment in consultation with Design Engineers.
 D. Draughtsmen capable of undertaving from design information the mechanical design and preparing test specifications.
 Deschemet Engineers for Laboratory to work on solution of specific industrial problems and in the development of new circuit techniques. Background on electronic circuit techniques. Background on electronic circuit techniques. Background on electronic circuit techniques. Background on schertiset. Applicatis should write, in the first instance, indi

of the reference letters. [4033 TEST gear design engineers and maintenance engineers required with practical experi-ence of this class of work, based on sound knowledge of electronic principles; these vacancies are permanent and progressive; a company pension scheme in operation: London area.—Please write, in confidence, giving full details of qualifications, to Box 0811 [4006

details of qualifications, to Box 0811 [4006 R ADIO testers equired, some v.h.f. experi-ence desirable together with some servicing knowledge on domestic or service equipment. --Applications, riving full details of previous experience and qualifications, should be sub-mitted in writing to The Personnel Manager. Pyer Telecommunications, Ltd., Newmarket Rd.. Cambridge. [306

A FULLY qualified Television Engineer re-Excellent wages plus generous weely bonus, pension fund, sick ply, etc.—Apply immediately in writing stating age, experience and qua'ifica-tions to the Personnel Manager, Co-operative Society, 110, Fratton Rd., Portsmouth. Endorse envelopes "Television Engineer." [3975

GALPIN'S ELECTRICAL STORES

408, HIGH STREET, LEWISHAM, S.E.13 Tel.: Lee Green 0309. Nr. Lewisham Hospital TERMS : CASH WITH ORDER. NO C.O.D. All goods sent on 7 days' approval against cash, EARLY CLOSING DAY THURSDAY.

HEAVY DUTY SPOT WELDER TRANS-FORMERS, input 200/250 volts. OUTPUT a combination of 2, 4, 6, 8, 10, 12 volts at 120/150 amps. New £6/15/- each, carriage 6/-. LIGHT ARC WELDING TRANSFORMERS, 200/250 volts input. output 40/60 volts, 30/40 amps, £7/5/- each.

amps, £7/5/- each. MEDIUM SPOT WELDING TRANS-FORMERS, input 200/250 volts, OUTPUT a combination of 2, 4, 6, 8, 10, 12 volts at 50/70 amps. New £5/2/6, C/paid. HEAVY DUTY L.T. OUTPUT TRANS-FORMERS, 200/250 volts input, output a combination of 6, 12, 18 and 24 volts at 30 amps. 647/16 each C/paid

£4!2/6 each. C/paid.

Another input as above, output 0, 6, 12, 18, 24 volts at 12 amps, 55/- each, post 2/-. Another input as above, output 0, 6, 12, 18, 24 volts, 6/8

volts at 12 amps, 55/- each, post 2/-. Another input as above, output 0, 6, 12, 18, 24 volts, 6/8 amps., 46/6 each. HEAVY DUTY L.T. TRANSFORMERS suitable for rectifiers, soil heating, etc. Input 200/250 volts. Output a combination of 6, 12, 18, 24 30, 36 volts at 15 amps., 67/6 each, post 2/6. Another input and output as above but at 6 amps. 47/6, post 2/-. Another input and output as above but at 4 amps. 36/6 ech. CONVERTORS, 400 watts output, 24 volts D.C. input 50 volts 50 cycles I phase output. Complete with step up transformer from 50 volts to 230 volts at 400 watts [12,10]- each C/F. Ditto 200 watts £9/10]-each C/F. july guaranteed. ROTARY CONVERTORS. 230 volts D.C. input 230 volts A.C. ouput. 50 cycles I phase at 250 watts. £15 each C.F. EX-RADAR MAINS TRANSFORMERS. In-put 230 volts. Output 4 or 5 Kilo volts at 30 min., also 3 L.T. windings 4, v.2 a, 6, 3. v. 2 a, 2 v. 2., these transformers are capable of a larger output than stated and are immersed in oil. £3/15/-each, carriage 5/-.

each carriage 5.

 Peach, carriage 3/-.
 MAINS TRANSFORMERS (NEW), input 200/250 volts in steps of 10 volts, output 350/0/350 volts; 180 m/amps. 4 volts 4 amps. 5 volts 3 amps. 6.3 volts 4 amps., 45/- each, post 1/6; another 350/0/350 volts 180 m/amps, 6.3 volts 8 amps., 0/4/5 volts 4 amps., 45/- each, post 1/6; another 500/0/500 volts 180 amps., 4 volts 4 amps., C.T., 5 volts 3 amps., 0/4/5 volts 4 amps., C.T., 5 volts 3 amps., 0/4/5 volts 4 amps., C.T., 5 volts 3 amps., 0/4/5 volts 4 amps., C.T., twice 5 volts 3 amps., 47/6 each, post 1/6; another 425/0/425 volts 160 m/amps., 6.3 volts 4 amps., C.T., twice 5 volts 3 amps., 0/4/5 each, post 1/6; another 200/240 volts 180 m/amps., 6.3 volts 4 amps., C.T., twice 5 volts 3 amps., 0/4/6 each, post 1/6.
 MAINS TRANSFORMERS, 200-250 volts input, output 400/0/400 volts, 280 m/amps., 6.3 volts 4 amps., C.T., twice 5 volts 0, 9, 18 volts at 4 amps., 25/- each, post 1/6.
 MAINS TRANSFORMERS, 200-250 volts input, output 400/0/400 volts, 280 m/amps., 6.3 volts 10, 0/230 volts input, output rapped 0, 9, 18 volts at 4 amps., 25/- each, post 1/6.
 EX-US.A. ROTARY CONVERTORS, 12 volts 0. MA. 275 v. 100 mA. Complete with smoothing 22/6 each, carriage 2/6. As new.
 EX-NAVAL ROTARY CONVERTORS, 110 v.D.C. input 230 volts A.C. 50 cy., 1 ph. 250 watts, output. Weight approx. 100 ib £12/10/-, C/F.
 ELCTRIC LIGHT CHECK METERS, useful for subleting, garages, etc., all for 200/250 volts A.C. mains, 53mp. load, 19/- each; 10 amps., 22/6; 20 amps., 27/-; 25 amps., 32/6.
 I,000 WATT AUTO WOUND VOLTAGE CHANGER TRANSFORMER tapped 0/110/200/230/250 volts. £5/15/- each, carriage 4/6.
 1,500 watt diro, £7/15/-, carriage 4/6.
 1,500 watt diro, £7/15/-, colts 30/- each; dicto 0 to 200 volts 35/- each; dicto 0 to 40 volts 27/6 each.
 CHAAGEING KITS CONSISTING OF REC-MAINS TRANSFORMERS (NEW), input 200/250 volts in steps of 10 volts, output 350/0/350

each

each. CHARGING KITS CONSISTING OF REC-TIFIER AND TRANSFORMER for charging 6 or 12 volt batteries at 2 amps, (input 200/250 volts) 32/6 each; ditto for 4 amps., 46/6 each. EX-R.A.F. DYNAMOTORS 24 28 volts D.C. input 1,200 volts, 17 milliamps $\frac{1}{2}$ hour rating, U/4 each 11/6 each

EX-RADAR IMPULSE TRANSFORMERS

EX-RADAR IMPULSE TRANSFORMERS 2 Mu-Metal transformer in oil, Output believed to be 15 k.v. at 3 kW. R.F., only 7/6 each. ROTARY CONVERTORS 24 volts D.C., Input 50 or 110 volts 500 cycles I phase, Output at 300 watts, £7/10,- each C/forward. D.C. MOTORS 230 volts 0.3 h.p., large 3,000 r.p.m. long shait, £3/5/- each.

Clients in Eire, please allow at least double the carriage stated to allow for Customs clearance charges.

WIRELESS WORLD

SITUATIONS VACANT RADIO and/or television engineer required for bench and outside repairs, driver; ref-erences, are, experience salary expected.— Field's Radio, Ltd., 52. Hall Gate, Doncaster, [3542

RADIO service mechanics required by Smi (Radiomobile). Ltd., for many parts of country.-Write details of experience and qu fications to Personnel Officer, Goodwood Won North Circular Rd., London, N.W.2. [0] [0342

PHYSICST.—Young graduate required for research and development work on transis-tors and their applications, excellent oppor-tunities and wide scope for man with initiative. —Applications, giving are, full details of quali-fications, experience and salary required, should be forwarded to Personnel Dept., Murphy Radio, Ltd., Welwyn Garden City. [3990

Ltd., Weiwyn Garden City. [3990 E LECTRONIC engineer required to supervise an ability to quickly diagnose faults, and a wide experience of modern test equipment are essential qualifications; this is a staff position offering good prospects to the right applicant. APPLY: The Wayne Kerr Engineering Co... Ltd., Tolworth Close, Surbiton, Surrey. [3992

TELEVISION service engineer required by leading dealer holding all main agencies; good position for first-class engineer with high standard of service; semi-detached modern house with garage available if required and good rate of salary.--Write, stating details of experience, etc. A. E. Huntes & Sons. 28, Clarence Place, Newport, Mon. [3681 TELEVISION

 $\begin{array}{c} \textbf{ELECTRONIC Engineer with practical experi-$ ence in industrial applications and goodtechnical knowledge is required by a large foodorganisation centred in London for the develop-ment. design and construction of electronicequipment. Applicants should have initiative andbe resourceful. Post will be of supervisorygrade and salary according to age and experi-ence.—Apply Box 0685. [3978]

ence.—Apply Box 0685. [3978 WANTED, deputy chief inspector to cover both mechanical and electrical inspection and test of electronic equipment, under A.I.D. conditions; successful applicant will be required to serve a probationary period as quality in-spector. 5-day week, excellent canteen facilitits. —Applications, stating salary required, to Per-ornely, Rhondda, S. Wales. [3985]

BRITISH ACOUSTIC FILMS, Ltd., Woodger Rd., W.12, have vacancies for laboratory engineers and scientists to work on sound recording and reproducing equipment and kindred projects for television, 35 and 16mm film, tape recorders, etc.; saisry according to experience and qualifications; pension scheme. -Application should be made, in writing, to the Personnel Manager. [4019]

E. K. COLE, Ltd., Malmesbury Division, require Draughtsmen for interesting work on radar and communications projects, mini-mum qualification O.N.C., knowledge of ministry design requirements to R.C.S. 1000 an advantage. Salary dependent upon ability. experience and qualification. Apply to Personnel Manager, Ekco Works, Malmesbury, Wiltshire. [4042]

RADIO and TV engineer with laboratory experience required by leading London firm of electrical component manufacturers for work in connection with printed circuits; H.N.C. standard: superannuation scheme.--Write, giving full details of education and experience, age and salary required, to Per-sonnel Manage., Box 3M.L2248, A.K. Advg., 212a, Shaftesbury Ave., London, W.C.2. 13649 13849

TEST department personnel required for ex-panding department engaged in the pro-duction department engaged in the pro-electronic and nucleonic equipment. his of interesting work with opportunities of raining experience of the latest developments in elec-tronic applications.—Write, stating age, ex-perience, and salary required to Personnel Manager, E. K. Cole, Ltd., Southend-on-Sea. [3967]

ELECTRONIC Engineers required: excellent opportunity for men of degree standard to broaden experience in a field of great interest and variety and involving latest techniques; restrictive specialization can be avoided by joining Marconi Instruments who produce light current communication, measuring, and test apparatus for a wide range of requirements.— Apply Marconi Instruments, Ltd., Longacres. Hatfield Rd., St. Albans. [3895]

MECHANICAL engineer read, for work on equipments; applicants should have served an engineering apprenticeship, or the equivalent, together with several years' experience in the field of design; small model shop facilities available to engineer; Greenford area; pension-able and salary commensurate with ability.-Apply giving age and fullest details of experi-ence to Boy: 0878.

RADIO technicians required by International Actadio, Ltd., for overseas service; perma-nent and pensionable positions, inclusive salary from £894 per annum to £1.375 per annum, tax free, according to marikal status; free accommodation; kt allowance; free air fares; genetous U.K. leave.—Qualified candidates to whom replies only wilb be sent please write quoting kT to Personnel Officer, 40, Park St., W.1.

FEBRUARY, 1955





AUTOMATIC (TIME) SWITCHES New and reconditioned 15 day clockwork and electric switches from 35/-Send S.A.E. for illustrated details to: DONOHOE (TIMERS) GEORGE STREET NORTH SHIELDS, NORTHUMBERLAND

Purchase or hire your VORTEXION TAPE RECORDER' & ASSOC. EQUIPMENT FROM GRIFFITHS HANSEN (Recordings) LTD. 32/33 GOSFIELD ST., LONDON, W.I. MUSeum 0642/2771. **FELECRAFT** TV AERIALS ARE CHEAPER AND BETTER Send for Lists

TELECRAFT LTD. Quadrant Works, Wortley Rd. West Groydon, Surrey. THOrnton Heath 1191-2-3

THE POLLOCK M.C. PICKUP Response 10 c.s. to 20 Kc/s. H.F. resonance 25 Kc/s., L.P. 20 Kc/s. Kit of parts to make pick-up complete, including 100 : 1 transformer and saphire stylus, 001 or .0025in., and full building instructions £4.88.6d. Parts sold sep-tative prices: head and setue. 20(6). head arately, prices: head and stylus 38/6; head for min. thorns 31/-; arm/pivot 26/-; trans-former 26/-; all prices post free. S.a.e. for details to:

BLUNDELL, 7 Sunnyside House, Child's Hill, London, N.W.2.

160

ON

Smith ...

NEW BOOKS RADIO & TELEVISION

48/-

4/9

72/-

43/6

5/3

18/6

\$/3

8/_

15/6 3/9

219

WORLD'S FINEST

KITS

TV

per a 7/029 W/E

HI-FI

CHEAPER IN

SMALL COILS

Modern Oschiosoppe by J. H. Ruiter Practical T.V. Aerial Manual for Bands I and 3, by R. Laidlaw. Radio and T.V. Engineers' Reference Modern Oscilloscopes and their Uses,

Book, by Molloy Radio Designers' Handbook, by Langford

Transistors and Crystal Diodes, by B. R.

Transistors and Bettridge Sound Reproduction, by G. A. Briggs... T.V. Fault Finding, by "Radio Con-structor "

structor " Loudspeakers, by G. A. Briggs The Oscilloscope at Work, by A. Haas and R. W. Hallows New Osram 912 Amplifier New Mullard 10 watt Amplifier

ALL POST FREE. Write for New List of

ENGLISH AND AMERICAN BOOKS AND PERIODICALS

UNIVERSAL BOOK CO.

12 LITTLE NEWPORT STREET,

LONDON, W.C.2. (Adjoining Lisle St.)

PHONOGRAPHS

Write for FREE Brochure

Radio Kits. Inc. . 120 CEDAR STREET

NEW YORK 6, NEW YORK . U.S.A.

No coil under 25 yds. unless requested. All prices 100-yd. lot. Less supplied, add 5%. 3/029 Twin Flat 1/044 3/029 W/E

ep ek a

TEST EQUIPMENT

RADIOS

CABLE

SOUTHERN RADIO'S

WIRELESS BARGAINS

TRANSRECEIVERS. Type "38" Mark II (Walkie-Talkie). With 5 valves and ready for use. Metal carrying case, 30/- per set. THROAT MICROPHONES, with long lead

JUNCTION BOX, 2/6. HEADPHONES JUNCTION BOX, 2/6. HEADPHONES IS/6 per pair, AERIALS, 2/6. ALL OF THESE ITEMS ARE FOR USE WITH THE "38 " Walkie-Talki

Taikie. TRANSRECEIVERS. Type "18" Mark III. Comprising Superhet Receiver and Transmitter. Two units contained in metal carrying case. Complete with 6 valves, £4/10/- per complete set. RECEIVERS. Type "109." Built-in speaker. 8 Valves with VIBRATOR PACK for 6 volts. Contained in metal case. Perfect, £5 each. TELESONIC 4-valve Battery Portable. Com-plete with Hivac valves in metal carrying case. Simply converted to Personal Portable, £2 per set including Conversion Sheet. BOMBSIGHT COMPUTERS. BRAND NEW ex-R.A.F. Contains gyro, motors, rev. counters,

BOMBSIGHT CONVERSION SNEET. BOMBSIGHT COMPUTERS. BRAND NEW ex-R.A.F. Contains gyro, motors, rev. counters, gear wheels, etc., etc. Ideal for model makers, experimenters, etc., £3/5/- each, plus 10/- carr. LUFBRA HOLE CUTTERS. Adjustable $\frac{3}{4}$ to $\frac{3}{4}$ in. For metal, wood, plastic, etc., 6/6. RESISTANCES. 100 Assorted, all useful values, etc. Wire end, 12/6 per 100. CONDENSERS. 100 Assorted. Mica, Metal, Tub, etc., 15/- per 100. CONDENSERS. 100 Assorted. Mica, Metal, Tub, etc., 15/- per 100. STAR IDENTIFIERS. Type I A-N. Covers both Hemispheres, in case, 5/6. CONTACTOR TIME SWITCHES. In sound-proof case, 2 impulses per second. Thermostatic control. Clockwork movement, 11/6 each. REMOTE CONTRACTORS for use with above, 7/6 each.

REMOTE CONTRACTORSTOTUSE MILLIAUS, 7/6 each. MORSE PRACTICE (WITH BUZZER) SET. Mounted, 6/9. Full List of Radio Books, 24d. METERS, 12 Instruments. May need adjustment or with broken cases, 35/- for 12. Postage and carriage extra. SOUTHERN RADIO SUPPLY LTD. II LITTLE NEWPORT STREET LONDON, W.C.2 Gerrard 6653

By Order of the Mortgagees IMPORTANT FREEHOLD PREMISES known as

GRAND THEATRE S.W.6. FULHAM

Situate in a prominent and accessible posi-tion, almost adjacent to Putney Bridge, and occupying a

VALUABLE ISLAND SITE

having an area of about 10,750 sq. ft. with Extensive Frontages to Three Roads, and comprising a

SUBSTANTIAL & IMPOSING BUILDING

with Stage; and S cony and Gallery. and Stalls, Dress Circle, Bal-

ACCOMMODATION SUFFICIENT FOR SEATING 830 PERSONS Suitable for re-use as a Theatre or for Public Entertainment as RECORDING, FILM OR TELEVISION STUDIO

or with Conversion and/or Development SHOWROOMS, OFFICES, WARE-HOUSE, ETC,

VACANT POSSESSION

(Subject to and with the benefit of agree-ments as to advertisement hoardings and newspaper stand.) To be offered for

newspaper stand.) To be offered for Sale by Auction at an early date (unless previously sold by Private Treaty) at The London Auction Mart, 155, Queen Victoria Street, E.C.4.

Particulars and Conditions of Sale of

HENRY BUTCHER & CO. Auctioners, Surveyors and Valuers, 73, Chancery Lane, London, W.C.2. HOLborn 8411

Solicitors: Messrs. HERBERT SMITH & CO., 62, London Wall, E.C.2. Tele: NATional 9771.

S ENIOR Electronic Engineers, Mechanical De-signers, Draughtsmen and Detail Draughts-men are required by a leading Midlands manu-facturing concern engaged on the design, development and production of domestic radio and televition and on Government contract work, an expanding programme will provide ex-cellent opportunities for promotion; applicants should write to-The Personnel Manager (Ref. GLB), Box 0742.

SENIOR and junior development engineers required for responsible work in radio and television development laboratorles, applicants for senior position should be able to under-take development work with minimum super-vision; excellent conditions and salary available for applicants who are accepted.—Apply in first case to Personnel Manager (Dept. R.D.), McMichael Radio, Ltd., Wexham Rd., Slough, Bucks. [3880

LAISON Engineer/Writer reqd. with sound basic knowledge of television and radar principles: he will be read, to work with design teams engaged on complex television and radar projects, to assimiliate the technical details and subsequently prepare technical notes in good and concise English.—Applicants should write, with full details, to the Per-sonnel Dept. (ED/182). Eng. Dev., Ltd., Hayes, Middx. [3968]

Middx. [3968 E LECTRONIC Wiremen required to assist in Television Transmission and similar equipment: applicants to possess fundamental knowledge of radio and television, to be capable of producing own component layouts and wiring to a high standard; pension scheme, canteen.-Write, stating ase, experience, and salary required, to Cinema-Television, Ltd., Worsley Bridge Rd., Lower Sydenham, S.E.26. [2028]

FIRST-CLASS Man is required for the inspection and test of industrial electronic apparatus. He should preferably have served an apprenticeship in the electrical industry, heing in possession of a Higher National Certificate and aged 25-35. Ogen to the right man. Write giving full details of age, experience and salary required to Philip's Baham Works, Ltd., 45, Nightngale Lane; Baham, S.W.12.

TEST engineers are required to assist in the production of a variety of precision elec-tronic laboratory instruments; previous test aepartment experience is essential (preferably in connection with electronic measuring in-struments); salaries in the range of £450-£575 p.a. according to qualifications and experience. —Apply, stating full details to the Personnel Manager, Furzehill Laboratories, Ltd... Bore-ham Wood, Herts. [3920]

MECHANIC required for duties in the Depart-ment of physics, good knowledge of elec-tronics essential, with experience in instrument making and repairing; duties will include main-tery and experimental apparatus; weekly rate of pay 59/5/2 (44 hours)—Written application should be addressed to the Head of the Depart-ment of Physics, Chelsea Polytechnic, Manresa Rd., S.W.3. [3995]

RADIO and TV engineer required by Mains Radio. Gramophones, Ltd., to take over position of chief of test; to be responsible for test standards and for technical lialson be-tween development and production; good pros-pects in expanding organization for right applicant; superannuated staff position.— Please send details of experience and salary expected to the Personnel Manager, 359, Man-chester Rd., Bradford.

JUNIOR apparatus techniclan required to assist Applicants should be working for City and Guilds certificates of the Ordinary National Certificate in electrical or radio engineering. Salary scale £150 (age 16) to £393 a year. Application forms, to be returned within 7 days, from Secretary. Institute of Psych'atry, Maudsley Hospital, Denmark Hill, London, S.E.S. (MRC)

E.M.I.-Domestic Electronics Division have a vacancy for a development engineer in their component laboratory, for work which in-cludes design of high fidelity equipment, loud speakers and pick-ups; applicants should have a good academic training and preferably experi-ence in the design of electro-mechanical com-ponents.-Please write with full details to Per-sonnel Dept. (DED/3), E.M.I. Factories, Ltd., Blyth Rd., Hayes, Middx.

Biyth Rd., Hayes, Midux. 14400 **E**LECTRICAI foreman with wide production medium electrical control gear manufacture. test and installation required by manufactures of materials handling vehicles in pleasant country Jistrict. 1 hour London; good pros-pects of advancement; housing assistance; can-teen and social facilities.—Please write, giving details of age, past experience, present salary, salary required, married/single, to Box 0803 [4004]



ELECTRO MAGNETIC COUNTERS. Post Office type 11A, counting up to 9,999, 2 to 6 volts D.C., 3 ohm coil 12/6 each, post 1/-. Many other types in stock, lists scut with order or scud S.A.E.

HEADPHONES. HIGH RESISTANCE 4,000 Q. Type CHE. New. 12/6 pair. Post 1/6.

CONDENSERS. PAPER BLOCK TYPE

.5mfd.,1,000 volt.. 2/6 8mfd., 500 volt .. 7/6 4mfd. 350 volt... 4/6 8mfd., 750 volt .. 10/6 4mfd.,2,000 volt.. 7/6 10mfd., 350 volt .. 10/8 R.F. UNITS TYPE 26. 50/65 Mc/s. V. complete with valves. 35/-. Post 2/6. Variable tuning,

complete with valves. 3b/r. rost 2/c. AMPLIFIERS, A high-fieldity unit with separate base-and treble controls, constant impedance attenuator for setting volume level. In metal case with handles. 15 watt output, for 200/220 v. A.C. mains operation, Intended for use with the Gaumont British Projector. Ideal for P.A. work, dances, etc. Less valves. £12/10/-. Or complete with all valves, £15/12/6. Carr. 10/-.

Cart. 307-BOTARY CONVERTERS. Input 12 volts D.C., output 230 volts A.C. 50 cycles, 100 wat, 92/6 cach. Also available with 24 volt input, cart. 7/6. LISTS AYAILABLE. Motors, Meters, Telephones, Rectilders, Relays, Potentiometers, Resistances. All types including High Stability Carbon and Wire-wound. Bend S.A.E.



161

WIRELESS WORLD

SITUATIONS VACANT TELEVISION engineers required by old-estab-lished common ho'ding every one of the experienced and preferably able to drive; top rates and primanent progressive positions to the right men -App'y to A. S. White & Sons. Ltd. 130/2. High Rd., S. Tottenham, London. N 15 Sta. 7861-2. [3178

SENIOR collwinding planning engineer re-quired, expirienced in the planning of radio and television colls; the selected candidate will have the drive and initiative necessary to deal rapidly with the day-to-day electrical and mechanical problems on the shop floor, East London area; this vacancy, for which a good salary will be paid, presents ample scope and opportunity to a man of first-class ability.-Please reply, giving full details of experience, to Box U/39. [3987

A VACANCY occurs for a Works Costing En-gineer for radio and television produc-tion, applicants should have had a good educa-tion, preferably with a degree, and should be members of the nstitute of Cost and Works Accounting: experience of Budgetry Control. Standard Costing and Estimating is essential; the situation is oermanent and offers good prospects to suitable applicant.-Apply in writing to Personel Department, Murphy Radio, Ltd., Weiwyn Garden City. 1403

Radio, Ltd., We wyn Garden City. MARCONI Instruments, Ltd., have an imme-diate vacancy at St. Albans in their Technical Literature (Telecommunications) Section; the applicants should have electrical engineering qualifications and/or experience in the design or development of electronic equip-ment; the duties are varied and interesting and the post provides a permanent and pensionable postition in a well-established company.—Apply Marconi Instruments, Ltd., Longacres, Hatfield Ed., St. Albans. [3894]

DECCA RADAR, Ltd., require technicians and eng.neers for radar installation at home and aoroad: previous industical and/or service ex-perience essential; ex-technical officers and semor N.C.O.s from H.M. Forces are particu-larly invited to apply.—Applications should be made in writing in the first instance giving full details of qualifications, past experience, and salary required to the Manager, Heavy Installa-tions Division, Decca Radar, Ltd., Malden Way, New Malden, Surrey [3896]

SENIOR and Junior Design Draughtsmen re-quired for interesting work in connection with electronic equipment, commercial radio and television and/or light electro-mechanical engineering; London area; the positions vacant offer ample scope and opportunity for future advancement to men of good ability; a high salary will be paid to the selected candidates; all recognised staff privileges available. –Please reply, giving full details of experience, to Box 0843.

14015 **ELECTRONICS** installation and service engineers required for work in field and laboratory; interesting and responsible posts in new expanding department; duties embrace V.H.F. electronic and nucleonic activities in commercial sphere; applicants must have prac-tical technical knowledge and servicing experi-ence, preferably with electronic instruments.--Write, stating age, qualifications and experi-ence, to Personnel Manager, E. K. Cole, Ltd., Southend-on-Sea. [4011

R ADIO Repairing Instructor (unestabilished) R creduired at Slouch Government Training Centre. Applicants must be skilled craftsmen who have completed articles of apprenticeship or a period of training acceptable to the appro-priate craft union and have not less than five years' recent practical experience at their trade. Comencing salary £550 per annum plus pay supplement of £55. on a scale of £550×£25 to £640, plus pay supplement. Lower rate if under 28.—Apply to any Employment Exchange. ISBME

[3981] THE GENERAL ELECTRIC Co., Ltd., Brown's antoal development engineers, designer draughtsmen and draughtsmen, preferably with experience of radar-type equipments for work on guided weapons and like projects; also re-quired, senior and junior electronic develop-ment enginers, particularly in the field of microwave and pulse applications; salary ac-cording to sse, qualifications and experience. - App.y by letter, stating age and experience, to the Personnel Manager, Ref. R.G. [0259]

Apply by letter, stating age and experience, to the Personnel Manager, Ret. R.G. [0259 Development Manager, Ret. R.G. [0259 Development of the state of the state of the state radio receiver circuitry by a progressive com-pany with laboratories situated in Central Candidates with H.N.C. or equivalent will get preference, and experience of magnetic tape recorders will be welcomed; attractive salaries are offered in accordance with experience and qualificaticns.-Reply in confidence to Chief Engineer, Hartley Baird, Ltd., 37-39, Thurloe St., S.W.7. Tel. Knightsbridge 2511. [4047 The GENERAL POST OFFICE has vacancies for radio operators at its coast radio stations and applications are invited from men between 21 and 35 years of age who hold the Postmaster-General's Inst-class certificate of profilency in radiotelegraphy. Selected candi-date will be considered later for permanent pest. S.W.I be considered later for permanent post and application should be made and Accommodation Depertment, Wireless Telegraph Section. Union House, St. Martins le Grand, London, E.C.1. [3608]

Electronic computing techniques are now being successfully applied to many accounting and statistical problems. There are excellent prospects with the expanding Production Development and Research Departments of the British Tabulating Machine Co. Ltd., Letchworth, Herts., for University Graduates and men of H.N.C. standard or higher with an interest in electronics and their application to computing machines. The Company will be pleased to hear from men seeking an opening in this Assistance with housing field. may be given to suitable applicants. Pension and Sick Pay Schemes are in operation. Enquiries should be addressed to Personnel Officer in the first instance.

THE ' Dust Bug" AUTOMATIC GRAMOPHONE RECORD CLEANER PATENT APPLIED FOR om CECIL E. WATTS nsultant and Engineer (Sound Recording and Reproduction)

From Oakleigh Grange, High Cross, nr. Uckfield, Sussex. Or your local dealer.

Price 18/6, plus 6/2 purchase tax

Introducing-THE "ELBAR" TAPE RECORDER Two speed, twin track, portable, for faithful reproduction of speech and music. 45 guineas complete with microphone. Write for illustrated leaflet. JACKSON RADIO 163 Edgware Road, London, W.2 PAD 0537

CABINETS

We specialise in making HIGH CLASS cabinets to Individual specification, particu-larly in high fidelity field. Competitive Prices,

ALAN CRANSTON (Cabinet Makers). 20, Lorrimore Bldgs., Olney Road, Walworth, Phone : RODney 2349. LONDON, S.E.17.

RADIO & TELEVISION COMPONENTS WE OPERATE A PROMPT & EFFICIENT MAIL ORDER SERVICE "VIEW MASTER" & "TELE-KING" specialists Easy terms available. Stamp (only) for lists JAMES H. MARTIN & CO., FINSTHWAITE, NEWBY BRIDGE, ULVERSTON, LANCS.

UNIVERSAL METER SHUNTS for I mA x 100 Ohm and 500 µA 500 Ohm No calibration or adjustment needed, SSIA (I mA) covers 2, 10, 50, 200 and 1,000 mA. SSO2A (<u>1</u> mA) covers 1, 5, 25, 100 and 500 mA. Price 15/- each Trade enquiries invited R. MASSEY, 58, WAKEFIELD AVE., HULL

COMPLETE WITH CIRCUIT TERMS : C.W.O. POST ORDERS ONLY THE WATSON WATCH Co. 29 Leigh Rd., London, N.5

RECORD CABINETS £5/10/- to £17. Write for

GRAMOPHONE

details. Easy Payments A. L. Stamford (Dept. H.22) 20, College Parade, Salusbury Rd., London, N.W.6.



RADIO

MECHANICS

wanted for testing

communications receivers

and transmitters.

Apply with full particulars

to -

PYE MARINE LTD.

OULTON WORKS,

LOWESTOFT - SUFFOLK

WEBB'S SERVICE

DEPARTMENT

for complete renovation of complex

communications receivers of any make

Test report issued showing sensitivity, selectivity, signal/noise equal to, or better than, makers'

WEBB'S RADIO,

14, SOHO STREET, LONDON, W.1

R.F. OSC. E.H.T. COILS

TYPE 'D' 6-9 K.V. 25/-

TYPE 'F' 9-14 K.V. 30/-

original figures.

MANCHESTER.

FERRANTI ELECTRONIC **COMPUTERS**

Ferranti Ltd. invite applications for vacancies in their ELECTRONIC

COMPUTER DEPARTMENT. The vacancies described below are in their LONDON COMPUTER AND

INFORMATION-HANDLING LABORATORY but vacancies of types (i) and(iii) exist also in the COMPUTER LABORATORIES in

(i) Electrical Engineers and Physi-

cists for Computer Design Groups

concerned with the design of analogue and digital computing circuits, visual displays, conver-sion equipment, storage systems,

etc., and for basic research on interesting new techniques. Reference WSE(i).

Designers on principles and details of construction. Keen interest in advanced methods of construction

is essential and experience of printed circuits or dip soldering and related techniques would be an

(iii) Electrical or Mechanical En-gineer for Engineering Design Group. For work on the design of precision instruments and com-

(iv) Electrical Engineer, Physicist or Mathematician for compiling

Technical Manuals primarily in-tended for use by maintenance personnel and covering both the logic and detailed electronics of

machines designed by the Labora-

tory. This work is an excellent introduction to digital systems in

general. The successful applicant may be required to assist in the

training of maintenance personnel. Reference WSE(iv).

other digital systems. Some background in electronics would be an

advantage, but is not essential. Reference WSE(v).

There are also vacancies for Project

Leaders to take responsibility for pro-jects through all stages. The positions

offer scope for the exercise of initiative and for advancement in an ex-panding organisation. The Company operates a Staff Pension Scheme.

Application forms from Mr. T. J. Lunt, Staff Manager, Ferranti Ltd.,

Please quote appropriate reference and indicate whether MANCHESTER or

Hollinwood, Lancs.

LONDON post is desired.

(v) Mathematicians for work on the logical design of computers and

some branch of instrument techonlogy is essential. Knowledge of optics and high-speed photo-graphy is an advantage. Reference WSE(iii).

WSE(ii).

Design experience in

asset. Reference

ponents.

(ii) Electrical or Mechanical Engineer for the Engineering Design Group. To work in close touch with Electronic Circuit

WIRELESS WORLD

SITUATIONS VACANT

SITUATIONS VACANT LEADING manufacturers of electronic equip-ment in the Provinces require a foreman for 'arge coll-winding sockon: appleants should be fully experienced on Wes inster and other automatic interleaving machines; good salary and prospects to suitable main: write stating age and experience, to—The Personne; Manatri, Box 0382

DEVELOPMENT DEVELOPMENT engineers, qualified men with experience, interested in the design and development of domestic radio and tele-vision equipment, are offered interesting and progressive work in this field, situated in Mid-lands; applicants should write stating qualifica-tions and experience, to—The Personnel Man-ager (Ref. GLB), Box 0861. [4029

ager (Ref. GLB), Box 0861. [4029 ELECTRICAL/Electronic Engineer.--Vickers-Armstrongs, Ltd., Supermaine Works, re-quire for employment at their experimental alffield, graduate with research and develop-mechanical devices and/or recording equipment. for interesting work on ground and alroome measuring apparatus; the right man for thi pot will be keen to suggert and assess new techniques and to design and engineer sultable and workmanike equipment; permanent pen-sionable pot with good prospects for suitable engineer.-Apply, Personnel Department, Hurs-ley Park, Nr. Winchester. [4000]

ley Park, Nr. Winchester. [4000] JUNIOR development engineers are urgently required to assist in the development of pre-cision electronic a oratory instruments; suc-cessul applicants will be engaged on inferesting-ment of a wide range of equipment; the appointments are permanent and carry con-siderable technical responsibility; applicants hould have had previous development exceri-ence preferably in the instrument field; academic qua ifications ranging from H.N.C. to degree standard are preferable; salaries are encedent upon age, qualifications and ex-verience.—Apply, stating full details to the personnel Manager, Furzehill Laboratories Ltd., Boreham Wood, Herts. [3921]

Dereinene. Manager, Furzehill Laboratories
 Etd., Boreham Wood, Herts.
 I and MiniSTRY requires Scientific Officer
 A IR MINISTRY requires Scientific Advances
 A IR MINISTRY requires Scientific Advances
 A IR MINISTRY requires Scientific Advances
 A IR MINISTRY requires and general
 electronics.
 A Qualifications: First or Second
 Class Honours degree in physics or electrical
 engineering, or equivalent. Salary: Within range 4467/10-2455. Post unestabilished with possibilities of establishment through Civil Service Commission whilst remaning under age 31 Opportunities for promotion to higher grade posts on staff of Scientific Adviser to Air Ministry.-Application forms, quoting A109/54A, from MLN.S. Technical and Scientific Adviser to Air Ministry. Application Laboratories for qualified engineers to design and develop the following: (1) V.H.F. and U.H.F. communications equipment; (2) alroorne and ground radar equipment; (3) computing devices and second seconsystems; (4) nucleonic equipment and measuring instruments; (5) transistors and associated circuitry; the salary range lis 2600-21,000 per annum depending upon experience; further posts are evailable to engineers of H.N.C. standardy range being 245 by 56 do per active three or and salary required, should be forwarded to Personnel Department, Murphy Radio, Edd., Weiwm Garden City.
 ELECTRONIC Engineer required at Ministry

Welwyn Garden City. [399] ELECTRONIC Engineer required at Ministry of Supply, Headquarters, London, to work in branch of Guided Weapons Directorate, responsible for planning and progressing con-tracts with various weapons firms. The officer there requires the four second second second tracts with various weapons firms. The officer tracts with various weapons firms and some experience in guided weapons field would be an asset. Salary within Experiment of £30 p.a. —Application orms from Ministry of Labour and National Service, Technical and Scientific Register (K). 26. King St., London, S.W.I. [4025] CLECTRONIC engineers with several years'

ducting D.SOJ34A. Closing date February [11] 1855. [2021] ELECTRONIC engineers with several years' research or development experience are in-vited to apply for posts with a well established company engaged primarily on the develop-ment of precision electronic laboratory instru-ments; applicants should preferably possess a degree or equivalent qualifications in physics or light electrical engineering, although this is not essential as considerable practical experi-ence is equally acceptable; the appointments are of a permanent nature for engineers able to undertake the responsibility for the de-velopment of new projects to the prototype stage, and they offer scope for the exercise of individual inflative; furthermore, the work overs a wide range of electronic instruments and similar devices; salaries are commensu-rate with qualifications and experience. Appli-cations should be made in writing, stating ful details to Bersonnet Manazer, Purzehil Labo-ratories Ltd. Boreham Word Herts [3922]




Complete S.A.E. FOR LEAFLET

BOMB SIGHT



makers paraduse. Each over 561b of magnificently Each nover 561b of magnificently bearings, miniature motor repeater motor, gyroscopes, etc. Ail supplied in a strong wooden transit case 24m, x 22m, x 11m. high which itself is ideal as a tool box.

AIR POSITION INDICATOR

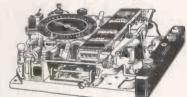

Containing a wealth of gears, drives and shafts, 3 infinitely variable gears, lampholders, repeater motors. Veeder counters. Been used by many Universities as a £2.7.6 tasks of a calculating machine.



SUPPLY COMPANY

164

<text><text><text><text>

TECHNICAL TRAINING TECHNICAL TRAINING IF you possess knowledge of radio and wish to train in television, obtain full details of a home study course using the latest training methods by writing to Box 0955. [4055 LEARN it as you do It-we provide practical equipment combined with instruction in radio, television, electricity, mechanics, chemis-try, photography, etc.-Write for full details to E.M.I. Institutes, Dept. WW.47, London, W.4. [000] [0001

CITY and Guilds (Electrical, etc.) on "No Pass-No Fee" terms over 95% successes. -For full details of modern courses in all branches of Electrical Technology send for our 144-page handbook, free and post free. B.I.F.T. (Dept. 388A), 29. Wright's Lane. London, W.8.

TUITION NOTHING succeeds like success! What we have done a thousand times we can do again for you—see the B.N.R.S. advt. page 148. [0172

WIRELESS operating; attendance and postal courses.—Stamp for reply to Manager, The Wireless School, Manor Gdns., London, N.7. 10104

T/V & Radio-A.M.Brit.I.R.E., City & Guilds, R.T.E.B. Cert. etc., on "No Pass -No Fee" terms; over 95% successes.-De-tails of Exams. and Home Training Courses in all branches of Radio and T/V. write for 144-page Handbook-Free, B.I.E.T. (Dept. 387A), 29. Wright's Lane, London, W.8. [Ol16

BRASS, COPPER, DURAL, ALUMINIUM, BRONZE ROD, BAR. SHEET, TUBE, STRIP, WIRE 3,000 STANDARD STOCK SIZES No Quantity too Small List on application H. ROLLET & Co., Ltd. 6 Chesham Place, S.W.1. SLOanc 3463 ALSO AT LIVERFOL, BIRMINGHAM. MANCHESTER, LEEDS

TUITION

FULL-TIME courses for P.M.G. Certs., F.C.G.L.I. Telecommunications. Radar Main-tenance Cert. and B.Sc. (Bm.): prospectus free. -Technical College, Hull. (11) A.M.I.Mech.E., A.M.Brit.R.E., City and Guilds. etc., on "No Pass-No Fee" terms; over 95% successes.-For details of Exams. and courses in all branches of Engineering, Building, etc., write for 144-page Handbook-Free: B.I.E.T. (Dept. 387B), 29, Wright's Lane, London, W.8. [0118]

PYE LIMITED CAMBRIDGE

Vacancies exist in the Engineering and Research Laboratories of the above progressive organisation for Senior and Junior Engineers and Drawing Office personnel to work in each of the following fields:-

- (1) T/V transmitters, aerials and ancillary equipment. (2) T/V studio and waveform equip-
- ment.
- (3) Radio and T/V broadcast receivers.
 (4) Microwave equipment.
 (5) Applications of transistors and other semi-conductor devices.
- Transformer design. (7) Precision electro-mechanical
- devices. (8) Electrical servo-mechanisms and
- control systems.

There are also vacancies for men qualified as radio mechanics for installation and maintenance work.

Salaries will be on a generous scale and in accordance with qualifications and experience. Basic 40-hour week, paid overtime, profit-sharing scheme, pension scheme, canteen, sports club, benevolent fund.

Please write indicating which of the Please write indicating which of the above fields interests you and giving brief details of your attainments to date, to the Chief Engineer, PYE LIMITED, CAMBRIDGE. Correspondence will be treated in strict confidence.

TESTERS

required for high grade RADAR and ELECTRONIC WORK. Ordinary or Higher National Certificate an advantage, but men with suitable Service or Civilian experience will be considered. Opportunities of advancement available for progressive candidates. Good rates of pay, canteen facilities, etc., etc. Apply to the Employment Department, Metropolitan-Vickers Electrical Co., Ltd., Trafford Park, Manchester 17.

MALVYN ENGINEERING WORKS

Precision Engineers Manufacturers of : Chassis, Small Pressings, Machined Components, Wiring and Mechanical Assemblies, to specification.

Single and Production Quantities. Enquiries Invited 100 PARK ROAD, WARE, HERTS. -Telephone : Ware 465 -

TUITION

SEE the world as a Radio Officer. Short training period-low fees. Scholarships, etc., available. Boarding and day students. Send 2d stamp for prospectus.-Wireless Col-lege, Colwyn Bay.

Send 2d stamp for prospectus.--wireless Coll-lege, Colwyn Bay. [0018] RACTICAL evening courses in radio and television engineering; commencing end of January; write for details.--Manchester Radio & Television School, 32, Young St., Manches-ter, 3. Bla. 8967. [3974] THE Institute of Practical Radio Engineers have available home study courses in every phase of tadio and television engineering, specialising in the practical radiing of appren-tices in the retail trade; enrolments limited, fees moderate.--The Sylabus of Instructional Text may be obtained post free from the Secretary, I.P.R.E., Fairfield House, 20, Fairfield Rd, Crouch End, London, N.8. [O089]

1.P.R.E., Fairfield House, 20, Fairfield Rd., Crouch End, London, N.S. [0098 OPPORTUNITIES in radio and television servicing; full-time theoretical and prac-tical 1-year course at E.M.I. Institutes in Lon-don; job assured on successful completion; nerolment is advised.-Free brochures giving details of these and other courses from E.M.I. Institute, Dept. WW36, 10, Pembridge Sg. London, W.2. Tel. Bayswater 5131/2. [3972] **FREE**I-Brochure giving details of Home Study Training in Radio, Television, and all branches of electronics; courses for the A.M.Brit.I.R.E., City and Guilds, R.T.E.B., and other professional examinations; train with the College operated by Britain's largest elec-tronics organisation; moderate fees.-Write to E.M.I. Institutes, Dept. WW.28, London, W.4.

WiRELESS telegraphy.—Merchant Navy offers to youths 16 upwards after oual-fication, lucrative positions as radio officers.— Apply British School of Telegraphy 179 Clan-ham Rd. S.W.9 (Est. 1906). Recognised by Ministry of Education, moderate fees, moder equipment, day and evening tuition: also tostal courses in theory of wireless telegraphy for P.M.G. Certs. and Amateur Transmitting Licence. [0124]

TRADE MARKS

TRADE MARKS TRADE Mark No. 706195 consisting of the very solarization of the second second second second respect of Electronic and electrical apparatus and instruments; scientific, nautical, survey-ing, radio, television, photographic, chemato-ing, objecal, weighing, measuring, signal-ling, objecal, weighing, measuring, signal-ing, accounting, adding and calculating apparatus and instruments; apparatus and in-struments; for recording and indicating pressure, temperature and speed; sund recording trans-mitting and reproducing apparatus and instru-ments; and parts, was assigned on 14th Sep-tember. 1954, by Solartron Laboratory Instru-ments Limited of Solartron Works. Queens Road, Thames Ditton. Surrey, to The Solartron Electronic Group Limited of the same address without the go dwill of the business in which it was then in use. 1400

BOOKS INSTRUCTIONS, ETC.

BOOKS, technical, 1953, half price, un-marked; write list.—Box 0856. [4018] WIRELESS World, Nov. 1937 to Dec. 1953; offers.—Loveland, 34, Crockford Park Rd., Addlestone, Surrey. [4050]

Addlestone, Surrey. [4050 P.R.E. technical publications, 5,500 Align-Iment Peaks for Superheterodynes, 5/9, post free, data for constructing TV aerial strength meter, 7/6; sample copy "The Practical Radio Engineer, "quaterly publication of the Institute 2/-; membership and examination data, 1/-Sec., I.P.R.E., 20, Fairfield Rd., London, N.8. [0089]

CASH From Your Camera." By Arthur [0089] Westleton, F.R.G.S. Shows how amateur photography can be made to pay for itself by the sale of pictures to newspapers, magazines, calendar publishers, etc., and deals with the many problems involved. 2nd dedition. 7/6 net from all booksellers. 7/10 by post from Illiffe & Sons Ltd., Dorset House, Stamford St., London, S.E.1.

S.E.I. "RALLIES and Trials." By S. C. H. Davis of "The Autocar." Describes in a colourful style the author's many adventures whilst driving in rallies and trials in all the so Britain and Europe. The Monte Carlo have the exciting Alpine Trials and many other apply. the exciting Alpine Trials and many other apply. the vents are recalled by this world-re-nowned racing driver. 15/- net from all booksellers. 15/7 by post from Tifle & Sons Ltd., Dorset House, Stamford St., London, S.E.I.

MORLEY TRANSFORMERS-

MORLEY TRANSFORMERS QUALITY P.P.O./P. TRANS, 20w., super Sileorians Section low leakage windings, prim. ind. 75H. leakage ind. 075H. Sec. 3 and 15 ohms Prim. to indiv. requirements. Shrouded and term., wt. 5 lbs. 3 ms. Ditto 15 w., 21 gns. L.F. CHOKES, 10H. 65 mA. 4(6.15H.100 mA.10/6, 20H. 160 mA.12/6. CRT Htr. Isolation Trans., 25% sec. boost rolt, 2 v., 10/6; 6.3 v., 10/6. MAINS TRANS. 0-200/250 v. tapped prim. 350-0-350 v. 80 mA. 5 v. 2 a., 63. v. tapped prim. 350-0-350 v. 80 mA. 5 v. 2 a., 63. v. 4 a., etc., from 21/- 6.3 v. 1 ja. Att. Trans., 7/6. Quotations for specials and rewinds. Part P. & P. 1/-2. PAWSONSED W. CROYDON THO 1665 2, PAWSONS RD., W. CROYDON, THO 1665



In Every Ship of the Royal Navy

FERRANTI LIMITED, EDINBURGH -FLIGHT TRIALS DIVISION-

APPLICATIONS ARE INVITED FOR

ELECTRONIC ENGINEER for interesting work in their Flight Trials division. The engineer will be engaged on trials to evaluate the technical and operational performance of fire control and navigational systems, air and ground. The qualifications required are to degree or equivalent standard with a minimum of three years' experience. Ref. No. 59/EE/TID.

are to degree of equilibrium sectors of the sector of the our new laboratories. Apply for an application form, quoting appropriate reference

number to the

PERSONNEL OFFICER, Ferranti Limited, Ferry Road, Edinburgh, 5.

ENGINEERS AND PHYSICISTS

Ferranti Limited in their new Laboratories are engaged in a pro-gramme of electronic development of great industrial importance. The work involves the use of digital computers to control machines and industrial processes, and covers a wide and expanding field of application, offering long-term interest to those engaged in it. Development activity for these projects is taking place in the fields of electronic circuitry (including pulse technique), digital computers, magnetic recording and servomechanisms. Engineers and Physicists having experience as well as interest in one or more of these subjects are invited to apply. The appointments are permanent and offer full scope for initiative in an expanding organisation. A salary commensurate with the qualifications required will be paid. Staff Pension Scheme, Applica-tion form will be sent on request (quoting Ref. 59/EP/AL) to the

NAME

ADDRESS.....

PERSONNEL OFFICER. Ferranti Limited, Ferry Road, Edinburgh, 5.

CLASSIFIED ADVERTISEMENTS

Use this Form for your Sales and Wants

To "Wireless World" Classified Advertisement Dept., Dorset House, Stamford Street, London, S.E.I

PLEASE INSERT THE ADVERTISEMENT INDICATED ON FORM BELOW

- RATE: 7/- for TWO LINES. 3/6 every Additional Line. Average six words per line.
- Name and address to be included in charge If used in advertisement.
- Box No. Allow two words, plus 1/~
- Cheques, etc., payable to lliffe & Sons Ltd.; and crossed "& Co."
- Press Day, January 27th for March issue.

REMITTANCE VALUE ENCLOSED

Please write in block letters with ball pen or pencil.

NUMBER OF INSERTIONS.....





Fluorescent 80w 5-ft Industrial Trough reflector fitting, white stove enamelled. Complete in every detail, ready to hang with tube for 210/240v a.c. mains. Cash £3-15-0.

Despatched free, by return anywhere Gt. Britain **NEW — GUARANTEED**

KINGSTON ELECTRICAL SUPPLIES, 134 London Rd., Kingston-on-Thames

INDEX TO ABVERTISERS

Acoustical Mig. Co., Lid. 153 Acoustical Mig. Co., Lid. 154 Acoust	PAGE	PAG	
Advince Los 10	Acru Electric Tool Mfg. Co., Ltd., The 74	Gardners Radio, td. 11 Gee Bros. Radio, Ltd. 13	Quartz Crystal Co., Ltd
Anders Belchend, Lud. 11 Anders Belchend, Lud. 11 Anders Belchen, Lud. 12 Anders Belchen, Lud. 13 Anders Belchen, Lud. 13 Anders Belchen, Lud. 14 Anders Belchen, Lud. 14 Anders Belchen, Lud. 14 Arrowstinen, Machine, Bartan, Lud. 14 Anders Belchen, Lud. 14 Arrowstinen, Machine, Bartan,		Glaser, L., & Co. 15 Glover, W. T., & Co., Ltd. 5 Joodmans Industries, Ltd. 5	Radio Component Specialists
Anders Belchend, Lud. 11 Anders Belchend, Lud. 11 Anders Belchen, Lud. 12 Anders Belchen, Lud. 13 Anders Belchen, Lud. 13 Anders Belchen, Lud. 14 Anders Belchen, Lud. 14 Anders Belchen, Lud. 14 Arrowstinen, Machine, Bartan, Lud. 14 Anders Belchen, Lud. 14 Arrowstinen, Machine, Bartan,	Alpha Radio Supply Co., The	Gramophone Co., Ltd., The	7 Radio Kits, Inc 160
Addies menes, Lui, 100 Add. Bischer, Lui, 53 Arzei, Bound 100 Add. Bischer, Lui, 53 Arzei, Bound 100 Add. Bischer, Lui, 56 Arzei, Bound 100 Rezen Inductions, Lui, 56 Arzei, Bound Sonda 100 Rezen Inductions, Lui, 56 Arzei, Bound Sonda 100 Rezen Inductions, Lui, 56 Antworth, B., Schwartz, M., & Co., Lui, 100 Rezen Induction, Lui, 166 Antworth, B., Schwartz, B., Lui, 100 Rezen Induction, Lui, 166 Antworth, B., K., & Co., Lui, 100 Rezen Induction, Lui, 166 Antworth, B., K., & Co., Lui, 100 Rezen Induction, Lui, 166 Barker, Natural Reproducters 151 Rezen Induction, Lui, 158 Beillong, G., Wawey, Luid, 160 168 Smith, G. V., Realo, Luid, 158 Beillong, G., Wawey, Luid, 168 Smith, G. V., Realo, Luid, 158 Beillong, G., Wawey, Luid, 168 Smith, G. V., Realo, Luid, 158	Amplex Appliances (Kent). Ltd. 118 Anders Electronics. Ltd. 66	Griffiths Hansen (Recordings), Ltd 16 Grundig (Gt. Britain), Ltd 16	Radiospares, Ltd 152
Athverth, B., Statistics, Lid. 163 Automatic Cull Winder & Electrical Issuer 110 Lid. 60 Automatic Cull Winder & Electrical Issuer 110 Lid. 60 Automatic Cull Winder & Electrical Issuer 110 Lid. 160 Automatic Cull Winder & Electrical Issuermas, Lud. 160 Sallord Electrical Instruments, Lud. 54 Barker Maural Reproduces 110 Lid. 160 Sallord Electrical Instruments, Lud. 56 Barker Maural, Reproduces 110 Hinds Electronic Devices, Lud. 160 Sallord Electrical Instruments, Lud. 56 Barker Maural, Reproduces 110 Hinds Electronic Devices, Lud. 160 Sallord Electrical Instruments, Col. 56 Barker Maural, Reproduces 110 Instruments, Electronic Devices, Lud. 160 56 Barker Maural, Reproduces 160 Sallord Electronic Devices, Lud. 56 Sallord Electronic Devices, Lud. 56 Barker Maural, Reproduces 160 Sallord Electronic Devices, Lud. 55 Sallord Electronic Devices, Lud. 56 Barker Maural, Reproduces	Antex		Radio Traders, Ltd
Athverth, B., Statistics, Lid. 163 Automatic Cull Winder & Electrical Issuer 110 Lid. 60 Automatic Cull Winder & Electrical Issuer 110 Lid. 60 Automatic Cull Winder & Electrical Issuer 110 Lid. 160 Automatic Cull Winder & Electrical Issuermas, Lud. 160 Sallord Electrical Instruments, Lud. 54 Barker Maural Reproduces 110 Lid. 160 Sallord Electrical Instruments, Lud. 56 Barker Maural, Reproduces 110 Hinds Electronic Devices, Lud. 160 Sallord Electrical Instruments, Lud. 56 Barker Maural, Reproduces 110 Hinds Electronic Devices, Lud. 160 Sallord Electrical Instruments, Col. 56 Barker Maural, Reproduces 110 Instruments, Electronic Devices, Lud. 160 56 Barker Maural, Reproduces 160 Sallord Electronic Devices, Lud. 56 Sallord Electronic Devices, Lud. 56 Barker Maural, Reproduces 160 Sallord Electronic Devices, Lud. 55 Sallord Electronic Devices, Lud. 56 Barker Maural, Reproduces	Appointments Vacant 148, 162, 165, 164, 165 Arcolectric Switches, Ltd.	Harriey, H. A., Co., Ltd.	Rexon Industries, Ltd
Athverth, B., Statistics, Lid. 163 Automatic Cull Winder & Electrical Issuer 110 Lid. 60 Automatic Cull Winder & Electrical Issuer 110 Lid. 60 Automatic Cull Winder & Electrical Issuer 110 Lid. 160 Automatic Cull Winder & Electrical Issuermas, Lud. 160 Sallord Electrical Instruments, Lud. 54 Barker Maural Reproduces 110 Lid. 160 Sallord Electrical Instruments, Lud. 56 Barker Maural, Reproduces 110 Hinds Electronic Devices, Lud. 160 Sallord Electrical Instruments, Lud. 56 Barker Maural, Reproduces 110 Hinds Electronic Devices, Lud. 160 Sallord Electrical Instruments, Col. 56 Barker Maural, Reproduces 110 Instruments, Electronic Devices, Lud. 160 56 Barker Maural, Reproduces 160 Sallord Electronic Devices, Lud. 56 Sallord Electronic Devices, Lud. 56 Barker Maural, Reproduces 160 Sallord Electronic Devices, Lud. 55 Sallord Electronic Devices, Lud. 56 Barker Maural, Reproduces	Ariel Sound Trialericion Co	Hatfield Radio Heath Spring & Notion Co., Ltd., 10 Henley's, W. T., Telegraph Works Co.,	6 Rogers Development Co 44
Automatic Coil Winder & Electrical Boult- ment Co. Ltd. 56 Autoset (Production). Ltd. 100 Barder Natural Reproduces 120 Barder Natural Reproduces 120 Barder Natural Reproduces. 120 Bardial Diarin Redo 120	Army Emergency Reserve (Royal Signals) 40 Ashworth. H	Ltd. 19 Henry's 14	Dunhakan Flactrical Duoduota 100
Barten, Trans, Supply Co.163Bernman, S. Lew, Dud.163Bernman, S. Lew, Dud.163Bernson, W. A. Wavey, Ltd.163Bernson, W. A. Wavey, Ltd.163Bernson, W. A. Wavey, Ltd.164Bernson, W. A. Wavey, Ltd.164Bernson, W. A. Wavey, Ltd.165Bernson, W. A. Wavey, Ltd.164Bernson, W. A. Wavey, Ltd.165Bernson, W. A. Wavey, Ltd.166Bernson, W. A. Wavey, Ltd.166Bernson, Charl, M. M. K. Co.166Bernson, Charl, M. M. K. Sons, M. M. M. K. Co.	Automatic Coil Winder & Electrical Equip-	Hivac, Ltd. 60, 11 Holley's Radio 10	Salford Electrical Instruments, Ltd 54
Barten, Trans, Supply Co.163Bernman, S. Lew, Dud.163Bernman, S. Lew, Dud.163Bernson, W. A. Wavey, Ltd.163Bernson, W. A. Wavey, Ltd.163Bernson, W. A. Wavey, Ltd.164Bernson, W. A. Wavey, Ltd.164Bernson, W. A. Wavey, Ltd.165Bernson, W. A. Wavey, Ltd.164Bernson, W. A. Wavey, Ltd.165Bernson, W. A. Wavey, Ltd.166Bernson, W. A. Wavey, Ltd.166Bernson, Charl, M. M. K. Co.166Bernson, Charl, M. M. K. Sons, M. M. M. K. Co.	Autoset (Production), Ltd 106	Household Electrix, Ltd. 10 H.P. Radio Services, Ltd. 14	2 Savage Transformers, Ltd
Belling & Les Ldd 100 Belling & Les Ldd 100 Bernson, W. A meet Lid	Barton's (Radio)		A Sherman's Supply Co 163
Bit X Partices Lid. 100 Bit X Particess Lid. 100 <td>Beamish, V. W. Belling & Lee. Ltd. Bell. John. & Croyden</td> <td>Iliffe Books 66. 79. 14</td> <td></td>	Beamish, V. W. Belling & Lee. Ltd. Bell. John. & Croyden	Iliffe Books 66. 79. 14	
Bindrade de la cale de	Bel Sound Products, Ltd. 153 Benson, W. A. 146 Berry's (Short Waye) Ltd. 68	international Correspondence Schools	Smith. H. L., & Co., Ltd. 152
Britalin, Luis, Co. 113 Communications Coron, Lid. 126 Sentroy, Lid. 156 Britalis, Conmunications Coron, Lid. 126 Sentroy, Lid. 156 Specialist Switches 156 Britalis, Conmunications Coron, Lid. 126 Kineston Electrical Supplies 166 Siamford, A. L. 152 Britalis, Dainiaet di Callender's Cables, Lid. Koske, B. 146 Shar Metal Plate Works 41.82, 22.125, 126, 120 Britalis, National Radio School 148 Laico Compounds, Lid. 127 Sterm Radio, Lid. 128 Britalis, Sarazol, Lid. 148 Laico, Compounds, Lid. 129 Sterm Radio, Lid. 120 Britalis, Arita, Senzaol, Lid. 148 Laico, Compounds, Lid. 129 Sterm Radio, Lid. 126 Brotokes, Crystala, Lid. 149 Laky's Radio Co. 129 Start Transformers, Lid. 140 Builtoher, H., & Co. 161 Laky's Radio Co. 129 Start Transformers, Lid. 160 Brotake, Lid. 146 146 Start Transformers, Lid. 160 Start Transformers, Lid. 160 Builtoher, H., & Co. 161 Lockwood, e. Co. Radio Stores, 16	Birmingham Sound Reproducers, Ltd. 80 B. K. Partners, Ltd. 52 Blatting Fraineering Ltd 118	Jackson Bros, (London). Ltd 11 Jackson Radio	2 Solarton Electronic Group, Ltd 102
British Chas (Radio), Lid. 140 140 Simulation (Communications Corp., Lid. 150 British Dommunications Corp., Lid. 155 156 156 British Dimensions College 155 156 British Communications College 155 156 British Standard Telephones & Cables, Lid. 156 Brown, S. G. Lid. 156 Buil, J. & Sons 70 Buil, J. & Sons 70 Buil, J. & Sons 70 Cander Ströphonics, Lid. 156 Cander Ströphonics, Lid. 156 Cander Ströphonics, Lid. 156 Cables Componer, Lid. 156 Cahodeon Crystals, Lid. 156 Cahodeon Crystals, Lid. 156 Cahodeon Crystals, Lid. 156 Cahodeon Crystals, Lid. 156		Kempner, S.	6 Specialist Switches
British 'Insulated Callender's Cables, Ltd. Cover 14 British 'Insulated Callender's Cables, Ltd. Cover 14 British 'Insulated Callender's Cables, Ltd. 140 British 'Insulated Callender's Cables, Ltd. 150 British 'Insulated Callender's Cables, Ltd. 150 British 'Insulated Callender's Cables, Ltd. 160 British 'Insulated Callender's Cables, Ltd. 160 Builer, Ltd. 160 Builer, Ltd. 160 Cander System Co. 150 Cahafey Cahlet, Co. 150 Cander System Co. 150 Cander System, Co. 150 Cander System, Co. 150 Cander System, Co. 150 Cander System, Co. 150 Cander Syste	British Communications Corpn., Ltd. 25 British Communications Corpn., Ltd. 25	Revenutch Co The	4 Stamford A T
British National Radio School11	British Distributing Co. British Institute of Engineering Tech- nology 153. 154	Kolectric, Ltd. Koskie, B	6 Star Metal Plate Works
British Physical Laboratories 13 ment Co. 129 116 clock and Frankformers, Lid. 60 British Serzaci, Lud. 56 clock and frankformers, Lid. 56 clock and frankformers, Lid. 56 Brookes Crackal, Lid. 56 clock and frankformers, Lid. 56 Supacols 50 Bull, J., & Sons 70 clock and frankformers, Lid. 56 Supacols 50 Bull, F., & Co. 16 clock and frankformers, Lid. 56 Supacols 50 Bull, F., & Sons 70 Light Soldering Developments, Lid. 150 Suiton Coldfield Electrical Engineers 74 Candler System Co. 166 Cockwood & Co. 116 Cockwood & Co. 116 Candler System Co. 155 C. R. Supply Co., Lid. 107 Takor Flectrical Industries, Lid. 150 Candler System Co. 155 Magnetic Coatings, Lid. 166 166 17 Telestrath Consenser Co., Lid. 107 Candler System Co. 166 166 166 166 166 166 17 Telestrath Industries, Lid. 110 Canadie Ald Co. 16		Lafco Compounds, Ltd. 15 Lancaster Hi-Fidelity Acoustical Equip-	7 Stead, J., & Co., Ltd
Butcher, H., & Co.161Löckwood & Co.114Candler System Co.156Lowther Mfg. Co.167Cander System Co.156Lowther Mfg. Co.167Cander Cristais, Ltd.156Lowther Mfg. Co.160Champion Products, Ltd.144Lyons, Caude, Ltd.147Champion Products160Cover 111Champion Products160Champion Products160Champion Products160Champion Products160Champion Products152Champion Products160Champion Products161Champion Products162Champion Products164Champion Products164		ment Co. 11 Lasky's Radio	6 Stewart Transformers, Ltd
Butcher, H., & Co.161Löckwood & Co.114Candler System Co.156Lowther Mfg. Co.167Cander System Co.156Lowther Mfg. Co.167Cander Cristais, Ltd.156Lowther Mfg. Co.160Champion Products, Ltd.144Lyons, Caude, Ltd.147Champion Products160Cover 111Champion Products160Champion Products160Champion Products160Champion Products160Champion Products152Champion Products160Champion Products161Champion Products162Champion Products164Champion Products164	Brown, S. G., Ltd. 56 Bulgin, A. F., & Co., Ltd. Edit. 99 Bulgins, Ltd. 48	Lee Products (Gt. Britain). Ltd.	6 Superior Radio Supplies 112 2 Sutton Coldfield Electrical Engineers 74
Cementation (Muffelite), Ltd. 15 Chaffey Cabinet Co. 160 Magnetic Coatings, Ltd. 166 Champion Products 159 Ciapman, C. T. (Reproducers), Ltd. 155 Magnetic Coatings, Ltd. 166 Magnetic Coatings, Ltd. 166 Magnetic Coatings, Ltd. 167 Cie Generale de Metrologie 120 Marcoul Instruments, Ltd. 161 Ciyre Radio, Ltd. 17 Marcoul Instruments, Co., Ltd. 10 Ciyre Radio, Ltd. 164 Ciyre Radio, Ltd. 164 Colarna, O. Ltd. 174 Marcoul Instruments, Co., Ltd. 162 Colarna, O. Ltd. 164 Colarna, C. C., Ltd. 164 Coberna, A. C., Ltd. 164 Coberna, A. C., Ltd. 164 Minnesota Mining & Manufacturing Co. 164 Minnesota Mining & Manufacturing Co. 164 Modern Book Co. 16	Buil, J., & Sons 70 Butcher, H., & Co. 161	Lookwood & Co	Tannov Products Ltd
Cementation (Muffelite), Ltd. 15 Chaffey Cabinet Co. 160 Magnetic Coatings, Ltd. 166 Champion Products 159 Ciapman, C. T. (Reproducers), Ltd. 155 Magnetic Coatings, Ltd. 166 Magnetic Coatings, Ltd. 166 Magnetic Coatings, Ltd. 167 Cie Generale de Metrologie 120 Marcoul Instruments, Ltd. 161 Ciyre Radio, Ltd. 17 Marcoul Instruments, Co., Ltd. 10 Ciyre Radio, Ltd. 164 Ciyre Radio, Ltd. 164 Colarna, O. Ltd. 174 Marcoul Instruments, Co., Ltd. 162 Colarna, O. Ltd. 164 Colarna, C. C., Ltd. 164 Coberna, A. C., Ltd. 164 Coberna, A. C., Ltd. 164 Minnesota Mining & Manufacturing Co. 164 Minnesota Mining & Manufacturing Co. 164 Modern Book Co. 16	Candler System Co. 156	Lowther Mfg. Co. L. R. Supply Co., Ltd.	5 Taylor Electrical Instruments, Ltd 43 7 Telecraft, Ltd
Citangman, Carl Cheproducers). Lid.155Mar Col. Destruction. Lid.10052Citangman, Carl Cheproducers). Lid.100Marconi Survesses. Telegraph Col. Lid.101City Sale & Exchange. Lid.110Marconi Survesses Telegraph Col. Lid.101City Sale & Exchange. Lid.110Marconi Survesses Telegraph Col. Lid.102City Sale & Exchange. Lid.110Marconi Survesses Telegraph Col. Lid.102City Sale & Exchange. Lid.113Marconi Survesses Telegraph Col. Lid.102Cipdesdale Supply Co.134135McGraw-Hill Publishing Col. Lid.162Cohen, D.155137McGraw-Hill Publishing Col. Lid.162Cossor, A. C. Lid.156McGraw-Hill Publishing Col.164Cossor, A. C. Lid.156McMudo Instruments Col.164Coventry Radio154156Minnesota Mining & Manufacturing Col.Cranston, Alan156Modern Book Co.156Davis, A., & Co.156Modern Sound Equipments160Davis, A., & Co.156Modern Sound Equipments160Direct TV, Replacements177Morley Transformers164Direct TV, Replacements177McGraw States, Lid.120Direct TV, Replacements177Morley Transformers164Direct TV, Replacements165Multard, Ltd.37Dubite Condenser Co. (1925). Ltd.157Multard, Etd.36Dubite Co.156Northern Radio Services3637Du	Cape Electrophonics. Ltd. 133 Cathodeon Crystais. Ltd. 4 Cementation (Muffelite), Ltd. 73	Lyons Radio	⁶ Tele-Radio (1943), Ltd Cover iii
Cranston, Alan 162 Ltd. 64 Valradio, Ltd. 116 Davies, A., & Co. 156 Modern Book Co. 150 112 Verdik Sales, Ltd. 61 Davies, Jack (Relays), Ltd. 116 Modern Techniques 94 112 Verdik Sales, Ltd. 120 Davies, Jack (Relays), Ltd. 117 Modern Techniques 94 112 Vitavox, Ltd. 120 Davies, Jack (Relays), Ltd. 117 Modern Techniques 94 166 162 164 Direct T.V. Replacements 70 Milard, Ltd. 37, 20, 48, 67, 82 93 93 Dinonders (Timers) 160 Multicore Solders, Ltd. 54. Cover iv Watson Watch Co., The 162 Dukie & Co. 157 157 157 157 157 157 162 Watrex, Ltd. 106 Duch-Sobleson Electrical Co. 156 Northern Radio Services 36, 37 97 Webb's Radio 106, 162 Vortex M. Ming, Ltd. 126 126 126 126 126 126 Dukie Co., Ltd., The 157 157 166 162 </td <td>Chaffey Cabinet Co. 160 Champion Products 159 Chapman, C. T. (Reproducers), Ltd. 155</td> <td>Magnetic Coatings, Ltd. Magnetic Devices, Ltd</td> <td>1 Trianon Electric, Ltd</td>	Chaffey Cabinet Co. 160 Champion Products 159 Chapman, C. T. (Reproducers), Ltd. 155	Magnetic Coatings, Ltd. Magnetic Devices, Ltd	1 Trianon Electric, Ltd
Cranston, Alan 162 Ltd. 64 Valradio, Ltd. 116 Davies, A., & Co. 156 Modern Book Co. 150 112 Verdik Sales, Ltd. 61 Davies, Jack (Relays), Ltd. 116 Modern Techniques 94 112 Verdik Sales, Ltd. 120 Davies, Jack (Relays), Ltd. 117 Modern Techniques 94 112 Vitavox, Ltd. 120 Davies, Jack (Relays), Ltd. 117 Modern Techniques 94 166 162 164 Direct T.V. Replacements 70 Milard, Ltd. 37, 20, 48, 67, 82 93 93 Dinonders (Timers) 160 Multicore Solders, Ltd. 54. Cover iv Watson Watch Co., The 162 Dukie & Co. 157 157 157 157 157 157 162 Watrex, Ltd. 106 Duch-Sobleson Electrical Co. 156 Northern Radio Services 36, 37 97 Webb's Radio 106, 162 Vortex M. Ming, Ltd. 126 126 126 126 126 126 Dukie Co., Ltd., The 157 157 166 162 </td <td>Cie Generale de Metrologie</td> <td>Marconi Instruments, Ltd. Marconi's Wireless Telegraph Co., Ltd.</td> <td>0 Truvox, Ltd 113</td>	Cie Generale de Metrologie	Marconi Instruments, Ltd. Marconi's Wireless Telegraph Co., Ltd.	0 Truvox, Ltd 113
Cranston, Alan 162 Ltd. 64 Valradio, Ltd. 116 Davies, A., & Co. 156 Modern Book Co. 150 112 Verdik Sales, Ltd. 61 Davies, Jack (Relays), Ltd. 116 Modern Techniques 94 112 Verdik Sales, Ltd. 120 Davies, Jack (Relays), Ltd. 117 Modern Techniques 94 112 Vitavox, Ltd. 120 Davies, Jack (Relays), Ltd. 117 Modern Techniques 94 166 162 164 Direct T.V. Replacements 70 Milard, Ltd. 37, 20, 48, 67, 82 93 93 Dinonders (Timers) 160 Multicore Solders, Ltd. 54. Cover iv Watson Watch Co., The 162 Dukie & Co. 157 157 157 157 157 157 162 Watrex, Ltd. 106 Duch-Sobleson Electrical Co. 156 Northern Radio Services 36, 37 97 Webb's Radio 106, 162 Vortex M. Ming, Ltd. 126 126 126 126 126 126 Dukie Co., Ltd., The 157 157 166 162 </td <td>Classic Electrical Co., Ltd</td> <td>Martin, J. H</td> <td>2 Unitelex (London), Ltd</td>	Classic Electrical Co., Ltd	Martin, J. H	2 Unitelex (London), Ltd
Cranston, Alan 162 Ltd. 64 Valradio, Ltd. 116 Davies, A., & Co. 156 Modern Book Co. 150 112 Verdik Sales, Ltd. 61 Davies, Jack (Relays), Ltd. 116 Modern Techniques 94 112 Verdik Sales, Ltd. 120 Davies, Jack (Relays), Ltd. 117 Modern Techniques 94 112 Vitavox, Ltd. 120 Davies, Jack (Relays), Ltd. 117 Modern Techniques 94 166 162 164 Direct T.V. Replacements 70 Milard, Ltd. 37, 20, 48, 67, 82 93 93 Dinonders (Timers) 160 Multicore Solders, Ltd. 54. Cover iv Watson Watch Co., The 162 Dukie & Co. 157 157 157 157 157 157 162 Watrex, Ltd. 106 Duch-Sobleson Electrical Co. 156 Northern Radio Services 36, 37 97 Webb's Radio 106, 162 Vortex M. Ming, Ltd. 126 126 126 126 126 126 Dukie Co., Ltd., The 157 157 166 162 </td <td>Cosmocord, Ltd. 84 Cosmocord, Ltd. 84</td> <td>Metropolitan-Vickers Electrical Co., Ltd 10 Mid.and Instrument Co.</td> <td>Universal Electrical Instruments Corpn 141</td>	Cosmocord, Ltd. 84 Cosmocord, Ltd. 84	Metropolitan-Vickers Electrical Co., Ltd 10 Mid.and Instrument Co.	Universal Electrical Instruments Corpn 141
Dun-Sobieson Electrical Co. 156 Northern Radio Services 36. 37 Norton & Gregory, Ltd. 120 Webby Radio 106, 162 Webby Relectrical Laboratories Ltd. 120	Cranston, Alan	Ltd. Modern Book Co.	4 Valradio, Ltd. 116
Dun-Sobieson Electrical Co. 156 Northern Radio Services 36. 37 Norton & Gregory, Ltd. 120 Webby Radio 106, 162 Webby Relectrical Laboratories Ltd. 120	Davies, A., & Co. Davis, Jack (Relays), Ltd.	Modern Sound Equipments	V.E.S. Wholesale Services, Ltd. 120 Vitayox, Ltd. 74
Dun-Sobieson Electrical Co. 156 Northern Radio Services 36. 37 Norton & Gregory, Ltd. 120 Webby Radio 106, 162 Webby Relectrical Laboratories Ltd. 120	Denco (Clacton), Ltd. 117 Direct T.V. Replacements 70 Dixon, L. & Co. 154	M.R. Supplies, Ltd. Mullard, Ltd. 3, 7, 20, 48, 67,	4 Vortexion, Ltd
Dun-Sobieson Electrical Co. 156 Northern Radio Services 36. 37 Norton & Gregory, Ltd. 120 Webby Radio 106, 162 Webby Relectrical Laboratories Ltd. 120	Donohoe's (Timers) Dubilier Condenser Co. (1925), Ltd	Mult.core Solders, Ltd. 54. Cover Multitone Electric Co., Ltd. Murex, Ltd.	Watson Watch Co. The
orrwegian M.ning, Ltd. 120 Welwyn Electrical Laboratories Ltd. 100, 162	Duki Co., Ltd., The 157 Dun-Sobleson Electrical Co. 156	Northern Radio Services	Wayne Kerr Laboratories, Ltd., The 9 7 Webber, R. A., Ltd
Edison Swan Electric Co. Ltd. 45 69 891		orwegian M.ning, Ltd. 12 Ju-Swift, Ltd. 16	Welwyn Electrical Laboratories, Ltd 104 West End Radio, Ltd 152
	Easco Electrical, Ltd. 160 Edison Swan Electric Co., Ltd. 45, 69, 89 Egen Electric, Ltd. 3 Electrical Instrument Repair Service, The 158	Oddle, Bradbury & Cull. Ltd	Westinghouse Broke & Fignal Co. FAL
Electro-Acoustic Developments 150 Electro-Acoustic Industries, Ltd. 150 Electro-Acoustic Industries, Ltd. 150 Electro-Acoustic Industries, Ltd. 150 Whitaker, H. 120 Painton & Co., Ltd. 13	Electro-Acoustic Developments 159 Electro-Acoustic Industries, Ltd. 12 Electro-Acoustic Edulyment 96, 97, 98, 99	Oxley Developments Co., Ltd.	Whiteley Electrical Radio Co. Ltd
Electro-Winds Lid 13 Winterey Lectrical Radio Co. Ltd. 31 Elison Transformers, Ltd 12 Parker, A. B. 16 Whitesey Lectrical Radio Co. Ltd. 16 Elison Transformers, Ltd 12 Parker, A. B. 16 Whitesey, A. J. (Aeradio), Ltd. 160 E.M.I. Factories, Ltd 2, 54, 91, 94 94 74 Willesden Transformer Co., Ltd. 161 E.M.I. Factories, Ltd 142 Willesden Transformer Co., Ltd. 161 E.M.I. Factories, Schere R. J. 164 142 Willesden Transformer Co., Ltd. 161 E.M.D. Fearce, T. W. 142 Willesden Transformer Co., Ltd. 161	Electro-Winds, Ltd. 120 Ellison Transformers, Ltd. 112 E.M.I. Factories, Ltd. 88	Parker, A. B. 11 Parsonage, W. F., & Co., Ltd. 11	White, S. S., Co. of Gt. Britain, Ltd., The 51 Whittemore, A. J. (Aeradio), Ltd 160
E.M.I. Institutes 2, 54, 91, 94 English Electric Valve Co., Ltd. 105 Pearce T. W. 146 Wilkinson, L. 161 Vearce T. W. 146 Woder Transformer Co., Ltd. 36 Pearce T. W. 146 Woder Transformers, Ltd. 117		P.C.A. Radio 14 Pearce, T. W. 14 Pearce, T. W. 14	Willesden Transformer Co., Ltd
Ever Ready Co. (Gt. Britain). Ltd., The 14 E.W.A. 158 Fillips Electrical, Ltd. 74 Wolf Electric Tools, Ltd. 42 Philips Electrical Supplies, Ltd. 42 Voolleys Radio & Electrical Supplies, Ltd. 118	Ever Ready Co. (Gt. Britain), Ltd., The 14	Phillips Control (Gt. Britain), Ltd.	Wolf Electric Tools, Ltd. 42 8 Voolleys Radio & Electrical Supplies, Ltd. 140
Plessey Co., Ltd., The 15 Woolwich Polytechnic 116 Post Radio Supplies 152 Wright & Weaire, Ltd. 5 Power Controls, Ltd. 27	Ferranti. Ltd	Post Radio Supplies	5 Woolwich Polytechnic 116 2 Wright & Weaire, Ltd. 5
Pilmer, J T. 25 Power Controls, Ltd. 27 Pilmer, J T. 156 Prat's Radio 27 Pisher Electronics Co. Ltd. 33 Premiler Radio Co. 76. 77. 78. 79 Poyle, W. & G., Ltd. 116 Proops Bross, Ltd. 138 Purrehill Laboratories, Ltd. 61 Pye, W. G., & Co., Ltd. 6	Fisher Electronics Co., Ltd	Props Bros. Ltd.	9 Young, C. H 138
Electron-Acoustic Industries. Ltd.12Electron-Winds. Ltd.120Electron-Winds. Ltd.120Elison Transformers. Ltd.120Elison Transformers. Ltd.120E.M.I. Factories, Ltd.120Enthown Solders, Ltd.120Enthown Solders, Ltd.120Enthown Solders, Ltd.120Enthown Solders, Ltd.120Ew.A.120Parkeir, A. B.121Enthown Solders, Ltd.120Enthown Solders, Ltd.100Perrent, Ltd.120Perranti, Ltd.120Perranti, Ltd.120Perranti, Ltd.120Pilmer, J. T.126Pisher Electronics Co., Ltd.136Pinker, J. T.126Power Controls Ltd.126Pisher Electronics Co., Ltd.136Pinker, J. T.136Pinker, J. T.136Pinker, J. T.136Pinker, J. T.136Premier Radio Co.76, 77, 78, 79Power Controls Co., Ltd.136Purnikit60Pye. Ltd.136Purnikit61Pye. W. G., & Co., Ltd.61Pye. W. G., & Co., Ltd.136Purnikit61Pye. W. G., & Co., Ltd.61Pye. W. G., & Co., Ltd.61 <td>Furnikit 60 Furzehill Laboratories, Ltd. 61</td> <td>Pye. U. G., & Co., Ltd. 24.</td> <td>9 6 Z. & I. Aero Services. Ltd 140</td>	Furnikit 60 Furzehill Laboratories, Ltd. 61	Pye. U. G., & Co., Ltd. 24.	9 6 Z. & I. Aero Services. Ltd 140

Printed in Great Britain for the Publishers. LLIFFE & SONS LFD., Dorset House, Stamford St., London, S.E.1, by CORNWALL PRESS LTD., Parly Garden, London, S.E.1 Wireless World can be obtained abroad from the following: AUSTRALLA AND NEW ZRALAND: Gordon & Gotch, Ltd. INDIA: A. H. Wheeler & Co. CANADA: The Wim. Dawson Summerphion World can be obtained abroad from the following: AUSTRALLA AND NEW ZRALAND: Gordon & Gotch, Ltd. INDIA: A. H. Wheeler & Co. CANADA: The Wim. Dawson Summerphion World can be obtained abroad from the following: AUSTRALLA AND NEW ZRALAND: Gordon & Gotch, Ltd. J. NITED STATES: The International News Co. The most promising manufacturing development for 20 years/

- Eliminates many expensive chassis operations.
- ★ Saves material and speeds assembly.
- ★ Virtually replaces all hand wiring.
- ★ Greater compactness cuts cabinet costs.
- Ensures uniformly consistent performance.

Thoroughly experienced in the accurate appraisal of all new electronic developments, T.C.C. has been quick to recognise the far reaching advantages to the Industry of the Printed Circuit.

For here, we predict, is something destined to revolutionise the whole process of assembly. Developments already carried out in the T.C.C. laboratories indicate that this new technique, by the elimination of much costly chassis presswork, permits great savings to be effected in time, labour and materials. But the advantages are not confined to production alone. Already much evidence has been accumulated to prove that the Printed Circuit permits the immediate achievement of higher standards of performance with a far greater degree of consistency and reliability than hitherto deemed possible.

Those interested in the various applications of Printed Circuits in the electronic industry are invited to register their names to receive our Technical Bulletins as issued. Manufacturers should apply to our Special Products Division for details of service available.

THE TELEGRAPH CONDENSER CO. LTD SPECIAL PRODUCTS DIVISION . North Acton . London . W.3 . Tel: ACORN 0061

PRINTED

CIRCUITS



Wireless World

FEBRUARY, 1955

Whatever your soldering problem

MULTICORE SOLDERS LTD.

give you the right answer

You will find the right solder for any soldering job in the comprehensive Multicore range of gauges, alloys and fluxes. And you will find it economical too, because the 5 separate cores of Ersin Flux in Ersin Multicore Solder provide a steady flux stream; no lengths of solder are wasted and the risk of making dry joints through insufficient flux is eliminated. Ersin Flux is a very fast activated rosin which cleans even the most heavily oxidised surfaces at great speed. As Ersin Multicore 5-core Solder is so fast, it is often possible to make considerable savings by equally effectively using an alloy of lower tin content.



QUID FIEL

EBSIN

FOR FACTORY USE

Ersin Multicore Solder is supplied on 7 lb. reels for factory use in 6 standard tin/lead alloys and 9 gauges from 10 to 22 s.w.g. Finer gauges are supplied on 1 lb. reels. It is also made in special high and low

melting point alloys and meets all A.I.D., G.P.O. and A.R.B. requirements. Prices on application.

SPECIALISED PRODUCTS FOR MANUFACTURERS LIOUID AND JELLY FLUXES

Ersin Flux in liquid form is available for processes where cored solder cannot be used. For large surfaces to which insufficient liquid flux would adhere, there is a high viscosity red jelly which is supplied in size JELEY FLOX 12 tins at 4/6 each (subject). It is approved by the Ministry of Supply.



FOR SERVICE ENGINEERS

For service engineers and radio enthusiasts the 5/-(subject) Size 1 Carton is the handiest size and there are 4 specifications to choose from. The 1 lb. reel (price 15/- subject) contains approximately 167 ft. of 18 s.w.g. Ersin Multicore Solder in 50/50 alloy.

AUG AUG	SIZE 1 CARTONS 5/-			(SUBJECT)		
	Catalogue Ref. No.	Alloy Tin Lead	s.w.g.	Approx. length per carton		ERSIN 911 Actorie
1 Ib. REEL	C 16014	60/40	14	21	feet	HT.
15/-	C 16018	60/40	18	55		SOLDEN
SUBJECT)	C 14013	40/60	13	19	10	A DOWN
	C 14016	40/60	16	33		Statement of the local division of the local

BID WIRE STRIPPER & CUTTER

For the modest price of 3/6 you can get a Bib Wire Stripper and Cutter-a handy 3 in 1 tool that will save you hours of time and irritation. The sturdy, nickel-plated tools strip insulation without nicking the wire, cut wires cleanly and split plastic extruded twin flex. They are adjustable to most wire thicknesses. 3/6 (SUBJECT).



SPLICER





Among the enthusiastic comments made by the press is the following one by P. Wilson, Technical Editor of 'The Gramophone', who says in the Jan. 1955 issue: "..... Everyone who uses a tape recorder will need this little tool. It is indispensable...." Price 18/6 (SUBJECT).

MULTICORE SOLDERS LTD., MULTICORE WORKS, HEMEL HEMPSTEAD, HERTS. (BOXMOOR 3636)