

TO ALL AEROVOX RESEARCH WORKER SUBSCRIBERS:

Once again we are happy to provide an opportunity to bring your Research Worker file up-to-date. This listing covers 135 issues published since 1931 that are presently available. Unless otherwise specified, all issues are Five Cents (5c) each. Each issue has been numbered and all the numbers appear on a convenient order form on the reverse side of this sheet. Simply circle the numbers of those issues that you want, enclose your remittance and mail to: Aerovox Research Worker, Aerovox Corporation, New Bedford, Mass. Please be sure to include your name and address.

DATE OF ISSUE	Vol.	No.	TITLE	DATE OF ISSUE	Vol.	No.	TITLE
1—March-April 1931 *	4	3	Filtering Amateur Transmitters to Meet U. S. Regulations.	47—June 1939	11	6	A Guide to the New Tubes (Part I).
2—November 1933	5	3	Developments in Design of Small-Size Electrolytic Condensers.	48—July 1939	11	7	A Guide to the New Tubes (Part II).
3—December 1933	5	4	Rectifier Developments During '33.	49—August 1939	11	8	Television Receivers (Part I).
4—March 1934	6	3	Uses of Concentrically-Wound Electrolytic Condensers.	50—September 1939	11	9	Television Receivers (Part II).
5—April 1934	6	4	The Proper Use of Condensers in High Voltage Filter Circuits.	51—October 1939	11	10	Television Receivers (Part III).
6—June 1934	6	6	A Modern Amateur Transmitter.	52—November 1939	11	11	Television Receivers (Part IV).
7—July 1934	6	7	Electrolytic Condensers for Condenser-Start Type Motors.	53—December 1939	11	12	Television Receivers (Part V).
8—August 1934	6	8	Important Features in Design of High Voltage Transmitting Filter Condensers.	54—January 1940	12	1	Television Receivers (Part VI).
9—December 1934	6	12	Voltage Dividers: Their Application and Design (Part I).	55—February 1940	12	2	Frequency Modulation.
10—January 1935	7	1	Voltage Dividers: Their Application and Design (Part II).	56—May 1940	12	5	Power Factor Correction.
11—February 1935	7	2	Methods of Calculating the Current Carrying Capacity of Resistors.	57—June 1940	12	6	Use of the L-C Checker for R. F. Measurements.
12—March 1935	7	3	Condenser Leakage and Its Effects.	58—July 1940	12	7	Measuring Distortion in Audio Frequency Amplifiers.
13—April 1935	7	4	The Use of Condensers in Radio Receivers (Part I).	59—August 1940	12	8	Receiver Tuned Circuits.
14—May 1935	7	5	The Use of Condensers in Radio Receivers (Part II).	60—October 1940	12	10	Modern Trends in Service Test Equipment (Part II).
15—June 1935	7	6	Connecting Condensers in Series.	61—March 1941	13	3	Fixed Condensers in Radio Transmitters.
16—July 1935	7	7	Simple Methods of Measuring Resistance.	62—April 1941	13	4	R. F. Power Amplifier Operation.
17—August 1935	7	8	The Proper Use of Resistors to Extend Meter Ranges.	63—May 1941	13	5	Radio Control Systems (Part I).
18—September 1935	7	9	Testing Electrolytic Motor-Starting Condensers.	64—June 1941	13	6	Radio Control Systems (Part II).
19—October 1935	7	10	The Functions of C and R in A. V. C. Circuits.	65—Oct.-Nov. 1941 *	13	10/11	Industrial Applications of Electronic Devices (Part II).
20—November 1935	7	11	Laws of Alternating Currents (Part I).	66—March 1942	14	3	Transformerless Power Supplies (Part II).
21—December 1935	7	12	Laws of Alternating Currents (Part II).	67—July 1942	14	7	High-Efficiency R. F. Amplifiers.
22—January 1936	8	1	Reactance and Resistance in Parallel.	68—August 1942	14	8	Capacitors in Control Circuits.
23—February 1936	8	2	Power Supplies (Part I).	69—Nov.-Dec. 1942 *	14	11/12	Design Data for m-Derived Type Filters (Part II).
24—March 1936	8	3	Power Supplies (Part II).	70—March 1943	15	3	Dry-Disc Rectifiers.
25—April 1936	8	4	Types of Condensers and Their Applications.	71—April 1943	15	4	H. F. Frequency Measurements (Part I).
26—May 1936	8	5	Vacuum Tube Methods of Measuring Insulation Resistance of Condensers.	72—July 1944	16	7	Capacitor Quality Factors.
27—June 1936	8	6	Peak Voltages.	73—August 1944	16	8	Design Data for Constant-k Band-Suppression Filters (Part V).
28—July 1936	8	7	Reactance and Resistance in Series.	74—September 1944	16	9	Design Data for m-Derived Type Filters (Part VI).
29—August 1936	8	8	Regulating Properties of Wet Electrolytic Condensers.	75—October 1944	16	10	Design Data for m-Derived Type Filters (Part VII).
30—October 1936	8	10	The Use of Mica Condensers in Transmitters.	76—November 1944	16	11	Design Data for m-Derived Type Filters (Part VIII).
31—December 1936	8	12	Volume Expansion.	77—December 1944	16	12	Design Data for m-Derived Type Filters (Part IX).
32—March 1937	9	3	The Use of Oil Condensers in Amateur Transmitters.	78—Jan.-Feb. 1945 *	17	1/2	Methods of Measuring High Voltages.
33—May 1937	9	5	Hints on High Fidelity.	79—March-April 1945 *	17	3/4	Design Data for Tuned R-C Circuits.
34—June 1937	9	6	Amplifiers (Part I).	80—July-August 1945 *	17	7/8	Methods of Testing Solid Dielectrics (Part II).
35—July 1937	9	7	Amplifiers (Part II).	81—January 1949	19	1	Video I. F. Amplifier Design.
36—February 1938	10	2	Practical Methods of Testing Condensers (Part II).	82—February 1949	19	2	The Transistor-An Amplifying Crystal.
37—March 1938	10	3	Practical Methods of Testing Condensers (Part III).	83—March 1949	19	3	A Television Booster Amplifier: (Part I—Design).
38—April 1938	10	4	Practical Methods of Testing Condensers (Part IV).	84—April 1949	19	4	A Television Booster Amplifier: (Part II—Design).
39—June 1938	10	6	Practical Methods of Testing Condensers (Part VI).	85—May 1949	19	5	Cathode-Ray Tube High-Voltage Supplies.
40—July 1938	10	7	Measurement of Inductance.	86—June 1949	19	6	Television Inter-Carrier Sound Reception.
41—August 1938	10	8	Vacuum-Tube Voltmeters (Part I).	87—July 1949	19	7	Directional VHF Antennas.
42—September 1938	10	9	Vacuum-Tube Voltmeters (Part II).	88—August 1949	19	8	Directional VHF Antennas: (Part II—Practical Designs).
43—October 1938	10	10	Measurement of Inductance (Part II).	89—September 1949	19	9	The Direct-Current Meter.
44—March 1939	11	3	The Measurement of Motor-Starting Capacitors.	90—October 1949	19	10	UHF Receiving Tubes and Circuits.
45—April 1939	11	4	Sweep Circuits.	91—November 1949	19	11	The Citizens Radio Service.
46—May 1939	11	5	New Tubes for Television.	92—December 1949	19	12	UHF Television.
				93—January 1950	20	1	Television Interference Filters.
				94—March 1950	20	3	Fixed Capacitors in Modern Circuitry.
				95—April 1950	20	4	Introduction to Pulse Modulation.
				96—May 1950	20	5	Amateur Applications of Crystal Diodes.
				97—August 1950	20	8	UHF Frequency Standards

* Combined issues — 10c. **Complete supplement — Cannot be ordered separately — 25c.

No. 35530M

(LISTING CONTINUED ON OTHER SIDE)

DATE OF ISSUE	Vol.	No.	TITLE	DATE OF ISSUE	Vol.	No.	TITLE
September 1950	20	9	Regulated Power Supply Design.	116—Oct.-Nov. 1952 *	22	10/11	Recent Developments in Transistors.
October 1950	20 10	10	Audio Frequency Distortion Measurements: (Part I—Methods of Measurement)	117—December 1952	22	12	New Trends in Transmission Lines.
100—December 1950	20	12	Television Antenna Installation: (Part I—Erecting the Fringe-Area Antenna).	118—January 1953	23	1	Proper Electronic Wiring Techniques.
101—January 1951	21	1	Television Antenna Installation: (Part II—A TV Field Strength Meter).	119—February 1953	23	2	The Magnetic Amplifier.
102—February 1951	21	2	Color Television.	120—March 1953	23 5	5	Phase Shift Method of Checking Distortion.
103—March 1951	21	3	R. F. Transmission Lines.	121—April-May 1953 *	23	4/5	Junction Transistor Circuits.
104—May 1951	21	5	UHF Power Measurements.	122—June 1953	23	6	Simplified Subminiature Assemblies for Experimenters.
105—June-July-Aug. 1951 *	21	6/7/8	Metallized Paper Capacitors.	123—July-Aug. 1953 *	23 7/8	7/8	UHF Instrumentation: Part II—A UHF Grid-Dip Oscillator.
106—October 1951 **	issued as one supplement		Introduction to Radar Techniques (Parts I—V).	124—September 1953	23 9	9	Millimeter Waves.
November 1951				125—Oct.-Nov. 1953 *	23 10/11	10/11	Non-Linear Resistors.
December 1951				126—Dec. 1953-Jan. 1954 *	23/4 12/11	12/11	Electronic Oscillators: (Part I).
April 1952				127—February 1954	24	2	High Resistance Non-Electronic D. C. Voltmeters.
May 1952				128—March 1954	24	3	Safety Procedures in Electronic Equipment.
111—Jan.-Feb. 1952 *	22	1/2	High-Temperature Metallized Paper Capacitors.	129—April 1954	24	4	Television Reception in "Shadowed" Locations.
112—June 1952	22	6	Using Standard Time and Frequency Broadcasts.	130—May-June 1954 *	24	5/6	Balanced Modulators.
113—July 1952	22	7	UHF Instrumentation: (Part I—A UHF Absorption Frequency Meter).	131—July-Aug. 1954 *	24	7/8	Applications of the Electrometer.
114—August 1952	22	8	The Dielectric Amplifier.	132—Sept.-Oct. 1954 *	24	9/10	Electronic Oscillators: (Part II—Local Oscillators in A-M Receivers).
115—September 1952	22	9	Directional VHF Antennas: (Part III—A High-Gain, All Channel TV Antenna).	133—November 1954	24	11	Electronic Oscillators: (Part III—Tracking).
				134—December 1954	24	12	Elementary Binary Arithmetic.
				135—January 1955	25	1	Class-B Transistor Amplifier.

* Combined issues — 10c. ** Complete supplement — Cannot be ordered separately — 25c.

Please use the convenient order form appearing below. Simply circle the number of the issue that you want. Be sure to print name and address clearly and to enclose your remittance. Please do not ask us to send C. O. D. shipments. Remittance may be made by personal check, money order or currency. All orders will be shipped as soon as possible on a first come, first filled basis.

**AEROVOX RESEARCH WORKER
AEROVOX CORPORATION
NEW BEDFORD, MASSACHUSETTS**

Please send me the issues which I have circled below:

- 1 2 3 4 5 6 7 8 9 10 11 12 13 14 15 16 17 18 19 20 21 22 23 24 25
26 27 28 29 30 31 32 33 34 35 36 37 38 39 40 41 42 43 44 45 46 47 48
49 50 51 52 53 54 55 56 57 58 59 60 61 62 63 64 65 66 67 68 69 70 71
72 73 74 75 76 77 78 79 80 81 82 83 84 85 86 87 88 89 90 91 92 93 94
95 96 97 98 99 100 101 102 103 104 105 106 111 112 113 114 115 116 117
118 119 120 121 122 123 124 125 126 127 128 129 130 131 132 133 134 135

NAME (Please Print)

STREET ADDRESS

.....ZONE.....STATE.....

Enclosed find \$.....for.....issues.